

# ADC10080

*High Performance, Scalable ADC Solves Many Circuit Problems Without the Expense of Power*



Literature Number: SNAA102

## Technology Edge

### High Performance, Scalable ADC Solves Many Circuit Problems Without the Expense of Power

*By: Bob LeBoeuf, Application Engineer*

ADCs are finding themselves in an increasingly vast number of applications. This increases the demand for versatility, and of course, the demand for lower and lower power. Certain systems may require certain dynamic ranges on the input of the ADC, and it is usually preferred not to scale the input voltage. Amplifying the input signal offers challenging THD and bandwidth issues, and attenuating typically lowers the SNR, and may pose transmission line problems. In battery applications, lower power consumption becomes a dominating concern, and powering down the ADC becomes attractive. In the digital domain, an ASIC designer might prefer the option of a 2's complement data format instead of the traditional offset binary format. The ADC10080 offers solutions to many of these problems, without the expense of high power.

The ADC10080 is a 10-bit, 80 MSPS analog-to-digital converter that consumes only 78.6 mW (Typ) of power. It has a high degree of versatility, which is best summarized by the circuit shown in Figure1:

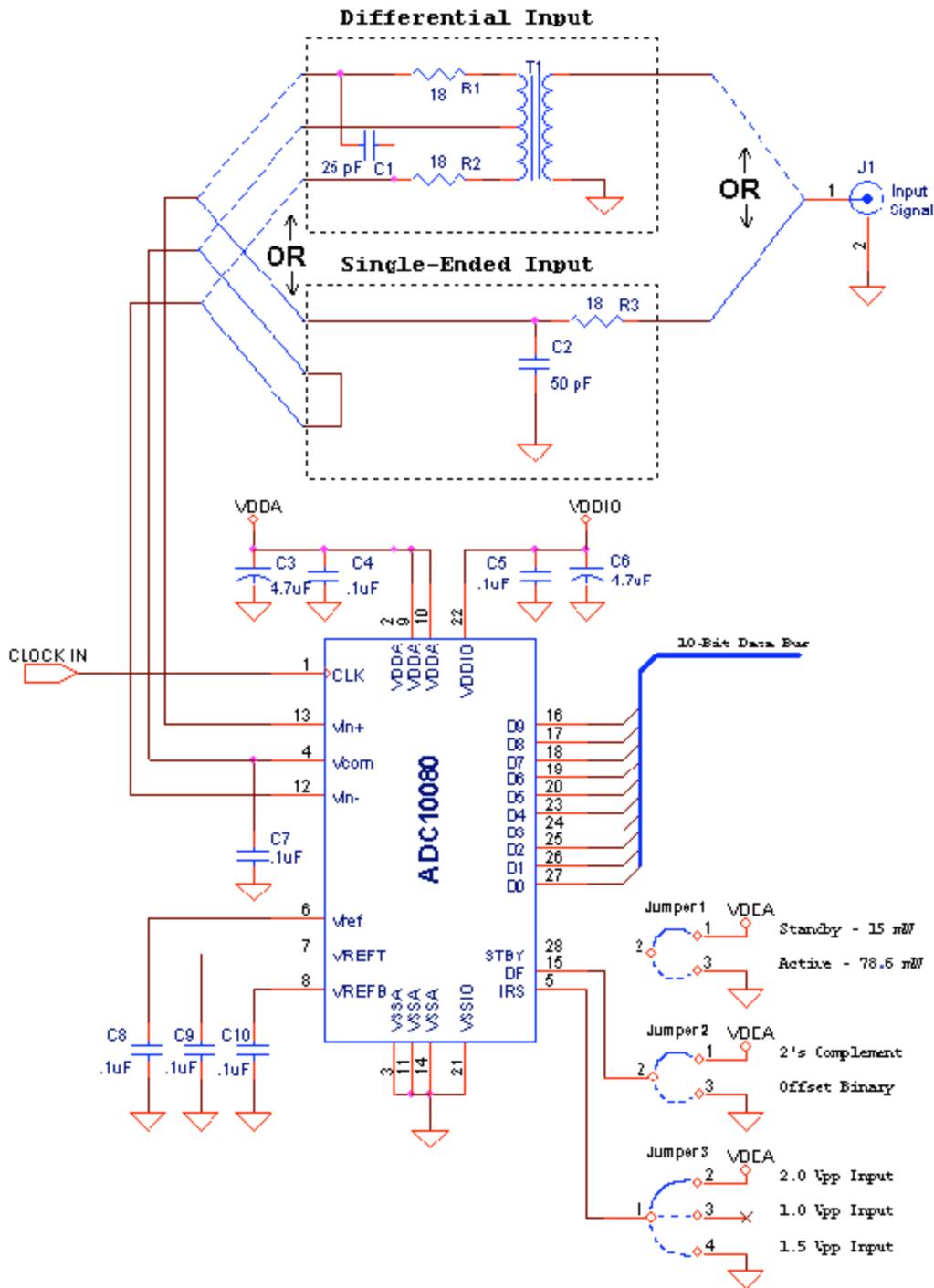


Figure 1

The input may be driven differentially, or single-ended, as shown in the top part of Figure 1. For a differential signal, a center-tapped transformer is sometimes employed because the center tap may be used to bias the input signal to the common mode voltage. This voltage is supplied by the chip at pin 4 (VCOM). R1, R2 and C1 form a low-pass filter that is used to limit the noise input. The -3 dB roll off occurs at  $1/(2 \cdot \pi \cdot (R1+R2) \cdot C1)$ . C1 also serves the purpose of dampening the charge 'kick-back' present in most ADCs.

For a single-ended input, the VIN- is tied to VCOM, and VIN+ is used for the input signal. A simple RC low pass filter (R3 &

C2) may be used to address the noise cut off, and charge kick-back.

In addition to the choice of differential or single-ended input, the peak-to-peak voltage is scalable using pin 5 (IRS - Input Range Select). By adjusting jumper 3, 2 V, 1.5 V or 1 V peak-to-peak is realized. The part may be powered down to 15 mW by applying VDDA to pin 28 (STBY - Standby).

The output format may be 2's complement, or offset binary by applying VDDA or VSSA to pin 15 (DF - Data Format) respectively. Each output data format has its advantages. The offset binary offers a simple direct scale that is proportional to the magnitude of the peak-to-peak input voltage. In some cases, it might be easier to divide the scale in half and assign the upper half to represent negative numbers. This would mean if the MSB is a '1', the number is negative, and the remaining 9 bits are understood to be the complement of the number. This is what the 2's complement format offers. A binary output of 000000000 through 011111111 is straight binary as usual, and maps to 0 through 511 in decimal. A 100000000 through 111111111 maps to -512 through -1 in decimal. An advantage to using the 2's complement scale is that subtracting two numbers can now be done by adding.

The ADC10080 also has a well-placed  $t_{od}$  specification to make it easy to capture the data. Figure 2 shows typical data lines and the clock:

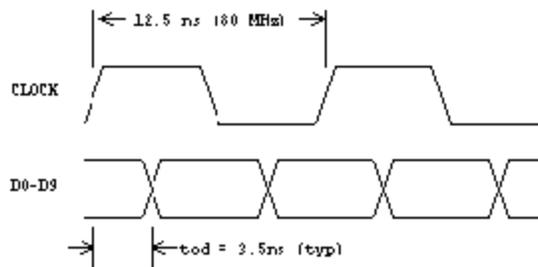


Figure 2

With all of these combinations available, the ADC10080 is suitable for many applications, including DTV, ultrasound, basestations, or general data acquisition. High performance specifications are preserved for even the most demanding systems, while consuming only 78.6 mW (Typ) of power.

For more information visit the [ADC10080](#) product folder.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Mobile Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Transportation and Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

TI E2E Community Home Page

[e2e.ti.com](http://e2e.ti.com)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2011, Texas Instruments Incorporated