

# Overcoming Challenges for Backlight LED Drivers in Automotive Display Solutions



Allie Zhang


High resolution and seamless operation are important for larger automotive display screens, shown in [Figure 1](#), as consumers want a clear picture with smooth functionality. Given the harsh environments in vehicles, system reliability and safety are also concerns. As a result, it's a challenge for designers to find a backlight LED solution that's designed for larger screens while also providing a high dimming ratio and ensuring system safety.



**Figure 1. Automotive display with an LCD screen**

To drive larger display screens, backlight LED drivers must have a high boost voltage and high current sink. Typically, automotive displays need to be greater than 1000 nits, which requires more LEDs or brighter, higher-current LEDs to achieve this level of brightness. Using more LEDs leads to higher boost voltage, while using stronger LEDs leads to more current. Using an external switching field effect transistor (FET), shown in [Figure 2](#), will provide higher power density to manage a larger-sized panel. Additionally, with an external FET, the power dissipation is spread further from the IC, enabling the thermal rise to be lower. A multichannel driver with a high current low-side current sink is also necessary to drive uniformity of display across the different channels.


TI's six-channel LP8866-Q1 automotive backlight driver maximizes power density and features an external switching FET. The device, designed for applications such as infotainment systems and head-up displays, offers a current sink as high as 200 mA. A high current sink is beneficial to ensure you will always have sufficient levels of brightness in your display – making it easy to read even on the sunniest days.

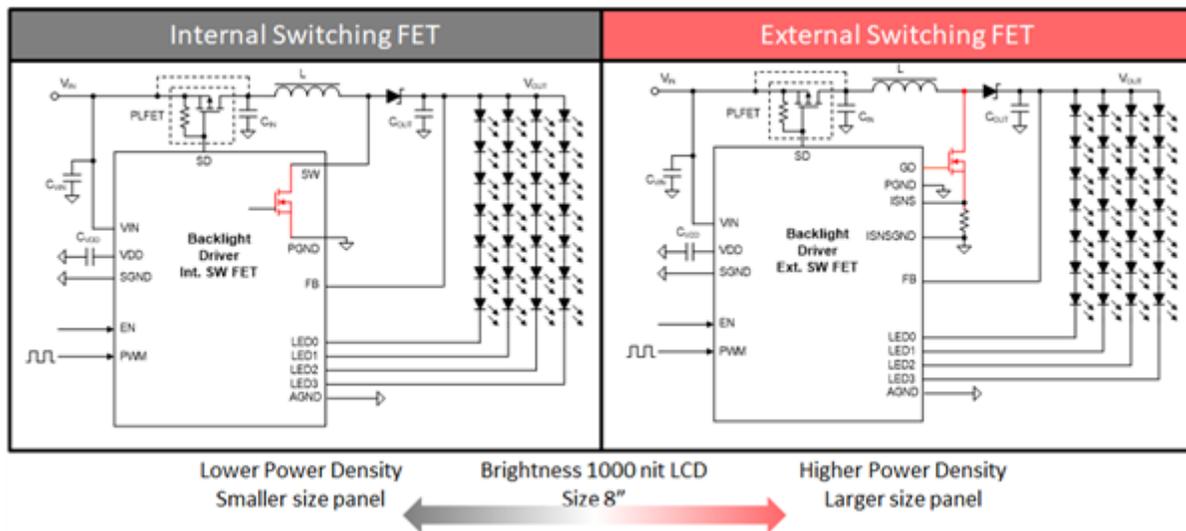

**Figure 2. Automotive backlight LED driver topology**

To achieve a smooth transition of brightness over a wide range, pulse width modulation (PWM) dimming is necessary and should have high resolution – especially in low-light situations. In bright conditions, analog dimming would be a better choice in order to avoid boost output ripple and audible noise issues.

TI uses an adaptive dimming control solution, known as hybrid dimming, illustrated in Figure 3. The LP8866-Q1 can begin dimming with 12-bit current digital-to-analog converter steps from 100% (0xFFFF) to 12.5% (0x2000) input brightness. Below 12.5% brightness, up to 16-bit PWM resolution can be achieved with the device (PWM duty control plus dither control). The benefits of hybrid dimming include reduced electromagnetic interference, lower boost output ripple and audible noise, improved LED optical efficiency, and an increased dimming resolution ratio for a given LED PWM frequency.

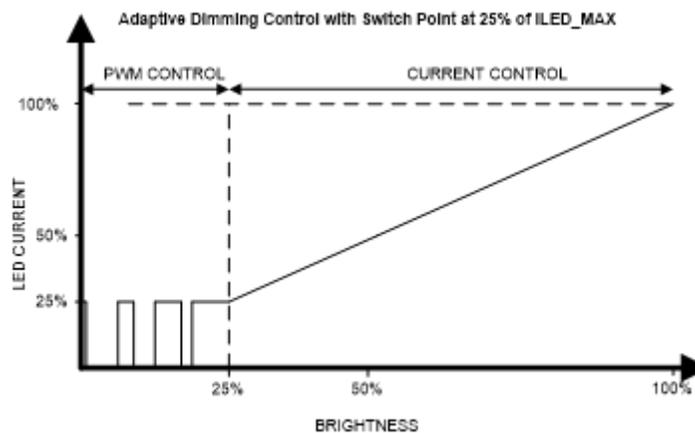

**Figure 3. Hybrid dimming mode**

**Additional resources**

- Check out these training videos about [analog dimming](#) and [PWM dimming](#) methods.
- Start your design today with the [LP8866-Q1 evaluation module](#).

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated