

3 Tips for Reducing Wireless Network Interference in Access Point Equipment

Mike(DC/DC) Wang

Oct 8, 2018

Equipping broadband modems, routers and gateways in home and enterprise networking with wireless access point (AP) functionality is experiencing explosive growth. [Figure 1](#) shows such a Wi-Fi® network. As the market keeps growing, the DC/DC converters used in this kind of equipment must fulfill several requirements.

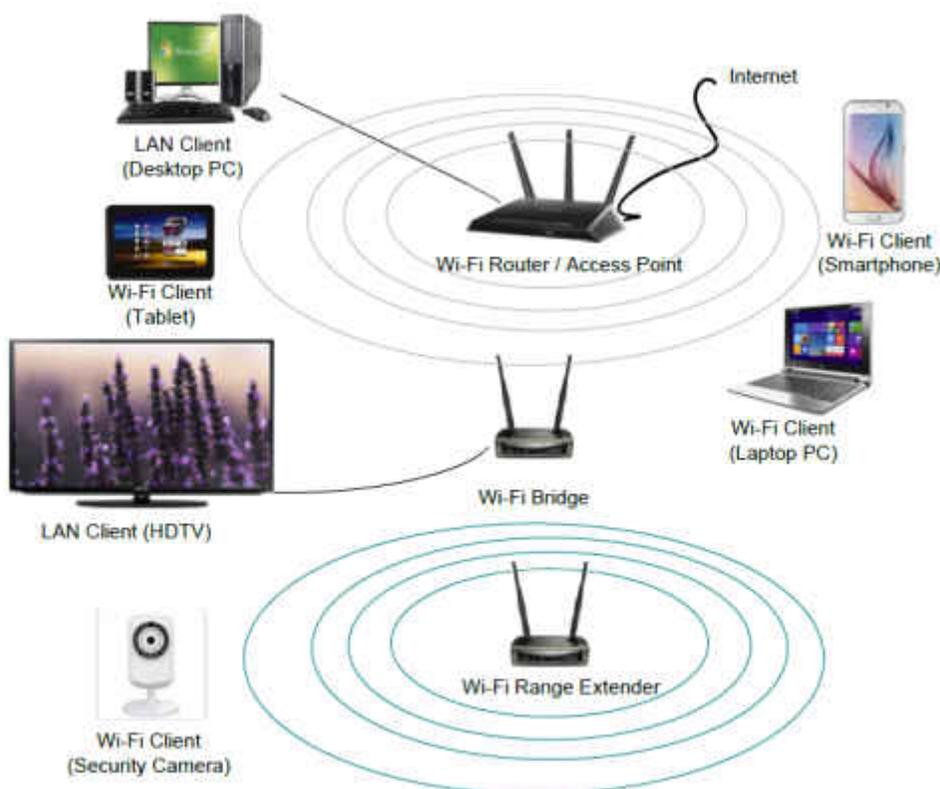


Figure 1. Typical Residential or Small Office Wi-Fi Network

Choose the Right Switching Frequency

The first requirement is at least a 1.2MHz switching frequency. [Figure 2](#) shows a diagram of a wireless AP. The switching noise of the DC/DC converter powering the Wi-Fi core chip will affect the error vector magnitude (EVM) of that Wi-Fi modem, thus degrading the communication quality. Fortunately, standard Wi-Fi chipset phase-locked loops (PLLs) have a frequency response that can serve as a low-pass filter with a cutoff frequency at ~1MHz.

Experiments show that it's possible to minimize this kind of EVM interference by using a high-frequency DC/DC converter. Most wireless AP chipset manufacturers, like Qualcomm and Broadcom, suggested a minimum switching frequency higher than 1.2MHz, with some margin reserved.

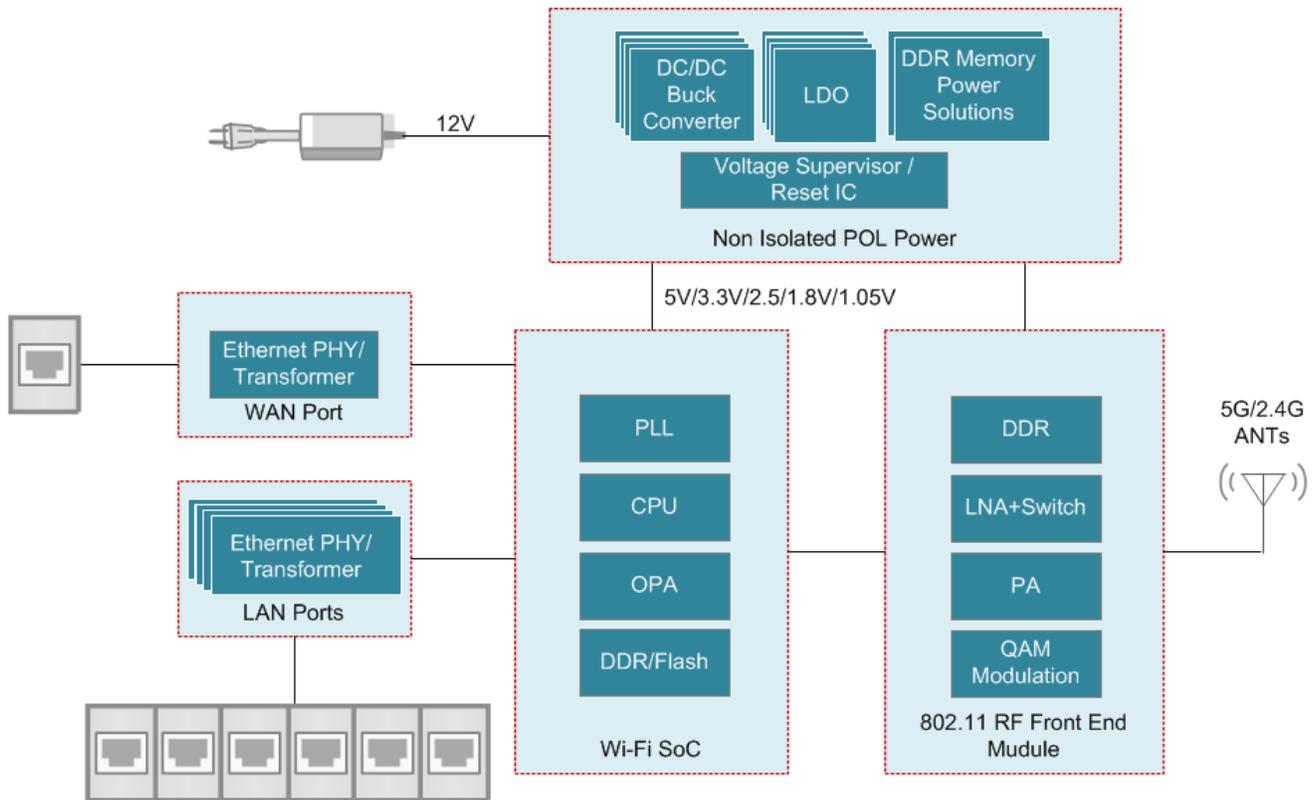


Figure 2. Diagram of a Wireless AP

To satisfy the minimum frequency requirement, you could use a converter based on current-mode control. This kind of converter usually has an internal clock to synchronize its operation. It's not very challenging to meet a design target such as 1.4MHz with a tolerance $\pm 200\text{kHz}$. The disadvantage is the converter's moderate load transient performance. Sometimes, to meet the fast load transient requirements of a Wi-Fi system, you have to use a larger output capacitance, which increases the total system cost.

Speed up Load Transient Response

The second requirement is the faster load transient response. The power consumption of the amplifier in a Wi-Fi block is quite different in the data transceiver and idle states, and the state change can be very fast. This imposes higher requirements on the load transient performance of your power-supply solution.

You could choose a converter with a constant on-time (COT) mode, which is famous for its faster loop response. Unfortunately, there is no internal clock in a COT converter; the converter simply generates a proper on-time for the high-side power field-effect transistor (FET) based on the input and output voltage to maintain a pseudo-constant switching frequency. The switching frequency of a COT converter changes greatly as the input and output voltage changes. It's very difficult to design a COT converter with a relatively tight frequency tolerance requirement.

Use a Frequency Lock

You need a high-frequency, cost-effective solution that has fast load transient performance like a COT converter, but can also maintain a relatively constant switching frequency like a current-mode converter.

Figure 3 illustrates a proposed solution that adopts the D-CAP3™ control mode and implements a proprietary frequency-lock function to achieve a constant frequency like a current-mode device.

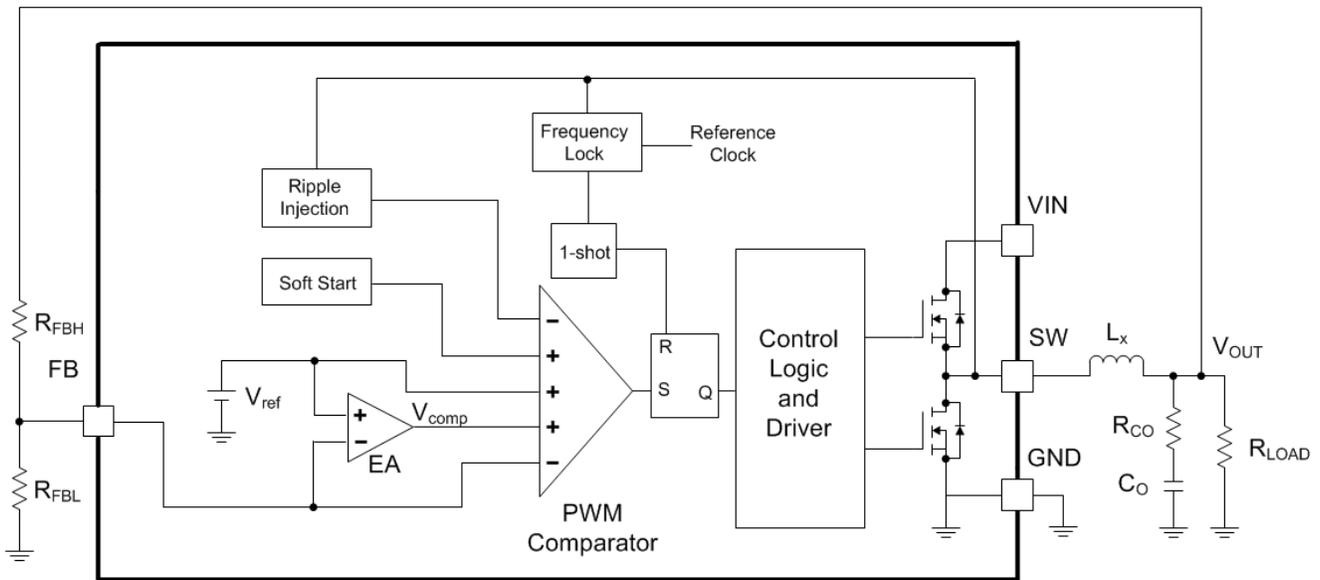


Figure 3. Block Diagram of a D-CAP3 Control-mode-based Converter

Compared with the traditional COT control mode, you can realize several benefits with this solution:

- The converter switching frequency is compared to a reference clock frequency. Based on the result, the on-time generated by a one-shot block adjusts to maintain a switching frequency within a relatively narrow variation range.
- An error amplifier removes DC voltage errors caused by the ripple amplitude of the output voltage. This DC error normally exists in a traditional COT control-mode converter.
- Instead of using the ripple of the output voltage as in a COT converter, a D-CAP3 control-mode-based converter will generate an internal ripple signal to emulate the inductor current ripple, eliminating the need for an equivalent series resistor on the output capacitor and achieving stable regulation even without output voltage ripple.

The frequency lock function makes it possible to achieve a relatively constant switching frequency. If the internal reference clock is set to 1.4MHz, you can easily guarantee a switching frequency higher than 1.2MHz in mass production, satisfying the first requirement. As to the second requirement, you can also meet a fast load transient response easily, since that is an inherent benefit of DCAP-3 control mode.

Turning Theory to Practice

Let's take TI's [TPS563249](#) 17V, 3A buck converter as an example to obtain the measurement result.

[Figure 4](#) shows the faster load transient response of the [TPS563249](#) compared to a current-mode converter. To make a direct comparison, the switching frequency of the current-mode converter is set at 1.4MHz, as is the [TPS563249](#), and the crossover frequency is set at about one-tenth the switching frequency. Both converters are using the same 1.5µH/22µF output inductor-capacitor filter.

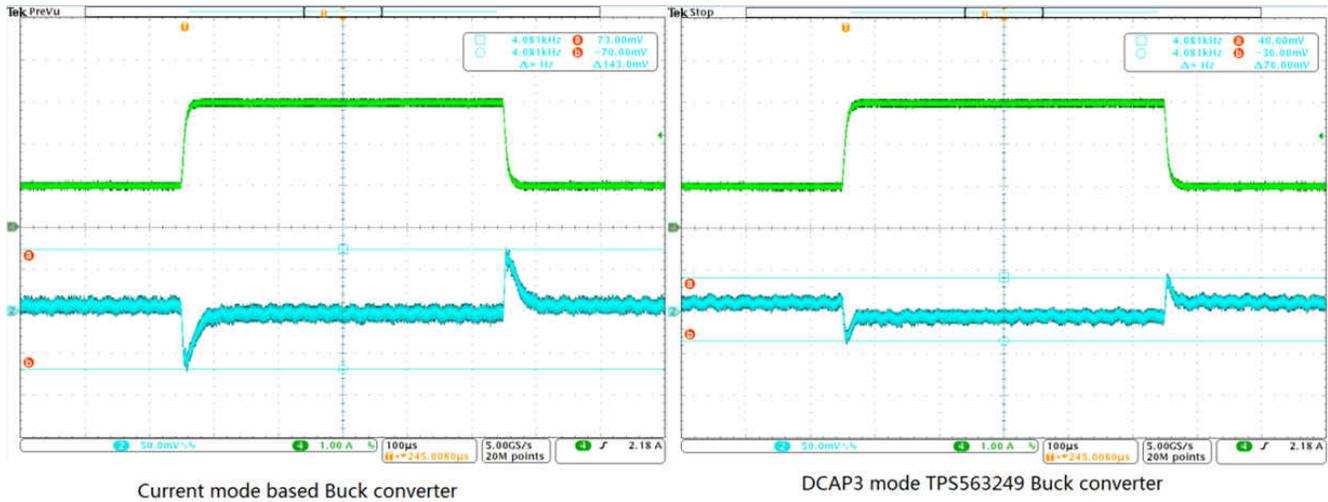


Figure 4. The Faster Load Transient Response of the TPS563249 Compared to a Current-mode-based Converter

The load step is from 1A to 3A with a 2.5A/µS slew rate; the target output voltage is 3.3V. The peak-to-peak output voltage ripple with the current-mode converter is 4.3% of the nominal output voltage, while it's only 2.3% with the TPS563249.

Figure 5 and Figure 6 show the constant switching frequency of the TPS563249 compared to a general COT converter without the frequency lock feature.

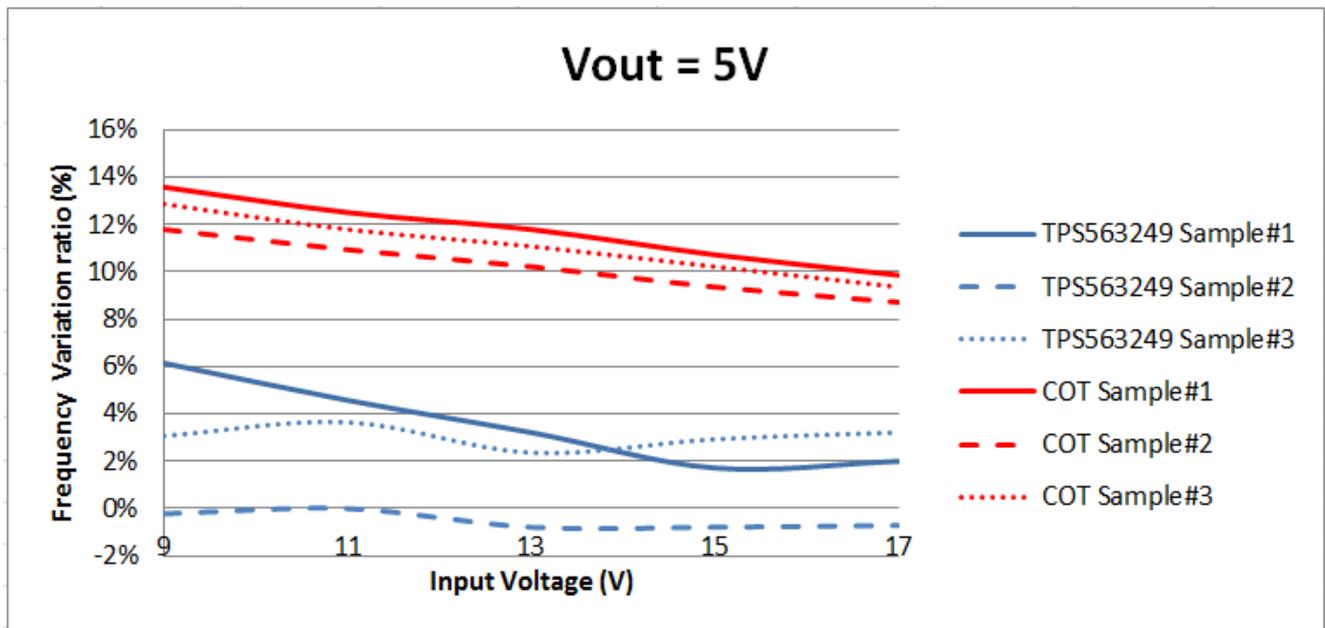


Figure 5. Frequency Variation versus a Different v_{IN} ($V_{OUT} = 5V$)

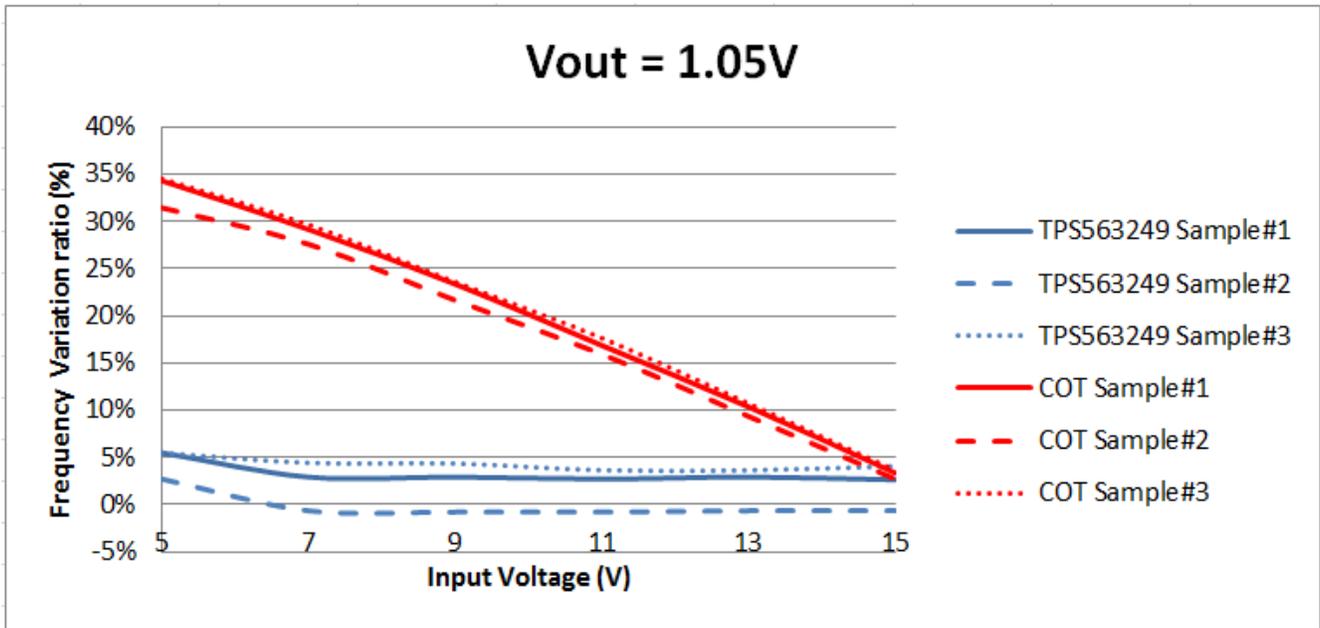


Figure 6. Frequency Variation versus a Different v_{IN} ($V_{OUT} = 1.05V$)

The [TPS563249](#) has a smaller variation range compared to a general COT converter. As you can see, the [TPS563249](#) also maintains a tight frequency range: there is around 5% of variation from the nominal frequency regardless of how the input and output voltage changes. However, for the general COT converter, the frequency varies ~35% from the nominal frequency in the worst case.

In general, the [TPS563249](#) works at a constant 1.4MHz switching frequency and removes the noise interference in a Wi-Fi system for all conditions. It also satisfies the fast load change requirement from a Wi-Fi amplifier by implementing D-CAP3 control mode.

The 1.4MHz high switching frequency is helpful to minimize total system size, as well as bill-of-materials cost. It's quite suitable for frequency-sensitive applications, such as broadband modems, routers and gateways with wireless AP.

Additional Resources

- Download the [TPS563249 data sheet](#).
- Watch our training video: [Power Tips: DCAP vs. Voltage Mode](#).
- Read these blogs:
 - [Design advantage of D-CAP control topology](#)
 - [Power Tips: How to reduce D-CAP control output capacitance](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated