## Technical Article How to Use PMBus Power Solutions for NXP QorlQ Processors



George Lakkas

NXP QorIQ processors are high-performance 64-bit Arm® multicore processors for cloud networking and storage applications. Two of the high-end QorIQ variants are the LS2085A and LS2088A.

There are several power-supply rails required on an LS2085A/2088A board: the most important are the core rail and the SerDes logic and receiver rail. Using the PMBus interface eases the programming and monitoring of these high-current rails.

TI offers the PMBus Voltage Regulator Reference Design for NXP QorlQ LS2085A/88A Processors, which fully meets LS2085A/88A tolerance specifications while requiring only 50% of the output capacitance necessary on NXP evaluation boards. The reference design consists of the TPS53681 dual-output PMBus controller and TI's CSD95490Q5MC smart power stages, as shown in Figure 1.



Figure 1. NXP LS2085A88A QorlQ Power Design

TI fully tested this reference design, and the board includes onboard load-transient generator circuits to test load transients and thus measure the AC output-voltage tolerance. The reference design board has all of the connections for complete power-supply testing, as well as programming of the TPS53681 and monitoring of the two voltage rails through the PMBus interface using TI's Fusion Digital Power™ Designer (Figure 2).

1





Figure 2. NXP LS2085A88A QorlQ Power Design Evaluation Board

Among the many tests are the important load-step and load-release transient tests, as shown in Figure 3 and Figure 4. In both cases, the reference design meets the NXP tolerance specifications.



Figure 3. NXP LS2085A88A QorlQ Load-step Test





Figure 4. NXP LS2085A88A QorlQ Load-release Test

The design even includes a Nyquist plot on top of the Bode plot to prove design stability, as shown in Figure 5. The Nyquist plot is stable if no encirclements (circle wrapping around) of the point (-1, 0) occur as the test frequency is swept during testing.



Figure 5. NXP LS2085A88A QorlQ GDD Rail Nyquist Plot

Finally, the design also offers thermal performance data of both VDD and GVDD power supplies, as shown in Figure 6.

3





## Figure 6. VDD Rail Power-stage Temperatures, 60A Load (Left); GVDD Power-stage Temperatures, 30A Load (Right)

NXP processors are now part of TI's power for processors portal, which will be updated with TI power solutions and designs for additional NXP networking processors. So if you are designing with NXP QorIQ processors and don't know where to start, download the reference design now.

## Additional Resources

- Read the blog post, Power Tips: How to use Nyquist plots to assess system stability.
- Download the LS2085A/88A QorlQ TI Design Guide.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2023, Texas Instruments Incorporated