

Do-it-yourself: Three Ways to Stabilize Op Amp Capacitive Loads



Collin Wells

Capacitive loads can cause stability problems in [operational amplifier \(op amp\)](#) circuits, resulting in large overshoots, ringing, long settling times – and in severe cases, sustained oscillations. These issues occur because the capacitive load interacts with the op amp output impedance, forming an additional pole in the open-loop gain (Aol) response that reduces the loop-gain (Aol*β) phase margin below acceptable levels.

Many resources present basic stability theory in great detail, including [TI Precision Labs' videos on op amp stability](#). There are different compensation circuits which allow the op amp to remain stable while driving the capacitive load. In this blog post, I'll review three common compensation circuits that can be designed and tested using the do-it-yourself amplifier evaluation module ([DIYAMP-EVM](#)).

Isolation Resistor – R_{ISO}

The most common and easiest-to-design method places an isolation resistor (R_{ISO}) in series with the capacitive load. The isolation resistor adds a zero to the Aol*β transfer function, which cancels the phase shift from the pole and returns the rate of closure (ROC) to 20dB/decade. As shown in [Figure 1](#), this compensation circuit produces stable results with phase margins greater than 60 degrees by following the design steps in the TI Precision Labs videos and placing the zero at or above the frequency where the loaded Aol curve is equal to 20dB. Moving the zero higher in frequency lowers the phase margin to achieve a more critically damped response. The main disadvantage to this compensation method is that there will be a voltage drop across R_{ISO}, which reduces the DC accuracy of the circuit when driving a load.

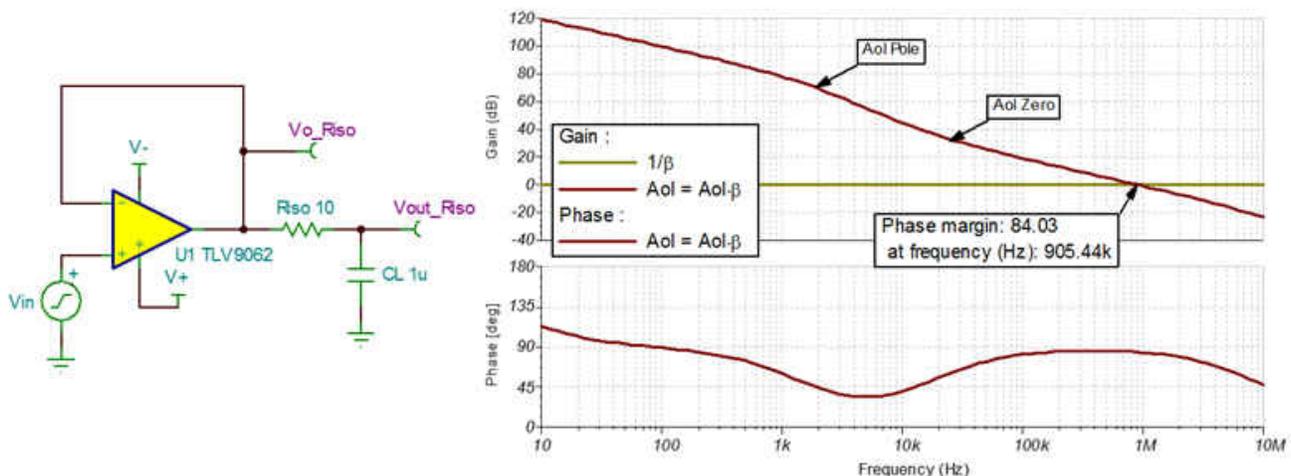


Figure 1. R_{ISO} capacitive load compensation circuit and open-loop results

R_{ISO} + DFB Circuit

A common solution to maintain DC accuracy while stabilizing the load is to use the R_{ISO} plus dual-feedback (R_{ISO} + DFB) circuit. As the name suggests, this compensation circuit has two feedback paths. There is a DC feedback path through RF that regulates the voltage at the load and an AC feedback path through CF, which

makes the circuit act like the R_{ISO} circuit at high frequencies to stabilize the capacitive load. Be sure to follow the guidelines in the TI Precision Labs videos for setting the feedback components to achieve proper operation.

Figure 2 shows the open-loop results for the R_{ISO} + DFB circuit. While this circuit restores the DC accuracy lost while using the R_{ISO} circuit, the R_{ISO} + DFB circuit has slower settling times than the original R_{ISO} circuit.

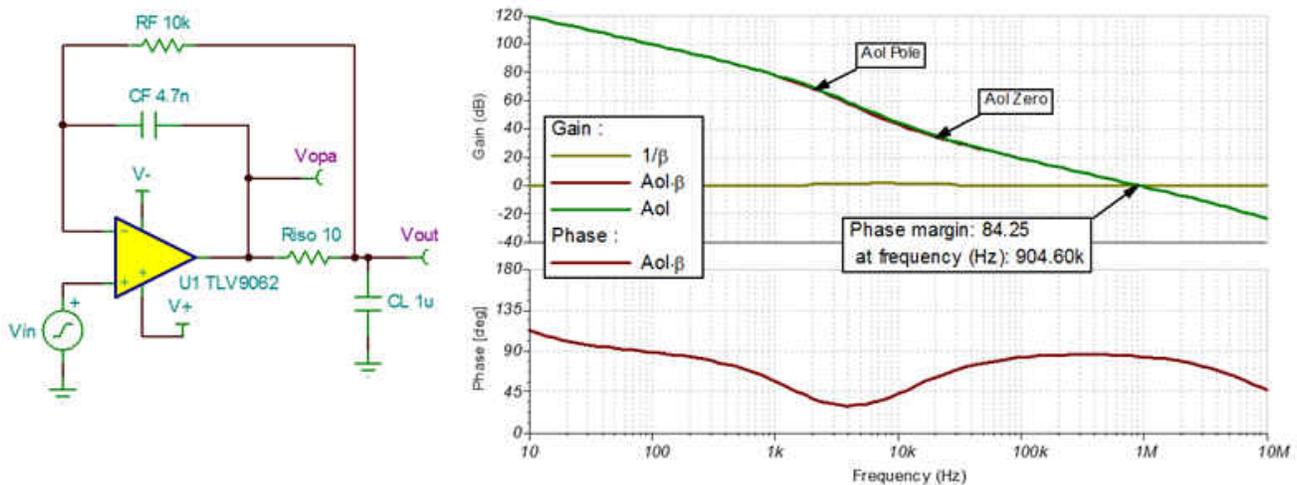


Figure 2. R_{ISO} + DFB compensation circuit and open-loop results

R_{ISO} + DFB + RFX Circuit

Another compensation method that maintains DC accuracy but offers improved transient response is the R_{ISO} + DFB + RFX circuit. This circuit is basically the same as the R_{ISO} + DFB circuit with an additional resistor, RFX, in series with CF. The addition of RFX will cause the circuit noise gain ($1/\beta$) to increase and flatten off at higher frequencies to a magnitude of $1 + RFX/RF$. This increase in noise gain can be helpful to compensate difficult capacitive loads, lower the loop-gain crossover frequency, adjust the phase margin and shape the closed-loop output impedance. For this circuit to be stable, the $1/\beta$ response must flatten off to the high-frequency level before it intersects with the Aol curve to achieve a 20dB/decade ROC. Figure 3 shows the R_{ISO} + DFB + RFX circuit and the open-loop results.

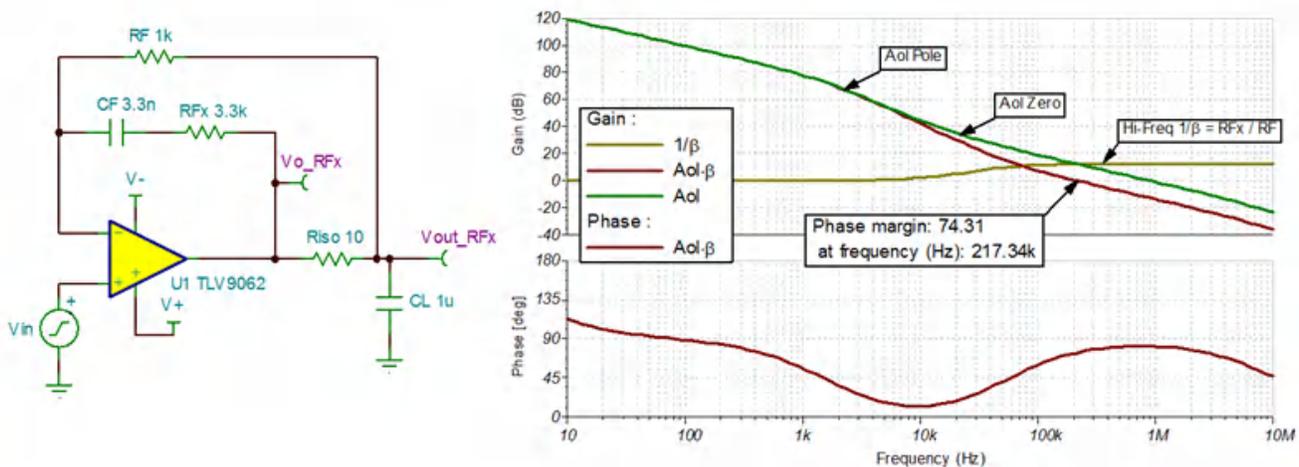


Figure 3. R_{ISO} + DFB + RFX Compensation Circuit and Open-loop Results

Figure 4 compares the transient results to a small-signal step input at both the op amp output (V_o) and the circuit output (V_{OUT}). The R_{ISO} circuit displays a typical overdamped response with a moderate settling time. The R_{ISO} + DFB circuit output has a rounded single-lobe overshoot and long settling tail resulting in slower settling times than the R_{ISO} circuit. The R_{ISO} + DFB + RFX output has a sharp single-lobe overshoot but settles very quickly to the final output value with a similar settling time to the original R_{ISO} circuit.

While the overshoot spike at the op amp output in the $R_{ISO} + DFB + RFX$ circuit (V_{o_RFX}) looks troubling, the behavior is a result of the complex nature of this circuit's transfer function and how the placement of the poles and zeros affects the transient response. Don't worry; the circuit is stable. The overshoot is aperiodic and not followed by the substantial ringing that would normally be associated with this level of overshoot if the circuit was unstable.

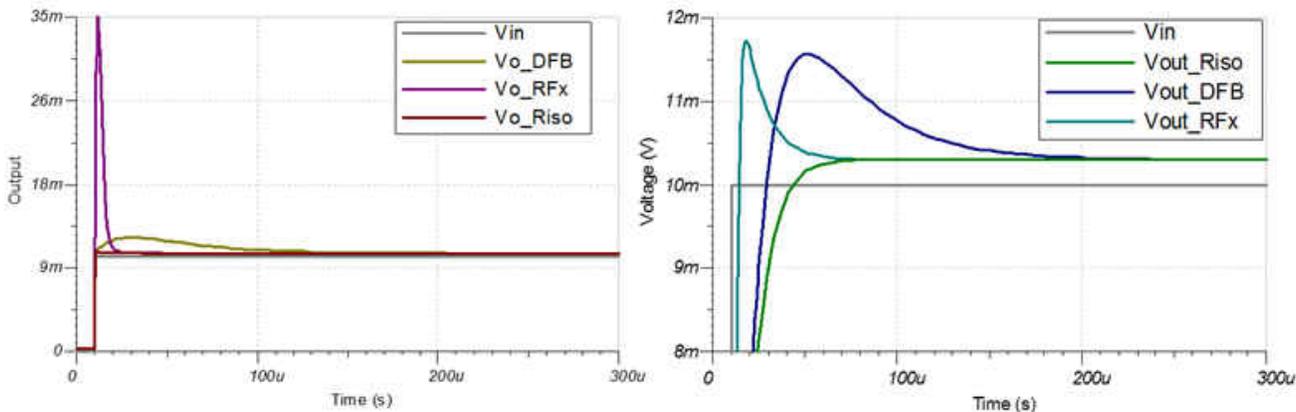


Figure 4. Comparison of Small-signal Step Responses for the Three Compensation Circuits

Figure 5 compares the total output noise of the three circuits. The R_{ISO} circuit has the lowest noise, followed by the $R_{ISO} + DFB$ circuit and then the $R_{ISO} + DFB + RFX$ circuit. The $R_{ISO} + DFB + RFX$ circuit has the highest noise because of the increase in noise gain at higher frequencies. Circuits with higher ratios of RFX/RF will have more noise than those with smaller ratios.

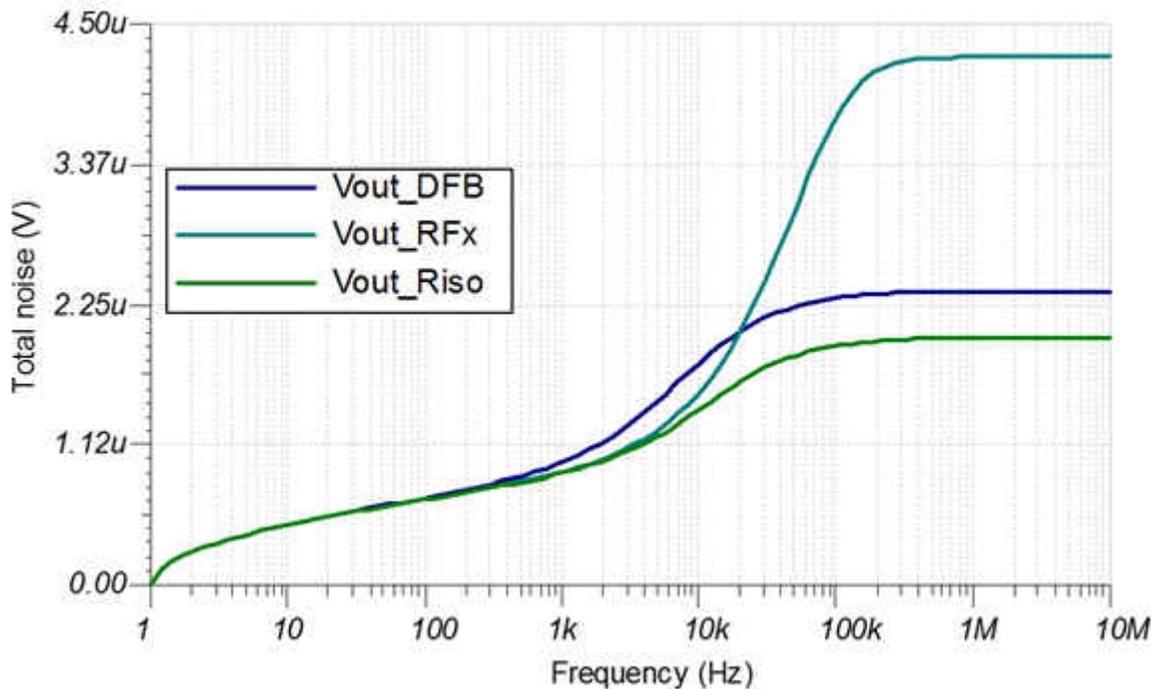


Figure 5. Total output-noise comparison for the three compensation circuits

You can evaluate all three of these circuits using the $R_{ISO} + DFB$ circuit in the DIYAMP-EVM shown in Figure 6. Table 1 lists the component configurations to create each of the three circuits using the DIYAMP-EVM $R_{ISO} + DFB$ circuit.

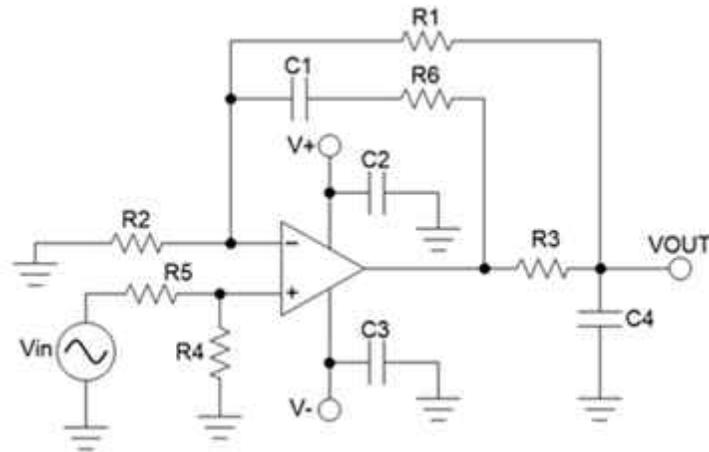


Figure 6. R_{ISO} + DFB Circuit in the DIYAMP-EVM

Table 1. R_{ISO} + DFB DIYAMP-EVM Circuit Component Configurations

	R1	R3	R6	C1	C4
Riso	Open	Riso	Short	Short	CL
Riso+DFB	RF	Riso	Short	CF	CL
Riso+DFB+RFx	RF	Riso	RFx	CF	CL

I hope that after reading this post, you'll feel confident doing your own stability analysis and compensation using the [DIYAMP-EVM](#).

Additional Resources

- Check out the [DIYAMP-SOIC-EVM User's Guide](#).
- Check out the [Dual-Channel DIY-AMP EVM](#).
- Download the [Analog Engineer's Pocket Reference Guide](#)
- Learn more about the [TLV9062 op amp](#).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated