

# Display Power: Why TFT LCD Needs Temperature Compensation



Ilona

If you ever had the pleasure to design the bias supply for a Thin Film Transistor Liquid Crystal Display (TFTLCD) module and you used the appropriate part from TI then you may have run into the temperature compensation function. This blog will handle the background on why a Liquid Crystal Display (LCD) needs temperature compensation and how it is implemented in TI's LCD Bias IC's.

Before I evaluate the temperature effect let's touch quickly on how the LCD actually shows a picture.

A LCD is built up like a sandwich. The actual liquid crystal is covered with two plates of glass, the upper side coated with the color filter and polarizer, the lower plate deposited with TFTs to address the pixels and a polarizer as well. The actual light is coming from the backlight at the bottom. Since the 70's we know that the liquid crystal twists if an electric field is applied. Dependent on the voltage level the crystal aligns such that it either blocks or passes the backlight.


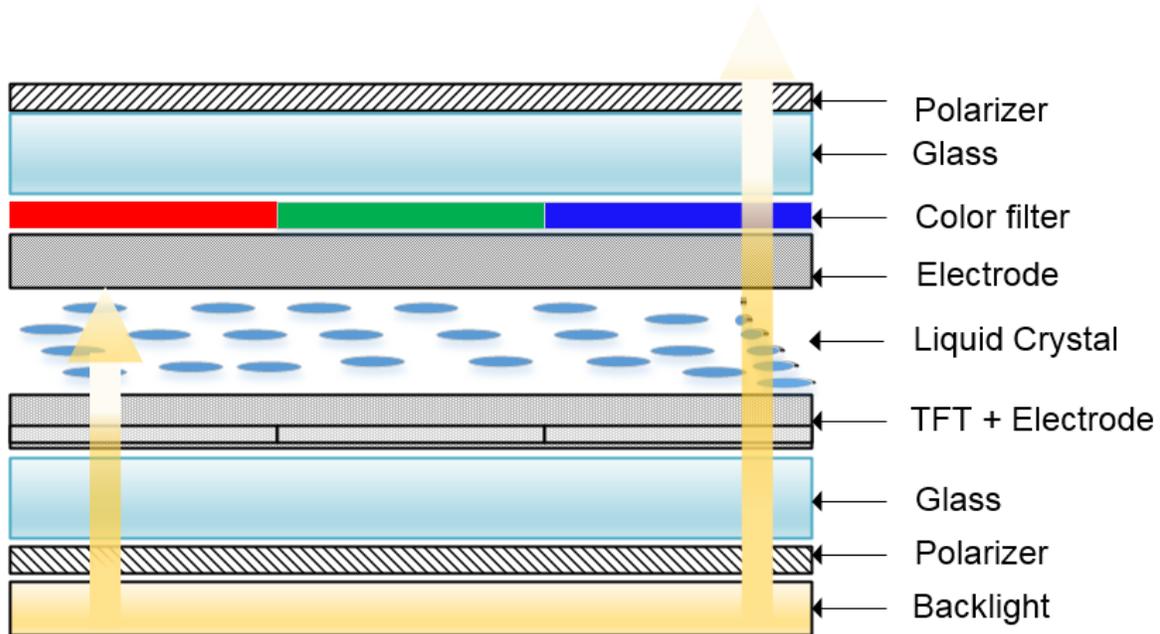


Figure 1. LCD Profile

Each pixel consists of three sub-pixels with different color filter (Red, Green and Blue). Each of the sub-pixels is controlled by a TFT, see the structure and equivalent circuit in [Figure 2](#).

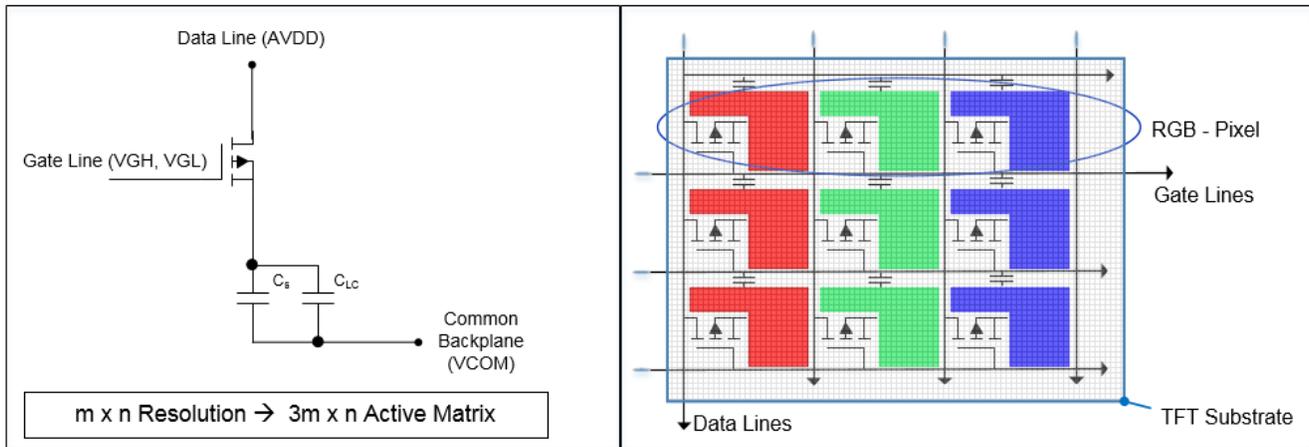

**Figure 2. Unit Pixel Structure + Equivalent Circuit**

The actual picture information (data line) decides the level of voltage across the crystal (equivalent to the storage capacitor  $C_s$  and the liquid-crystal capacitor  $C_{lc}$ ).

The time frame to activate the pixel is set by the voltage at the gate of the TFT (gate line).

Now, a positive voltage (also commonly called  $V_{GH}$  or  $V_{ON}$ ) is applied to the gate and the TFT (here N-channel) turns on.  $C_{lc}$  and  $C_s$  charge up to the voltage applied to the data line. The maximum voltage on the data line is called  $AVDD$  or  $V_S$ . This is transferred to the pixel electrode and becomes visible. Vice versa, a negative voltage (also called  $V_{GL}$  or  $V_{OFF}$ ) turns off the transistor, the intrinsic capacitors of the LC discharge and the data voltage will not be transferred.


On a FHD / 60 Hz display for example each cycle (turn-on, turn-off) needs to happen within approx.  $10 \mu s$ .  $*FHD = 60 \text{ Hz} / (1920 \times 1080 \text{ pixel} \times 3 \text{ (RGB)}) = 9.6 \mu s$

Temperature has two big impacts on the performance of the LCD.

The first is that the actual LC fluid changes its viscosity over temperature. At cold temperatures, the viscosity of the LC fluid decreases and this increases the response time of the crystal to the applied voltages. This effect comes with the LCD technology and can only be tailored accordingly by the panel supplier.

The second effect is that the operating conditions of the TFTs are changing. Studies have shown that the threshold voltage of an amorphous silicon (a-Si) TFT increases as the temperature decreases. [Figure 4](#) shows how this can affect the on-time transition ( $V_{GH}$ ). In a warm environment ( $25^\circ\text{C}$  to  $80^\circ$ ) the thresholds are quite low, the transistor switches fast enough to make sure that the picture information (Data Line) is put through to the pixel and transfers the correct light intensity.

However, cold temperatures cause the switch to turn on slower. This steals time ( $t_{\Delta th}$ ) to put through the picture information, see figure below. Less light comes through the filter glass and the contrast gets lower. Visible results are flickering and/or image sticking of the display.

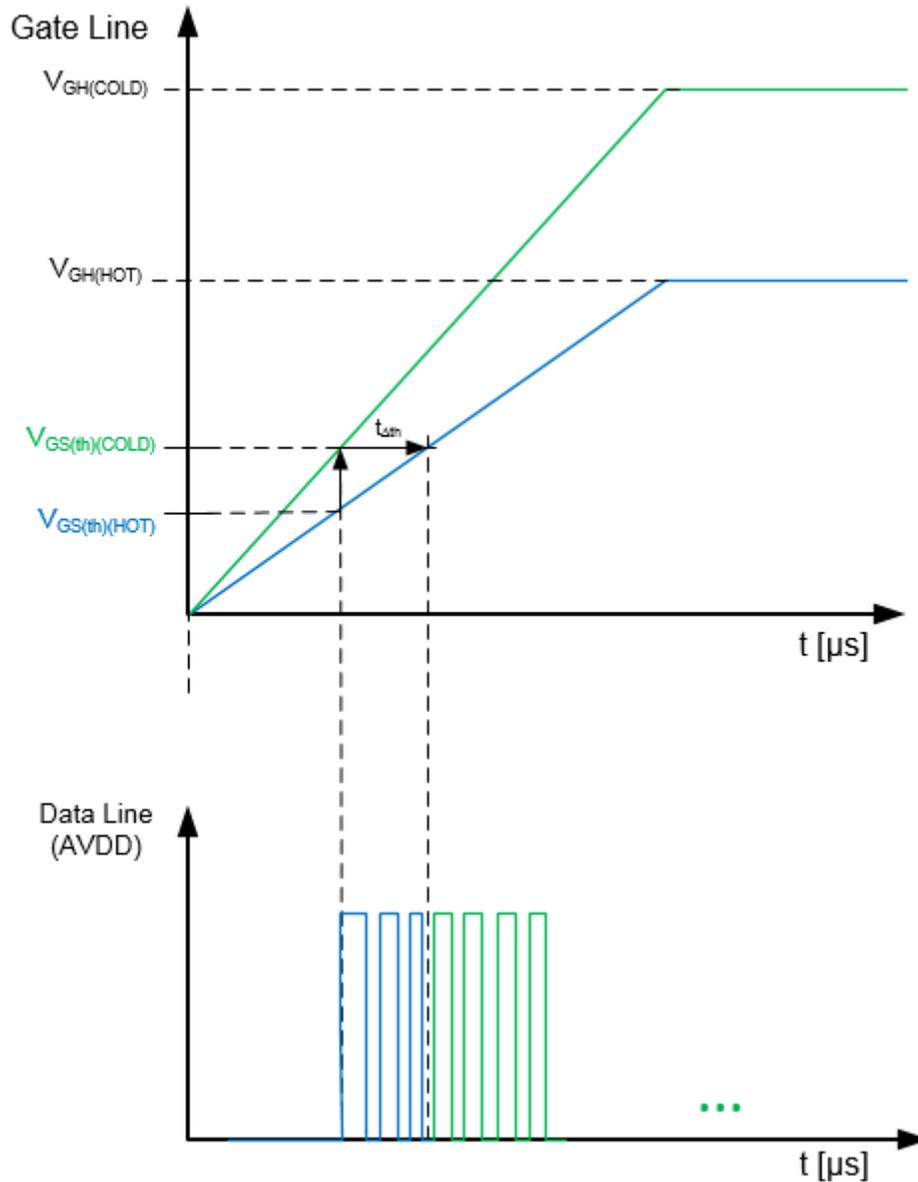


**Figure 3. Temperature Behavior TFT**

In order to maintain the correct throughput of the picture information at a lower temperature, the turn-on voltage  $V_{GH}$  needs to be increased. This is where the temperature compensation kicks in. From the experience with panel suppliers, it is an empirical approach to set the hot and cold voltage requirements.

How is the temperature compensation implemented?


If you need to build up your own compensation network, the simplest solution to adjust a temperature dependent voltage is the circuit as below:

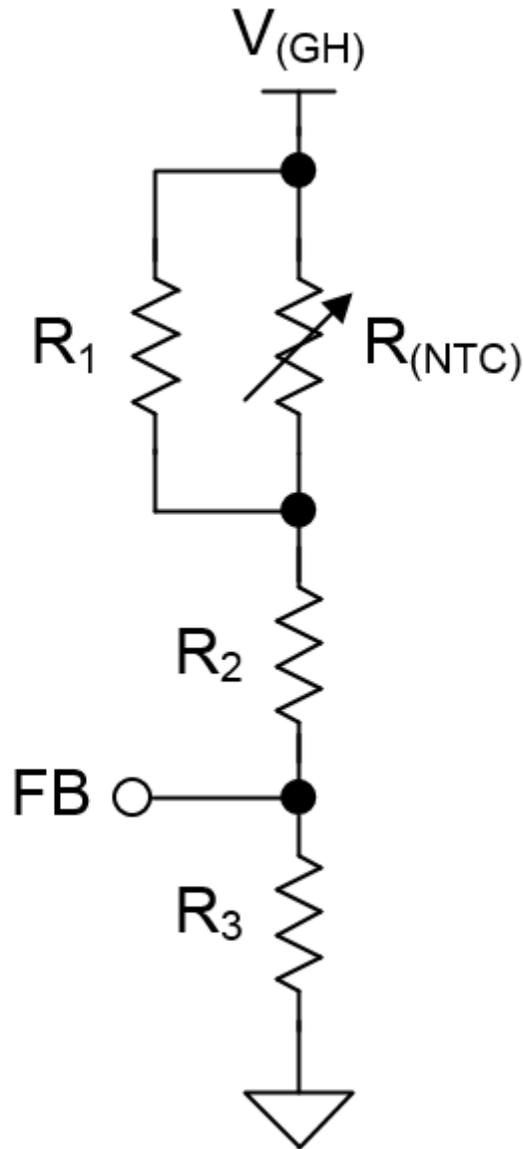

**Figure 4. Simple Compensation Network**

The most common way to measure the ambient temperature is to use a negative temperature coefficient thermistor and place it on the LCD control PCB where it represents the ambient temperature the best. As described the LCD module should specify the normal operating turn-on voltage  $V_{GH}$  and the temperature coefficient requirements. With this, you can apply the thermistor in parallel to the upper resistor of the feedback network of the voltage regulator. This solution has the disadvantage that the voltage cannot be monitored and cannot be covered by a maximum and a minimum value. Many of today's LCD bias solutions are programmable with an I2C compatible interface and feature the temperature compensation with an NTC thermistor network.

Let's take the TPS65642 for example. [Figure 5](#) shows the block diagram of how the gate-charge voltage rail  $V_{GH}$  can be compensated in this part.

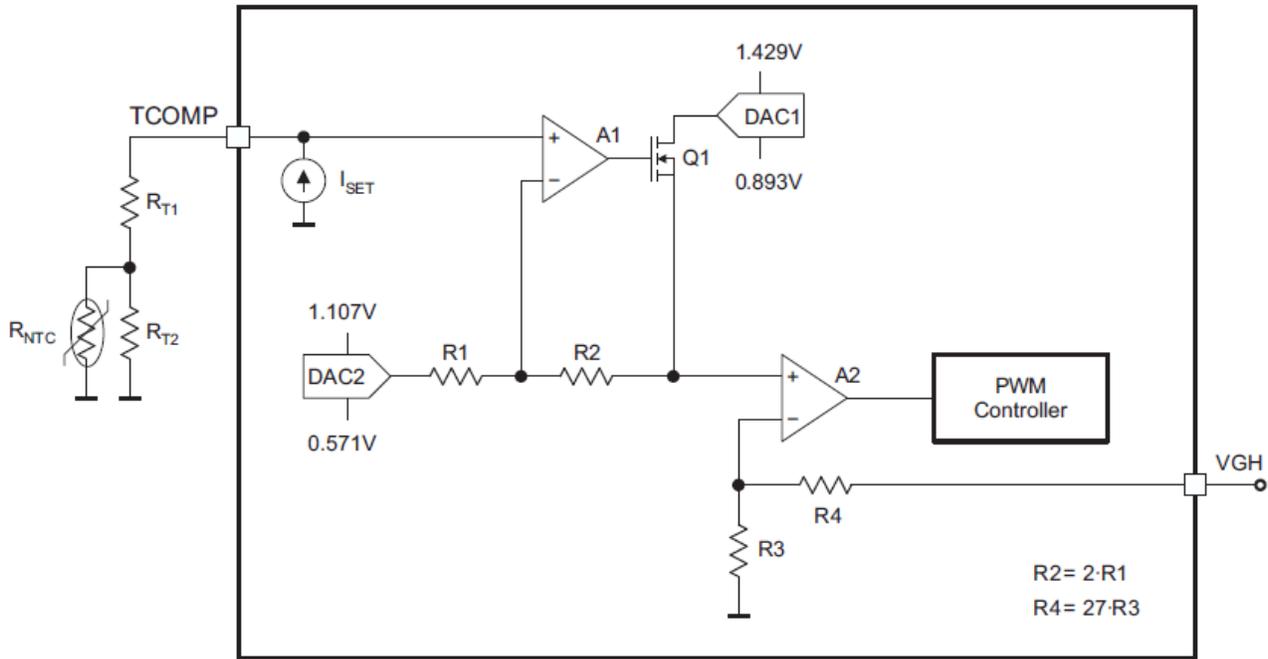

**Figure 5. Temperature Compensation Network TPS65642**

The external resistive voltage divider  $R_{T1}$ ,  $R_{T2}$  and  $R_{NTC}$  sinked by a fixed current source  $I_{SET}$  set the initial voltage and the adjustment range from  $T_{COLD}$  to  $T_{HOT}$ . Use this calculation [sheet](#) to get the maths.

Once the temperature corners are set on hardware the device needs to be programmed with the voltage corners  $V_{GH(HOT)}$  and  $V_{GH(COLD)}$ . The value for  $V_{GH(COLD)}$ , usually the upper value is set in DAC1 (25 V to 40 V scaled down to 0.893 V to 1.429 V) and the value for  $V_{GH(HOT)}$ , usually the lower value is set in DAC2 (16 V to 30 V scaled down to 0.571 V to 1.107 V).

The resistance of the NTC network increases with decreasing temperature. This means that the voltage on TCOMP increases with decreasing temperature. If the voltage exceeds the lower corner, Q1 turns on and sets the signal for the PWM controller to increase VG<sub>H</sub>. The resistive dividers  $R2/R1$  set the transition slope and  $R3/R4$  is the feedback divider for VG<sub>H</sub>.

It is also possible to set a positive temperature slope. For this, you either use a PTC thermistor instead or place the NTC thermistor parallel to the upper resistor  $R_{T1}$ .

If you have experienced your panel having different requirements regarding temperature behavior just leave your comment below, we are interested to know.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated