

# Create a 24W Power Supply for Automotive LED Lighting Systems



Martin Moss

LEDs were initially limited to a few niche applications. They didn't enter the mainstream general lighting market until recently, given the confluence of a variety of technologies, better manufacturing techniques and cost optimization. The global market is still in the developing phase, with the automotive and smartphone markets providing a strong boost to LED market growth. Yet challenges remain related to the investment costs of replacing conventional lighting, which hinders the pace of the market. See [Figure 1](#).



**Figure 1. Typical LED Applications**

Automotive designers are moving away from standard bulbs in favor of LED arrays, which offer the ability to style the lighting differently and cater to advanced features like beamforming and even mood lighting.

Implementing LEDs in an automotive system is not a simple matter, however. LEDs by their very nature have unique needs, and automotive systems behave erratically under conditions like cold cranking and load dumps. They are also susceptible to noise – either generated by the lighting or the lighting affecting external noise. As I said earlier, there's often pressure to optimize cost as well as thermals, as any power losses will translate to heat generation and ultimately reliability issues in extended usage.

TI has developed several reference designs to overcome these issues. For example, the [TI Designs 24W Boost and Boost-to-Battery Reference Design for Automotive LED \(TIDA-01234\)](#) in [Figure 2](#) is a 24W, high-efficiency (94%), low-cost, asynchronous boost design for automotive LED applications based on the LM3481-Q1.

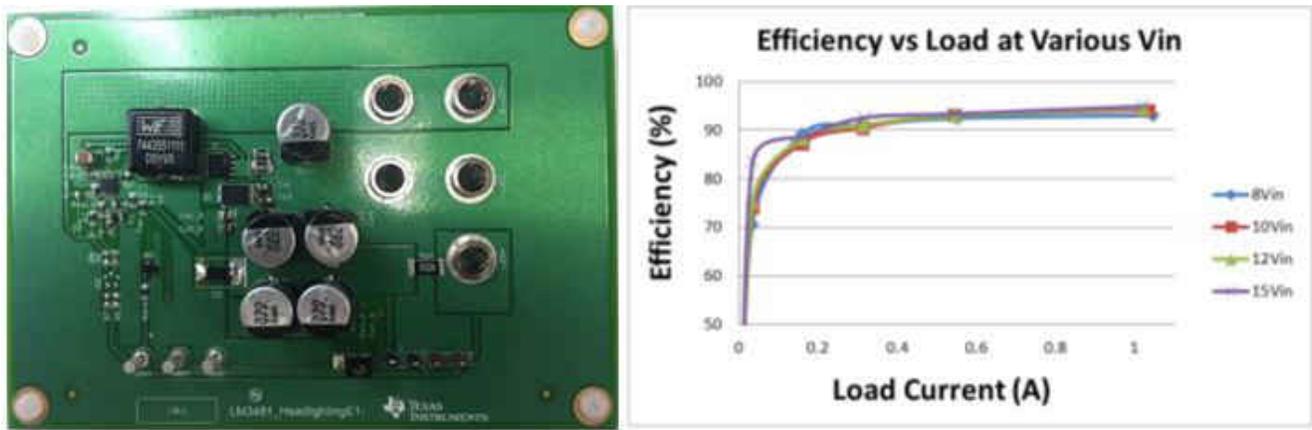


Figure 2. 24W LED Driver Reference Design – TIDA-01234

This reference design applies to automotive high-brightness lighting such as headlights, taillights and interior LED lighting systems. It is designed to operate with an input range from  $6V_{IN}$  to  $18V_{IN}$  and can drive multiple strings of six to seven LEDs ( $16V$  to  $24V$ ) in series at a  $1A$  constant current. While optimized for typical operating conditions, the design will also operate down to  $3V_{IN}$  for cold-crank conditions and up to  $42V_{IN}$  for load-dump conditions. The design supports analog LED brightness control and output open protection. In a boost-to-battery configuration, the input voltage can either be higher, lower or equal to the required LED strings voltage. See Figure 3.

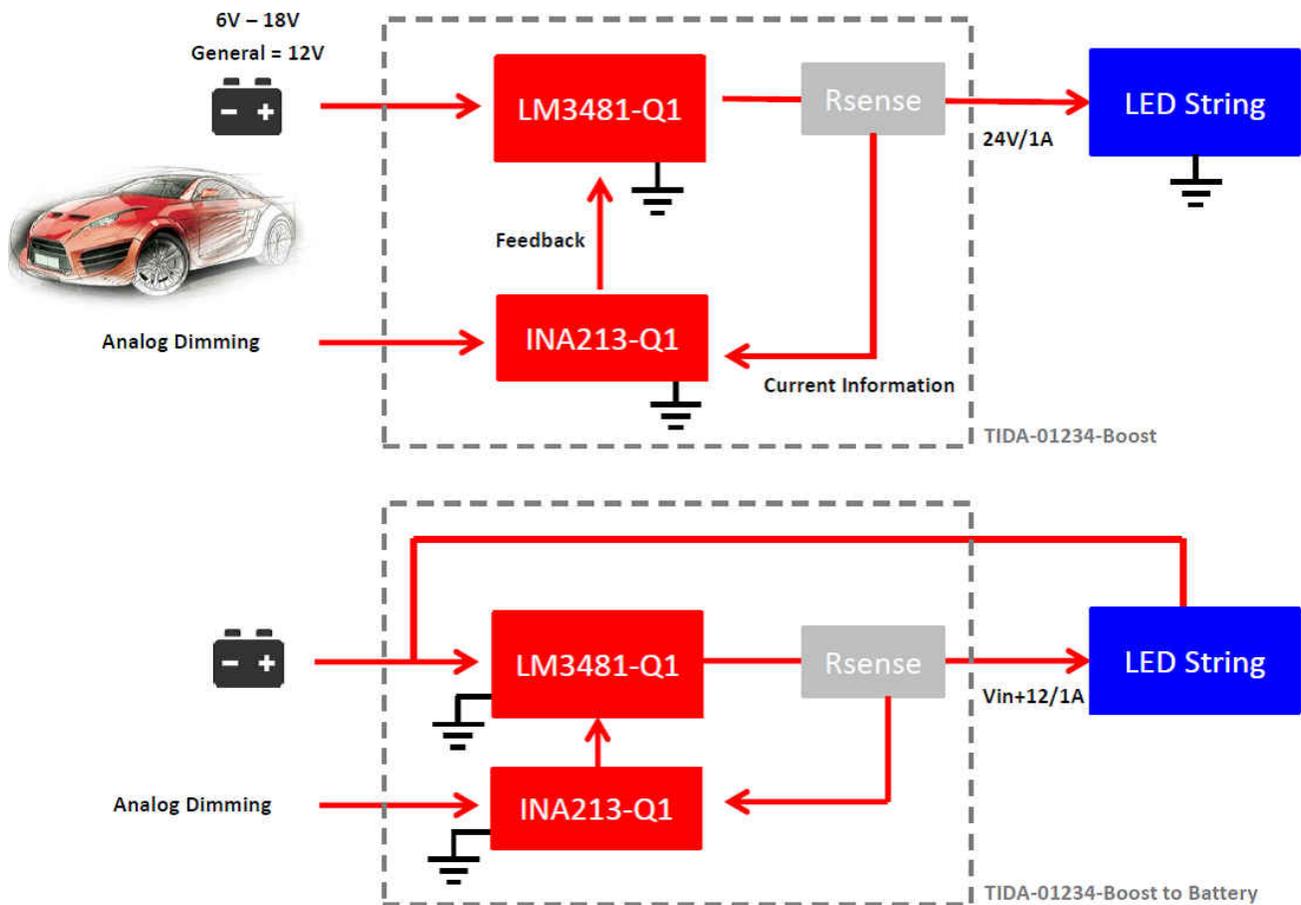


Figure 3. Boost-to-LED and Boost-to-battery Configurations

The output voltage is programmable using a resistor divider and feedback pins; this is necessary, as the value of the resistors will dictate the voltage output. The output current will depend on the load requirements and

the desired intensity of the LEDs. For an LED application, constant current is necessary in order to keep a specific desired brightness; maintaining that brightness under all conditions in an automotive system is part of the challenge. This reference design used current sensing to achieve constant current with the LM3481-Q1 boost controller.

In order to keep constant-current flows through the LEDs, there is a current-sense resistor,  $R_{shunt}$ , at the output of the controller to sense current flow. The design used a 50m $\Omega$  current-sense resistor to generate a 50mV crossing voltage. The INA213-Q1 amplifies this crossing voltage, which provides a gain = 50. Using an external voltage injected into the current-sense amplifier reference enables analog dimming of the LEDs at the output by changing the output current.

In case the output LED burns out or goes open at the output circuit (which will cause the output voltage to continuously rise), the reference design provides output open-circuit protection. In the boost configuration, a Zener diode connected between  $V_{OUT}$  and the voltage feedback divider clamps the output voltage at the Zener voltage ( $V_z$ ), plus the output voltage of the current-sense amplifier.

In order to generate constant current with the output voltage closed to the input voltage, you may think that you need to use a buck-boost or single-ended primary-inductor converter (SEPIC) structure, which is complex and costly. But by connecting the cathode of LED strings to input instead of ground, you can modify the reference design to a boost-to-battery configuration. In such a configuration, the input voltage can either be higher, lower or equal to the required LED strings voltage.

For the boost-to-battery, the reference design provides another solution for open-circuit protection. Using transistor Q2 (see [schematic](#)) combined with R5, R6, R7, R8 and D2 detects the differential voltage between output voltage and input voltage. When the differential voltage rises up to the overvoltage at output ( $V_{ov}$ ), Zener diode D2 will turn on and pull the compensation pin voltage down by Q3. As a result, the output voltage will stay low until the load appears again.

TI designed and tested the 24W Boost and Boost-to-Battery Reference Design for Automotive LED to support full automotive system conditions and issues that designers must overcome to make their designs successful. It also serves as a simple solution to meet the tough system-implementation costs and complexities of LED lighting circuits. Watch the video [“24W Boost and Boost-to-Battery Reference Design for Automotive LED Lighting”](#) and get more information on the [LM3481-Q1](#) and [INA213-Q1](#).

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated