

Precision Current Measurement Enhances Electronic Power-Steering Systems



DHarmon

As vehicles become more electrified – not just electric vehicles or hybrid-electric vehicles, but even good-old gasoline/diesel power machines – it becomes more critical to accurately monitor the current consumed to ensure performance as well as long-term reliability. One area where this has become vital is in electronic power-steering (EPS) systems.

EPS systems enhance vehicle safety by tailoring variable steering ratios to driver needs, minimizing drive-train interference and potentially modifying the applied torque in safety-critical situations. Driving conditions such as speed can determine the required level of torque and help optimize performance for different driving situations. Consider the different torque requirements required to turn the vehicle when traveling at highway speeds on the German autobahn versus parking at your local grocery store. EPS will provide higher levels of assistance at low speeds than at higher speeds, when it's not as necessary.

Current measurement is a common requirement across EPS systems. [Figure 1](#) is a high-level block diagram that shows the basics of a typical EPS implementation. I'll review several types of current sensing implementations for EPS and the advantages of each.

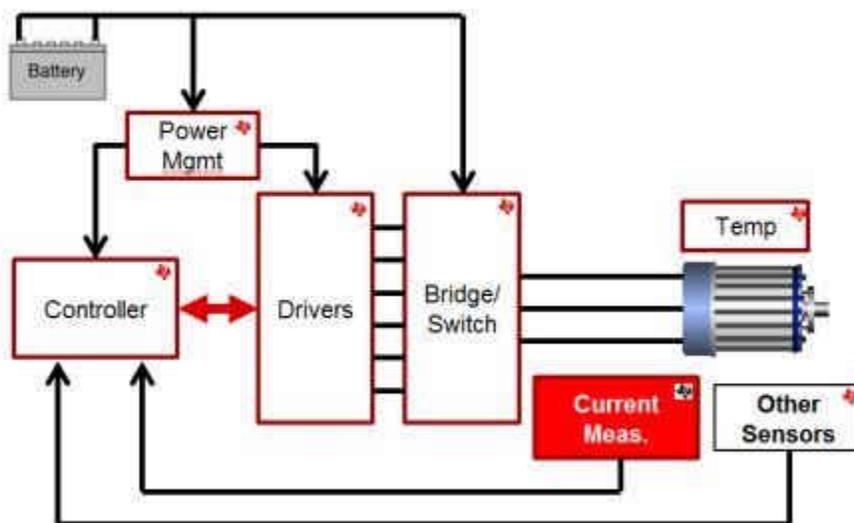


Figure 1. A Typical EPS System

[Figure 2](#) shows four options for current sensing in an EPS system: high-side over-current protection (OCP), low-side OCP, low-side phase current, and in-line phase current. The needs of the system will determine which of the four current-measurement options will be chosen by the system designer. To ensure vehicle safety, it is important to accurately monitor the torque applied to the steering column and translate this into a vehicle response. Precision current measurement ensures the accuracy of this torque detection.

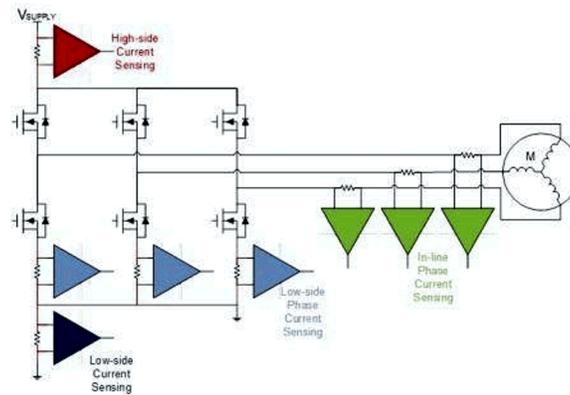


Figure 2. Circuit Diagram Showing Four Potential Current-measurement Options for Three-phase Motor Implementations

Systems wanting to achieve maximum performance require precise regulation of the current through the motor to control the motor torque. In-line motor phase current is the only method that will provide continuous phase current, as well as providing the most accurate phase-current representation. However, precisely recreating this in-line phase current presents challenges in selecting an appropriate current sense amplifier for the motor control system. These challenges include the need to identify an amplifier that supports a negative common-mode voltage range to handle the motor’s inductive kickback or to protect the system from a reverse-battery condition. The common-mode voltage at the inputs of the measurement system may be higher than what normal amplifiers can support, as well as having a high dV/dT pulse-width modulated (PWM) nature.

To learn more about the challenges of precise in-line current measurement and how Texas Instruments current-sense amplifiers can help you solve the challenge, see the short, use-case technical documents called TI TechNotes, “[Low-Drift, Precision, In-Line Motor Current Measurements with Enhanced PWM Rejection](#)” and “[Low-Drift, Low-Side Current Measurements for Three-Phase Systems](#)” for additional EPS system options. In addition, you can check out the Texas Instruments portfolio of [current-sense amplifiers](#).

Additional Resources

- [Getting Started with Current Sense Amplifiers video training series](#).
- Download the “[Current Sense Amplifiers](#)” brochure.
- Download the “[TI Over-Current Detection Products](#)” brochure.
- [Automotive Precision eFuse Reference Design \(TIDA-00795\)](#).
- Browse current sensing use cases in short, easy-to-read [TI TechNotes](#).

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated