

Power Tips: Designing an LLC Resonant Half-bridge Power Converter



Sheng-yang Yu

Unlike traditional pulse-width modulation (PWM) power converters, resonant converter output voltages are regulated by frequency modulation. Therefore, the design methodology of a resonant converter will be different from a PWM converter.

Among various types of resonant converters, the LLC series resonant converter (LLC-SRC) in [Figure 1](#) attracts interest because of its better output regulation, lower circulating current and lower circuit cost.

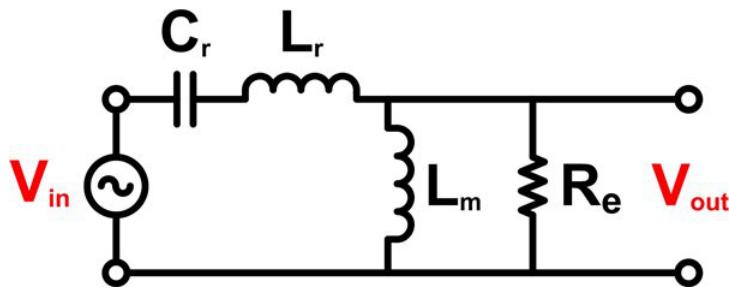


Figure 1. LLC-SRC with AC Input/output Voltage

The series resonant characteristics allow the switching network in a DC/DC LLC-SRC, such as that shown in [Figure 2](#), to have very wide region of zero-voltage switching (ZVS); hence, the LLC-SRC can easily achieve over 94% efficiency in front-end power-supply applications and operate at a high switching frequency.

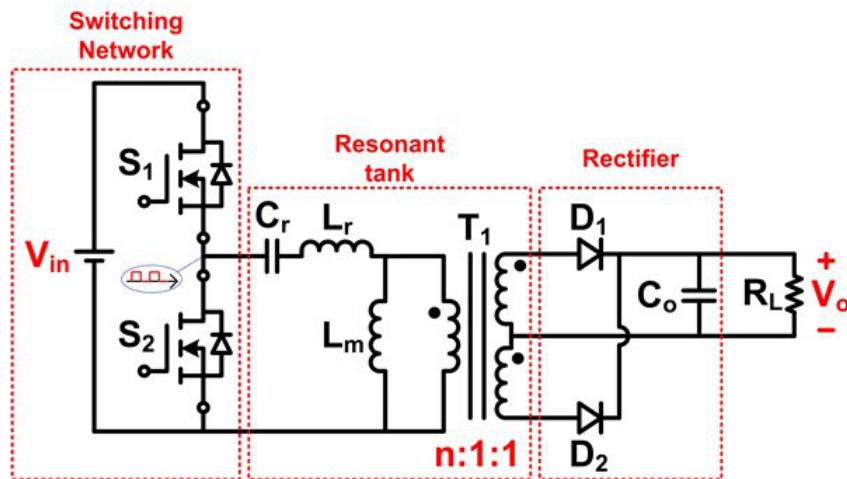


Figure 2. LLC Resonant Half-bridge Converter

Similar to the design process for PWM converters, the first step when designing an LLC-SRC is to select the desired operation frequency at full load. The remaining steps are different, because there is no duty-cycle factor in a resonant converter. The duty cycle remains unchanged in an LLC-SRC and is ideally 50%. [Figure 3](#) shows a design flow chart for an LLC-SRC from [TI Power Supply Design Seminar](#) topic “Designing an LLC Resonant Half-Bridge Power Converter.”

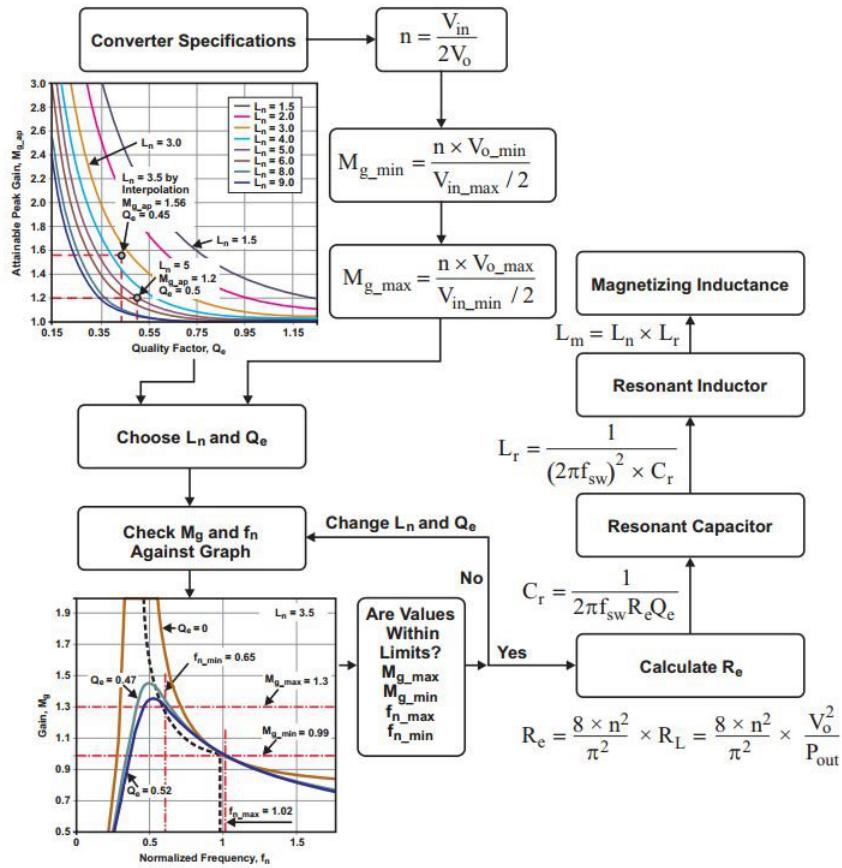


Figure 3. LLC Resonant Half-bridge Converter Design Flow Chart

Notice that M_g is the DC voltage gain, L_n is the ratio of L_m and L_r , and the quality factor is defined as Equation Figure 4:

$$Q_e = \frac{\sqrt{L_r / C_r}}{R_e} \quad (1)$$

Figure 4. (1)

Also, f_n is the normalized frequency defined as $f_n = f_{sw}/f_o$, where

$$f_o = \frac{1}{2\pi\sqrt{L_r C_r}}$$

The gain curves in both the M_g/Q_e and M_g/f_n charts are derived from the LLC resonant tank shown in Figure 1, which is also a linearized circuit of a LLC resonant half-bridge converter.

Figure 3 provides a simple circuit parameter selection process of an LLC resonant half-bridge converter. By checking the f_{n_min} , f_{n_max} locations on the gain curves, you will be able to design a high-efficiency LLC resonant half-bridge converter with ZVS on the switching network under all input conditions.

When designing a LLC resonant half-bridge converter, keep in mind that:

- f_{n_min} needs to be above the ridges of the gain curves in the M_g/f_n chart at all times. This is to make sure that the MOSFETs maintain ZVS.

- LLC-SRC efficiency can only be optimized at one operation point. When $f_{sw} = f_o$, the series L_r and C_r become zero impedance (Figure 5); the converter has best efficiency at that point. You will need to decide the line/load condition that you want to optimize and make sure that your switching frequency is at resonant frequency at that condition.

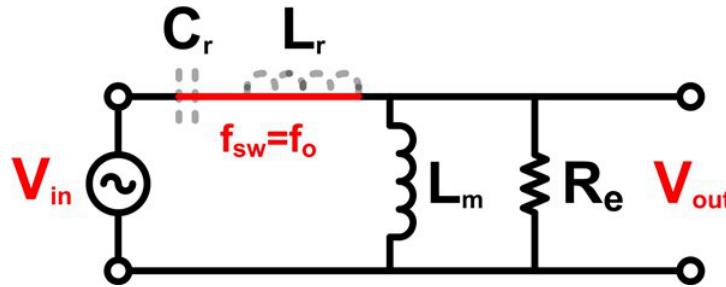


Figure 4. LLC-SRC with AC Input/output Voltage When $F_{sw} = F_o$

Additional Resources

- Find more information about LLC-SRC design and optimization in the [TI Power Supply Design Seminars](#) papers.
- Read my previous blogs on LLC converters
 - [Get to know LLC series resonant converter design](#)
 - [How much can a LLC series resonant converter do?](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated