


Test Report: PMP30524

Isolated 24-W Flyback Reference Design for Industrial and Automotive Applications



Description

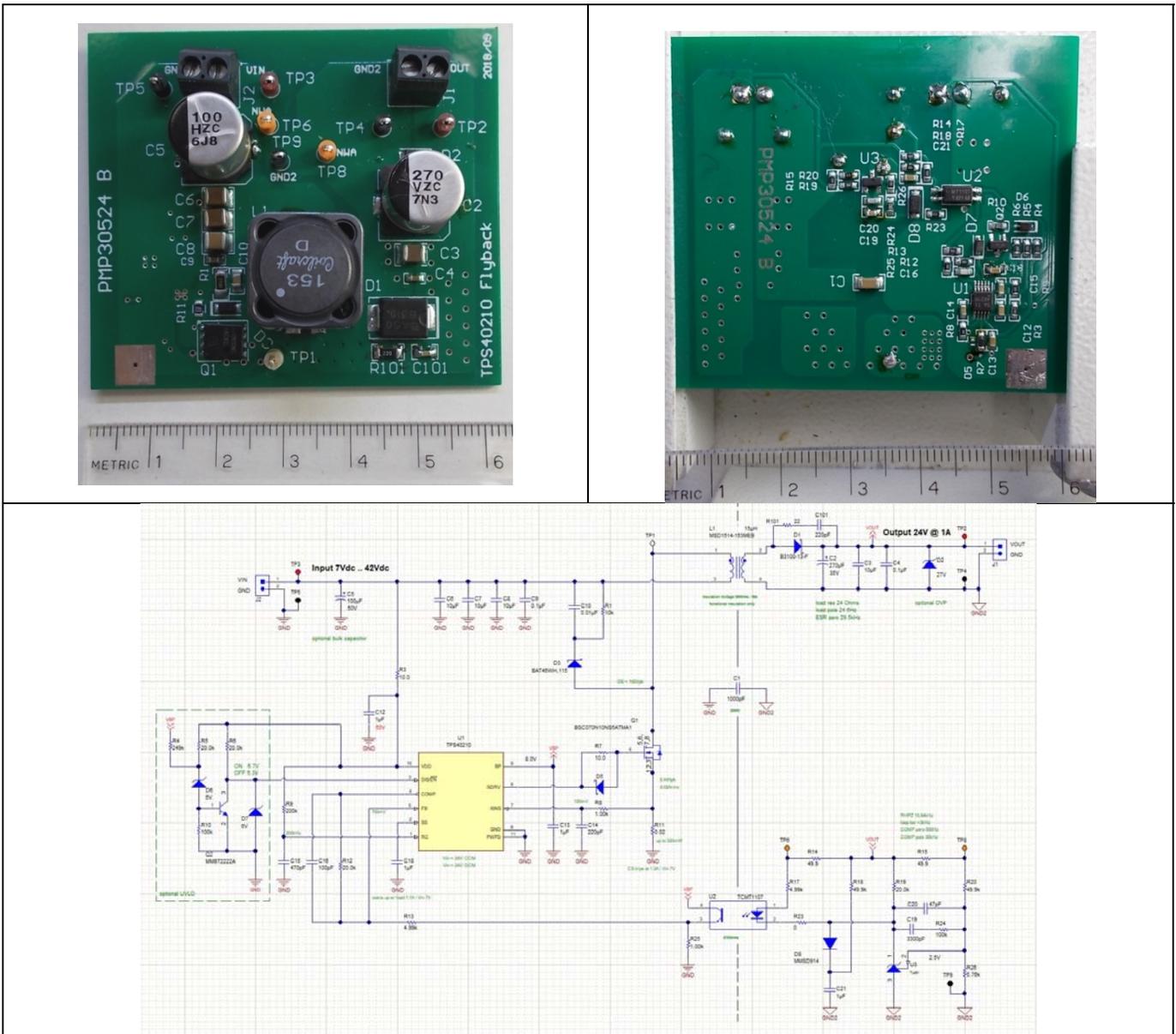This reference design provides functional isolation 500 Vrms by simply using a dual inductor from stock. Overall, the design is driven by minimum cost using TPS40210 and adding discrete UVLO. Also, the input range of 1:6 exceeds industrial standard by 7 V to 42 V, which makes this reference design ideal for several applications.



 An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1. Voltage and Current Requirements

PARAMETER	SPECIFICATIONS
Input Voltage	7 V to 42 V
Output Voltage	24V
Output Current (max)	1A
Isolation	here: 500Vrms functional*

* limited by dual inductor; Xcap allows up to 2kV, opto isolator up to 3.75kV

1.2 Considerations

Unless otherwise indicated, resistor was used as load. The output current was adjusted to 1A. The circuit switches on at 6.7 V and off at 6.3 V. This individual circuit switches around 205 kHz.

The converter itself works in boundary mode, means CCM at low input voltage and respectively DCM at high input voltage. Reducing magnetizing inductance results in smaller transformer geometry and increased loop bandwidth due to bigger RHPZ – but accepting slightly increased peak currents.

The transfer region DCM to CCM could be seen around:

$7V_{in}$ $150mA_{out}$
 $12V_{in}$ $350mA_{out}$
 $24V_{in}$ $800mA_{out}$
 $>32V_{in}$ $1000mA_{out}$

2 Testing and Results

2.1 Efficiency Graphs

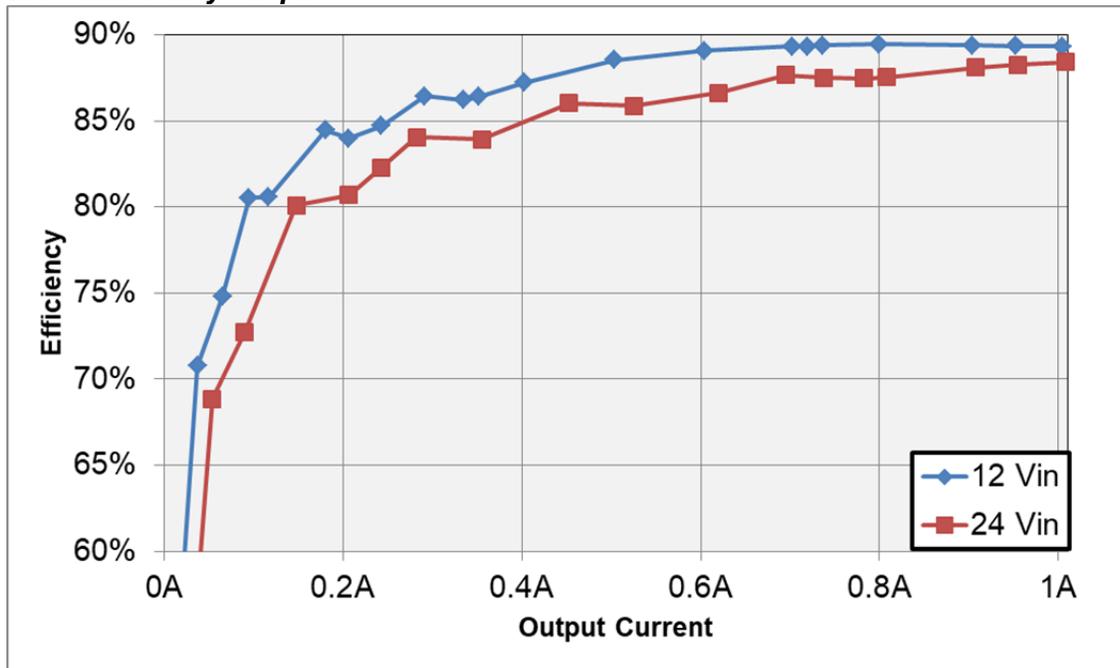


Figure 1 Efficiency vs Output Current

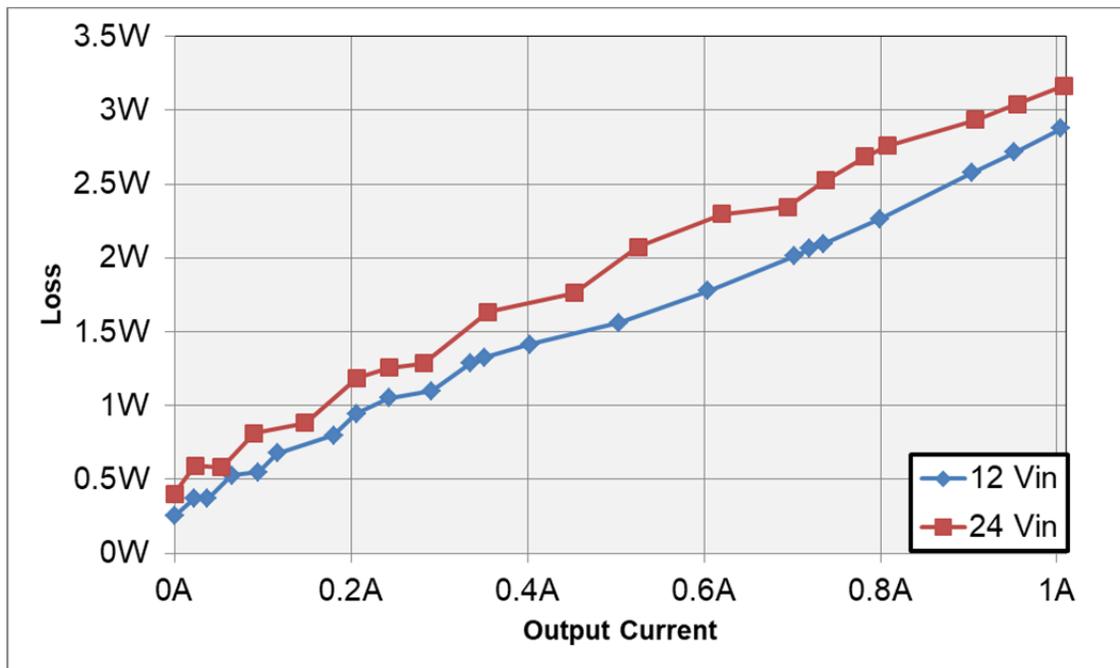


Figure 2 Loss vs Output Current

2.2 Load Regulation

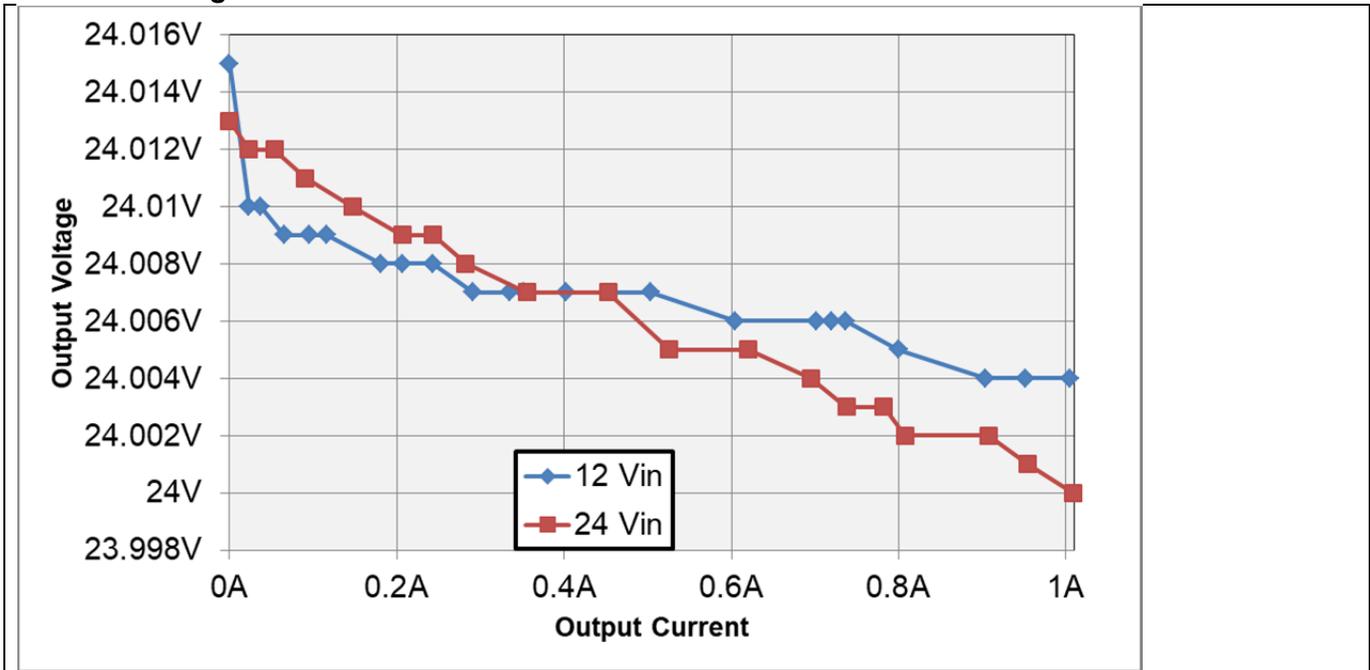


Figure 3 Load Regulation

2.3 Line Regulation

The output current was adjusted to 1A.

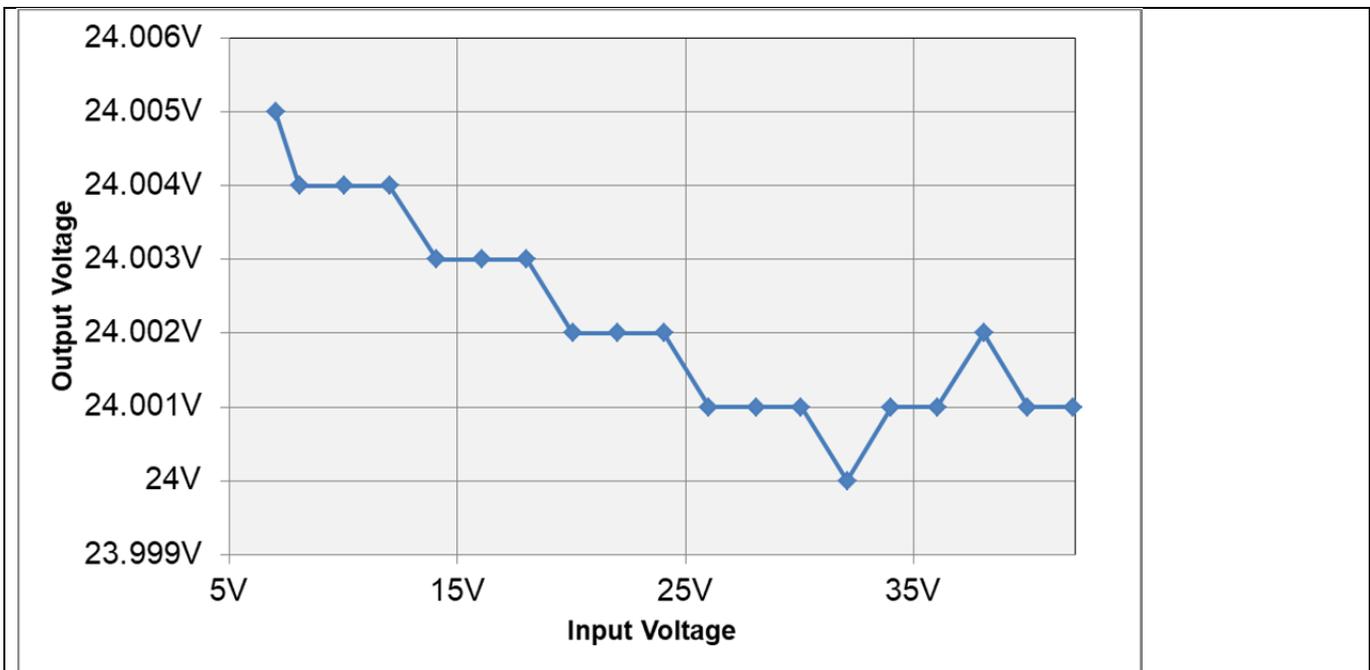


Figure 4 Line Regulation

With the same setup efficiency and loss were calculated.

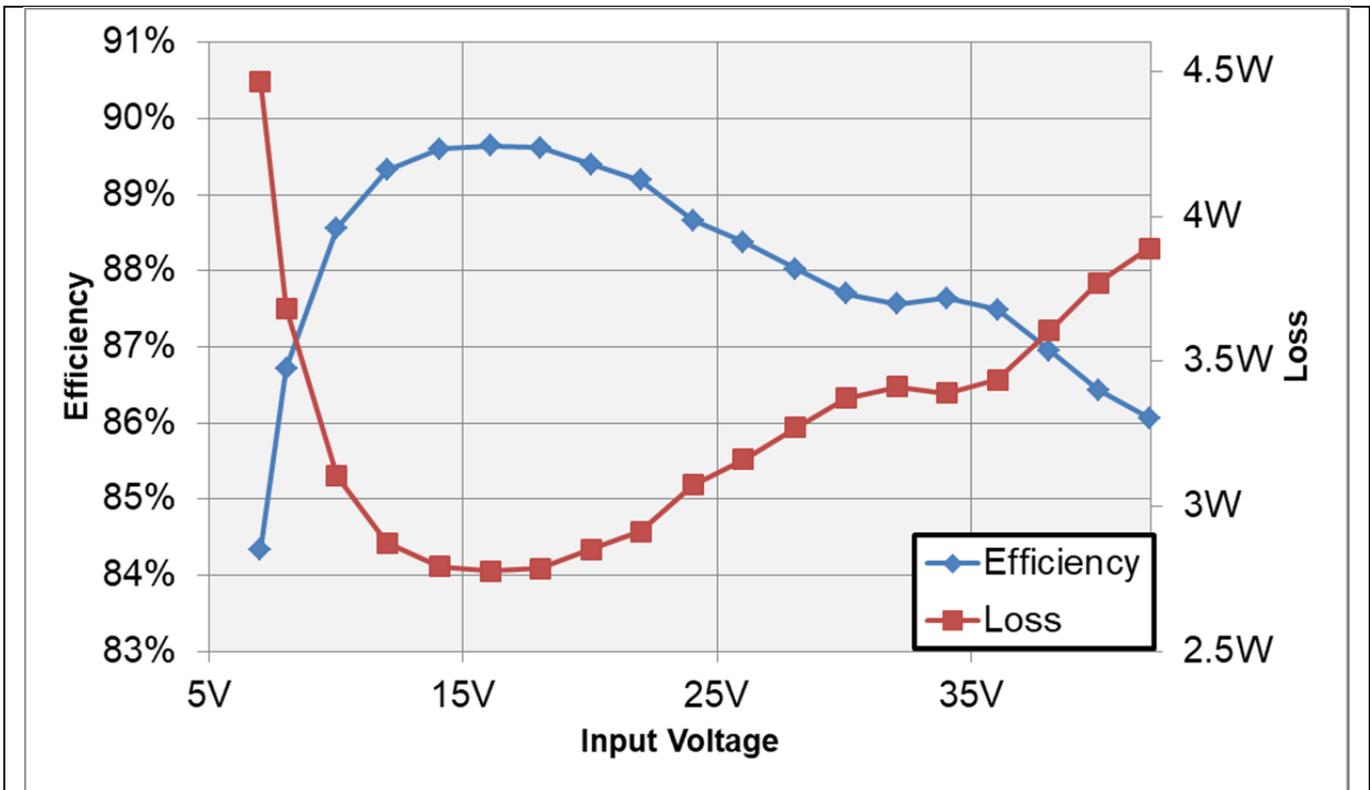


Figure 5 Efficiency and Loss vs Input Voltage

2.4 Thermal Images

2.4.1 12 V Input Voltage - full load 1A

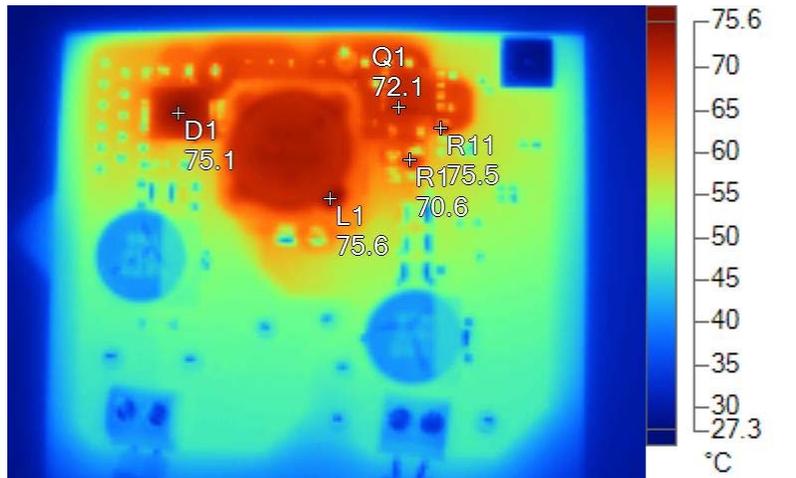


Figure 6 IR Photo for 12 V Input Voltage

Name	Temperature
D1	75.1°C
L1	75.6°C
Q1	72.1°C
R1	70.6°C
R11	75.5°C

2.4.2 24 V Input Voltage - full load 1A

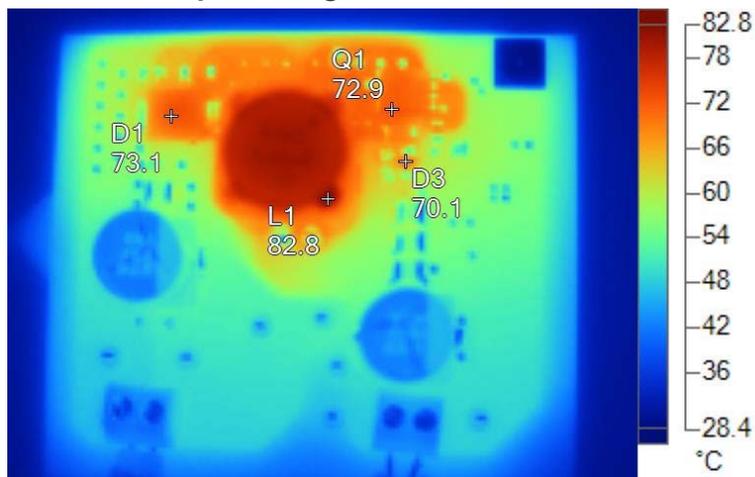


Figure 7 IR Photo for 24 V Input Voltage

Name	Temperature
D1	73.1°C
D3	70.1°C
L1	82.8°C
Q1	72.9°C

2.4.3 24V Input Voltage and 700mA Output Current

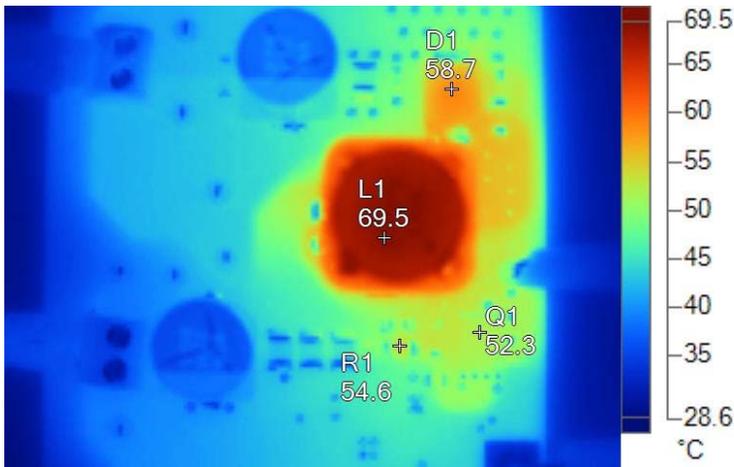


Figure 8 IR Photo for 24 V Input Voltage and 0.7 A Output Current

Name	Temperature
D1	58.7°C
L1	69.5°C
Q1	52.3°C
R1	54.6°C

3 Waveforms

3.1 Switching

3.1.1 Transistor Q1, 100V FET (Drain-Source)

3.1.1.1 12 V Input Voltage

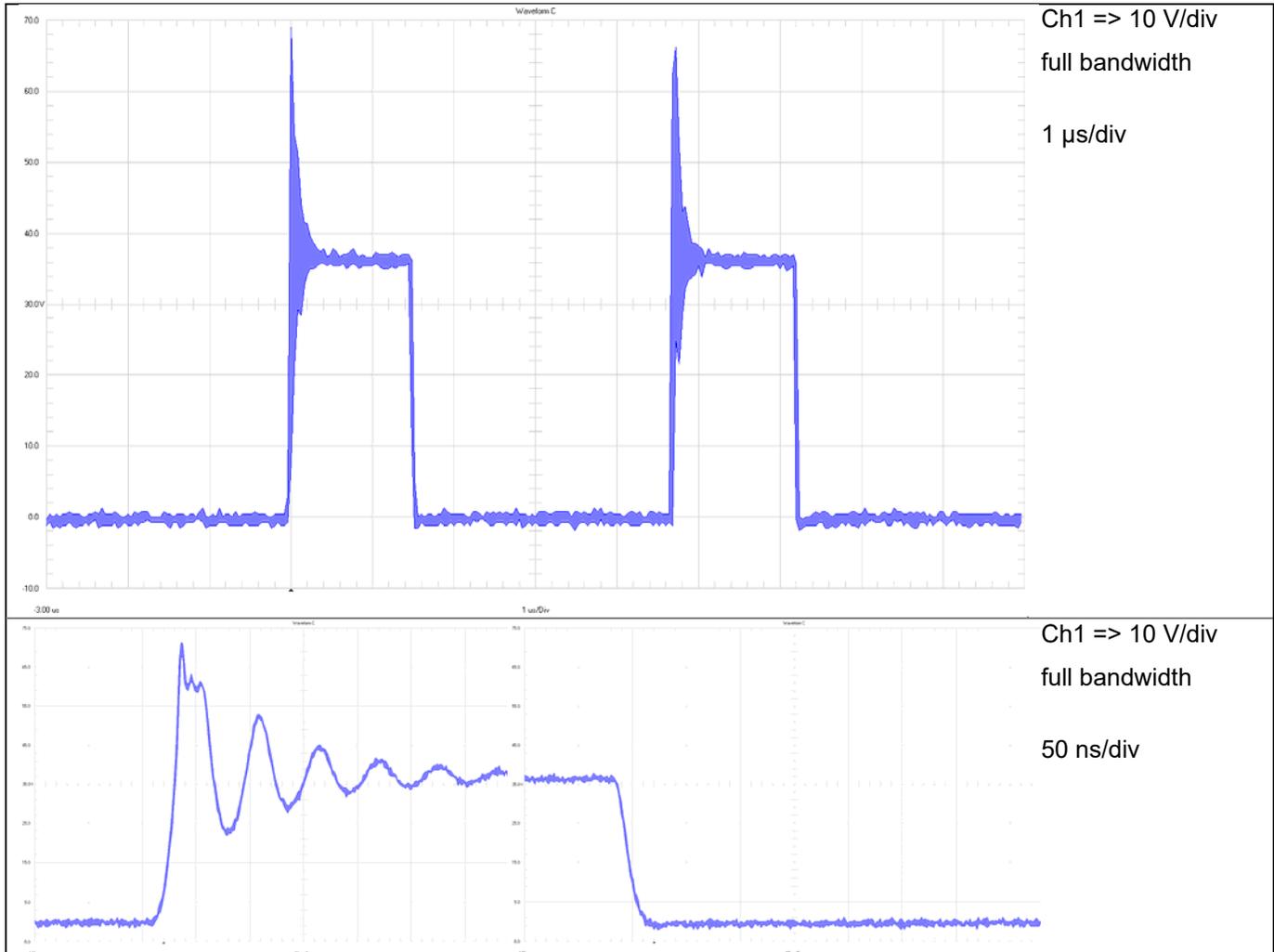


Figure 9 Switchnode Q1 at 12 V Input Voltage

3.1.1.2 24 V Input Voltage

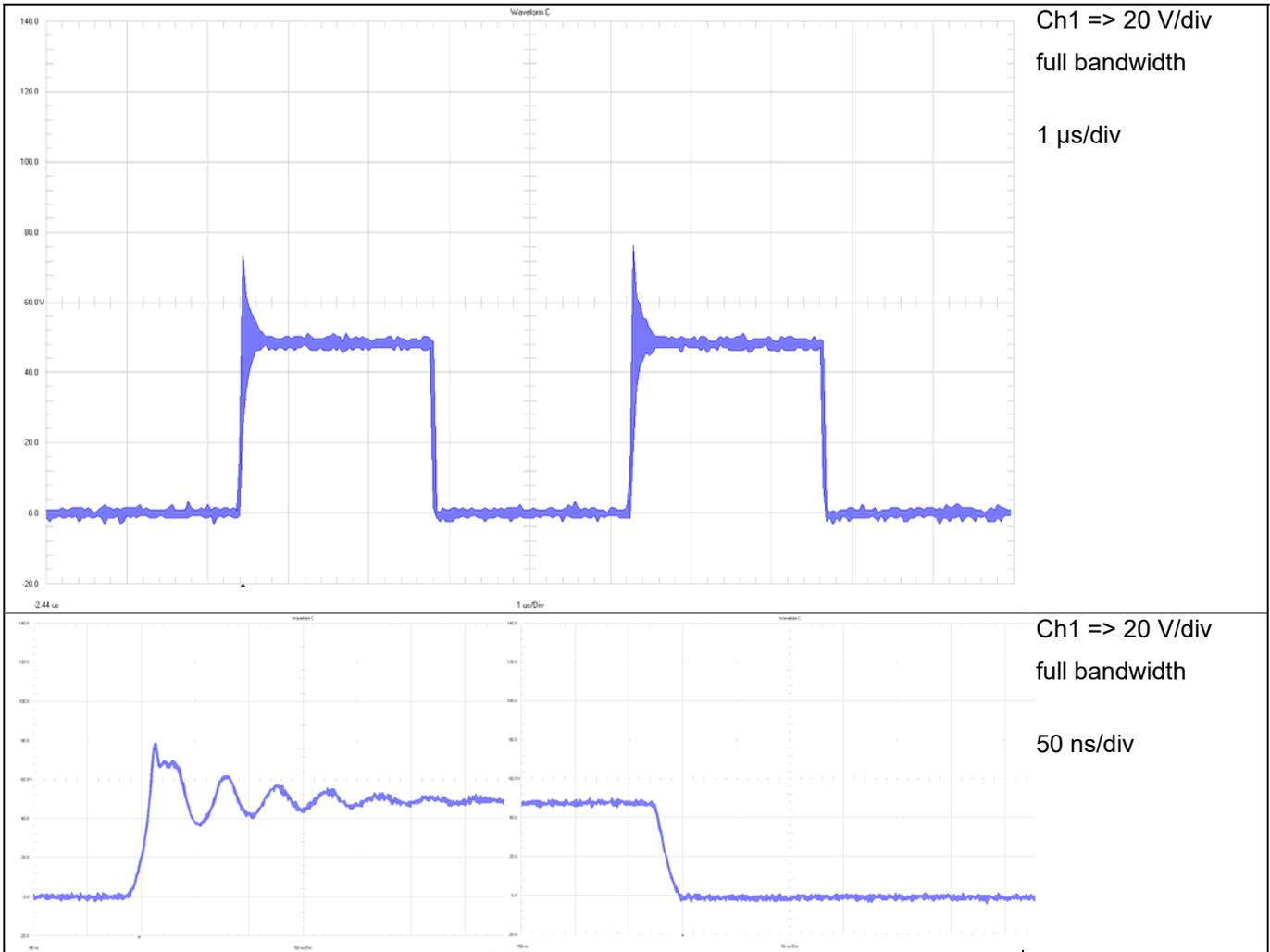


Figure 10 Switchnode Q1 at 24 V Input Voltage
(at maximum input 42V Vds is clamped to less than 90Vpk)

3.1.2 Transistor Q1 Gate (Gate to Source)

3.1.2.1 12 V Input Voltage

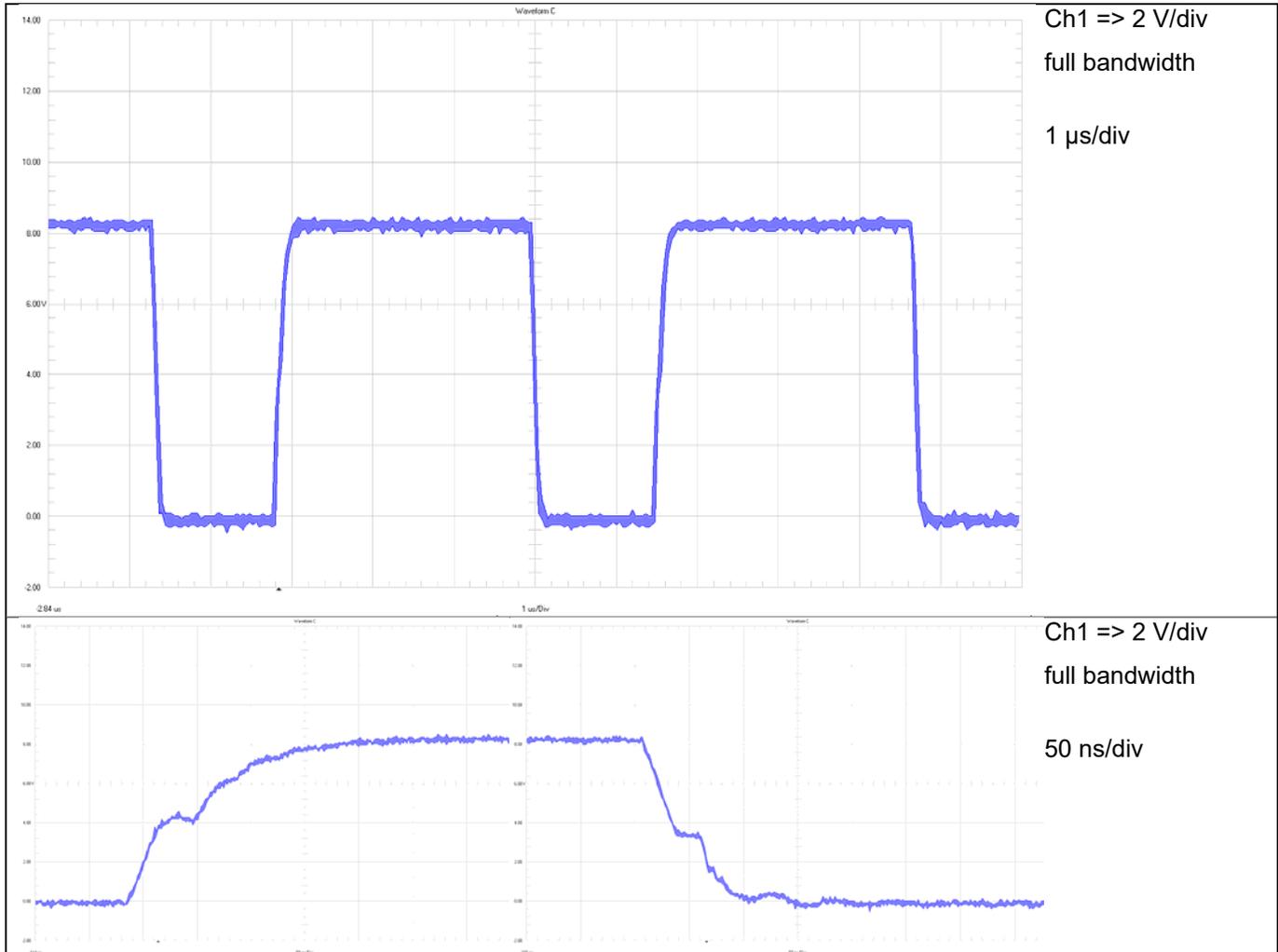


Figure 11 Q1 Gate at 12 V Input Voltage

3.1.2.2 24 V Input Voltage

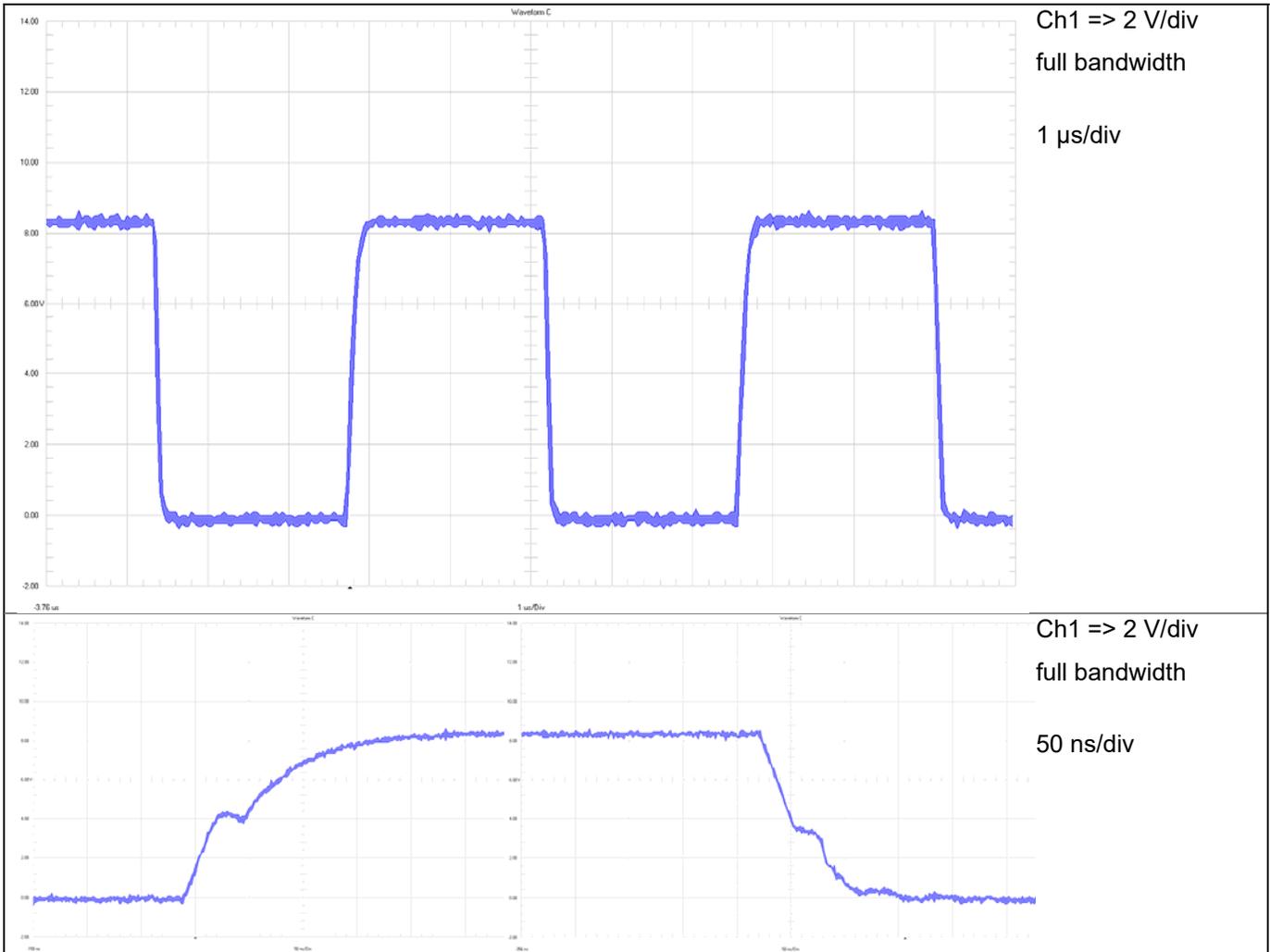


Figure 12 Q1 Gate at 12 V Input Voltage

3.1.3 Diode D1

These waveforms were measured with reference to output voltage.

3.1.3.1 12 V Input Voltage

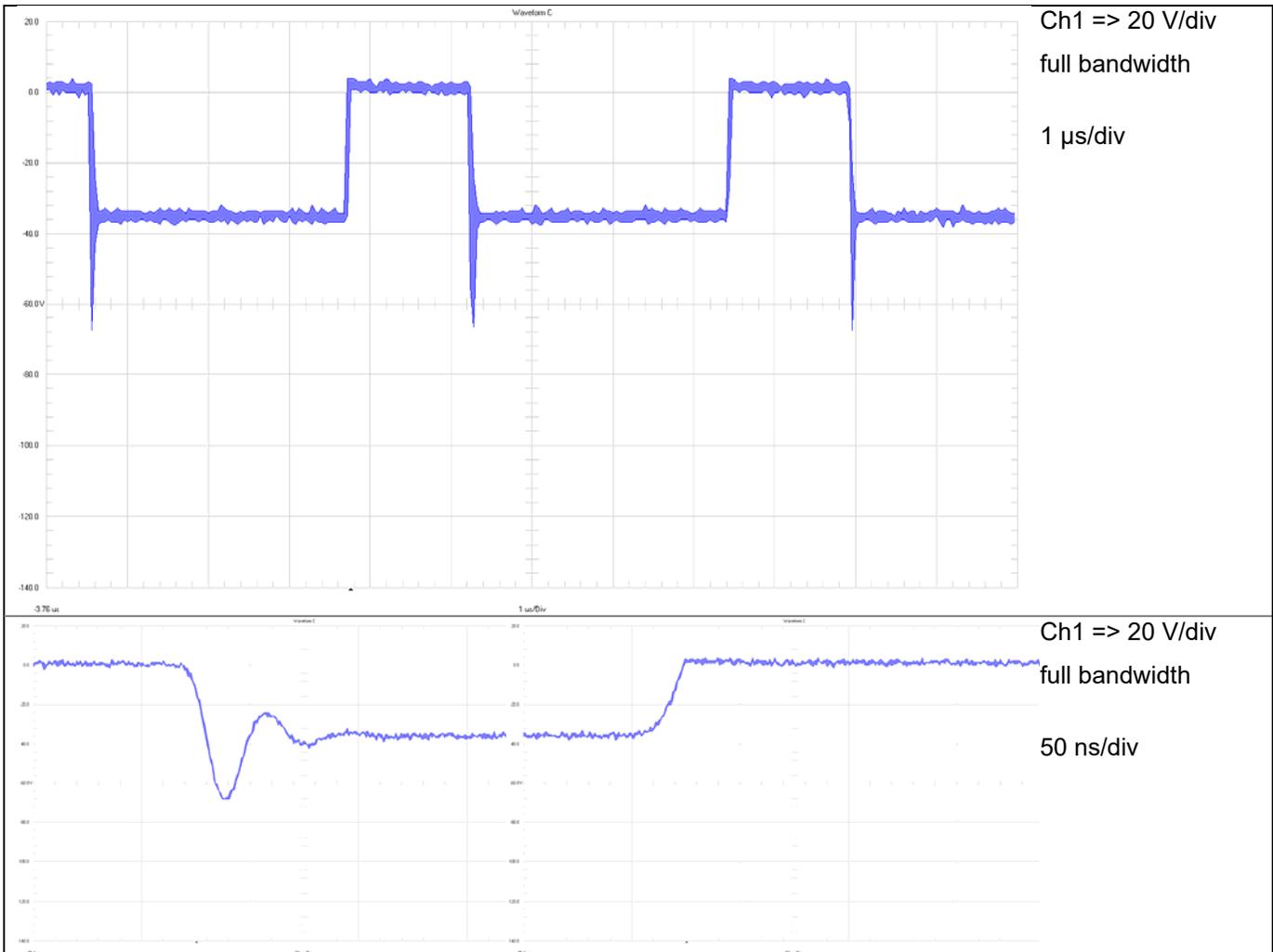


Figure 13 Diode D1 at 12 V Input Voltage

3.1.3.2 24 V Input Voltage

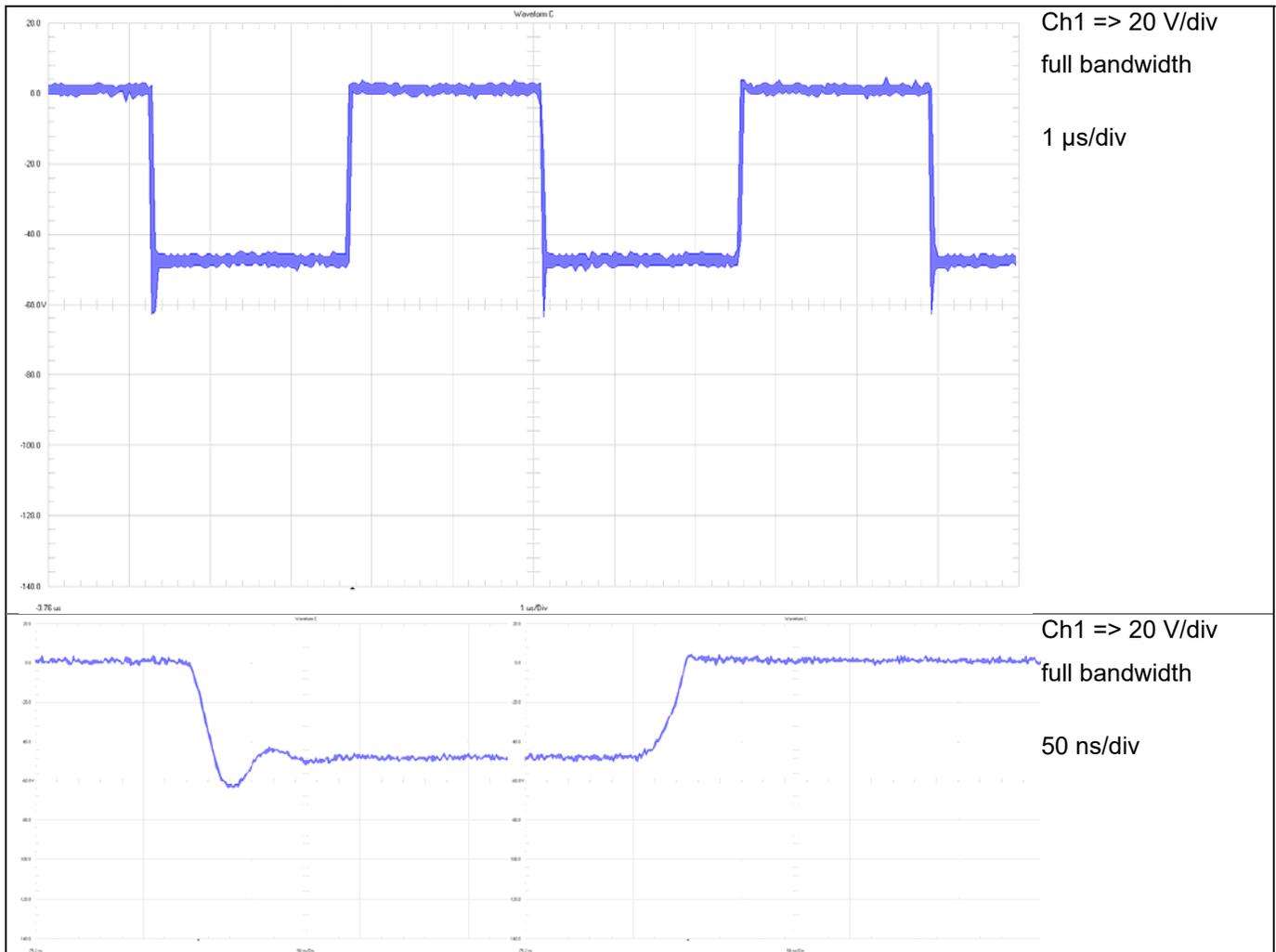


Figure 14 Diode D1 at 24 V Input Voltage

3.2 Output Voltage Ripple

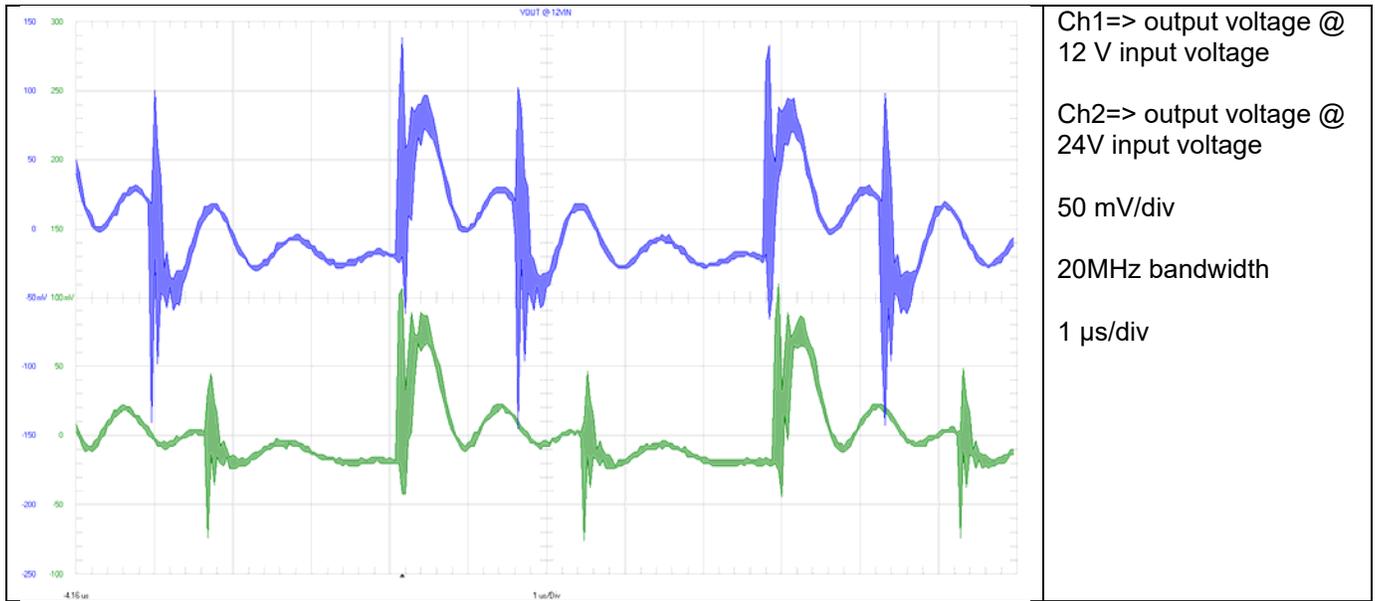


Figure 15 Output Ripple Voltage

3.3 Input Ripple Voltage

3.3.1 12 V Input Voltage

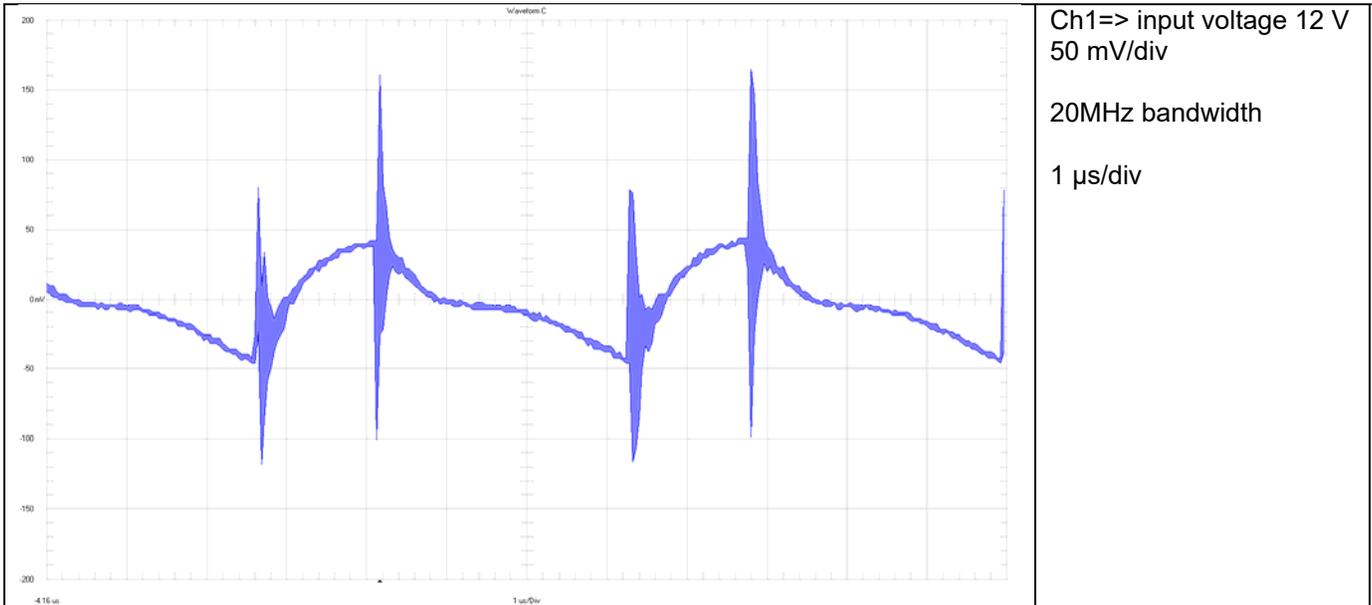


Figure 16 Input Ripple Voltage (12V Input Voltage)

3.3.2 24 V Input Voltage

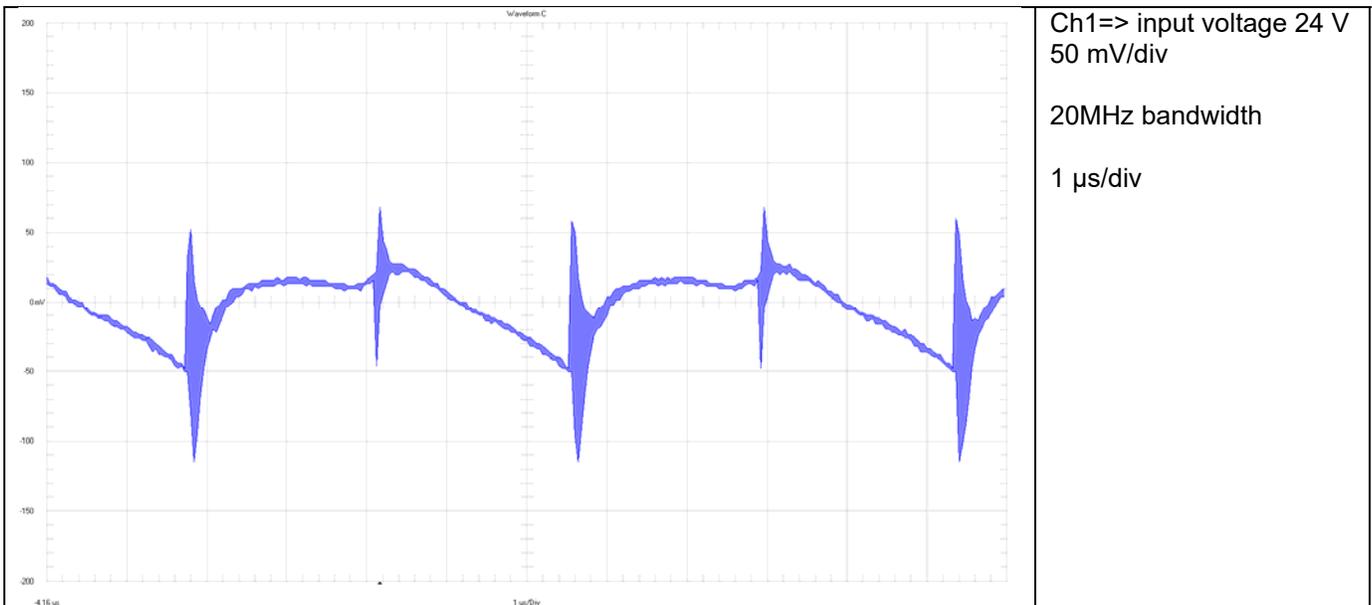


Figure 17 Input Ripple Voltage (24 V Input Voltage)

3.4 Bode Plot

Table 1 summarizes the results from Figure 18, Figure 19 and Figure 20. Bode box good for 100Hz to 10kHz were used.

	7 V	12 V	24 V
Bandwidth (Hz)	907	1300	1795
Phasemargin	83°	93°	98°
slope (20dB/decade)	-1.0	-0.87	-0.75
gain margin (dB)	18	21	20
slope (20dB/decade)	-0.7	-1.2	-1.6
freq (kHz)	10.9	16.2	17.3

Table 1 Summary of the Bodeplots

3.4.1 7 V Input Voltage

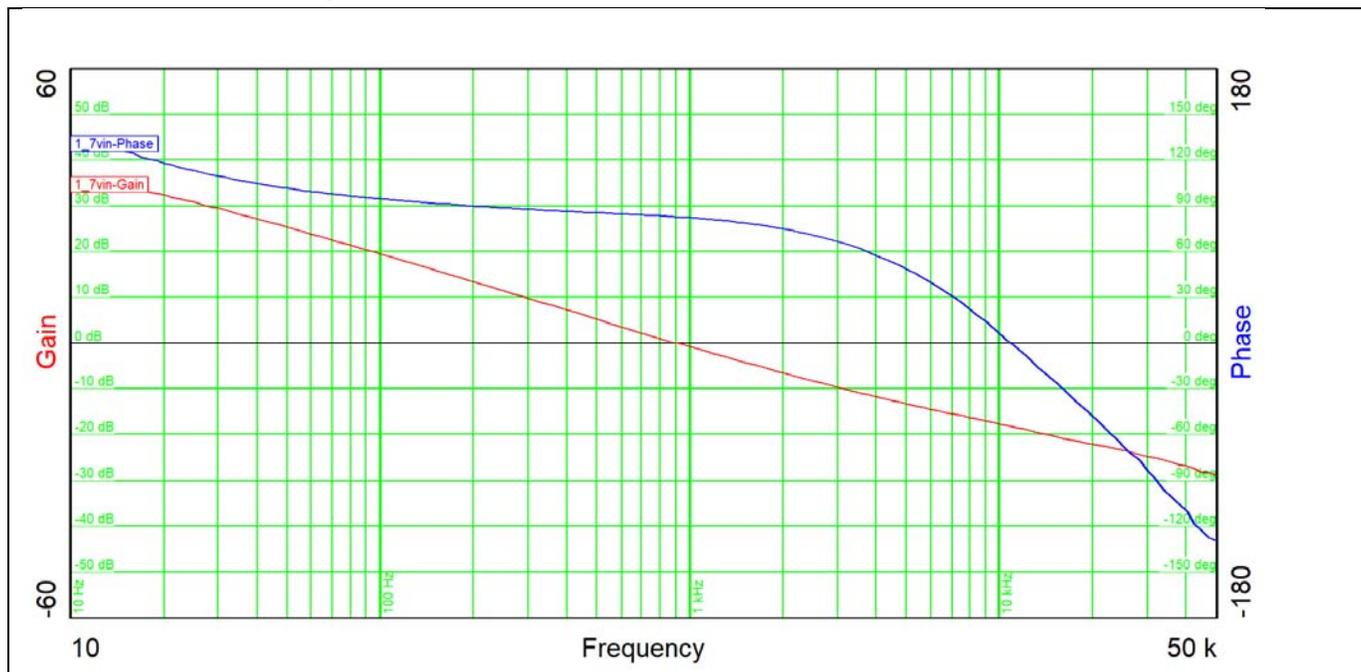


Figure 18 Bode Plot for 7 V Input Voltage

3.4.2 12 V Input Voltage

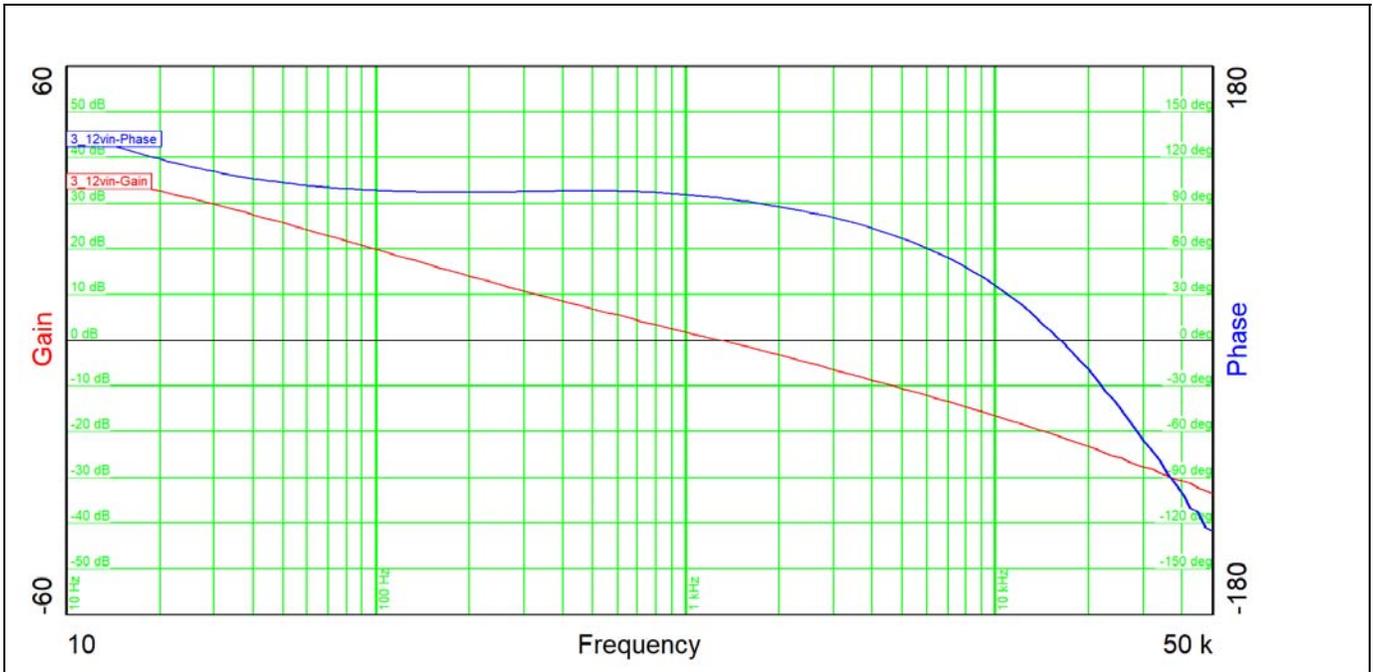


Figure 19 Bode Plot for 12 V Input Voltage

3.4.3 24 V Input Voltage

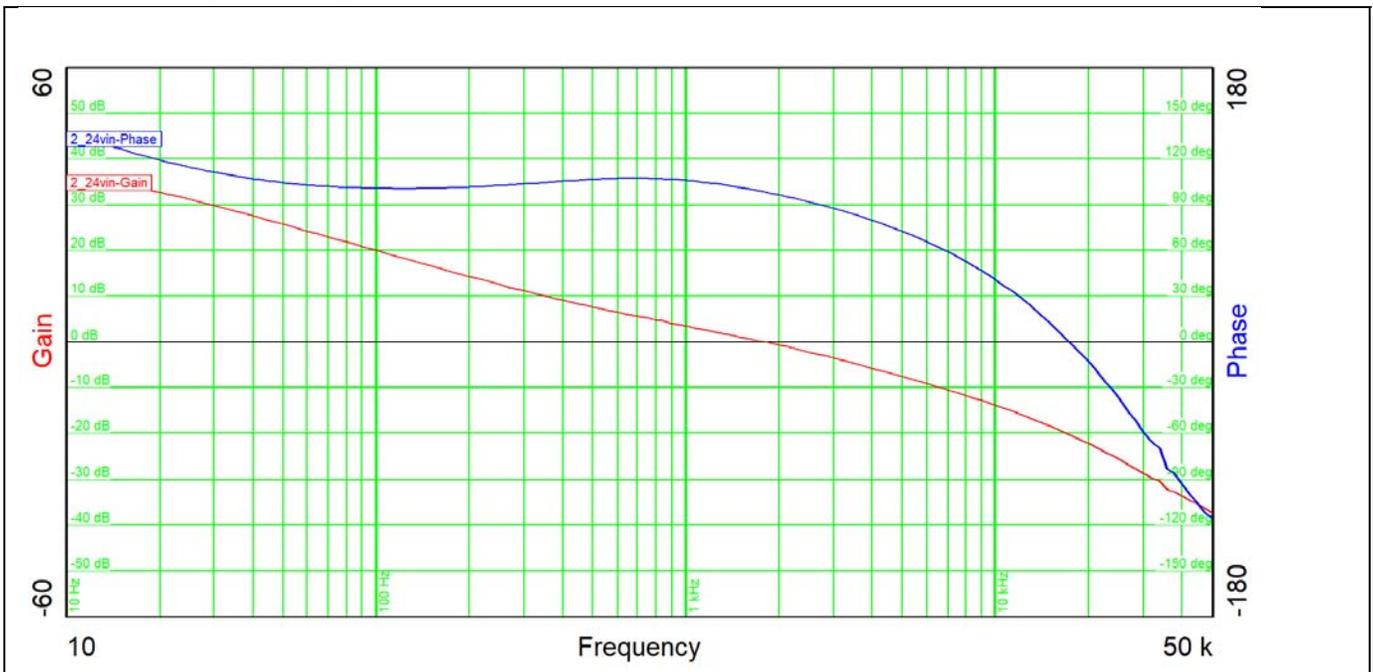


Figure 20 Bode Plot for 24 V Input Voltage

3.5 Load Transients

Electronic load has been used to create the load steps of 0.5 A to 1 A (100 Hz);
The deviation is only around 1% Vout !

3.5.1 12V Input Voltage

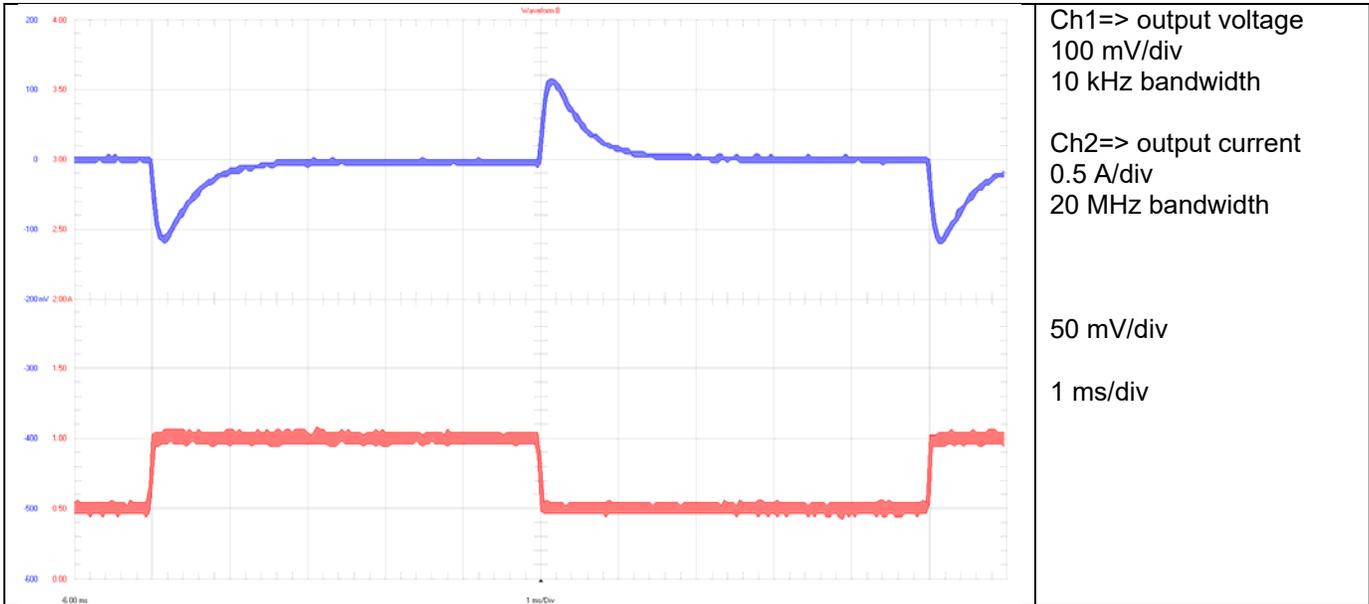


Figure 21 Load Transient with 12V Input Voltage

3.5.2 24V Input Voltage

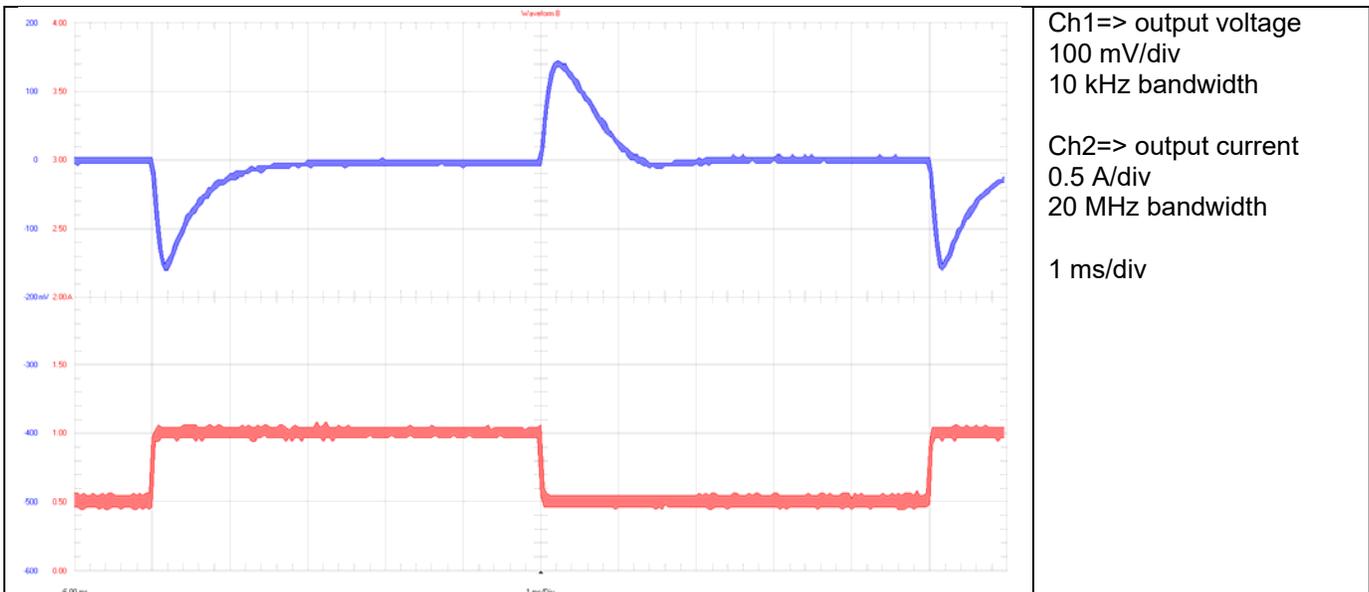


Figure 22

3.6 Start-up Sequence

Oscilloscope with isolated channels was used. The power supply was plugged in.

3.6.1 12 V Input Voltage

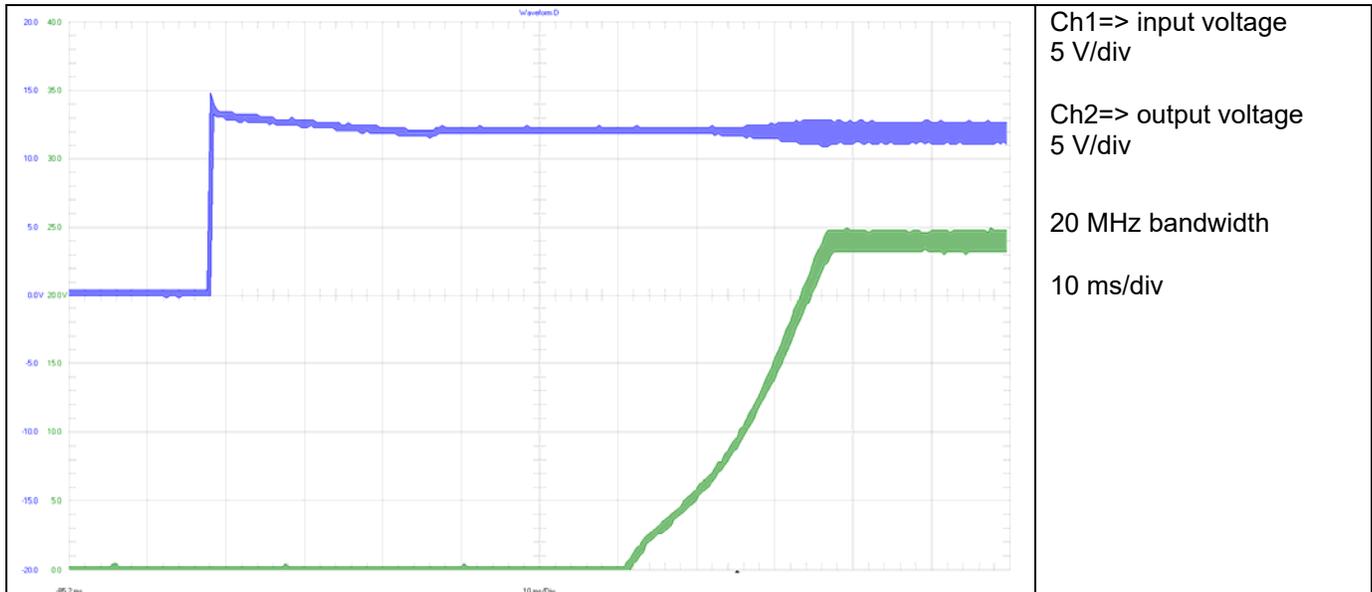


Figure 23 Start-Up with 12 V Input Voltage

3.6.2 24 V Input Voltage

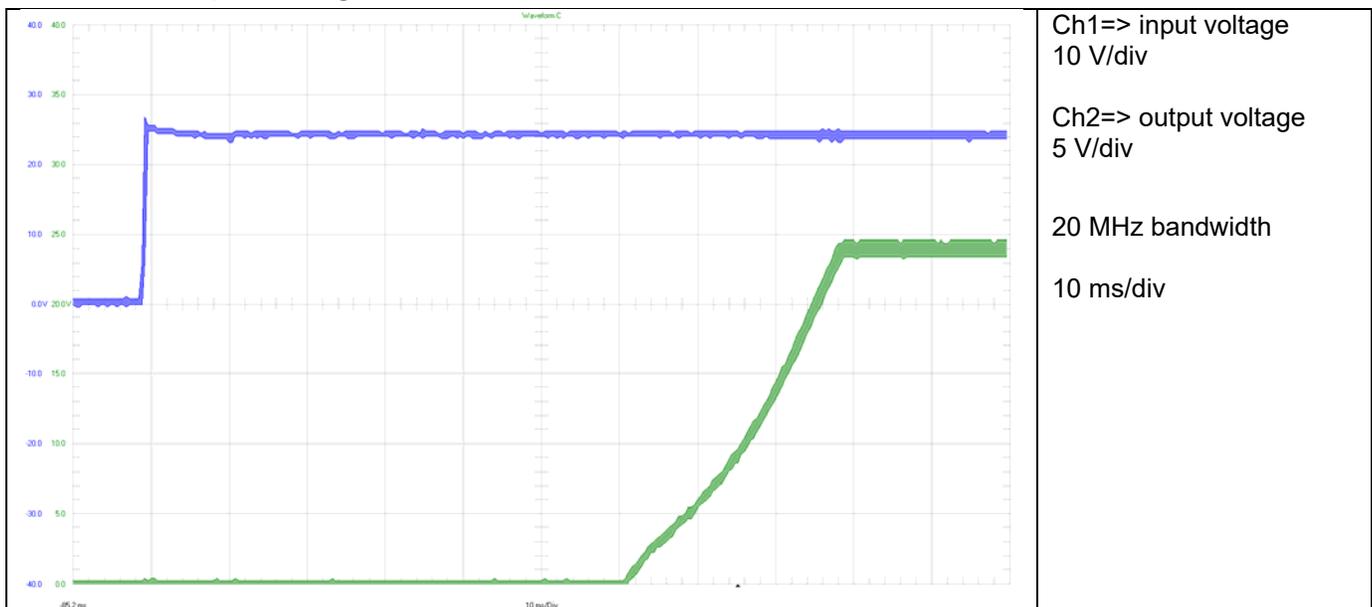


Figure 24 Start-Up with 24 V Input Voltage

3.7 Shutdown Sequence

Oscilloscope with isolated channels was used. The power supply was disconnected.

3.7.1 12 V Input Voltage

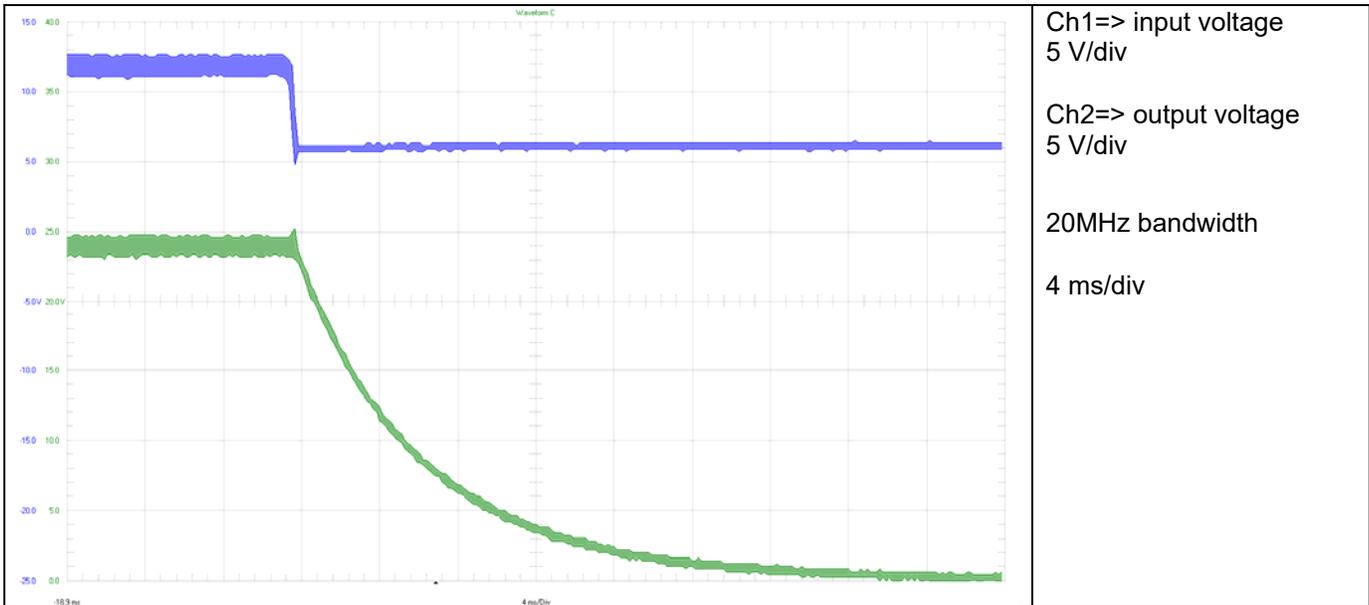


Figure 25 Shutdown with 12 V Input Voltage

3.7.2 24 V Input Voltage

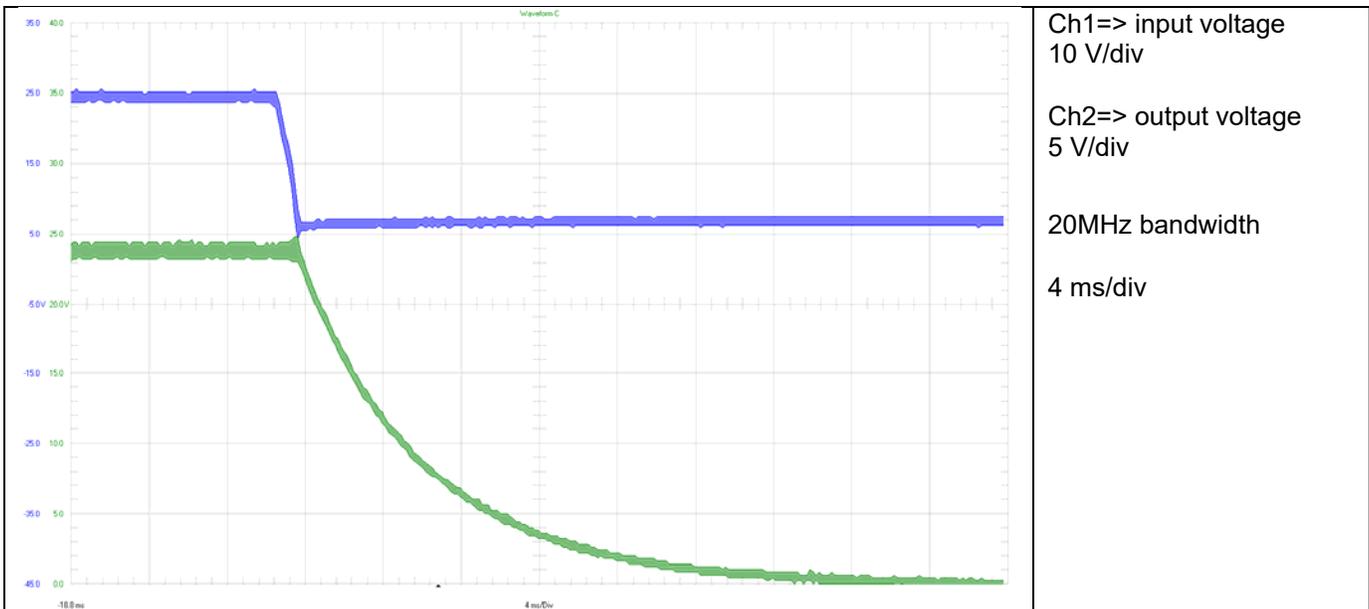


Figure 26 Shutdown with 24 V Input Voltage

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated