

# Reinforced-Isolation LLC Converter Reference Design for SiC and GaN Driving Supply



## Description


This small form factor power supply provides bias power to isolated silicon carbide (SiC) or gallium nitride (GaN) MOSFET gate drivers when extremely high  $dV/dt$  on the secondary side are expected, like in the case of wideband gap switches. The board accepts 24V input and supplies 12V at 200mA. The resonant inductor-inductor-capacitor (LLC) topology, combined to low primary to secondary winding capacitance, makes this converter an excellent choice for all low-noise and high CMTI (common mode transient immunity) applications, while significantly reducing common-mode current injection through the transformer. Even though this isolated LLC converter works in open-loop, the output voltage keeps tracking  $V_{IN}$  and has very low variation versus load current.

## Features

- Reinforced insulation
- Extreme low primary-secondary winding capacitance
- Regulated  $24V_{IN}$  to  $12V_{OUT}$
- Tested with  $30\mu F$  switched output capacitance (first activation of high-side GaN or SiC-FET)
- Resonant (secondary side) LLC topology
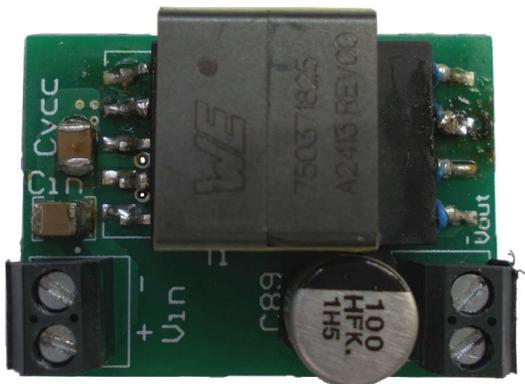
## Applications

- [Onboard charger](#)
- [AC charging \(pile\) station](#)
- [Central inverter](#)
- [Mobile robot motor control](#)



Top Photo



Bottom Photo

## 1 Test Prerequisites

### 1.1 Voltage and Current Requirements

**Table 1-1. Voltage and Current Requirements**

PARAMETER	SPECIFICATIONS
Input Voltage	24V
Output Voltage	12V
Maximum Output Current	0.2A
IC	UCC25800-Q1

### 1.2 Considerations

Unless otherwise indicated, all test were done with 24V input voltage and 0.2A output current adjusted with a sliding resistor.

### 1.3 Dimensions

The size of the two-layer board is 35mm × 26mm.

## 2 Testing and Results

### 2.1 Efficiency Graphs

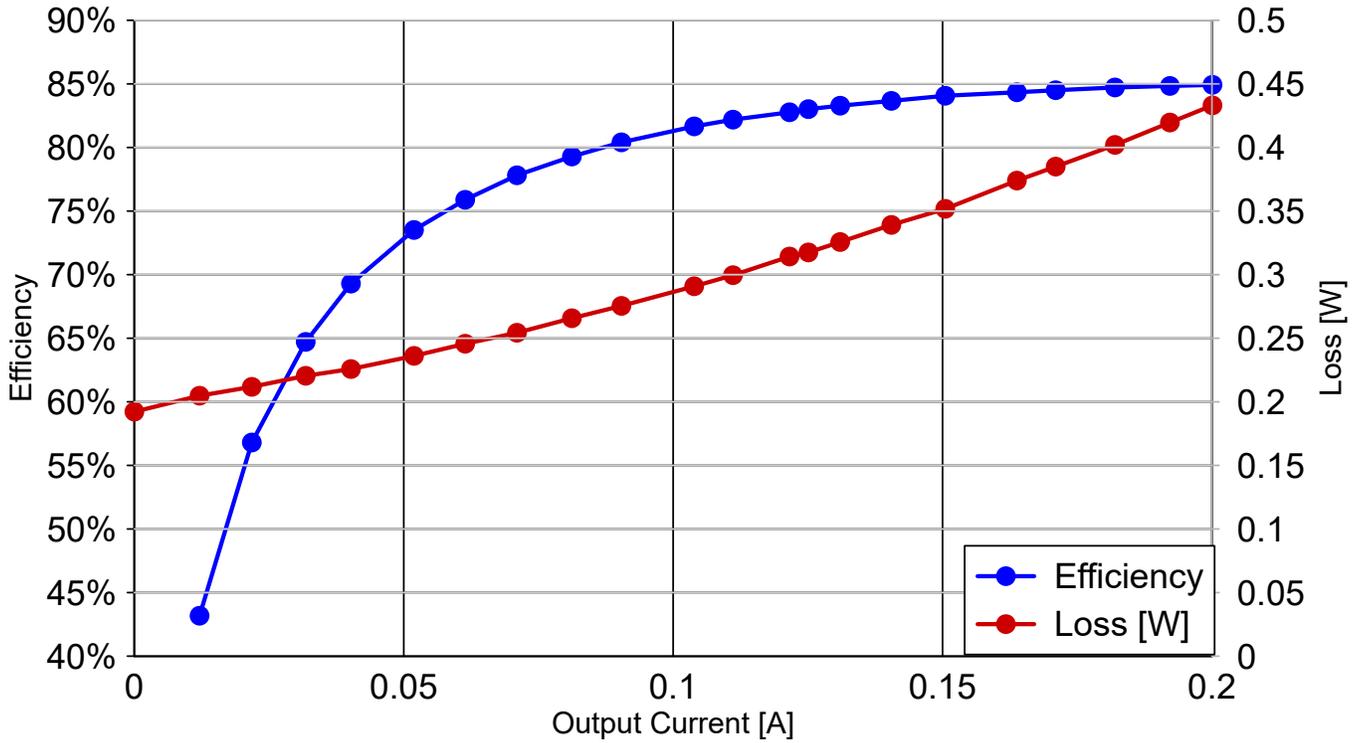


Figure 2-1. Efficiency and Loss Versus Output Current

### 2.2 Load Regulation

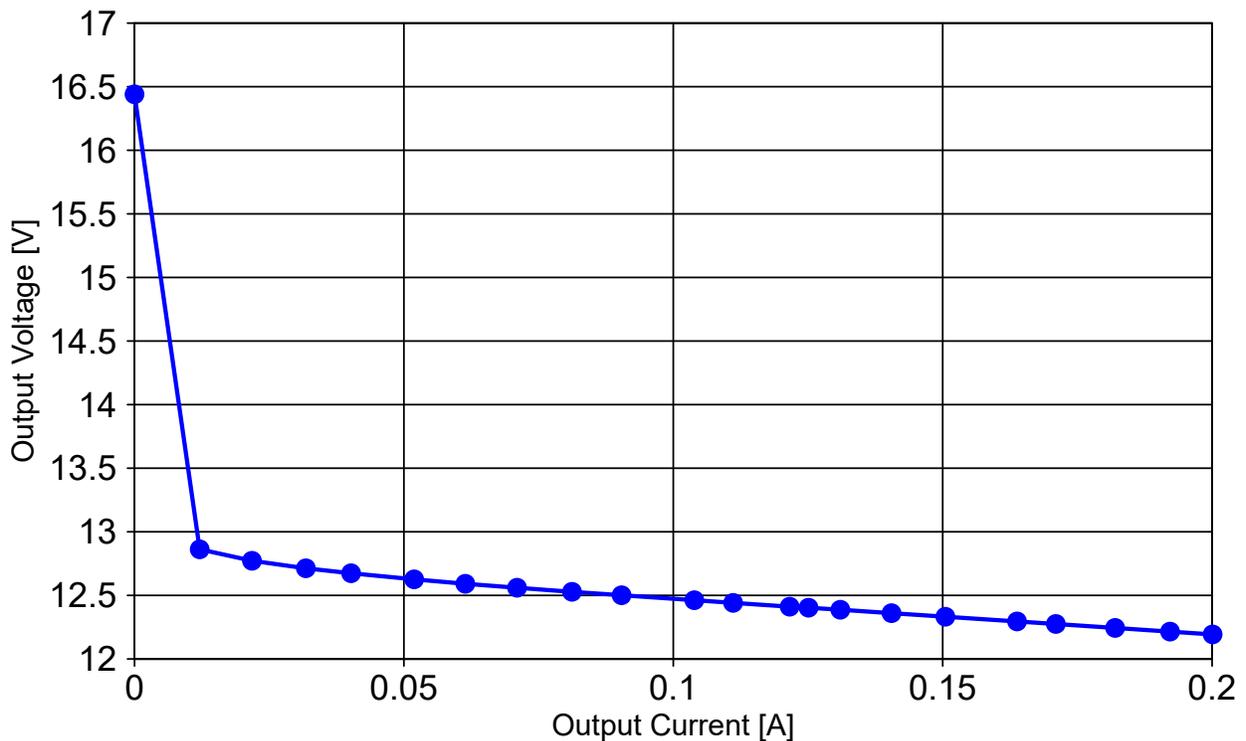


Figure 2-2. Output Voltage Versus Output Current

### 2.3 Dependency of the Output Voltage to Input Voltage

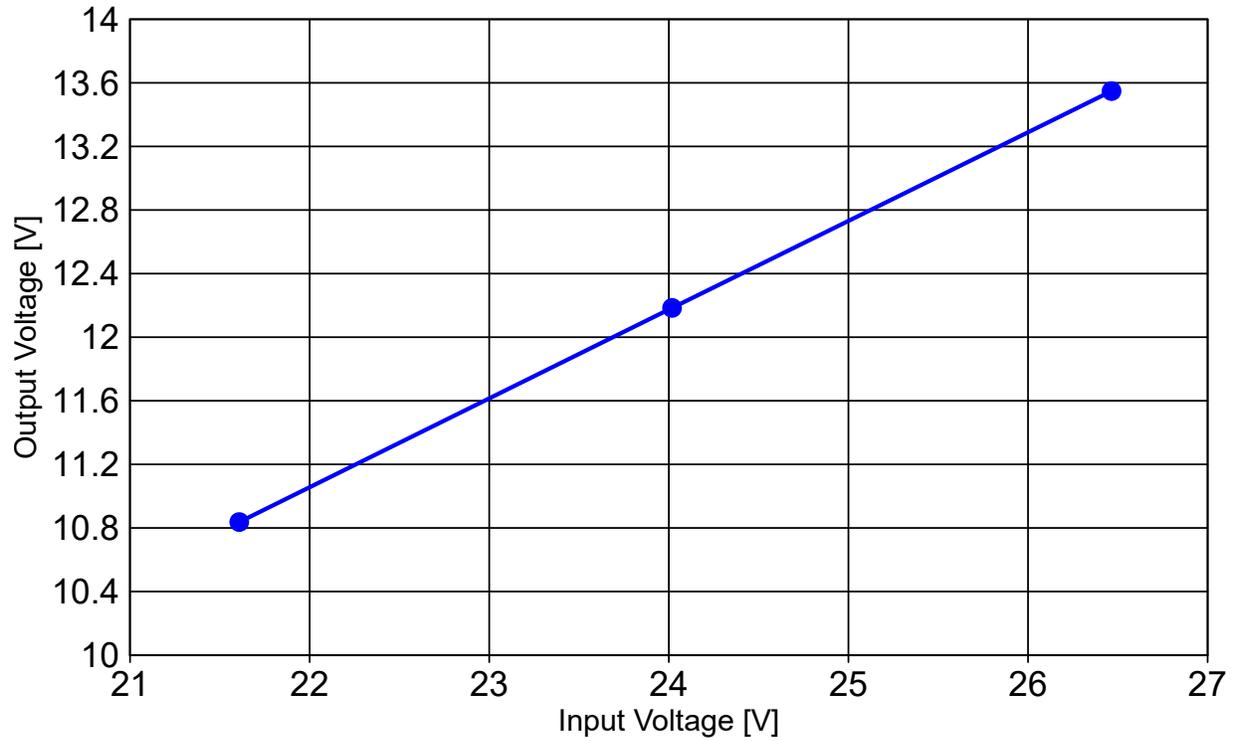


Figure 2-3. Output Voltage Versus Input Voltage

## 3 Waveforms

### 3.1 Switching

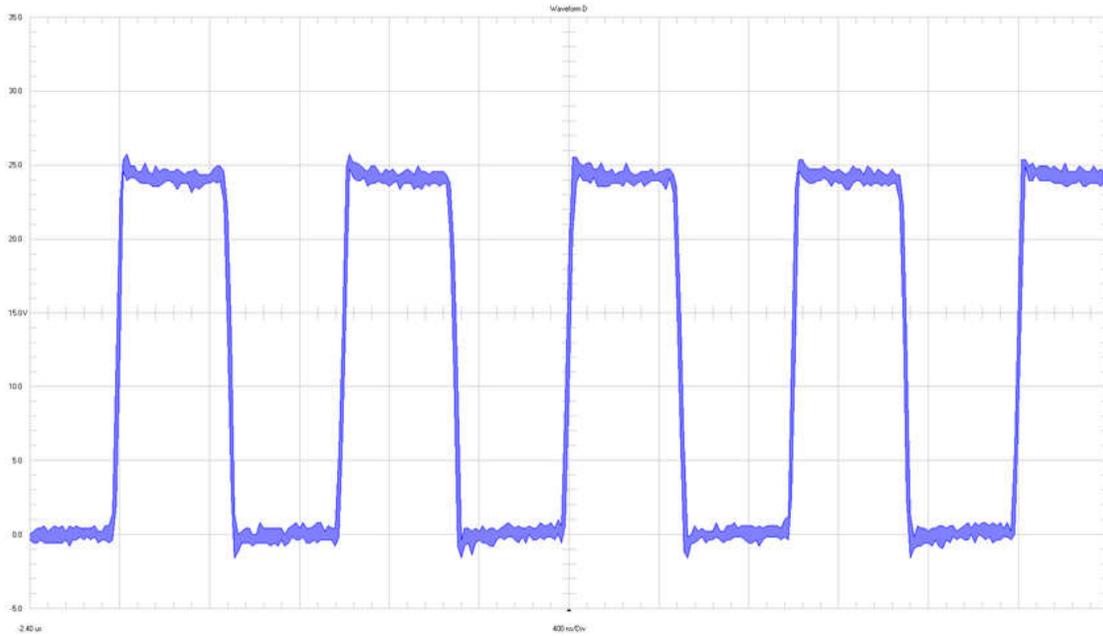


Figure 3-1. Switch-Node (Primary Side, 24V<sub>in</sub>, 0.2A<sub>out</sub>), 5V/div, 400nsec/div, Full Bandwidth



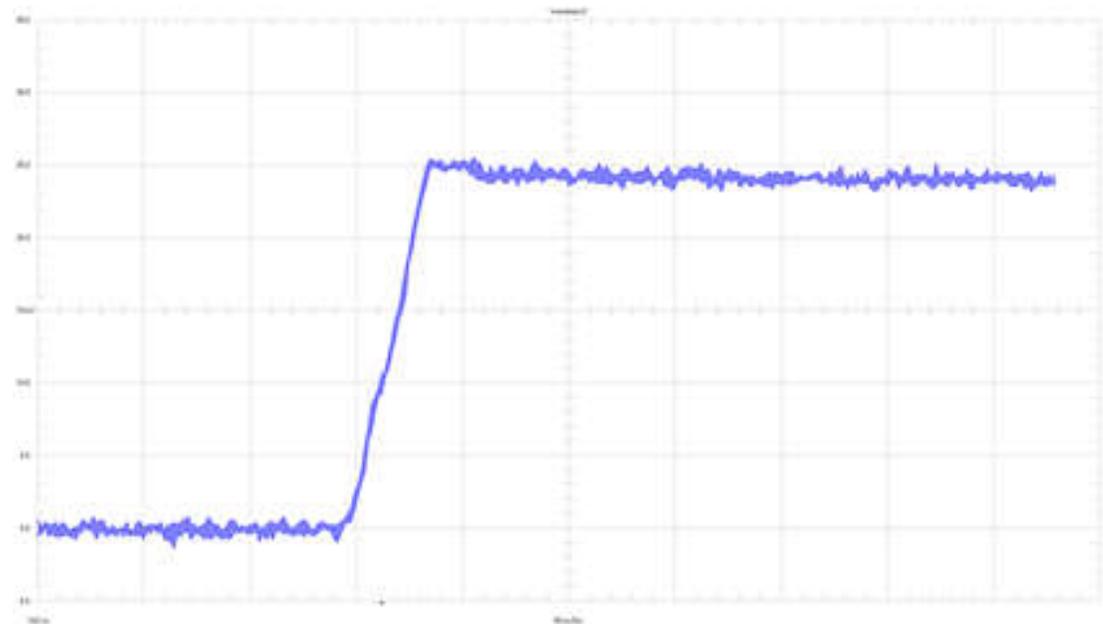


Figure 3-2. Switch-Node (Primary Side, 24V<sub>in</sub>, 0.2A<sub>out</sub>), 5V/div, 400nsec/div, Full Bandwidth

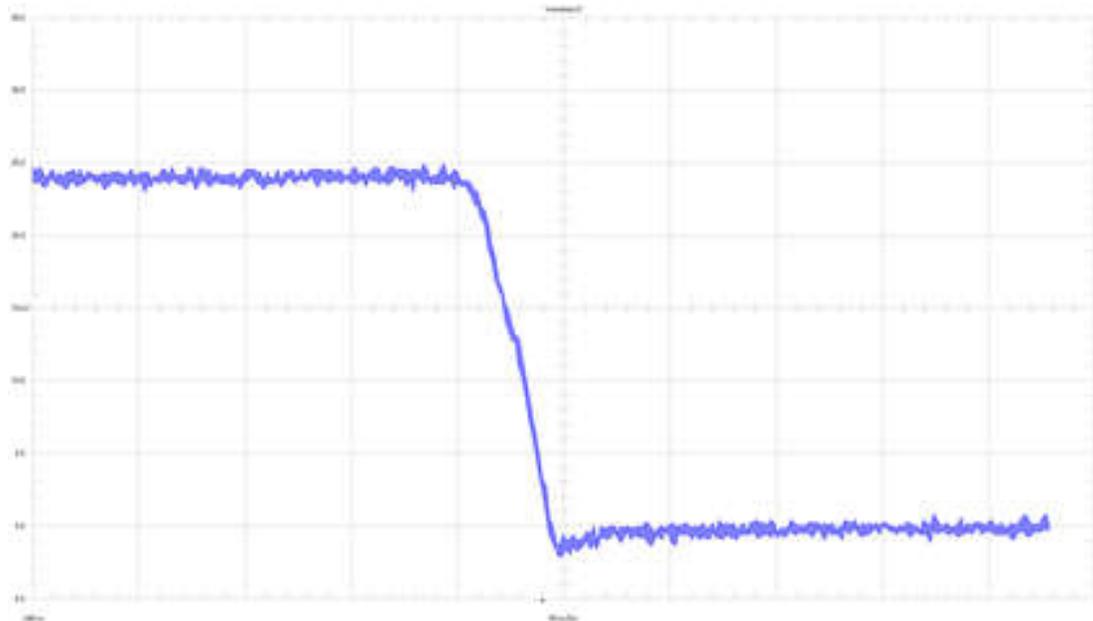


**Figure 3-3. Switch-Node Fall Time (Primary Side, 24V<sub>in</sub>, 0.2A<sub>out</sub>), 5V/div, 50nsec/div, Full Bandwidth**

### 3.2 Input Voltage Ripple

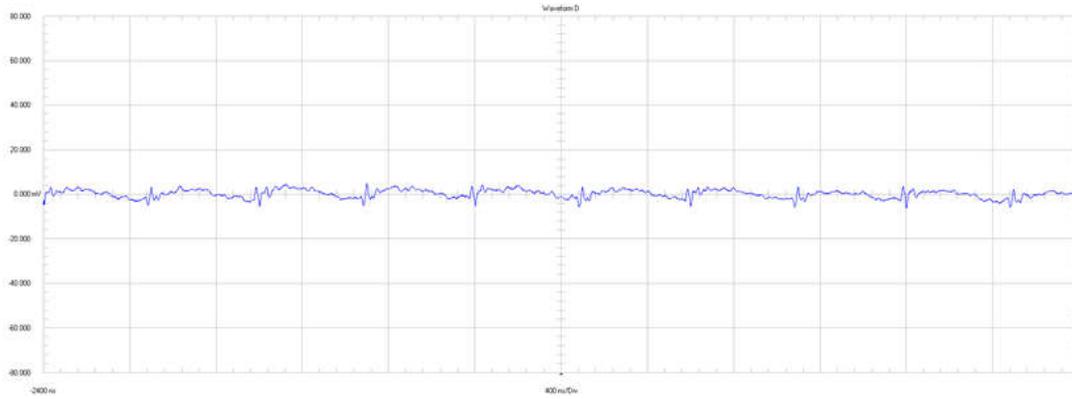

**Figure 3-4. Input Voltage Ripple (24V<sub>IN</sub>, 0.2A<sub>OUT</sub>) 20mV/div, 400ns/div, 20MHz Bandwidth**

### 3.3 Output Voltage Ripple

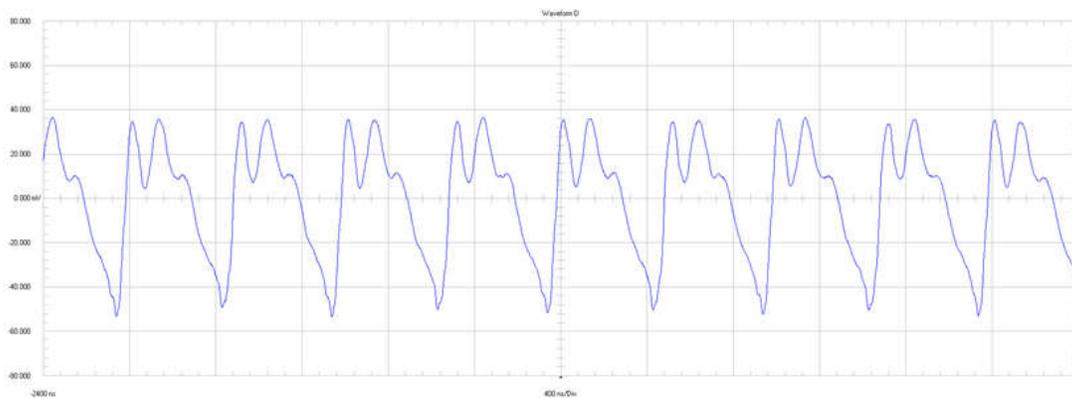

**Figure 3-5. 20mV/div, 400ns/div, 20MHz Bandwidth**

### 3.4 Load Transients

The electronic load switches between 0.1A and 0.2A with a frequency of 100Hz.

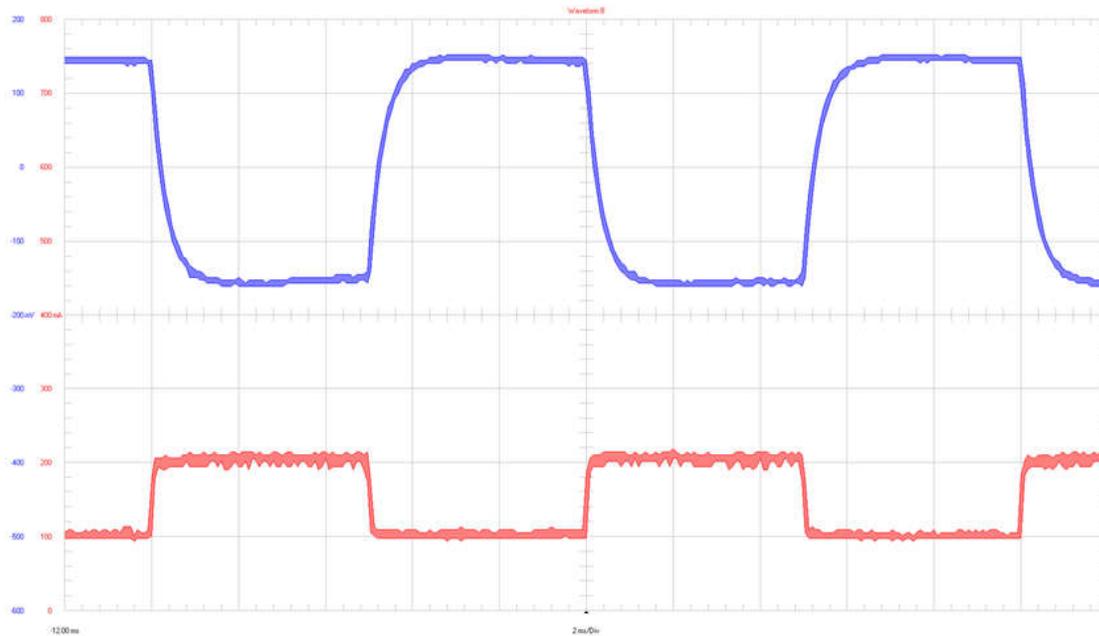


Figure 3-6. Load Transient ( $24V_{IN}$ )  $V_{out}$  (100mV/div),  $I_{out}$  (100mA/div), 2ms/div, 10kHz Bandwidth

### 3.5 Start-up Sequence

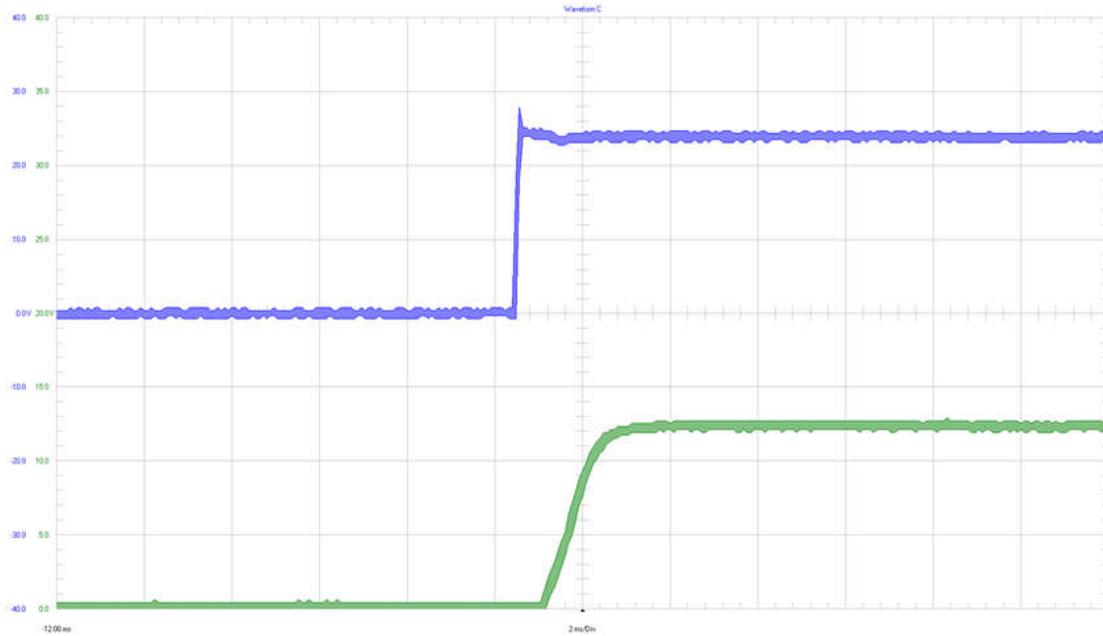


Figure 3-7. Start-up with Electronic Load ( $24V_{IN}$ ,  $0.2A_{OUT}$ )  $V_{in}$  (10V/div),  $V_{out}$  (5V/div), 2ms/div, 20MHz Bandwidth

### 3.6 Shutdown Sequence

The power supply was disconnected.

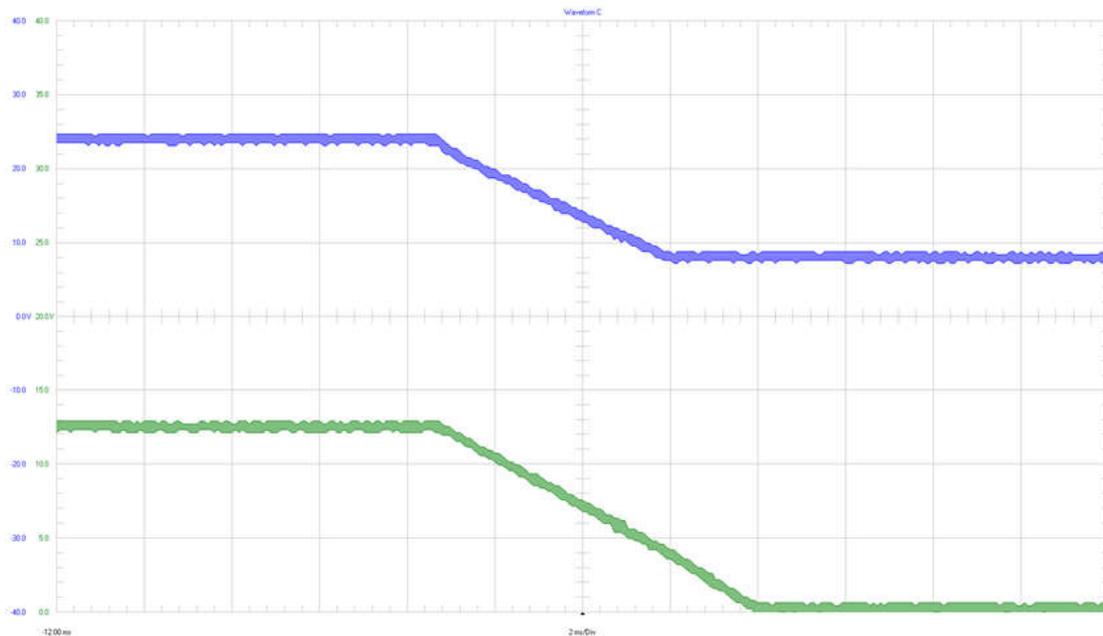


Figure 3-8. Shutdown with Electronic Load ( $24V_{IN}$ ,  $0.2A_{OUT}$ )  $V_{in}$  (10V/div),  $V_{out}$  (5V/div), 2ms/div, 20MHz Bandwidth

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265

Copyright © 2025, Texas Instruments Incorporated