

TI Designs

Parallel Load Switches for Higher Output Current & Reduced ON-Resistance Design Guide



TI Designs

TI Designs provide the foundation that you need including methodology, testing and design files to quickly evaluate and customize the system. TI Designs help *you* accelerate your time to market.

Design Resources

TIDA-00513	Tool Folder Containing Design Files
TIDA-00514	Design Folder
TPS22966	Product Folder
TPS22959	Product Folder
TPS22966EVM-007	Product Folder






[ASK Our E2E Experts](#)
[WEBENCH® Calculator Tools](#)

Design Features

- Increased Maximum Output Current
- Reduced Total ON-Resistance (R_{ON})
- Faster Output Rise Time
- Lower Power Dissipation
- Reduced Quick Output Discharge (QOD) Resistance

Featured Applications

   - Servers
- Enterprise Computing
- Industrial Systems
- High Current Voltage Rails



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

All trademarks are the property of their respective owners.

1 System Description

Users can expand the functionality of existing load switches by placing multiple channels in a parallel configuration. This TI Design demonstrates two examples of paralleling load switches.

1.1 Dual TPS22966

The first example uses both channels of the dual-channel TPS22966 for a total output current of 10 A.

 


Figure 1. Dual TPS22966 Block Diagram

1.1.1 Key Specifications

Table 1. Key Specifications

PARAMETER	SPECIFICATION	DETAILS
Maximum Continuous Output Current	10 A	See Section 4.1
Typical ON Resistance	8 mΩ	See Section 7.1
Rise Time at 5 V	262 us	See Section 7.2

1.2 Triple TPS22959

The second uses three TPS22959 in parallel for a total output current of 30 A.

 


Figure 2. Triple TPS22959 Block Diagram

1.2.1 Key Specifications

Table 2. Key Specifications

PARAMETER	SPECIFICATION	DETAILS
Maximum Continuous Output Current	30 A	See Section 4.1
Typical ON Resistance	1.5 mΩ	See Section 8.1
Rise Time at 5 V	2.4 ms	See Section 8.2

2 Block Diagram

The block diagrams for the two parallel load switch circuits are shown in [Figure 3](#) and [Figure 4](#).

 


Figure 3. TPS22966 Functional Block Diagram

 


Figure 4. TPS22959 Functional Block Diagram

3 Highlighted Products

3.1 TPS22966

- Integrated Dual-Channel Load Switch
- Input Voltage Range: 0.8 V to 5.5 V
- ON-Resistance
 - $R_{ON} = 16 \text{ m}\Omega$ at $V_{IN} = 5 \text{ V}$ ($V_{BIAS} = 5 \text{ V}$)
 - $R_{ON} = 16 \text{ m}\Omega$ at $V_{IN} = 3.6 \text{ V}$ ($V_{BIAS} = 5 \text{ V}$)
 - $R_{ON} = 16 \text{ m}\Omega$ at $V_{IN} = 1.8 \text{ V}$ ($V_{BIAS} = 5 \text{ V}$)
- 6-A Maximum Continuous Switch Current per Channel
- Low Control Input Threshold Enables Use of 1.2 V or Higher GPIO
- Configurable Rise Time
- Quick Output Discharge (QOD)
- SON 14-Pin Package With Thermal Pad

3.2 TPS22959

- Integrated Single Channel Load Switch
- V_{BIAS} Voltage Range: 2.5 V to 5.5 V
- V_{IN} Voltage Range: 0.8 V to 5.5 V
- Ultra Low R_{ON} Resistance
 - $R_{ON} = 4.4 \text{ m}\Omega$ at $V_{IN} = 5 \text{ V}$ ($V_{BIAS} = 5 \text{ V}$)
- 15 A Maximum Continuous Switch Current
- Low Quiescent Current (20 μA for $V_{BIAS} = 5 \text{ V}$)
- Low Shutdown Current (1 μA for $V_{BIAS} = 5 \text{ V}$)
- Low Control Input Threshold Enables Use of 1.2 V or Higher GPIO
- Quick Output Discharge (QOD)
- SON 8-Terminal Package with Thermal Pad

4 System Design Theory

This section will discuss how placing multiple load switch channels in parallel will effect functionality.

4.1 Increased Maximum Output Current

When multiple load switch channels are placed in the parallel, the maximum output current increases for two reasons:

1. The total ON Resistance is lower reducing the amount of $V = IR$ voltage drop.
2. The power dissipation will be more distributed leading to better thermal performance.

4.2 Reduced Total ON-Resistance (R_{ON})

Placing multiple load switch channels in parallel will reduce the typical and maximum ON Resistance proportionately to the number of channels in parallel. For example, two channels will half the ON Resistance, and three channels will result in one third. This event is critical in systems with tight tolerances on the voltage rails.

4.3 Faster Output Rise Time

When a single-load switch channel is turned on, the inrush current is limited by a controlled slew rate. When multiple channels are in parallel, the total inrush will increase, allowing for a faster output rise time.

4.4 Reduced Quick Output Discharge (QOD) Resistance

For load switches that connect a quick output discharge resistance to the output when disabled, the total QOD resistance will be reduced because multiple QOD resistors will be in parallel. This lower QOD resistance will reduce the output fall time, leading to a faster system power down sequencing.

5 Getting Started Hardware

This section will provide an overview of PCB hardware.

5.1 Dual TPS22966 Connections and Test Points

Table 3 shows a summary of the connections and test points for the dual TPS22966:

Table 3. Dual TPS22966 Connections and Test Points

CONNECTION	NAME	DESCRIPTION
J21	V_{IN}	DC Input to V_{IN}
J22	V_{OUT}	Load Connection for V_{OUT}
JP22	V_{BIAS} Power	Connects V_{BIAS} to V_{IN}
JP21	ON Control	Connects ON pin to V_{IN} or GND
TP21	V_{IN} Sense	Sense Connection to V_{IN}
TP26	V_{OUT} Sense	Sense Connection to V_{OUT}
TP24	V_{BIAS}	V_{BIAS} Connection
TP23	ON	Enable Connection
TP22, TP27, TP28, TP29	GND	Connection to Board Ground

5.2 Triple TPS22959 Connections and Test Points

Table 4 shows a summary of the connections and test points for the triple TPS22959:

Table 4. Triple TPS22959 Connections and Test Points

CONNECTION	NAME	DESCRIPTION
J31	V_{IN}	DC Input to V_{IN}
J32	V_{OUT}	Load Connection for V_{OUT}
JP31	V_{BIAS} Power	Connects V_{BIAS} to V_{IN}
JP32	ON Control	Connects ON pin to V_{IN} or GND
TP31	V_{IN} Sense	Sense Connection to V_{IN}
TP35	V_{OUT} Sense	Sense Connection to V_{OUT}
TP33	V_{BIAS}	V_{BIAS} Connection
TP34	ON	Enable Connection
TP32, TP36, TP37, TP38	GND	Connection to Board Ground

6 Test Setup

Figure 5 and Figure 6 show how to collect ON Resistance and turn on measurements for the dual TPS22966 circuit. A similar setup can be used for the triple TPS22959 circuit.

 


Figure 5. ON Resistance Test Setup

 


Figure 6. Turn On Test Setup

7 Dual TPS22966 Test Data

This section will cover the test data from the dual TPS22966 circuit.

7.1 ON Resistance vs. Load Current

Table 5 provides a summary of the ON Resistance measured at various loads:

Table 5. ON Resistance vs. Load Current

LOAD CURRENT	$V_{IN} = V_{BIAS} = 5\text{ V}$	$V_{IN} = V_{BIAS} = 3.3\text{ V}$
200 mA	7.8 mΩ	8.7 mΩ
1 A	7.8 mΩ	8.7 mΩ
5 A	7.9 mΩ	8.8 mΩ
10 A	8.6 mΩ	9.7 mΩ

7.2 Turn On Waveforms

 


Figure 7. Dual TPS22966 Turn On Waveform with $V_{IN} = V_{BIAS} = 3.3\text{ V}$

 


Figure 8. Dual TPS22966 Turn On Waveform with $V_{IN} = V_{BIAS} = 5\text{ V}$

8 Triple TPS22959 Test Data

This section will cover the test data from the triple TPS22959 circuit.

8.1 ON Resistance vs. Load Current

Table 6 provides a summary of the ON Resistance measured at various loads:

Table 6. ON Resistance vs. Load Current

LOAD CURRENT	$V_{IN} = V_{BIAS} = 5\text{ V}$	$V_{IN} = V_{BIAS} = 3.3\text{ V}$
200 mA	1.4 mΩ	1.4 mΩ
1 A	1.4 mΩ	1.4 mΩ
5 A	1.4 mΩ	1.4 mΩ
10 A	1.4 mΩ	1.4 mΩ
15 A	1.5 mΩ	1.5 mΩ
30 A	1.6 mΩ	1.7 mΩ

8.2 Turn On Waveforms

 


Figure 9. Triple TPS22959 Turn On Waveform with $V_{IN} = V_{BIAS} = 3.3\text{ V}$

 


Figure 10. Triple TPS22959 Turn On Waveform with $V_{IN} = V_{BIAS} = 5\text{ V}$

9 Design Files

9.1 Schematics

To download the Schematics, see the design files at [TIDA-00513](http://www.ti.com/design-files/TIDA-00513).

 


Figure 11. Dual TPS22966 Schematic

 


Figure 12. Triple TPS22959 Schematic

9.2 **Bill of Materials**

To download the bill of materials (BOM), see the design files at [TIDA-00513](#).

9.3 **Layout Recommendations**

For best performance, all traces should be as short as possible. To be most effective, the input and output capacitors should be placed close to the device to minimize the effects that parasitic trace inductances may have on normal operation. Using wide traces for V_{IN} , V_{OUT} , and GND helps minimize the parasitic electrical effects along with minimizing the case to ambient thermal impedance. The CT trace should be as short as possible to avoid parasitic capacitance.

9.4 **Layer Plots**

To download the layer plots, see the design files at [TIDA-00513](#).

9.5 **Altium Project**

To download the Altium project files, see the design files at [TIDA-00513](#).

9.6 **Layout Guidelines**

To download the Layout Guidelines, see the design files at [TIDA-00513](#).

9.7 **Gerber Files**

To download the Gerber files, see the design files at [TIDA-00513](#).

9.8 **Software Files**

To download the software files, see the design files at [TIDA-00513](#).

10 **References**

1. Texas Instruments Application Report, *Load Switch Thermal Considerations*, 2004 ([SLVUA74](#))

11 About the Author

ADAM HOOVER is a Systems Engineer at Texas Instruments, where he is responsible for developing solutions for the industrial segment. Adam earned his Bachelors of Science in Electronics Engineering Technology (EET) from Texas A&M University in College Station, TX.

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.