



LM5020-2 Constant Current Input Boost Converter for 2 LED Strings

TI reference design number: PMP10523 REV A

**Input: 230mA Constant Current
Output: 141 VDC @ 130mA**

DC – DC Test Results

Table of Contents

1	Test Specifications.....	3
2	Circuit Description.....	3
3	Board Photos	4
4	Efficiency	6
4.1	Efficiency Results	6
4.2	Efficiency Data.....	6
4.3	Constant Current Ballast and LED Data	6
5	Thermal	7
5.1	Thermal Image	7
6	Startup and Shut Down.....	8
6.1	Startup and Shut Down using Ballast and LEDs.....	8
7	Switch Voltage and Sense Voltage Ripple.....	8
8	Load Transient Response.....	9
9	Control Loop Frequency Response	10
9.1	Constant Current Ballast and LED Load.....	10

1 Test Specifications

V_{in}	85 VDC
I_{in}	230mA Constant Current
V_{out}	141 VDC
I_{out}	130mA


2 Circuit Description

PMP10523 is a constant current input boost converter for LEDs which utilizes the LM5020-2 controller. The switching frequency is set to 100 kHz for high efficiency at a nominal output power of 18.5W. The design features switch current limiting and input under-voltage lockout. Input voltage regulation from a constant current source provides constant output power to the load. For LEDs with relatively constant output voltage, the output current is proportional to the input current.


Operating from a constant current source into the negative input impedance of a dc-dc converter creates a phase inversion of 180 degrees. The LMV431 shunt regulator is added in series with the LM5020-2 internal error amplifier. The fixed dc gain of this non-inverting feedback allows the control loop response to be determined by the dominant pole of the input capacitor. The system is unconditionally stable for any value of input capacitance.

3 Board Photos

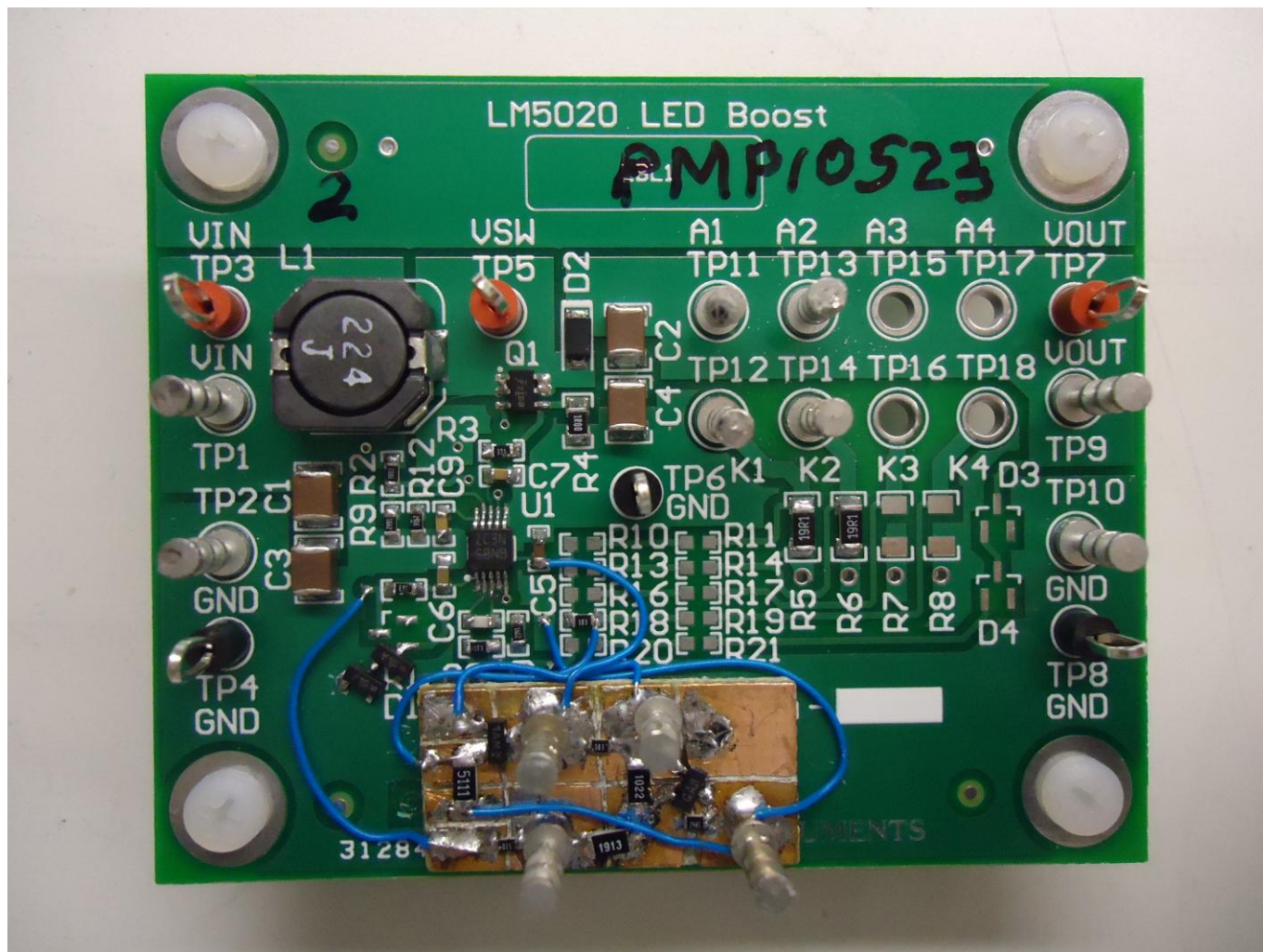The design is built on PMP10505 Rev A printed circuit board. This is a 2-layer PCB with 1 oz. copper. PCB dimensions are 2.75 x 2.2 inch.




PMP10523 Test Results

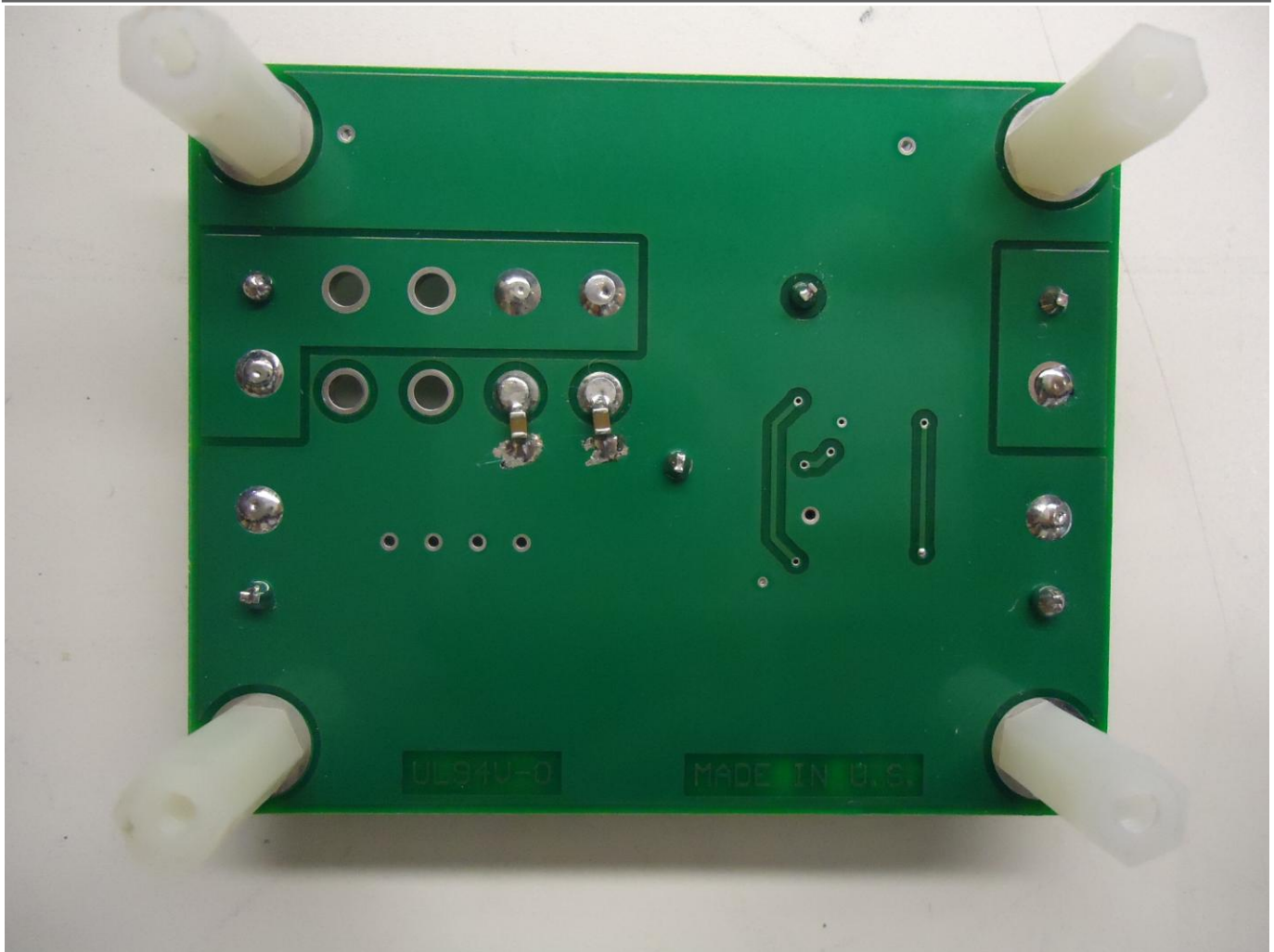

4 Efficiency

4.1 Efficiency Results

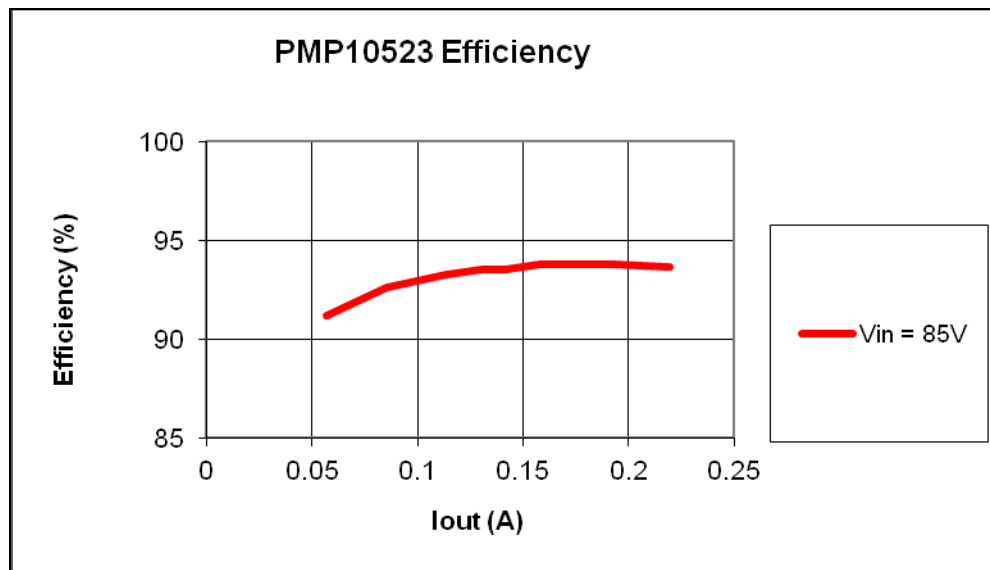

4.2 Efficiency Data

Test using 133V constant voltage load and 50Ω series resistor.

Vin (V)	Iin (A)	Vout (V)	Iout (A)	Pin (W)	Pout (W)	Pdis (W)	Efficiency (%)
84.84	0.1000	136.48	0.0567	8.48	7.74	0.75	91.212
84.91	0.1500	138.17	0.0854	12.74	11.80	0.94	92.645
84.99	0.2002	139.82	0.1135	17.01	15.87	1.15	93.268
85.05	0.2304	140.80	0.1302	19.60	18.33	1.26	93.553
85.09	0.2504	141.44	0.1409	21.31	19.93	1.38	93.534
85.15	0.2806	142.40	0.1573	23.89	22.40	1.49	93.749
85.19	0.3004	143.01	0.1678	25.59	24.00	1.59	93.771
85.29	0.3505	144.56	0.1940	29.89	28.04	1.85	93.813
85.40	0.4006	146.05	0.2193	34.21	32.03	2.18	93.621

4.3 Constant Current Ballast and LED Data


Test using ac ballast, bridge rectifier into 3.3μF 250V film capacitor at input and 2 strings of 24 LEDs.

Vac (V)	Iac (A)	Pac (W)	Power Factor	Vin (V)	Iin (A)	Vout (V)	Vs1 (V)	Vs2 (V)
120	0.19	23.3	0.999	89.2	0.2023	136.4	1.153	1.205

5 Thermal

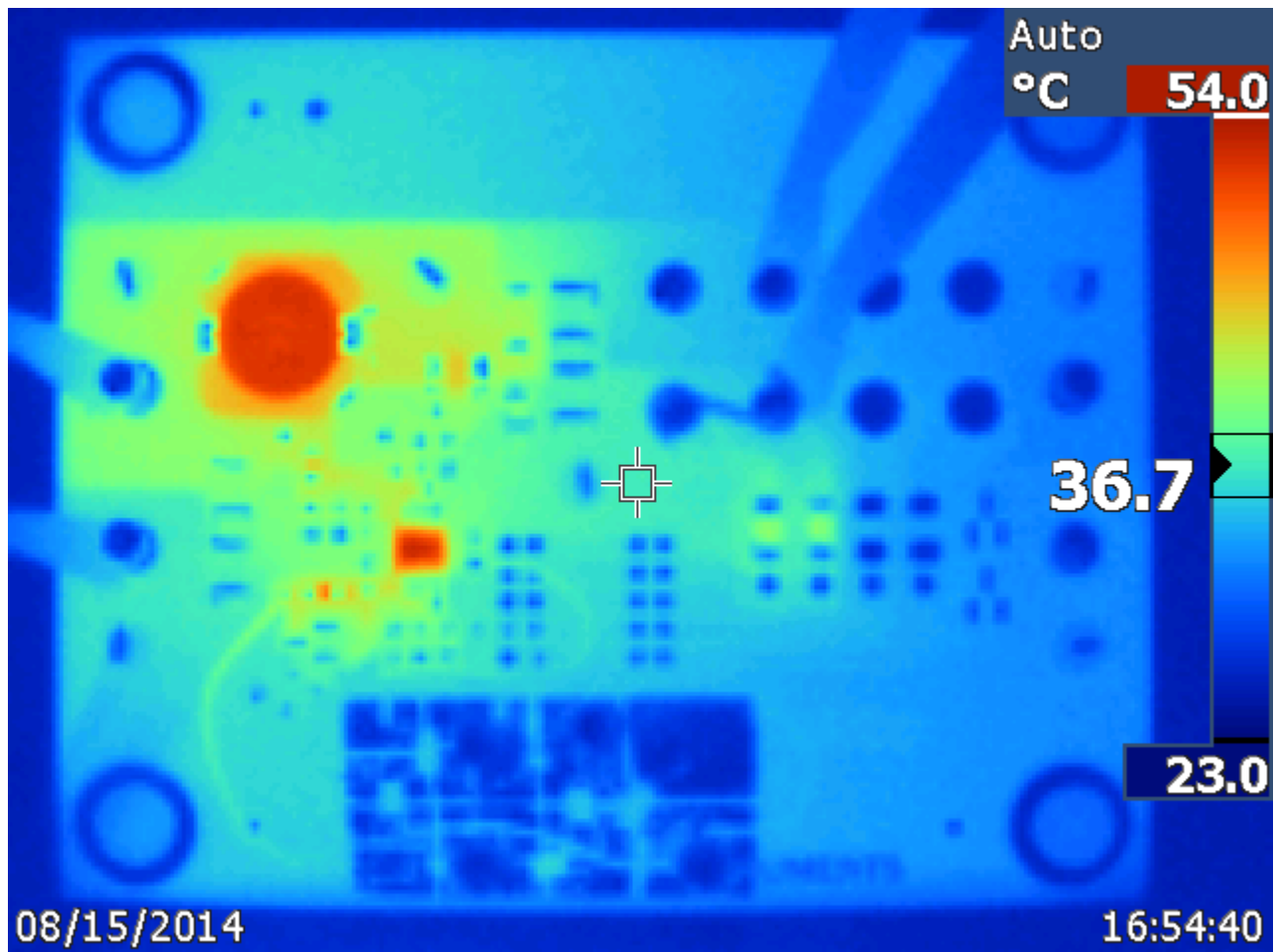
5.1 Thermal Image

85V input 230mA to 141V output 130mA load.




6 Startup and Shut Down

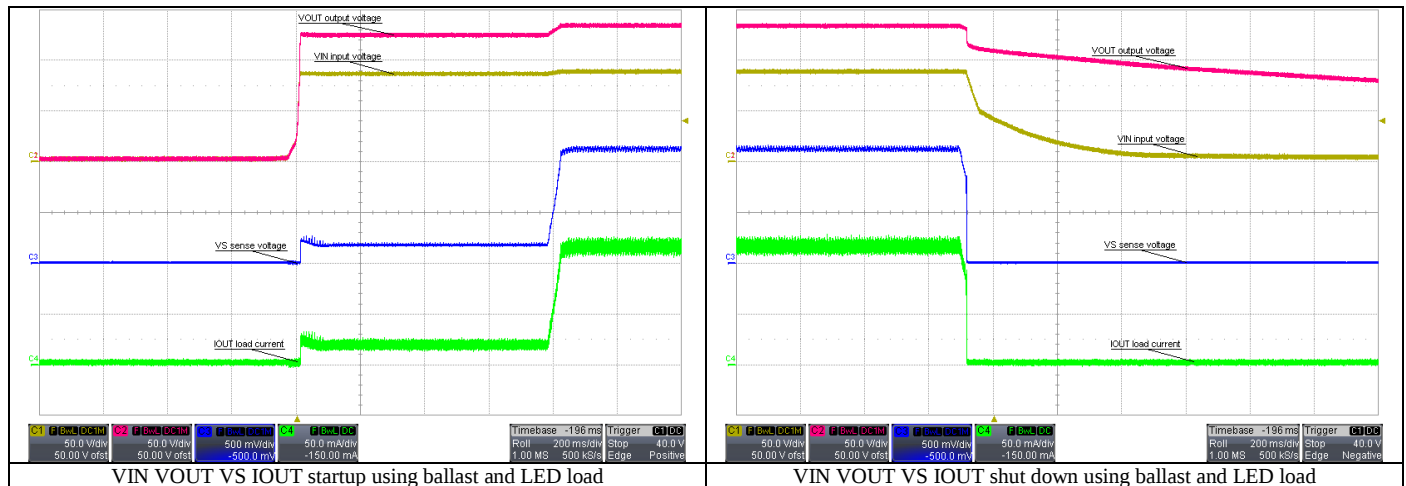6.1 Startup and Shut Down using Ballast and LEDs



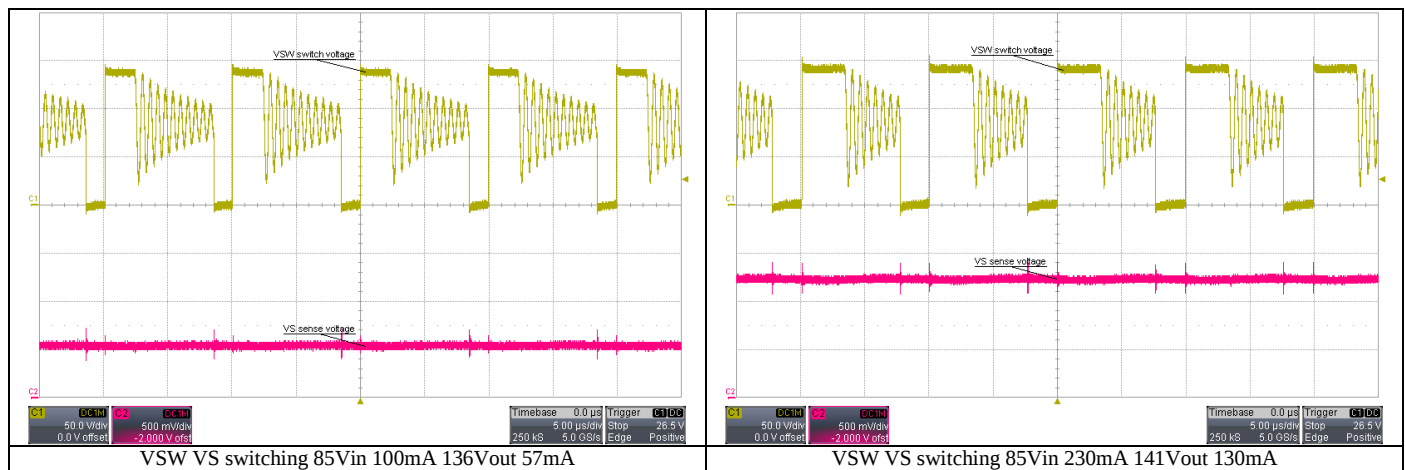
7 Switch Voltage and Sense Voltage Ripple



PMP10523 Test Results





8 Load Transient Response

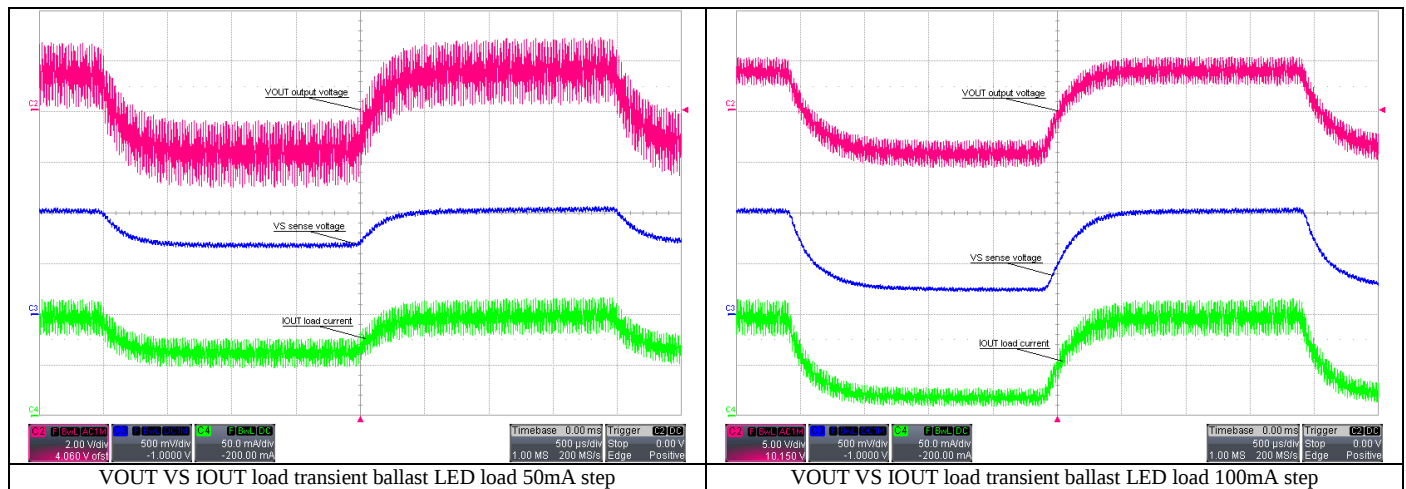

9 Control Loop Frequency Response

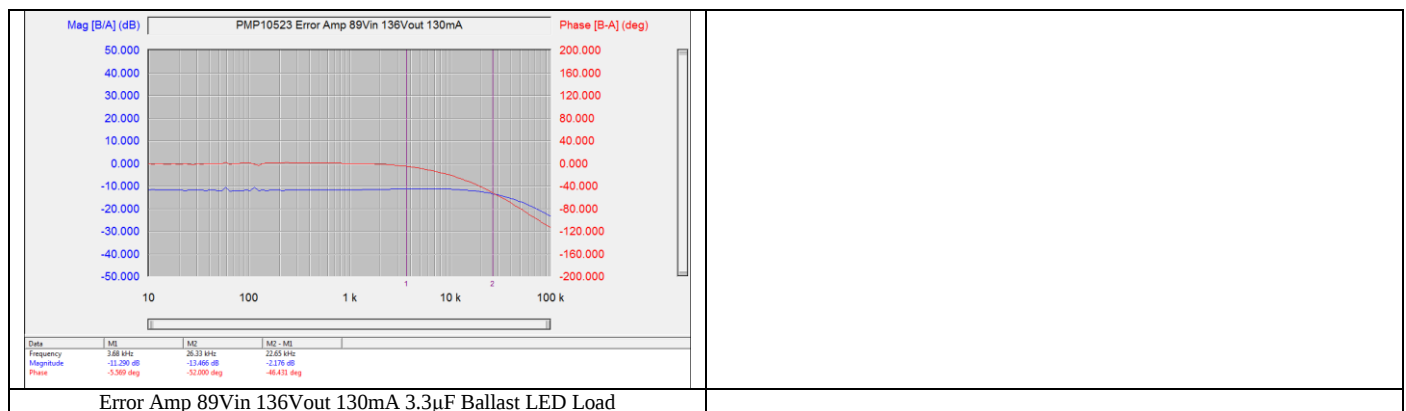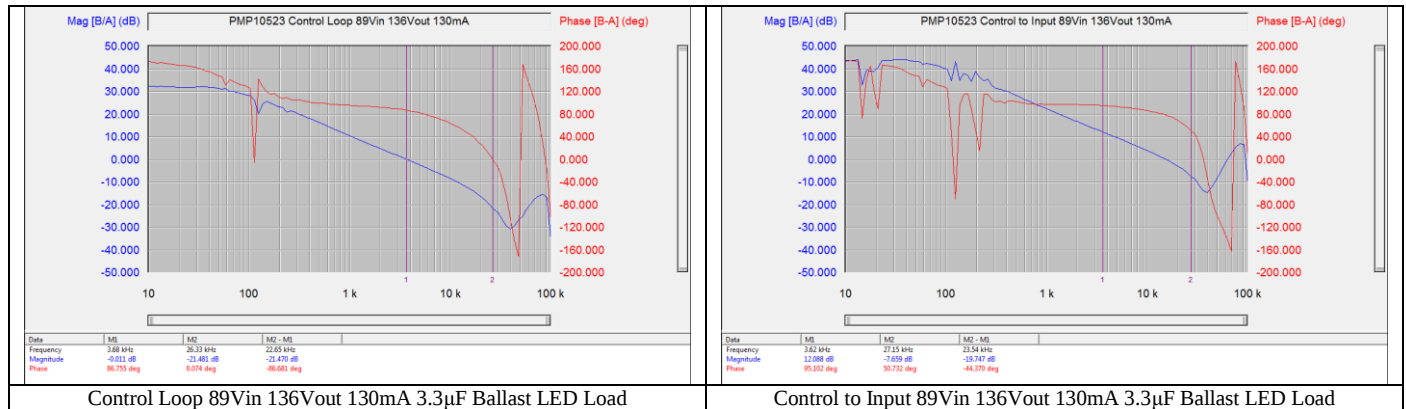9.1 Constant Current Ballast and LED Load

Test using ac ballast, bridge rectifier into 3.3 μ F 250V film capacitor at input and 2 strings of 24 LEDs.



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated