

Dual Bipolar Power-Supply Considerations for Amplifiers

Aaron Paxton, Mark Sellers



Dual bipolar power supplies are paired with amplifiers to widen their input and output ranges. Additionally, well-designed, dual power supplies like [TPS7A39](#) can also prevent power supply noise from adversely affecting conditioned signals. This note covers these benefits and other considerations regarding bipolar supplies.

Improved input range

The common-mode voltage range of amplifiers is very much dependent upon the amplifier topology. Traditional amplifiers have a common-mode range that is narrower than the supply voltage range. This presents a problem when the input nears one or both of the supply rails.

Violating the common-mode range will yield different types of distortion, or damage, depending on the type of op amp. Figure 1 shows the time domain representation of one type of distortion:

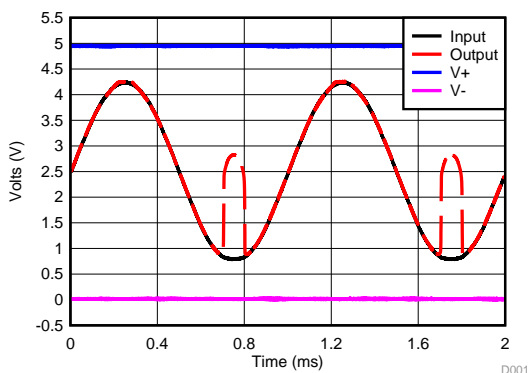


Figure 1. A signal violating the common-mode voltage range (G=1)

There are few methods to avoid such distortion. One involves attenuating the input signal and/or level-shifting it in such a way that it occurs within the specified common-mode range.

If this is not possible, the supply voltage rails can be extended in order to extend the common-mode range. For a single-supply op amp, this means extending the negative rail slightly below ground. In Figure 2, TPS7A39 is used to create supply rails of -0.25 V and +5.25 V to avoid non-linearity.

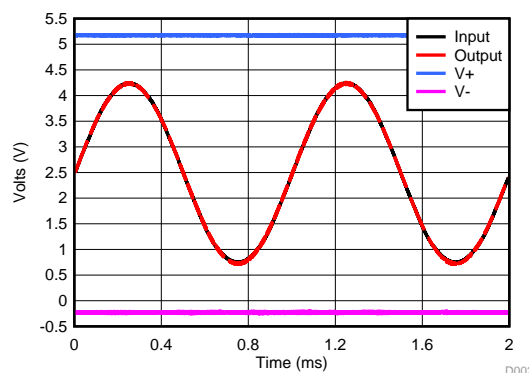


Figure 2. Widened supply rails to accommodate the signal (G=1)

It is worth noting that many newer amplifiers, such as [OPA388](#), offer rail-to-rail input ranges. These op amps have a common-mode range that extends slightly beyond the supply voltage rails and do not necessarily require adjusting the supply rails to avoid damage. However, the signal could still experience non-linearity as it nears the supply rails.

Improved output range

The output range of amplifiers is also limited by the supply voltage range. Even amplifiers with 'rail-to-rail' output ranges cannot truly swing from V+ to V- as the output approaches the positive or negative supply before being limited by the load-dependent voltage drop across the internal output transistors.

The distortion caused by saturation can be measured with a differential ADC in the circuit shown in Figure 3.

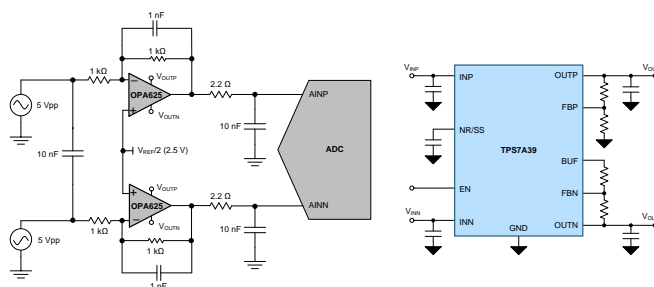


Figure 3. ADC differential input signal driver powered by TPS7A39

The drive circuitry generates the differential voltage of two 5 Vpp sinusoids with a frequency of 1 kHz and a phase offset of 180°. This is subsequently sampled by a differential ADC (ADS8900B) which should ideally encode a 10 Vpp, 1 kHz sinusoid. However, if the OPA625 devices are powered by 0 V and 5 V supply rails, their outputs will encounter some non-linearity when attempting to output 0 V or 5 V. The FFT of the signal is shown in Figure 4:

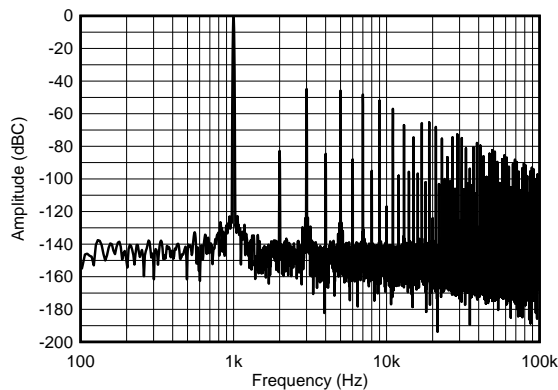


Figure 4. FFT of the ADC output when $V_{OUTN} = 0\text{ V}$ and $V_{OUTP} = 5\text{ V}$

This yields an SNR of 54.89 dB and a THD of -40.86 dB. The supply rails are then extended to -0.2V and 5.2V and the FFT is taken once again in Figure 5:

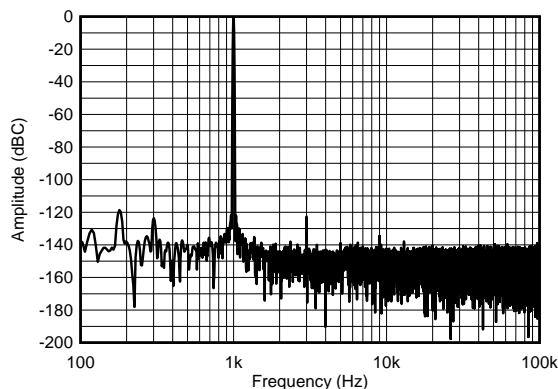


Figure 5. FFT of the ADC output when $V_{OUTN} = -0.2\text{ V}$ and $V_{OUTP} = 5.2\text{ V}$

The SNR improves to 102.535 dB while the THD is now -121.66 dB. By extending the supply rails slightly above 5V and slightly below 0V, the full scale range of the ADC can be realized and distortion avoided.

Improved PSRR

Perhaps the greatest advantage of a low-noise, dual power supply is the rejection of ripple voltage emanating from switched-mode power supplies. Unimpeded, switching noise has the potential to couple into the output signal.

Op amps reject a good deal of noise of their own accord. However, it should be noted that most PSRR plots are taken with the op amp in unity gain. PSRR plots like these do not take into account how a gain greater than 1 will affect overall PSRR. Plotting PSRR against several gain ratios yields different results as shown in Figure 6:

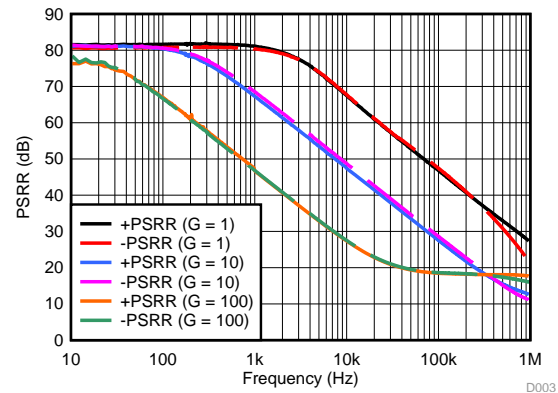


Figure 6. Op Amp PSRR vs frequency and gain

Since PSRR decreases with gain, it is necessary to preemptively filter power supply noise to prevent its coupling onto the output. Using a low-noise LDO like TPS7A39 is an effective way to ensure the supply rails are free of switching noise. By creating the supply rails with TPS7A39, we measure PSRR once again:

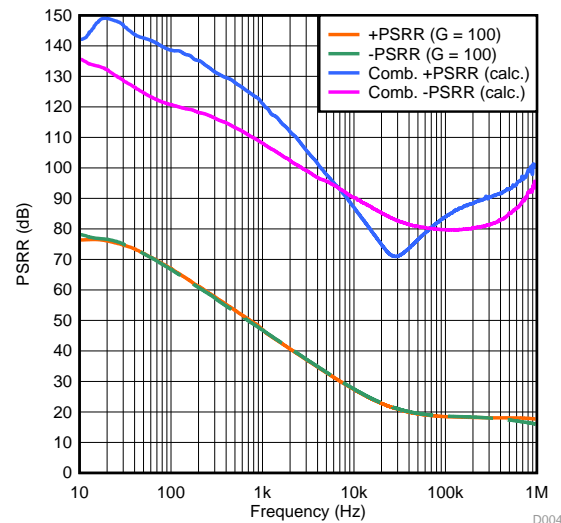


Figure 7. Op Amp & TPS7A39 PSRR vs frequency

As shown, PSRR is improved greatly with the implementation of TPS7A39. This is especially true at higher frequencies (> 500 kHz) where switching noise is more likely to occur.

In conclusion, using a low-noise dual bipolar power supply is safe bet to ensure minimal distortion and optimal signal integrity.

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated