



## **LM5021-1 Dual Flyback Converter**

**TI reference design number: PMP7917 Rev A**

**Input: 40V – 60V**

**Outputs: 6V @ 4.33A, 4V @ 3.5A**

**DC – DC Test Results**

---

## Table of Contents

1	Circuit Description .....	3
2	Photos .....	3
3	Efficiency and Regulation .....	4
3.1	Efficiency Data at 50V Input .....	4
3.1	Regulation Data at 50V Input .....	4
4	Power Up .....	5
4.1	Power Up at 50V Input – No Load .....	5
4.2	Power Up at 50V Input – Full Load .....	5
5	Switching Voltages .....	6
5.1	50V Input – Full Load .....	6
5.2	50V Input – Full Load .....	6
6	Ripple Voltages .....	7
6.1	50V Input – 6V Output – 2.17A Load .....	7
6.2	50V Input – 6V Output – 4.33A Load .....	7
6.3	50V Input – 4V Output – 1.75A Load .....	8
6.4	50V Input – 4V Output – 3.5A Load .....	8
7	Transient Response .....	9
7.1	50V Input – 6V Output – 2.17A Load Step .....	9
7.2	50V Input – 4V Output – 1.75A Load Step .....	9
8	Frequency Response .....	10
8.1	50V Input – No Load .....	10
8.2	50V Input – Full Load .....	10



## 1 Circuit Description

PMP7917 is a dual output flyback converter capable of 40W output power. This design uses the LM5021-1 current-mode PWM controller. The operating input voltage range is 40V to 60. The outputs are 6V at 4.33A and 4V at 3.5A. Self-driven synchronous operation is employed for the secondary rectifiers, resulting in good cross regulation.

All tests were performed at room temperature on an open bench.
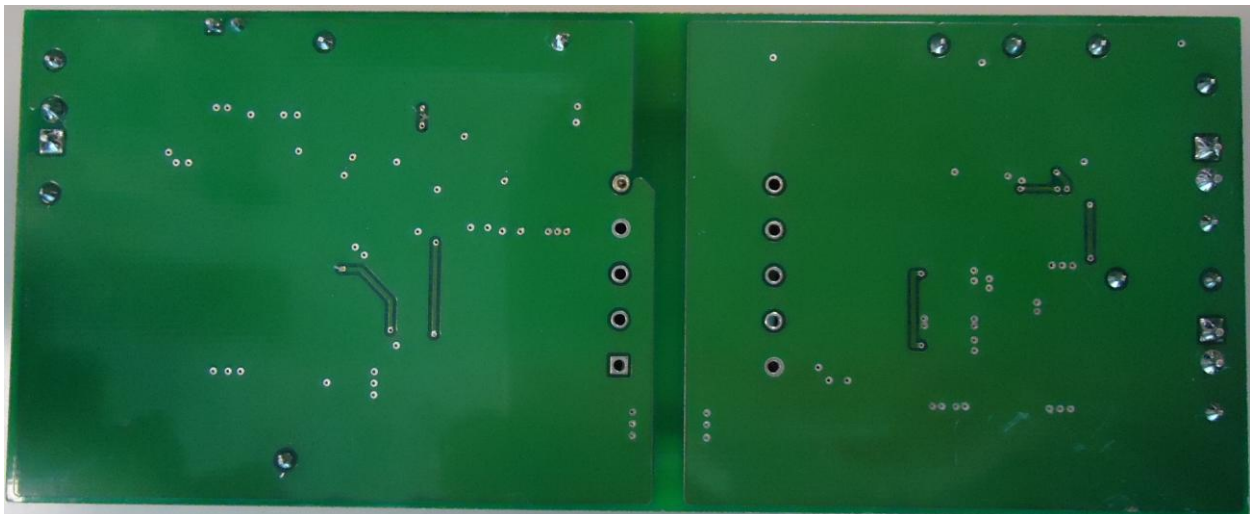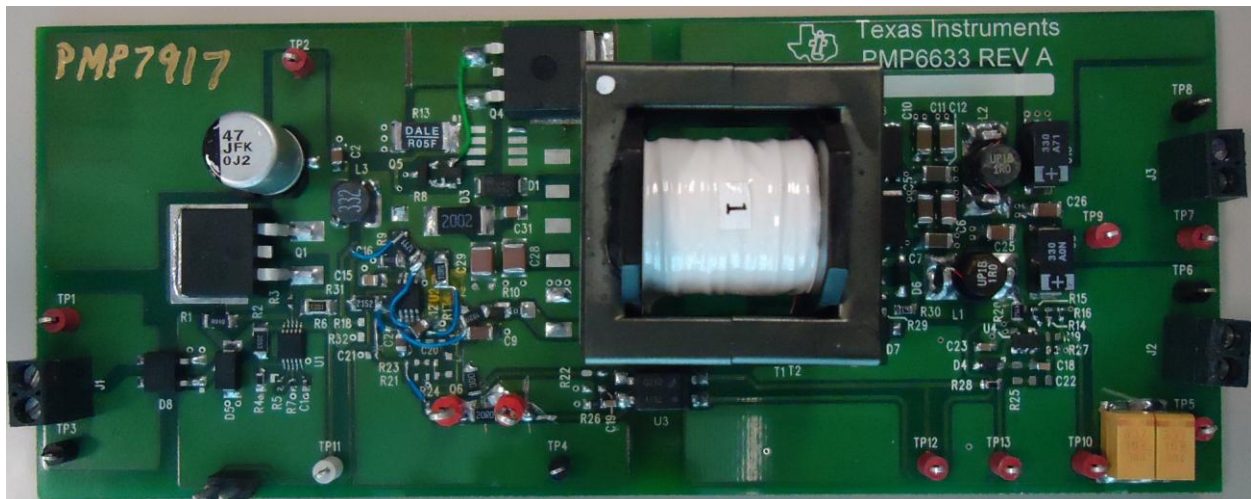
## 2 Photos

The circuit was built on PMP6633 Rev A printed circuit board.



### 3 Efficiency and Regulation

#### 3.1 Efficiency Data at 50V Input



Vin (V)	Iin (A)	6Vout (V)	6V Iout (A)	4Vout (V)	4V Iout (A)	Pout (W)	Efficiency (%)
49.342	0.5021	6.0797	2.17	4.0945	1.75	20.36	82.18
49.176	0.9527	6.0554	4.33	4.0735	3.50	40.48	86.40

#### 3.1 Regulation Data at 50V Input



6V Iout (A)	4V Iout (A)	6Vout (V)	4Vout (V)
0	0	6.1014	4.1145
2.17	0	6.0771	4.2180
4.33	0	6.0515	4.3272
0	1.75	6.1024	3.9939
2.17	1.75	6.0767	4.0954
4.33	1.75	6.0517	4.2028
0	3.50	6.1018	3.8687
2.17	3.50	6.0765	3.9711
4.33	3.50	6.0507	4.0767

## 4 Power Up

### 4.1 Power Up at 50V Input – No Load

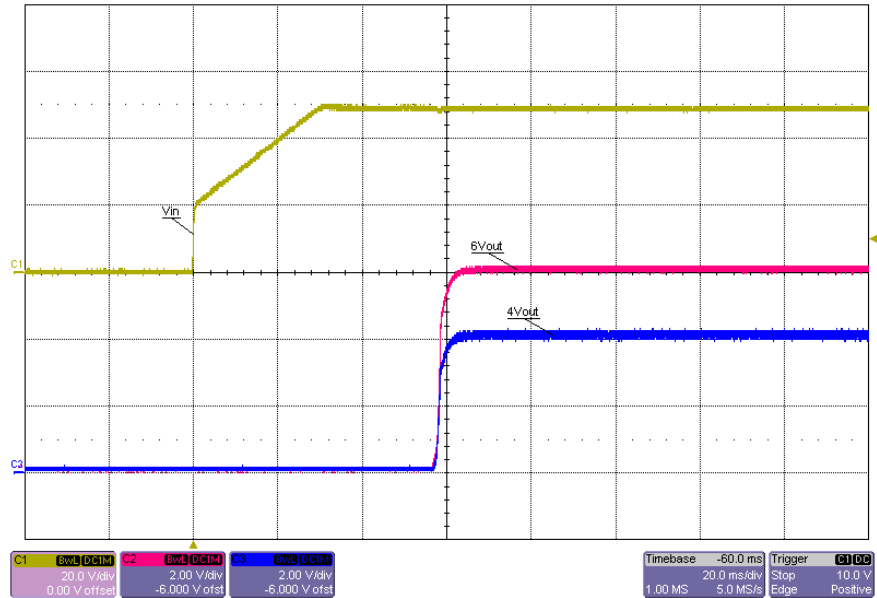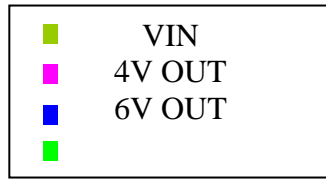

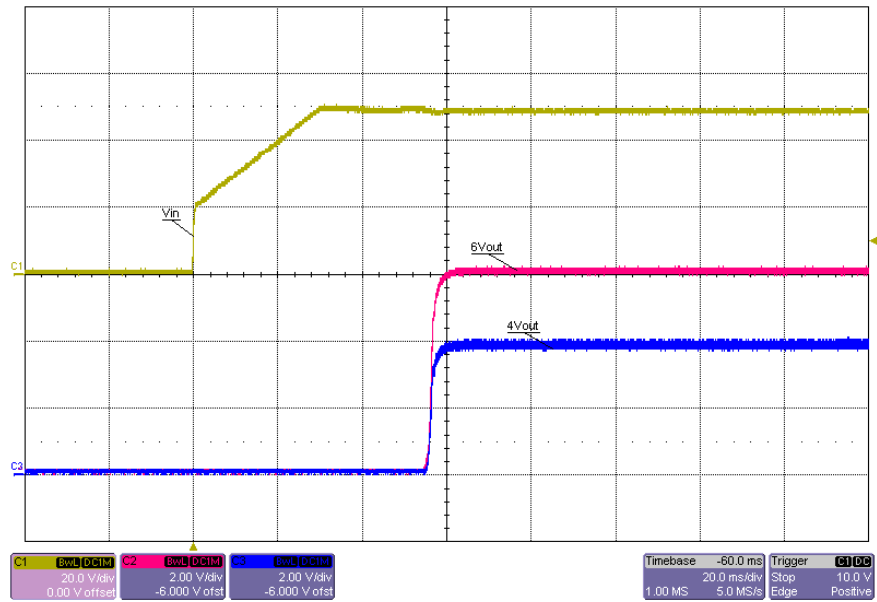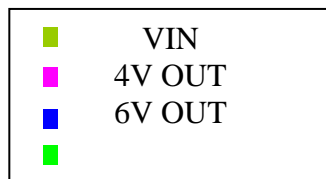
### 4.2 Power Up at 50V Input – Full Load




## 5 Switching Voltages

### 5.1 50V Input – Full Load

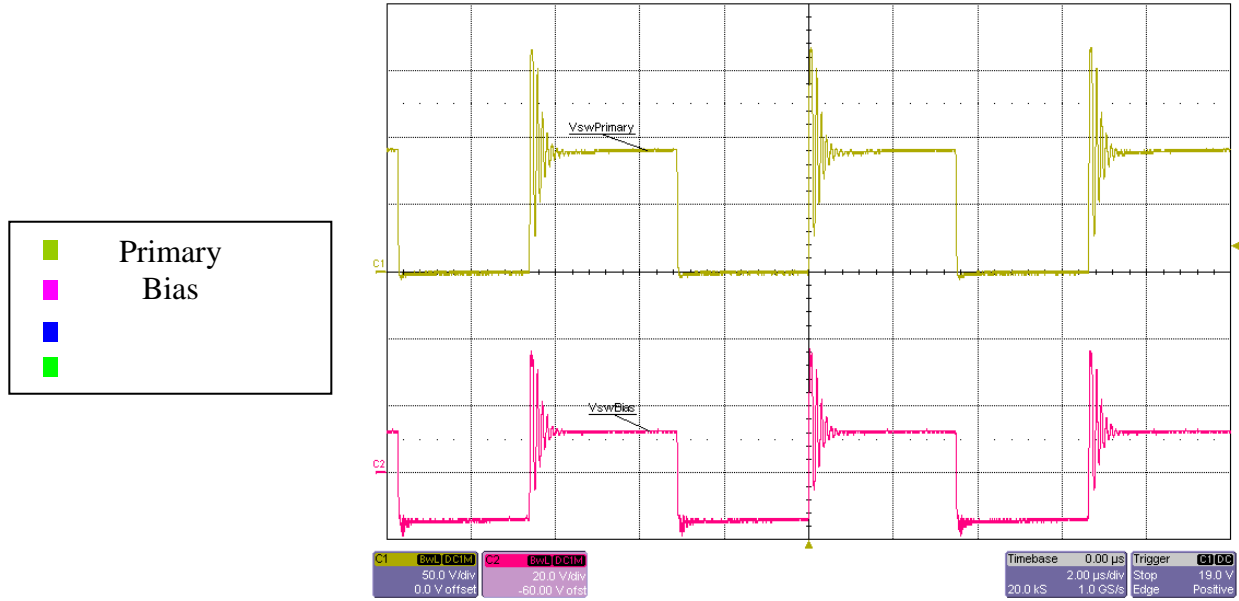


### 5.2 50V Input – Full Load

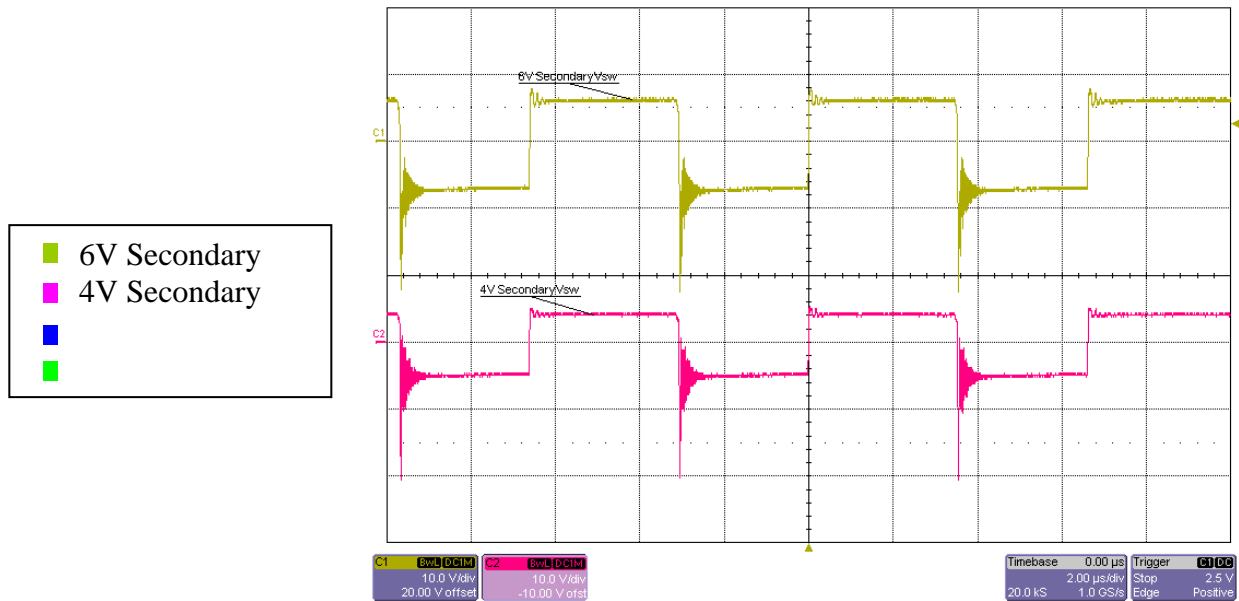


## 6 Ripple Voltages


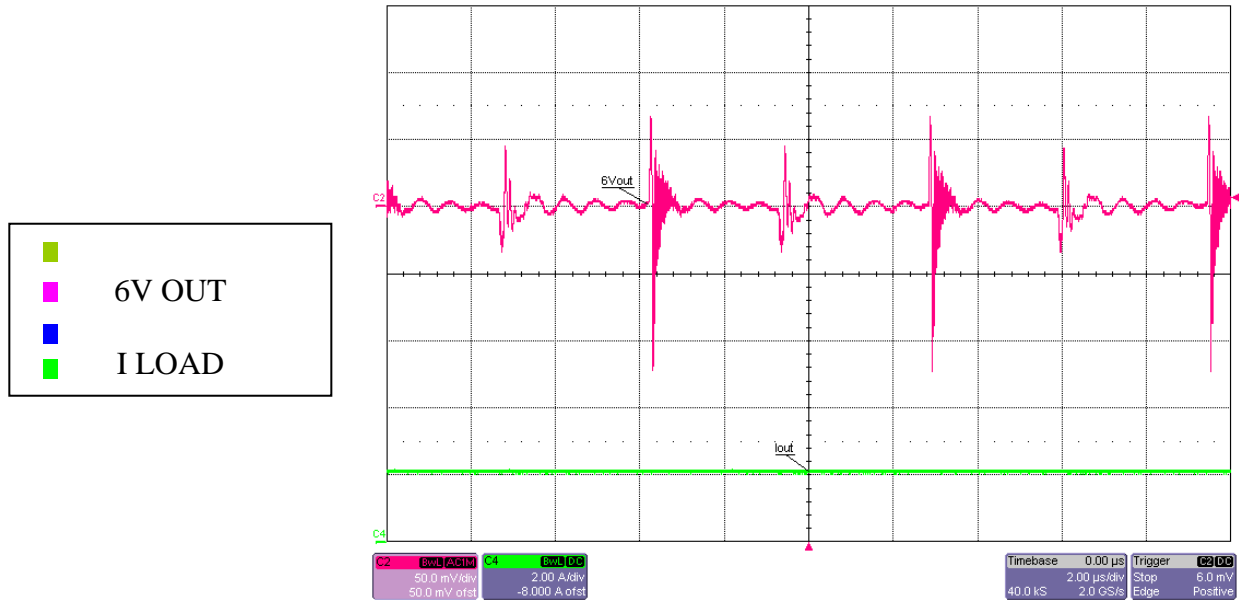
### 6.1 50V Input – 6V Output – 2.17A Load




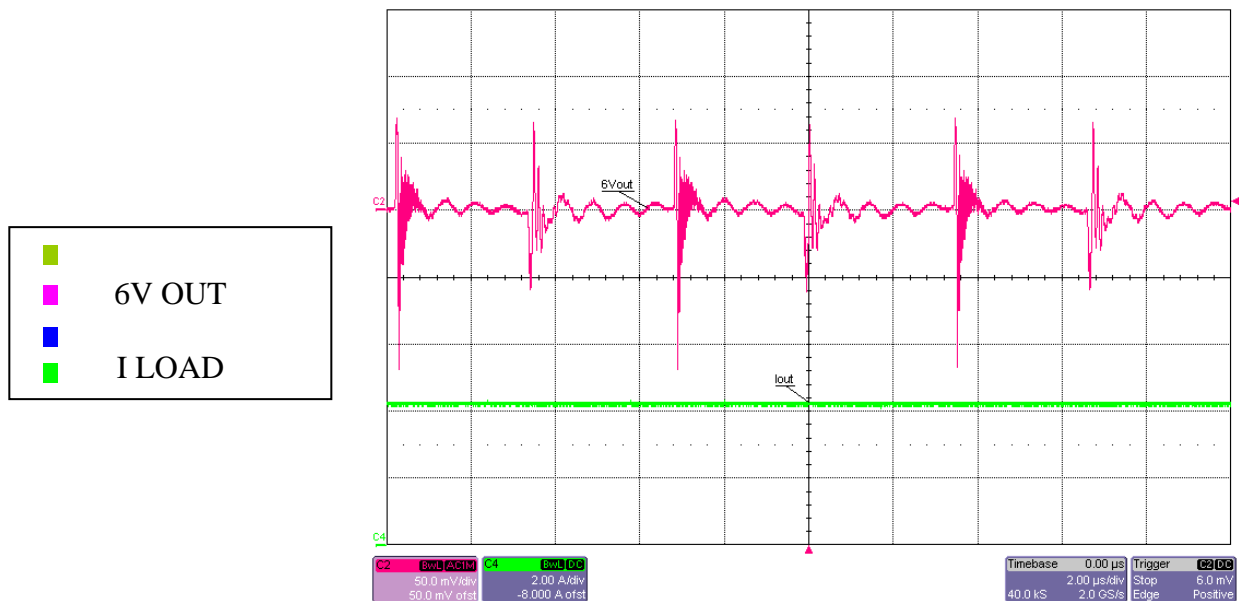
### 6.2 50V Input – 6V Output – 4.33A Load


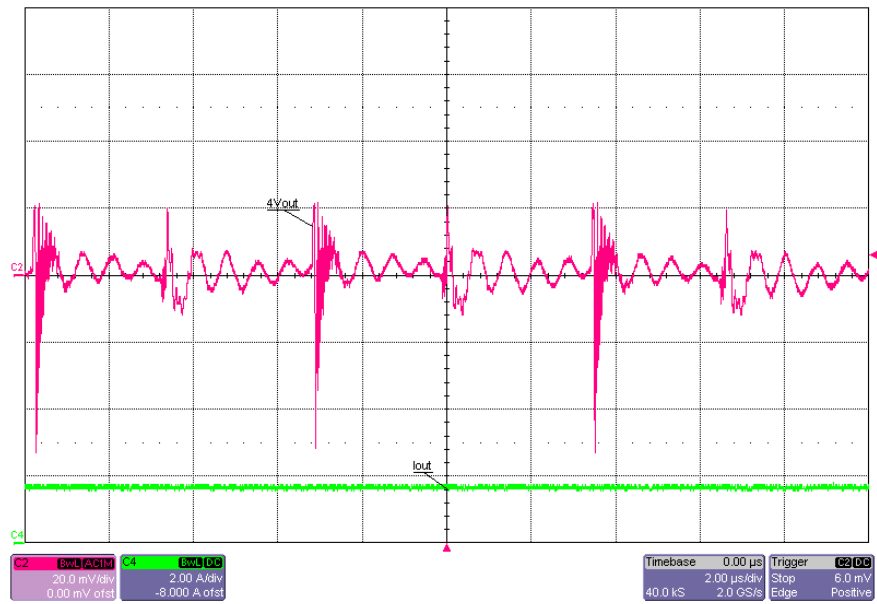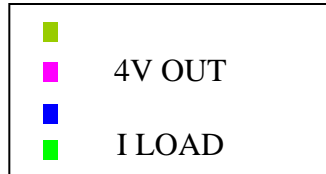
## 6.3 50V Input – 4V Output – 1.75A Load




## 6.4 50V Input – 4V Output – 3.5A Load

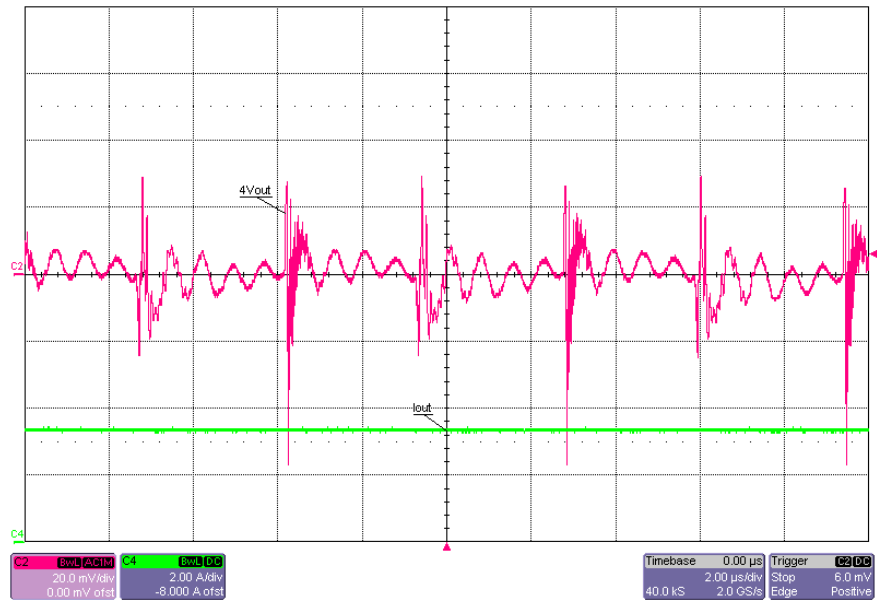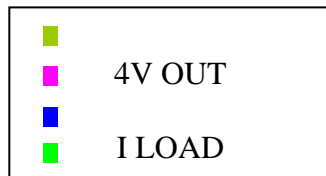




## 7 Transient Response
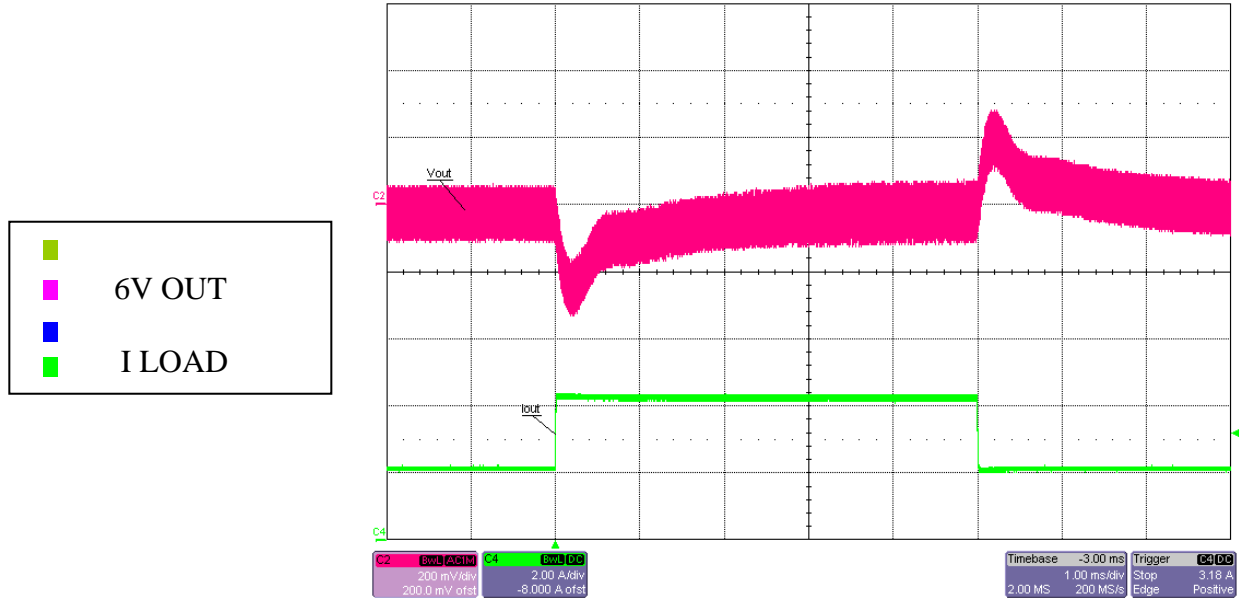
### 7.1 50V Input – 6V Output – 2.17A Load Step



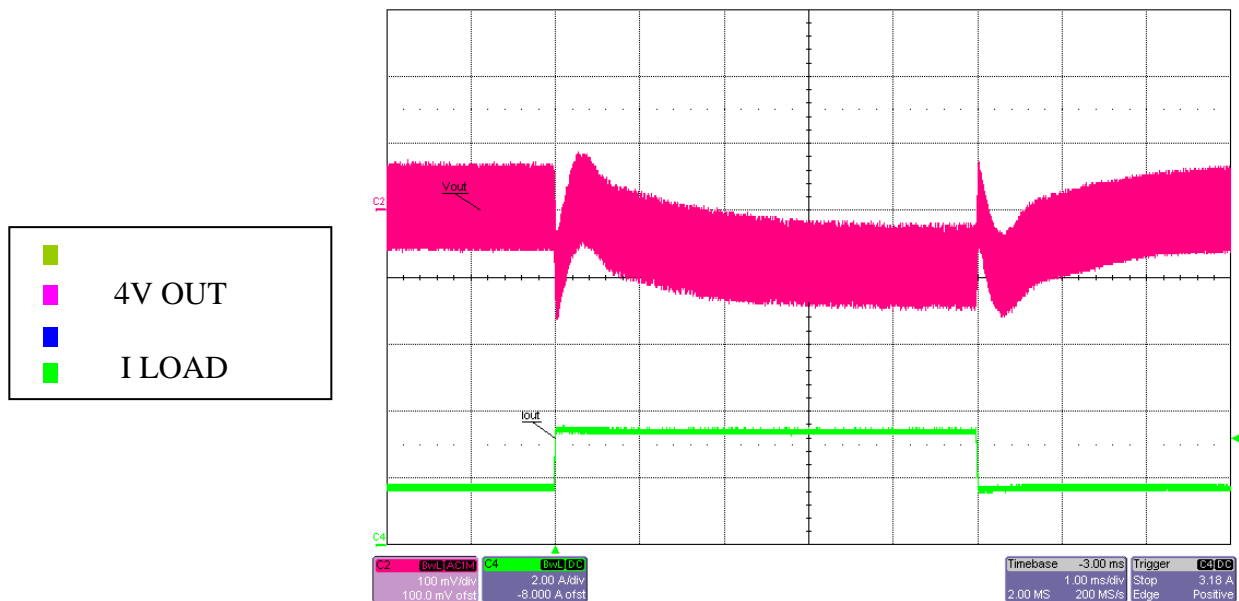
### 7.2 50V Input – 4V Output – 1.75A Load Step




## 8 Frequency Response

### 8.1 50V Input – No Load

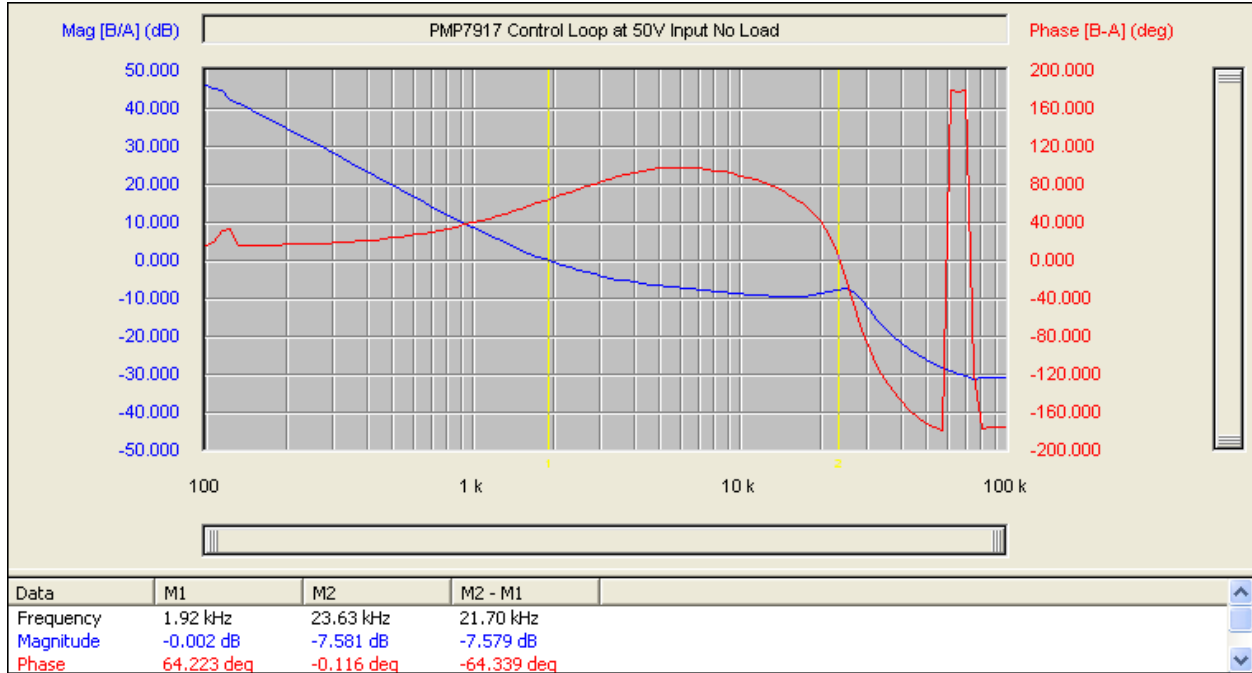

### 8.2 50V Input – Full Load

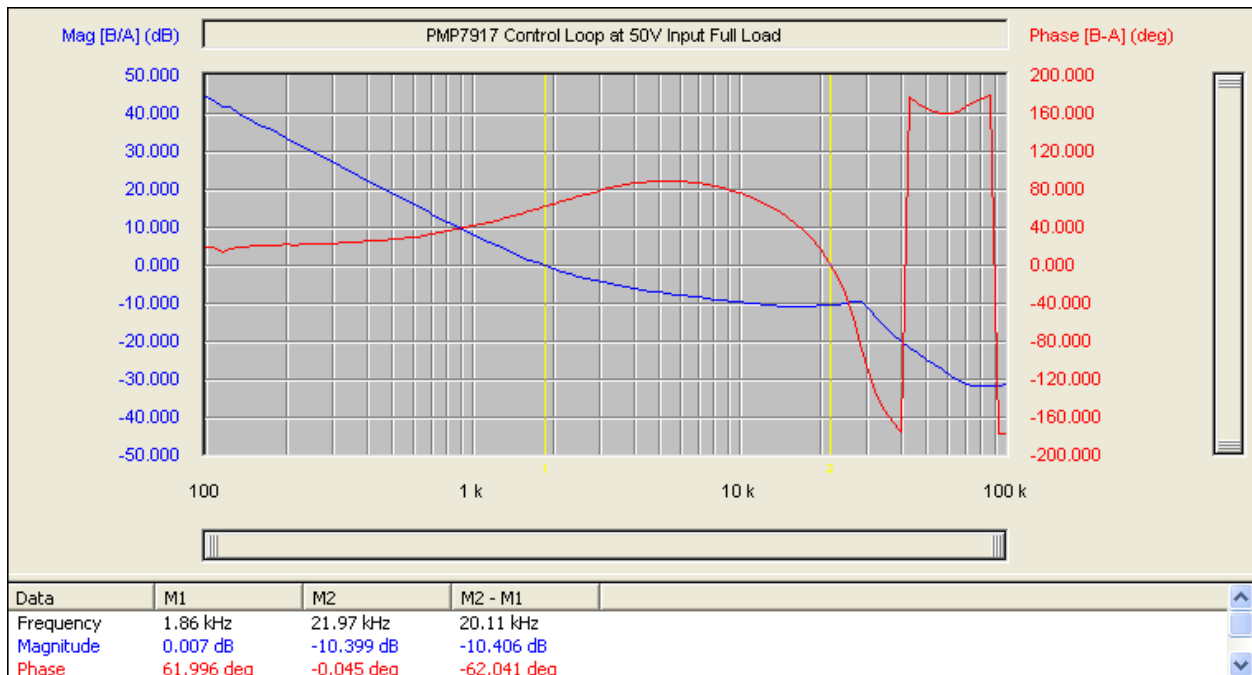

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated