 


Table of Contents:

Page 1:	Proposed improved layout
Page 2:	Vout vs. Load (load line) and conversion eff. off 12Vin
Page 3:	Ripple out at 14A load
Page 4:	Load dynamics on EVM
Page 5:	Major waveforms
Page 6:	Thermal picture at max thermal load rating of 10A

Proposed improved layout approach:



Q1 is the high side FET; Q2 is the low side FET; C1 and C2 are the input caps (ceramic size 1210); C8 and R6 is the snubber. Key is rotating Q1 and Q2 such that drain of high side FET and source of low side FET face same side where the input caps are to be placed. Snubber then should be placed as close to drain source of low side FET as feasible. Traces to gates are much less critical and can be on other layers and be signal trace (10 to 25 mils) width.

With improved layout, efficiency can be improved as less snubbing and less slowing of high side gate drive by R10 will be needed.

Output load line and conversion efficiency from the 12V input. Bias was always 5.007V and bias input power for gate drive is not included in calculations below. Based upon FETs used and 300kHz operation, 3mA will be needed off the 5V Bias for gate drive when switching at 300kHz.

Note: operation above 10A load (max thermal requirement) is with about 200 LFM airflow

Regulation, losses and efficiency (from 12V excluding bias power):

Vin Volts	Iin mA	Vout1 mVolts	Iout1 A	Efficiency %	Losses in mW
13.23	1487	1092	14.01	77.8	4374
13.21	1246	1100	12.01	80.3	3249
13.22	1021	1109	10.01	82.2	2397
13.20	804	1117	8.01	84.3	1666
13.21	595	1125	6.01	86.0	1099
13.20	396.5	1133	4.01	86.8	690
13.21	206.5	1141	2.01	84.1	434
13.20	108	1142	1.01	80.9	272
13.21	5	1141	0	N/A	66
12.02	1630	1092	14.01	78.1	4294
12.02	1364	1100	12.01	80.6	3184
12.03	1117	1108.5	10.01	82.6	2341
12.01	879	1117	8.01	84.8	1610
12.02	650.5	1125	6.01	86.5	1058
12.03	432.5	1132.5	4.01	87.3	662
12.00	225	1141	2.01	84.9	407
12.04	117.5	1142	1.01	81.5	261
12.00	6	1141	0	N/A	72
10.80	1806.5	1092	14.01	78.4	4211
10.80	1513	1100	12.01	80.8	3129
10.81	1239	1108.5	10.01	82.8	2298
10.80	974	1117	8.01	85.1	1572
10.79	720.5	1125	6.01	87.0	1013
10.80	479	1133	4.01	87.8	630
10.80	248	1141	2.01	85.6	385
10.81	130	1142	1.01	82.1	252
10.80	6	1141	0	N/A	65


Load line is -4mV per A for loads greater than 2A set by R6 at 2.61k.

Output voltage follows slope very well from 2A thru 14A. Below 2A it does not rise 8mV to 1149mV as per slope, but stays at the 2A output level. This may be due to reduction in duty cycle / frequency at these light loads to save power loss. At no load Vout is still well within the +/- 1.5% limits of target 1.150V.

Ripple out at max load and max Vin:

2-Aug-10
13:54:41

10 μ s
5.0mV

 

pkpk(1) 25.78mV
 maximum(1) 16.44mV
 rise(1) 3.4980 μ s
 Fall(1) 1.6780 μ s
 Freq(1) 425.936 kHz

PMP5835 TPS51610 300kHz CSD16411Q3/16406
 Snubber 1 ohm plus 1500pF; R10=2.2
 Vin = 13.23V; Iin=1487mA; Vout = 1.092V at 14.14A is Electrical max load
 Max Vin and Max load Output ripple at TP3
 2x330uF 7mOhm caps plus 8x10uF caps on Output
 With 1x probe 20MHz BW
 26mV p-p


10 μ s B/WL
 1 5 mV AC
 2 .5 V DC
 3 50 mV DC
 4 10 mV 500

1 DC 0.0mV

STOPPED


Step load response using 'on board' dynamic load: step size ~9.75A

3-Aug-10
11:48:43

 

Load dump response using same on board dynamic load: step size ~9.75A


3-Aug-10
11:47:01

 

Qq


Major waveform at 10A load off 13.26Vin:

2-Aug-10
13:41:20

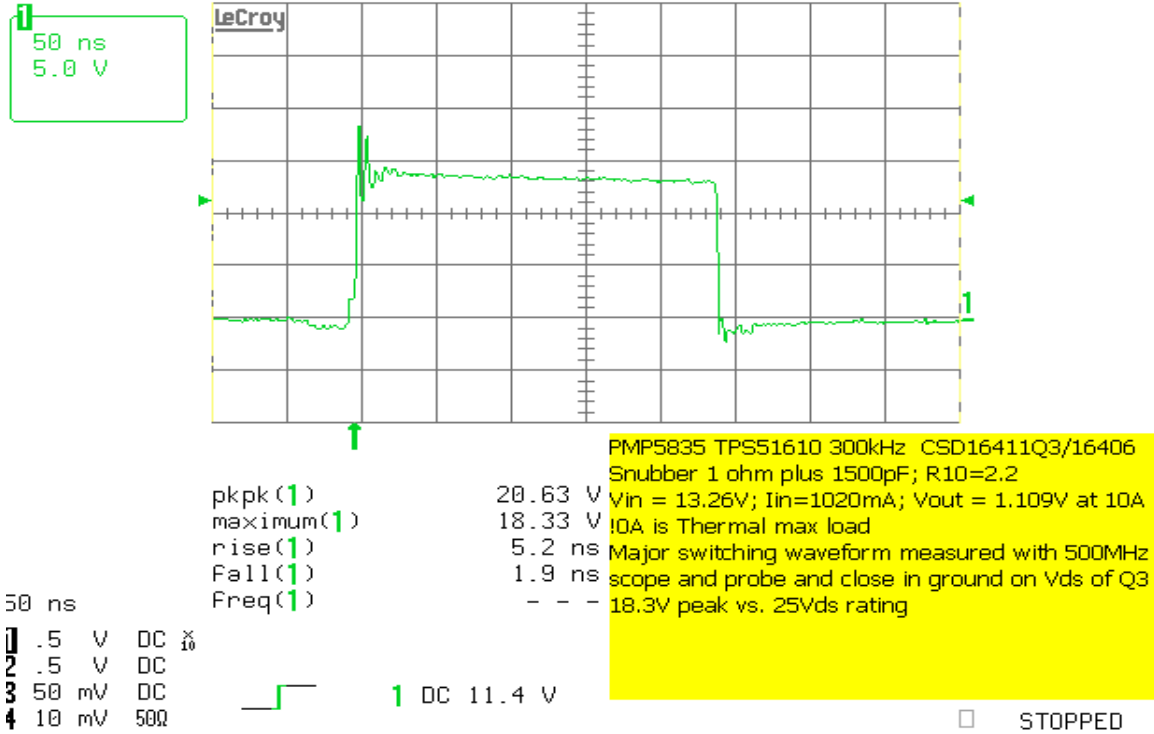

Major waveform at 14A load off 13.2Vin:

2-Aug-10
13:51:13

 

Qq

Thermal results:

Run for >10 minutes at 10A Thermal max off Vin max of 12V+10%: No forced air


Snubber added (1500pF size 805 plus 1 ohm size 2010 across Vds of lo side FET and

R10 increased from zero to 2.2 ohm to slow down hi side turn on)

PMP5835 with snubber and R10=2.2; 13.26Vin, 5.007Vbias, 1020mA in 1.109Vout at 10.0A ambient 23-25 deg. C

Low side FET hottest at 76 deg C, hi side 72, choke 69, snubber resistor (1 ohm size 2010) 74

Qq

 

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.