

## TIDA-00331- "Precision Power Limiting Solution"

---

### 1. System Description:

This solution limits the power delivered to a maximum of 15W to ensure IEC60730 compliance in Human-Machine-Interaction (HMI) ports, making it very easy for the end equipment to meet safety regulations.

This design uses TI's TPS25921AD to monitor the voltage and current flowing through the connected system and controls the power output within 2%. Along with the power limit function, TPS25921AD also protects against over voltage, under voltage, inrush current and short circuits.

### 2. System Operation

Figure 1 shows a very simple and cost effective way to limit the power delivered to the downstream load. This concept uses TI's TPS25921 and supplies power to the connected output load in such a way that load power never exceeded 15W to meet IEC60730 compliance requirements. The operation of the circuit is as follows.

For the given load condition, higher input will produce more power at the load and that may be more than 15W if the load current is not reduced.

The maximum current limit of the device can be set up to 1.5A by R<sub>ILIM</sub> resistor. A small circuit wired around Q1 with R3, R4 and R5 is utilized to reduce the current whenever output power exceeds more than 15W. The Q1 remains inactive until V<sub>out</sub> is less than 10V and can deliver up to 15W load. The Q1 plays a role to reduce the effective resistance at ILIM pin by diverting some current from ILIM pin through R5 and Q1 as the V<sub>out</sub> starts increasing higher than 10V. This reduces impedance at ILIM, altering current limit setting and now current limit will be lower than 1.5A for the increased input voltage.

The R3, R4 and R5 are selected in such a way that allows Q1 keep altering the TPS25921 current limit dynamically as V<sub>out</sub> increases.

For example if V<sub>in</sub> or V<sub>out</sub> is 12V, the Q1 will program 1.25A current limit and for 16V output, the current limit will be altered to 1.066A in order to maintain the output power not exceeding 15W.

TIDA-00331- "Precision Power Limiting Solution"

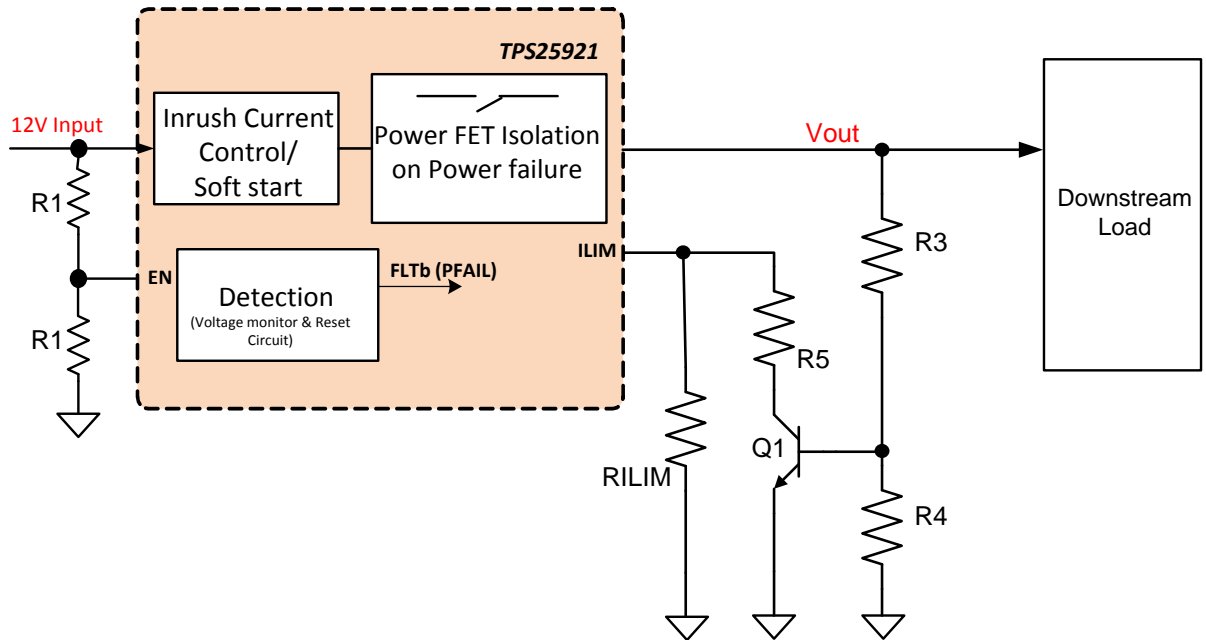


Figure 1: Block Diagram Precision Power Limiting Solution

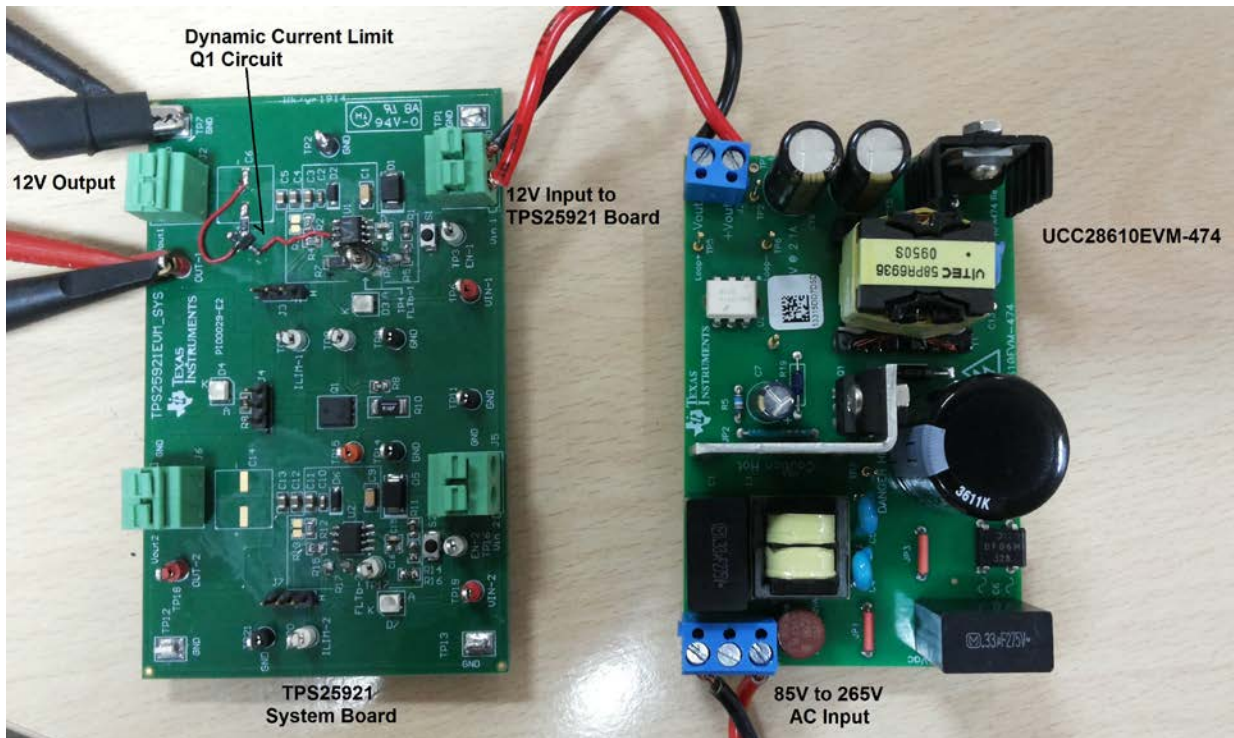


Figure 2 Test Set-up made by using TPS25921 System Board and UCC28610 EVM

### 3. Test Results

#### Test setup Precision Power Limiting Solution

- Vin from AC/DC converter (UCC28610EVM-474) = 12V@2.5A
- Output Voltage from TPS25921 system board = 12V
- TPS25921 EVM current limit set by RILIM= 1.5A
- Output Load Variation- 1A to 1.5A
- Additional power supply used for the test – 0-20V,10A

#### Scope label Information

- VIN- Input supply voltage to TPS25921 system board.
- IN= Iout = Load current
- Vout – Load voltage
- Pout – Power delivered to the load with varying load current or volatge

#### Test Result 1:

The input voltage is set to 12V and load current (Iout ) is varied from 1A to 1.25A, the figure 3 show the dymanic adjustment of the current limit to limit output power when load current is incread beyond 1.25A and load power is limited to 15W.The device enters retry-mode when it reaches the adjusted power limit.

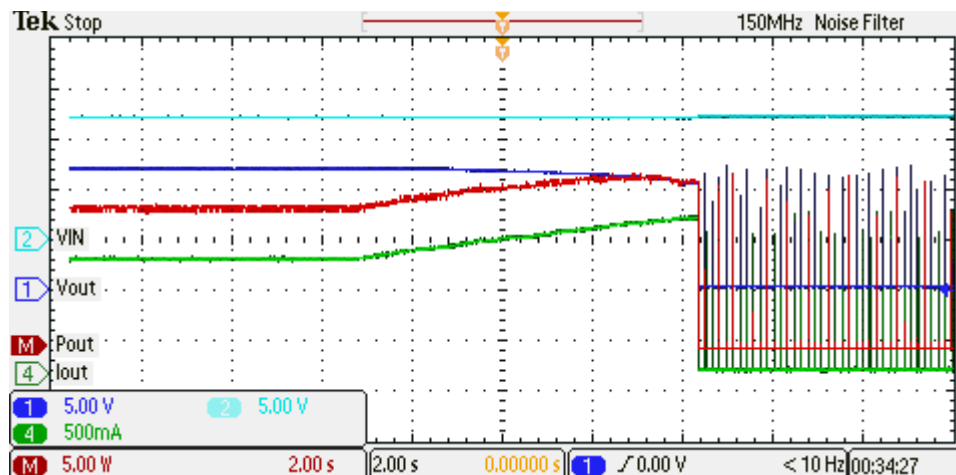


Figure 3: Load Power is limited to 15W for VIN= 12V, Iout varied from 1 to beyond 1.25A

**Test Result 2:**

In this case the input voltage is set to 10V and load current ( $I_{out}$ ) is varied from 1.0A to 1.5A. Figure 4 shows this design adjusts the current limit and limits the output power at 15W, when load current is increased beyond 1.5A.

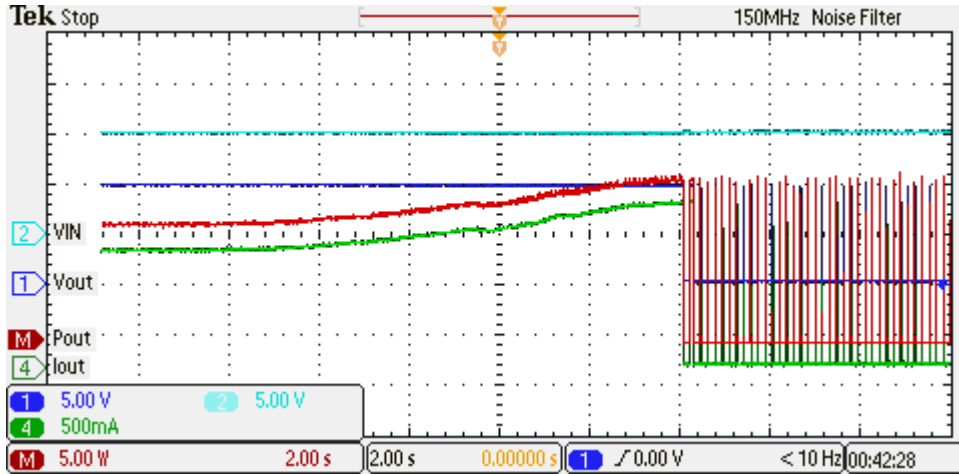


Figure 4: Load Power limited to 15W, for  $V_{IN}$ = 10V and  $I_{out}$  is increased from 1A to beyond 1.5A

**Test Result 3:**

In this case, the input voltage is set to 15V and load current ( $I_{out}$ ) is varied from 0.5A to 1.0A and figure 5 show the dynamic power limiting feature of the solution limits the power at 15W, when load current is increased beyond 1A. This is shown in figure 5.


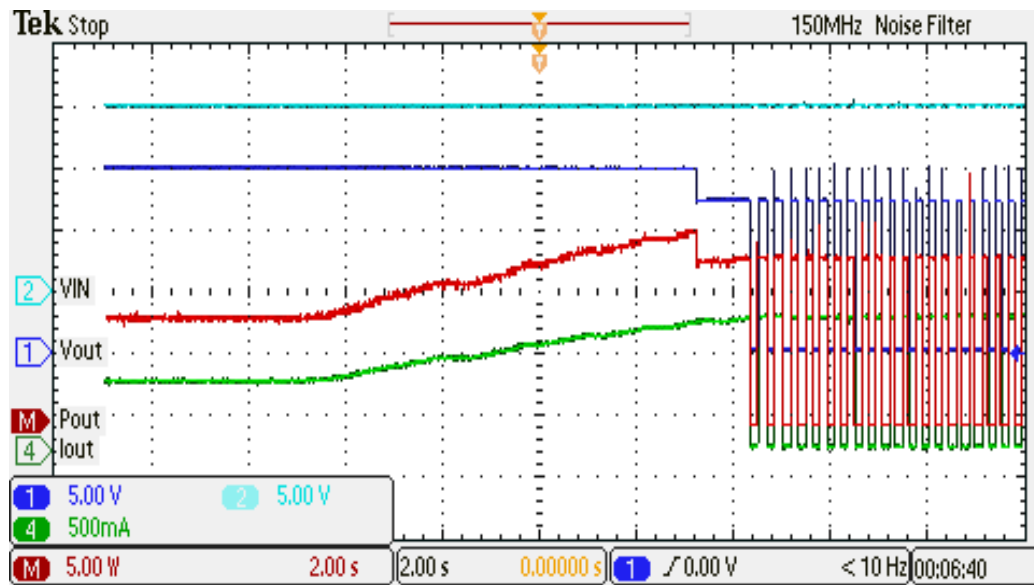


Figure 5: Load Power limits at 15W, for  $V_{IN}$ = 15V,  $I_{out}$  is increased from 0.5A to beyond 1A

**Test Result 4:**

Figure 6, shows, Input voltage is varied from 8V to 15V at the constant load ( $I_{out} = 1.1A$ ) and demonstrates that  $V_{out}$  start falling when load power goes beyond 15W. This also shows, the current limit is not adjusted until load power exceeding 15W. The device enters retry-mode when it reach the adjusted power limit.

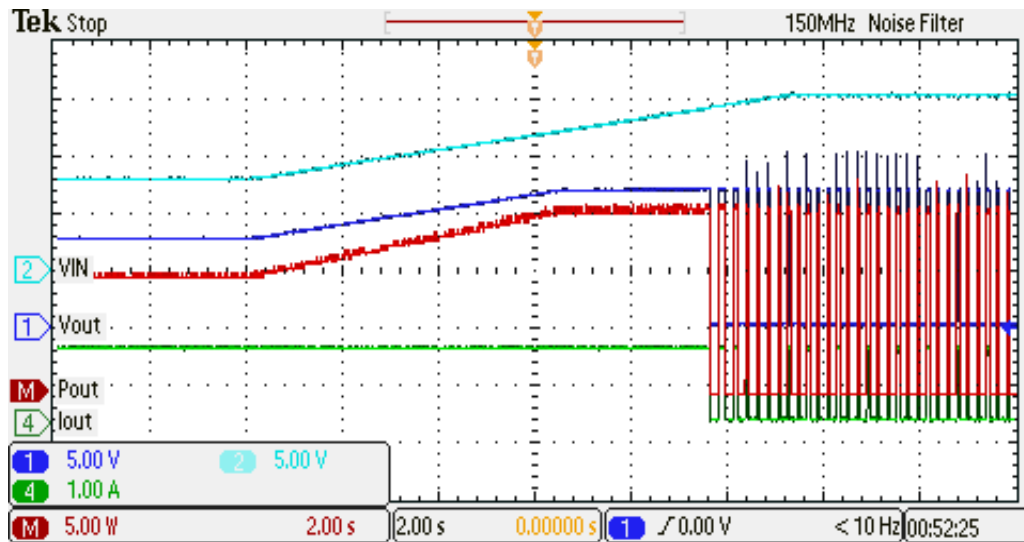

**Figure 6 : Load Power limit at 15W, for VIN= 8V to 15V @ 1.1A load**

## IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.