

# PMP9768 - Automotive E-Call Power Supply Reference Design with High Intermediate Voltage

Emergency call devices (e-call) for automotive need to be powered reliably during the complete phase of the emergency call. In an emergency situation which requires the emergency call in a car, the car may have been severely damaged including a breakdown of the car battery supply. For this reason usually an integrated backup power solution is required. This reference design shows a complete power solution for such an e-call application including the backup power. It uses a battery configuration with a maximum terminal voltage of less than 9V for backup power. For providing power to all required circuit blocks it uses suitable switching regulators. It also manages seamless transition from main to backup power and back during all possible power conditions in the car. Charging the backup battery is included as well.

## 1 Overview

For regulating the supply voltage for the required circuit blocks and for interfacing with the high voltage of the main car battery rail, switchmode power supplies are used. Figure 1 shows the structure of the circuit. At normal conditions the system is supplied from the main car battery rail. Over voltage protection is active in case of overvoltage events to limit input voltage for DC/DC converts. All regulators supplying the individual circuit blocks are connected to this system rail. During backup operation the power path control block switches the backup battery to the system rail. Depending on the battery type and the state of charge of the battery, it is expected that the system voltage during backup operation can vary between 5V and 9V. The nominal main car battery voltage and the backup system voltage range defines the topology for all regulators supplying the individual circuit blocks. To keep the solution size small and to avoid interference with other systems in the car, the switching converters are selected to be capable to operate at switching frequencies above 2 MHz at nominal load conditions.

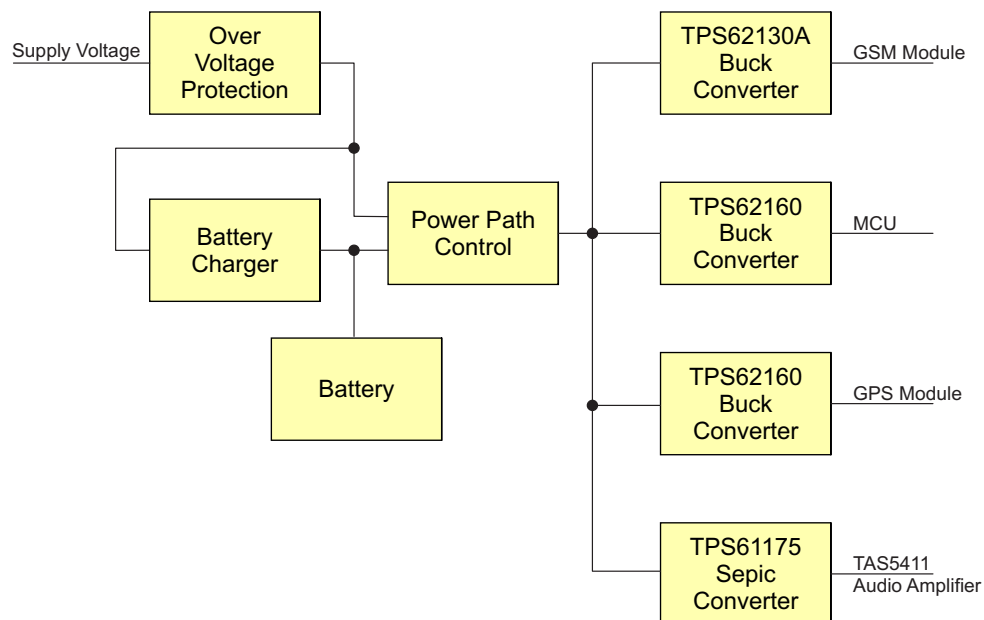


Figure 1. Block Diagram

## 2 Measurements

As shown in [Figure 1](#) the functional blocks of the system are supplied with 4 dedicated regulators. For the GSM module a supply voltage of 3.8 V is needed. This requires buck conversion, so TPS62130 is selected for this rail. The MCU and the related logic components which are used to control the system require 1.8 V. This only needs a step down converter like the TPS62160 which is selected here. For the 5 V required for the GPS or GLONASS system the TPS62160 is used in buck operation. The audio amplifier TAS5411 is supplied with 9 V. This requires a sepic converter like the TPS61175 which is used here.

Most of the converters operate at switching frequencies above 2 MHz by default and the frequency cannot be adjusted. For the converters which allow programming the switching frequency, frequencies above 2 MHz are selected. Details on how to configure the features of the individual devices in this circuit can be found in their respective datasheet ([TPS62130A](#), [TPS62160](#), [TPS61175](#), [TAS5411](#)).

The peak load expected for the GSM module is 2.5 A with a duty cycle of 25%. All other rails are designed for maximum 1 A. All power measurements have been done at a nominal average load current. Nominal average load current for the testing of the GSM rail is 0.62 A, for the MCU rail 0.5 A, for the GPS rail 0.8 A and for the audio amplifier 0.5 A. Standby operation is defined with each of the rails operating at 10% of their maximum output power.

The measurements documented in this report are captured at the defined nominal load condition and at the defined standby load condition.

### 2.1 Total Efficiency

[Table 1](#) shows the efficiency of the total solution at the defined nominal average output conditions. The input currents are measured for operation from the main input supply and for operation from the backup battery.

**Table 1. Efficiency at Nominal Load**

Voltage Rail	Voltage [V]	Current [A]	Power [W]
Main Input (normal operation)	14.0	0.99	13.79
Battery Input (backup operation)	7	1.93	13.51
GSM Module	3.8	0.62	2.39
MCU and Logic	1.8	0.50	0.90
GPS Module	5.0	0.80	3.97
Audio Amplifier	9.0	0.50	4.51
<b>Efficiency</b>			
<b>Main input operation</b>			<b>85.16%</b>
<b>Battery operation</b>			<b>87.01%</b>

[Table 2](#) shows the efficiency of the total solution at the defined standby average output conditions. The input currents are measured for operation from the main input supply and for operation from the backup battery.

**Table 2. Efficiency at Standby Load**


Voltage Rail	Voltage [V]	Current [A]	Power [W]
Main Input (normal operation)	14.0	0.24	3.19
Battery Input (backup operation)	7	0.43	3.02
GSM Module	3.8	0.25	0.95
MCU and Logic	1.8	0.10	0.18
GPS Module	5.0	0.10	0.50
Audio Amplifier	9.0	0.10	0.90
<b>Efficiency</b>			
<b>Main input operation</b>			<b>78.96%</b>
<b>Battery operation</b>			<b>83.62%</b>

## 2.2 Functional Power Blocks

In this section measurement results for the individual converters are shown which are specific for this implementation. Since the converters are configured very similar to their default recommended configuration standard performance measurements like for example DC regulation, efficiency at various line and load conditions and typical load transient measurements are not repeated here. They can be found in the individual datasheets of the converters ([TPS62130A](#), [TPS62160](#), [TPS61175](#), [TAS5411](#)).

### 2.2.1 Input Overvoltage protection


The input voltage range of the e-call is up to 40V. The higher input voltage than main battery voltage can appear for example during start of the engine. In this case it is not necessary to provide nominal output power from e-call power tree. To protect DC/DC converts from higher input voltage than maximum recommended operating voltage the overvoltage protection is implemented because the converters selected for the power tree are DC/DC converters are rated maximum recommended operating voltage 17 and 18V . The overvoltage protection clamps the voltage at the input of the DC/DC converters below maximum operating voltage. This solution of the overvoltage protection allows continuous operation of the power tree and avoid reset of the MCU ,GPS module or any other load connected to DC/DC converters output. [Figure 2](#) shows input voltage of the e-call power tree during overvoltage event and intermediate voltage which is supplying the converters.

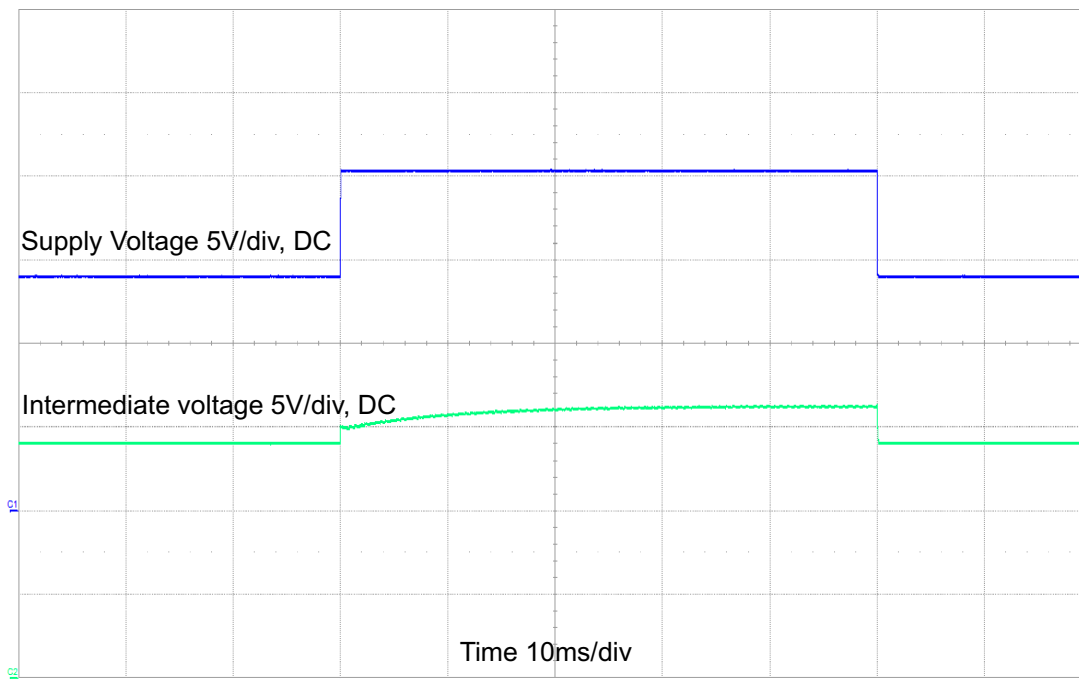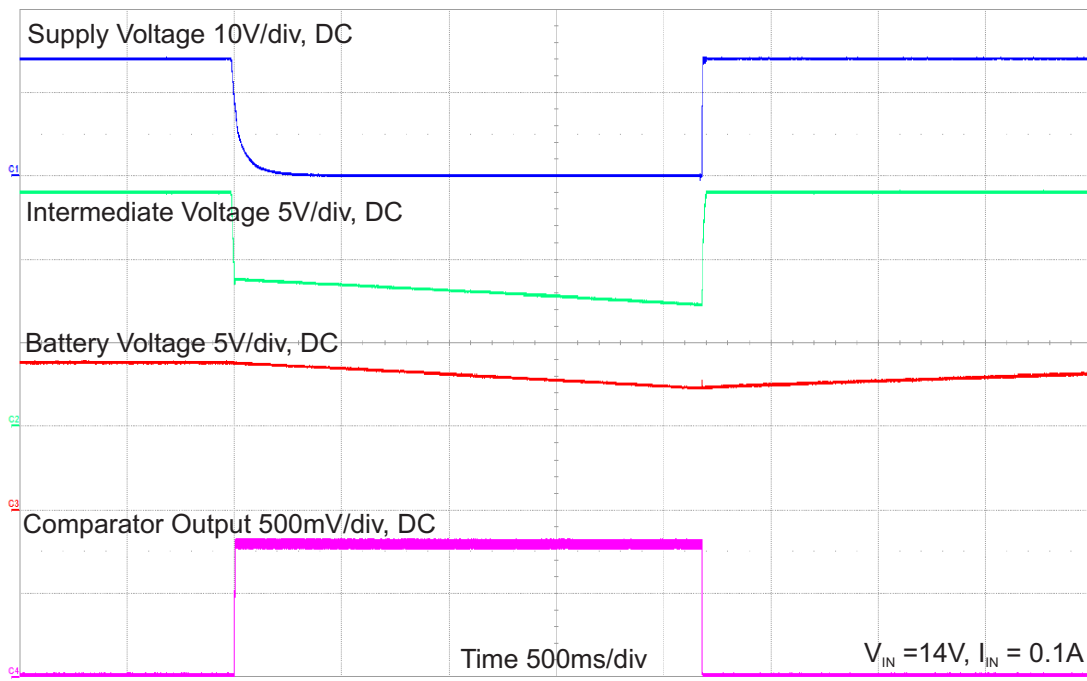

**Figure 2. Input Overvoltage event**


### 2.2.2 Power Path Control

[Figure 3](#) shows all supply voltage rails during a transition from the main input supply rail to backup supply and back. At main input supply operation the intermediate voltage is used to supply the system. When the main power is disconnected the intermediate voltage drops to the backup battery voltage. Since the backup battery is discharging the voltage is decreasing over time. As soon as the main power is back the intermediate voltage is again at the main supply voltage.


**Figure 3. Power Path Control**

### 2.2.3 Modem Supply

Figure 4 shows voltage and current waveforms related to the operation of the modem. The test condition here is a load current pulse of 2.5 A for 500 ms which is considered worst case for GSM communication. The high current pulses can be supplied by the buck converter which is used here. The waveforms of inductor current and output voltage show the control performance of this solution and the waveform of the intermediate voltage shows the impact on the intermediate voltage which is supplying the converter.

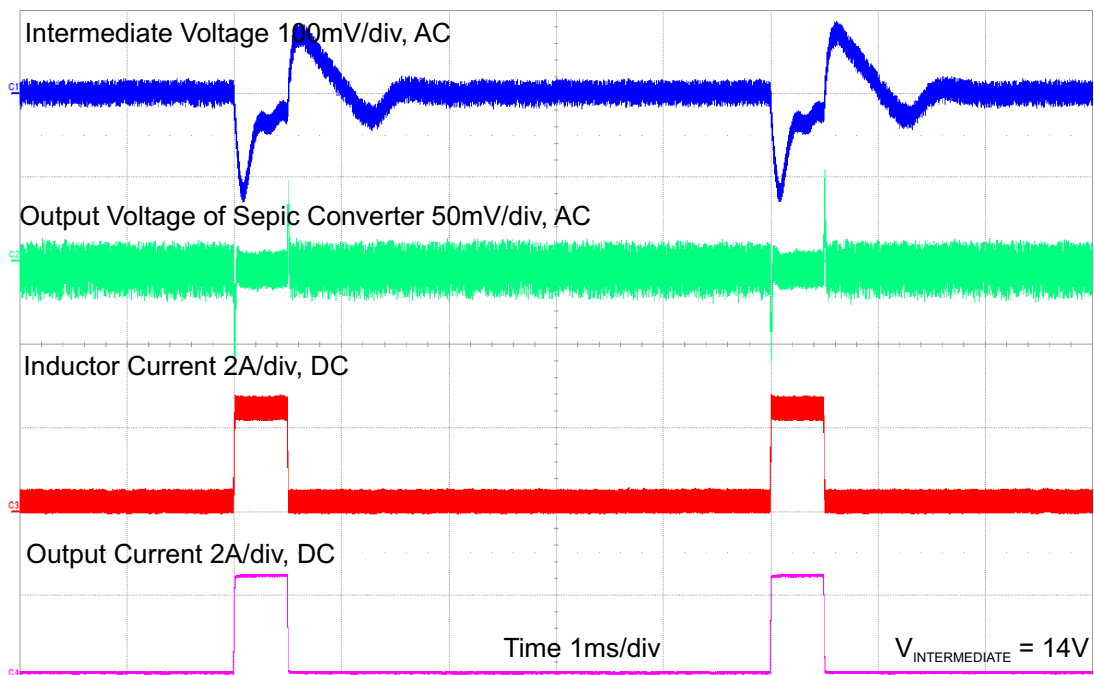
**Figure 4. Modem Power Supply**

### 2.2.4 Audio Supply

Figure 5 shows voltage and current waveforms related to the operation of the supply of the audio amplifier. The audio amplifier was operated with a test signal with a frequency of 2 kHz at a load of 8.7Ω.

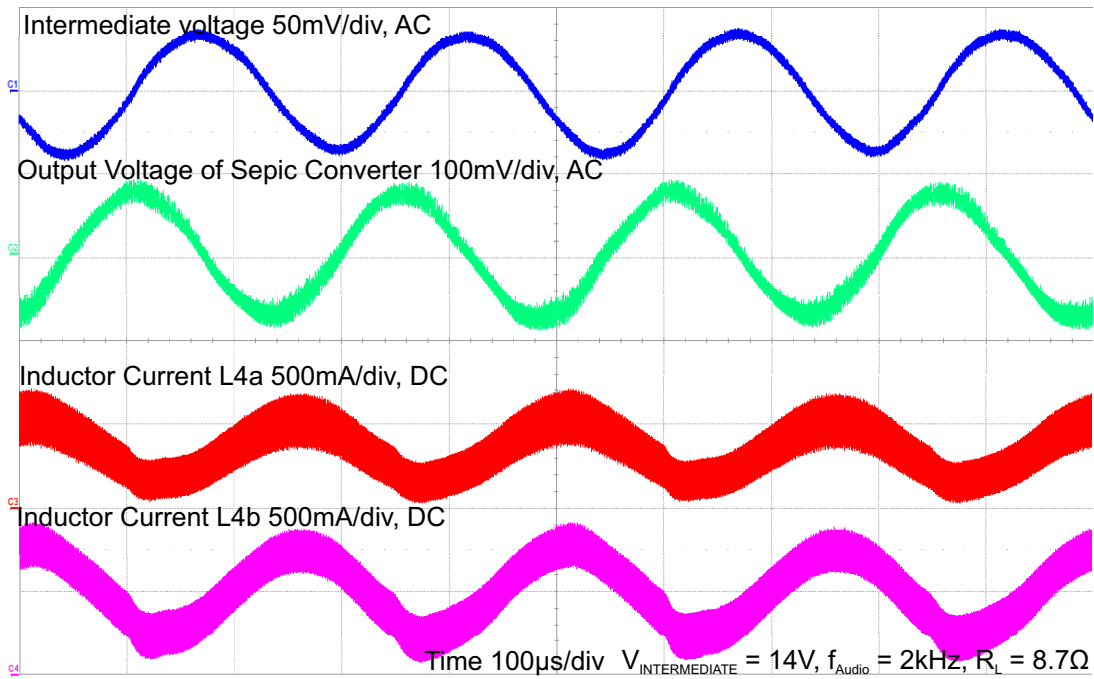


Figure 5. Audio Power Supply

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)