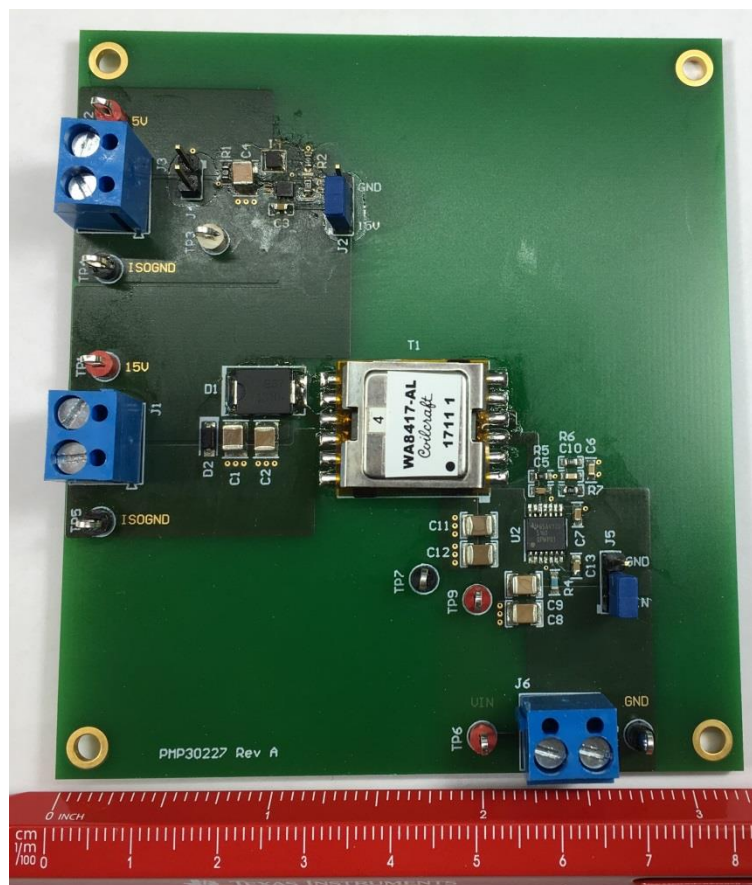


## Automotive Flyback-Boost Converter with 15V @ 0.25A

- Input 8.0 .. 16.0V, 28V peak
- Output 15.0V @ 0.25A
- Free-Running-Switching Frequency of 440 kHz

## Automotive Buck Converter with 5V@0.2A

- Input 12.0 .. 16.0V
- Output 5.0V @ 0.2A
- Free-Running-Switching Frequency of 2.25 MHz



## Automotive Flybuck-Boost Converter with 15V @ 0.25A

### 1. Startup

The startup waveform at 12.0V input voltage and no load on the output is shown in Figure 1.

Channel C1 **12.0V Input Voltage**

10V/div, 10ms/div

Channel C3 **15.0V Output Voltage**

10V/div, 10ms/div

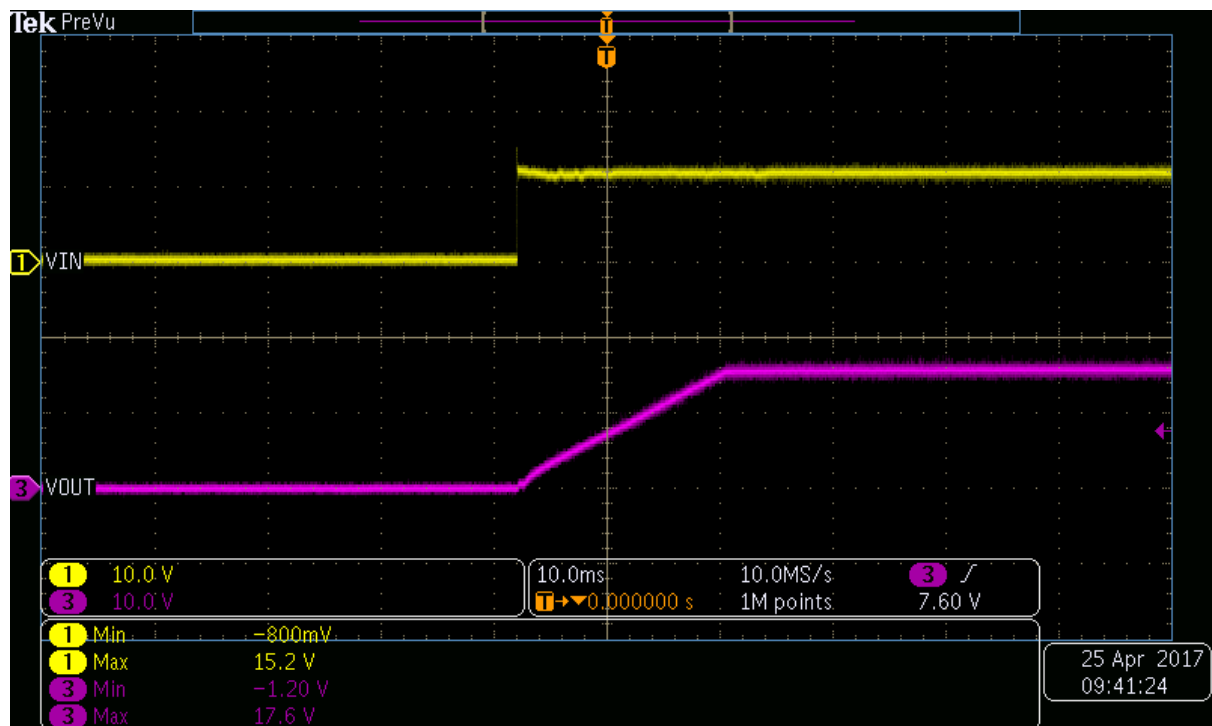


Figure 1

## 2. Shutdown

The shutdown waveform at 12.0V input voltage and 0.25A load on the output is shown in Figure 2.

Channel C1 **12.0V Input Voltage**

10V/div, 4ms/div

Channel C3 **15.0V Output Voltage**

10V/div, 4ms/div

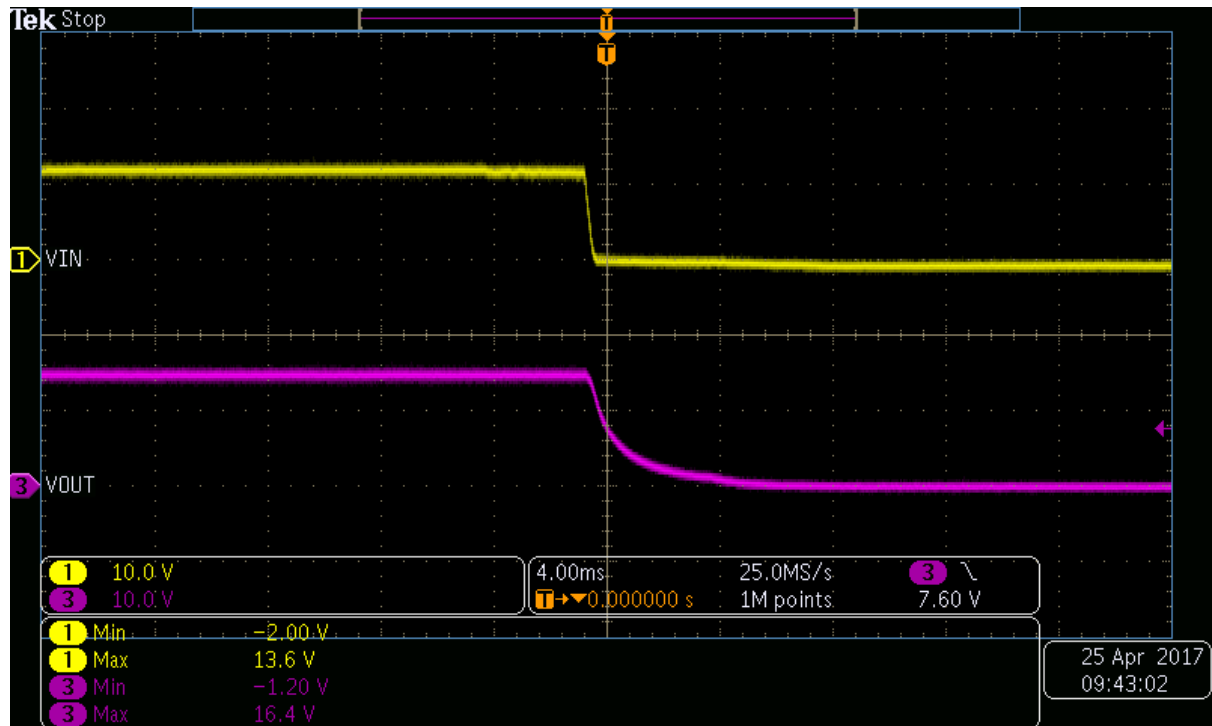


Figure 2

### 3. Efficiency

The efficiency and load regulation with MBRS3100 (D1) are shown in Figure 3 and Figure 4.

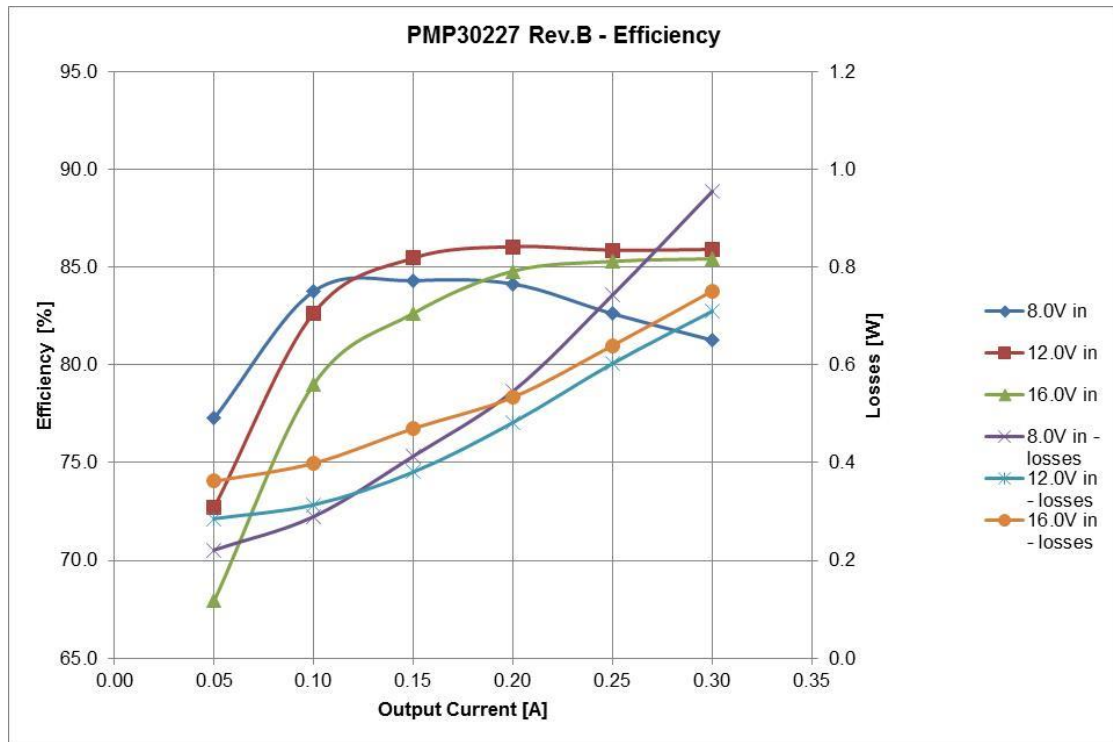


Figure 3

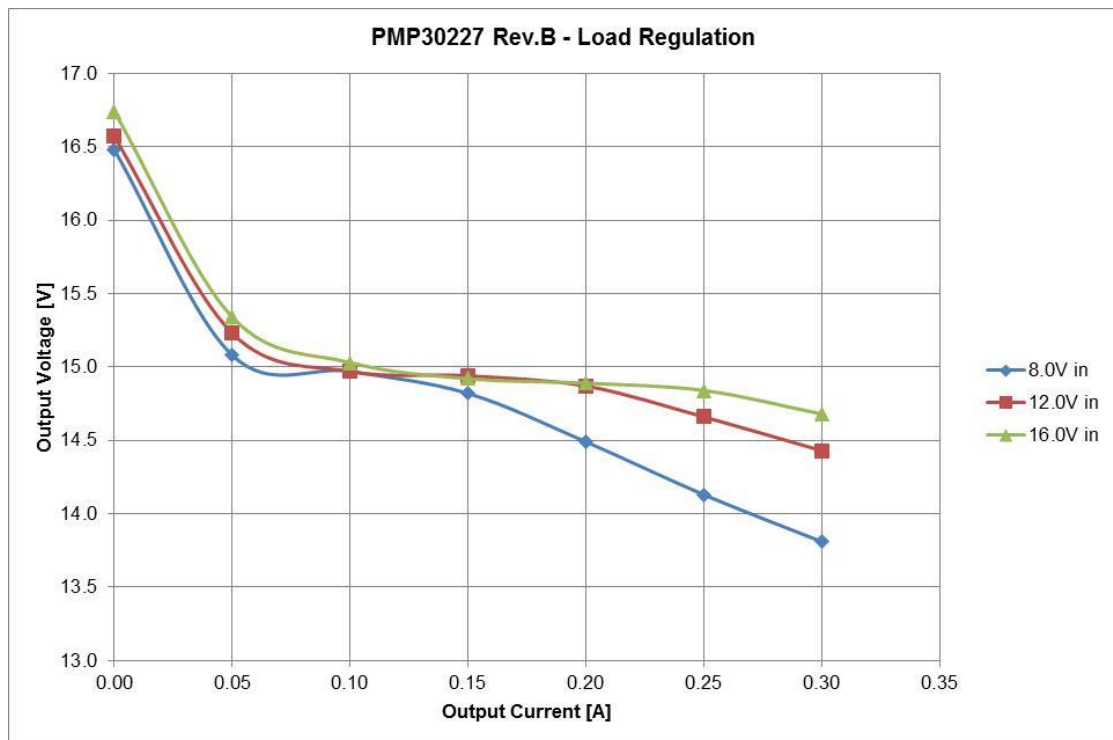


Figure 4

### 4. Transient Response

The response to a load step at 12.0V input voltage is shown in Figure 5.

Channel C1 **Output Current**, Load Step 0.125A to 0.25A  
 100mA/div, 1ms/div

Channel C2 **Output Voltage**, -283mV undershoot (1.9%), 345mV overshoot (2.3%)  
 200mV/div, 1ms/div, AC coupled

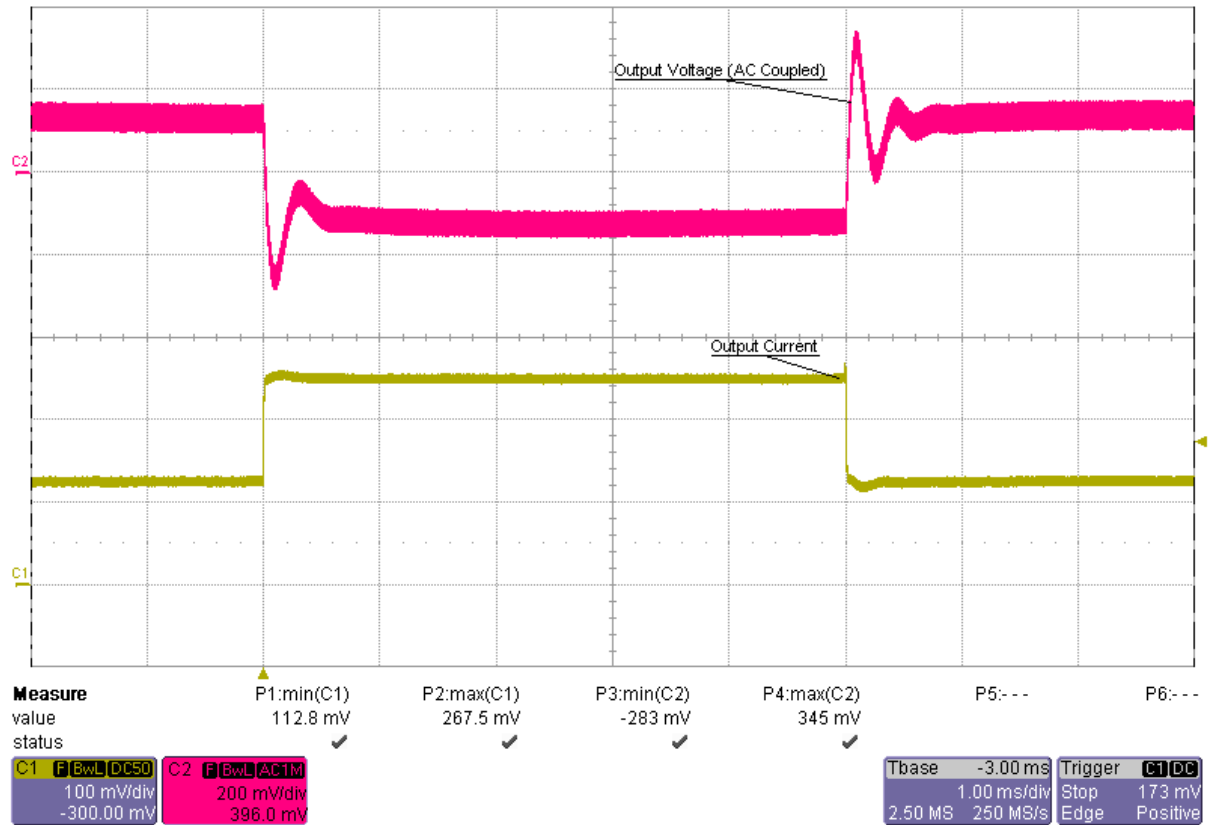


Figure 5

## 5. Input Ripple

The input ripple voltage at 0.25A load is shown in Figure 6.

Channel R1 **Input Voltage @ 16.0V Input**, 156mV peak-peak  
100mV/div, 1 $\mu$ s/div

Channel R2 **Input Voltage @ 12.0V Input**, 168mV peak-peak  
100mV/div, 1 $\mu$ s/div

Channel R3 **Input Voltage @ 8.0V Input**, 192mV peak-peak  
100mV/div, 1 $\mu$ s/div

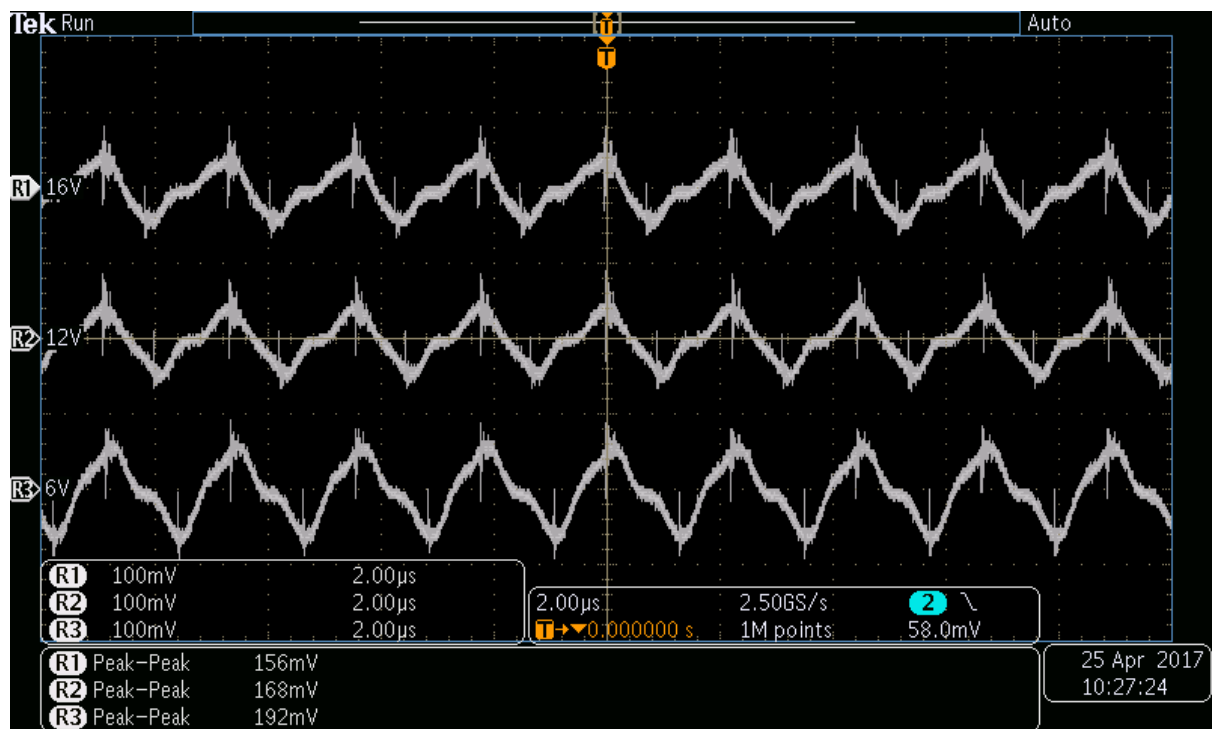


Figure 6

## 6. Output Ripple

The output ripple voltage at 0.25A load is shown in Figure 7.

Channel R1 **Output Voltage @ 16.0V Input**, 92.0mV peak-peak  
50mV/div, 1us/div

Channel R2 **Output Voltage @ 12.0V Input**, 100mV peak-peak  
50mV/div, 1us/div

Channel R3 **Output Voltage @ 8.0V Input**, 116mV peak-peak  
50mV/div, 1us/div



Figure 7

## 7. FET (Switching Node)

The drain-source voltage of the low-side FET at 12.0V input voltage and 0.25A load on the isolated output is shown in Figure 8.

Channel C2     **Drain-Source Voltage**, -8.70V minimum, 12.7V maximum  
5V/div, 1us/div

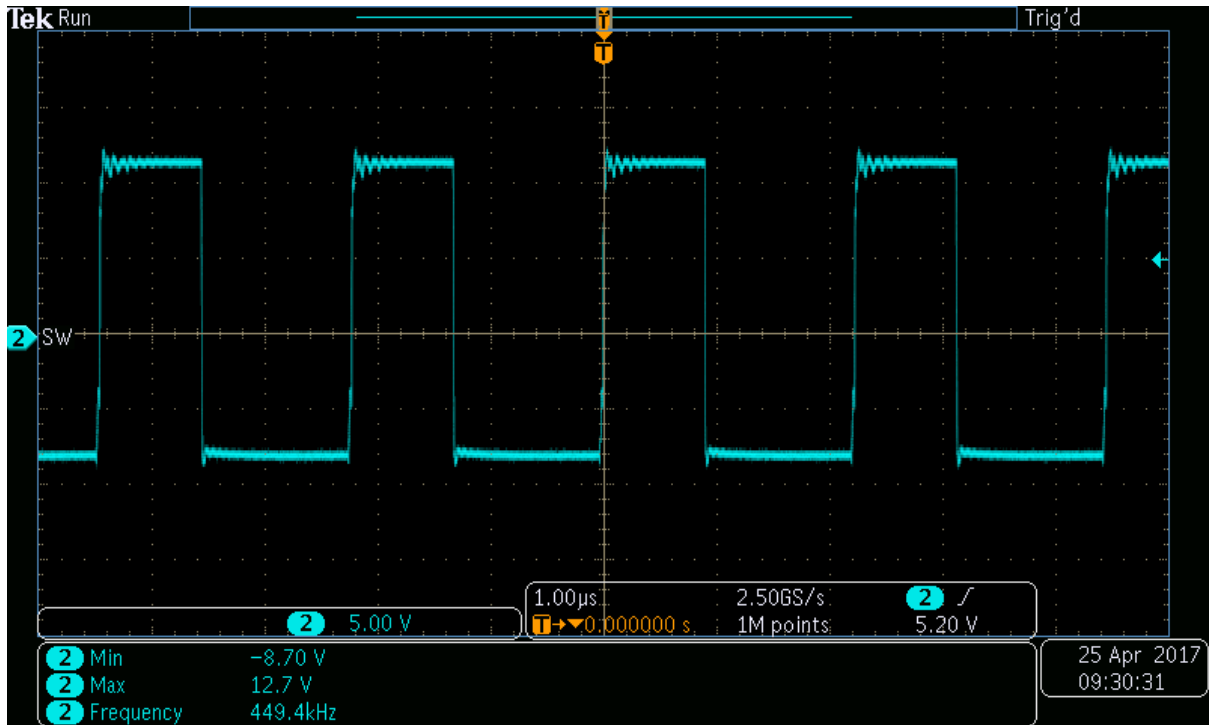


Figure 8



## Automotive Buck Converter with 5V@0.2A

### 8. Startup

The startup waveform at 15.0V input voltage and no load on the output is shown in Figure 9.

Channel C1 **15.0V Input Voltage**

10V/div, 400us/div

Channel C3 **5.0V Output Voltage**

5V/div, 400us/div

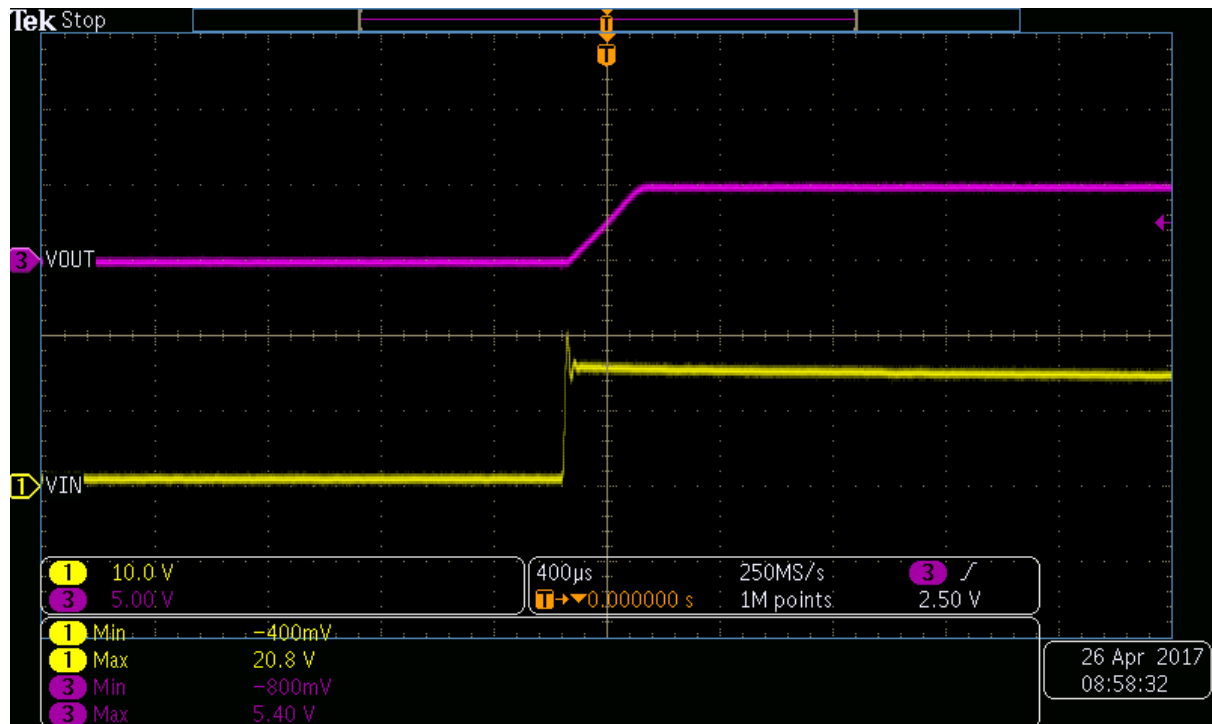


Figure 9

## 9. Shutdown

The shutdown waveform at 15.0V input voltage and 0.2A load on the output is shown in Figure 10.

Channel C1 **15.0V Input Voltage**  
10V/div, 1ms/div

Channel C3 **5V Output Voltage**  
5V/div, 1ms/div

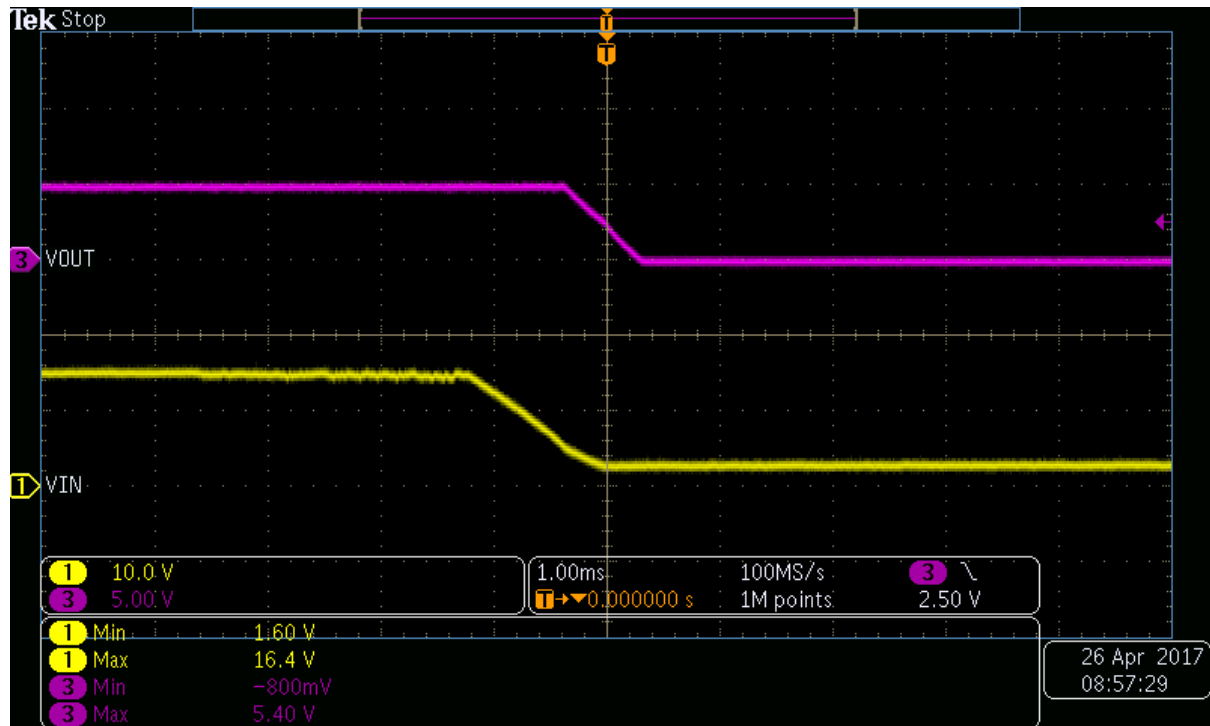


Figure 10

## 10. Efficiency

The efficiency and load regulation of the 5V Buck converter are shown in Figure 11 and Figure 12.

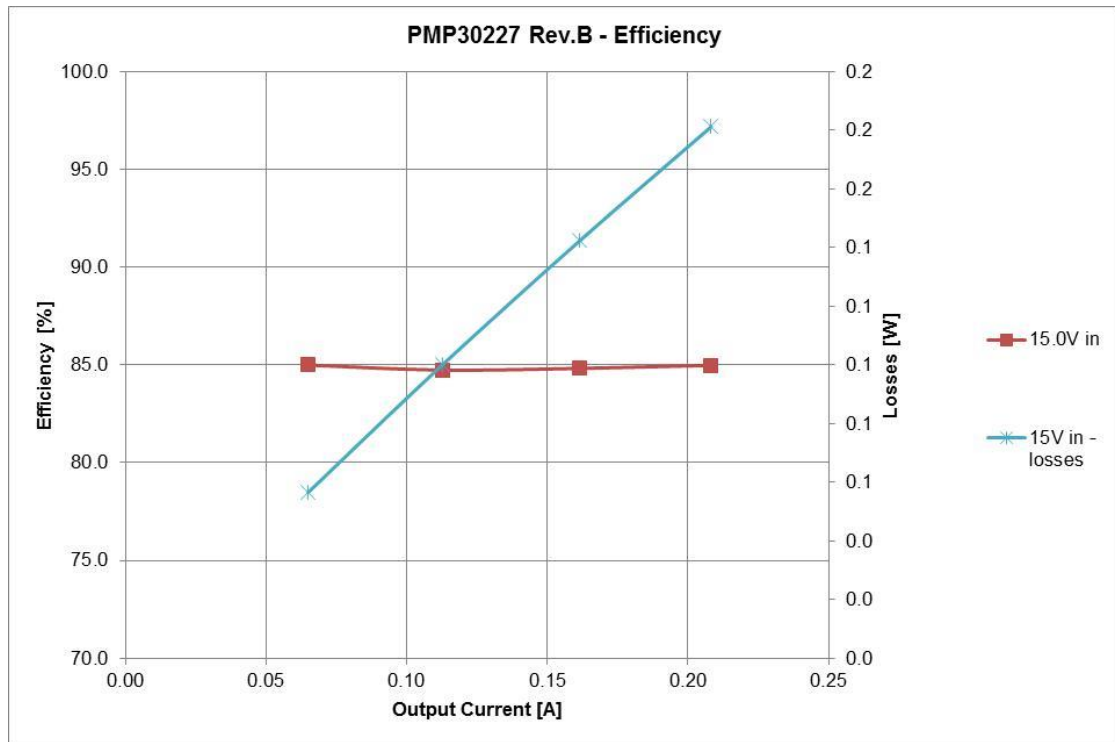


Figure 11

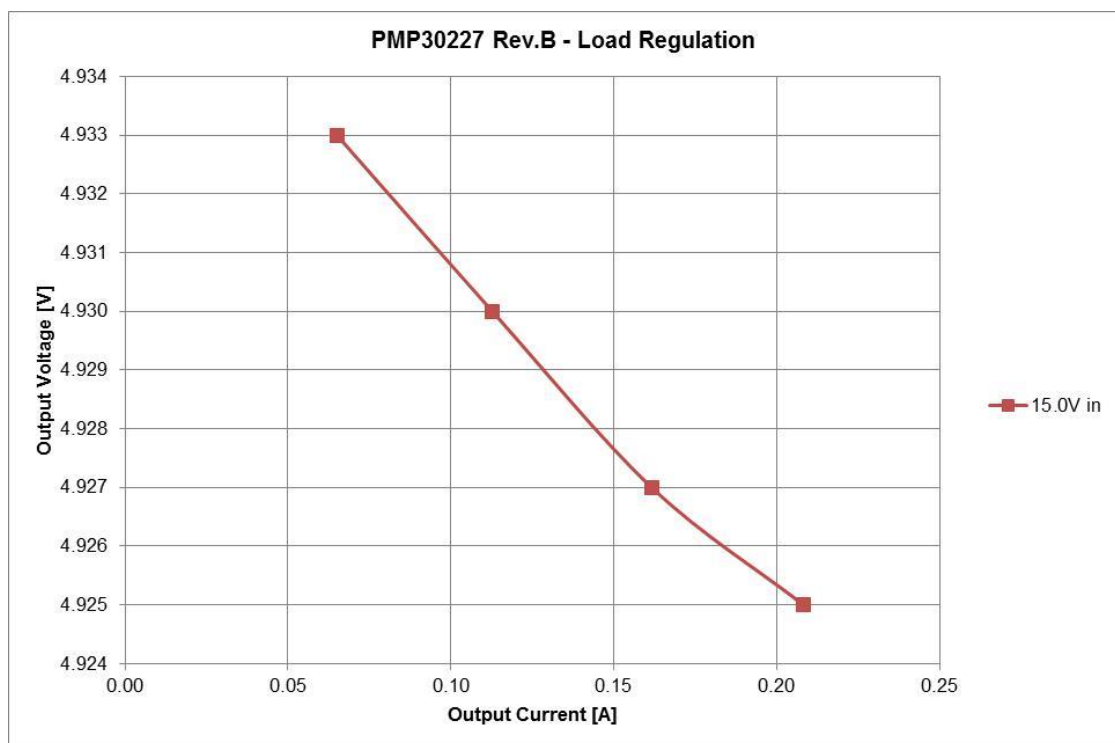


Figure 12

## 11. Transient Response

The response to a load step at 15.0V input voltage is shown in Figure 13.

Channel C4 **Output Current**, Load Step 0.15A to 0.3A  
200mA/div, 2ms/div

Channel C2 **Output Voltage**, -14.4mV undershoot (0.3%), 17.6mV overshoot (0.4%)  
20mV/div, 2ms/div, AC coupled

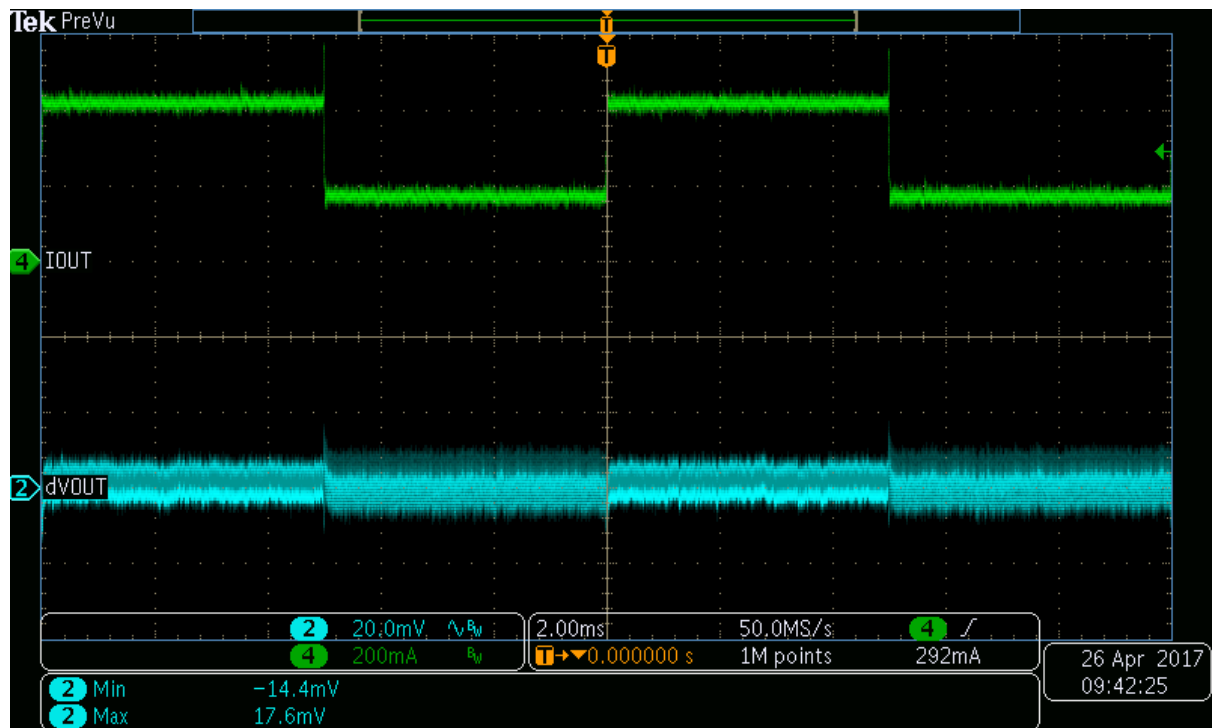


Figure 13

## 12. Input Ripple

The input ripple voltage at 0.2A load is shown in Figure 14.

Channel C2    **Input Voltage @ 15.0V Input**, 280mV peak-peak  
100mV/div, 1us/div

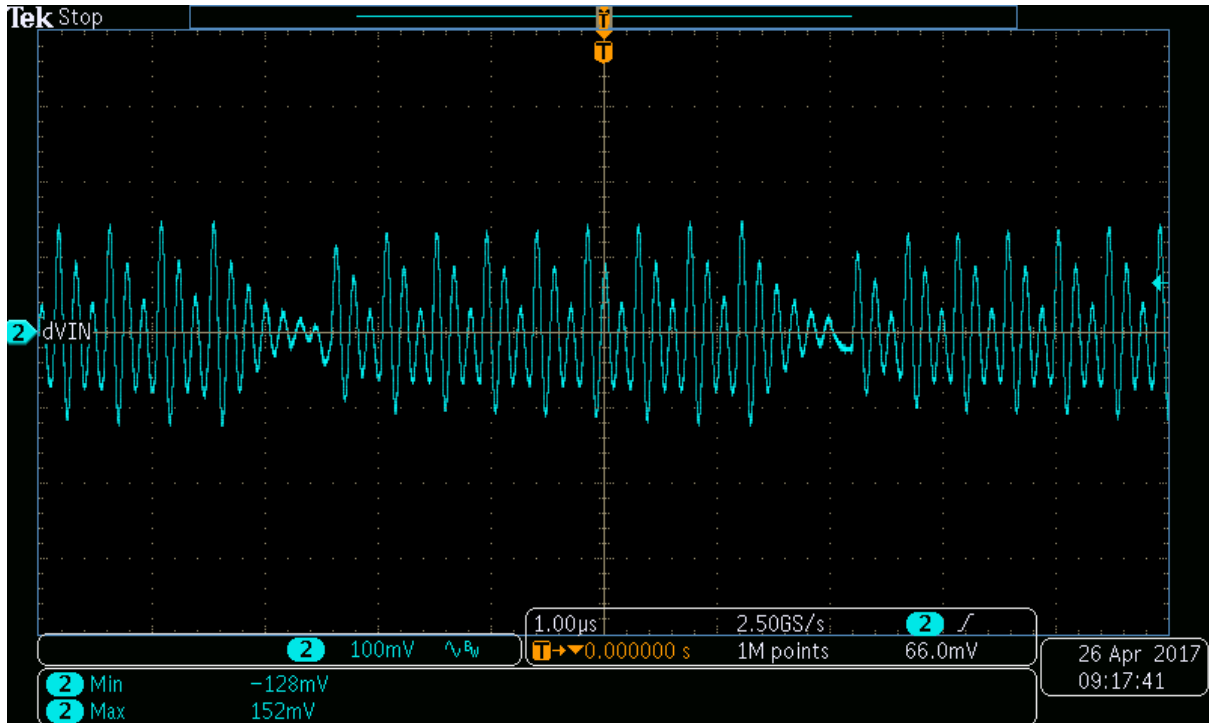


Figure 14

### 13. Output Ripple

The output ripple voltage at 0.2A load is shown in Figure 15.

Channel R2     **Output Voltage @ 5.0V Input**, 8.96mV peak-peak  
2mV/div, 400ns/div

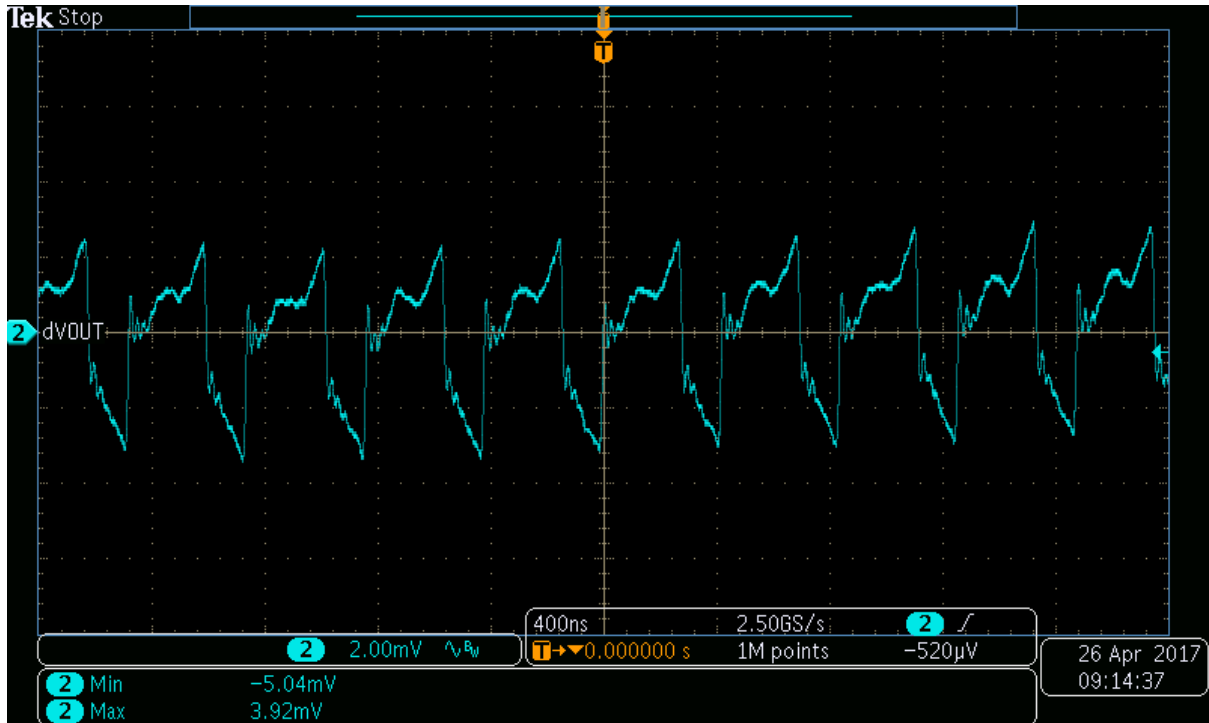


Figure 15

### 14.FET (Switching Node)

The drain-source voltage of the low-side FET at 15.0V input voltage and 0.2A load on the 5V output is shown in Figure 16.

Channel C2 **Drain-Source Voltage**, -1.60V minimum, 18.2V maximum  
 5V/div, 2us/div

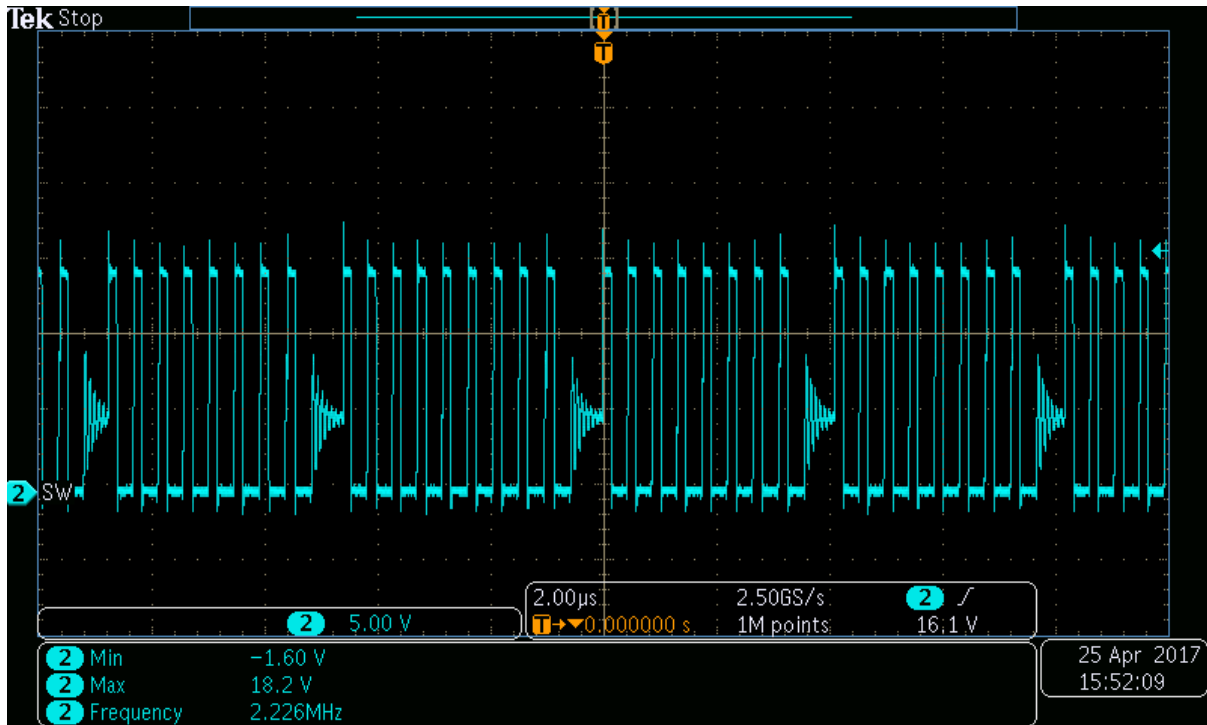


Figure 16

## 15. Thermal Image

The thermal image (Figure 17) shows the circuit at an ambient temperature of 20°C with an input voltage of 12.0V and 0.15A load on the 15V output and 0.2A load on the 5V output.

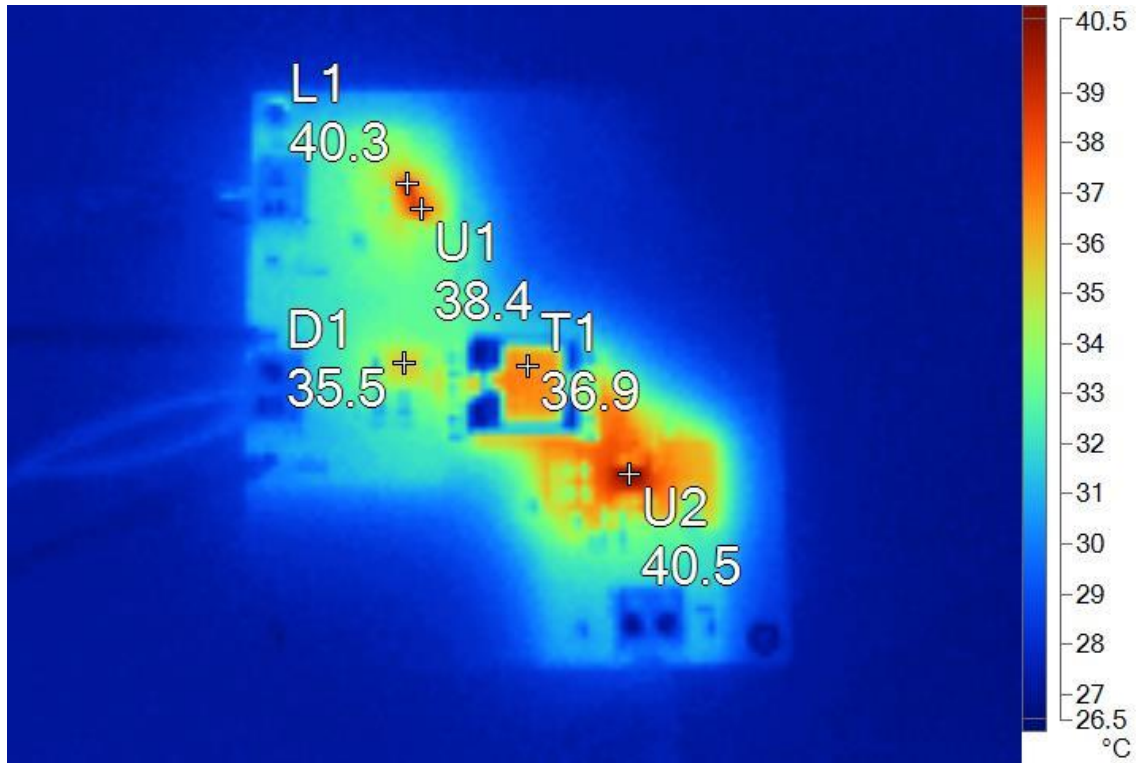


Figure 17



## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2017, Texas Instruments Incorporated