

Conserve Power With Simple LED Flasher



Literature Number: SNOA847

Technology Edge

Conserve Power With Simple LED Flasher
BY: Clayton B. Grantham, Test Engineer

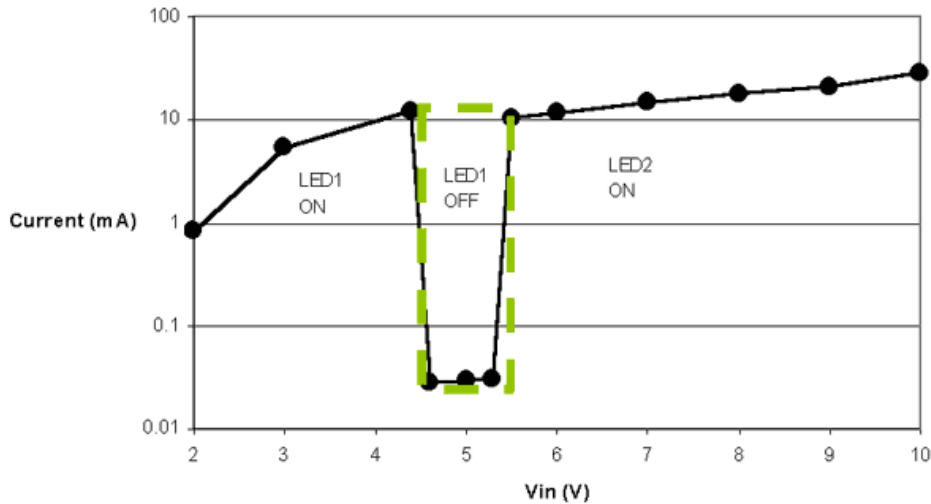


Figure 1. This 'power good' controller blinks the green LED1 ON, which results in less than 0.2 mA average current drain

The LED is a commonly used device that indicates when power is ON for most electronic devices. For the LED to produce discernible visible light in daylight the forward bias current needs to be in the moderate range (10mA-20mA). This amount of current may be too large in many low power designs. And, it results in wasted power when all that is needed in most cases is a once-in-a-while or on-demand indication that there is power to an electronic device. In figure 1, the supervisory circuit, LM3710, is configured to reduce the power consumption of a traditional LED indicator by 99%.

With Vin above 4.4V, the green LED1 blinks ON for 200ms and OFF for 25.6s, repetitively. IC1's reset timeout pulses the LED1 ON for 200ms. This 200ms ON period is customizable from 1.4ms to 1600ms from the factory. The LED1 OFF period is controlled by IC1's watchdog timeout period, which is also customizable from 6.2ms to 25.6s. The watchdog input monitors transitions at WDI; if there are no changes at WDI, then reset engages. The WDI in figure 1 is grounded to prevent a change. Thus the reset timeout and watchdog timeout form two one-shots that produce a repetitive pulse train. The 25.6s pause between the LED1 flashes can be short cycled by pressing the momentary switch, SW1. The average current in LED1 is reduced by the ratio of these two time periods, thereby providing immediate feedback of good power. A 13mA continuous bias current would be reduced to 0.1mA in average LED1 current. This is a power savings of 130X.

LED1's current is limited by IC1's RESET pin, which is approximately 13mA. The 28uA quiescent current of IC1 can be ignored. The approximate Vin set-point equation to initiate blinking is:

$$V_{in}(\text{blink}) = 3.08V + R1 * I_{\text{RESET}}. \quad (I_{\text{RESET}}=13\text{mA for } R1 < 200 \text{ ohm})$$


If Vin goes above 5.5V, the red LED2 illuminates as an over voltage indicator. The resistor divider of R2 and R3 and the PFI input of IC1 set this power fault level. IC1's PFI threshold voltage is 1.225V. This over-voltage condition causes PFO to drive LED2 continuously. The Vin set-point equation to initiate over-voltage is:

$$V_{in}(\text{over-voltage}) = 1.225V * (R2 + R3)/R3.$$

Any brief time before Vin reaches 4.4V, the LED1 is on continuously. Figure 2 shows the current-voltage waveform of the circuit.

Here are a couple of other examples. For a 5V±5% monitor set R1=121 ohm and R3=301 Kohm. For a 3.3V±10% monitor set R1=0 ohm and R3=511 Kohm. Remember the absolute maximum ratings of IC1 in your design.

You can add an optional capacitor, C1, to provide an energy reservoir that will increase the brightness of LED1's flash and its average current. You should select values in the microfarad range for a noticeable change.

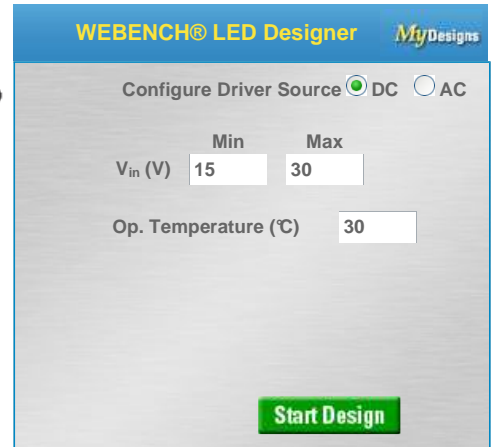

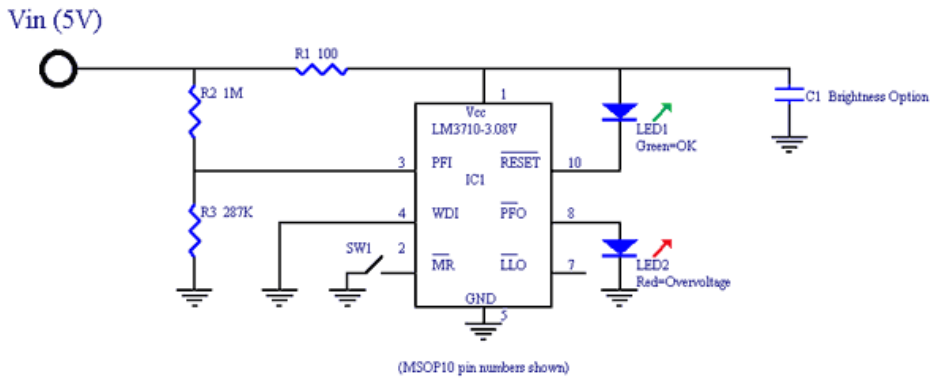


Figure 2. The average input current becomes very low for an input voltage from 4.5V to 5.5V

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated