



Summary of Control Architectures for LM and TPS Families of DC/DC Step- Down Regulators



Agenda

- Elements of the Control Loop
- Loop Compensation Basics
 - Compensation schemes
 - Power Stages of Linear Architectures
 - Bode Plots
- Linear Control Loop Architectures
- Non-Linear Control Loop Architectures
- Popular Devices and “Best to Use When” Summary

Note – Intermediate level

- This presentation is a summary to briefly highlight the differences and similarities of various control architectures.
- This presentation does not explain the art of loop compensation



Control Architecture Summary

Linear





- Voltage Mode
- Voltage Mode with Voltage Feed Forward
- Current Mode
- Emulated Current Mode

Non-Linear

- Hysteretic
- DCAP™ – Adaptive On-Time
- Constant ON Time (COT)
- DCAP-2™ – Adaptive On Time
- Constant On Time with Emulated Ripple Mode
- DCS™ (Direct Control w/ Seamless transition to Power Save Mode)



Circuit Block Elements of Loop Control

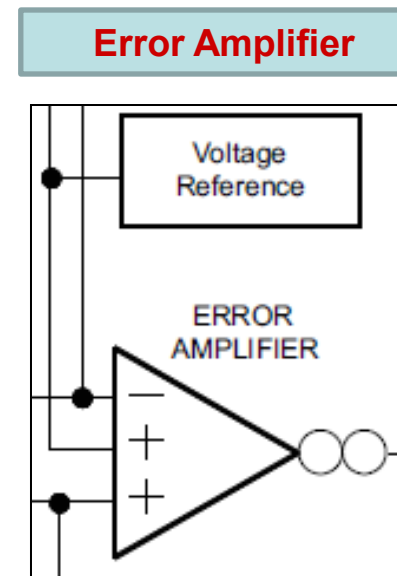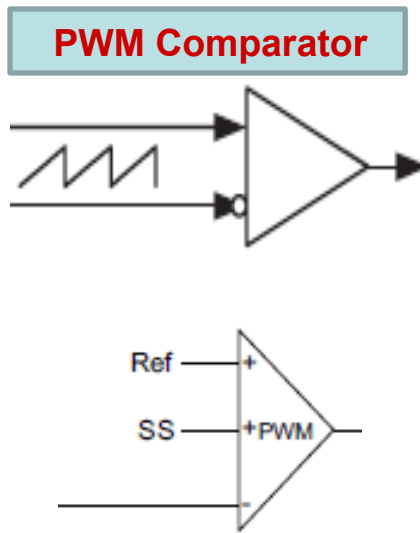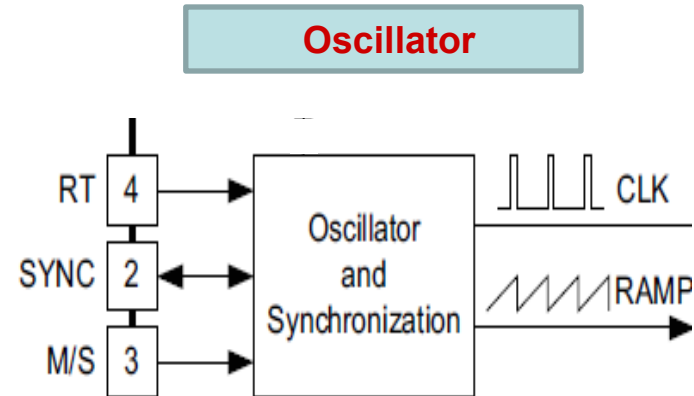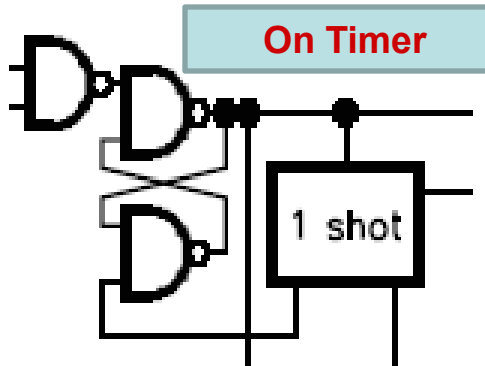




Control Architecture Summary

Linear Control Architectures

- Voltage Mode
- Voltage Mode with Voltage Feed Forward
- Current Mode
- Emulated Current Mode






Why do we Compensate?

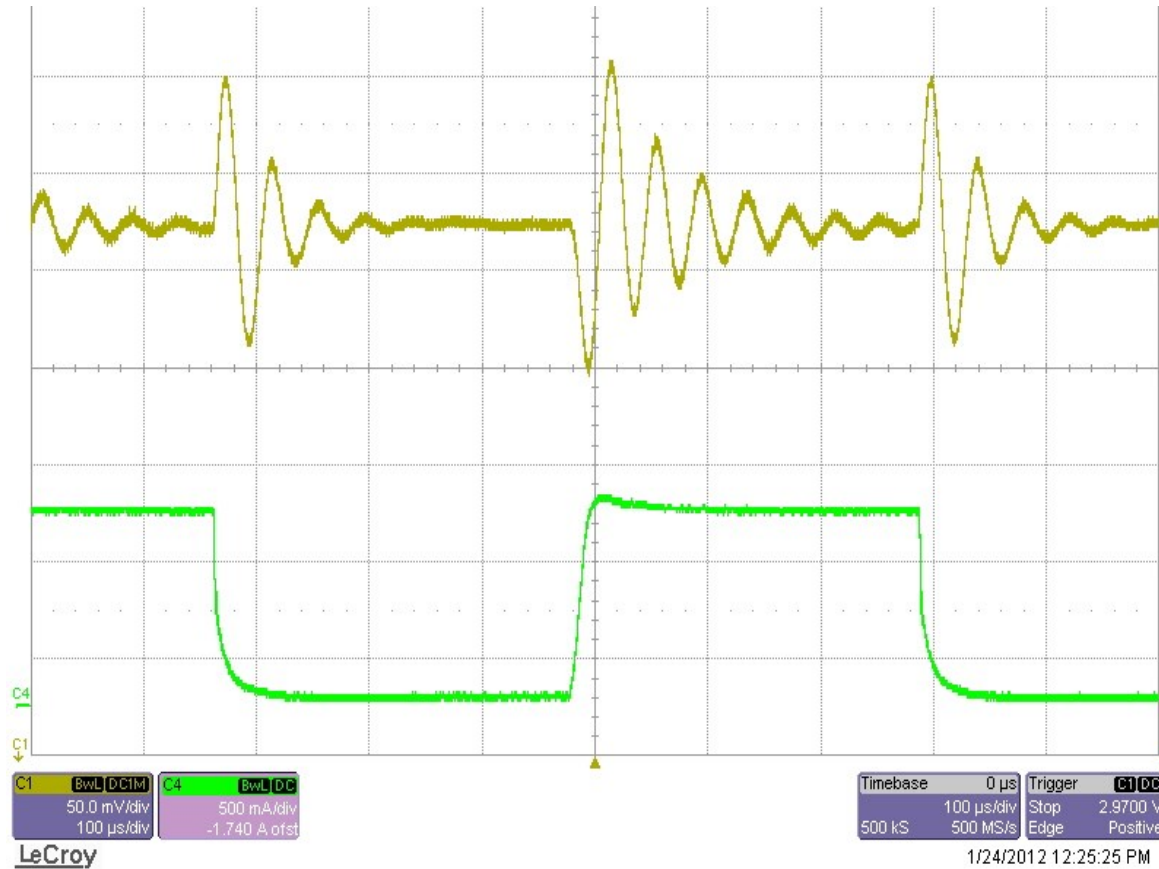



Type 1 Compensation

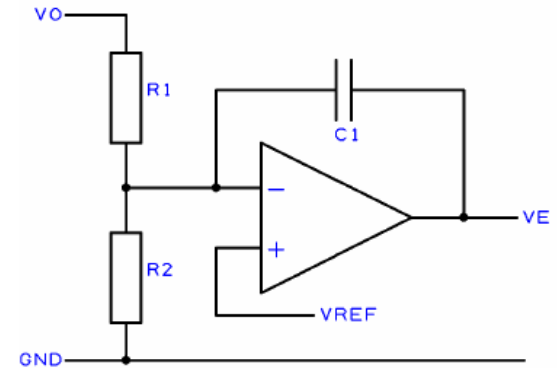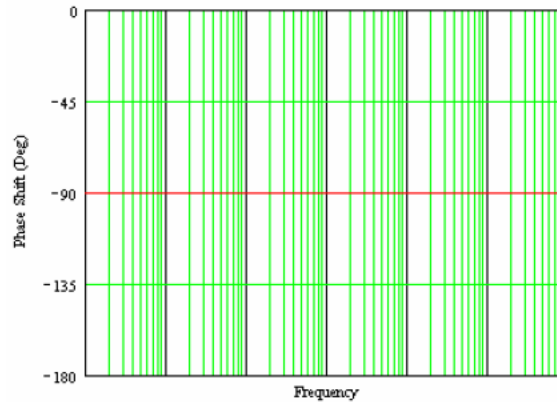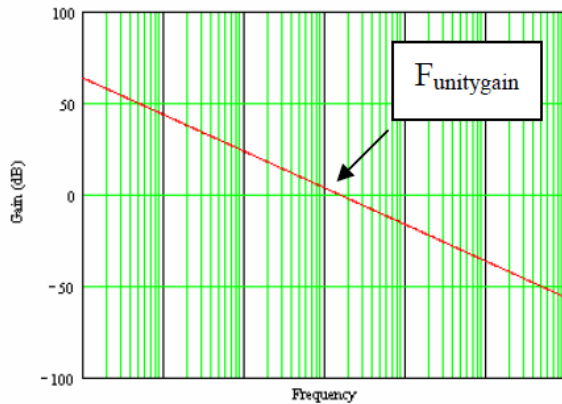




Slope is -20dB/decade

Type 1 Compensation (Dominant Pole Compensation)

- Minimum number of external components to get needed phase margin
- Adjust phase margin by choosing unity gain cross over frequency
- Poor transient response time since cross-over frequency is low
- Good load regulation due to high DC gain.
- Gain falls at a uniform -20dB per decade and phase is shifted by 90°
- Useful for troubleshooting - easy to stabilize by making C_1 big enough.



Type 2 Compensation

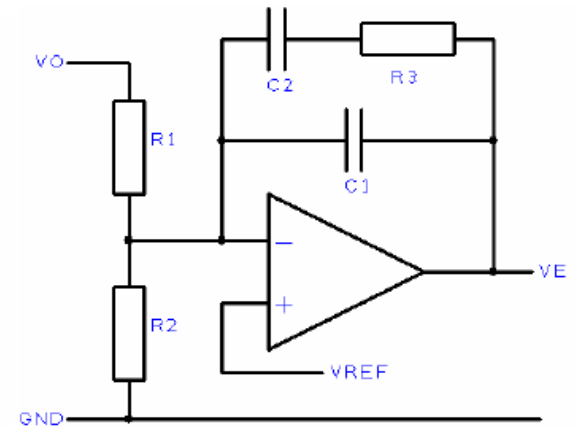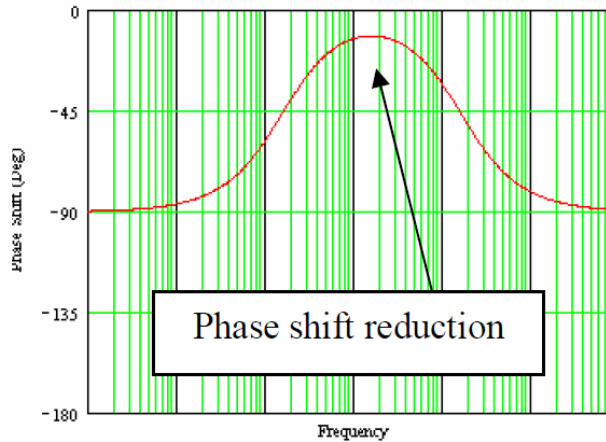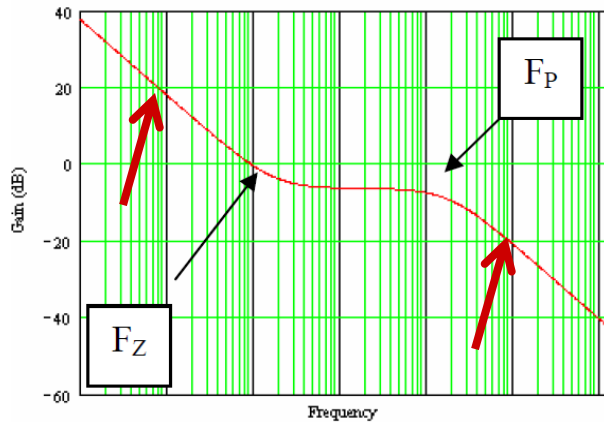


Slope is -20dB/decade

Type 2 Compensation



- A zero is added to cancel the low frequency dominate pole of the power stage
- A pole is added to cancel the ESR zero of the output capacitor
- Reduces compensation network phase shift at cross-over frequency
- Allows for higher cross-over frequency than type 1 – Better transient response
- Useful in Current Mode controlled buck converters
- Gives 180 degrees of phase shift at the peak



Type 3 Compensation

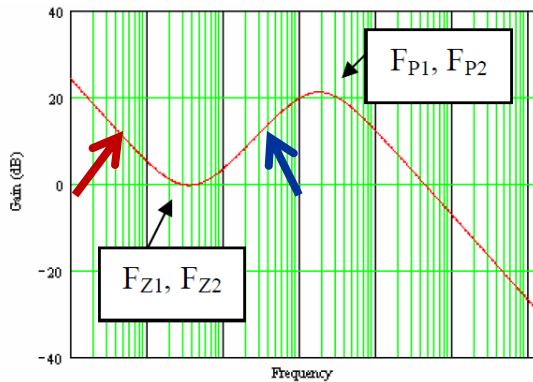

-20dB/decade
20dB/decade

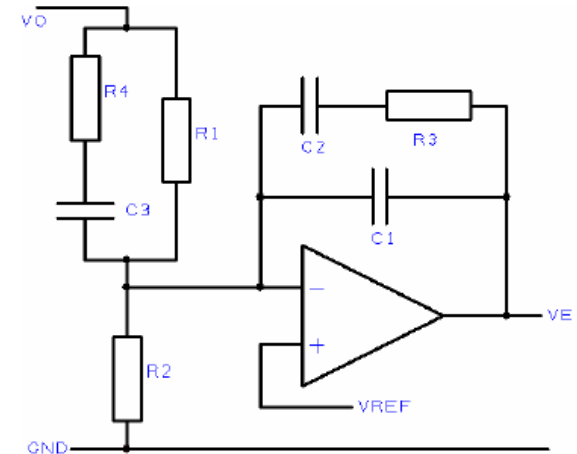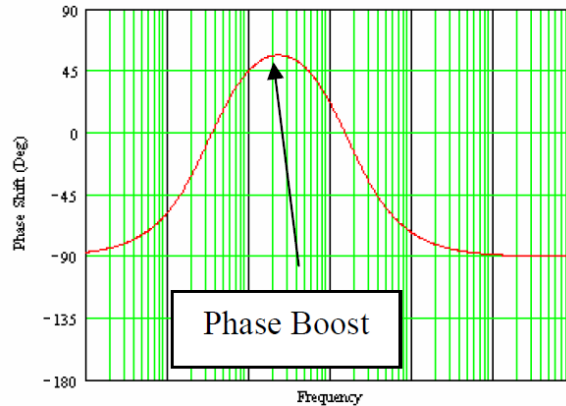



Type 3 Compensation

- More external components required
- Adds another pole and zero to type 2 for enhancement and provides another 90° phase boost (270 degrees total) for a higher cross-over frequency
- Useful in Voltage Mode controlled buck converters (-40dB / decade roll off above the poles of the output filter and -180° phase shift)





Voltage and Current Mode Power Stages

Voltage Mode

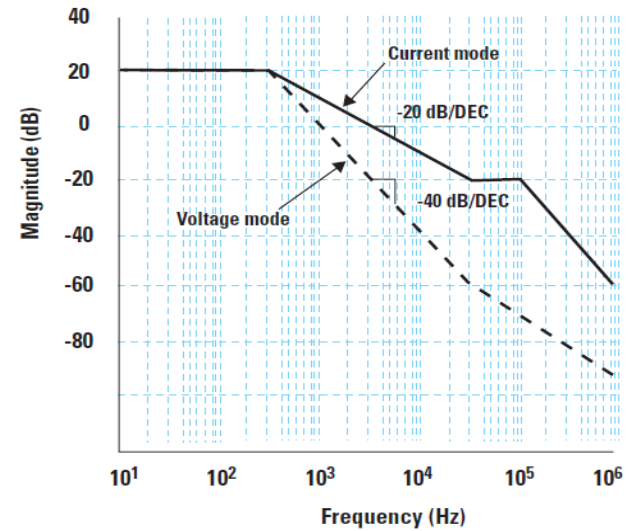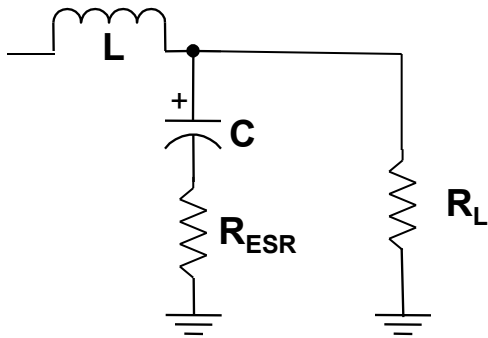


Current Mode

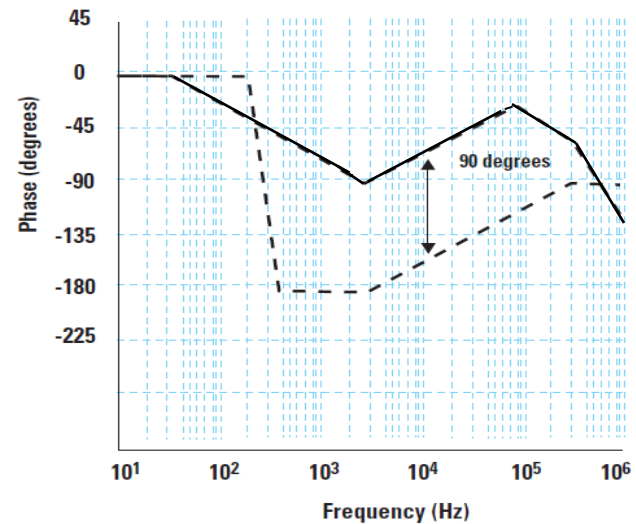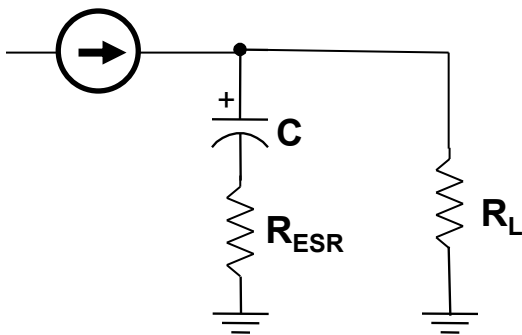



Basic Stability Criterion Example

Loop Response Graph

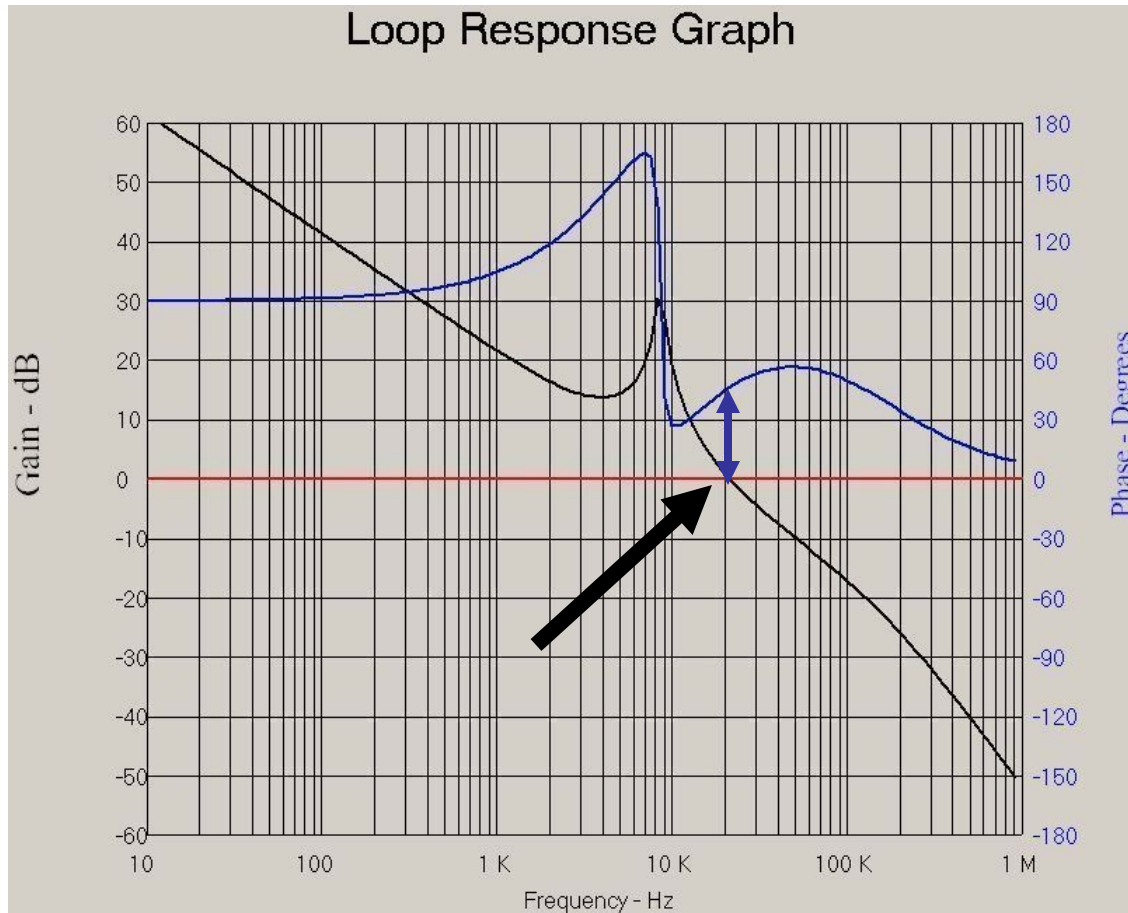


Reading Bode Plot

- 1) Find Cross Over Frequency at 0dB
 - 21 kHz Cross Over
- 2) Find Phase Margin at the Cross Over Frequency
 - 45° at 21kHz
- 3) Goal is to have Phase Margin in between 45° and 90° to maintained a well-damped transient response



Bode Plot Example

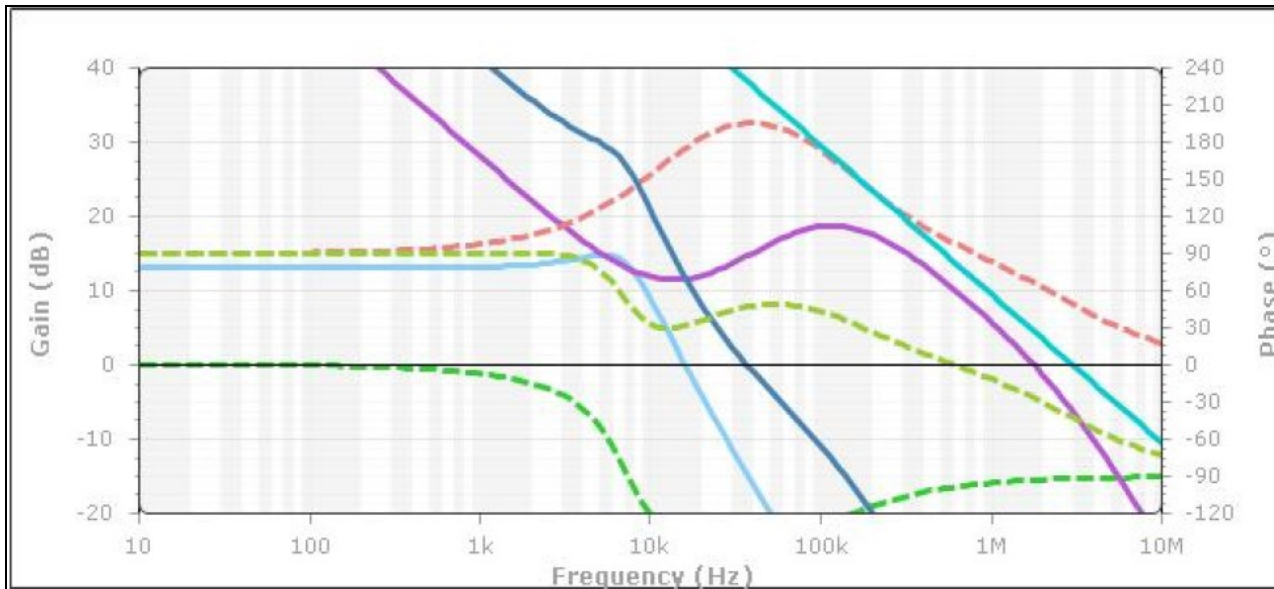

— Power Stage Gain
- - - Power Stage Phase
— Compensation Gain
- - - Compensation Phase
— Error Amp Gain
— Total Gain
- - - Total Phase



Cross Over – 37kHz
LC Corner – 6kHz
ESR Zero – 95kHz
Phase Margin - 47°

When in dB, $\log A + \log B = \log(A \times B)$ & $\log C - \log D = \log(C/D)$

- Start with the Power Stage gain and phase. What's the Control Mode?
- Add the Compensation gain to Power Stage gain to get Total Gain
- Add the Compensation phase to Power Stage phase to get Total Phase



Voltage Mode Control

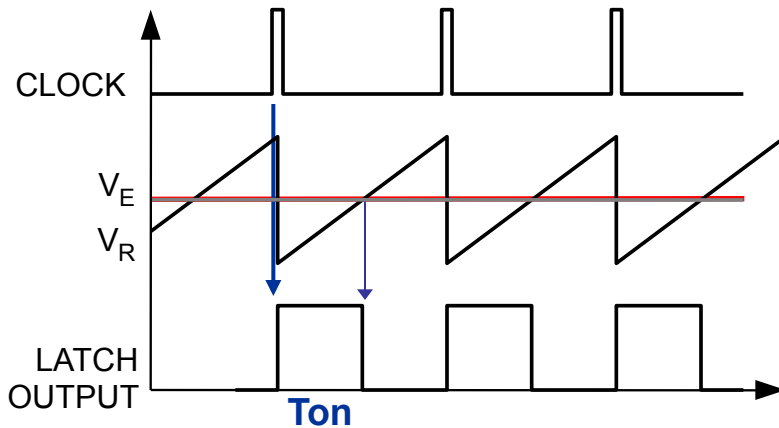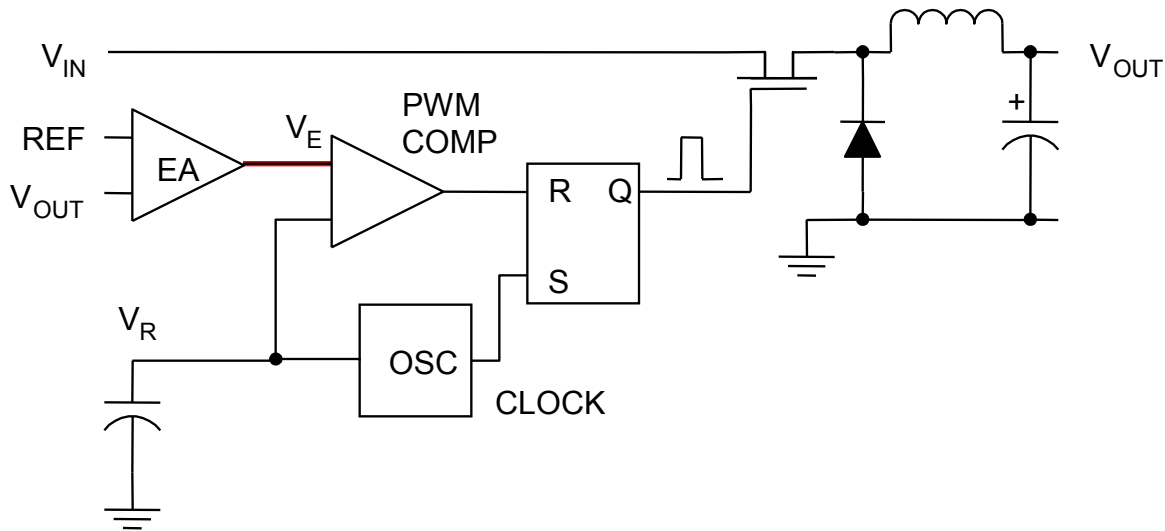

ADVANTAGES



- Single feedback loop
- Good noise margin
- Voltage regulation is independent of current

DISADVANTAGES

- High BW EA required
- More difficult double-pole compensation
- Output caps affect compensation
- V_{IN} affects loop gain



Voltage Mode w/ Voltage Feed-Forward

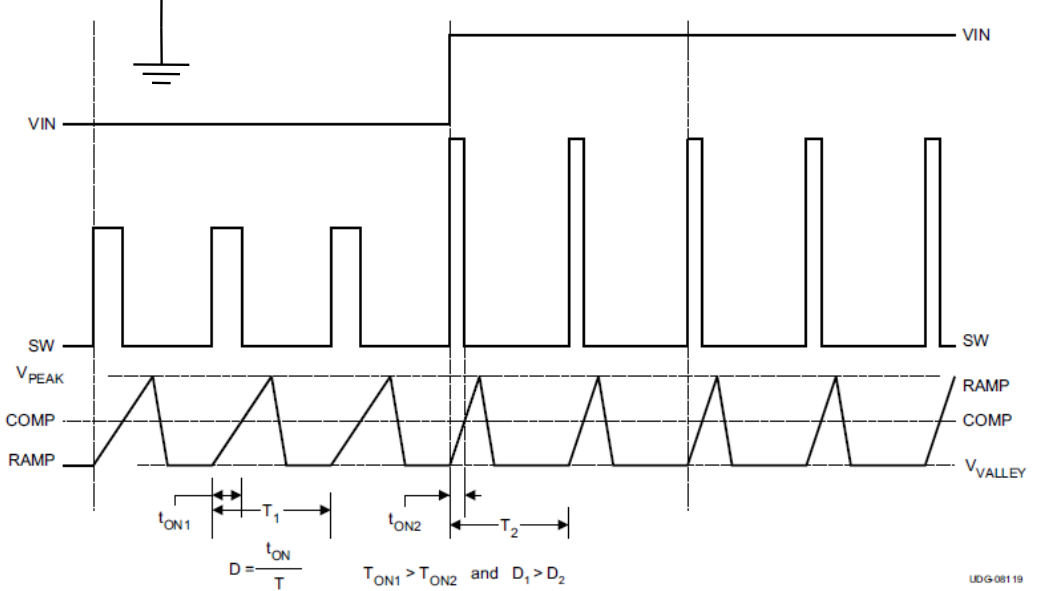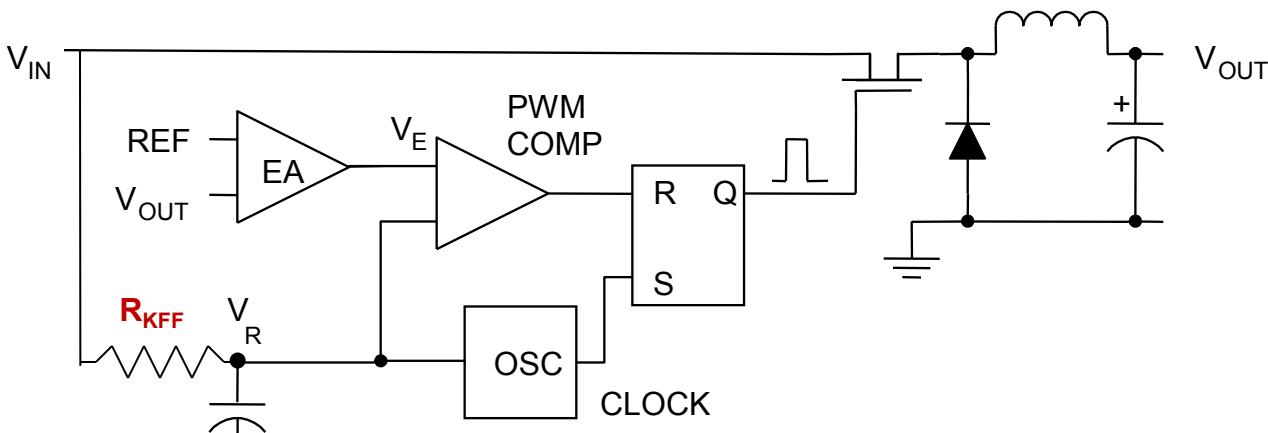



Ramp Generator Circuit

- Varies the PWM ramp with line voltage
- Maintains constant ramp magnitude
- Excellent response to line variations
- PWM does not have to wait for loop delays to change the duty cycle
- **Useful when input voltage varies**

UDG-08119



Current Mode Control

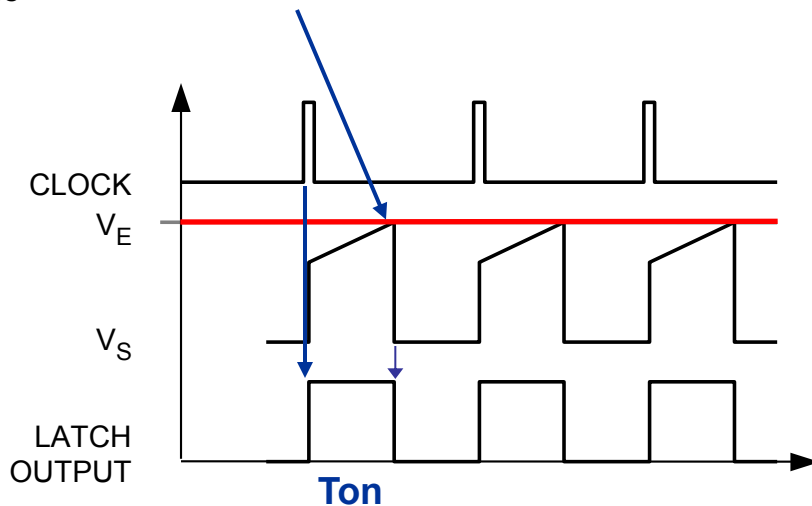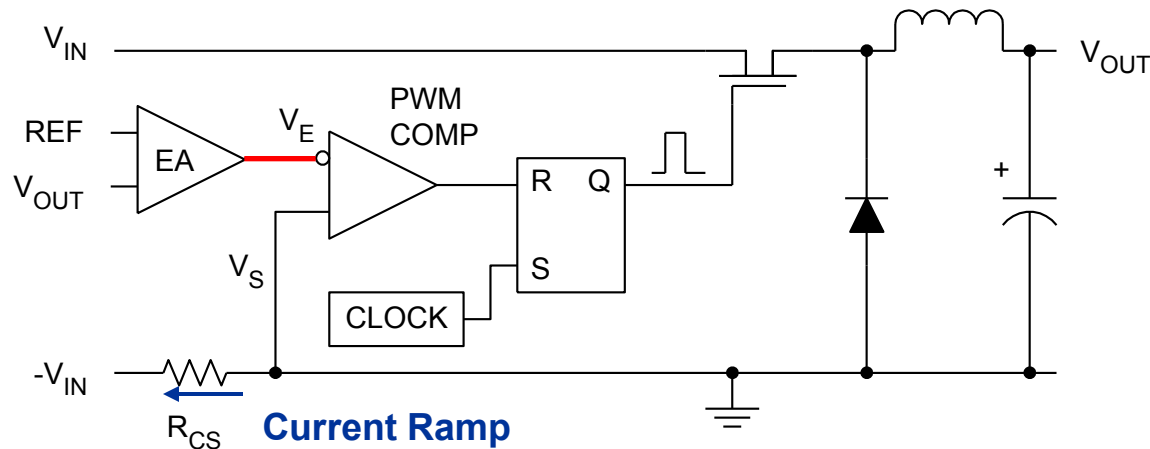

ADVANTAGES

- Fast response to output current changes
- Single-pole compensation
- Inherent current limiting
- Inherent feed forward
- Multiple phase current sharing possible


DISADVANTAGES

- Two feedback loops if a current amplifier is used
- Need for slope compensation
- Current limit “tail”
- Noise sensitivity due to leading edge current spike




Current Mode Leading Edge Spike

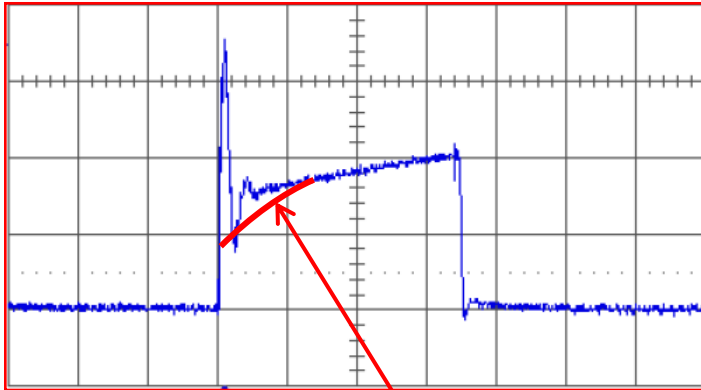Filter out the leading edge spike with a RC filter




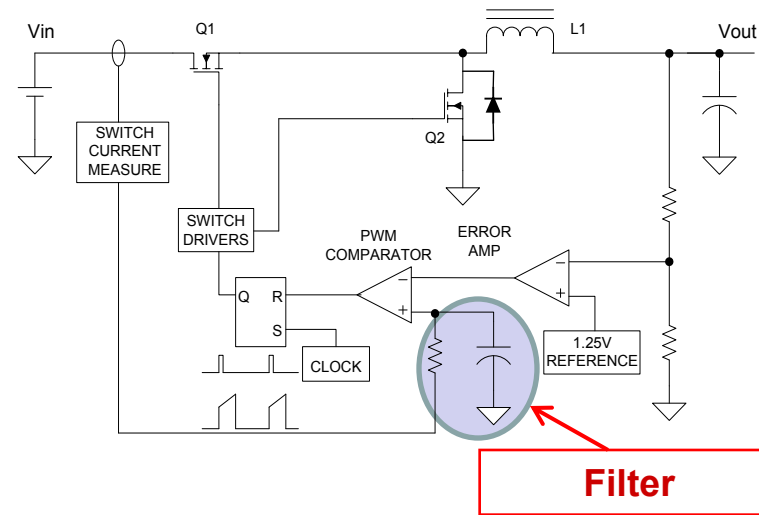Waveform Distortion is a problem for small duty cycles



Use leading edge blanking

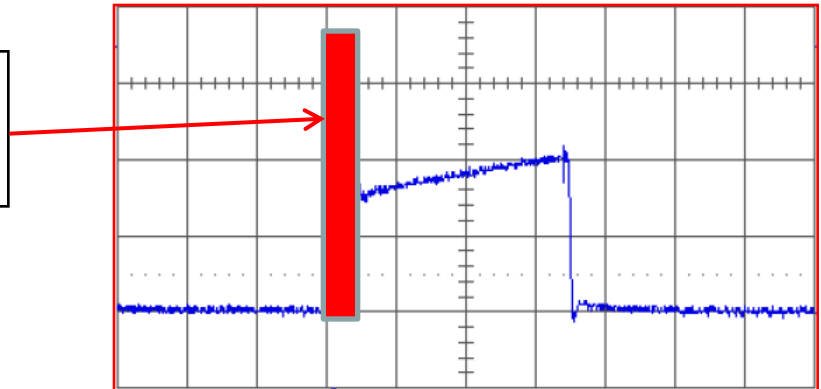This portion of the duty cycle is un-available Precludes narrow pulses (high Vin to Vout ratios)






Emulated Current Mode Control

Sample and Hold

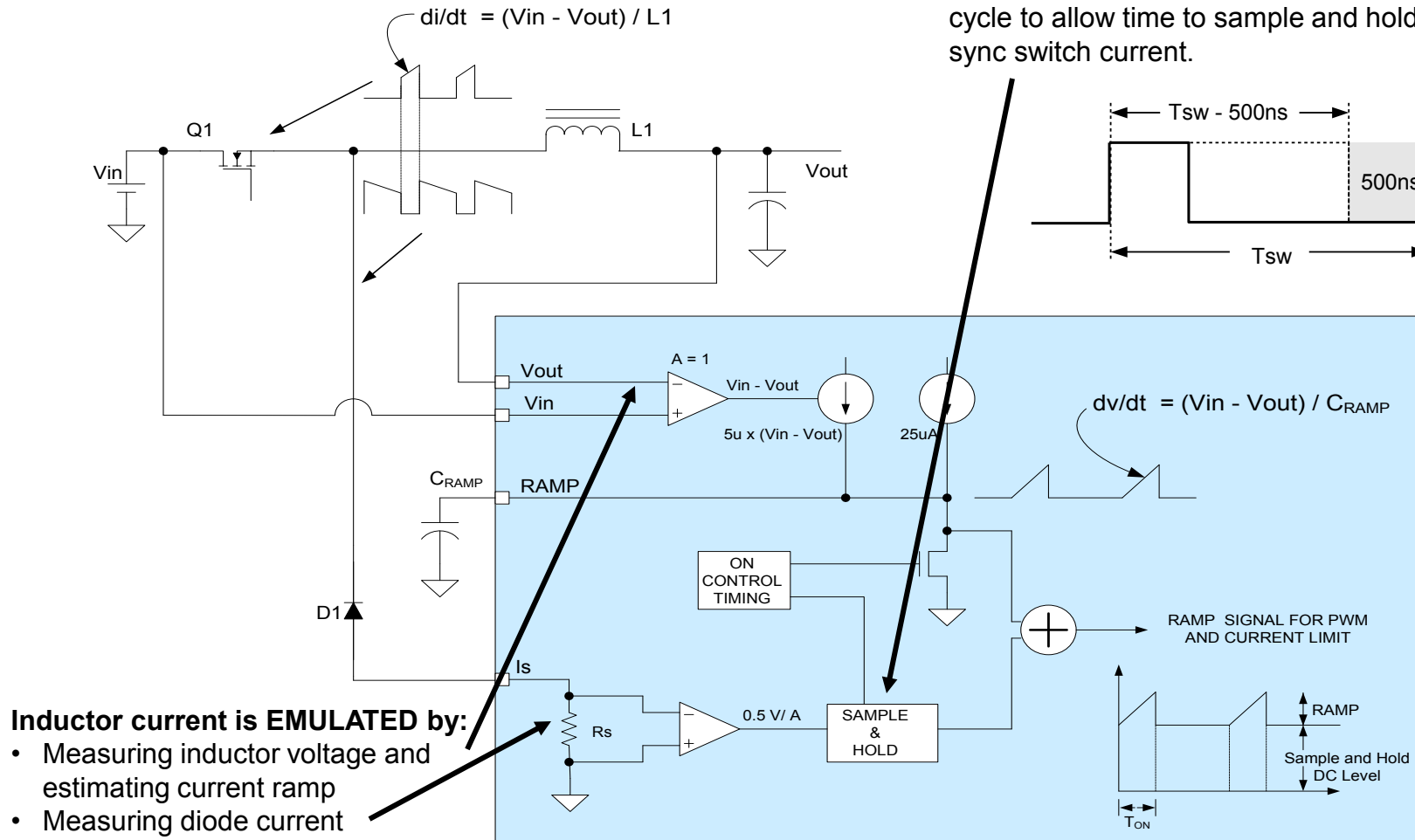- A forced off-time of 500ns is implemented each cycle to allow time to sample and hold diode or sync switch current.






Emulated Current Mode

Advantages

- Eliminates the leading edge spike
 - Allows much smaller duty cycles
 - Eliminates false triggering
- Ensures a clean current waveform when operating near the minimum on-time.
- The low current noise problem is much improved
 - Less need for a minimum load
- All the other advantages of current mode control remain

Disadvantages

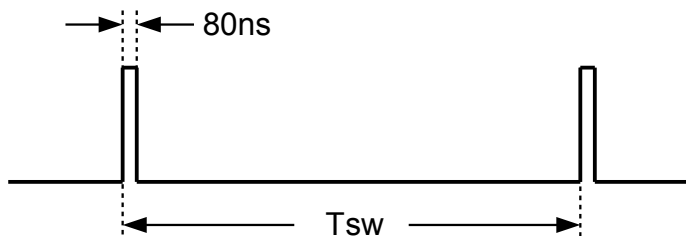- Maximum frequency and duty cycle is limited
 - Forced off-time is fixed and becomes a higher % of switching period
 - Less % of on-time is available at high frequency
 - Forced off-time of ~500ns needed for Sample and Hold current sensing circuit






Non- Linear Control Architectures

- Hysteretic
- Constant On Time (COT)
- COT with Emulated Ripple Mode
- D-CAPTM (Adaptive On Time)
- D-CAP2TM
- DCSTM (Direct Control w/ Seamless transition to Power Save Mode)




Hysteretic Control Scheme

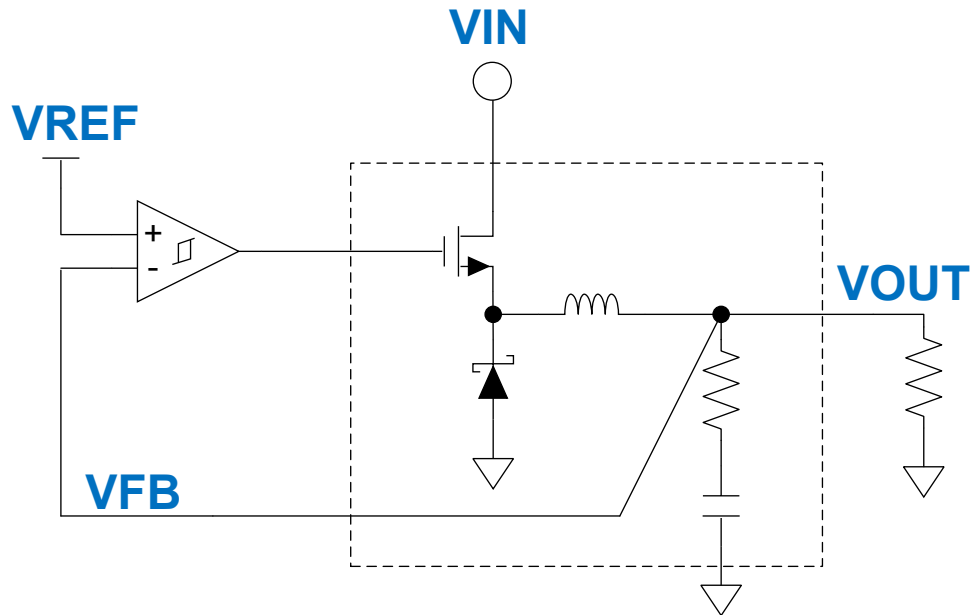

TON - Terminated by $V_{FB} > V_{REF (HIGH)}$

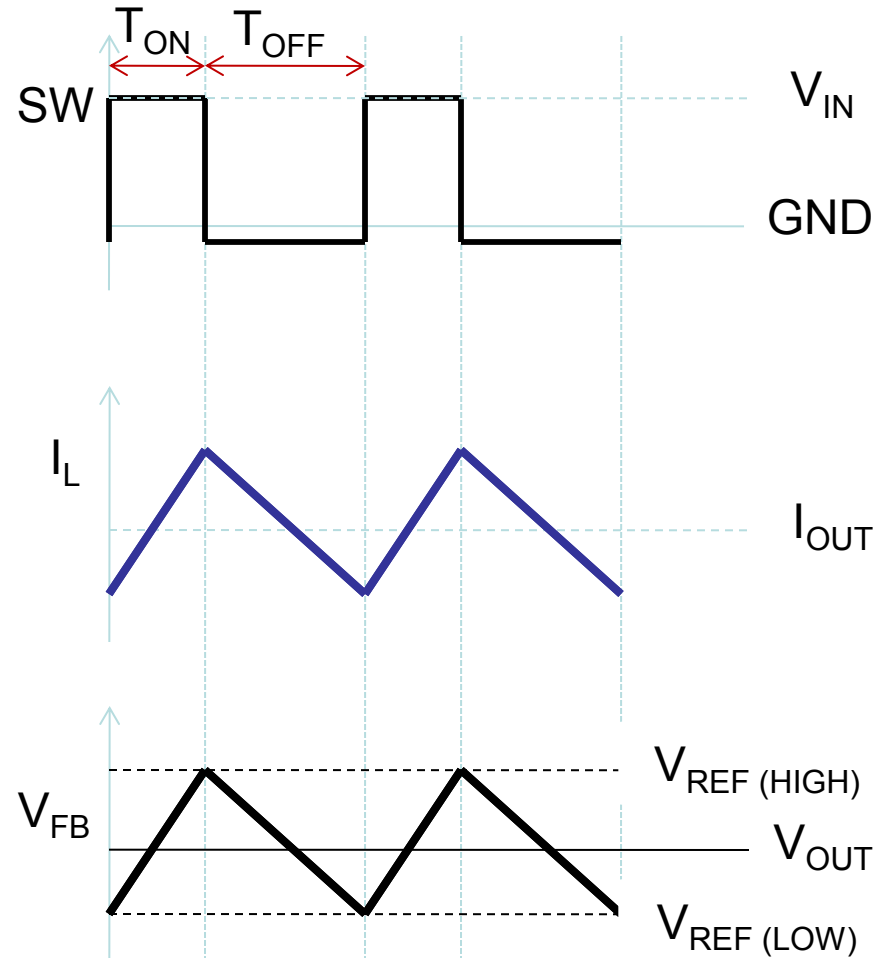TOFF - Terminated by $V_{FB} < V_{REF (LOW)}$





Hysteretic Control

ADVANTAGES



- Simple controls - bang/bang system
- No loop compensation
- Fastest response to load changes

DISADVANTAGES

- Variable switching frequency
- Needs protection against magnetic saturation
- Requires some output ripple - ESR
- Sensitive to output noise
- Circuit delays limit maximum frequency



Constant-On-Time (COT)

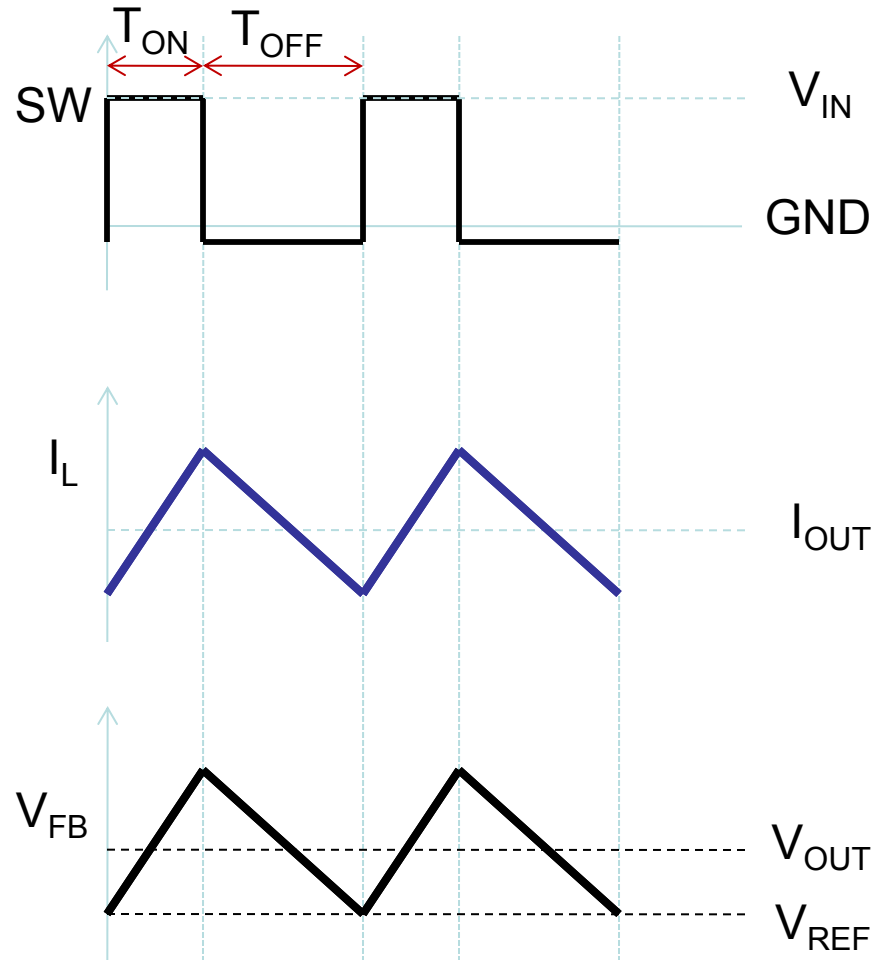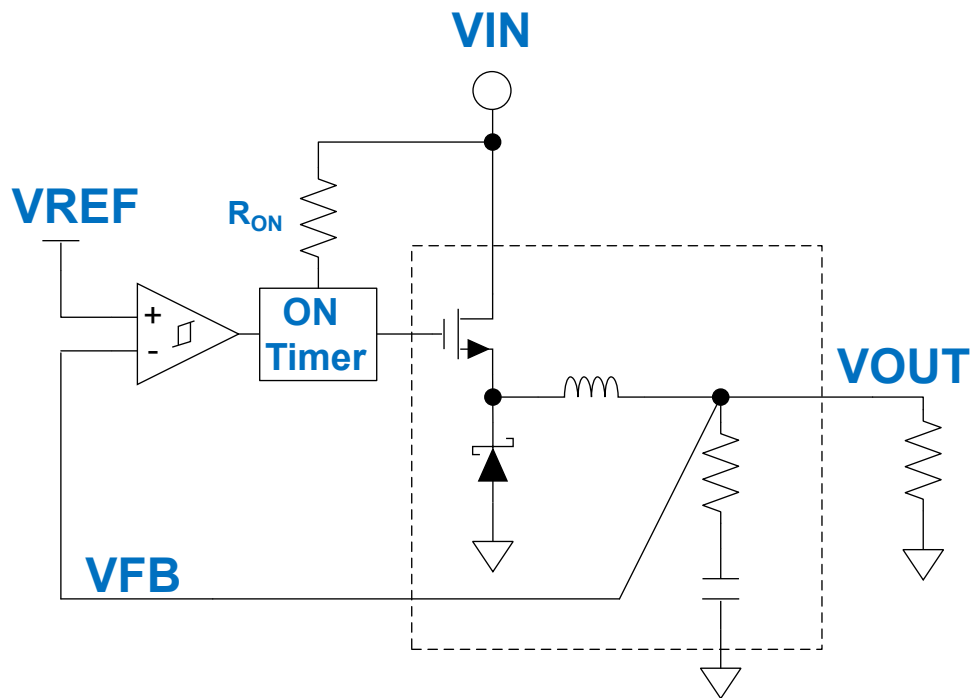



TON - Terminated by On-Timer

TOFF - Terminated by $V_{FB} < V_{REF}$



COT Fast Transient Response

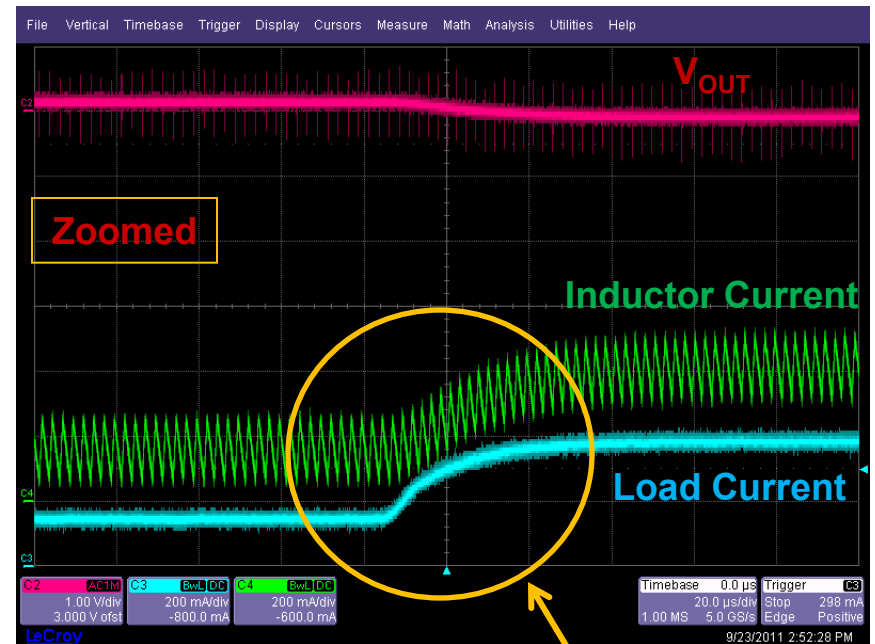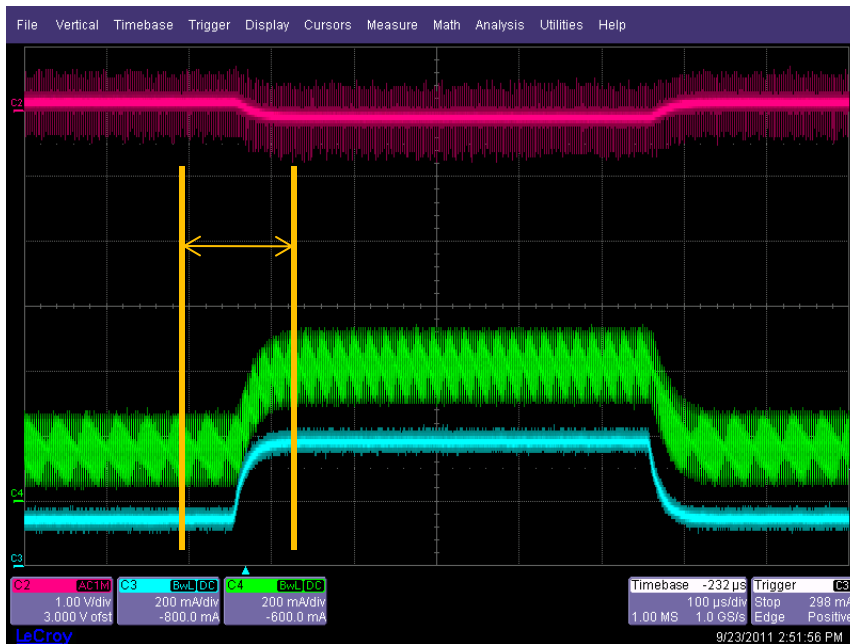
- COTs have no error amplifier and compensation to limit the bandwidth
- This results in very fast response to load/line transients.



Fast Response




COT Ripple Requirement

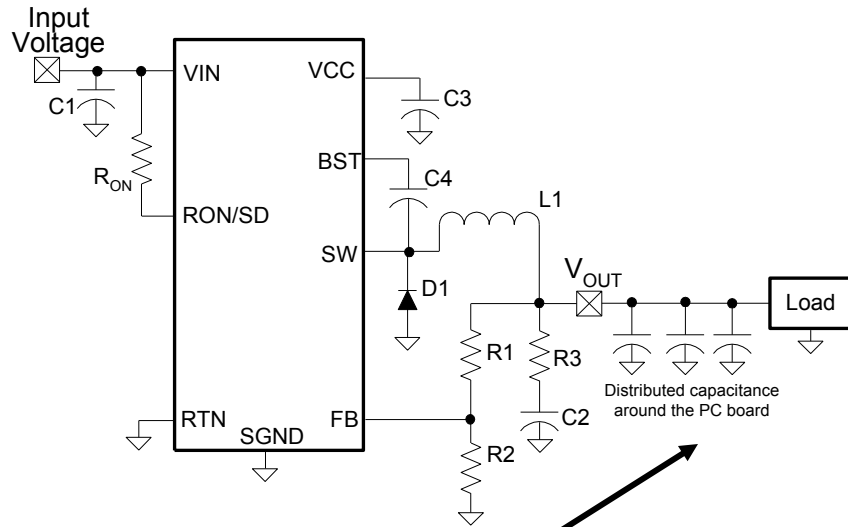

A BIG NO-NO!

However.....

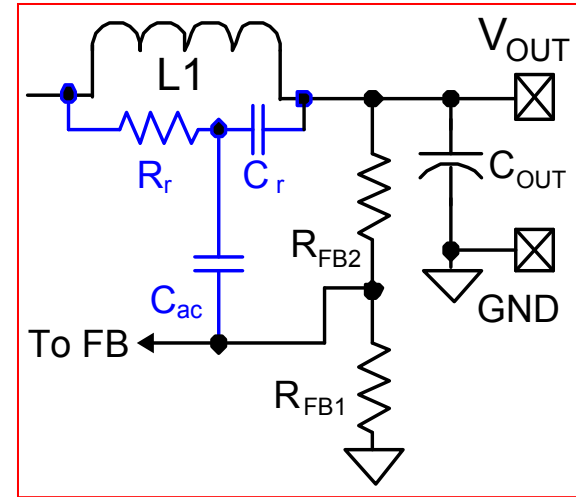


An external ripple injection circuit can be used to help generate a new on pulse



COT w/ Emulated Ripple Mode (ERM)

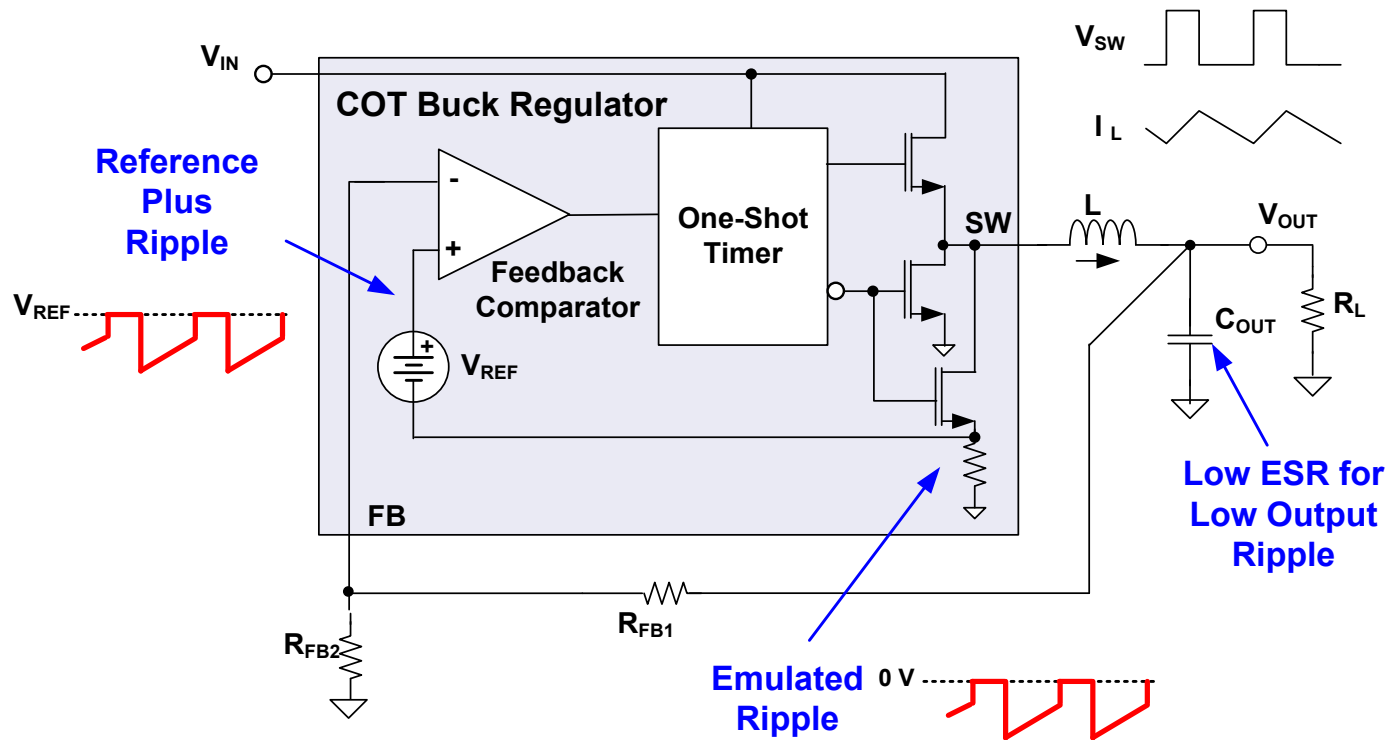- **Patented ERM technology satisfies ripple requirements of COT control:**
 - Emulated Ripple is coupled internally to feedback comparator from low-side switch of buck power stage
 - No ripple required at regulator output (clean V_{OUT})





COT Advantages and Disadvantages

Advantages



- Simple design
- No compensation required
- Excellent transient response
- Works for high step-down ratios
- Minimizes frequency shift compared to hysteretic

Disadvantages

- Requires ripple at feedback node for stability (ESR)
 - ERM or injection circuit solves this
- No oscillator for fixed frequency (or Synchronizable) operation
- Sensitive to output noise as it translates to feedback ripple



D-CAP™ Mode (Adaptive On-time)

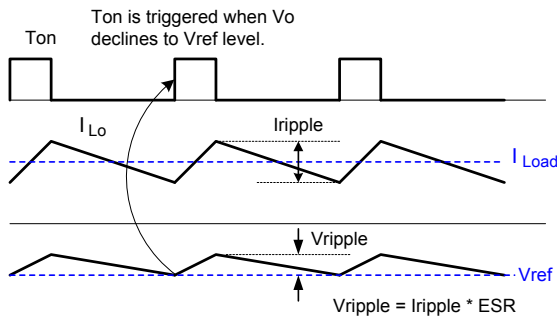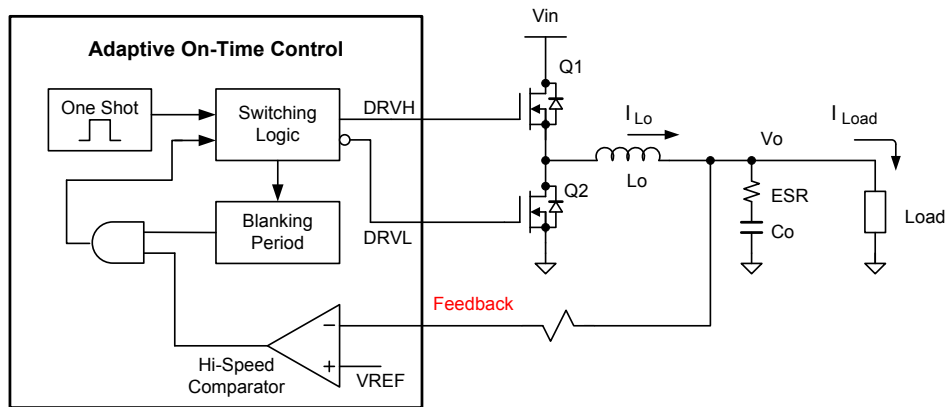

ADVANTAGES

- No loop compensation
- Fastest response to load changes

DISADVANTAGES


- Quasi fixed switching frequency
- Output voltage has a ripple component
- Ton and T jitter is expected, with smaller L and C
- Requires some output ripple (ESR)
- Sensitive to output noise

Direct Connect to the Capacitor (D-CAP)


- Each Ton pulse duration is calculated based upon V_{in} , V_{out} , nominal f_{out}
- Each time the falling feed-back voltage equals V_{ref} , a new ON pulse is generated
- There is no loop lag time. Pulse by pulse adjustment, comparator and the 'one shot block' lag are smaller



Compared Transient Response

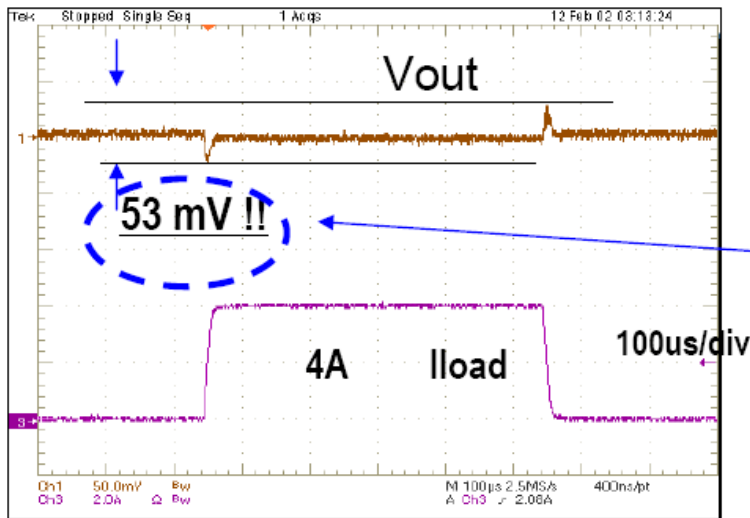

D-cap mode transient response

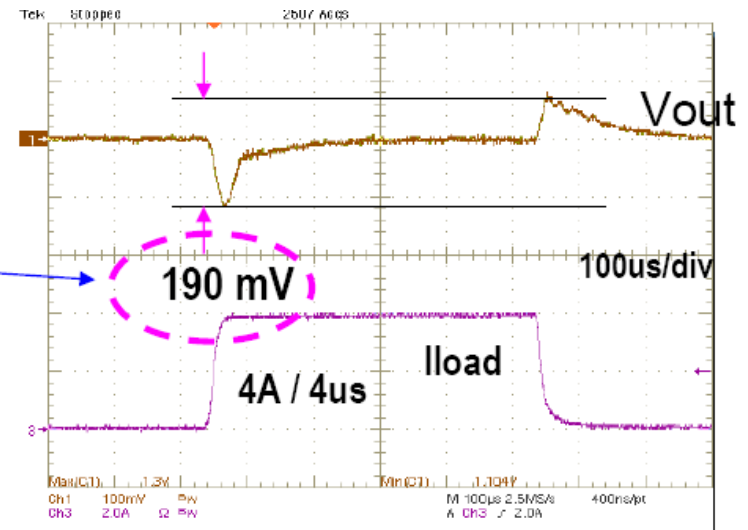

Voltage mode transient response

$C_{out}=22\mu F \times 3$




$C_{out}=100\mu F \times 4$



D-CAP2™ Control Mode

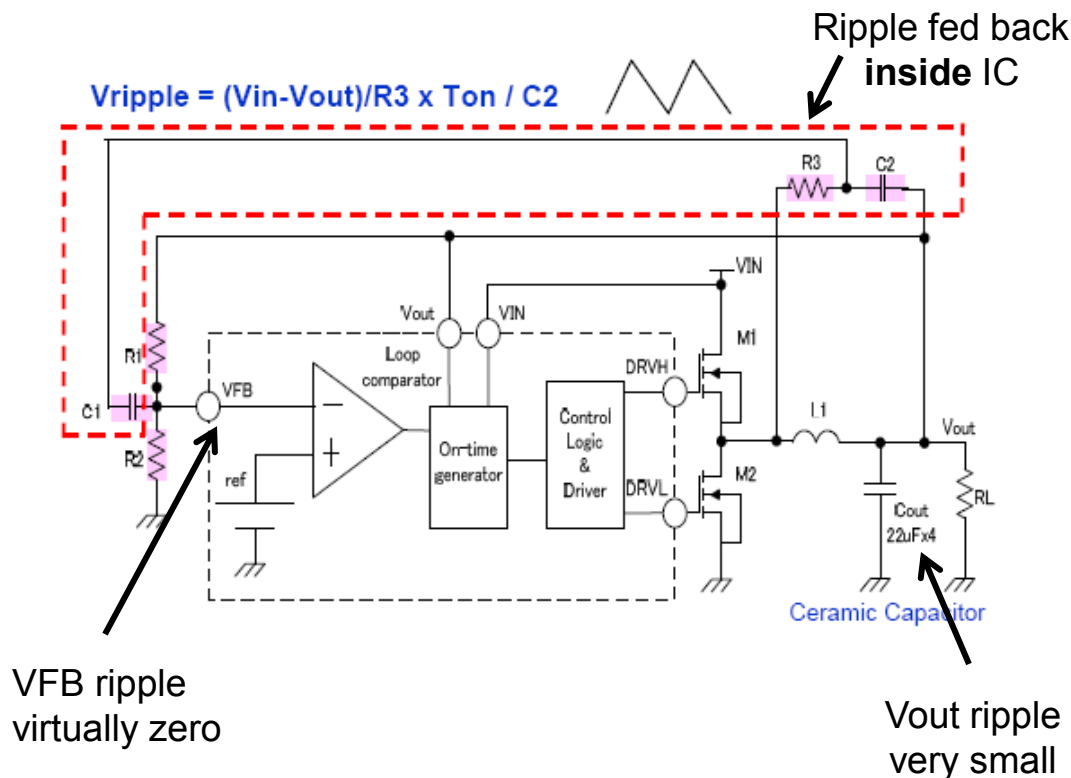Basically, D-CAP2™ is D-CAP™ plus **internal** ripple injection allowing for output ceramic capacitors use without added components




Advantages over DCAP

- Use when ceramic output caps are required: Less jitter but output voltage accuracy is degraded by emulated current information.




Constant versus Adaptive On-Time


10Vin, 5Vout, 1MHz

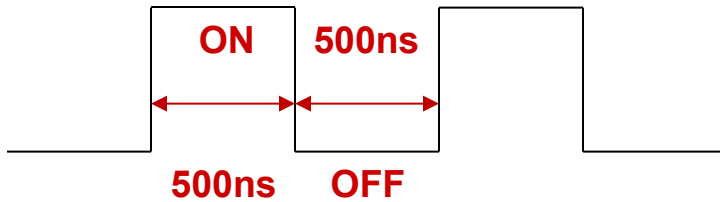


10Vin, 5Vout, 1MHz

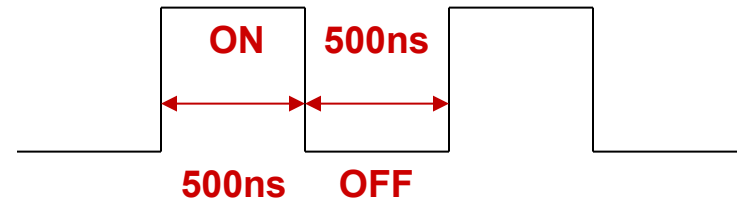

10Vin, 2.5Vout, 500kHz

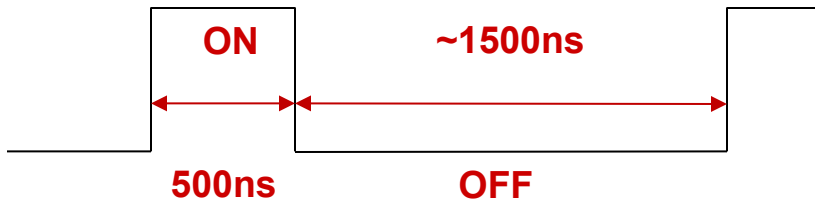

10Vin, 2.5Vout, 1MHz

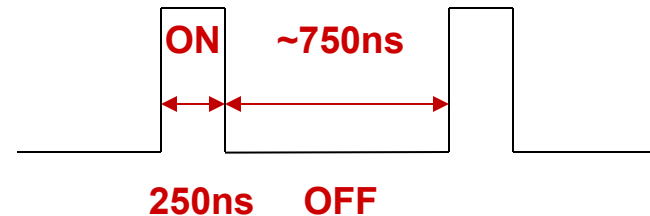

Constant On Time (COT)

- On Time is Fixed
- Off Time is Hysteretic
- Frequency Varies with V_{in} , V_{out} , and I_{out} (slightly)

Adaptive On Time (D-CAP)


- On Time is function of V_{in} , V_{out}
- Off Time is Hysteretic
- Frequency less variable than COT since On-Time is dynamic with V_{in} , V_{out} , & I_{out}

Adaptive On-Time allows control of the switching frequency



DCS-Control™

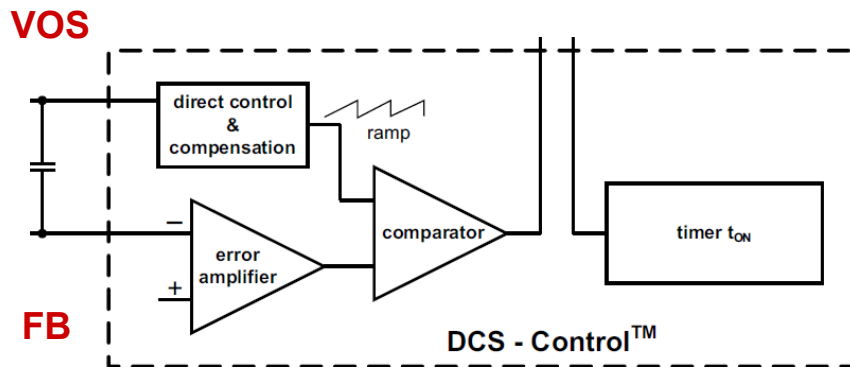Proprietary Ramp Circuitry Feeds VOS (Vout) to Comparator



- **Feed Forward Capacitor Required for PFM Mode Performance**
- **Error Amplifier for Precise DC Regulation**
- **Hysteretic Comparator for Fast Response to Changes in Output Voltage**
- **On Timer for PFM mode and Constant Operating Frequency**

Advantages

- Fast transient response by direct path to output voltage (VOS).
- Additional Voltage mode loop for high dc accuracy (FB).
- Seamless transition between PWM and Power Save Mode (single building block – no switch, no glitch).
- Supports low ESR output caps.



Disadvantages

- Frequency variation at extreme duty cycles
- Forced PWM mode at high duty cycles



DCS Performance

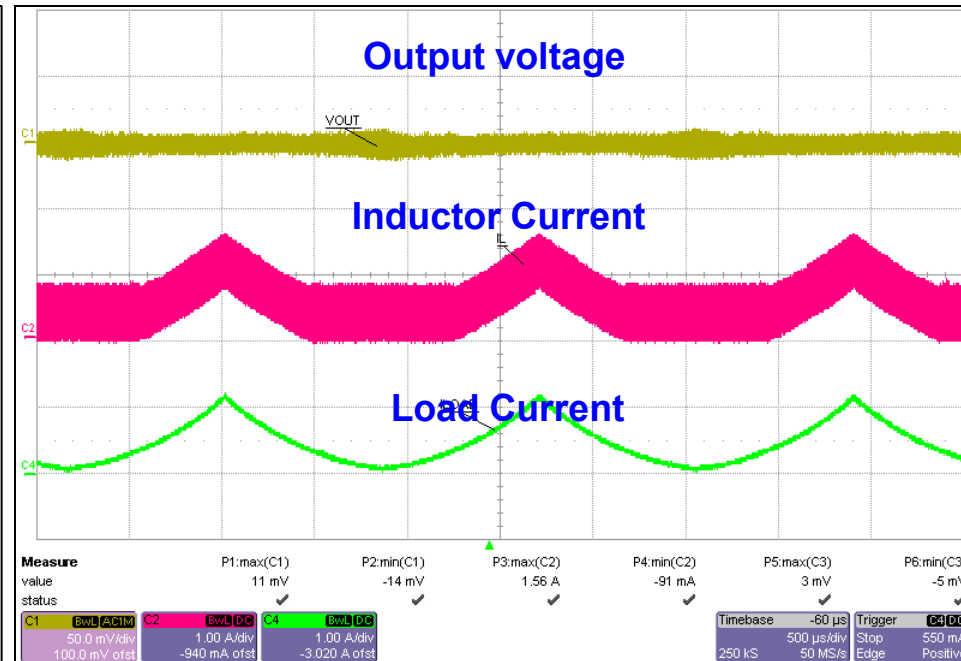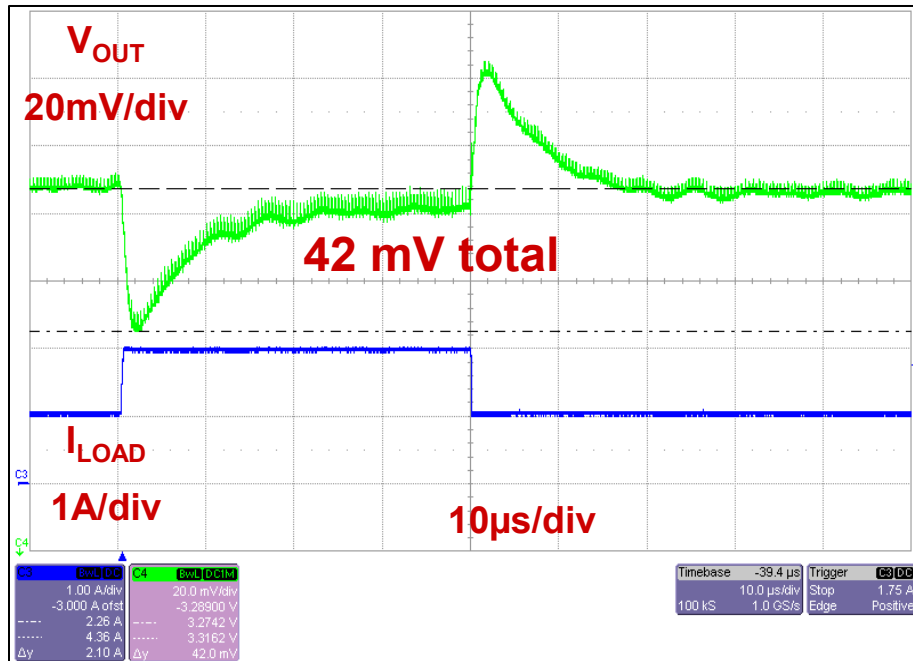CH1 – VOUT @ 50mV/div
CH2 – IL @ 1A/div
CH3 – ILOAD @ 1A/div



12V to 3.3V, 1A to 2A step with 2.2µH and 22µF

No disturbing bursts during the transition between PWM and Power Save Mode



Popular Devices

Voltage Mode

- LM2267x , TPS5430, LM21215, TPS54610, LM285x

Voltage Mode with Voltage Feed Forward

- TPS40170, TPS4005x, TPS56221, TPS40400

Current Mode

- TPS54620, TPS54160, LM21305, TPS54618

Emulated Current Mode

- LM557x, LM2557x, LM5005, LM5117, LM5116, LM5119

Hysteretic

- LM5007, LM3485, LM3475

DCAP – Adaptive On-Time

- TPS51124, TPS51216, TPS53355, TPS53219

Constant ON Time

- LM2501x, LM5006, LM5007/8/9, LM310x

DCAP2 – Adaptive On Time

- TPS54327/8, TPS54527/8, TPS53114, TPS5312x

Constant On Time with Emulated Ripple Mode

- LM315x, LM310x, LM25011

DCS (Direct Control w/ Seamless transition to Power Save Mode)

- TPS62230, TPS62120/30/40/50



High Level “Best to Use When” Summary

Voltage Mode

- Use when synchronized / fixed switching frequency is needed. Better for higher duty cycles than current mode.

Voltage Mode with Voltage Feed Forward

- Input Voltage changes – Useful in Automotive, Battery Back up.

Current Mode

- Synchronized / fixed switching frequency is needed with lower parts count. Fast transient response when fixed frequency is needed.

Emulated Current Mode

- Low duty cycles versus traditional current mode, without current noise susceptibility.

Hysteretic

- Low cost – Few parts count. Fast transient response. Frequency not critical.

DCAP, Constant On Time

- Fast transient response when using POSCAP or medium ESR Cout, reduced parts count.

DCAP2, Constant On Time with Emulated Ripple Mode

- Fast transient response when using ceramic cap. Reduced parts count.

DCS (Direct Control w/ Seamless transition to Power Save Mode)

- Light load efficiency is needed, fast transient response, reduced parts count.



Thank You!