



# Switching Power Supply Component Selection


## 7.1d Capacitor Selection – High Frequency Ripple

# Source of High Frequency Output Noise



- Parasitic capacitance of the inductor couples high frequency noise onto the parasitic inductance of the output capacitor.

## Buck Low Pass Filter

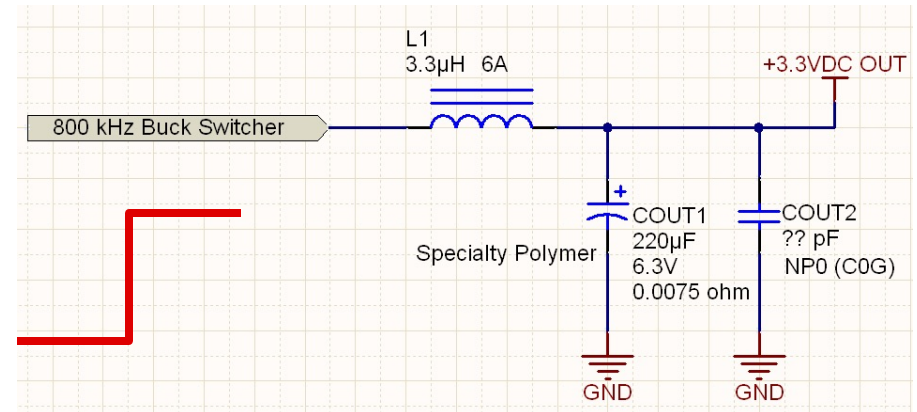


Switching  
Transition

# Ideal capacitor compared to actual capacitor




You buy this

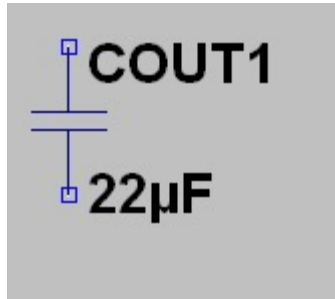

22uF 4V X5R 0603 Ceramic

You get this

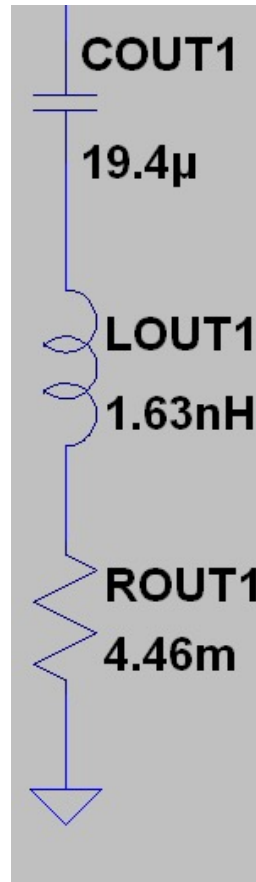

Voltage and Temperature  
De-rated Capacitance

(ESL)

Effective Series Inductance

- Parasitic inductance term -

(ESR)

Effective Series Resistance


- Parasitic resistance term -

Buy one part – Get three for the price of one!
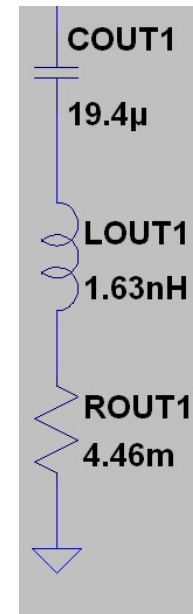
# Know your parasitics! They are very important!





- Equipment to use to measure capacitor parasitic elements.
- **RLC Analyzer**
  - Some can apply DC bias
- **RF Network Analyzer**
  - DC bias can easily damage analyzer source and receiver inputs
  - AC performance measurement very accurate.
  - Agilent (aka Hewlett Packard) i.e. HP3755A goes to 200MHz
  - Many other brands
- **Frequency Response Analyzer**
  - Allows DC bias so voltage coefficient can be measured. RLC results are less accurate. Frequency range is lower than network analyzer
  - 30 MHz max; Usually just 1 or 2 MHz range. May allow plotting on reactance paper with line of constant capacitance and constant inductance. **FRA is also used for loop stability analysis.**
  - Brands – Venable Industries – Ridley (A/P) several others.
  - → Measure the parasitic terms and include them in the design ←



# First Pass Parasitic Inductance for Ceramics



PACKAGE	ESL (pH)
0201	400
0402	550
0603	700
0805	800
1206	1250
0612	63

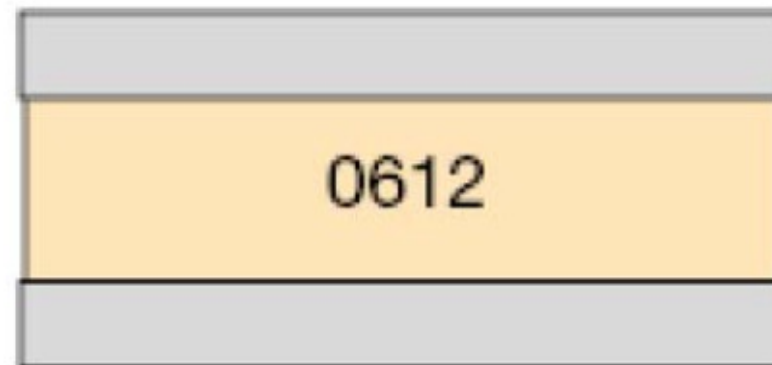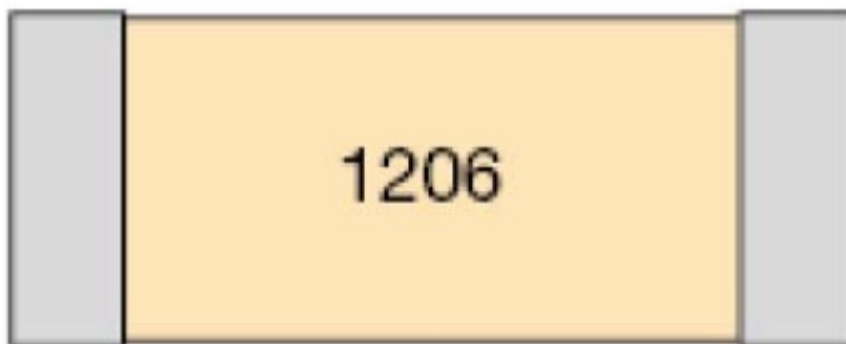

# First Pass Trace Inductance for FR-4, microstrip




## Typical Inductance for a 2500um (60mil) wide 1oz Trace

19.5 nH / inch, 19.5pH / mil , **767pH / mm**

## Typical Inductance for a 250um wide (6mil) wide 1oz Trace

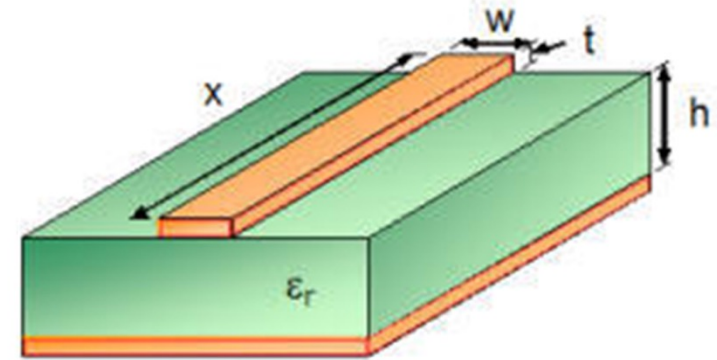26.4 nH / inch, 26.4pH / mil , **1.039nH / mm**



$$L = 0.00508 * b * (\ln(2 * b / (w + h)) + 0.5 + 0.2235 * (w + h) / b)$$

where:

w is width of the strip in inches,

b is the length in inches,

h is the distance between the strip and the ground plane, and


L is inductance in uH.

From ARRL Handbook

6




# First Pass Trace Inductance for Via

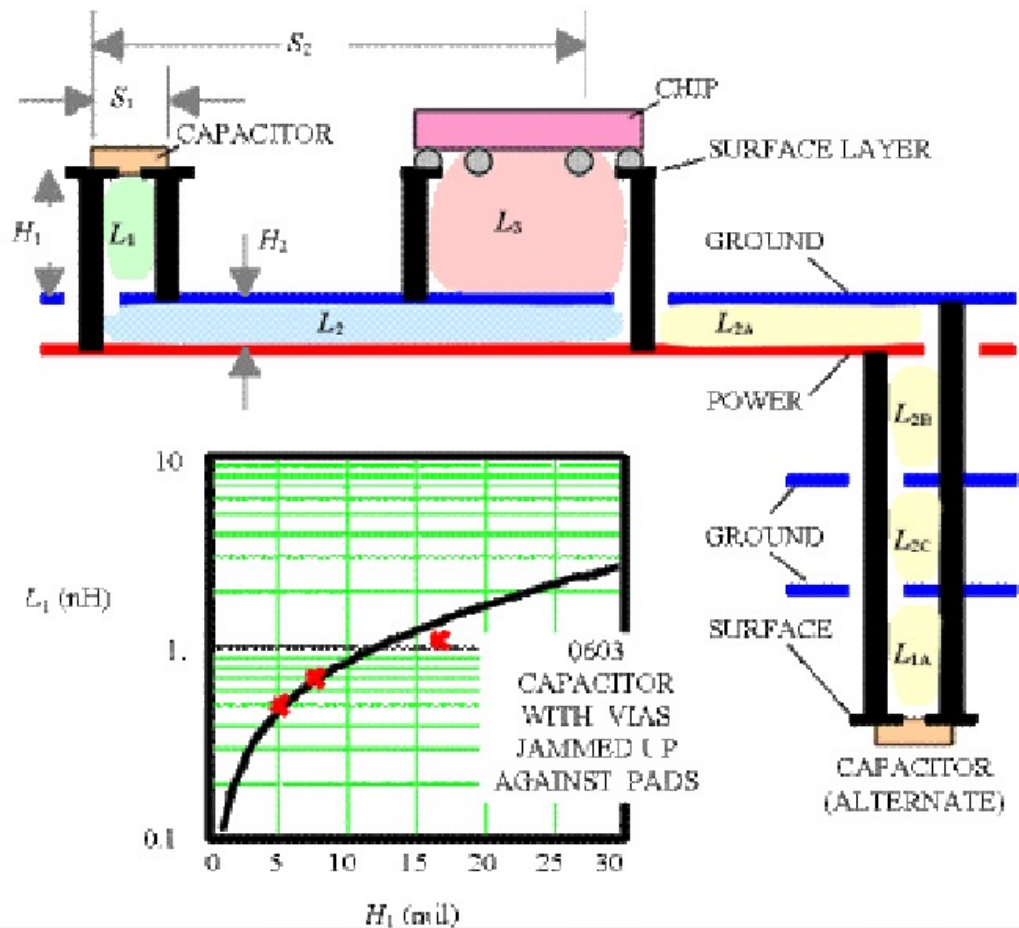

<http://www.signalintegrity.com/Pubs/edn/ParasiticInductance.htm>

From Dr. Howard Johnson
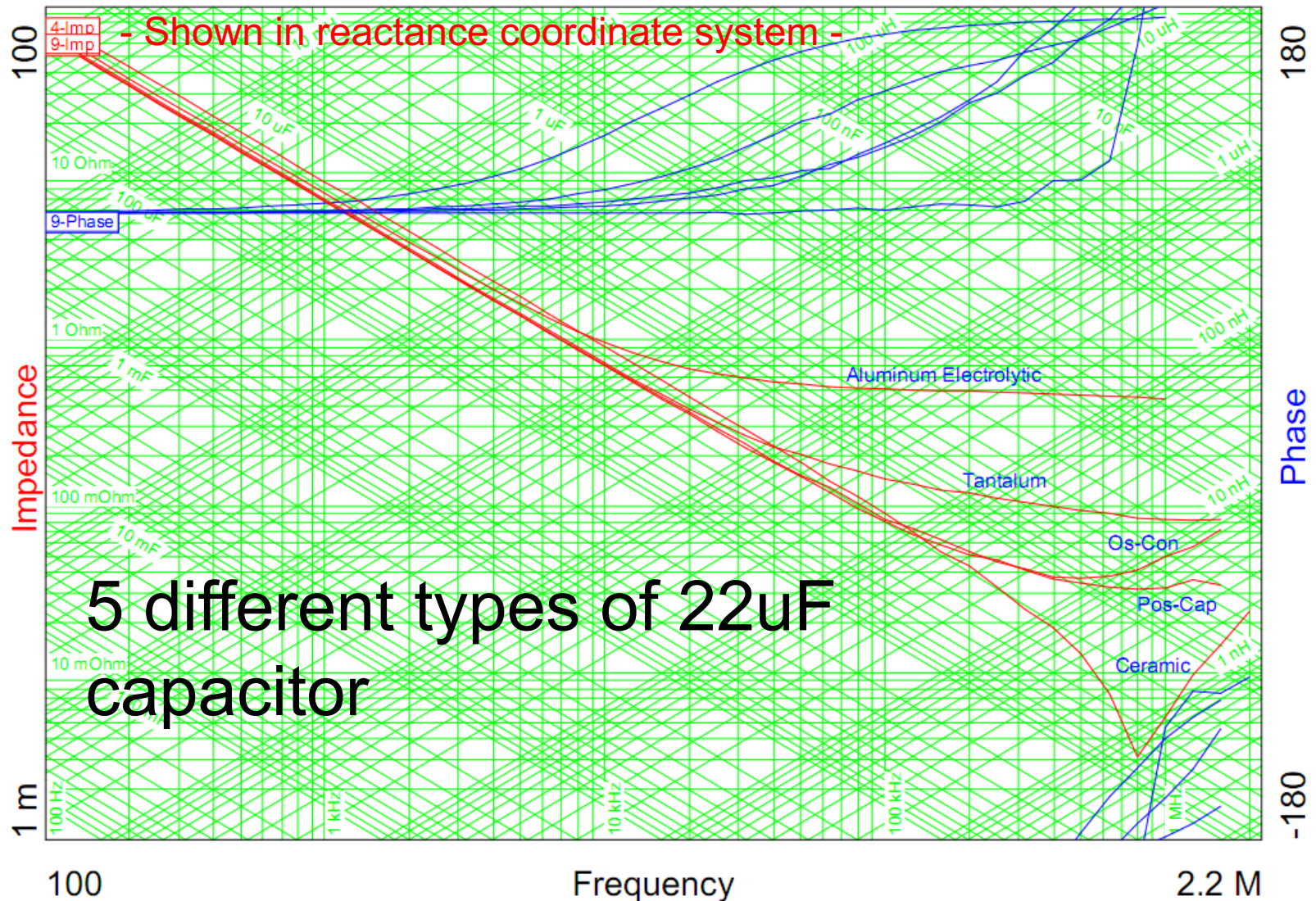
# Comparison of capacitor types using Frequency Response Analyzer





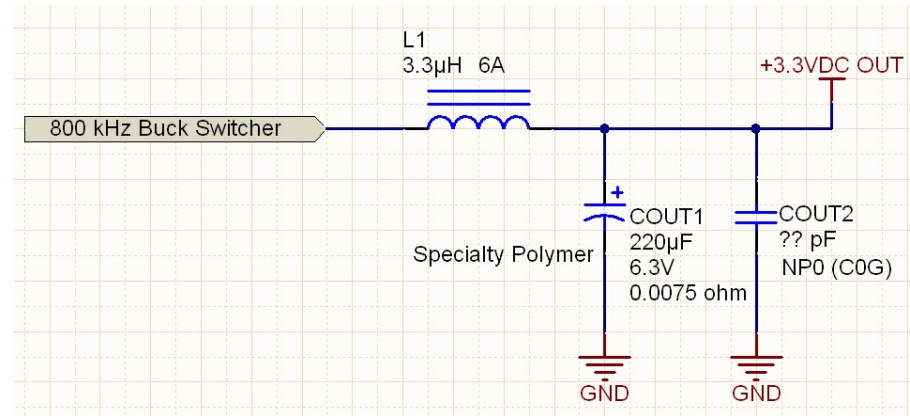
# Techniques to Reduce High Frequency Output Noise



- If the output capacitor(s) is not ceramic; then adding a small ceramic(s) in parallel with the output will reduce high frequency ripple
- Choose a ceramic capacitor that has an impedance null (self resonance) that is the same as the frequency to be attenuated
- One, two or three small ceramics can give 10X improvement (-20 dB)



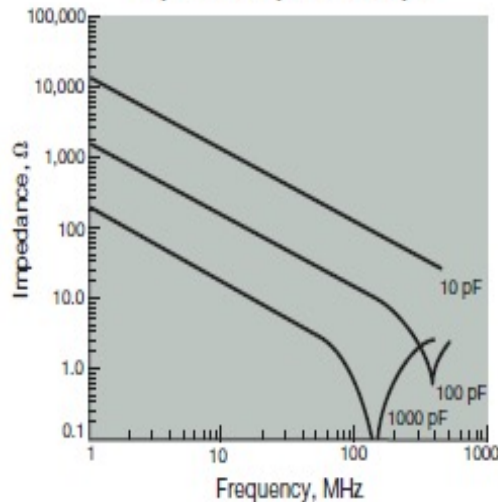
# Use C0G (NP0) Dielectric for High Frequency Shunt Filter Capacitors




Lower ESR – more stable over temp


Variation of Impedance with Cap Value  
Impedance vs. Frequency  
0805 - C0G (NP0)  
10 pF vs. 100 pF vs. 1000 pF



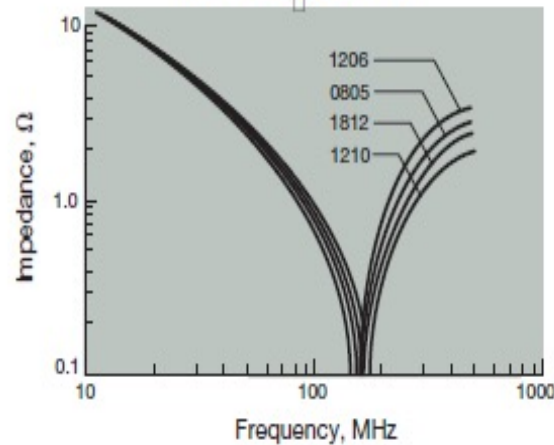Variation of Impedance with Chip Size  
Impedance vs. Frequency  
1000 pF - C0G (NP0)



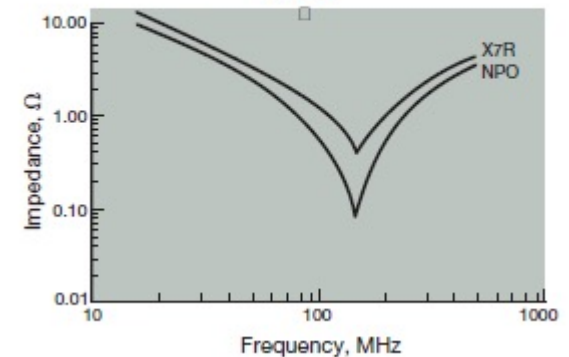Variation of Impedance with Ceramic Formulation  
Impedance vs. Frequency  
1000 pF - C0G (NP0) vs X7R  
0805



Start with manufacturer data sheets, then measure SRF on bench to confirm

# High Frequency Ripple




Switch waveform  
(scope trigger)

$V_{out}$  ripple w/ 20 MHz  
bandwidth (bw)

5 mV /div  $\rightarrow$   
10 mv p-p

HF spikes ignored !

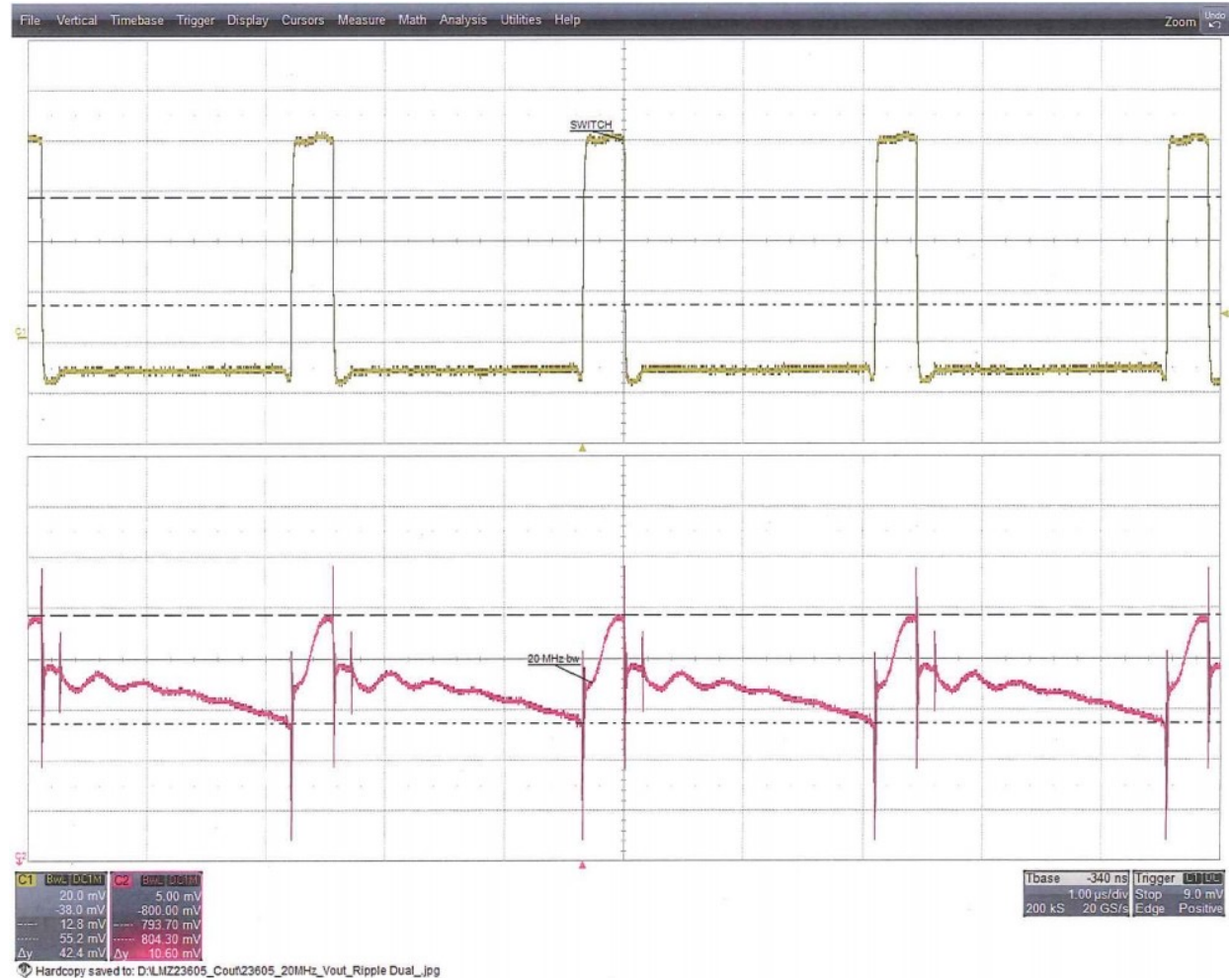


# Use Zoom Function to Measure Ring Frequency


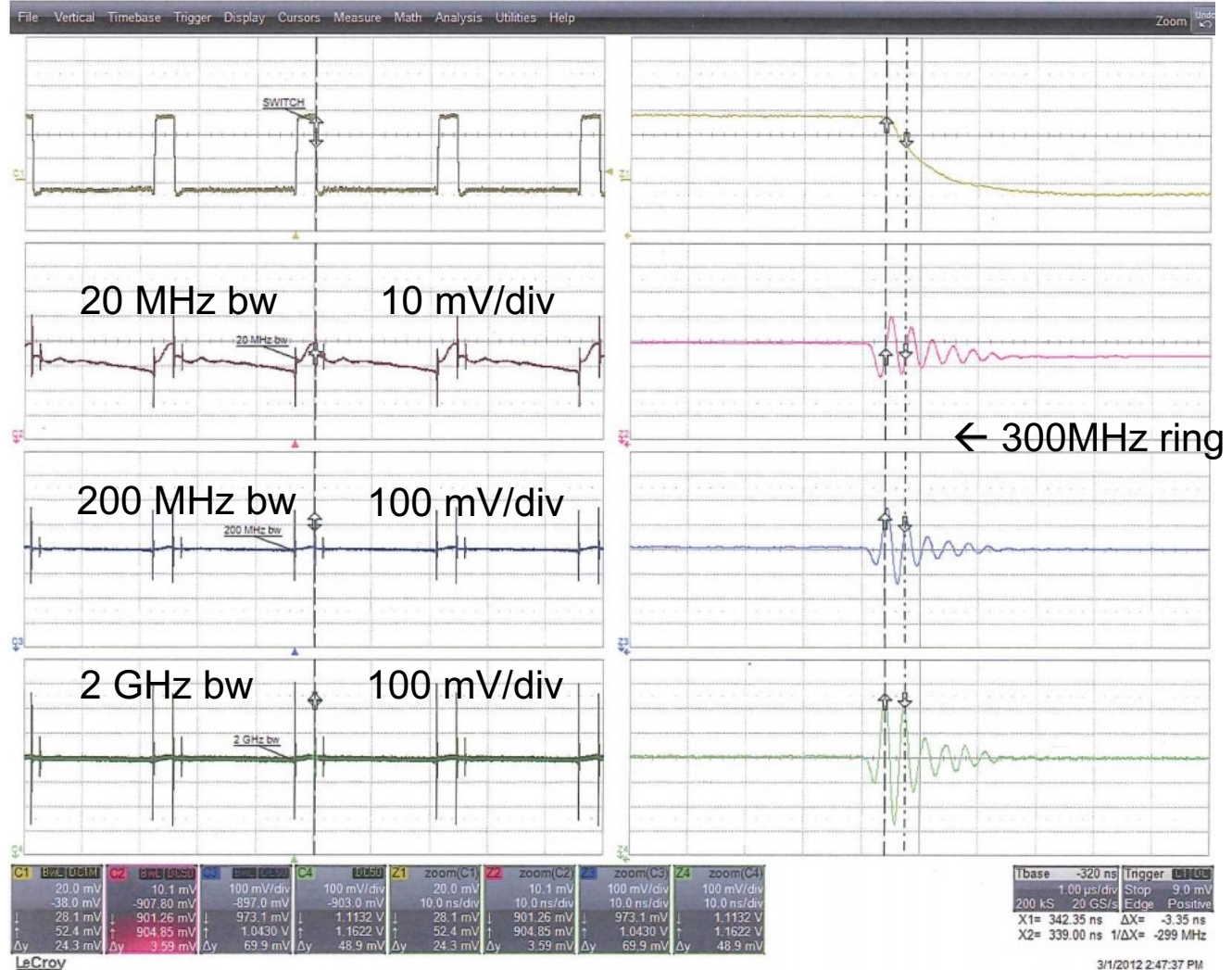
## Timebase Zoomed traces

Need to add  
470 pF 0603  
bypass SRF ~  
300 MHz




3/1/2012 2:47:37 PM

# Continue the Method



Measured after adding a 470 pF 0603 but before adding 2200pF 0603

Timebase Zoomed traces

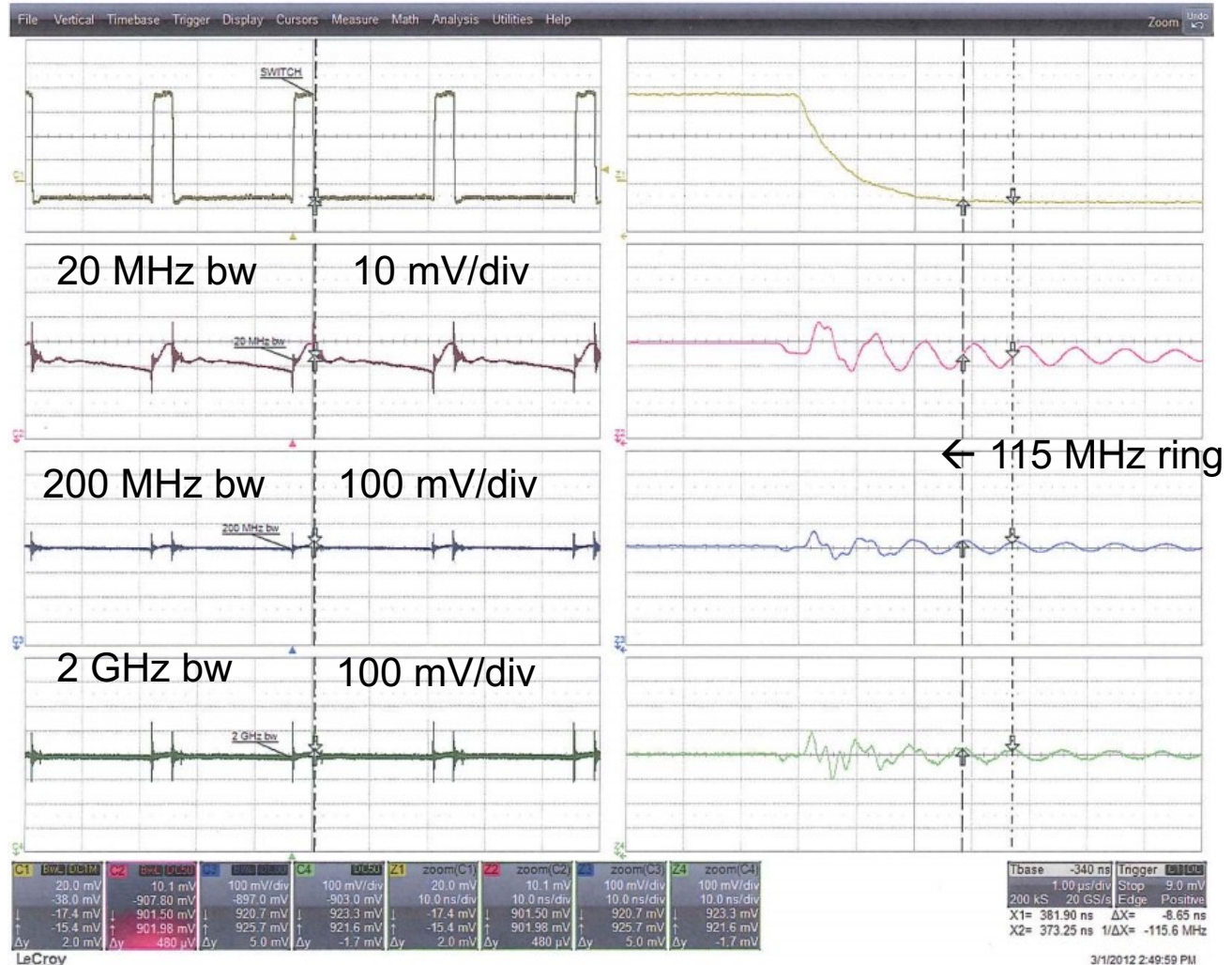


← 115 MHz ring


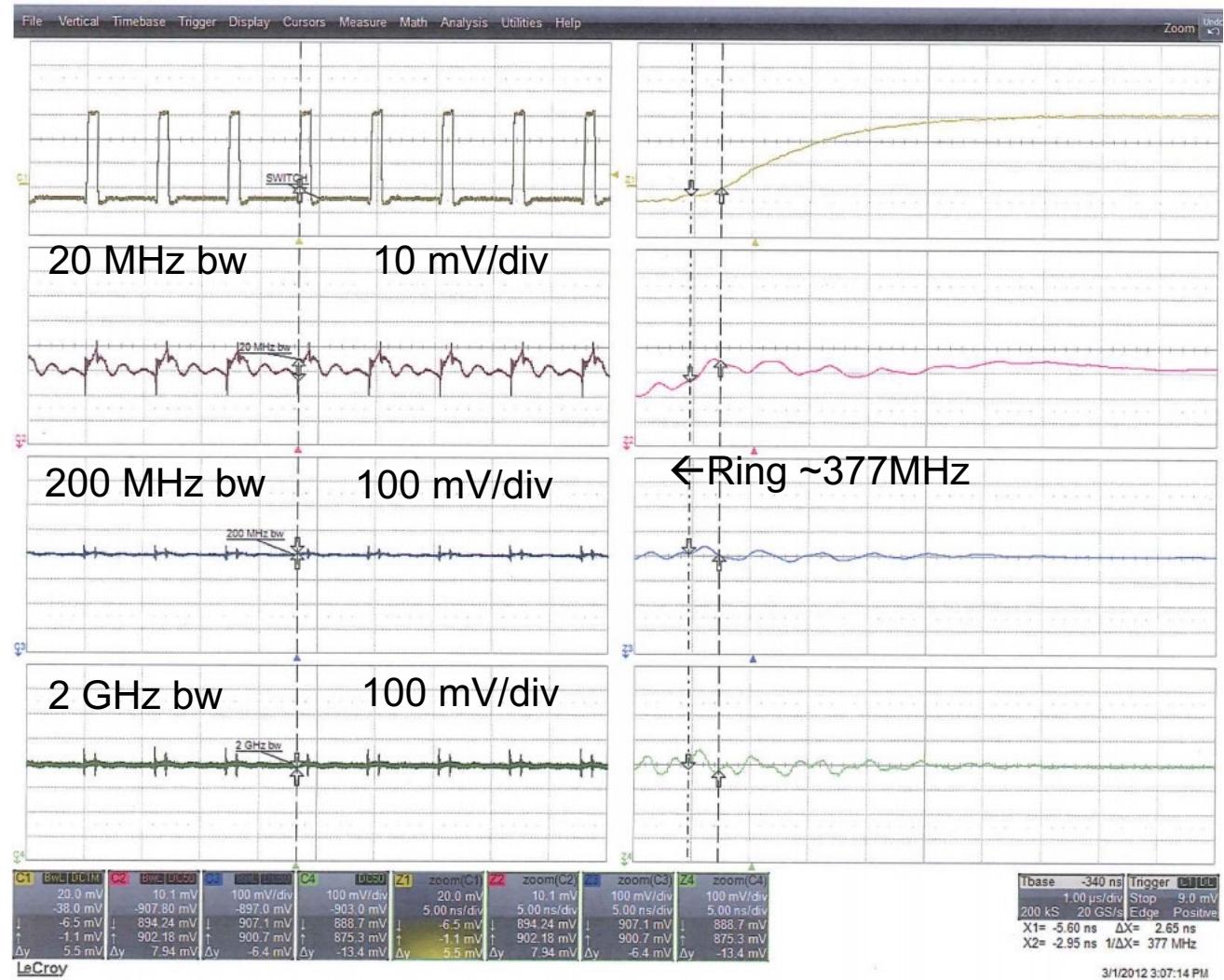
# Results After 3rd Added Small Capacitor




Measured after adding a 470pF 0603, 2200pF 0603, and 4700pF 0805



# Final Amplitude Improvement Results




After 470pF  
2200pF 4700pF

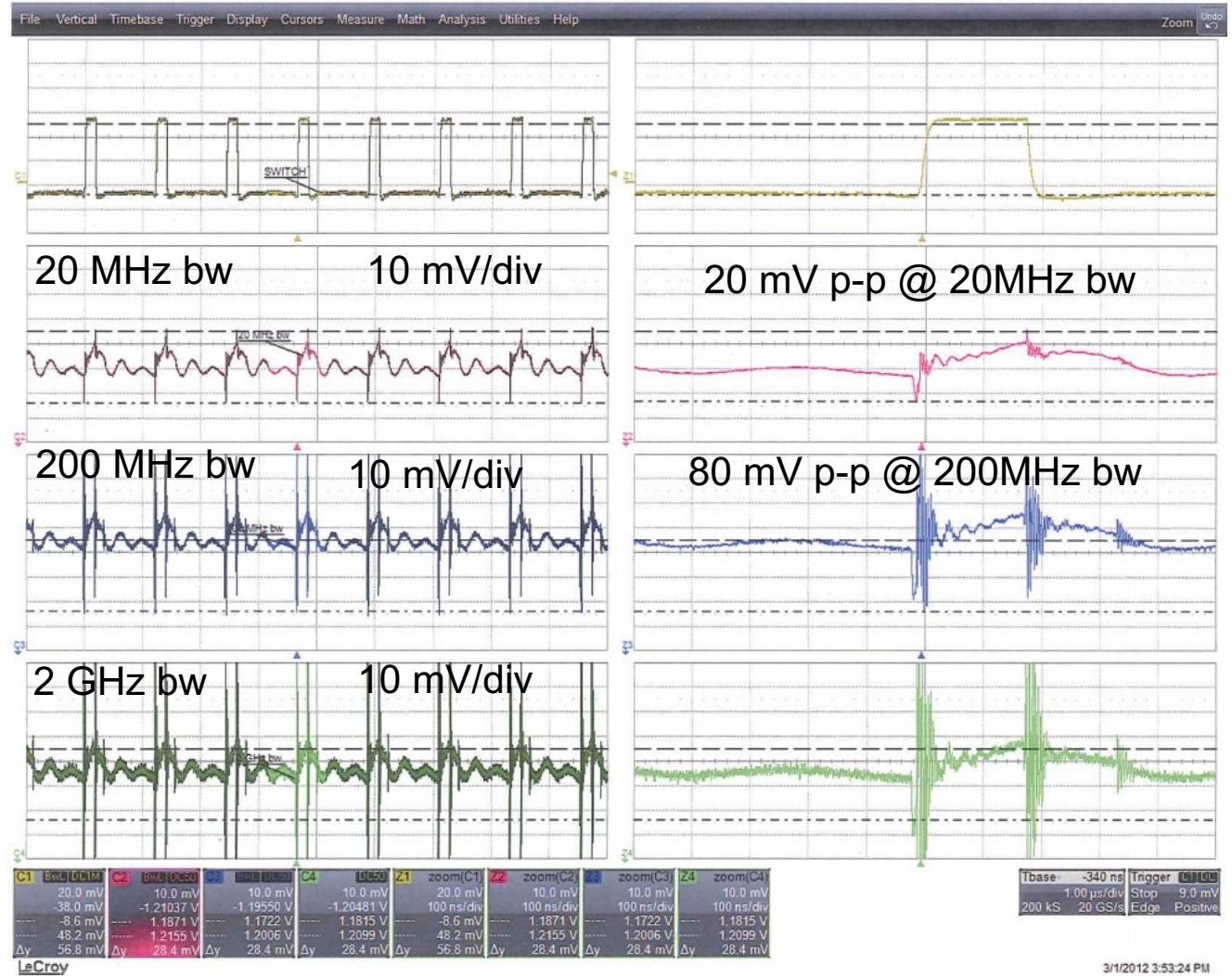



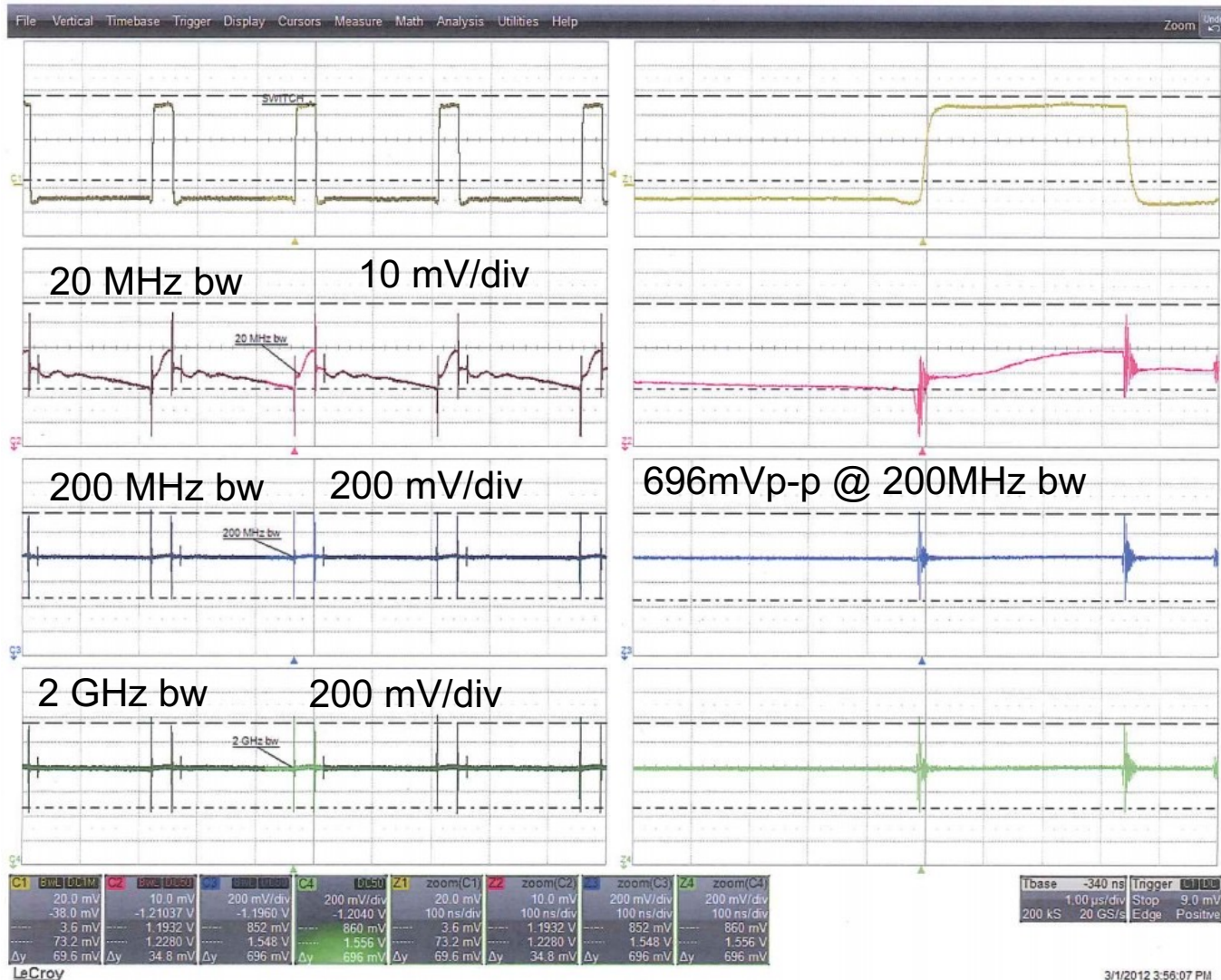
# Starting Point for Comparison – 3 Caps Removed


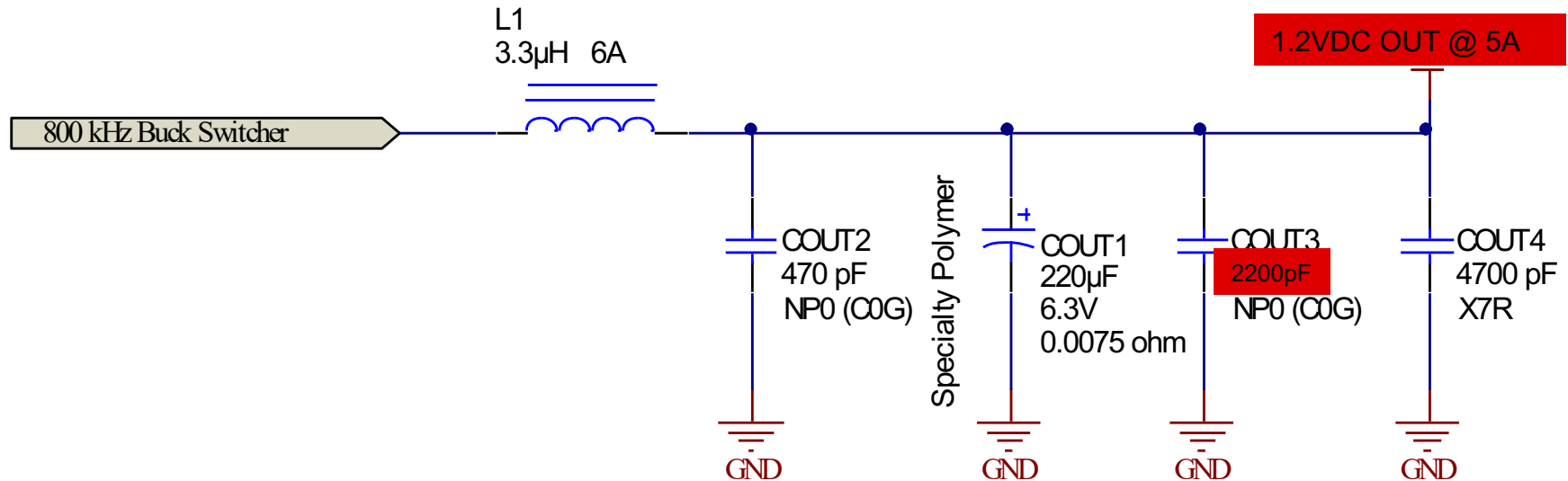
# Final Schematic & Bill of Materials



15 minutes later  
Cost Approximately < \$0.03 USD



- Remember to reserve locations on the schematic and PCB for these parts
- You will not know the capacitor values until **after** you test the running power supply for ringing noise
- → Plan ahead ←



**Thank you!**