


# Nuances in Ultra-Low Power Designs for Wearable Products

**Steven Schnier and Chris Glaser**

**March 2016**
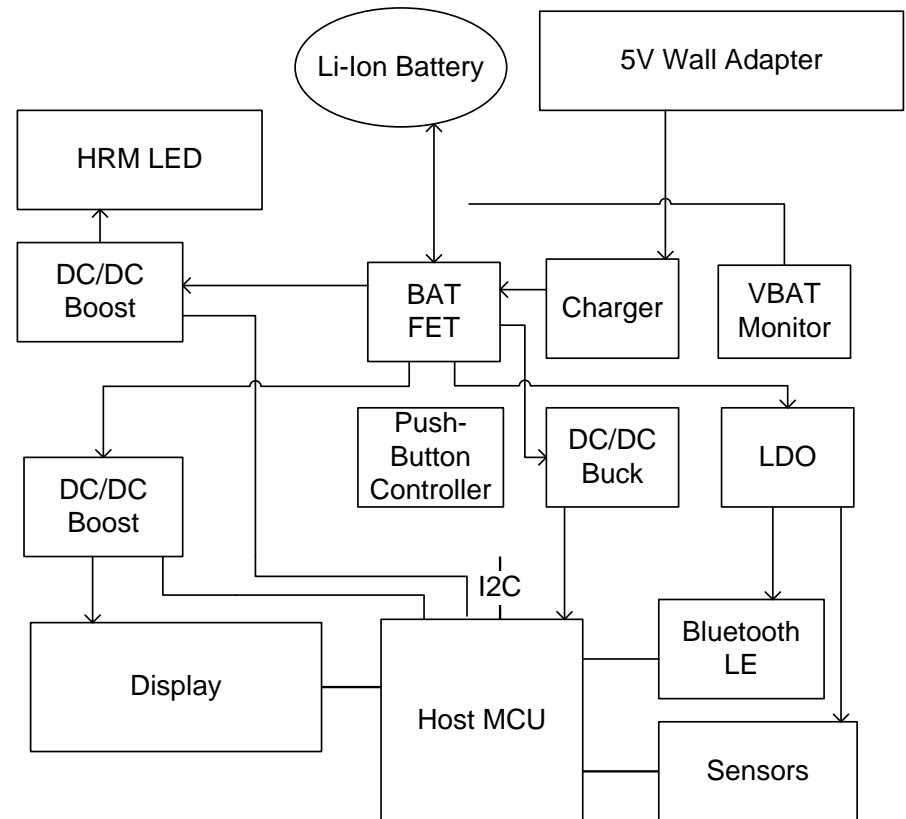
# Why is Low Power Needed?

- Wearables consist of many functions
  - Small Battery with Charger
  - Display (AMOLED, PMOLED, LCD, eInk, etc.)
  - Radio (BLE, WLAN, LTEM, etc.)
  - MCU (microcontroller to mobile chipset)
  - Sensors (6-axis sensor, temperature, humidity, light, heart rate, etc)
  - Vibration Motor
- How long the battery lasts depends on carefully managing each function



# Why is Low Power Needed?

- Wearable Device Power
  - Requires Small Size to be Worn on the Body

BUT



  - More Functionality = Greater Power Usage
  - Greater Power Usage = Larger Battery Capacity
  - Larger Battery Capacity = Larger Physical Size
- A better approach:
  - Create separate power domains for each key function
  - Determine the best power approach and maximize the solution based on
    - Function
    - Size
    - Cost

# Optimizing Power Domains

- Complex Wearable Systems = Multiple Power Domains
- Some domains focus on lowest leakage when off
  - Good candidates are radio's and highly duty cycled functions that are not time dependant
- Some domains focus on lowest power when in standby
  - Good candidates are processors and sensors that are low power in standby, but need to be able to respond quickly
- Some domains focus on highest efficiency when in use
  - Good candidates are the highest power consumption devices
- Additionally, for the best “Out of the box experience” you need to ensure that the battery does not die while the product is on the shelf ready for sale!
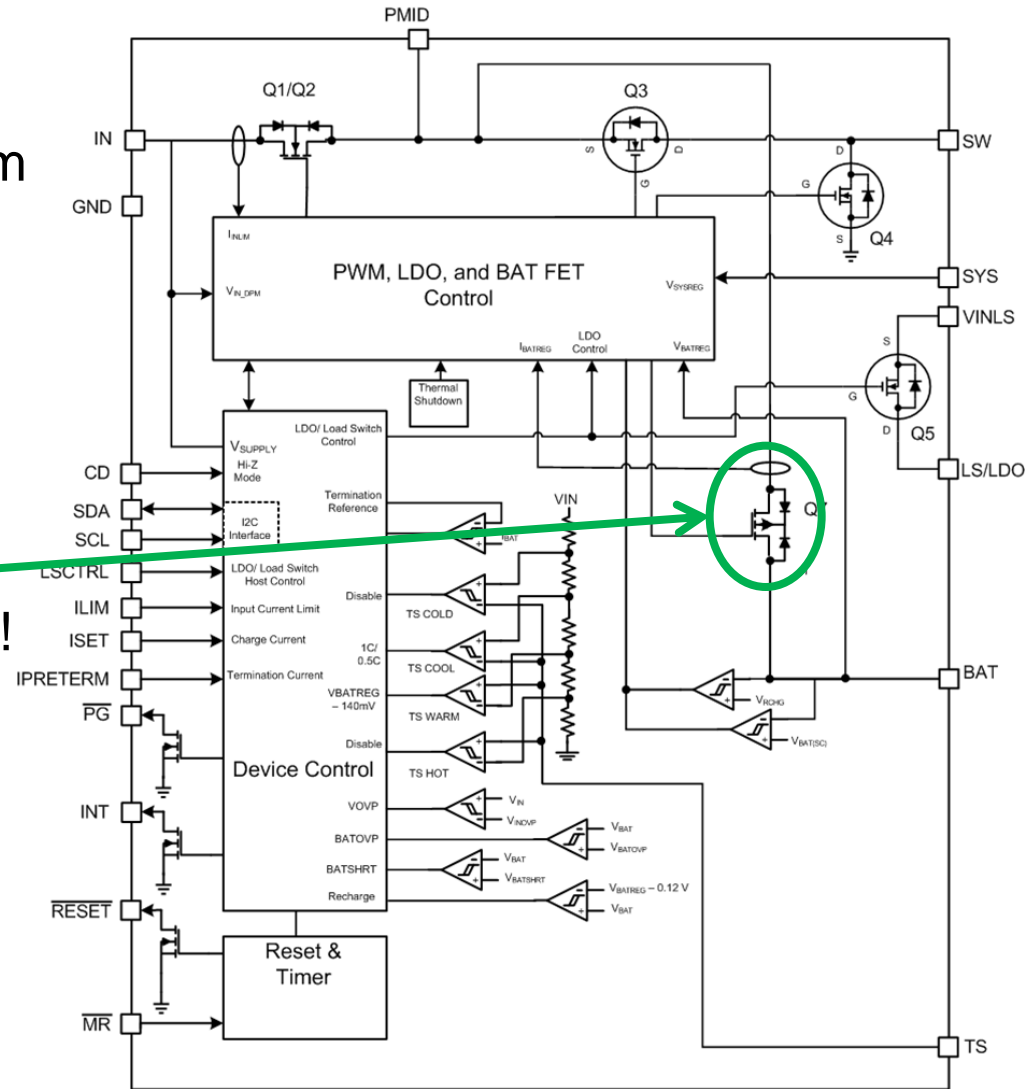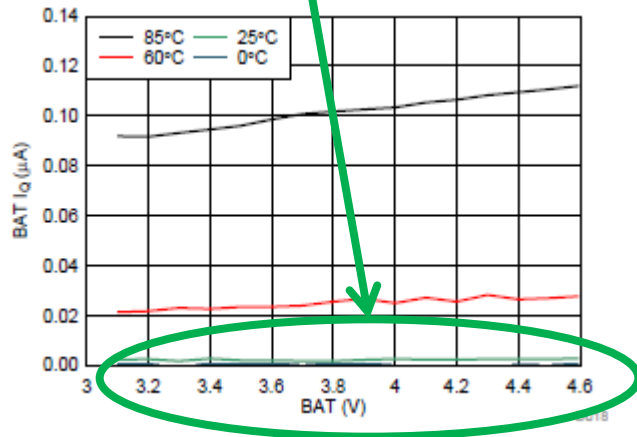
# Low Off Current – Ship Mode

- Choose an architecture that can disconnect the battery from the rest of the system for the lowest leakage when the device is being shipped or on the shelf
- Power Path chargers have a BAT FET that enables this function to  $\sim 2\text{nA}$  at room temp!




Example: [bq25120](#)

# Low Off Current – True Disconnect Switch


- When a sub-system is 'off' → you want 0 current consumption
  - This is not physically possible – some nA always remain
- All systems have leakage currents
  - This is the current consumed when it is 'off'
- Different DC/DC topologies have different **leakage paths**

Buck

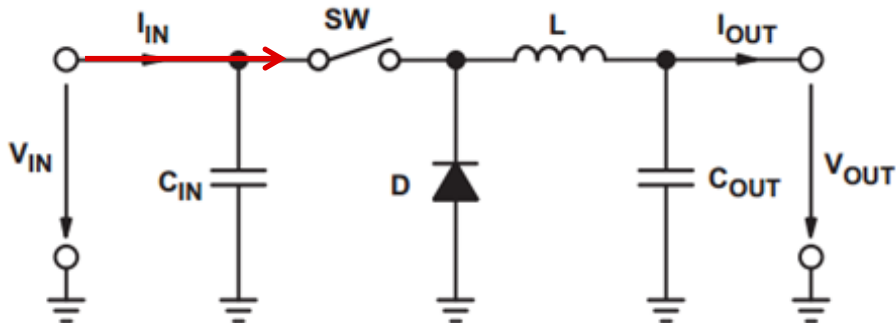

Leakage is mainly in high-side FET


Boost

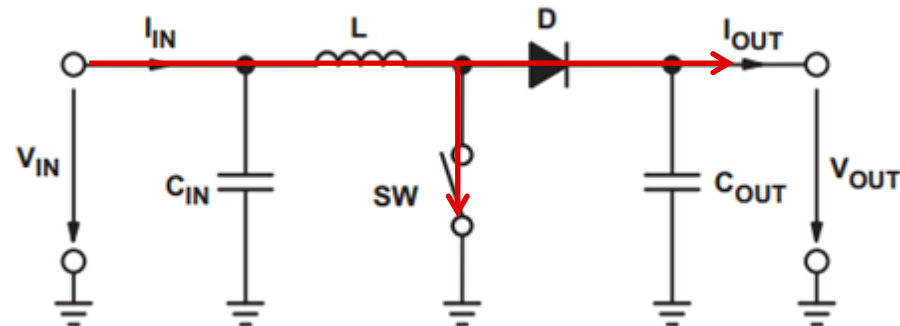

Leakage is in low-side FET  
and to output!

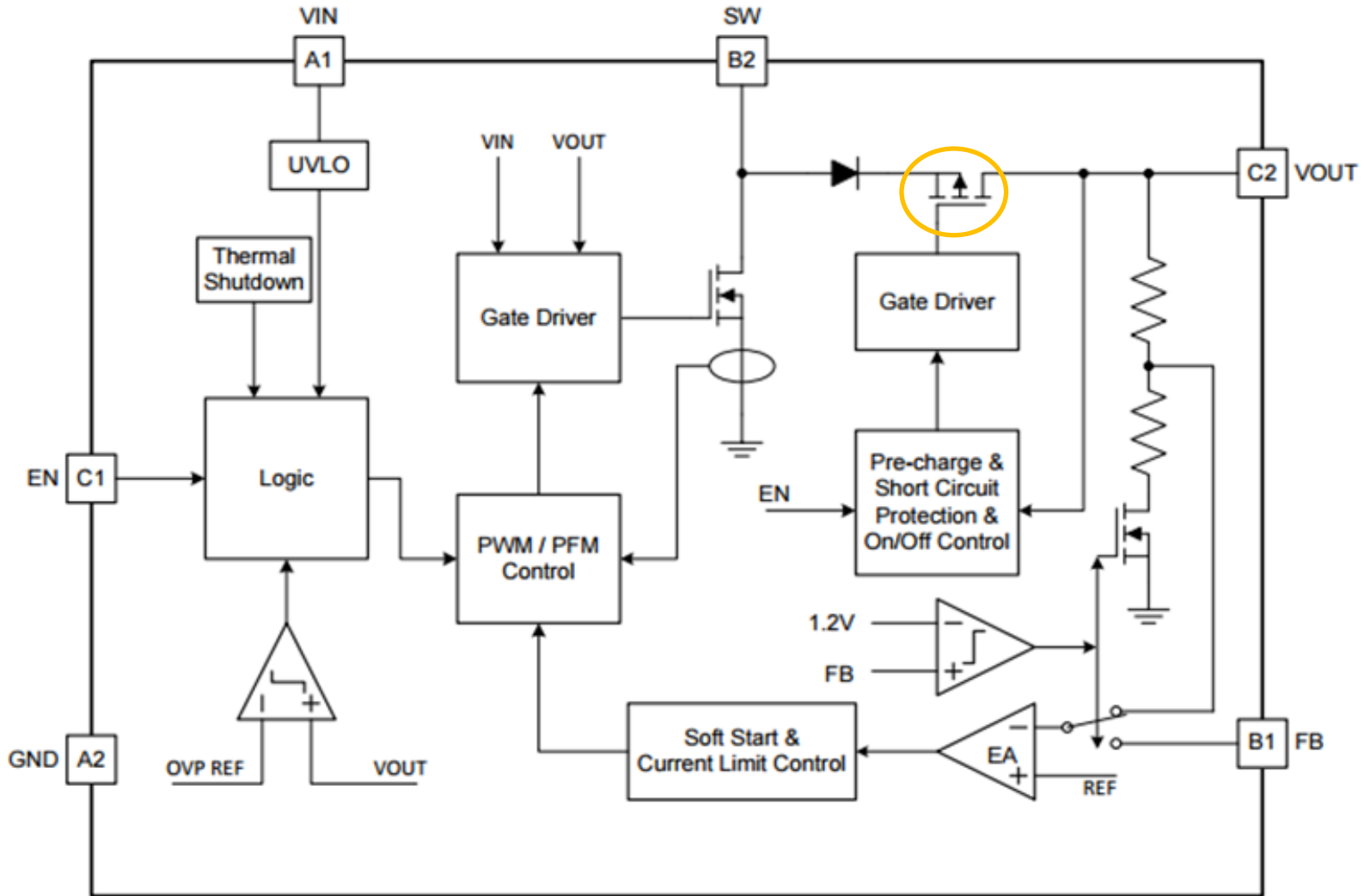
# Removing boost converter leakage

TPS61046 contains an internal isolation switch to separate  $V_{in}$  from  $V_{out}$


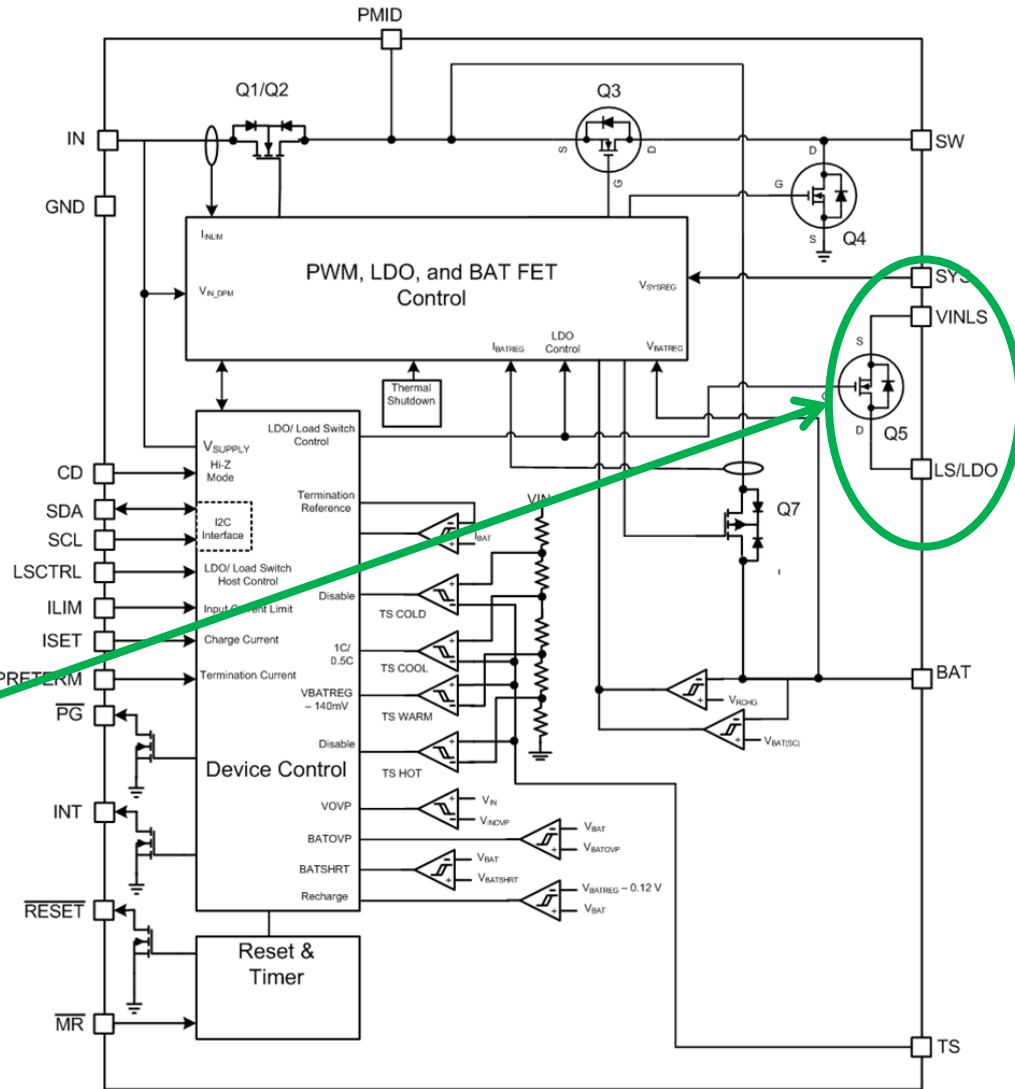
# Low Off Current – Load Switch

- For devices that don't have load disconnect switches, a load switch can provide the same function
- Standalone load switches can be used, or they can be integrated into a larger battery management IC
- The bq25120 has a load switch that can be configured as a regulated LDO output if needed
- The input can be run from the battery, or from the DC/DC converter to optimize efficiency



Example: [bq25120](#)



# Low Quiescent Current ( $I_Q$ )

- What is  $I_Q$ ?
  - “Current drawn by the IC in a no-load and non-switching but enabled condition”
  - Current required to operate the IC (and nothing else)
  - Does not include: load/leakage on output, FB (feedback) resistor current, switching required to keep  $V_{out}$  in regulation, etc.
  - Not no-load input current!
  - Useful for comparing the low-power performance of different ICs
  - Not useful for estimating power drawn in your system’s standby state

See [I<sub>Q</sub>: What it is, what it isn't, and how to use it](#) for a thorough explanation

# Buck $I_Q$

- Almost always drawn from  $V_{in}$
- TPS62743  $I_Q$  specification:

$I_Q$	Operating quiescent current	EN = $V_{IN}$ , $I_{OUT} = 0\mu A$ , $V_{OUT} = 1.8V$ , device not switching	360	1800	nA
		EN = $V_{IN}$ , $I_{OUT} = 0mA$ , $V_{OUT} = 1.8V$ , device switching	460		

IC enabled

No-load input current (IC switching)

True  $I_Q$  (non-switching)

- For a buck, no-load input current is usually slightly greater than  $I_Q$
- Do you have **no load** or just a very light load (some  $\mu A$  or 100s of nA)?

# The power of an ultra-low $I_Q$ buck

TPS62125: 13  $\mu\text{A}$   $I_Q$

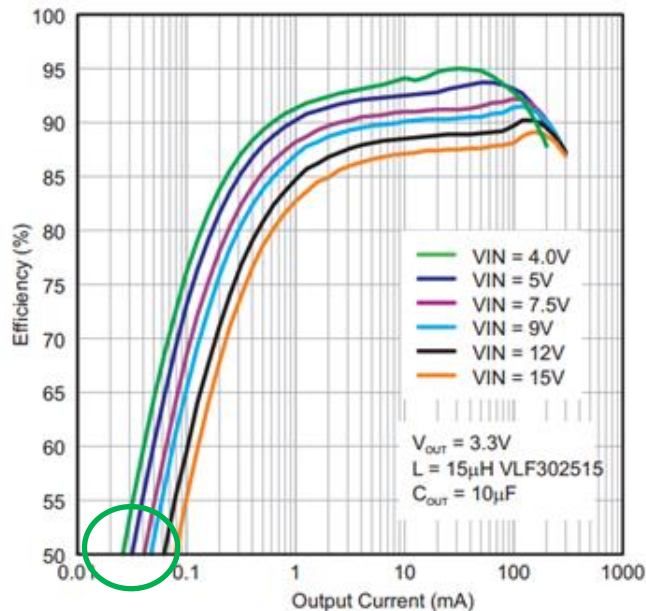


Figure 14. Efficiency vs. Output current,  $V_{OUT} = 3.3\text{ V}$

50% efficiency at 30  $\mu\text{A}$  load

TPS62743: 360 nA  $I_Q$

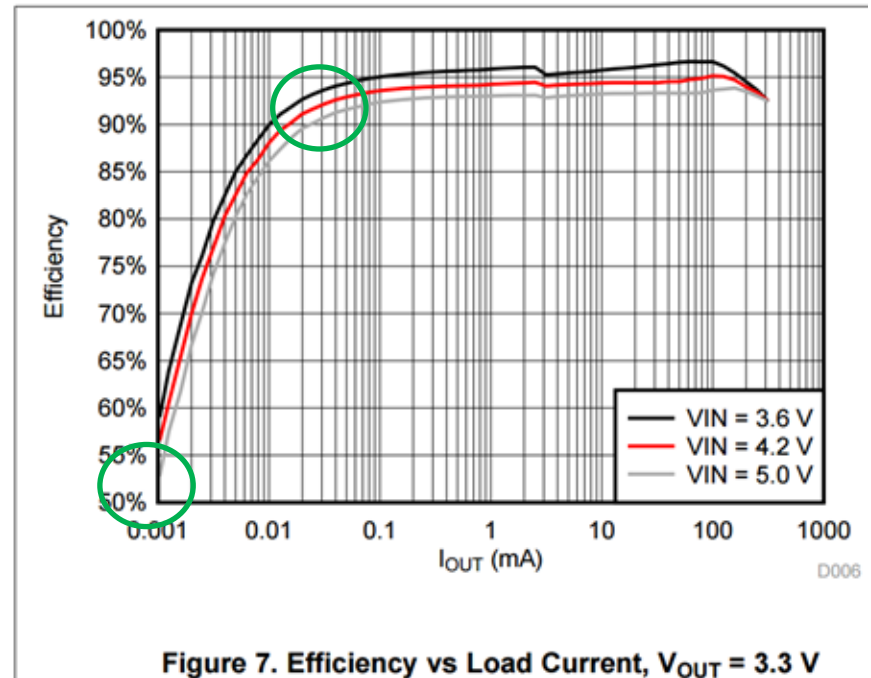


Figure 7. Efficiency vs Load Current,  $V_{OUT} = 3.3\text{ V}$

91% efficiency at 30  $\mu\text{A}$  load  
50% efficiency at  $< 1\ \mu\text{A}$  load!


# Boost $I_Q$

- Some drawn from  $V_{IN}$  but usually some drawn from  $V_{OUT}$  as well
  - $V_{OUT}$ 's  $I_Q$  ultimately comes from  $V_{IN}$  → creates higher no-load input current
- TPS61220  $I_Q$  specification:

$I_Q$	Quiescent current	$V_{IN}$	$I_O = 0 \text{ mA}$	$V_{EN} = V_{IN} = 1.2 \text{ V}, V_{OUT} = 3.3 \text{ V}$	0.5	0.9	$\mu\text{A}$
		$V_{OUT}$			5	7.5	$\mu\text{A}$

IC enabled

- Resulting no-load input current:


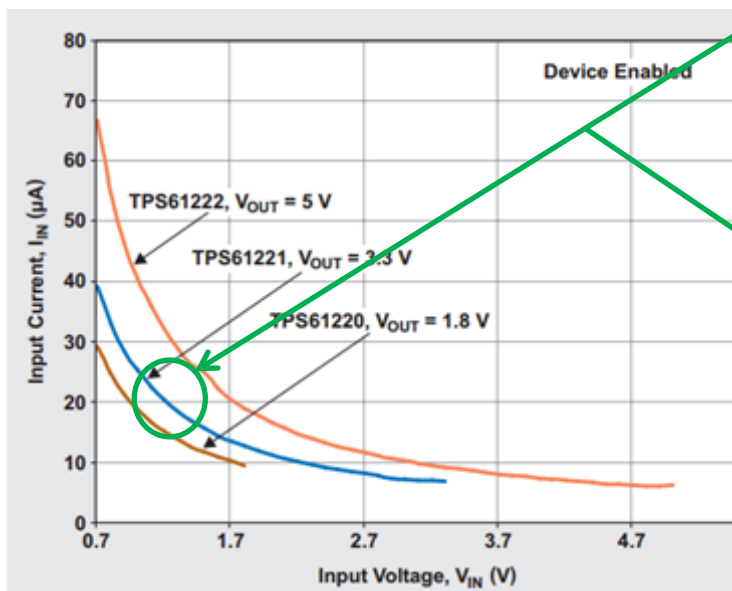


Most current is drawn from  $V_{OUT}$ !

No-load input current =  $20 \mu\text{A}$ !!
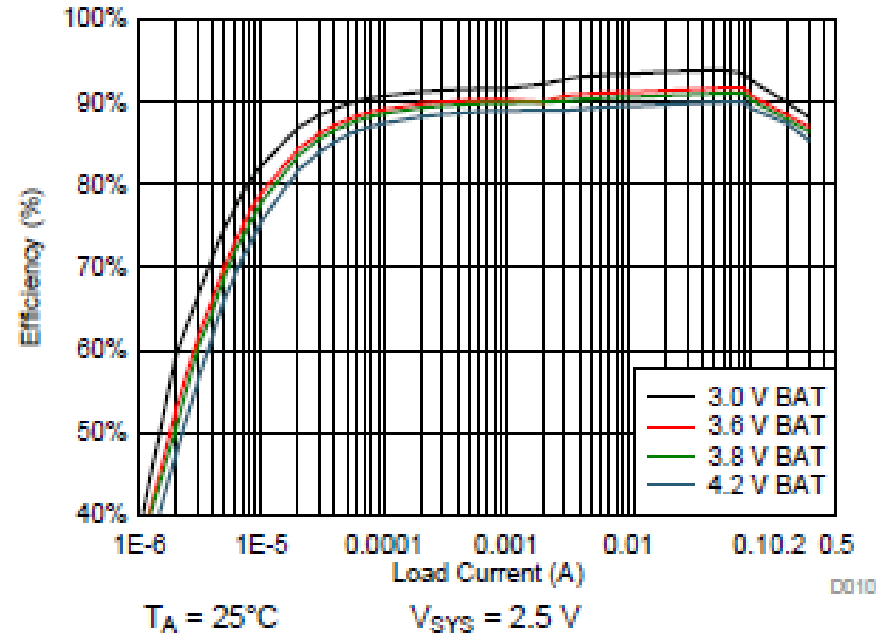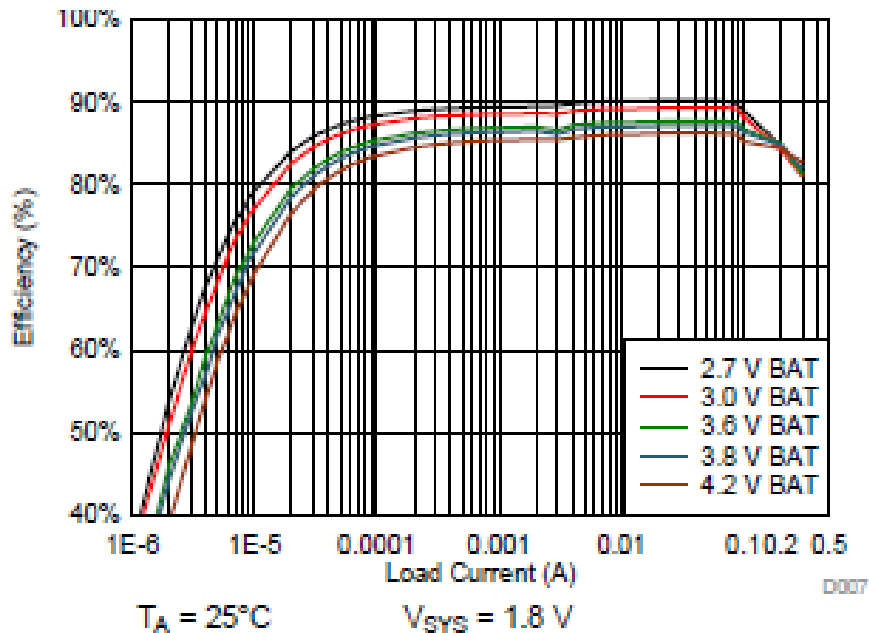
# High Efficiency at Full Load

- Light load efficiency is dependant on  $I_q$  and switching losses
- Full load efficiency is dependant on
  - The ratio of input and output voltages
  - The resistance of the FET from drain to source ( $R_{DS(ON)}$ ) when conducting
  - The DCR of the inductor



Example: [bq25120](#) using inductor with  $240\text{ m}\Omega$  DCR

# Wearables Solutions Coverage

## Audio Devices



- bq2510x  
Smallest Linear Charger
- [TPS62743](#)  
Smallest Low Iq DC/DC Converter

Smallest Solution IF power path and I2C configurability is not needed

## Activity Monitor



- [bq25120](#)  
Meets all basic functional requirements

Smallest Solution Size and Lowest Power Consumption

## Activity Monitor With Display



- [bq25120](#)
- Add [TPS61046](#) boost for display
- Add [TPS62743](#) buck if needed

Most Flexible Solution

## Activity Monitor With Display and Additional Features

## Sports Watch With Display and Full Featured



- [bq25120](#)
- Add TPS62770 for boost and buck and current sink

Smallest Solution for Full Featured Applications

# bq25120: Battery Management for Wearables

Low Iq Linear Charger with Power Path Management, PWM Output, Load Switch, Voltage Based Battery Monitor, and Push-Button Reset

## Features

### 1. Low battery current draw (Iq)

< 750nA (typ) BAT Iq with 1.8V Output Enabled  
< 50nA (typ) BAT Iq in Shipmode

Low Iq allows wearables to be always-on without draining the battery. Shipmode allows shipping the device with the longest battery shelf life.

### 2. Small size

2.5mm x 2.5mm WCSP Package  
15 mm<sup>2</sup> solution size (components)

### 3. Integration

**Linear Charger:** 300mA, 3.4V-5.5V input, 20V max

**LDO:** 100mA

**Buck Converter:** 300mA, 2.2V- 6.6V input


**Power path (switcher)**

**Load switch**

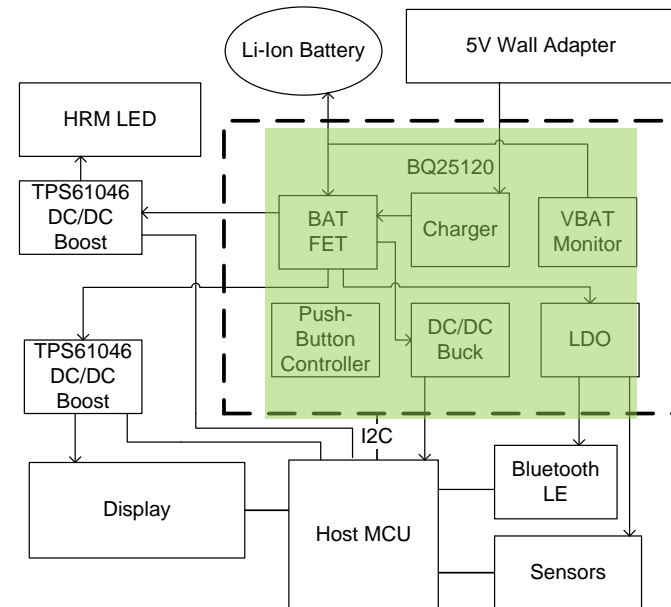**pushbutton control**

**battery voltage monitor:** Accurate 2% VBATREG

I2C programmable flexibility to set all key parameters including ICHG, VBATREG, ITERM




## Applications

- Fitness Accessories
- Smart Watches and other Wearable Devices
- Health Monitoring Medical Accessories
- Rechargeable Toys
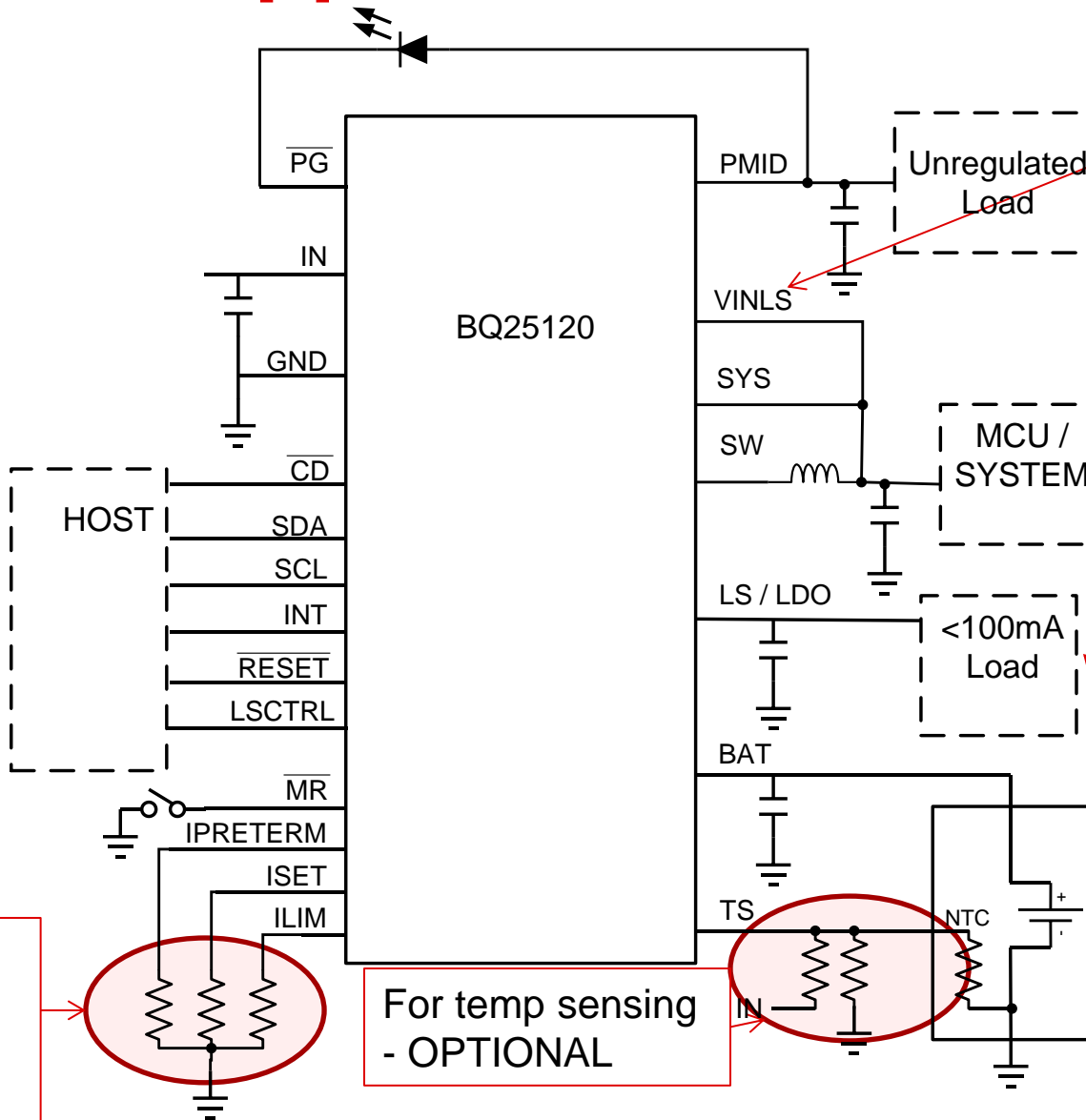
# bq25120 – Application Schematic

HOST can control  
CD, ILIM, ITERM, ISET, Hi-Z, LS/LDO, SYS VBATREG, TIMER, RESET, VINDPM, SHIPMODE and see STATUS and FAULTS

For default and non-HOST Operation - OPTIONAL



Load Switch / LDO input

For Radio, Sensor, Motor or other infrequently used functions

For temp sensing - OPTIONAL




# Solution with bq25120 (PMP11311)

For Activity Monitor  
With Display and  
Additional Features



- bq25120
- bq51003 for Wireless Charging
- TPS61046 boost for OLED display
- TPS61240 boost for Heart Rate Monitor or LCD display
- TPS62743 buck

Most Flexible Solution

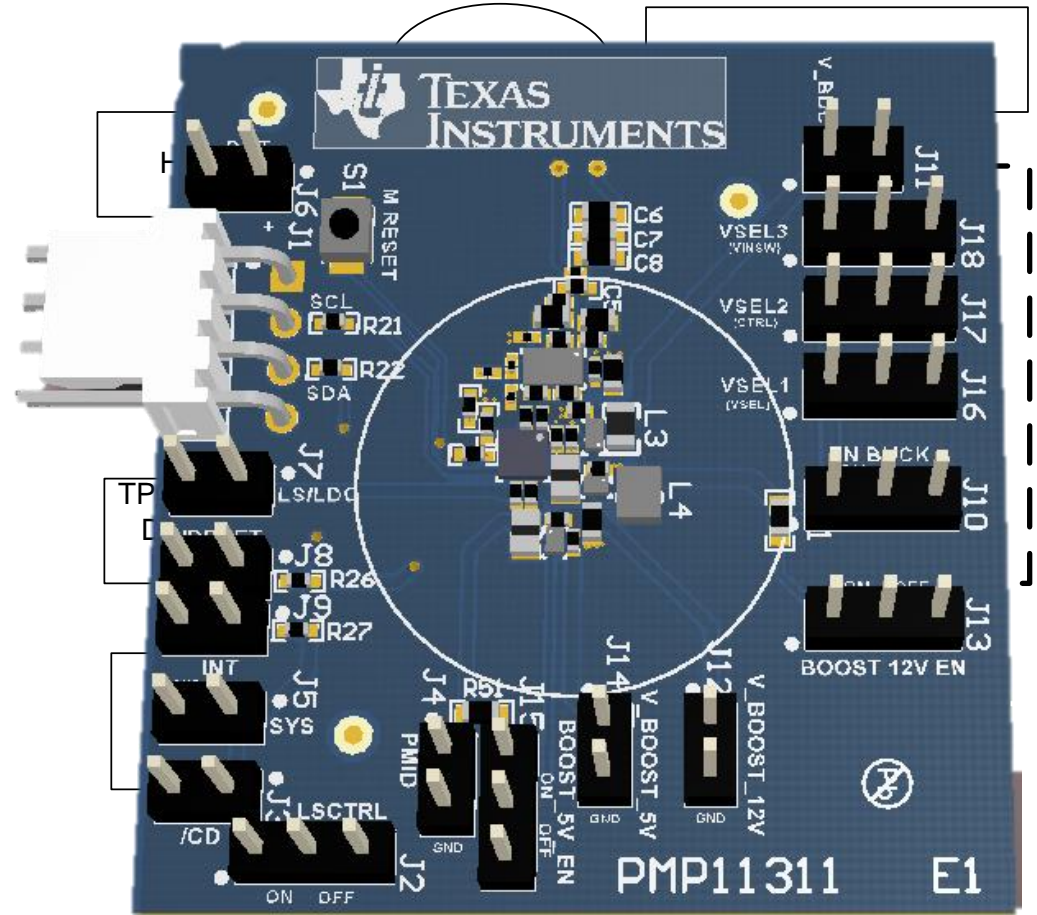

# TPS62770

Tiny single-chip dual solution with 360nA Iq Buck and up to 15V Boost in WCSP

Sampling now.  
RTM: March 2016

## FEATURES


- VIN range 2.5V to 5.5V
- 1x 360nA Iq buck converter (300mA)
  - VOUT selectable with VSEL1-3  
1.0V, 1.05V, 1.1V, 1.2V, 1.8V, 1.9V, 2.0V, 3.0V
- 1 x Slew rate controlled load switch
- Discharge on VO1 / Load
- 1 x Dual mode boost converter
  - Mode selection with BM pin
  - LED current driver with PWM to current conversion (max  $V_{FB}$  voltage 200mV @ D = 100%)
  - Adjustable constant output voltage up to 15V ( $V_{FB}$  0.8V)
- Tiny CSP16 package, 1.65mm x 1.65mm x 0.5mm, Pitch 0.4mm

## APPLICATIONS


- MCU, BLE and Sensor Supply
- Wearable Electronics( HRM,PMOLED, Backlight display)
- Medical Healthcare
- Home Automation (IoT)
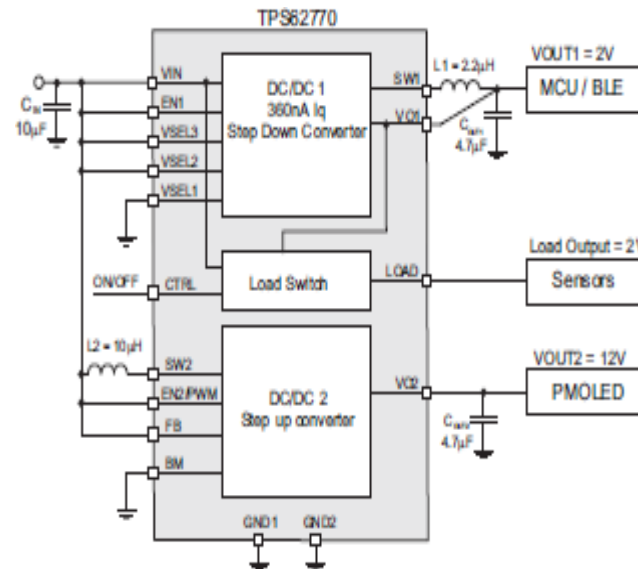
## BENEFITS

- RF Friendly DCS-Control™
- Discharge VOUT
- On board LOAD Switch to disconnect sub-system to extend battery run time
- Minimum external components to optimize board space
- Cover wide range of applications with single device
- Total solution-size: only 21mm<sup>2</sup>.  
12% smaller solution compared with TPS62743+TPS61046.


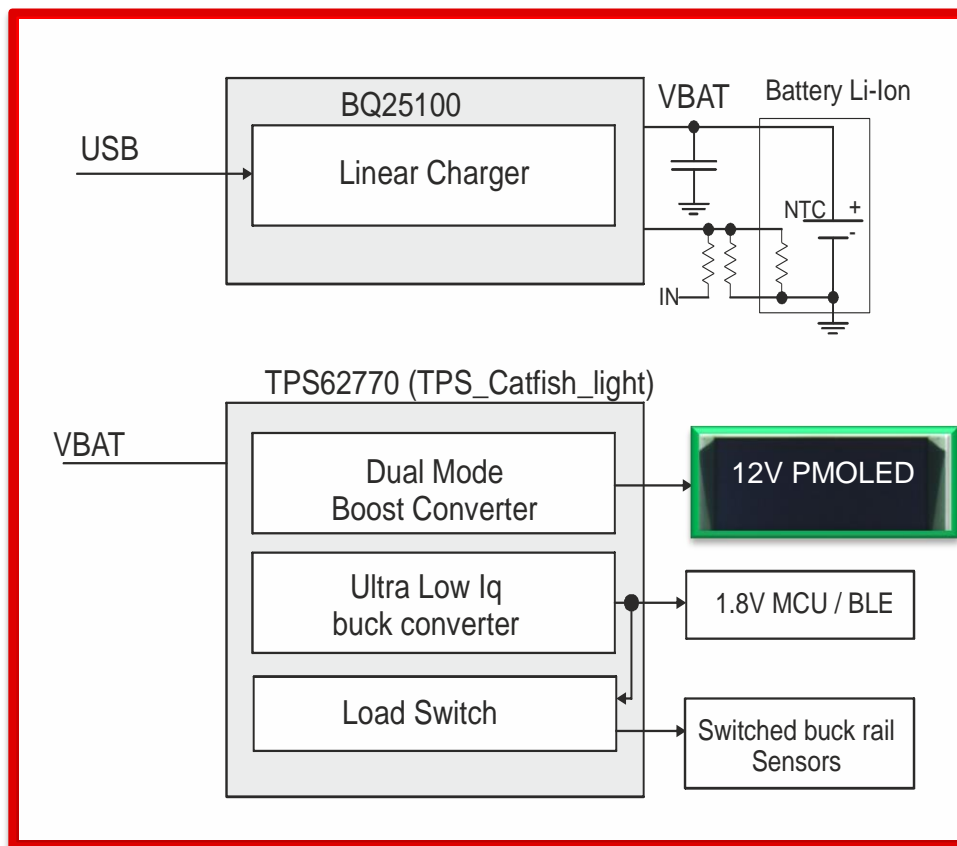
# TPS62770 Solution 1: Powering PMOLED with BQ25100





Two chip power solution without power path management:

**BQ25100**  
(1.6 mm x 0.9 mm WCSP)

+

**TPS62770**  
(1.65mm x 1.65mm WCSP)  
Or use as standalone!
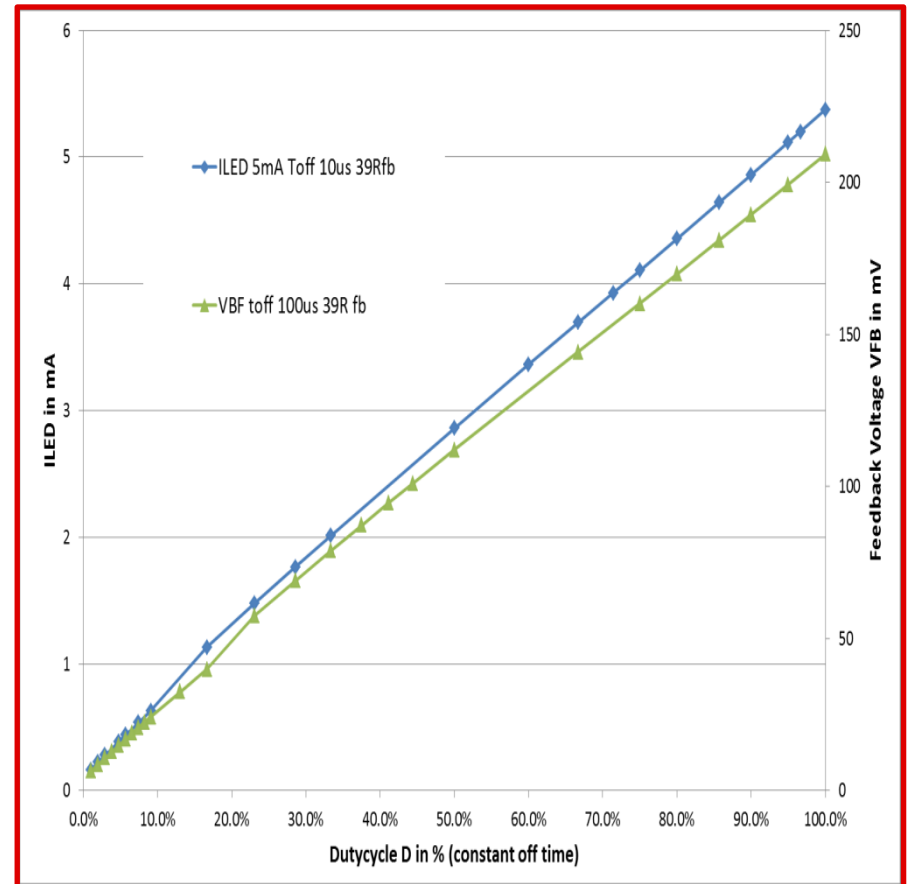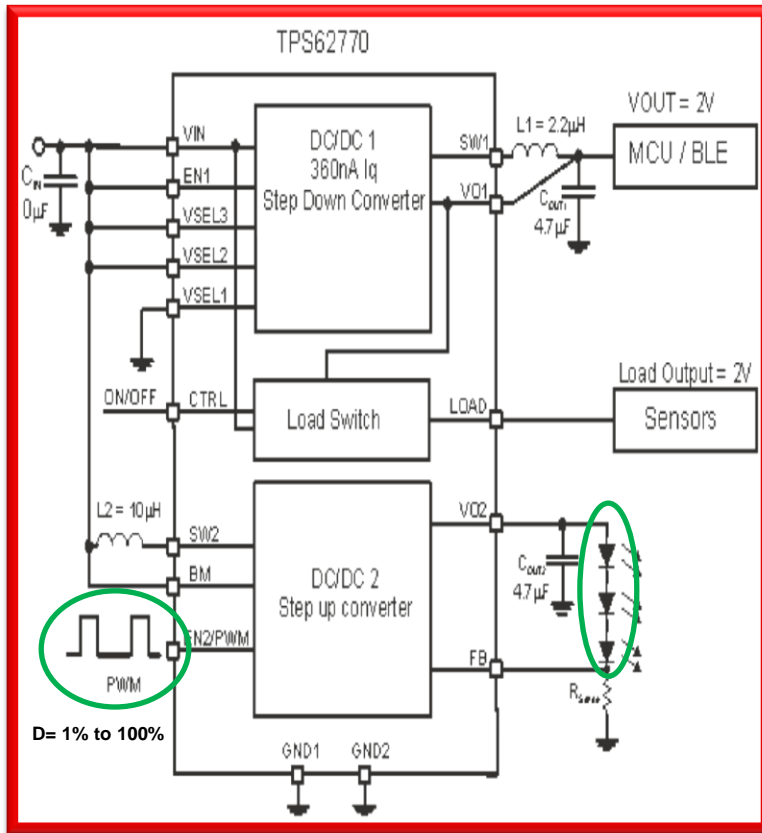
# TPS62770 Solution 2: Driving LED in Series for Backlight Display



# TPS62770 Solution 3: Driving Green LED for HRM

