

High **VOLT** Interactive

Where power supply design meets collaboration

When can synchronous rectification increase efficiency?

Created by: Bing Lu, Bernard Keogh

Presented by: Bing Lu

What will I get out of this session?

- **Purpose:**

- Explain how SRs work
- Show when they can be effective
- Various control methods
- Downsides to watch out for
- Design examples

- **Relevant part numbers mentioned:**

- UCC24612, UCC24610, UCC24630, UCC24624

- **Relevant reference designs:**


- TIDA-01501 450-W 80+ platinum desktop
- TIDA-01494 24-V 480/720-W industrial
- TIDA-01495 24-V 480-W low-profile TV PSU
- TIDA-01557 12-V 200-W desktop 100 mW stdby
- TIDA-01622 65-W USB-C PD 30 W/in³ adapter

- **Relevant applications:**

- Isolated supplies that require high efficiency and/or thermal management

Synchronous rectification – how does it work?

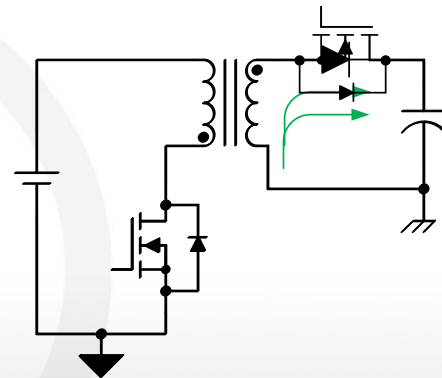- Diode rectifier “easy” – automatically turns on/off
- Replace diode, with body diode in same direction
- Usually N-channel enhancement-mode device
- SR gate off – body diode conducts, same as rectifier diode
- SR gated on => low-resistance bi-directional conducting channel
- SR gate => high when current flows in body diode
- SR gate => low when current in channel decays to zero




Why use an SR? → higher efficiency and power density

- To meet necessary efficiency standards
 - E.g. US DoE & EU CoC for external adapters
 - 80 Plus® Platinum etc. for desktop PSUs
- Higher power density for smaller PSU size
 - Compact travel adapters
 - Smaller DIN-rail industrial PSU
- Solve thermal issues and increase reliability
 - Eliminate diode rectifier hot-spot – increase robustness, reliability and life-time
 - Lower total internal power dissipation, lower running costs, less heat to be removed



Diode rectifier loss

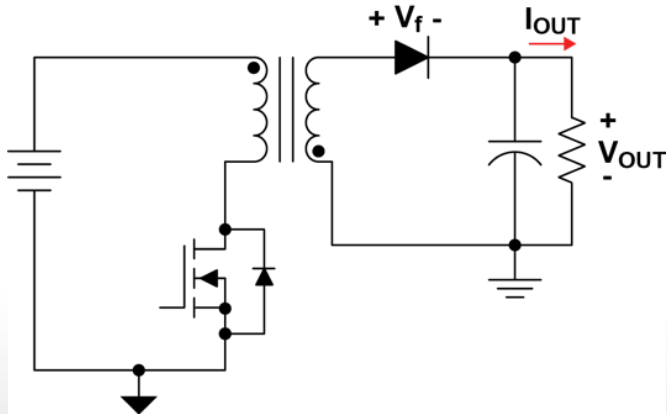

Diode loss


$$P_{DIODE} = V_f \times I_{OUT}$$

Diode rectification efficiency



$$\eta_{DIODE} \approx \frac{V_{OUT}}{V_{OUT} + V_f}$$

- Output diode often carries entire load current
- Diode forward voltage drop is directly related to rectification efficiency
- Efficiency gets worse when output voltage is lower

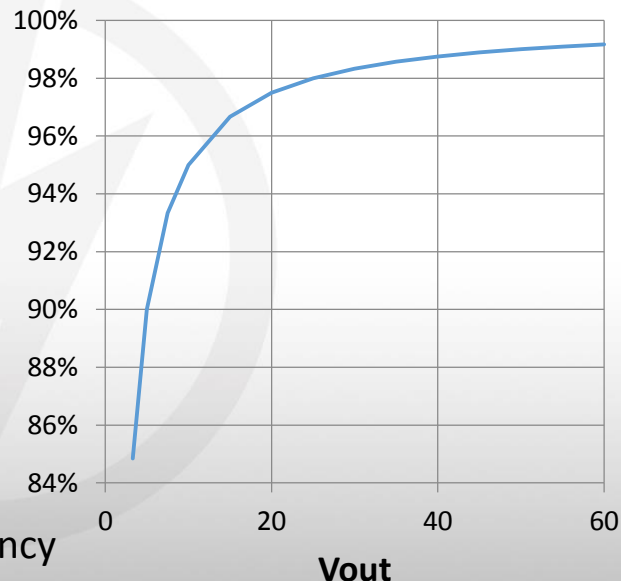**Rectification efficiency
(Fixed $V_f = 0.5$ V)**



Schottky diode vs. synchronous rectifier


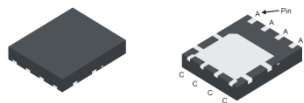
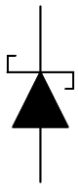


SBRT25U60SLP

25-A, 60-V POWERDI5060

V_f 0.37 V @ 10 A 25°C

V_f 0.32 V @ 10 A 125°C

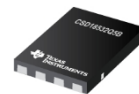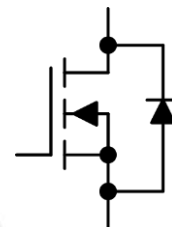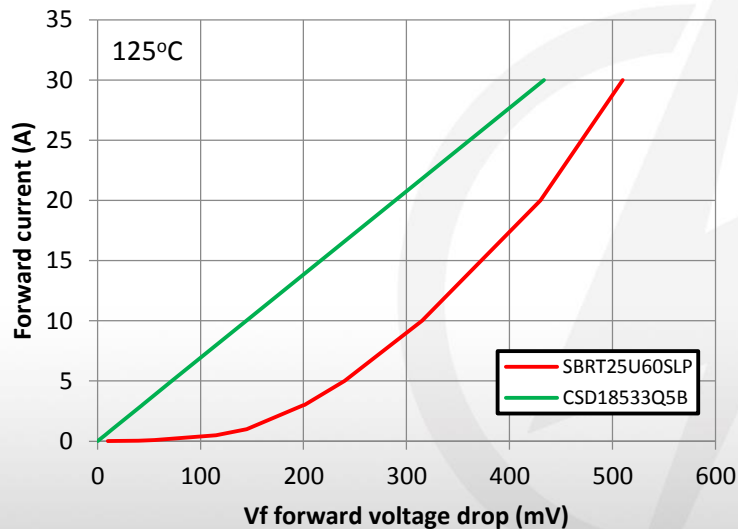

CSD18533Q5B

60-V SON5x6



$R_{DS(ON)} = 8.5 \text{ m}\Omega$ @ 25°C, $V_{gs} 4.5 \text{ V}$

$R_{DS(ON)} = 15.3 \text{ m}\Omega$ @ 125°C, $V_{gs} 4.5 \text{ V}$

- By replacing diode with synchronous rectifier, conduction loss can be significantly reduced
- Higher efficiency can be expected for low voltage applications


Loss comparison for a typical flyback rectifier

SBRT25U60SLP loss model

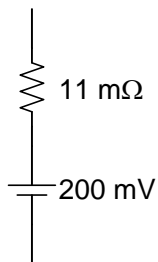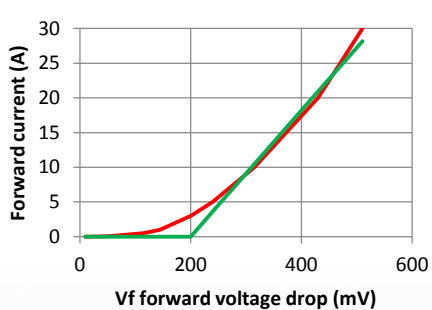


- Large conduction loss saved by replacing diode with synchronous rectifier



Flyback secondary side current

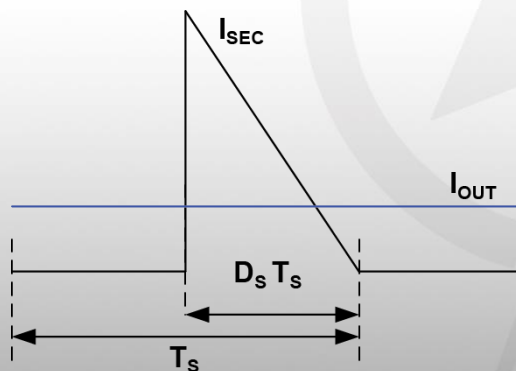


Assuming 50% duty-cycle QR flyback

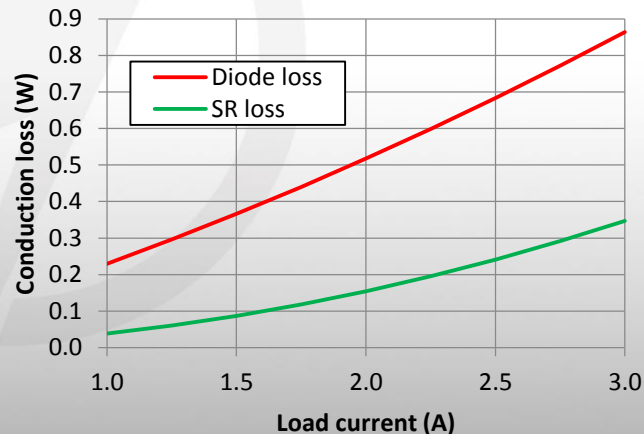


CSD18533Q5B loss model

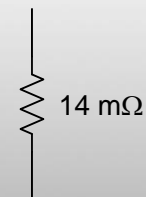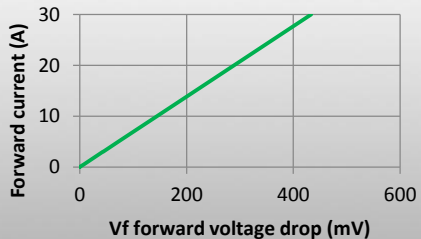

How to calculate LLC SR current?

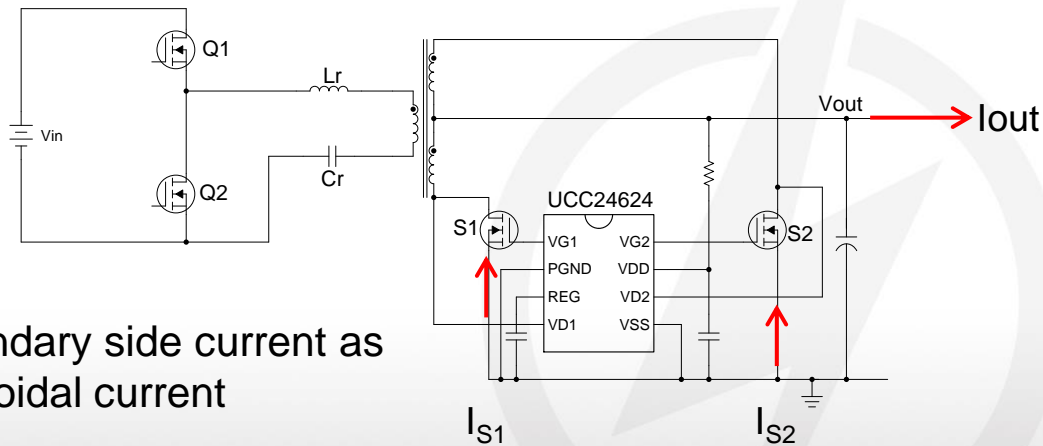

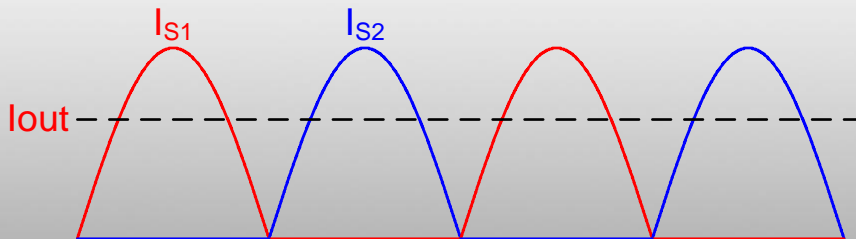Approximate the secondary side current as rectified sinusoidal current




$$I_{S1}(avg) = I_{S2}(avg) = \frac{I_{out}}{2}$$


$$I_{S1}(rms) = I_{S2}(rms) = \frac{\pi}{4} I_{out}$$

Direct control of SRs

Synchronous buck

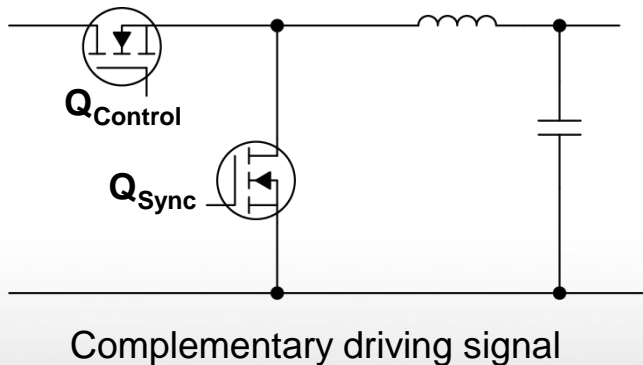




Active clamp forward converter

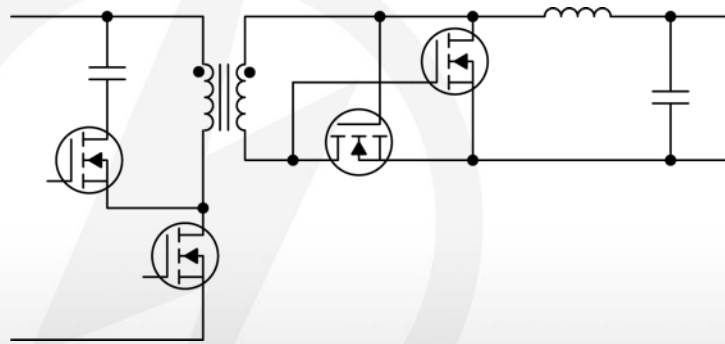

Self-driven based on transformer voltage



- Some topologies can easily implement SR control without dedicated controller IC
- Flyback, active clamp flyback, LLC, etc., applications usually need dedicated SR-controller due to its complexity
- For example: PMP8740 uses UCC28950 phase-shift full-bridge controller that controls both the primary side switches and the secondary side SRs

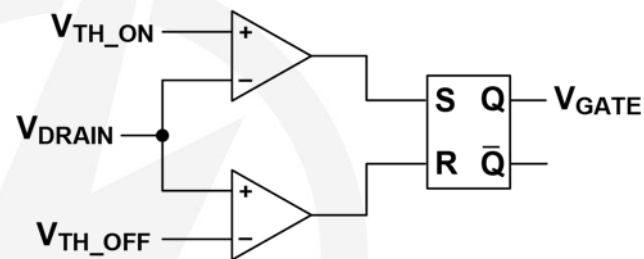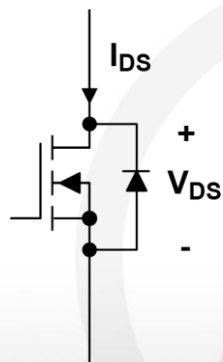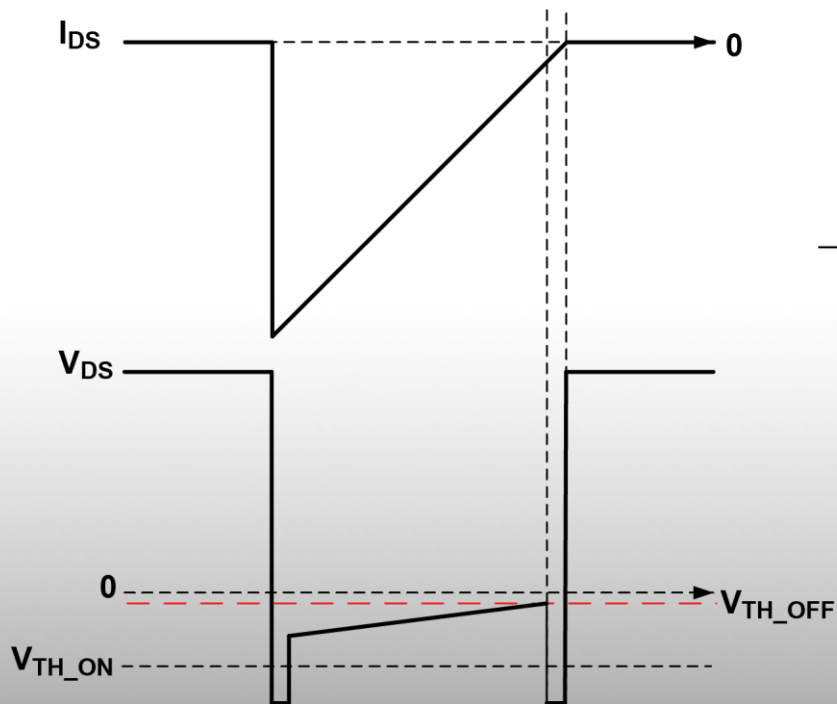SR control based on V_{DS} sensing – UCC24610



- Monitoring SR drain-to-source voltage (V_{DS})
 - When body-diode is conducting, V_{DS} crosses V_{TH_ON} , controller turns ON SR
 - When V_{DS} decreases to V_{TH_OFF} , current is approaching zero, controller turns OFF SR

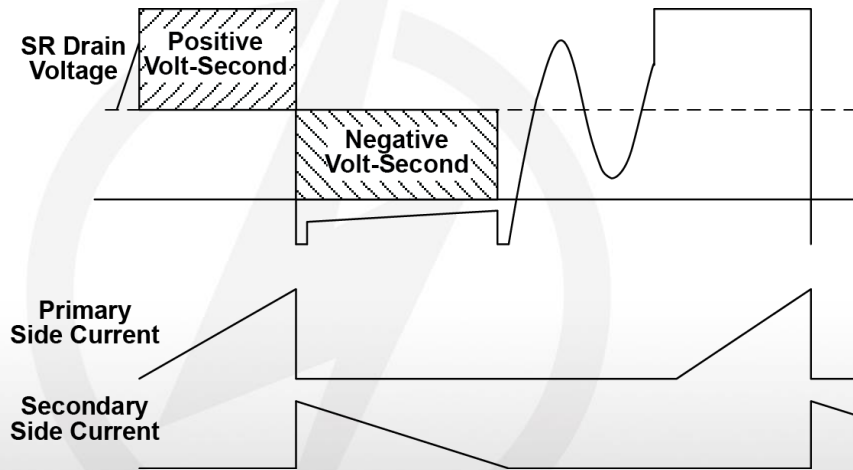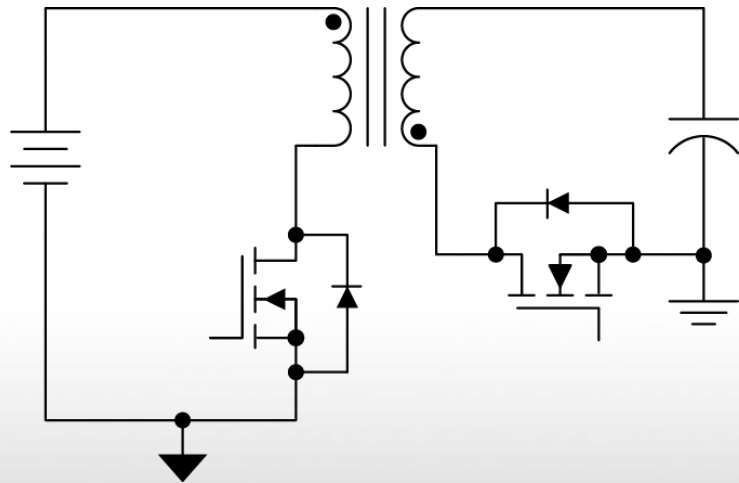
SR control based on volt-second balancing – UCC24630



- Volt-seconds are balanced in each switching cycle for DCM flyback — it can be used for SR control – less sensitive to noise
- Only valid for DCM, can't work for LLC or active clamp flyback


SR selection: conduction loss

Simplified SR control scheme

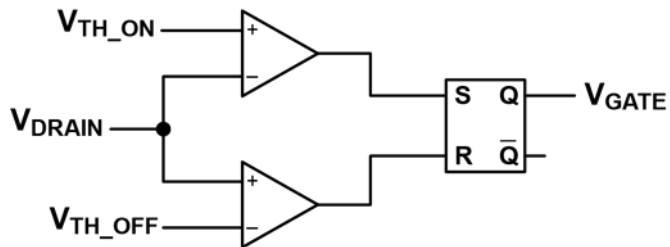

$$I_{OFF} = \frac{V_{TH_OFF}}{R_{DS(ON)}}$$

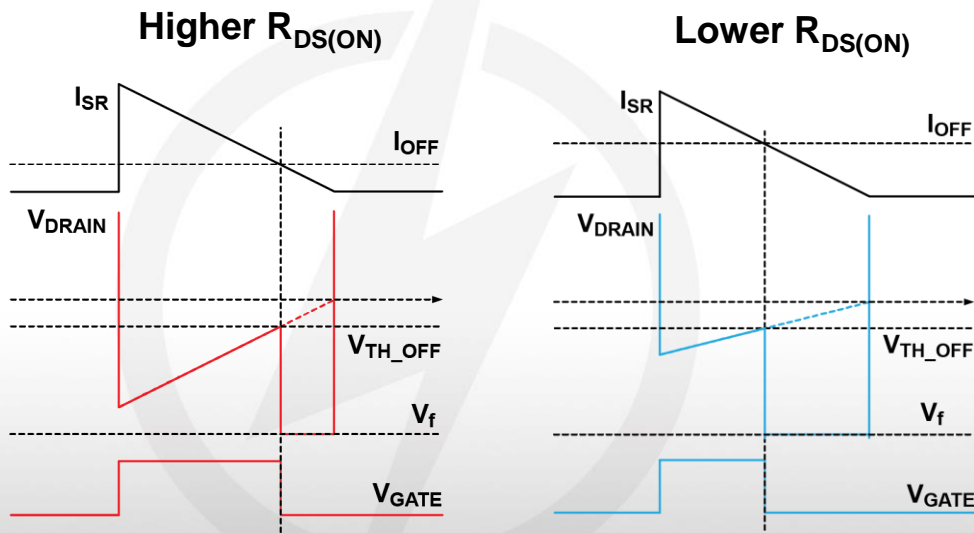- Turn-off threshold is a fixed value
 - Larger $R_{DS(ON)}$ results in smaller turn-off current and less body diode conduction time
 - Smaller $R_{DS(ON)}$ causes larger turn-off current and more body diode conduction time
- $R_{DS(ON)}$ should be chosen with consideration of turn-off threshold



SR selection: switching loss


$$P_{SR} = P_{CON} + P_{SW} + P_{DRV}$$

Conduction loss $P_{CON} = I_{RSM}^2 \times R_{DS(ON)}$

Switching loss $P_{SW} = \frac{1}{2} C_{OSS(eq)} \times V_{DS}^2 \times f_{SW}$


Driver loss $P_{DRV} = C_{ISS} \times V_{DRV}^2 \times f_{SW}$

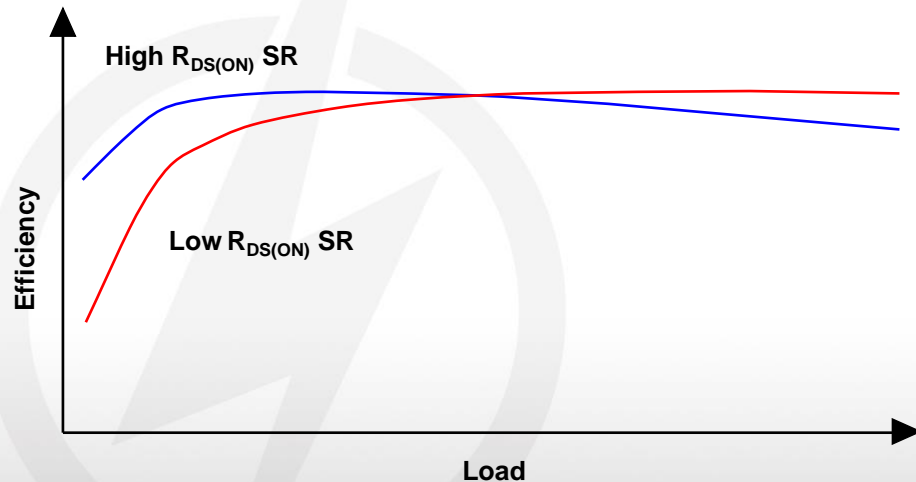- Lower $R_{DS(ON)}$ results in lower conduction loss, but larger C_{OSS} and C_{ISS}
- SR should be chosen to consider balance between conduction loss and switching loss
 - Efficiency is measured at 4-point average
 - 10% load efficiency concern




SR operation in CCM

Flyback

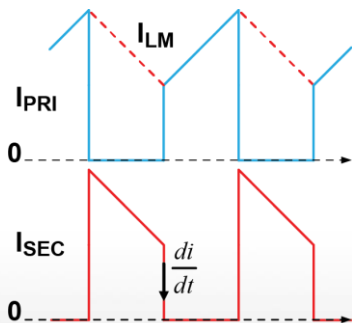


$$\frac{di}{dt} = \frac{V_O + \frac{V_{IN}}{N_{PS}}}{L_{LK}}$$

Forward

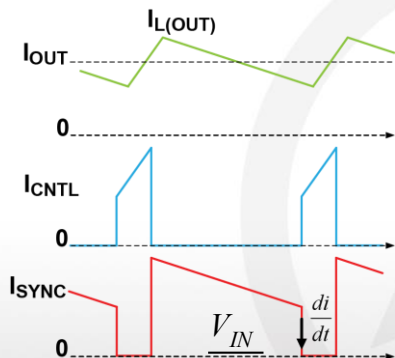

$$\frac{di}{dt} = \frac{\frac{V_{IN}}{N_{PS}}}{L_{LK}}$$


LLC

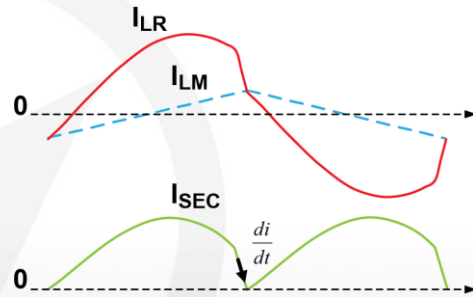

$$\frac{di}{dt} = \frac{V_O + \frac{V_{IN} + V_{CR}}{N_{PS}}}{\frac{L_R}{N_{PS}^2}}$$


- High di/dt caused by high voltage and low inductance
- Need to turn off SR really fast

V_{DS} sensing operation in CCM

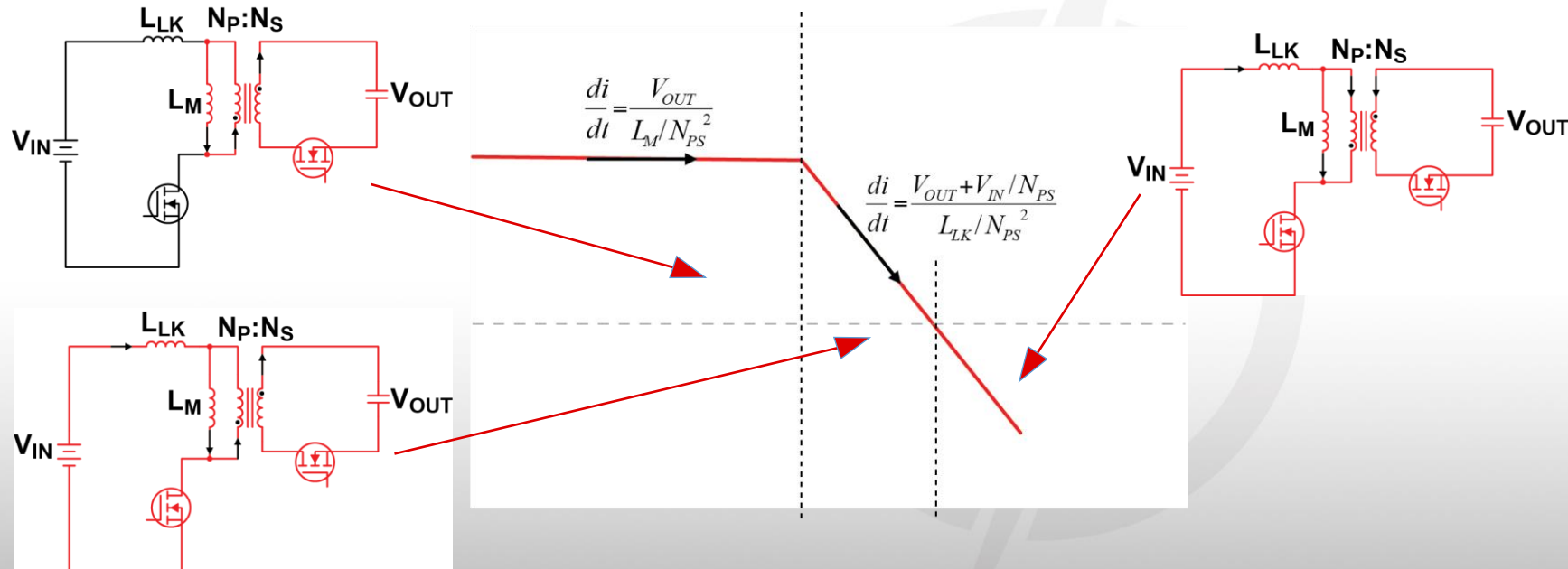

- di/dt is determined by leakage inductance
- Comparator needs to respond fast to minimize negative current

Diode operation in CCM

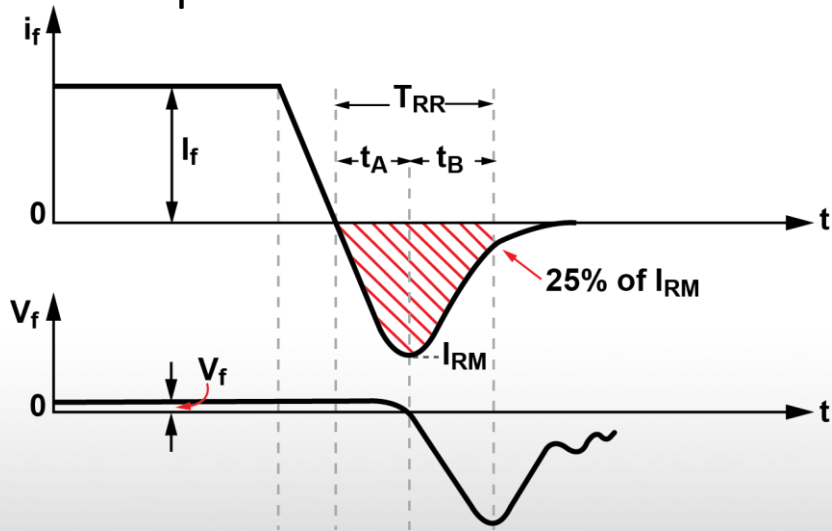


SR body diode and reverse recovery loss
 (Based on 100 kHz estimation)

SR	Q_{RR}	Reverse recovery loss
SR1@ 30 V V_{DS}	127 nC	0.381 W
SR2@ 75 V V_{DS}	385 nC	2.887 W


- Diode causes negative current due to reverse recovery
 - Fast reverse recovery time results in less negative current
 - Less Q_{RR} results in less switching loss
- Turning off SR too late is similar to large reverse recovery current

Early vs. late turn-off

Turn off SR early

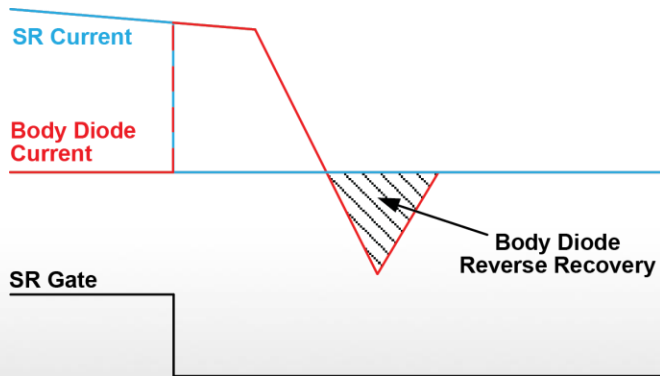


Turn off SR late

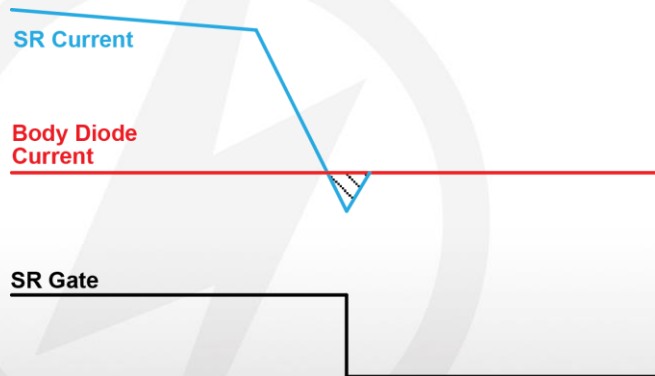

- Ideally, SR should turn off late but not too late to cause too much negative current
- Bottom line, shoot through time should be shorter than body diode reverse recovery time
- Beware CCM operation in “diode-mode” – startup and severe overload – where SR driver may have no bias rail
- Access to the turn-on signal of the main switch would be beneficial, for example: sync. buck


Dealing with ringing

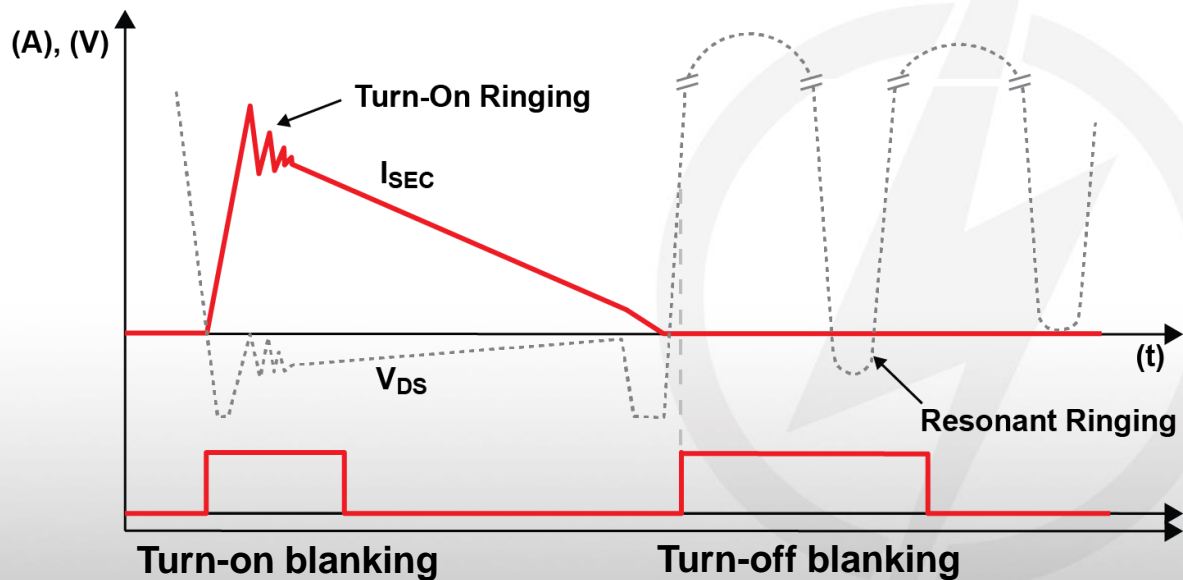


- Turn-on blanking is required to avoid false turn-off
- Turn-off blanking is required to avoid false turn-on

Special current shape, LLC converter

LLC resonant converter

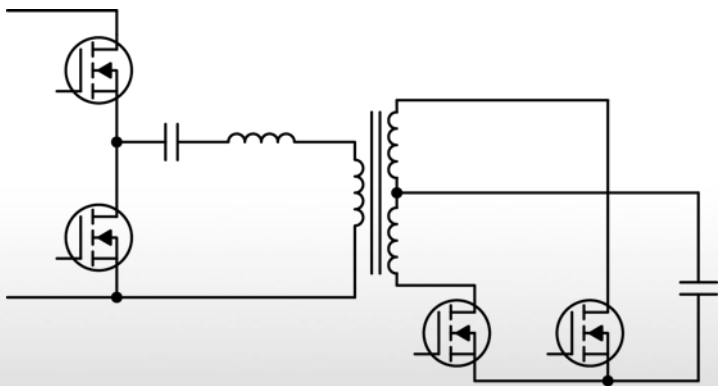


SR voltage and current

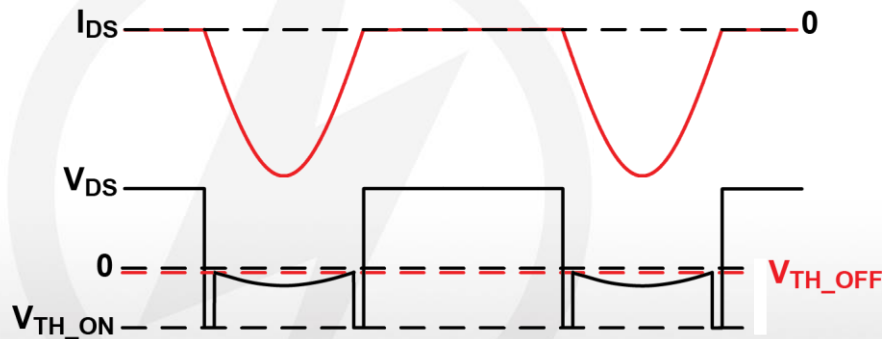


- Due to sinusoidal current shape, SR controller could interpret initial low current as current approaching zero and turn off SR too early
- To avoid early turn-off, a minimum on-time is required until current rises above turn-off threshold (V_{TH_OFF})

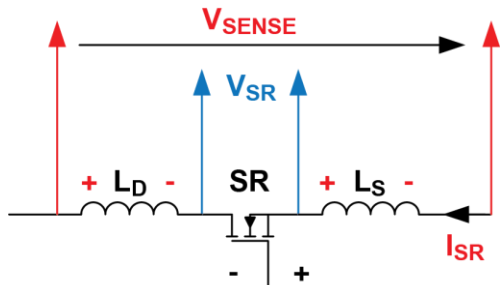Parasitic inductor impacts on SR operation



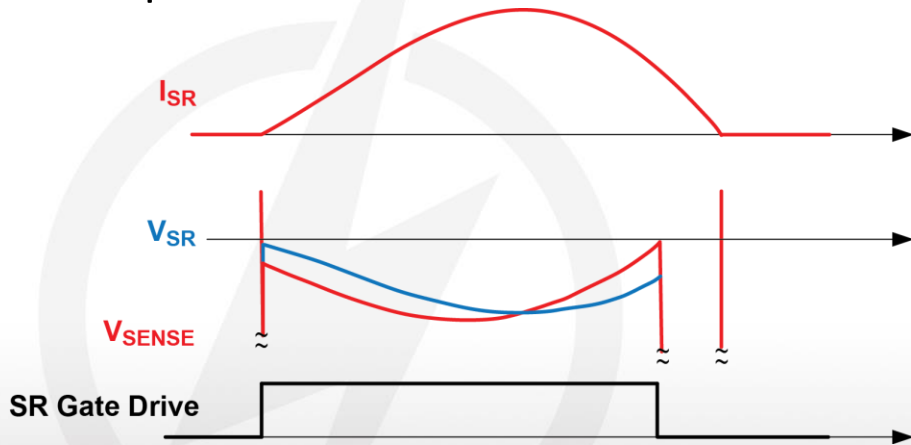
$$V_{SENSE} = - \left[I_{SR} \cdot R_{DS(ON)} + (L_D + L_S) \cdot \frac{dI_{SR}}{dt} \right]$$



- L_D and L_S are packaging parasitic inductances and can't be eliminated
- Negative di/dt on L_D and L_S causes voltage drop and offsets $R_{DS(ON)}$ drop
- Voltage drop causes SR early turn-off and generates more conduction loss
- Low package inductance devices should be used

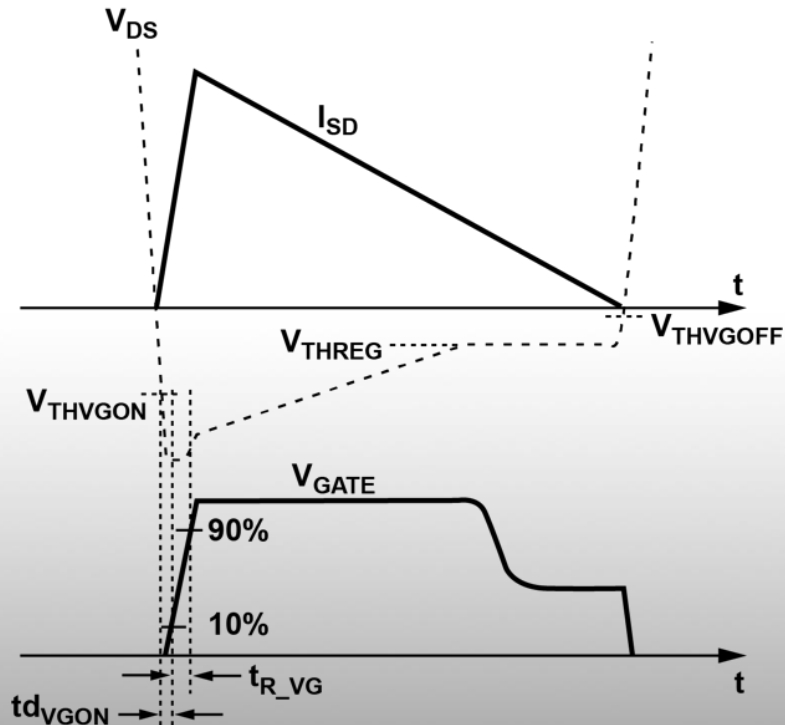
V_{DS} sensing and proportional gate drive – UCC24612, UCC24624



- When SR current is small, conduction loss is small
 - Instead of fully turning on SR into a resistor, SR can be controlled as a voltage source (like a low forward voltage drop diode)
- This extra control makes SR gate drive voltage proportional to current
 - Speed up turn-off, easier for CCM operation
 - Higher voltage drop, less sensitive to parasitic inductor
 - PMP21251 and UCC28780EVM-002 use UCC24612 to achieve high efficiency for LLC and active clamp flyback converters


Where to put the SR high-side?

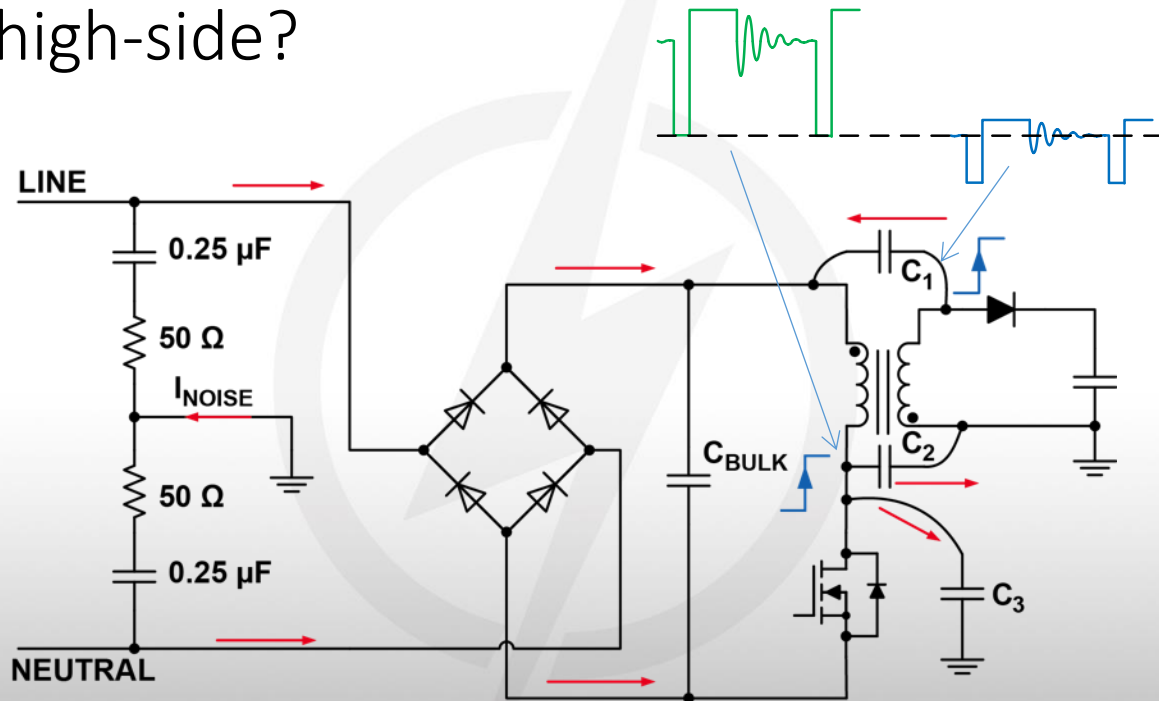- High-side SR:
 - Harder to drive gate, need level-shift
 - Need high-side bias
 - Better/lower EMI
- Currents on C_1 and C_2 are flowing in opposite directions and can cancel each other



Where to put the SR low-side?

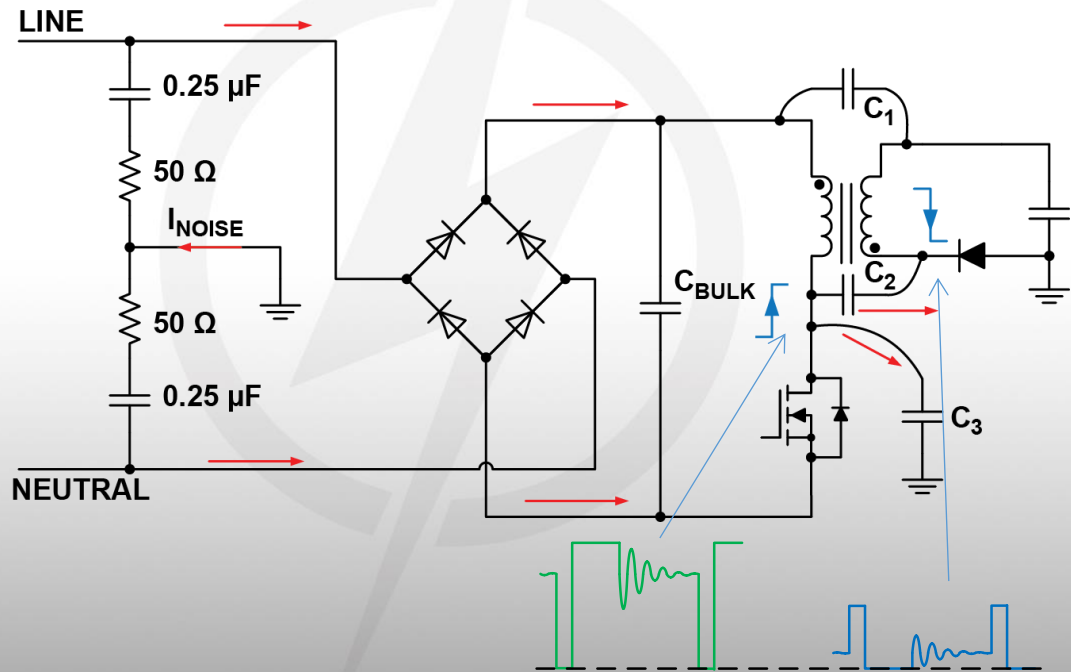- Low-side SR:
 - Gate referenced to output ground, easy drive, no level-shift
 - Ground-referenced bias for driver IC
 - Higher/worse EMI
- When moving rectifier to ground side, cancellation effect is lost



Summary

- SR MOSFET offers much lower on-state drop and conduction loss vs. diode
- SR may not always make sense
 - Depends on output voltage and output current/power level
- Beware the trade-offs between low $R_{ds(on)}$ and high C_{oss}
- Beware the impacts of going too low in $R_{ds(on)}$ with V_{ds} -sensing control
- Beware of early turn-off and body diode reverse recovery
 - Can actually be worse than short CCM shoot-through
- Beware of the EMI implications of low-side rectifier position

Further reading

- “Control and design challenges for synchronous rectifiers,” TI Power Supply Design Seminar 2017/8, <http://www.ti.com/lit/slup378>
- [Power Tips: How to Implement Synchronous Rectifiers in a Resonant LLC Half-Bridge](#)
- [Power Tips: What’s the best way to drive synchronous rectifiers in a flyback supply?](#)
- [Power Tips: Self-drive your synchronous rectifier](#)
- [Synchronous rectification boosts efficiency by reducing power loss](#)



© Copyright 2018 Texas Instruments Incorporated. All rights reserved.