

# High **VOLT** Interactive

Where power supply design meets collaboration


Maximizing efficiency of your LLC power stage:  
design, magnetics and component selection

Ramkumar S

## What will I get out of this session?


- In this session we will look at the design considerations for developing high efficiency LLC converters
- Reference design examples based on TI's LLC and SR controllers
- Part numbers mentioned:
  - UCC25630x
  - UCC24612
  - UCC24624
- Reference designs mentioned:
  - TIDA-01494 (Industrial AC/DC)
  - TIDA-01501 (PC PSU AC/DC)
  - TIDA-010015 (Industrial AC/DC, TV PSU)
  - TIDA-01495 (PC PSU AC/DC)
  - TIDA-01557 (PC PSU AC/DC)

## Industrial AC/DC, $D_{IN}$ rail

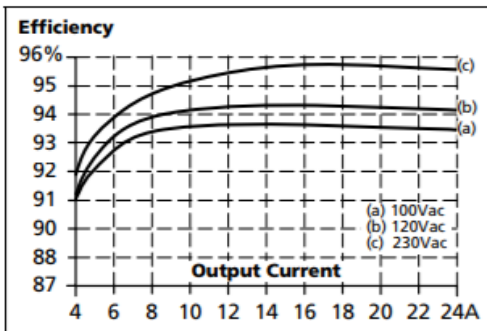

~97% efficiency  
DC/DC stage

## Next gen gaming PC adaptor

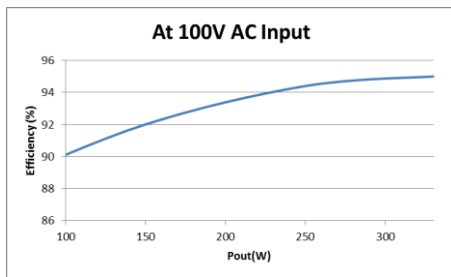

160x75x35 cm



~97% efficiency at 90V  
AC input

## Server PSU

>98% efficiency from PFC stage


80 Plus test type <sup>[4]</sup>	115V internal non-redundant			230V internal redundant				230V EU internal non-redundant					
Percentage of rated load	10%	20%	50%	100%	10%	20%	50%	100%	10%	20%	50%	100%	
80 Plus		80%	80%	80%							82%	85%	82%
80 Plus Bronze		82%	85%	82%		81%	85%	81%			85%	88%	85%
80 Plus Silver		85%	88%	85%		85%	89%	85%			87%	90%	87%
80 Plus Gold		87%	90%	87%		88%	92%	88%			90%	92%	89%
80 Plus Platinum		90%	92%	89%		90%	94%	91%			92%	94%	90%
80 Plus Titanium	90%	92%	94%	90%	90%	94%	96%	91%	90%	94%	96%	94%	

Overall peak efficiency >96%

Apart from using bridgeless PFC  
need >97.5% peak efficiency DC/DC stage




## Switching losses

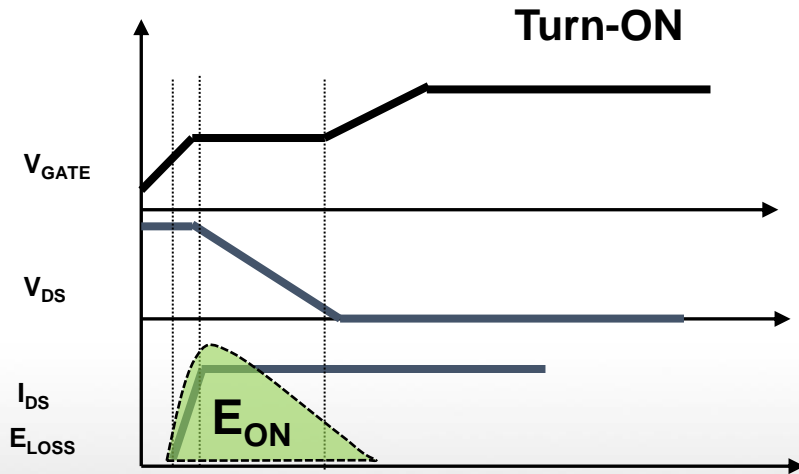
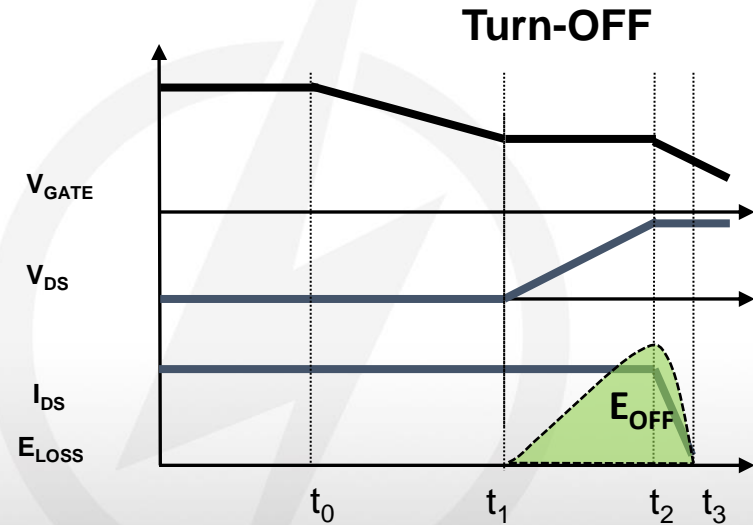
### In hard-switched converters


- Current & voltage overlap @ turn-on & turn-off
- Results in significant switching losses
- Limits switching frequencies, power density
- Increased EMI issues



- Additional losses due to output capacitance ( $C_{OSS}$ )
- In half-bridge configurations, reverse recovery ( $Q_{rr}$ ) losses can also be present
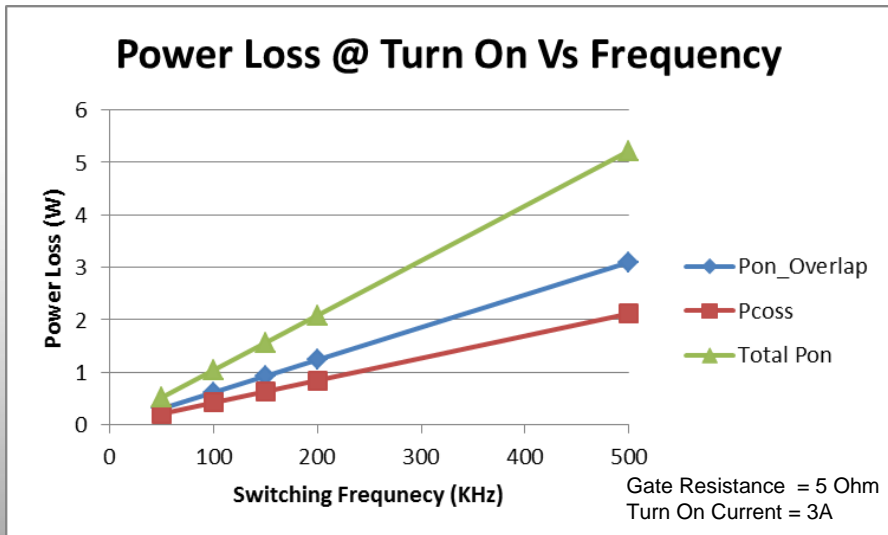
## Why soft switching?

- As the demand for higher power density in power supplies increases:
  - Need to increase switching frequency
  - Hence need to reduce losses associated with switching
- An example: using a state of the art SJ MOSFET in a 400W power supply IPB60R180C7




- For a hard switched half bridge converter operating @ 200KHz
- $P_{on}$  losses  $2 \times 2.1W = 4.2W$
- A soft switched converter will have >1% efficiency improvement in this example.
- And the EMI signature?

Data taken comparing CCM PFC with SiC diode
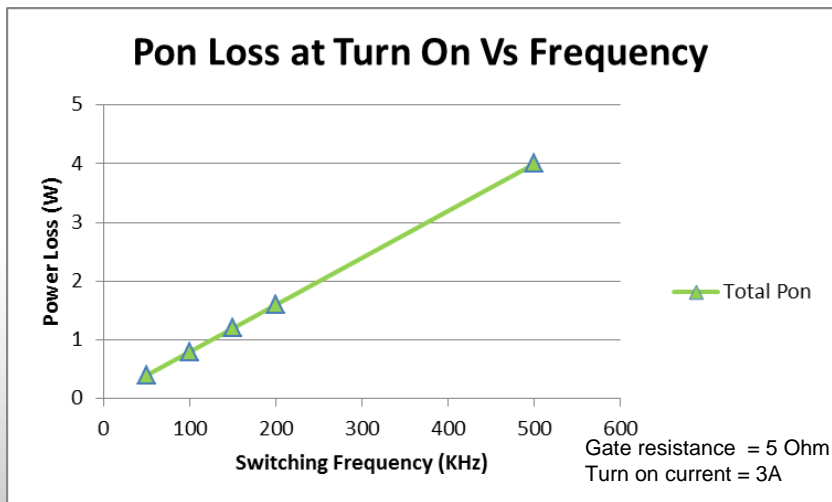
## If I use GaN, do I need to worry about switching loss?



- Let's look at a popular GaN in the market



- Compared to the latest generation SJ MOSFET, under hard switching:
  - GaN has lower turn-off losses
  - Turn-on losses are almost similar
- Higher  $dv/dt$  also results in more EMI concerns.


Soft switched topologies are even more important for exploiting GaN

## Resonant converters

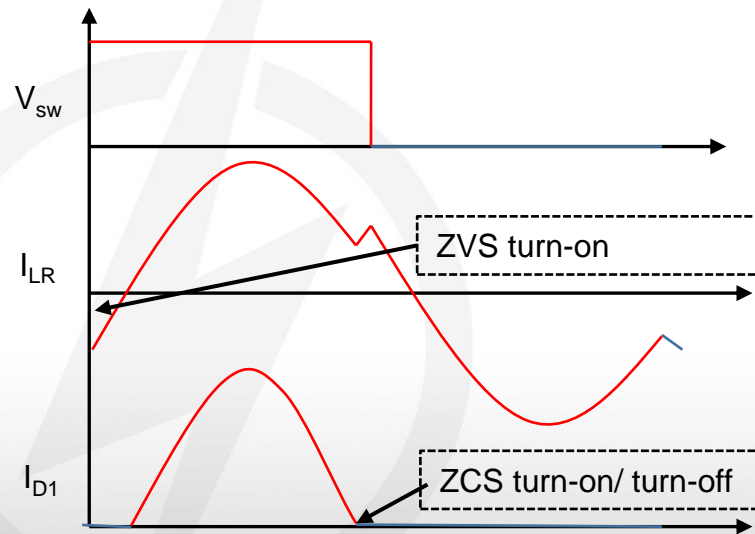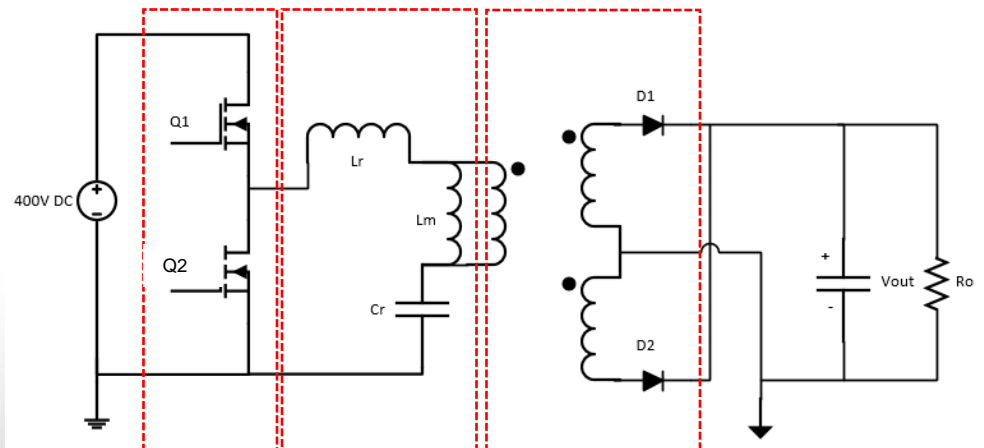

- The switch network on the primary applies a square wave to the resonant tank
- The resonant tank's fundamental frequency is close the frequency of the square wave
- The rectifier on the secondary side applies a rectified and filtered sinusoidal current to the load

## LLC resonant converter

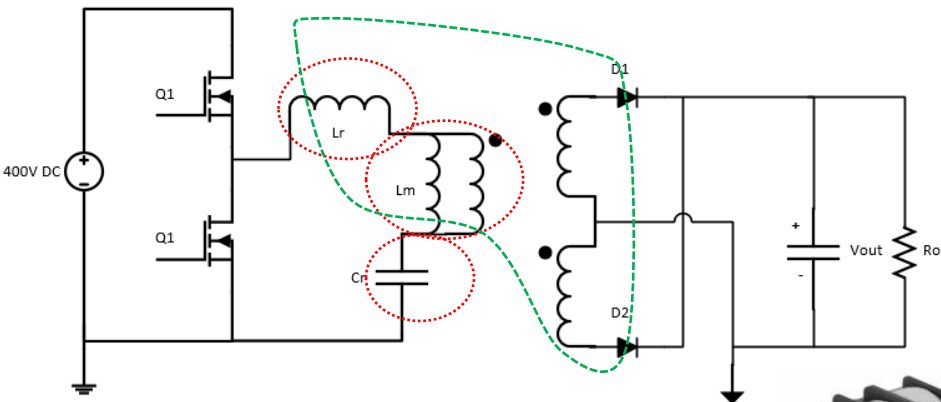

The  $L_r$ ,  $L_m$  &  $C_r$  form the resonant tank

Using integrated magnetics, it's possible to implement  $L_r$  (leakage inductance) &  $L_m$  (magnetizing inductance) using the same transformer core





## Advantages of LLC converters


- The low magnetizing inductance enables ZVS even at no load (higher magnetizing current)
- LLC converters can regulate output voltage even under no load conditions
- Can be designed to operate in a narrow frequency range over a wide output load range




## The gain curve

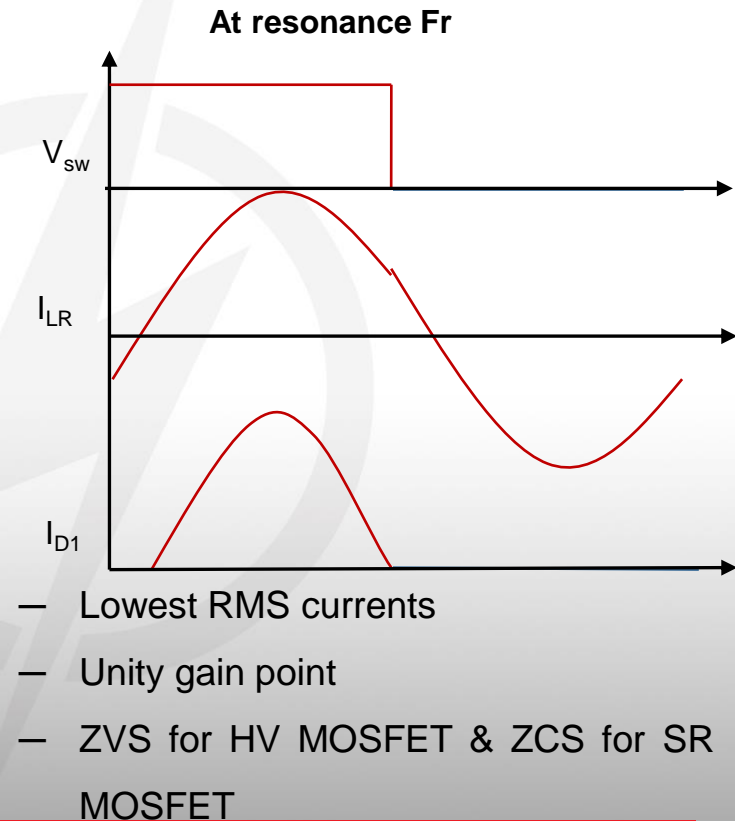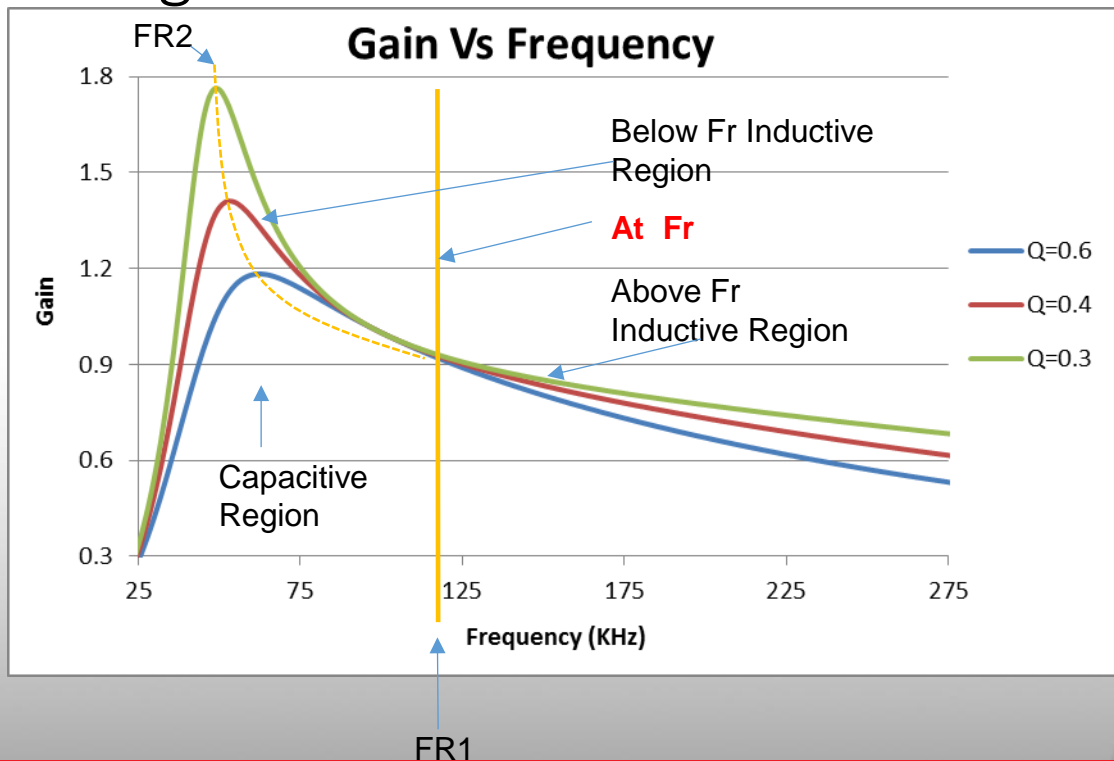

## The gain curve

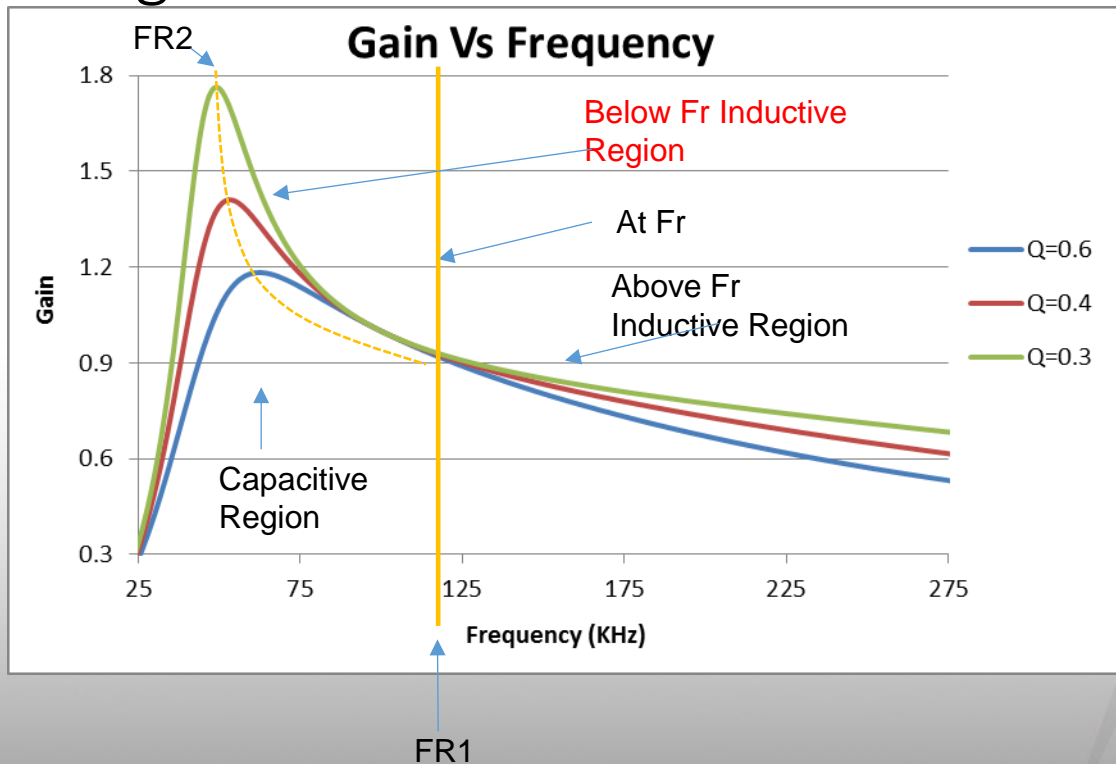


### Below Fr Inductive region

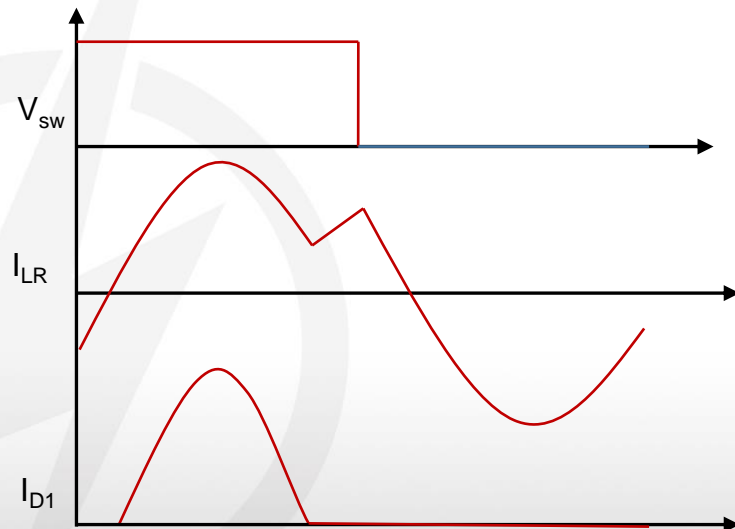


- Higher RMS currents
- Can get high gain
- ZVS for HV MOSFET & ZCS for SR MOSFET

## The gain curve

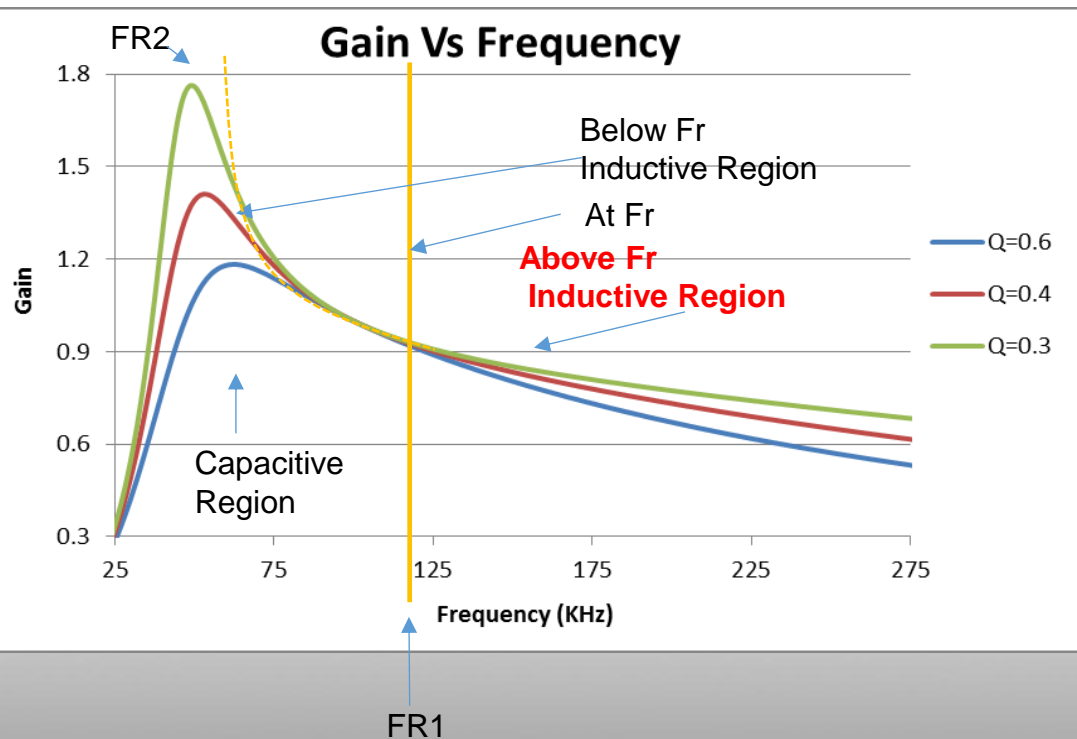

### Above Fr inductive region

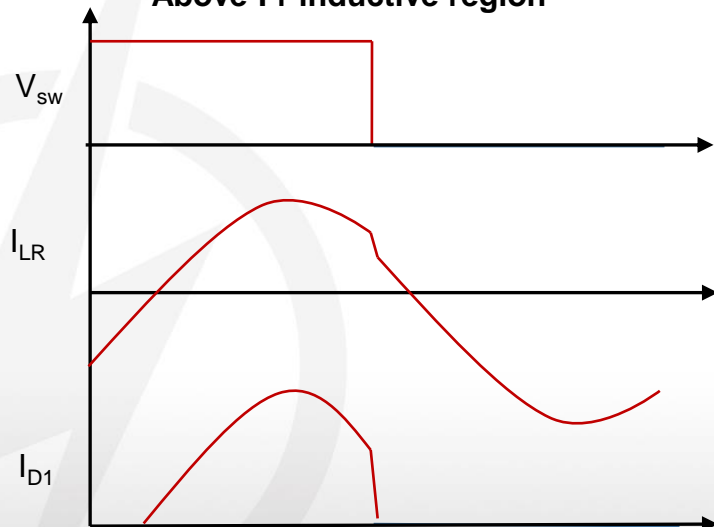

- Frequency Increases to operate at light load
- ZVS for HV MOSFET
- High  $di/dt$  on SR MOSFET at turn-off results in  $Q_{rr}$  losses

## Design procedure

- As an example we look at a 500W HB-LLC design
- The key design input parameters are given below


Parameter	Value
Output voltage & current	24V, 21A
Nominal input voltage	390V
Minimum input voltage*	310V
Full load efficiency @ nominal input	96.5%

- The minimum input voltage is EE dependent
  - In industrial, server PSU, it could be based on holdup time
  - In TV power supplies, it might need to operate even from 90VDC (standby load conditions)
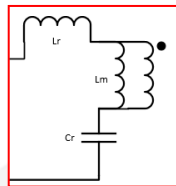
## Dimensioning the Resonant Tank


Resonant tank components are very critical for high efficiency:

- High  $L_m$  reduces circulating current, hence reduces conduction losses
- But high  $L_m$  reduces the available energy at light load to create ZVS condition
- Ratio of  $\left(\frac{L_m}{L_r}\right) = L_n$  &  $Q$  of the tank determines the  $M_{max}$
- $Q$  is determined by  $L_r$  &  $C_r$



If  $L_m$  is very high

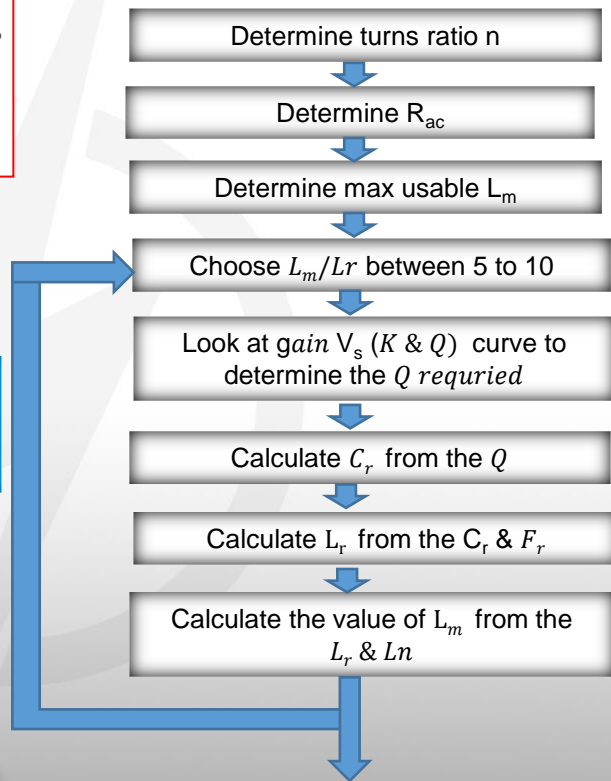- Multiple parameters affect the choice
- How do we start?



## Effect of magnetizing inductance on dead time

- Magnetizing inductance ( $L_m$ ) determines the dead time ( $T_d$ ) required to achieve ZVS
- As  $L_m$  increases the  $T_d$  increases
- As  $L_m$  increases, primary RMS currents ( $I_{rms}$ ) decrease up to a certain point


$$L_m \leq \left( \frac{T_d}{Fr * 16 * C_{OSSeq}} \right) = 274 \mu H$$

<b>Fr</b>	<b>100kHz</b>
<b>T<sub>d</sub></b>	<b>200ns</b>

A similar converter designed with LMG3410 70mΩ R<sub>dson</sub> results in Max L<sub>m</sub> = 398μH, ~60% reduction in conduction losses

Parameter	Symbol	Values			Unit
		Min.	Typ.	Max.	
Input capacitance	C <sub>iss</sub>	-	1330	-	pF
Output capacitance	C <sub>oss</sub>	-	24	-	pF
Effective output capacitance, energy related <sup>2)</sup>	C <sub>o(er)</sub>	-	44	-	pF
Effective output capacitance, time related <sup>3)</sup>	C <sub>o(tr)</sub>	-	453	-	pF

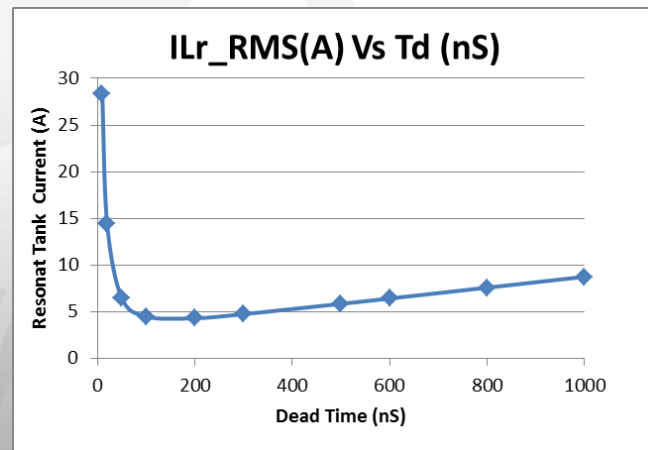MOSFET with  $R_{dson} = \sim 150m\Omega$



- LLC tank max gain:  $M_{max}$

Tank gain at  $V_{innom}, M_{nom} = 0.95$

$$M_{max} = M_{nom} * \left( \frac{V_{in_{nom}}}{V_{in_{min}}} \right) = \frac{390}{310} = 1.19$$

— High value of  $L_n$  results in lower losses


- Find required  $Q$  to get peak gain 110% of  $M_{max} = 1.31$
- Calculate the value of the  $C_r$ ,  $L_r$  &  $L_m$  from this

- $C_r = \frac{1}{2\pi * Fr * Q * Rac} \cong 94nF$

- $L_r = \frac{1}{(2\pi * Fr)^2 * Cr} = 27\mu H$

- $L_m = L_n * L_r = 243\mu H$

Lower than max  $L_m$

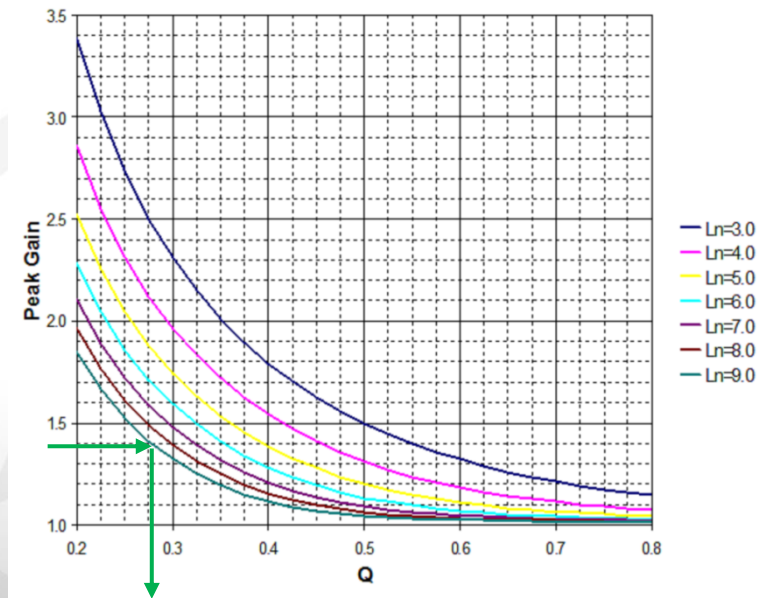

Choosing  $L_n = 9, Q = 0.275$

## Component selection & losses: HV MOSFET

### Conduction loss


Resonant inductor current has 2 components:

- Load current carried by the HV MOSFET  $I_{pri_{ref}}$
- Resonant tank magnetizing current  $I_{lm}$

$$I_{pri_{ref}} = \frac{\pi}{2\sqrt{2}} \left( \frac{I_{out}}{N} \right) = 3.04 \text{ A}$$

$$I_{lm} = \left( \frac{N * V_{out}}{4 * F_{sw} * L_m} \right) = 2.013 \text{ A}$$
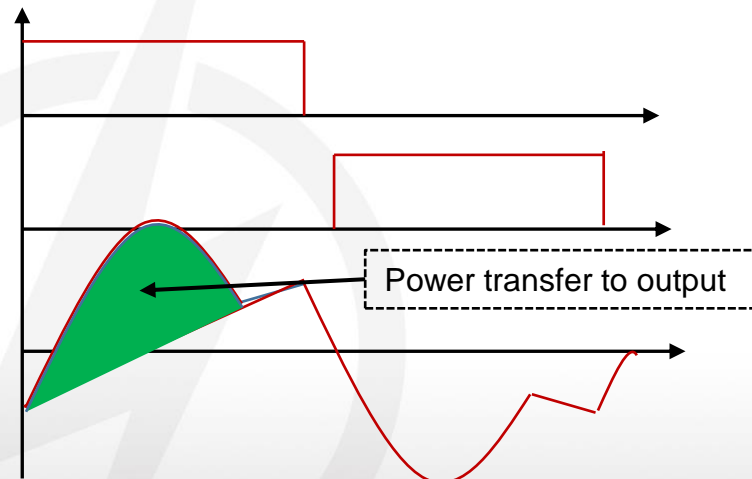
$$I_{lr} = \sqrt{I_{pri_{ref}}^2 + I_{lm}^2} = 3.64 \text{ A}$$



$$I_{HV_{rms}} = I_{lr} / \sqrt{2} = 2.57 \text{ A}$$

$$IPD60R145CFD7 R_{dson} = 145m\Omega$$

$$P_{Cond_{HV}} = I_{HV_{rms}}^2 * R_{ds} = 0.957 \text{ W}$$



## Component selection & losses: HV MOSFET

### Switching loss: turn-off

At full load, converter operates mostly closer to  $Fr$

$$IHV_{toff} = I_{lm} = 1.89 A$$


$$t_{off} = t_2 + t_3$$

$$t_{off} = (Q_{gd}/V_{ds}) * R_{gate} * \left( \frac{V_{ds} - V_{pl}}{V_{pl}} \right) + C_{iss} * R_{gate} * Ln * \left( \frac{V_{pl}}{V_{th}} \right)$$

$$t_{off} = 14.1nS$$

$$E_{off} = 0.5 * V_{ds} * IHV_{toff} * toff = 5.35\mu J$$

$$PSw_{HV} = F_{sw} * E_{off} = 0.535W$$

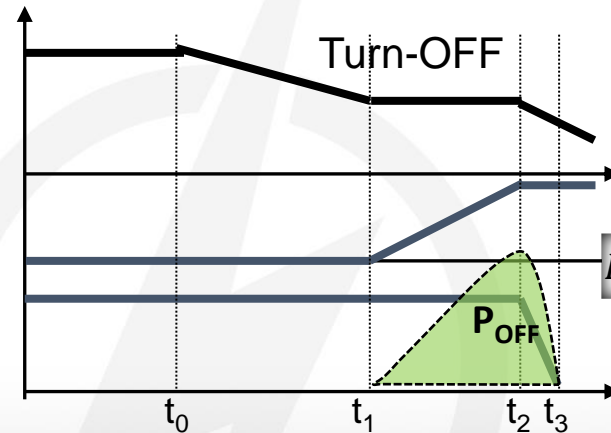

IPD60R145CFD7

Symbol	Parameter	Value
$C_{iss}$	Input capacitance	1060 pf
$C_{rss}$	Reverse transfer capacitance	2.2pF
$R_{gate}$	Gate resistance	5Ω
$Q_{gd}$	Miller charge	12nF
$V_{pl}$	Miller plateau voltage	5.5V
$V_{th}$	Threshold voltage	3V

## Component selection & losses: SR MOSFET

*Using CSD19501KCS, UCC24612*

$$ISR_{rms} = I_{out} * \frac{\pi}{4} = 16.4 A$$

$$P_{cond_{SR}} = ISR_{rms}^2 * R_{ds_{on}} = 1.4W$$

$$P_{diode_{SR}} = F_{sw} * ISR_{turnoff} * V_f * T_{diode} = 0.18W$$

$$P_{SRV_{sw}} = F_{sw} * Q_g * V_{drive} = 34mW$$


$$P_{SR_{tot}} = 1.63 W$$

Reduces losses by **3W** on each leg compared with Schottky diode based rectifier

*Below  $F_r$   
operation*




*Reliable  
above  $F_r$   
operation*

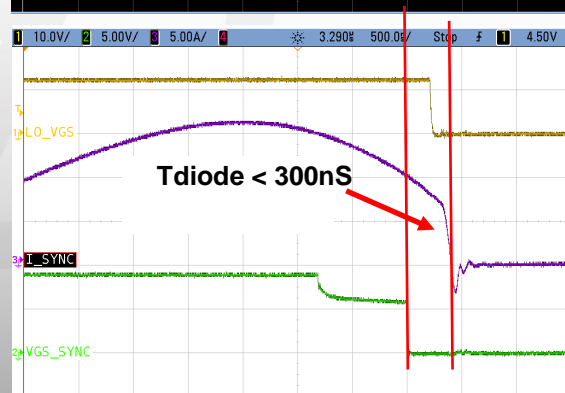

## Magnetics design : transformer
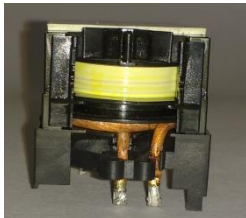
### Integrated magnetics:


Use single magnetic structure to implement resonant inductor and transformer



- Occupies less space
- Requires special (split) bobbin, but cheaper if manufacturing quantity is high
- Less core losses, increases efficiency at light load
- Increased “AC resistance” due to proximity effect. Higher conduction loss.

### Discrete magnetics:

Use two separate magnetic structure

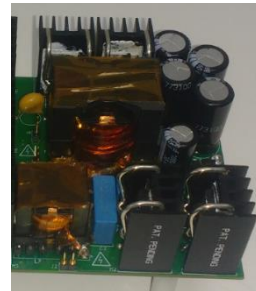

- Slightly more expensive
- Occupies more space
- Huge reduction in “proximity” effect. Reduces “AC resistance” conduction loss significantly.
- For high output current applications, integrated magnetics reduce conduction losses
- More core choices for high performance applications

## Magnetics design : transformer

### Calculating number of turns:

Secondary turns:  $N_s$

$$N_s = \frac{V_{out}}{2 * F_{res} * \Delta B * A_e} = 3 \text{ turns}$$

Primary turns:  $N_p$


$$N_p = 7.67 * N_s = 23 \text{ turns}$$

Use the operating points  $F_{res}$  &  $\Delta B$  to estimate the core loss before choosing

$$P_{trans_{FE}} = \frac{120KW}{m^3} * V_e = 1.5 W$$

$$P_{trans_{FE}} = 1.5 W$$

Symbol	Parameter	Value
Core geometry		PQ3230
$A_e$	Effective area	162mm <sup>2</sup>
$A_n$	Window area	99mm <sup>2</sup>
$V_e$	Effective volume	12500mm <sup>3</sup>
MLT	Mean length of turn	66.7mm <sup>2</sup>

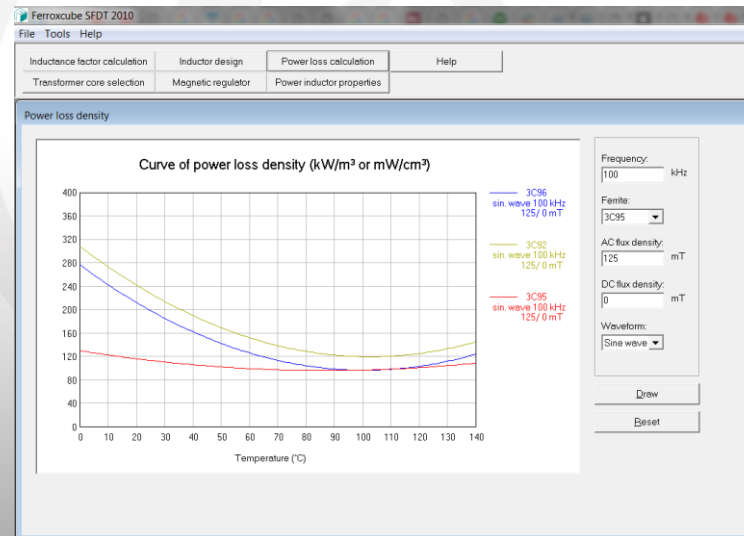

## Magnetics design : transformer

- Take bobbin fill factor ( $K$ ): 30%
- Equal division for primary and secondary

### Secondary Winding Loss:

$$L_{wire_{sec}} = MLT * N_s = 200 \text{ mm}$$

$$A_{wire_{sec}} = \frac{\frac{K}{2} * A_n}{2 * N_s} = 2.22 \text{ mm}^2$$

$$R_{ac_{sec}} = 1.5 * R_{dc_{sec}} = \rho_{cu} * \frac{L_{wire_{sec}}}{A_{wire_{sec}}} = 1.66 \text{ m}\Omega$$

$$P_{trans_{sec_{cu}}} = 2 * I_{L_{rms}}^2 * R_{dc_{sec}} = 1342 \text{ mW}$$

$$P_{trans_{cu}} = 2.02 \text{ W}$$

Symbol	Parameter	Value
$A_n$	Window area	99mm <sup>2</sup>
$MLT$	Mean length of turn	66.7mm
$N_p$		23
$N_s$		3

### Primary Winding Loss:

$$L_{wire_{pri}} = MLT * N_p = 1518 \text{ mm}$$

$$A_{wire_{pri}} = \frac{\frac{K}{2} * A_n}{N_p} = 0.65 \text{ mm}^2$$

$$R_{ac_{pri}} = 1.5 * R_{dc_{pri}} = \rho_{cu} * \frac{L_{wire_{pri}}}{A_{wire_{pri}}} = 43.76 \text{ m}\Omega$$

$$P_{trans_{pri_{cu}}} = I_{l_{rms}}^2 * R_{dc_{pri}} = 680 \text{ mW}$$

## Magnetics design : resonant inductor

$$I l r_{pk} = 1.414 * I l r = 4.55A$$

$$L_r = 17 \mu H$$

With  $B_{pk} = 0.16$  at  $I l r_{pk}$

### Calculate resonant inductor turns:

$$N_r = \frac{L_r * I l r_{pk}}{B_{pk} * A_e} = 12.2 \text{ turns}$$

### Core losses:

Following the same procedure as the transformer  
Estimate core loss from Ferroxcube tool

$$Pres_{FE} = 250 \left( \frac{KW}{m^3} \right) * V_e = 0.71 W$$

$$Total Pres = 1.014 W$$

Symbol	Parameter	Value
Core geometry		PQ2020
$A_e$	Effective area	62.9mm <sup>2</sup>
$A_n$	Window area	36mm <sup>2</sup>
$V_e$	Effective volume	2850mm <sup>3</sup>
$MLT$	Mean length of turn	44mm

### Conduction losses:

Assuming ( $K$ ) 30% fill factor, AC resistance factor 2.7  
 $L_{wire_{sec}} = MLT * N_r = 528 \text{ mm}$

$$A_{wire_{res}} = \frac{K * A_n}{N_r} = 0.9 \text{ mm}^2$$

$$R_{dc_{res}} = 1.5 * \rho_{CU} * \frac{L_{wire_{sec}}}{A_{wire_{sec}}} = 16.7 \text{ m}\Omega$$

$$Pres_{cu} = I l r^2 * R_{dc_{res}} = 0.33W$$

Proximity effect  
from 2 layer winding


## Total losses

Component	Loss/ Pc (W)	Total loss(W)
HV MOSFET	1.759	3.568
SR MOSFET	1.63	3.26
LLC transformer		3.52
Resonant inductor		1.014
Total		11.36

*Using GaN  $R_{dson}$  70m $\Omega$ , very low  $E_{off}$ , can reduce loss by 1.8W*

*Using SR driver which minimizes dead time increasing efficiency*

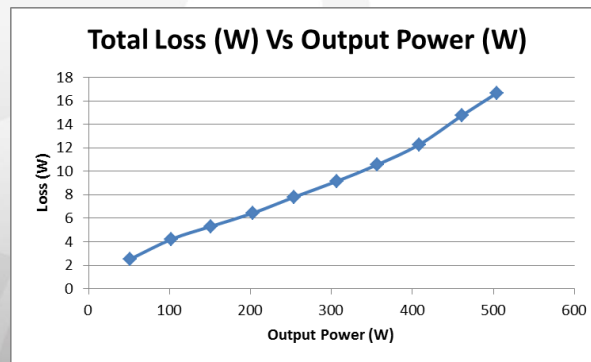- The estimated losses above do not include losses from resonant capacitor, output filter components or transformer termination losses
- Overall, the losses for this design will be up to 16W



*Actual data for TIDA – 010015*

## 80 PLUS® platinum, 93% efficiency, super transient, 450W AC/DC - single-layer PCB TI Design: TIDA-01501




Leading transient performance (half duty-cycle response for line transient & dynamic load)  
Meets 80 PLUS Platinum specs peak efficiency 92.4% @ 115V<sub>AC</sub>, 94.0% @ 230V<sub>AC</sub>  
**Single layer PCB design to achieve low solution cost**  
UCC28180, UCC256301, UCC24612

## 24V, 480W nominal 720W peak, >93.5% efficient, robust AC/DC industrial power supply TI Design: TIDA-01494



- Meet 80 PLUS Platinum overall efficiency >93.5% with peak efficiency > 94% at 230V<sub>AC</sub>
- ZCS avoidance in the LLC stage, enabling wider input voltage range operation and robustness
- Peak output power of up to **720W for a short duration of 3 seconds**
- UCC28180, UCC256301, UCC24612
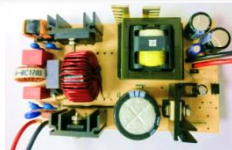
## 93% efficiency, 200W, fast transient, desktop PC PSU reference design TI Design: TIDA-01557



No load <0.1W; >50% at 0.25W; > 79% at 2W; >81% at 4W  
Meet 80 PLUS Platinum spec peak efficiency 93% @ 230V<sub>AC</sub>  
Output OCP, OVP, short-circuit protection, OTP with single layer PCB  
UCC28056, UCC256301, UCC24612



## 480W, thin profile (<17 mm), 94% efficiency, fast transient response AC/DC TI Design: TIDA-01495



Thin profile <17 mm with small PCB form factor of 185 x 110 mm  
PFC phase shedding and advanced burst mode in the LLC enables high efficiency at light load conditions  
Peak efficiency of 94.1% @ 230 V<sub>AC</sub>, light load efficiency >85% (230 V<sub>AC</sub>) at 5% load  
UCC28063, UCC256303, UCC24612

## 94.5% efficiency, 500W industrial AC/DC with <250mW standby



**Peak efficiency 95% @ 230V<sub>AC</sub> and 93.5% @ 115V<sub>AC</sub>**  
PFC phase shedding, burst mode in the PFC, LLC enables high efficiency at light load conditions  
Peak efficiency 95% @ 230V<sub>AC</sub> and 93.5% @ 115V<sub>AC</sub>  
UCC28064, UCC256303, UCC24612

## Conclusions & key takeaway

- Resonant converters are a preferred topology for high efficiency isolated DC/DC
- With GaN switches finding more of a commercial usage, soft switched topologies remain relevant
- We looked at ways to estimate losses in the major components of an LLC converter , which can be used to make optimized design choices
- Multiple TI Designs developed based on TI's latest generation LLC and SR controllers developed to act as a quick start reference for industrial/consumer AC-DC applications