

Designing a Front-End Circuit for Driving a Differential Input ADC


TI Precision Labs – Op Amps

Presented and prepared by Morgan Haggerty

Topics to review before continuing

- Fully Differential Amplifiers
 - [TI Precision Labs – Op Amps: Fully Differential Amplifiers – Introduction to FDAs and Differential Signaling](#)
- Noise
 - [TI Precision Labs – Op Amps: Noise 1](#)
 - [TI Precision Labs – Op Amps: Fully Differential Amplifiers – Noise Analysis, Advanced Compensation Techniques, and Variable Gain FDAs](#)
- Stability
 - [TI Precision Labs – Op Amps: Stability 1](#)
 - [TI Precision Labs – Op Amps: Fully Differential Amplifiers – FDA stability and Simulating Phase Margin](#)
- Total Harmonic Distortion
 - [Application Note: Maximizing Signal Chain Distortion Performance Using High Speed Amplifiers](#)
- Settling Time
 - [TI Precision Labs – ADCs: Building a SAR ADC Model](#)
 - [TI Precision Labs – ADCs: Refine the Rfilt and Cfilt Values](#)

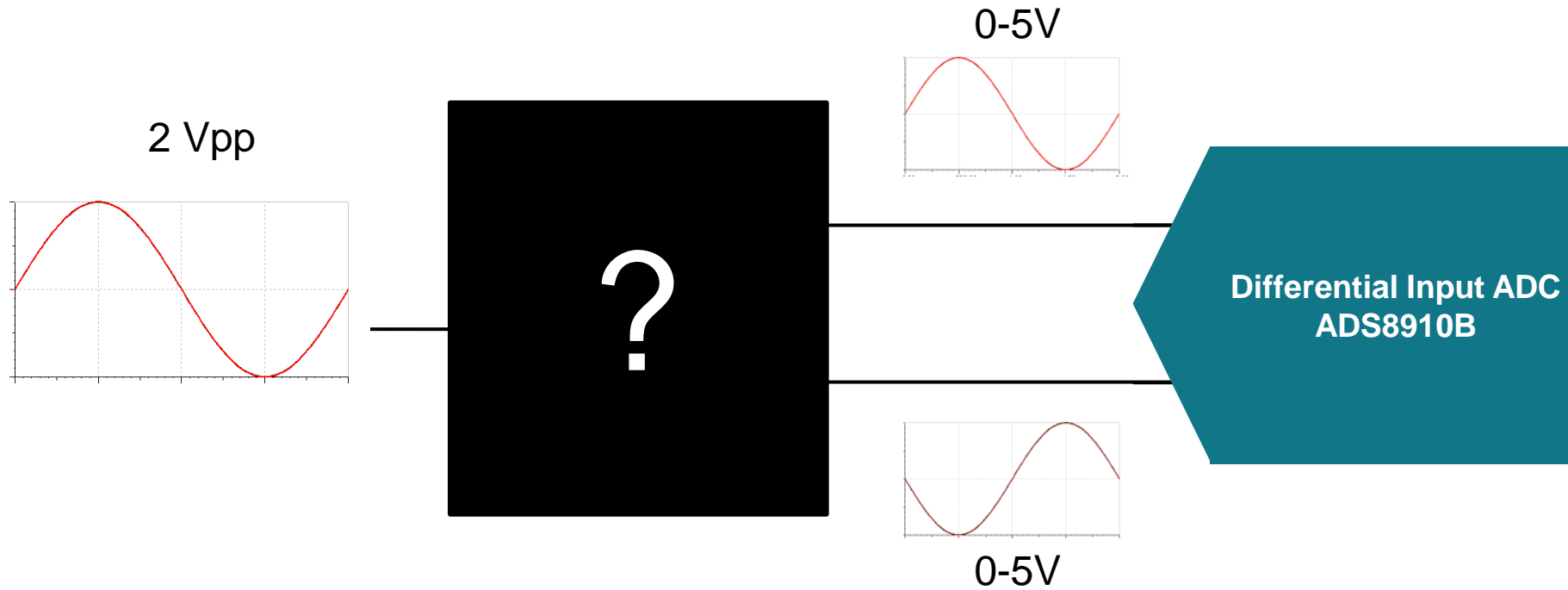Converting a single-ended signal to differential



ADC Driver Requirements

Input Signal

- Single ended signal
- $2 V_{pp}$ amplitude
- 500 kHz frequency

ADS8910B Specifications

- Differential Input
- ADC input voltage: $-V_{REF}$ to V_{REF}
- 1 MSPS
- THD $f_{in} = 100$ kHz is -110 dB
- 18 bit resolution

- Least Significant Bit (LSB) = $\frac{\text{Full Scale Range}}{2^N} = \frac{2 \times 5V}{2^{18}} = 38.14 \mu V$


PARAMETER	TEST CONDITIONS	MIN	TYP	MAX	UNIT
ANALOG INPUT					
FSR	Full-scale input range (AINP – AINM)	$-V_{REF}$		V_{REF}	V
V_{IN}	Absolute input voltage (AINP and AINM to REFM)	0		V_{REF}	V

ADC driver requirements


- The differential range is -5V to 5 and the range of each input is 0 to 5gain of 4.6 to allow for dynamic range and for some room
- Amplifier supply voltage of 5.2V
- Bandwidth > 500 kHz
- Better or equal distortion performance to maintain signal fidelity
- Good noise performance to maintain signal fidelity
- Minimize the power consumption

Specifications	Units	OPA625	Comment	THS4551
Number of Channels	#	2		1
Total Supply Voltage min	V	2.7		2.7
Total Supply Voltage max	V	5.5	Ability to maximize dynamic range of the ADC (5V)	5.4
GBW typical	MHz	120	Sufficient Bandwidth	135
Voltage Noise typical	nV/ $\sqrt{\text{Hz}}$	2.5	Low noise to maintain signal fidelity	3.3
THD typical	dBc	-110	Low distortion to maintain signal fidelity	-138
Iq per channel (mA)	mA	2	Low power consumption	1.35

Discrete Solution

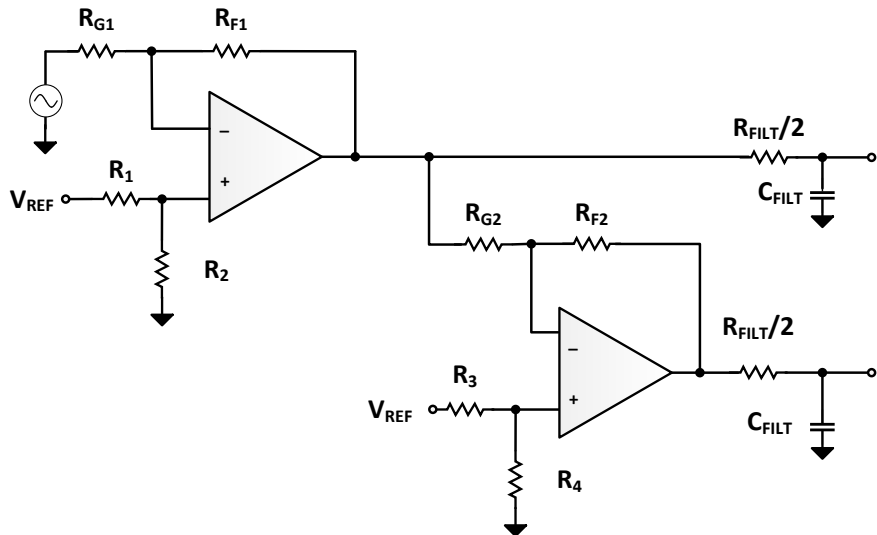

Fully Differential Amplifier Solution

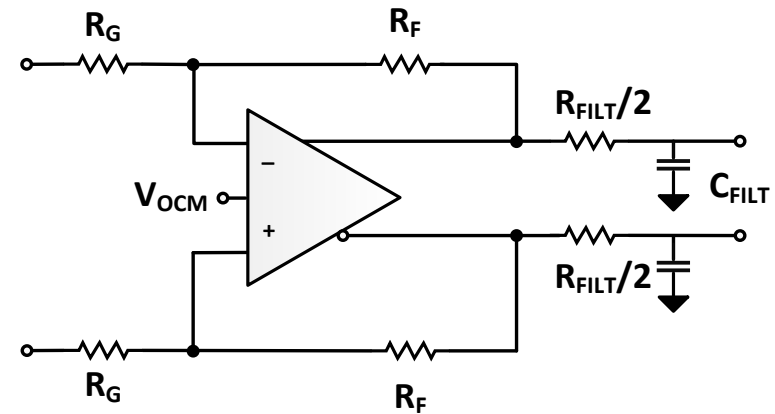

Discrete Solution Resistor Values

Amplifier 1 - Gain Resistors

$$V_{in} = 2V_{pp}$$

$$V_{out} = 4.6V_{pp}$$

$$G = V_{out}/V_{in} = 2.3$$

$$G_{inverting} = -\frac{R_F}{R_G} = -2.3 \frac{V}{V}$$

RF1 = 246 RF2 = 107 – Analog engineers calculator



Amplifier 1 - V_{SHIFT} Resistors

$$G_{non\ inverting} = 1 + \frac{R_F}{R_G} = 3.3 \frac{V}{V}$$

$$V_{OCM} = 2.5 V$$

$$V_o = \frac{V_{OCM}}{G} = \frac{2.5V}{3.3} = 0.7575V$$

$$i_1 = i_2$$

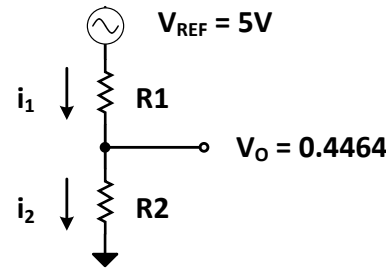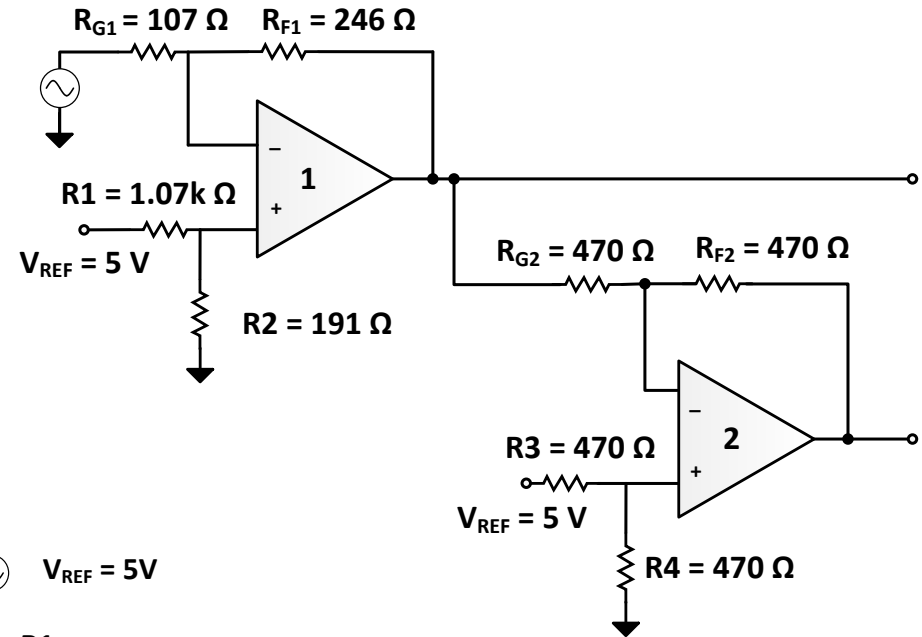

Discrete Solution Resistor Values

Amplifier 2 - Gain Resistors

$$G_{inverting} = -\frac{R_{F2}}{R_{G2}} = -1 \frac{V}{V}$$


$$R_{F2} = R_{G2} = 470 \Omega$$

Amplifier 2 - V_{OCM} Resistors

$$G_{non\ inverting} = 1 + \frac{R_{F2}}{R_{G2}} = 2$$

In a voltage divider, when the resistors are the same value the input voltage will be divided in half.

$$R_3 = R_4 = 470 \Omega$$

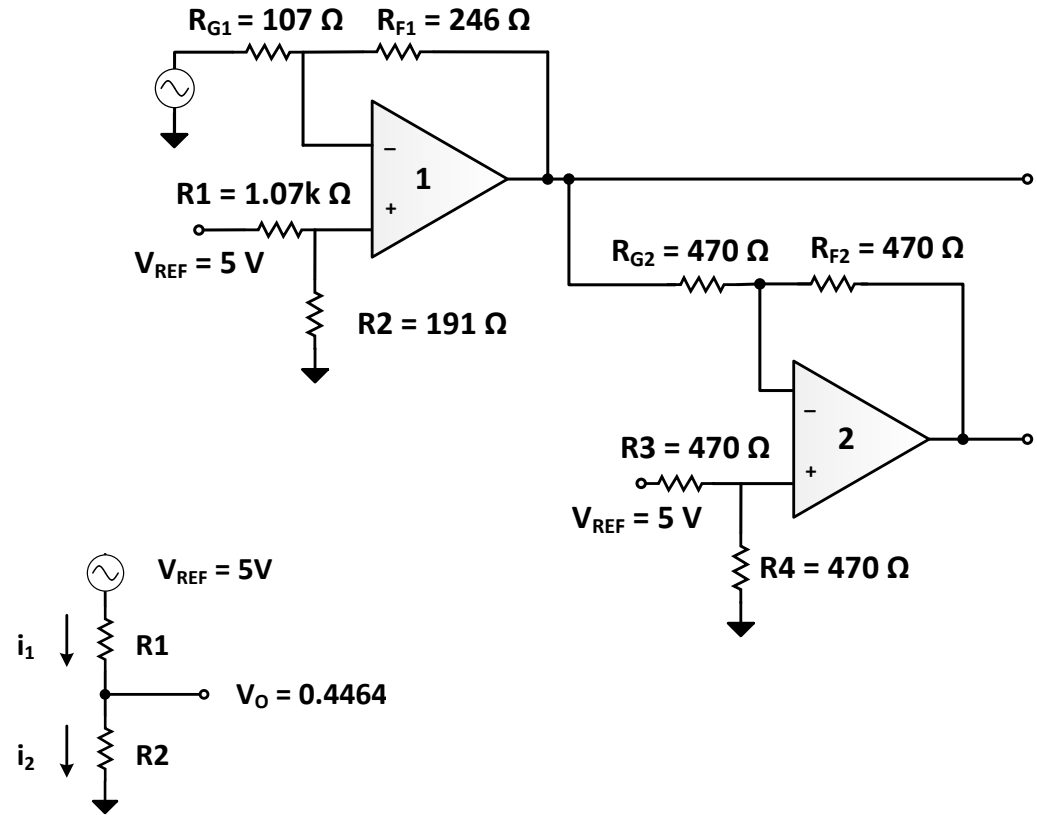


FDA Solution Resistor Values

Output Common Mode Voltage

FDA's have a V_{OCM} pin

Voltage at the V_{OCM} pin sees a $G = 1$

No resistors are required

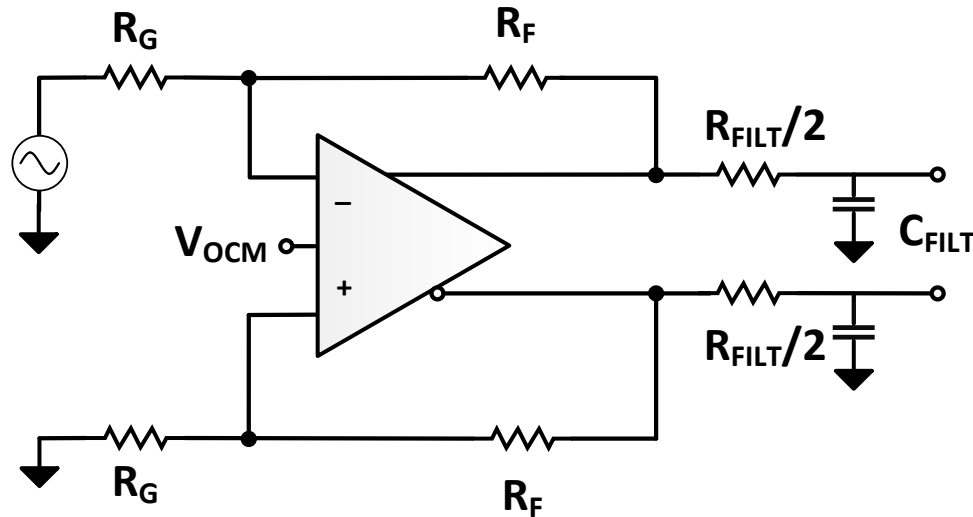

To maximize the dynamic range of the input of our ADC:


$$R_F = 493$$

$$R_G = 107$$

$$G = -\frac{R_F}{R_G} = -\frac{493}{107} = -4.6$$

Both Solutions Resistor Values

Charge Bucket Filter

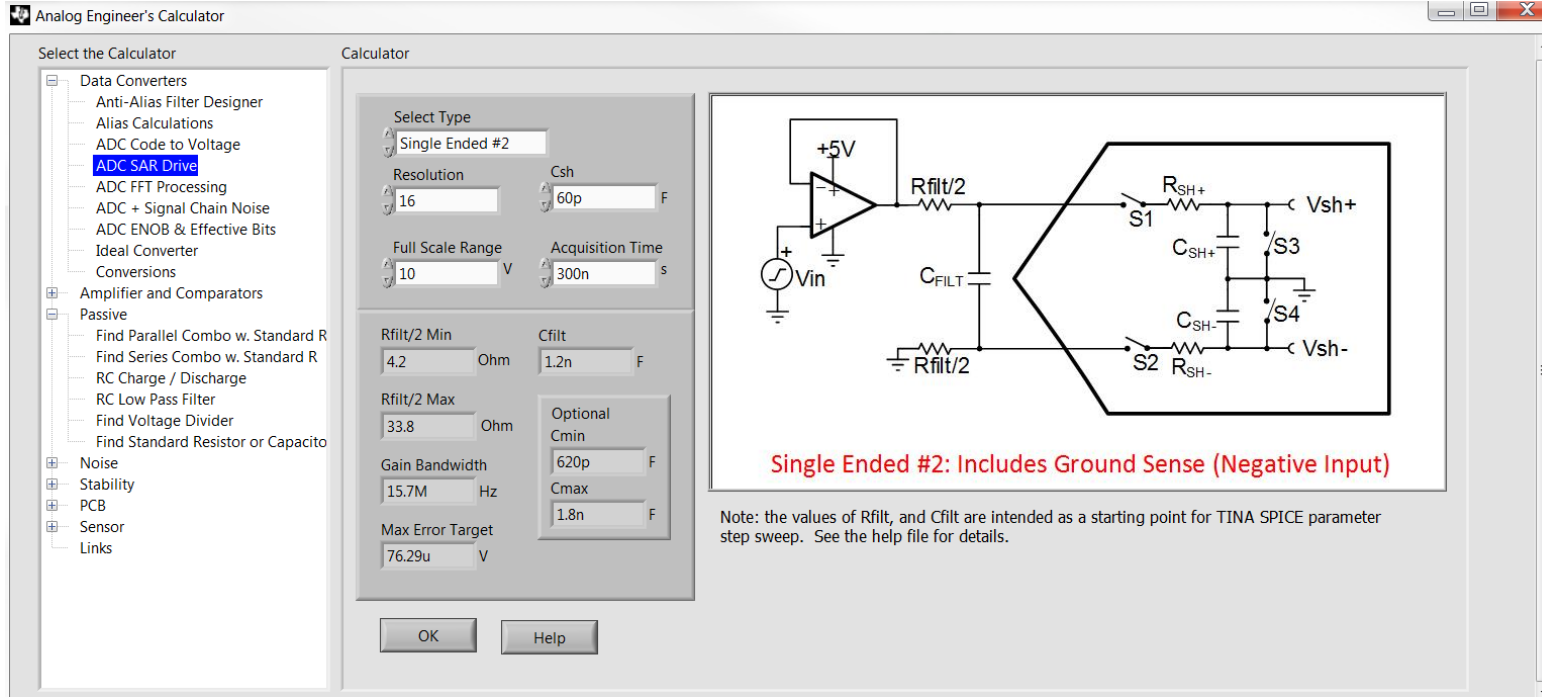

Select the Calculator

- Data Converters
 - Anti-Alias Filter Designer
 - Alias Calculations
 - ADC Code to Voltage
 - ADC SAR Drive**
 - ADC FFT Processing
 - ADC + Signal Chain Noise
 - ADC ENOB & Effective Bits
 - Ideal Converter
 - Conversions
- Amplifier and Comparators
- Passive
 - Find Parallel Combo w. Standard R
 - Find Series Combo w. Standard R
 - RC Charge / Discharge
 - RC Low Pass Filter
 - Find Voltage Divider
 - Find Standard Resistor or Capacitor
- Noise
- Stability
- PCB
- Sensor
- Links

Calculator

Select Type: Single Ended #2

Resolution: 16, Csh: 60p F

Full Scale Range: 10 V, Acquisition Time: 300n s

Rfilt/2 Min: 4.2 Ohm, Cfilt: 1.2n F

Rfilt/2 Max: 33.8 Ohm, Optional Cmin: 620p F, Cmax: 1.8n F

Gain Bandwidth: 15.7M Hz

Max Error Target: 76.29u V

OK Help

Single Ended #2: Includes Ground Sense (Negative Input)


Note: the values of Rfilt, and Cfilt are intended as a starting point for TINA SPICE parameter step sweep. See the help file for details.

[Link for free download of Analog Engineer's Calculator](#)

[Math Behind the R-C Component Selection](#)



[Refine the Rfilt and Cfilt Values](#)

Noise Theory

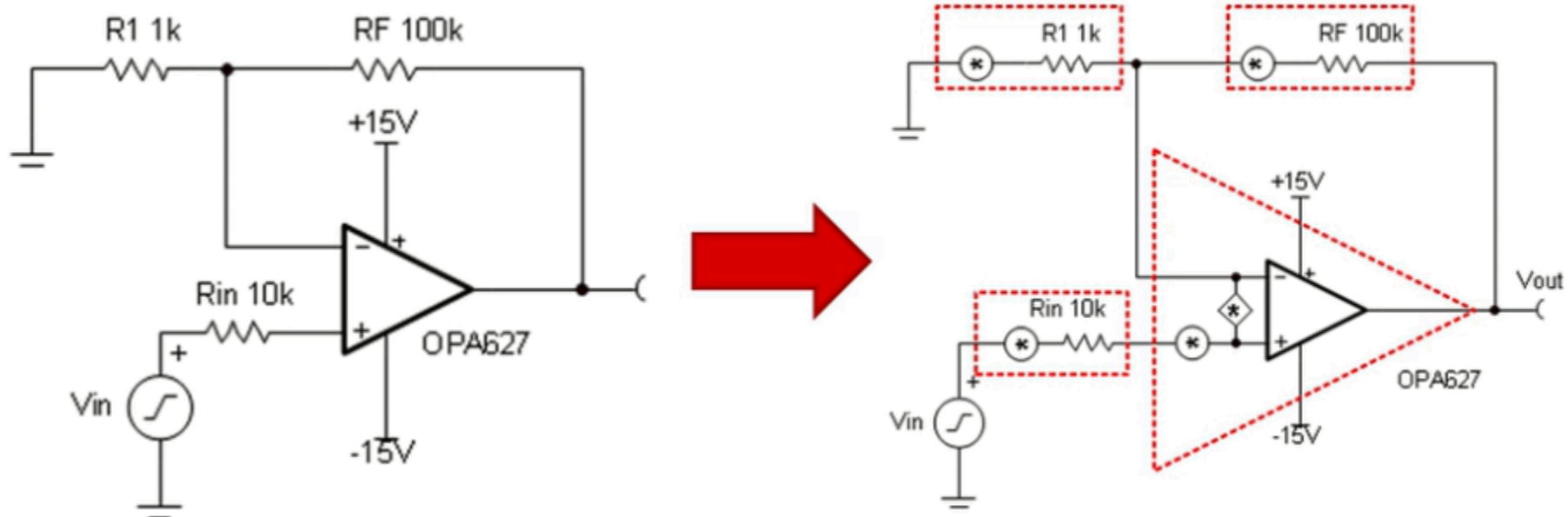

TI Precision Labs – Operational Amplifier Noise

1/f Noise is Negligible

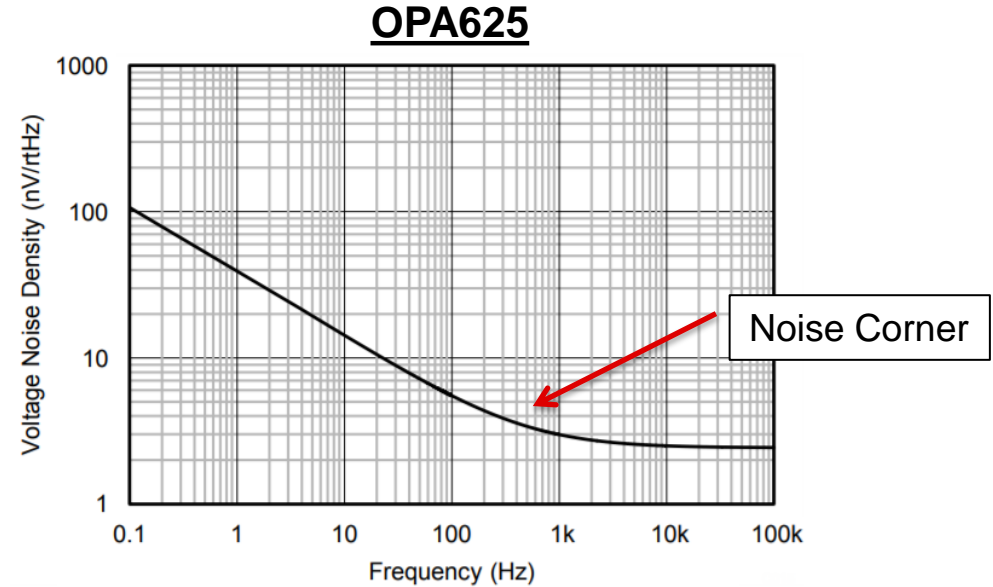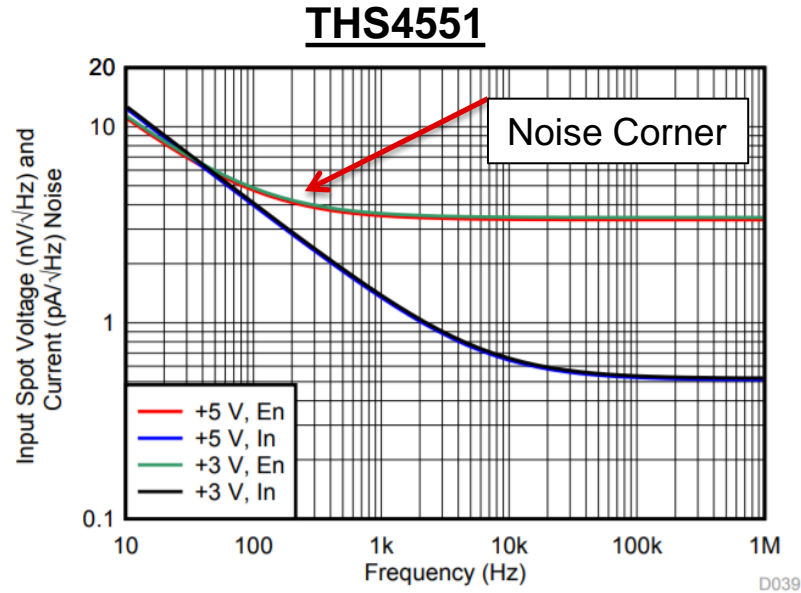


If $BW_N > 10 * f_{FLICKER}$
 If $BW_N < 10 * f_{FLICKER}$

then 1/f noise will be negligible
 then 1/f noise will need to be considered

$$BWN = k * \frac{1}{2\pi R F I L_{TCFILT}} = 1.57 * \frac{1}{2\pi * 16.25\Omega * 690pF} = 22 \text{ MHz}$$

Noise Calculations

Discrete Stage 1

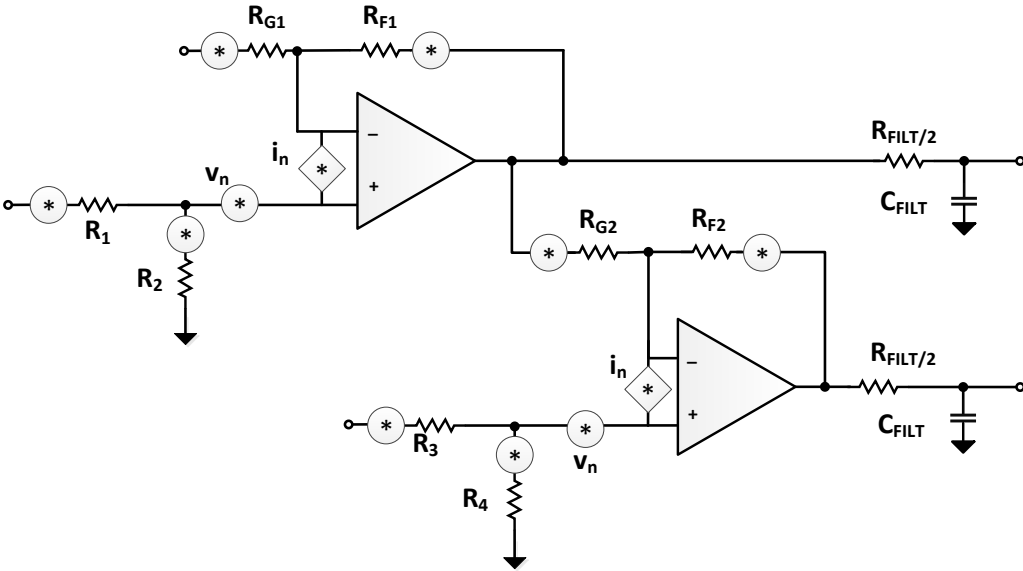

Key Specifications

$$GBW = 120 \text{ MHz}$$

$$R_{F1} = 246 \Omega$$

$$R_{G1} = 150 \Omega$$

$$K = 1.38 \times 10^{-23} \text{ (J/K)}$$

$$k = 1.57$$

$$T = 25^\circ\text{C} = 293 \text{ K}$$

$$v_{n(OPA625)} = 2.5 \text{ nV}/\sqrt{\text{Hz}}$$

$$i_{n(OPA625)} = 2.8 \text{ pA}/\sqrt{\text{Hz}}$$

$$R_{FILT/2} = 16.25 \Omega$$

$$C_{FILT} = 690 \text{ pF}$$

Key Calculations

$$G_N = (1 + R_{F1}/R_{G1}) = 3.3 \text{ V/V}$$

$$Req_{RF} = R_{F1} || R_{G1} = 74.5 \Omega$$

$$Req_{12} = R_1 || R_2 = 162 \Omega$$

$$fc = \frac{1}{2\pi R_{FILT} C_{FILT}} = 14.1 \text{ MHz}$$

Voltage Spectral Noise

$$e_{vn} = vn = 2.5 \text{ nV}/\sqrt{\text{Hz}}$$

Current Spectral Noise

$$e_{in1} = in * Req_{RF} = 0.209 \text{ nV}/\sqrt{\text{Hz}}$$

$$e_{in2} = in * Req_{12} = 0.454 \text{ nV}/\sqrt{\text{Hz}}$$

Resistor Spectral Noise

$$e_{ReqRF} = \sqrt{4KTReq_{RF}} = 1.1 \text{ nV}/\sqrt{\text{Hz}}$$


$$e_{Req12} = \sqrt{4KTReq_{12}} = 1.62 \text{ nV}/\sqrt{\text{Hz}}$$

Stage 1 Spectral Noise

$$e_1 = 2 * GN \sqrt{e_{vn}^2 + e_{in1}^2 + e_{in2}^2 + e_{ReqRF}^2 + e_{Req12}^2} = 21 \text{ nV}/\sqrt{\text{Hz}}$$

Noise Calculations

Discrete Stage 2 and V_{RMS}

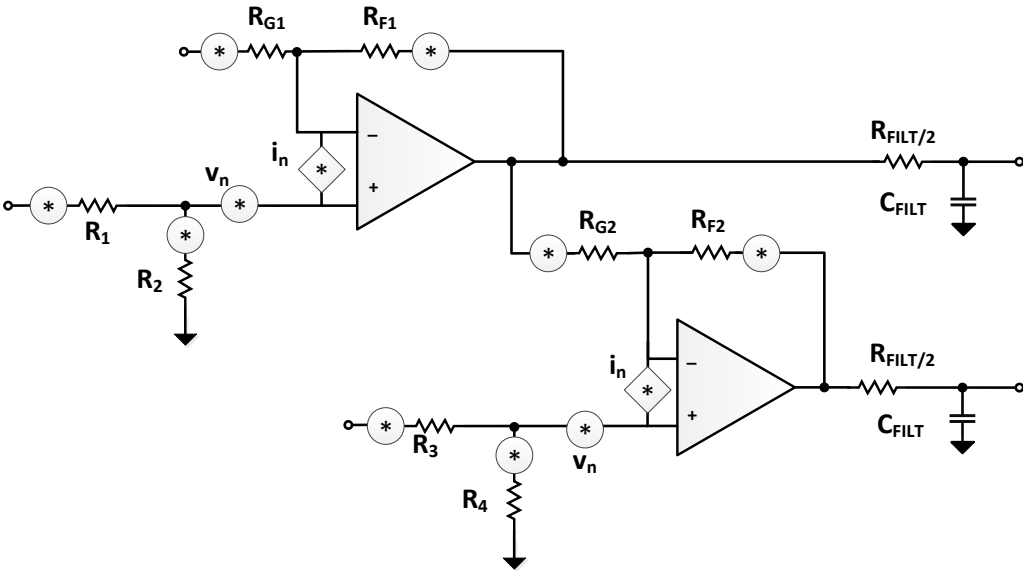

Key Specifications

$$GBW = 120 \text{ MHz}$$

$$R_{F2} = 246 \ \Omega$$

$$R_{G2} = 107 \ \Omega$$

$$K = 1.38 \times 10^{-23} \text{ (J/K)}$$

$$k = 1.57$$

$$T = 25^\circ\text{C} = 293 \text{ K}$$

$$v_{n(OPA625)} = 2.5 \text{ nV}/\sqrt{\text{Hz}}$$

$$i_{n(OPA625)} = 2.8 \text{ pA}/\sqrt{\text{Hz}}$$

$$R_{FILT/2} = 16.25 \ \Omega$$

$$C_{FILT} = 690 \text{ pF}$$

Key Calculations

$$G_N = (1 + R_F/R_G) = 2 \text{ V/V}$$

$$Req_{RF} = R_{F2} || R_{G2} = 235 \ \Omega$$

$$f_c = \frac{1}{2\pi R_{FILT} C_{FILT}} = 14.1 \text{ MHz}$$

Voltage Spectral Noise

$$e_{vn} = v_n = 2.5 \ \mu\text{V}/\sqrt{\text{Hz}}$$

Current Spectral Noise

$$e_{in1} = i_n * Req_{RF} = 0.658 \text{ nV}/\sqrt{\text{Hz}}$$

$$e_{in2} = i_n * Req_{34} = 0.658 \text{ nV}/\sqrt{\text{Hz}}$$

Resistor Spectral Noise

$$e_{ReqRF} = \sqrt{4KTReq_{RF}} = 1.95 \text{ nV}/\sqrt{\text{Hz}}$$

$$e_{Req34} = \sqrt{4KTReq_{34}} = 1.95 \text{ nV}/\sqrt{\text{Hz}}$$

Stage 2 Spectral Noise

$$e_2 = G_N \sqrt{e_{vn}^2 + e_{in1}^2 + e_{in2}^2 + e_{ReqRF}^2 + e_{Req34}^2}$$

$$= 7.67 \text{ nV}/\sqrt{\text{Hz}}$$





Total RMS Noise

$$e_{TOTAL} = \sqrt{e_1^2 + e_2^2} = 22.5 \text{ nV}/\sqrt{\text{Hz}}$$

$$E_{TOTAL} = e_{TOTAL} \sqrt{k * f_c} = 106 \ \mu\text{V}_{RMS}$$

Noise Simulation

Discrete Solution

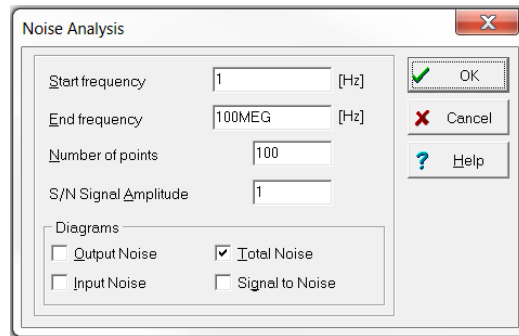
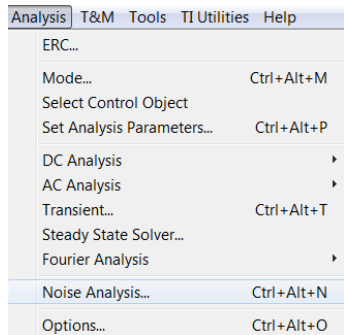
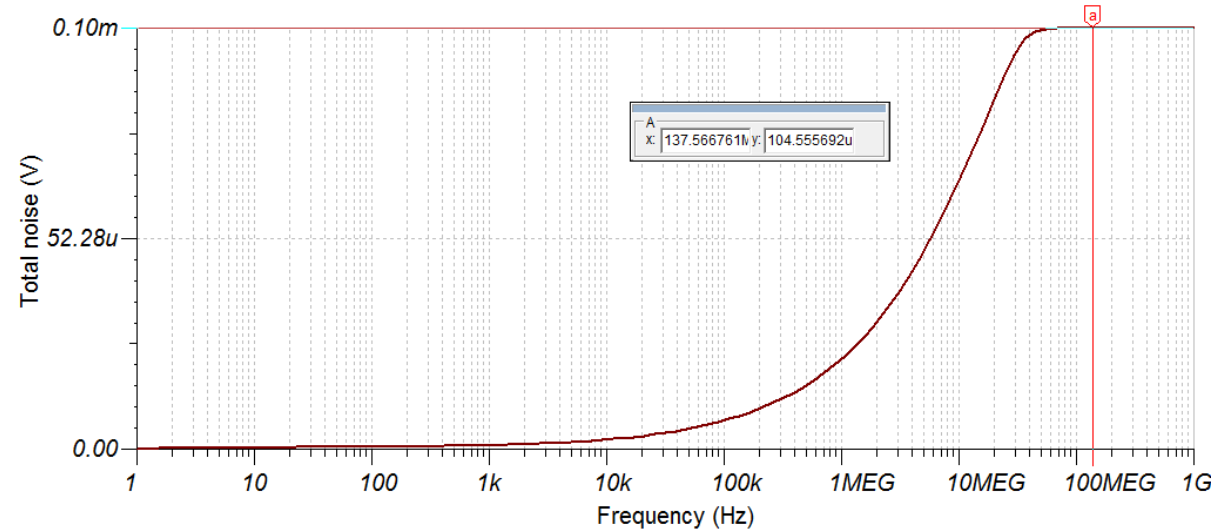
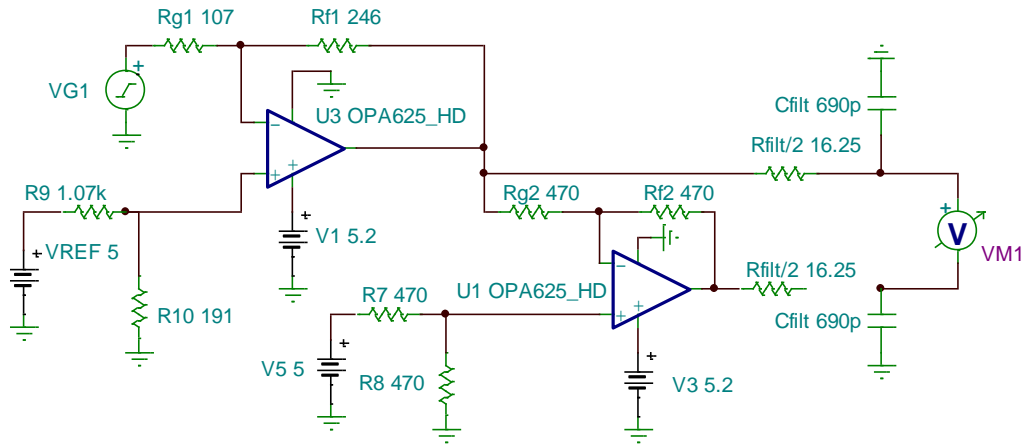


$$E_{TOTAL\ SIM} = 104\ \mu V_{RMS}$$

$$E_{TOTAL\ CALC} = 106\ \mu V_{RMS}$$

Noise Simulation

Discrete Solution with Capacitor

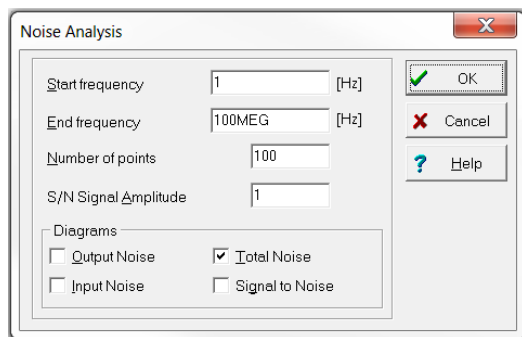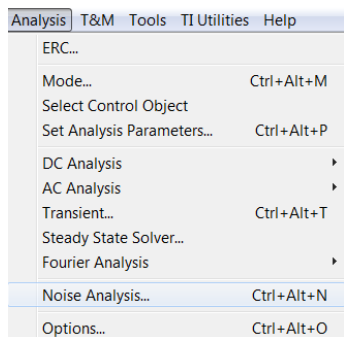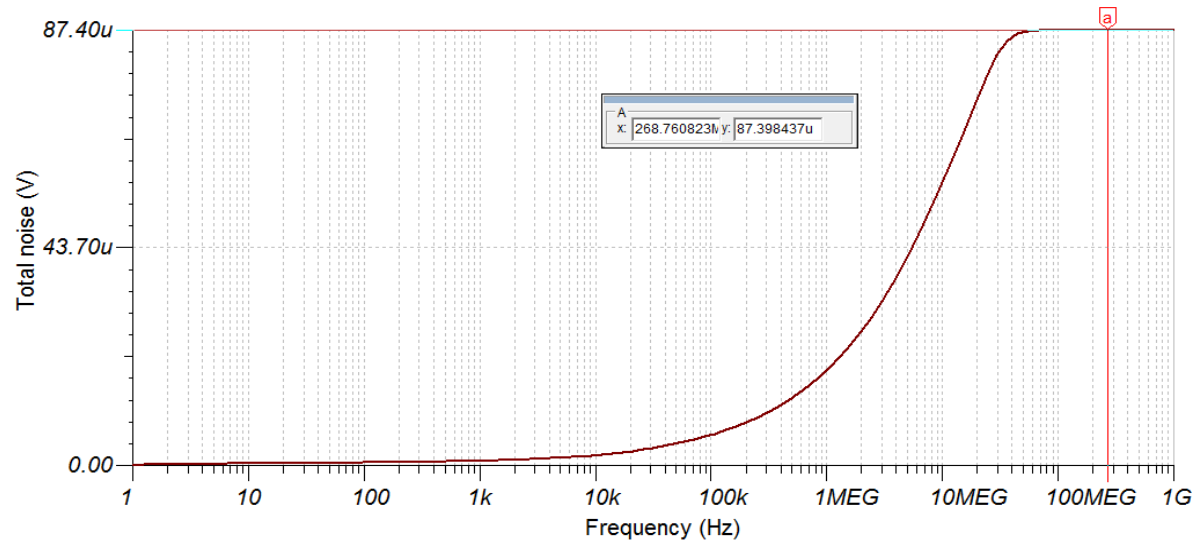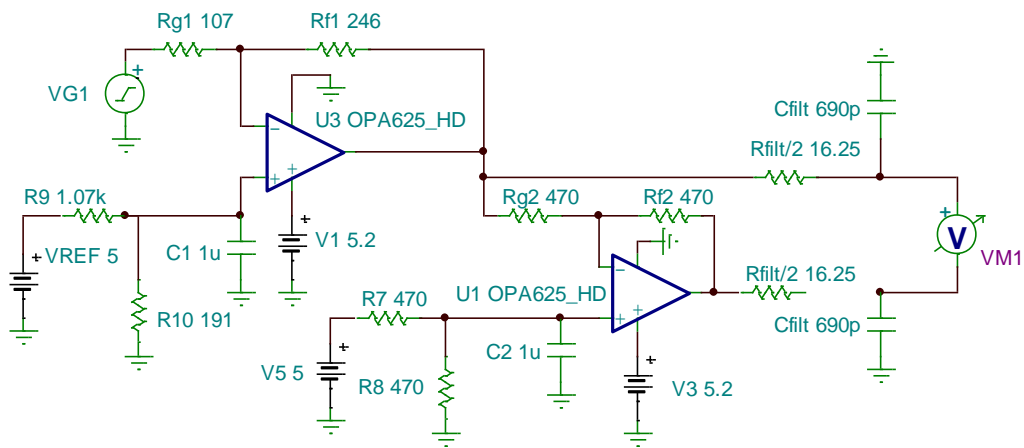


$$E_{TOTAL\ SIM} = 87\ \mu V_{RMS}$$

$$E_{TOTAL\ CALC} = 87.4\ \mu V_{RMS}$$

Noise Calculations

Fully Differential Amplifier

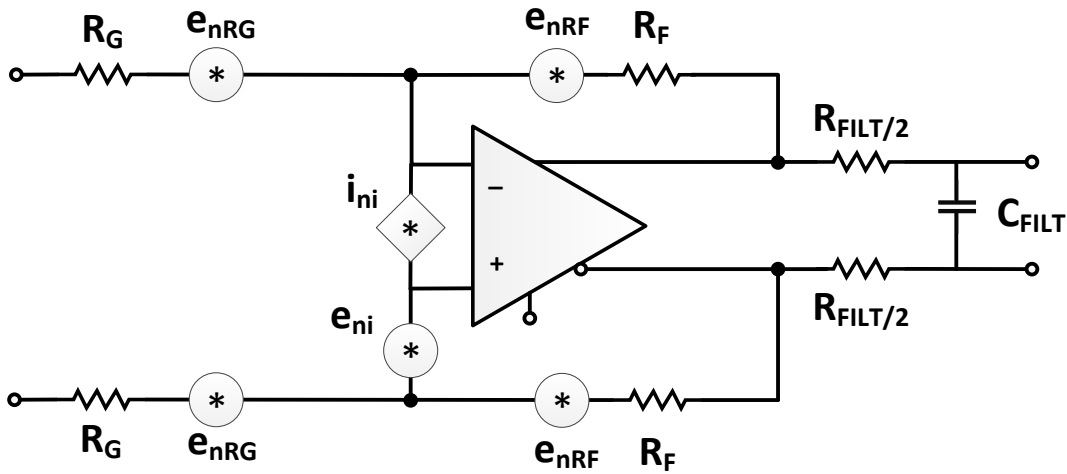

Key Specifications

$$R_F = 493 \Omega$$

$$R_G = 107 \Omega$$

$$K = 1.38 \times 10^{-23} \text{ (J/K)}$$

$$k = 1.365$$

$$T = 25^\circ\text{C} = 293 \text{ K}$$

$$v_{n(THS4551)} = 3.3 \text{ nV}/\sqrt{\text{Hz}}$$

$$i_{n(THS4551)} = 0.5 \text{ pA}/\sqrt{\text{Hz}}$$

$$R_{FILT}/2 = 16.25 \Omega$$

$$C_{FILT} = 690 \text{ pF}$$

Key Calculations

$$G_N = (1 + R_F/R_G) = 5.6 \text{ V/V}$$

$$Req_{RF} = R_F || R_G = 87.9 \Omega$$

$$f_c = \frac{1}{2\pi R_{FILT} C_{FILT}} = 14 \text{ MHz}$$

$$BW_N = \sqrt{k * f_c} = 4.4 \text{ kHz}$$

Voltage Spectral Noise

$$e_{vn} = vn = 3.3 \text{ nV}/\sqrt{\text{Hz}}$$

Current Spectral Noise

$$e_{in1} = in * Req_{RF} = 0.04 \text{ nV}/\sqrt{\text{Hz}}$$

$$e_{in2} = in * Req_{12} = 0.04 \text{ nV}/\sqrt{\text{Hz}}$$

Resistor Spectral Noise

$$e_{Req_{RF}} = \sqrt{4KT R_{eq_{RF}}} = 1.19 \text{ nV}/\sqrt{\text{Hz}}$$

$$e_{Req_{RF}} = \sqrt{4KT R_{eq_{RF}}} = 1.19 \text{ nV}/\sqrt{\text{Hz}}$$

Total Stage 1 Spectral Noise

$$e_{TOTAL} = G_N \sqrt{e_{vn}^2 + e_{in1}^2 + e_{in2}^2 + 2e_{Req_{RF}}^2}$$





$$= 20.7 \text{ nV}/\sqrt{\text{Hz}}$$

Total FDA Solution RMS Noise

$$E_{TOTAL} = e_{TOTAL} \sqrt{f_c * k} = 92 \text{ uVrms}$$

Noise Simulation

Fully Differential Amplifier Solution

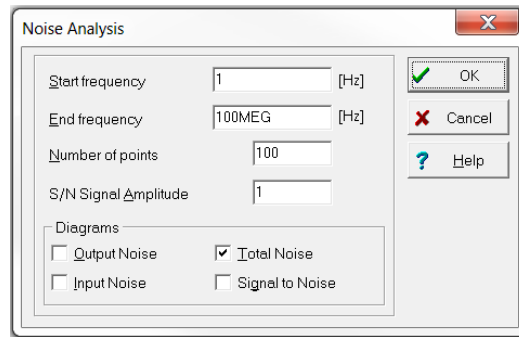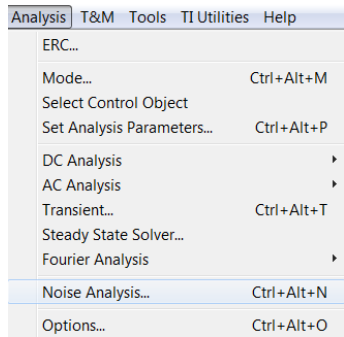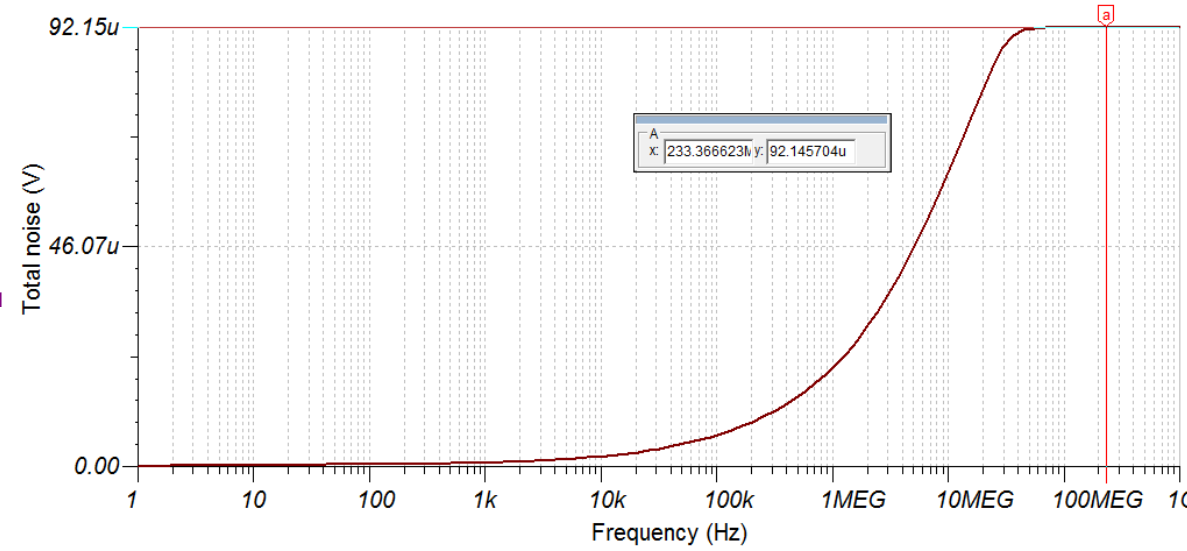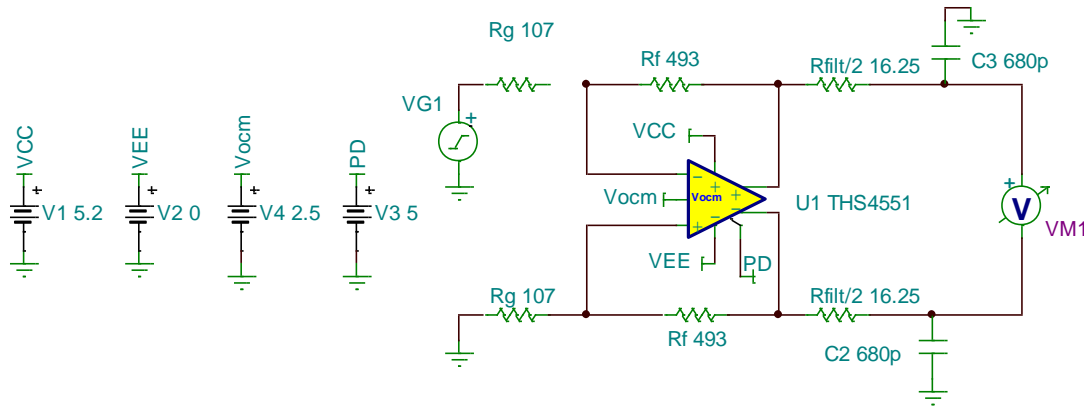

$$E_{TOTAL\ SIM} = 92\ \mu V_{RMS}$$

$$E_{TOTAL\ CALC} = 92\ \mu V_{RMS}$$

Noise Results



Solution	Discrete	Discrete with Cap	Fully Differential
Calculation	106 μV_{RMS}	89 μV_{RMS}	92 μV_{RMS}
Simulation	104 μV_{RMS}	87 μV_{RMS}	91 μV_{RMS}

Stability Theory

Stability rule of thumb

If phase margin $> 45^\circ$ then amplifier is considered **optimally stable**

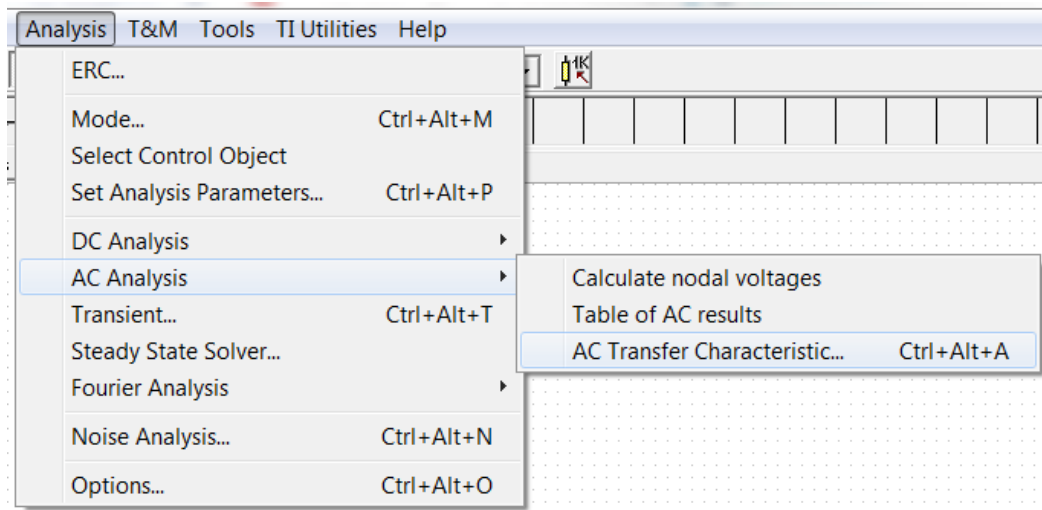
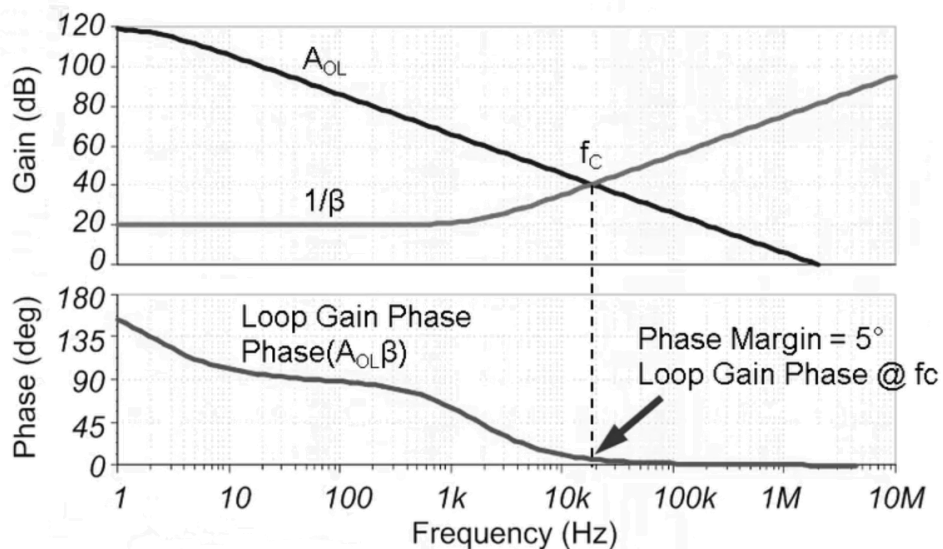
If phase margin $< 45^\circ$ then the amplifier is considered **marginally stable**



TI Precision Labs – Op Amp: Stability

Stability Simulation



Discrete Amplifier 1

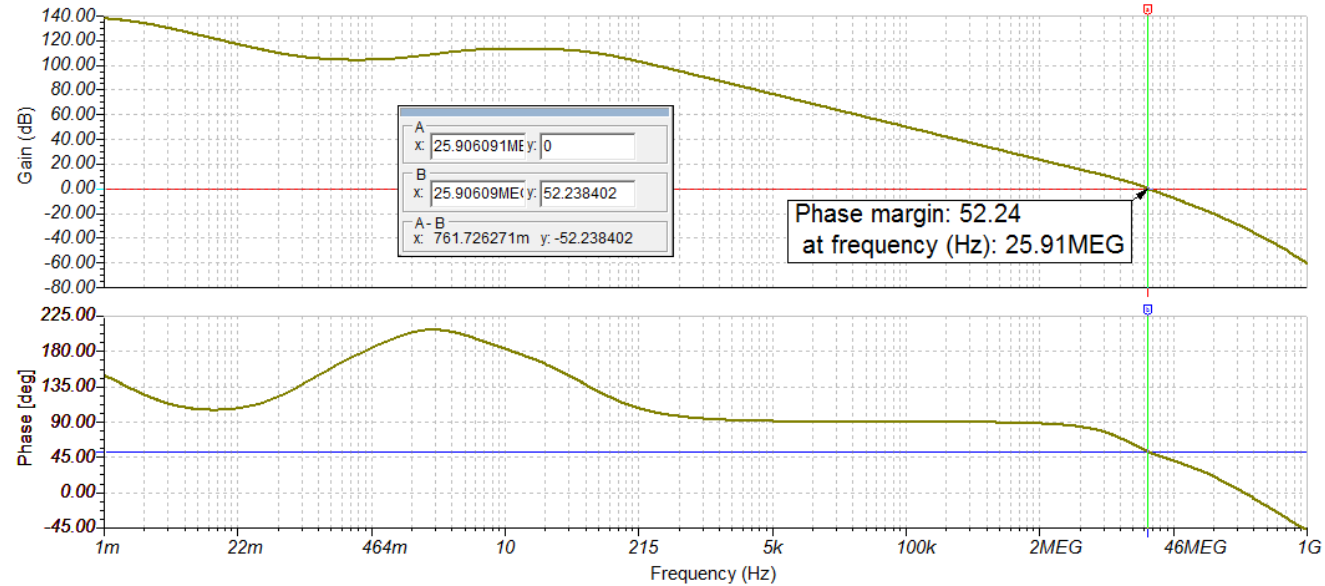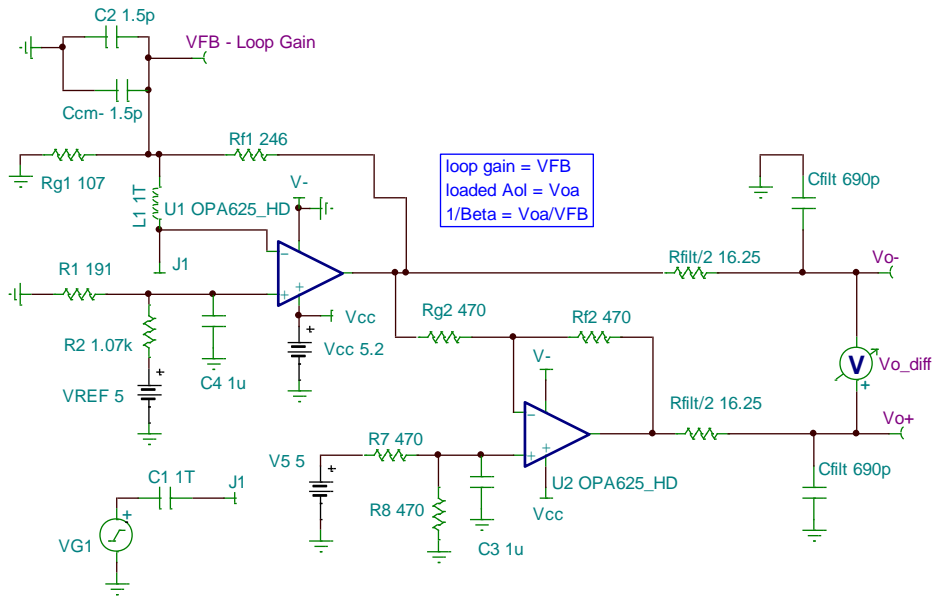

Marginally Stable!

Stability Simulation



Discrete Amplifier 2

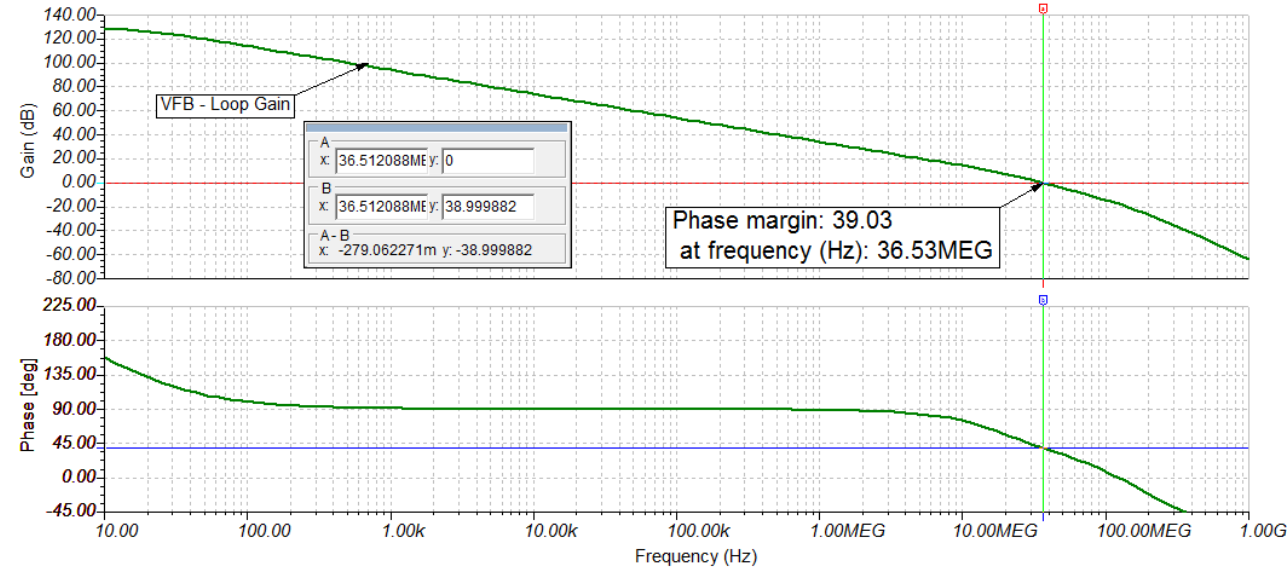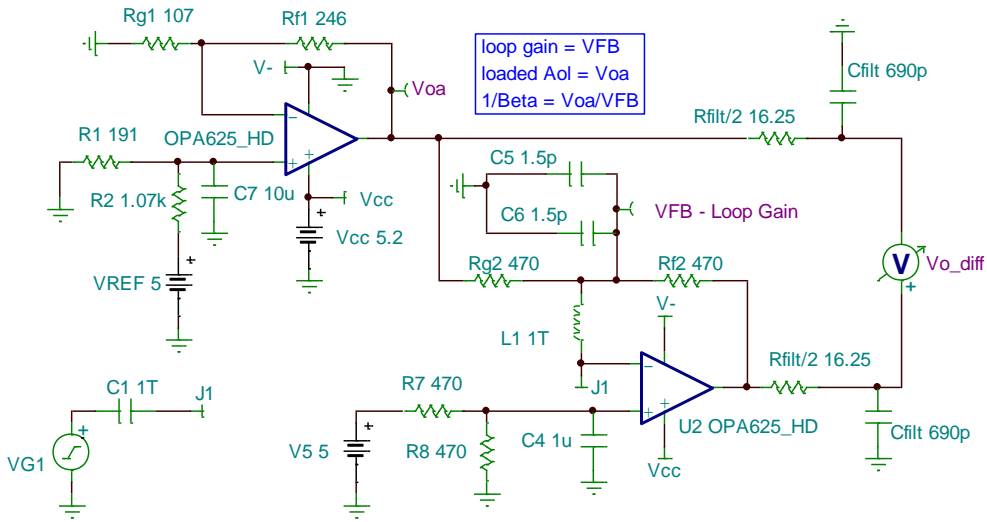

Marginally Stable/Potentially Unstable

Stability Simulation

Fully Differential Amplifier

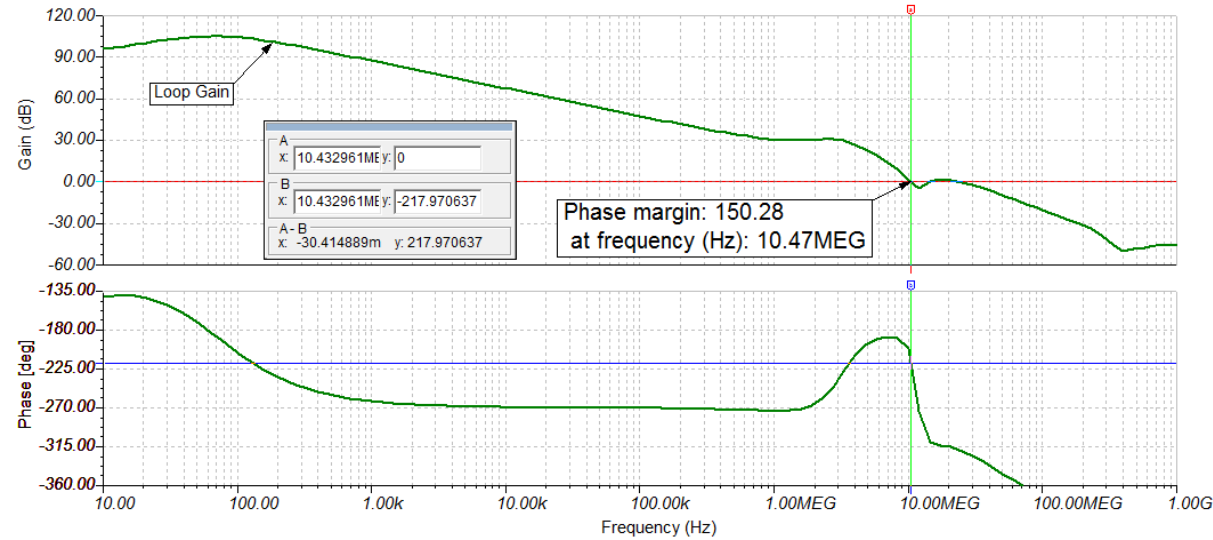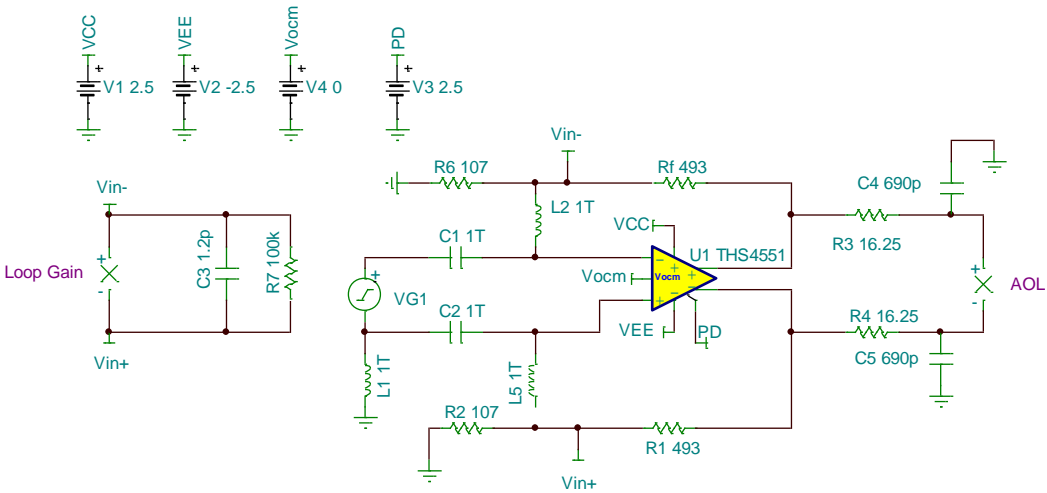

STABLE!

Total Harmonic Distortion Theory

FDEs Even Order Harmonic Distortion

$$V_{out+} = k_1V_{in} + k_2V_{in}^2 + k_3V_{in}^3 + k_4V_{in}^4 \dots \quad (1)$$

$$V_{out-} = k_1(-V_{in}) + k_2(-V_{in})^2 + k_3(-V_{in})^3 + k_4(-V_{in})^4 \dots \quad (2)$$

Where $k_1, k_2 \dots k_N$ are constants

Taking the differential output:

$$\begin{aligned} V_o &= V_{OUT+} - V_{OUT-} \\ &= k_1V_{in} - (-k_1V_{in}) + k_2V_{in}^2 - k_2(-V_{in})^2 + k_3V_{in}^3 - (-k_3V_{in}^3) \dots \\ &= 2k_1V_{in} + 2k_3V_{in}^3 + 2k_5V_{in}^5 \dots \quad (3) \end{aligned} \quad \rightarrow \quad \text{No added even-order harmonics}$$

Calculations Total Harmonic Distortion

6.5 Electrical Characteristics: $(V_{S+}) - (V_{S-}) = 5\text{ V}$ THS4551

at $T_A \approx 25^\circ\text{C}$, VO_{CM} pin = open, $R_F = 1\text{ k}\Omega$, $R_L = 1\text{ k}\Omega$, $V_{OUT} = 2 V_{PP}$, 50- Ω input match, $G = 1\text{ V/V}$, $\overline{PD} = V_{S+}$, single-ended input, differential output, and input and output referenced to default midsupply for ac-coupled tests (unless otherwise noted); see [Figure 61](#) for a gain of 1-V/V test circuit


HD2	Second-order harmonic distortion	$f = 100\text{ kHz}$, $V_{OUT} = 2 V_{PP}$, $G = 1$, $R_L = 1\text{ k}\Omega$	-128	dBc	C
		$f = 100\text{ kHz}$, $V_{OUT} = 8 V_{PP}$, $G = 1$, $R_L = 1\text{ k}\Omega$	-124		C
HD3	Third-order harmonic distortion	$f = 100\text{ kHz}$, $V_{OUT} = 2 V_{PP}$, $G = 1$, $R_L = 1\text{ k}\Omega$	-139	dBc	C
		$f = 100\text{ kHz}$, $V_{OUT} = 8 V_{PP}$, $G = 1$, $R_L = 1\text{ k}\Omega$	-131		C

6.5 Electrical Characteristics High-Drive Mode OPA625

at $T_A = 25^\circ\text{C}$, $V_+ = 5\text{ V}$, $V_- = 0\text{ V}$, MODE pin connected to V_- pin, $V_{COM} = V_O = 2.5\text{ V}$, gain (G) = 1, $R_F = 1\text{ k}\Omega$, $C_F = 2.7\text{ pF}$, $C_{LOAD} = 20\text{ pF}$, and $R_{LOAD} = 2\text{ k}\Omega$ connected to 2.5 V (unless otherwise noted)

HD2	Second-order harmonic Distortion	$V_O = 2 V_{PP}$, $G = 2$	$f = 10\text{ kHz}$	144	dBc
			$f = 100\text{ kHz}$	122	
			$f = 1\text{ MHz}$	80	
HD3	Third-order harmonic Distortion	$V_O = 2 V_{PP}$, $G = 2$	$f = 10\text{ kHz}$	155	dBc
			$f = 100\text{ kHz}$	140	
			$f = 1\text{ MHz}$	80	

Settling Time Theory

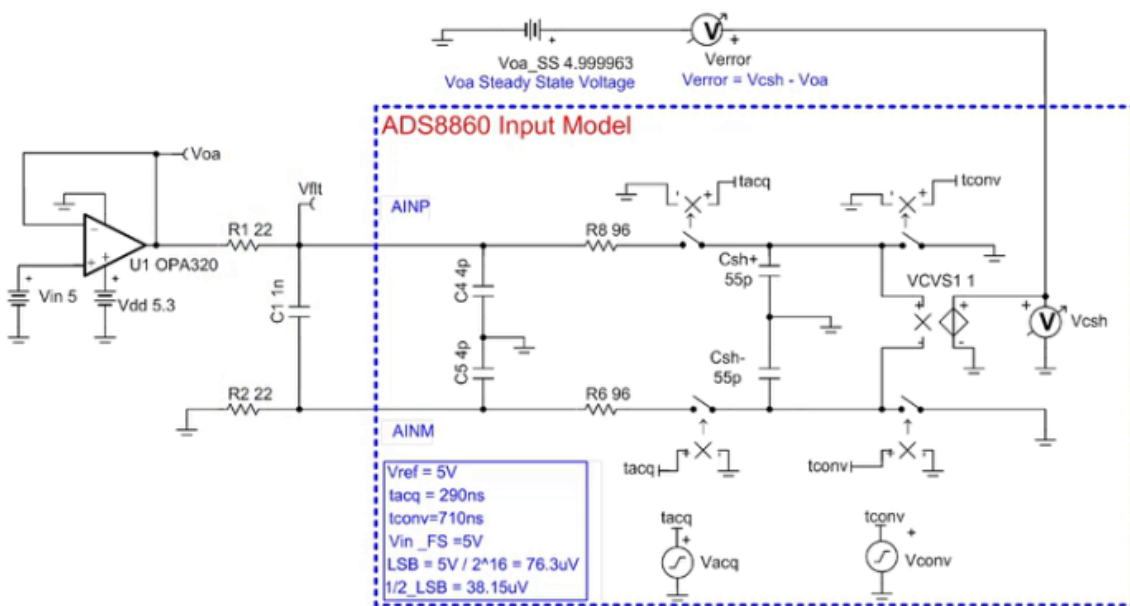

Analysis	T&M	Tools	TI Utilities	Help
ERC...				
Mode...				Ctrl+Alt+M
Select Control Object				
Set Analysis Parameters...				Ctrl+Alt+P
DC Analysis				
AC Analysis				
Transient...				Ctrl+Alt+T
Steady State Solver...				
Fourier Analysis				
Noise Analysis...				Ctrl+Alt+N
Options...				Ctrl+Alt+O

Transient Analysis

Start display: 0 [s] OK

End display: 1u [s] Cancel

Calculate operating point
 Use initial conditions
 Zero initial values



Draw excitation

? Help

TI Precision Labs - ADCs: Building the SAR ADC Model

Settling Time Simulation



Discrete Amplifiers – 1/2 LSB

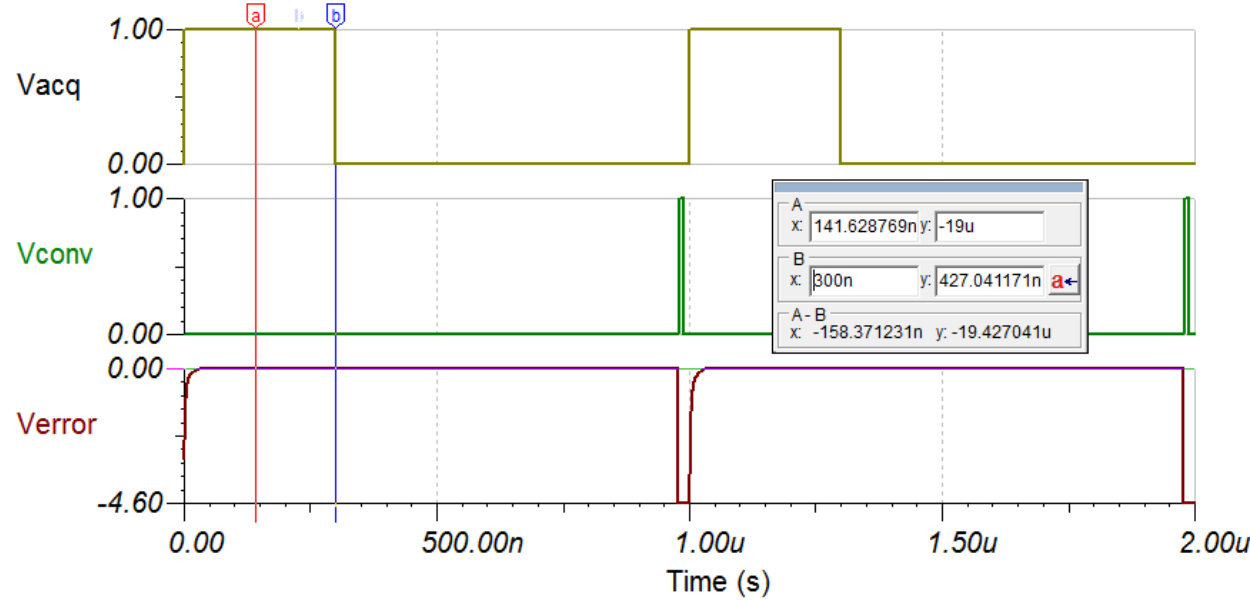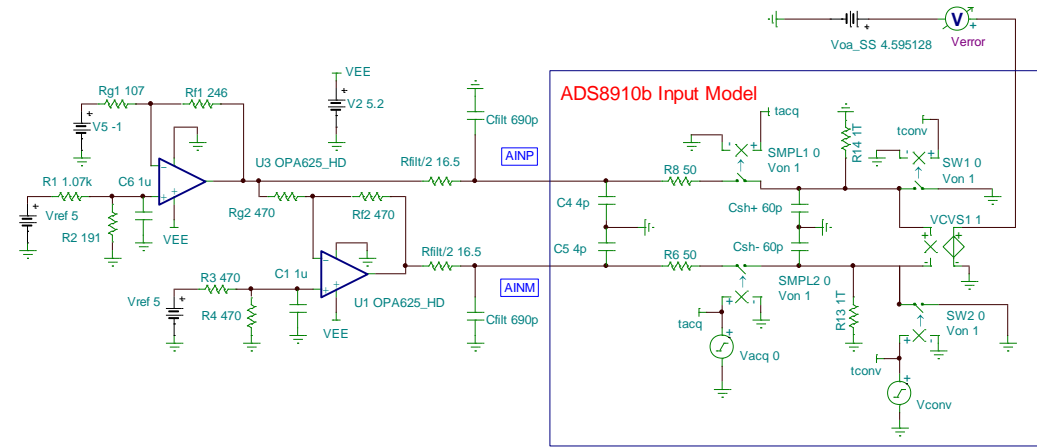

Settling time = 141 ns
Final Error Voltage = 427 nV



Settling Time Simulation

Fully Differential Amplifier – 1/2 LSB

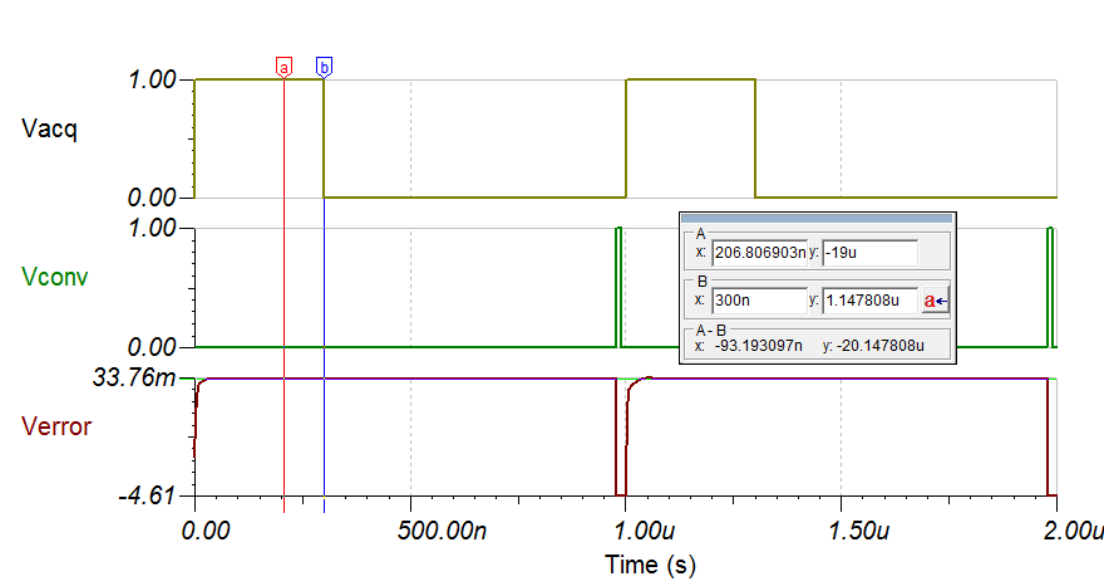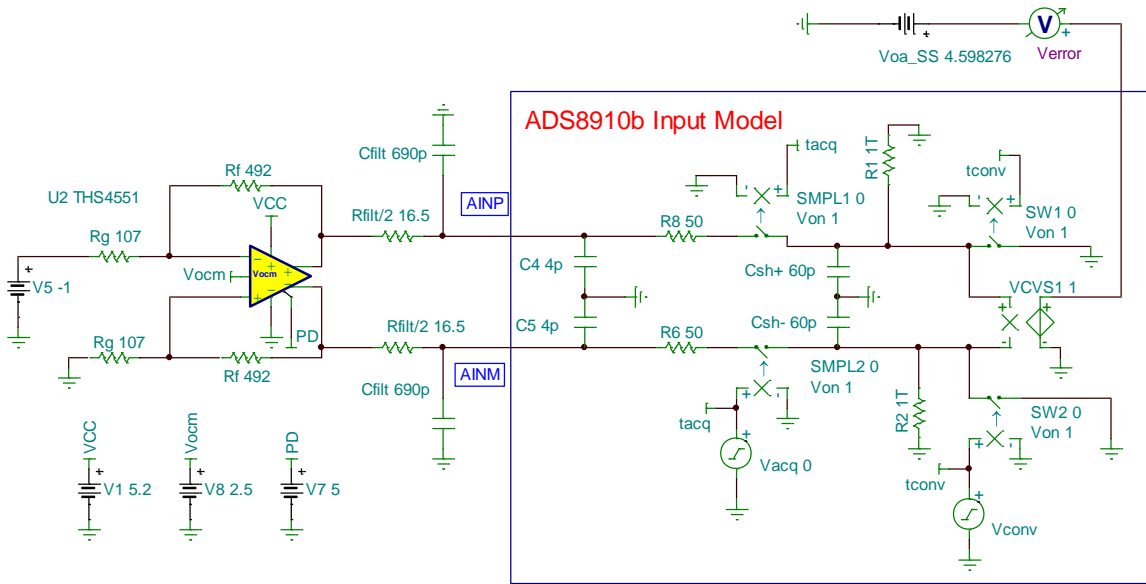

Settling time = 206 ns
Final Error Voltage = 1.147 μV

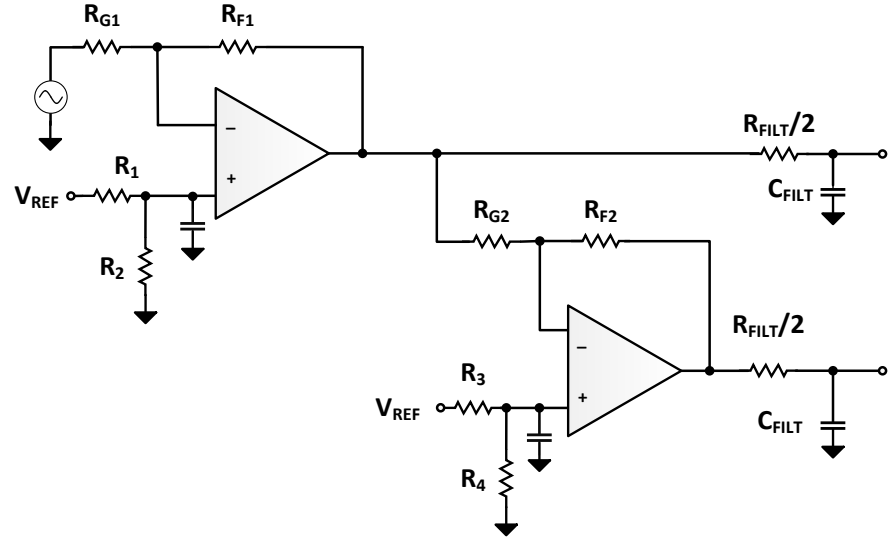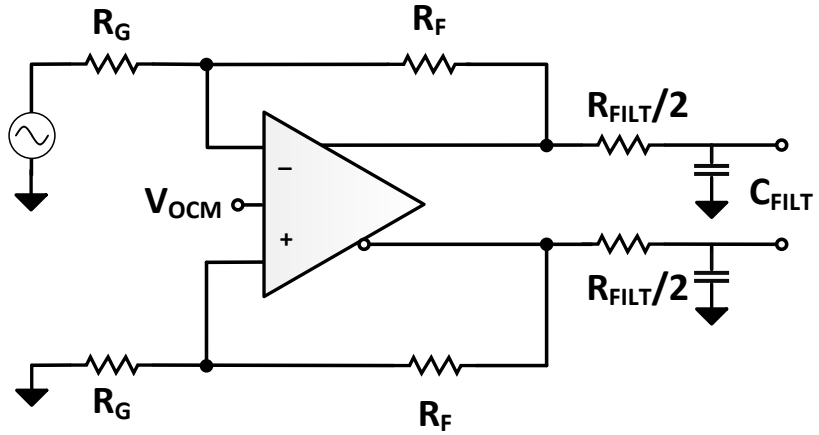Fully Differential Amplifier vs Discrete Solutions



Specifications	FDA	Discrete (w/Capacitor)
Noise	91 μV_{RMS}	87 μV_{RMS}
Stability	Stable	Marginally Stable
THD (HD2, HD3)	(-128 dBc, -139 dBc)	(-122 dBc, -140 dBc)
Settling Time	208 ns	141 ns
Quiescent Current	1.35 mA	4 mA
Components	9	16

THANKS FOR YOUR TIME!