

# High **VOLT** Interactive

Where power supply design meets collaboration

Isolated Bias Power Supply Architecture and Topology Trade-offs  
for HEV/EVs

**By Jacob Vasquez**

Acknowledgement: Peter Meaney, Billy Long, Xun Gong, Benjamin Lough

What will I get out of this session?

## **Purpose:**

- Review the isolated bias power supply architectures and topologies and discuss their trade-offs**

1. Isolated Bias Power Overview
2. Power Architecture
3. Topology Review
4. TI Solution Comparison


## • Part numbers mentioned:

- UCC21530-Q1
- UCC2808A-1Q1
- TPS40210-Q1
- LM5180-Q1
- SN6505B-Q1
- LM5160-Q1

## • Relevant applications:

- On-board charger
- DC/DC converter
- Traction inverter
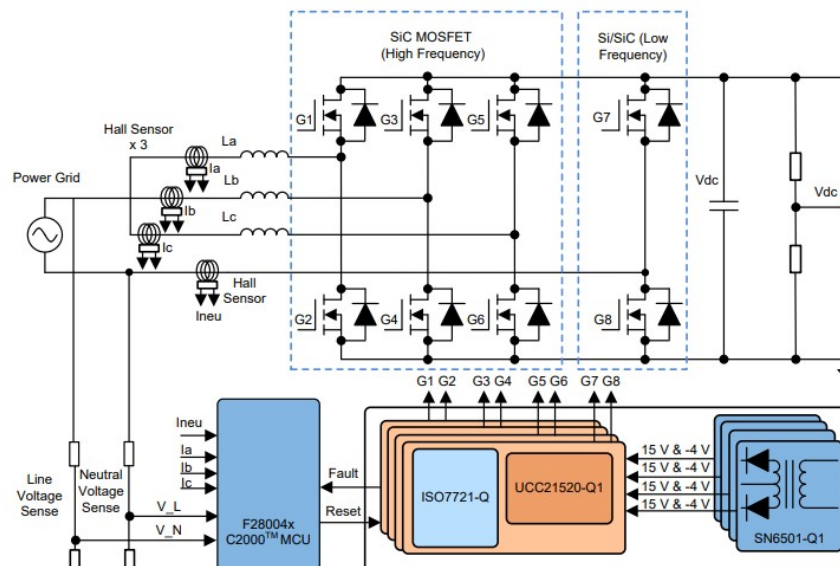
### Isolated Bias Supply and Isolated Gate Driver Applications




**TIDA-01604 98.6% Efficiency, 6.6-kW Totem-Pole PFC for OBC**

Isolated gate drivers and their bias supplies are required to drive high-side and low-side SiC FETs or IGBTs in the:

- On-board charger
  - **PFC stage**
  - Isolated DC/DC stage
- DC/DC Converter
- Traction inverter

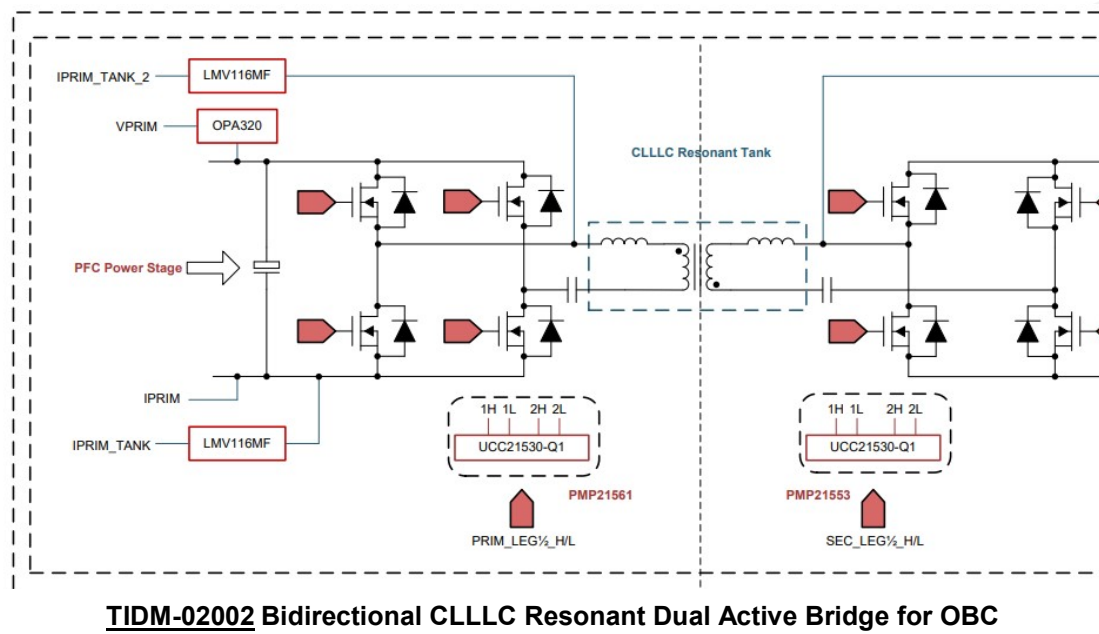
### Isolated Bias Supply and Isolated Gate Driver Applications



Isolated gate drivers and their bias supplies are required to drive high-side and low-side SiC FETs or IGBTs in the:

- On-board charger
  - PFC stage
  - **Isolated DC/DC stage**
- DC/DC Converter
- Traction inverter
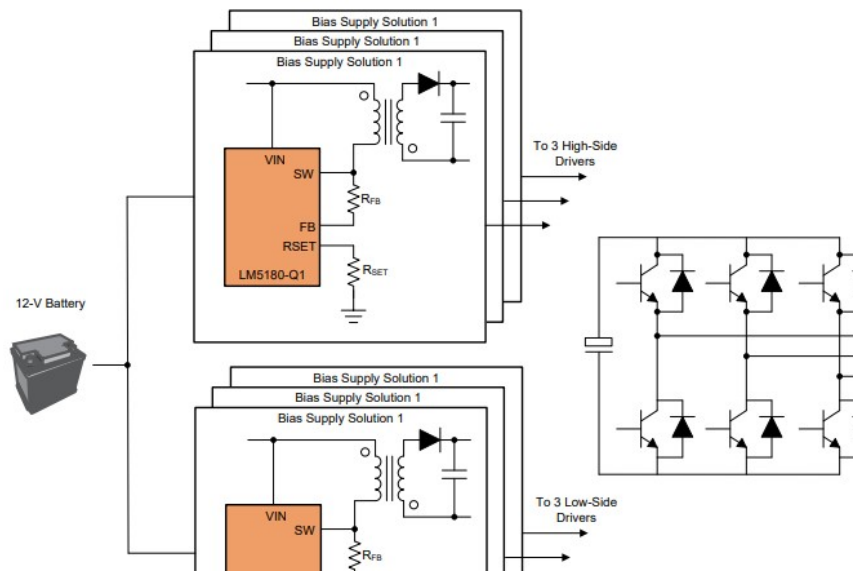
### Isolated Bias Supply and Isolated Gate Driver Applications




**TIDA-020014 Traction Inverter Power Stage with 3 options for IGBT/SiC Bias Supply Solution**

Isolated gate drivers and their bias supplies are required to drive high-side and low-side SiC FETs or IGBTs in the:

- On-board charger
  - PFC stage
  - Isolated DC/DC stage
- DC/DC Converter
- **Traction inverter**

### Isolated Gate Driver and Power Device Overview

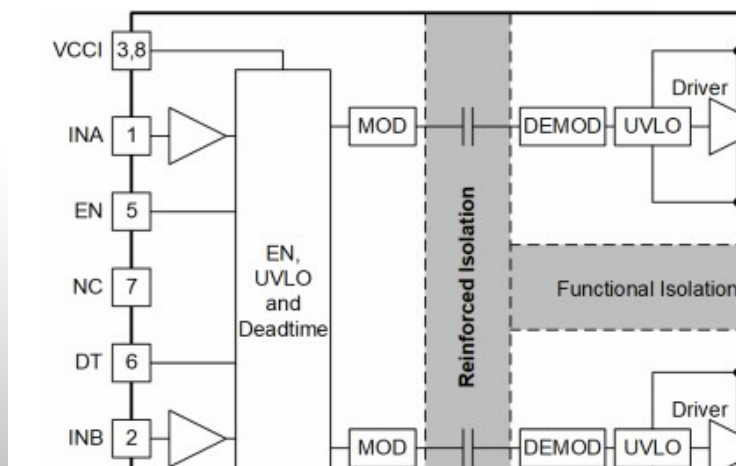**UCC21530-Q1 4-A, 6-A, 5.7-kV<sub>RMS</sub> Isolated Dual-Channel**



$$V_{GS}/V_{GE} = VDDA-VSSA, VDDB-VSSB$$

Si MOSFETs

Si IGBTs


SiC MOSFETs

	Si MOSFETs	Si IGBTs	SiC MOSFETs
Circuit symbol			
Voltage rating	20 V-650 V	≥650 V	≥650 V
$f_{sw}$	Medium-high (>20 kHz)	Low-medium (5 kHz-20 kHz)	High (>50 kHz)
VDD	15 V	15 V	20 V
VSS	0 V	-10 V	-5 V
Optimal $V_{GS}/V_{GE}$	15V	25V	25 V
Typical applications	On-board charger, DC/DC Converter	HEV/EV traction inverters	On-board charger, DC/DC Converter, HEV/EV traction inverter
Power level	<3 kW	>3 kW	>5 kW


Power device ratings and applications
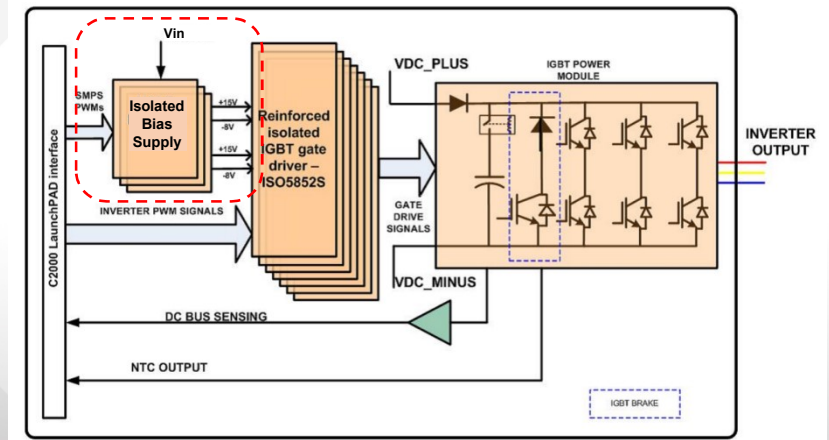
### Isolated Bias Supply Requirements

- Tight output voltage regulation ( $\pm 5\%$  for IGBT)
- Relatively high efficiency (Greater than 80%)
- Robust EMI/EMC performance
- Small solution size
- Protection features (OVP, OCP, short circuit protection, OTP)




### Centralized Power Architecture

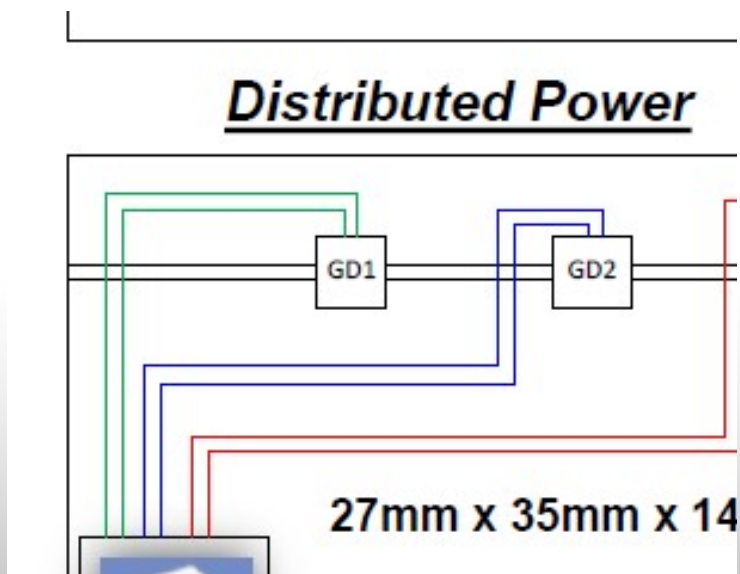

- **One transformer is used to generate the bias voltages for all IGBT or SiC gate drivers**
- Advantages
  - ✓ Low component count
  - ✓ Low cost
  - ✓ Generic controllers and external FETs allows second sourcing
- Disadvantages
  - Bulky transformer, harder to pass shock test.
  - Common mode current can disturb functionality of low voltage circuits
  - Complex PCB routing
  - Lack of Redundancy




### Semi-distributed Power Architecture

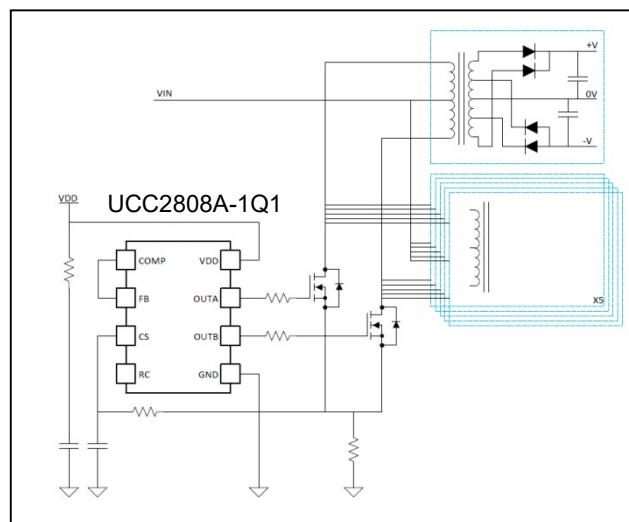

**Semi-Distributed Power**


- **Multiple transformers are used to generate the bias voltages for IGBT or SiC gate drivers, but there is not an individual power stage for each gate driver**
- Advantages
  - ✓ Simpler transformer construction and PCB Layout
  - ✓ Better bias power quality
  - ✓ Distribution of weight for ease of passing shock
  - ✓ Generic controllers and external FETs allows second sourcing
- Disadvantages
  - Higher component count than centralized
  - Relatively high cost
  - Lack of Redundancy

### Distributed Power Architecture

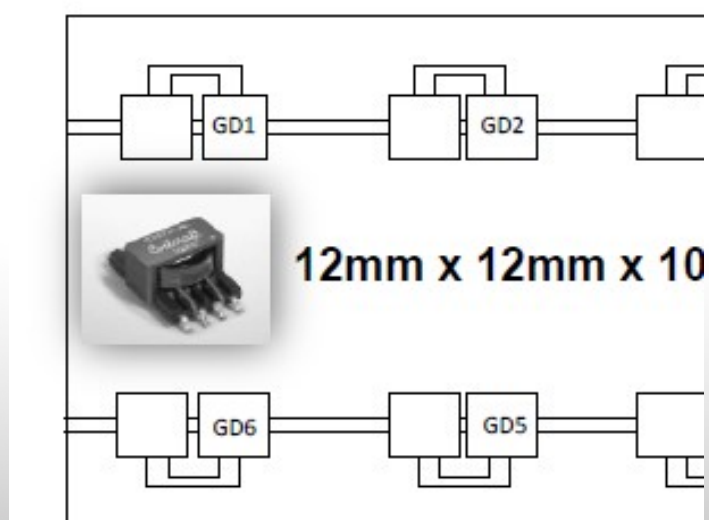

- **Individual gate driver bias supply for each IGBT or SiC gate driver**
- Advantages
  - ✓ **Robustness against power supply failure**
  - ✓ Simpler transformer construction and PCB Layout
  - ✓ Better bias power quality
  - ✓ Distribution of weight for ease of passing shock
- Disadvantages
  - Higher component count
  - High cost






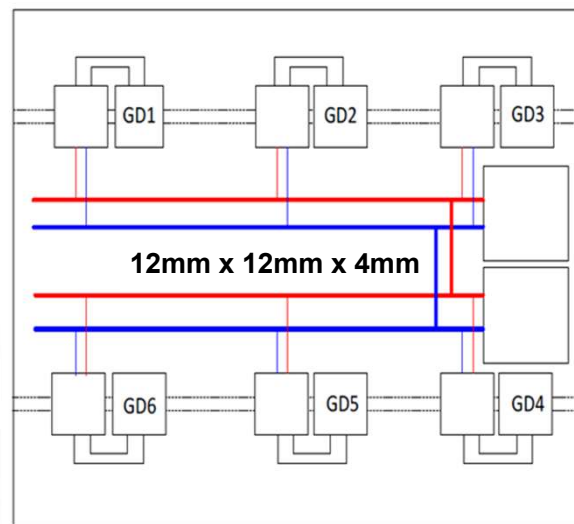
### Two-Stage Distributed Power Architecture




Two-stage Power Architecture

- **Individual gate driver bias supply for each IGBT or SiC gate driver with 2 pre-regulated rails for redundancy**
- Advantages
  - ✓ **Increased robustness against power supply failure**
  - ✓ Simpler transformer construction and PCB layout
  - ✓ Better bias power quality
  - ✓ Distribution of weight for ease of passing shock
- Disadvantages
  - Highest component count
  - High cost

### Topology Overview

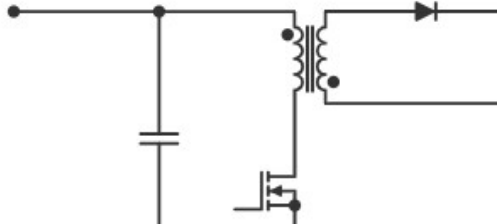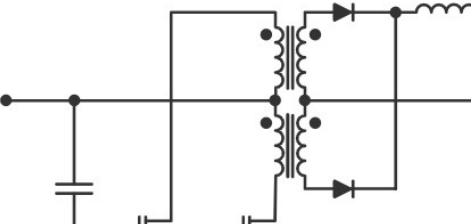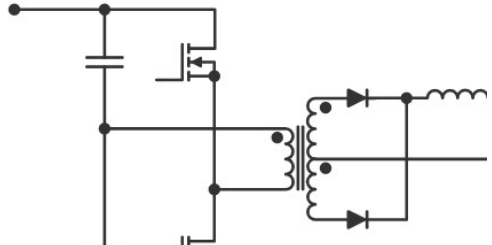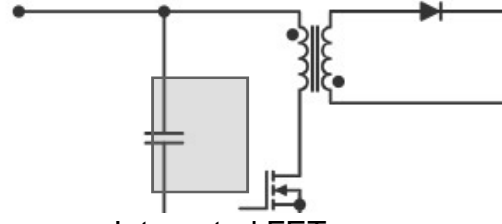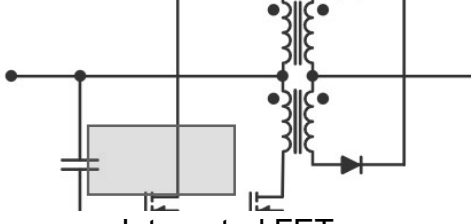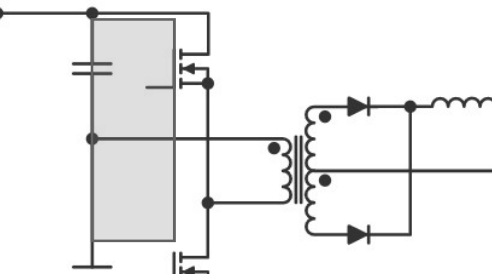
		Flyback	Push-pull	Half-Bridge
Semi-Distributed	Centralized	 <p>External FET</p>	 <p>External FETs</p>	 <p>External FETs</p>
	Distributed	 <p>Integrated FETs</p>	 <p>Integrated FETs</p>	 <p>Integrated FETs</p>

### Flyback Topology

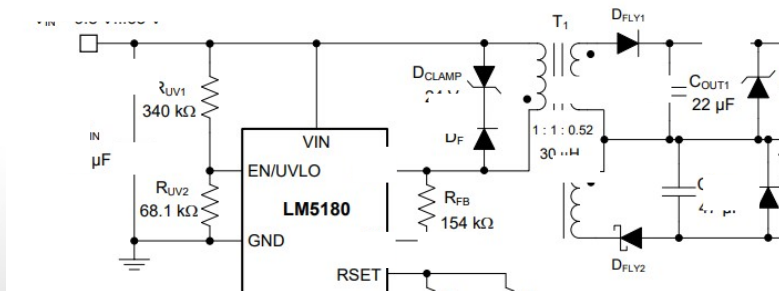


- Advantages
  - ✓ Operation directly off 12V battery for single stage solution
  - ✓ Regulated output (PSR)
  - ✓ Low component count
- Disadvantages
  - Switching frequency limitation
  - Prone to EMI issues due to switch node ringing and primary-secondary capacitance
  - Requires a snubber to avoid overstress on power MOSFET

### Fly-Buck Topology

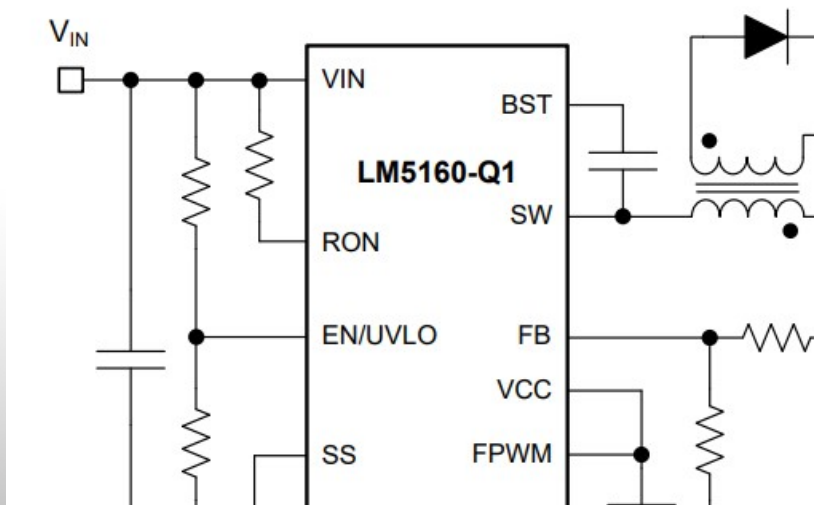


- Advantages
  - ✓ Operation directly off 12V battery for single stage solution
  - ✓ Regulated output without optocoupler
  - ✓ Low component count
- Disadvantages
  - High leakage inductance can degrade load regulation
  - Duty cycle limitation
  - Magnetic design complexity

### Push-pull Topology

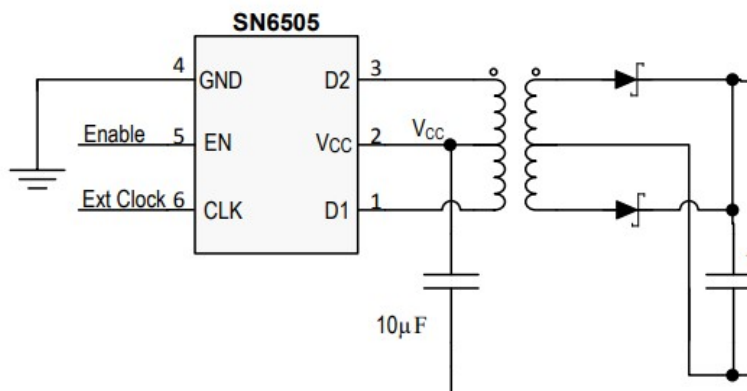

- Advantages
  - ✓ Design simplicity due to open loop configuration
  - ✓ More efficiently utilizes the transformer core's magnetizing current enables **smaller transformer** than flyback
  - ✓ Suitable for high frequency operation
  - ✓ Lower primary – secondary capacitance for **reduction in common mode noise** compared to flyback
- Disadvantages
  - Two primary windings
  - FETs see twice the input voltage
  - Requires a pre-regulated rail
  - Output regulation can be challenging


### Half-bridge Topology

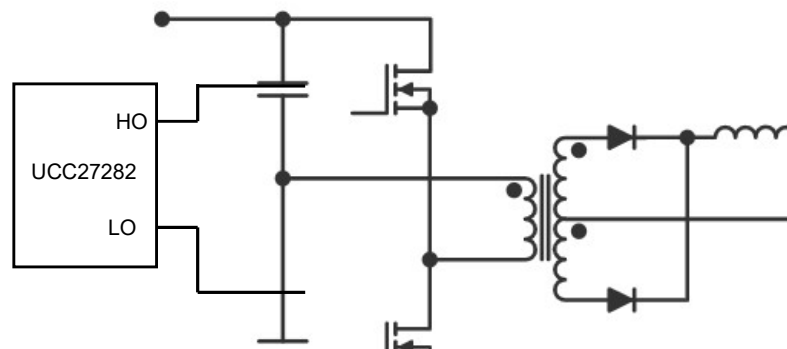

- Advantages
  - ✓ Design simplicity due to open loop configuration
  - ✓ More efficiently utilizes the transformer core's magnetizing current enables **smaller transformer** than flyback
  - ✓ Suitable for high frequency operation
  - ✓ Lower primary – secondary capacitance for **reduction in common mode noise** compared to flyback
- Disadvantages
  - Requires floating high side gate drive
  - Requires capacitor bridge
  - Requires a pre-regulated rail
  - Output regulation can be challenging



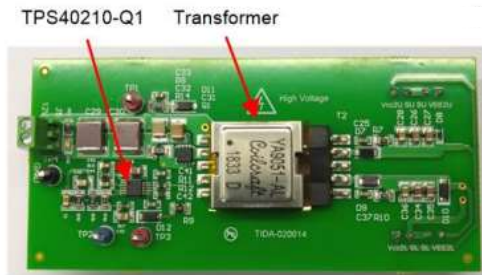
### TI Solution Comparison – TIDA-020014 and PMP10654




Top side

TPS40210-Q1 Flyback Controller

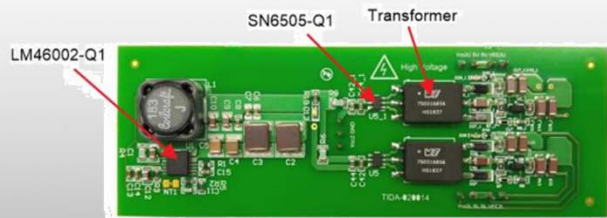


Top side

Buck + SN6505B-Q1 Push-Pull

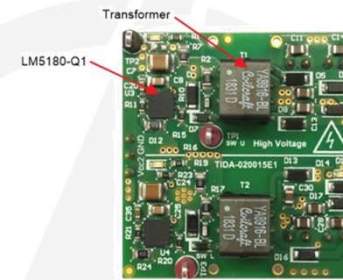




Top Side

LM5180-Q1 Flyback Converter

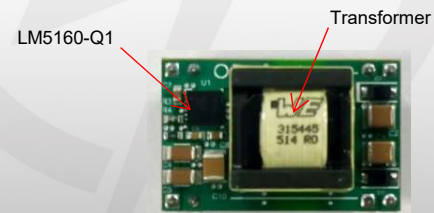

LM5160-Q1 Fly-Buck Converter
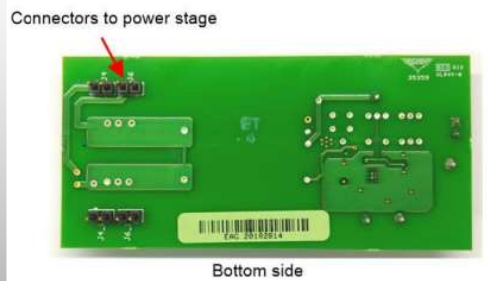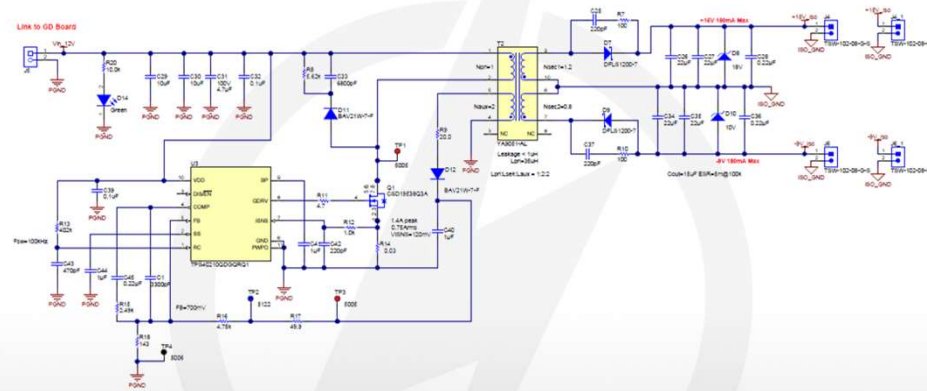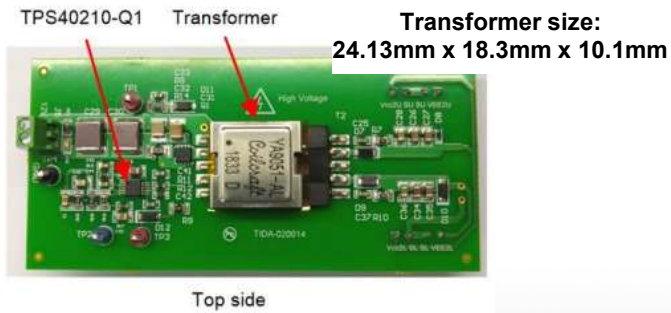
### TPS40210-Q1 flyback controller solution



PARAMETER	SPECIFICATION
Input voltage ( $V_{IN}$ )	5 V–42 V DC (52-V transient)
Output voltage ( $V_{OUT}$ )	+15 V, –9 V
Output ripple	±3%
Maximum output current ( $I_{out\_max}$ )	180 mA
Switching frequency	100 kHz
Output power ( $P_{out\_max}$ )	4.32 W
Efficiency	> 81% peak, 80% at full load


### TPS40210-Q1 Efficiency and Thermal performance

Measured Efficiency Under Input Voltages of 5V, 12V, and 18V



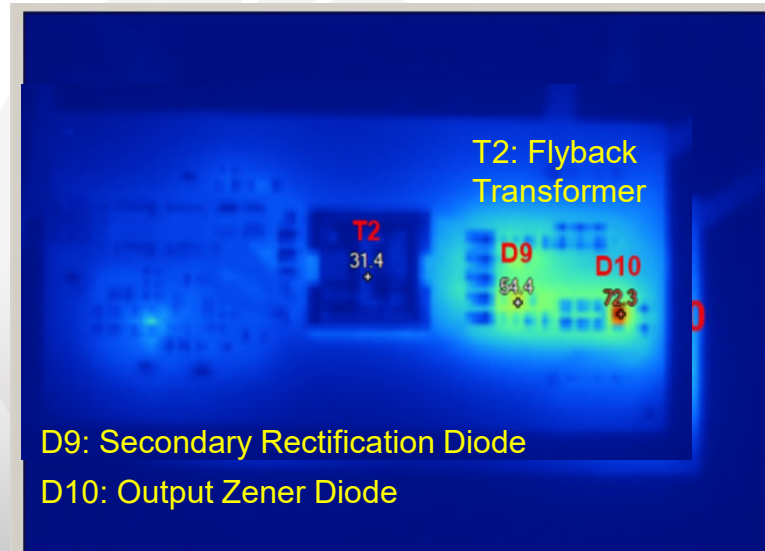81.3% peak efficiency at 12Vin


Thermal Image with Vin = 12V and Iout = 180mA



Secondary rectification diode: 54.4°C  
Output zener diode: 72.3°C

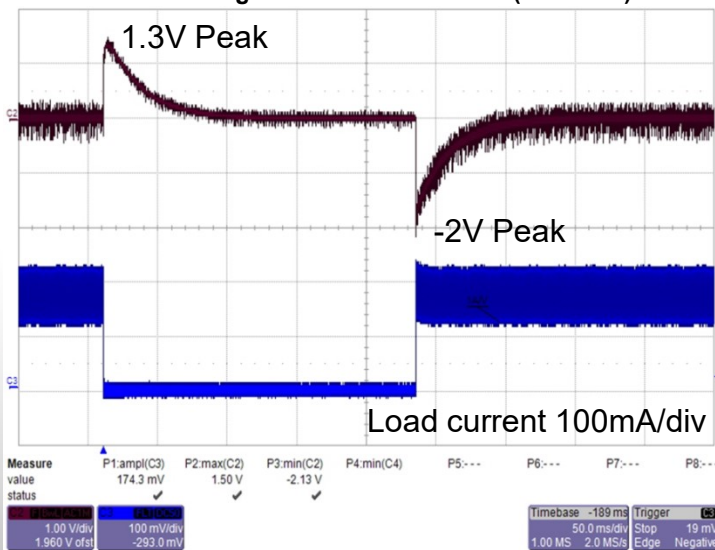
### TPS40210-Q1 Load Transient Response

Load transient response of the +15V rail under Vin = 12V and Iout switching between 0 and 180mA (50ms/div)



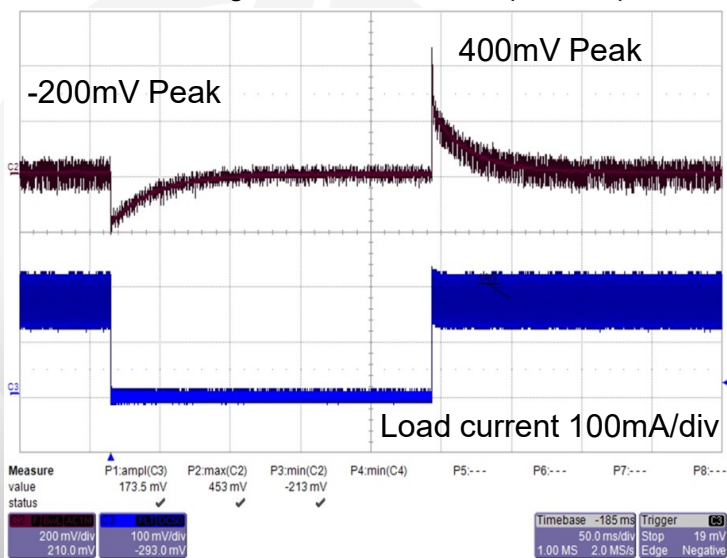1.3 V peak overshoot  
2V peak undershoot


Load transient response of the -9V rail under Vin = 12V and Iout switching between 0 and 180mA (50ms/div)



200 mV undershoot  
400 mV peak overshoot

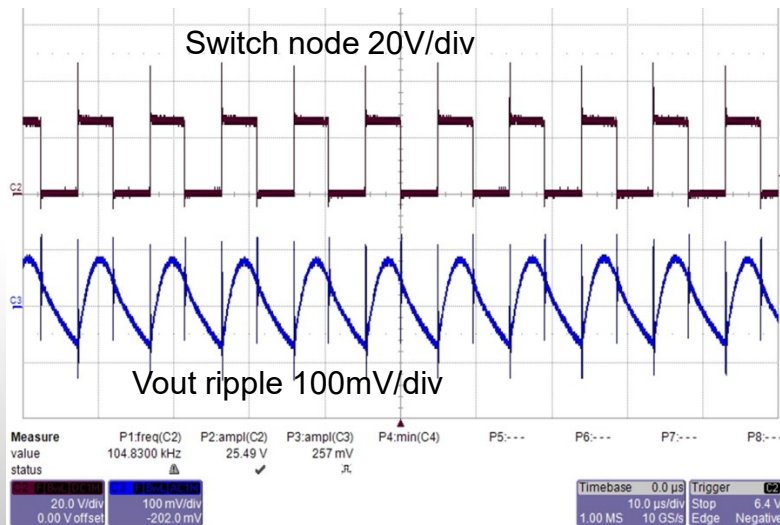
### TPS40210-Q1 Output Voltage Ripple and Load Regulation

Switching node waveform and output voltage ripple of +15V rail with 12V<sub>in</sub> and 180mA<sub>out</sub> (10µs/div)



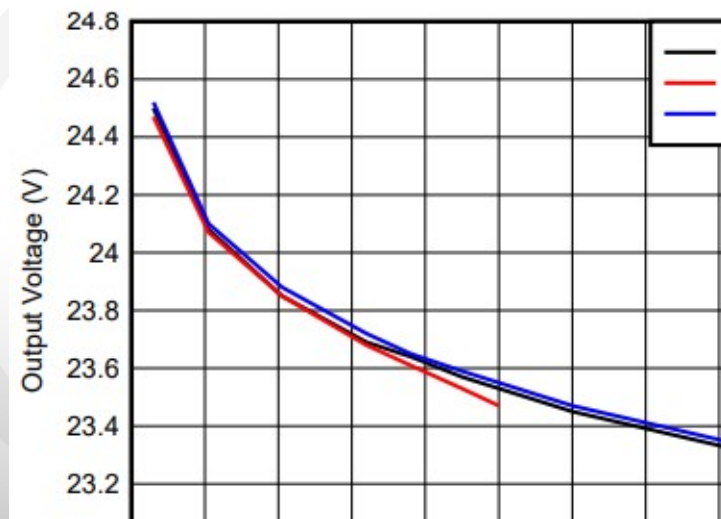
**180 mV peak to peak output voltage ripple**

Load Regulation Under Input Voltages of 5V, 12V, and 18V




**5.1% decrease in load regulation between 0 and 180mA load**

### TPS40210-Q1 Common Mode EMI and CMTI



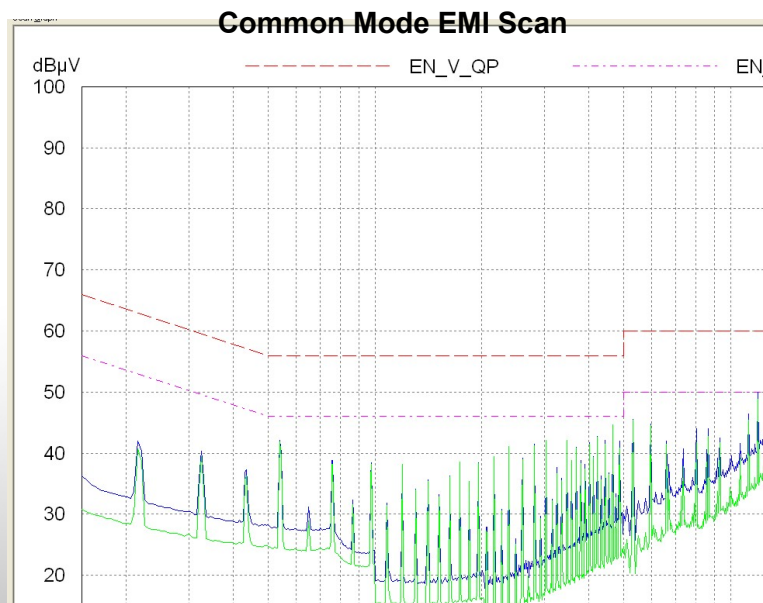


75 dBuV peak observed at around 22 MHz

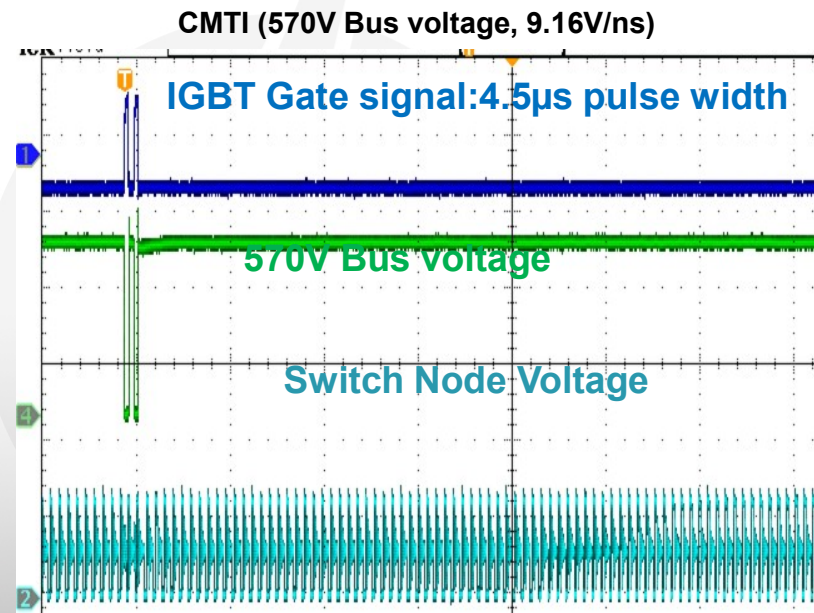

Supply operates smoothly without interruption to double pulse test
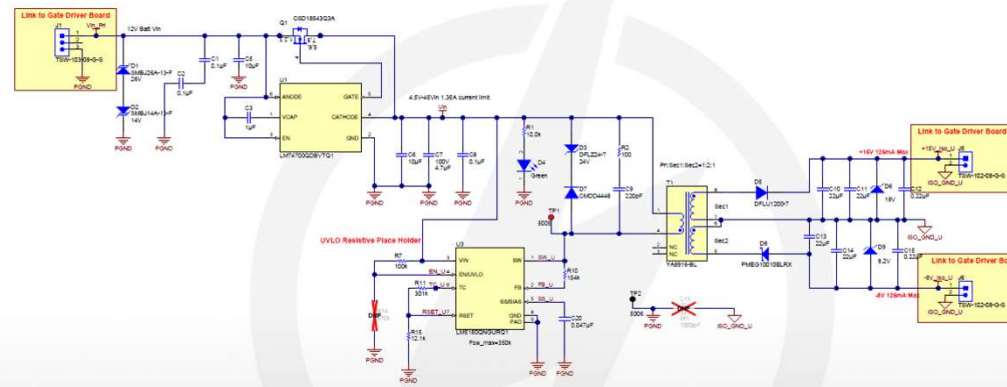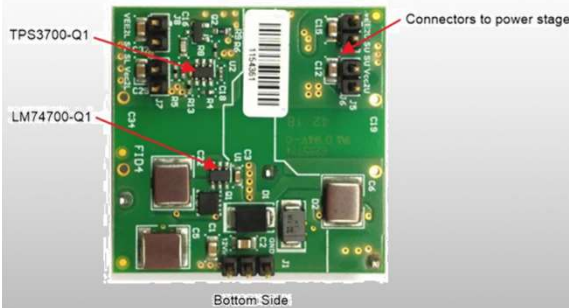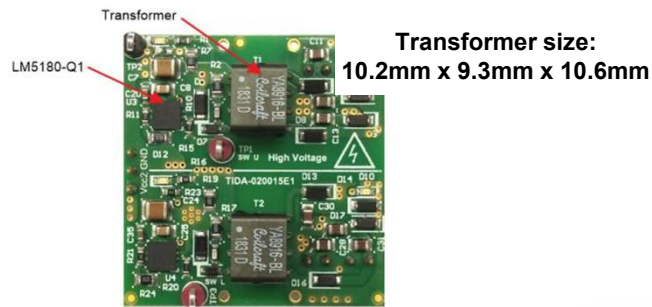
## LM5180-Q1 flyback converter solution overview



PARAMETER	SPECIFICATION
Input voltage ( $V_{in}$ )	4.5 V–65 V DC (For flyback converter only, TVS limits the system input to 26 V DC)
Output voltage ( $V_{OUT}$ )	15 V, -8 V
Output ripple	±3%
Maximum output current ( $I_{out,max}$ )	180 mA
Switching frequency	< 350 kHz
Output power ( $P_{out,max}$ )	4.14 W
Efficiency	86.2% peak at 12V <sub>in</sub>


### LM5180-Q1 Efficiency and Thermal Performance

Measured Efficiency Under Input Voltages of 5V, 12V, and 18V



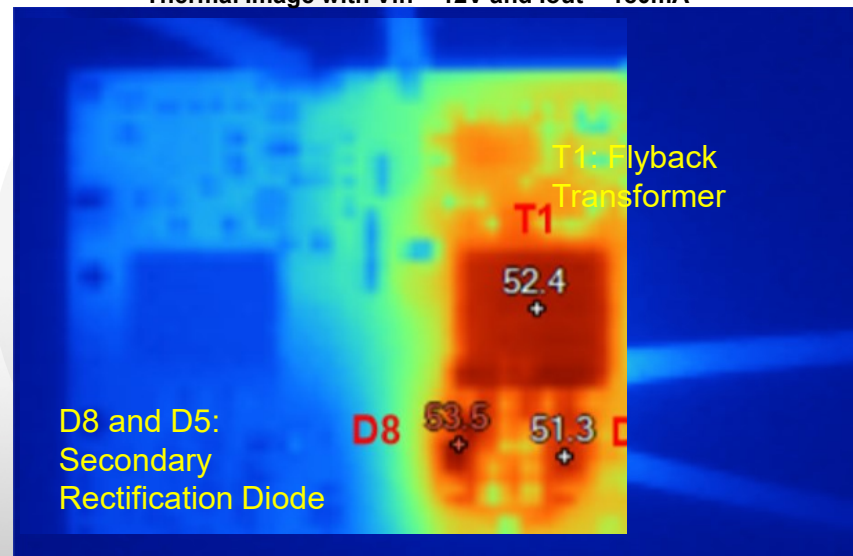86.2% peak efficiency at 12Vin

Thermal Image with Vin = 12V and Iout = 180mA




Flyback transformer: 52.4°C  
Rectification Diodes: 53.5°C/51.3°C



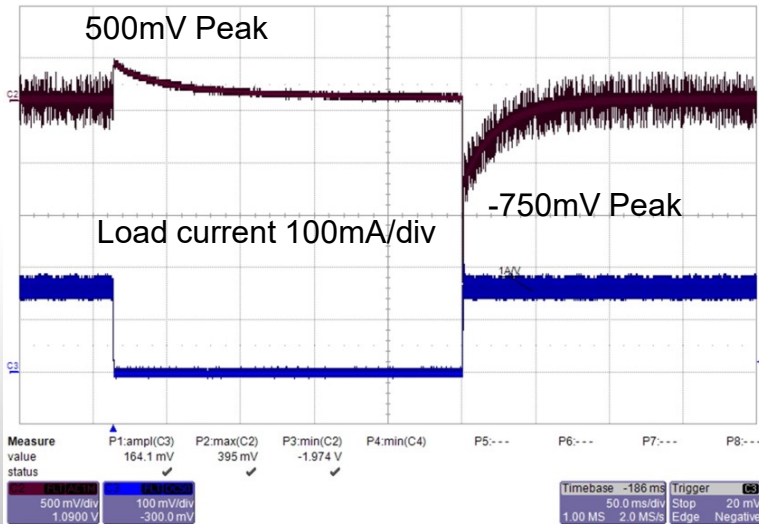
### LM5180-Q1 Load Transient Response

Load transient response of the +15V rail under  $V_{in} = 12V$  and  $I_{out}$  switching between 0 and 180mA (50ms/div)



500 mV peak overshoot  
750mV peak undershoot

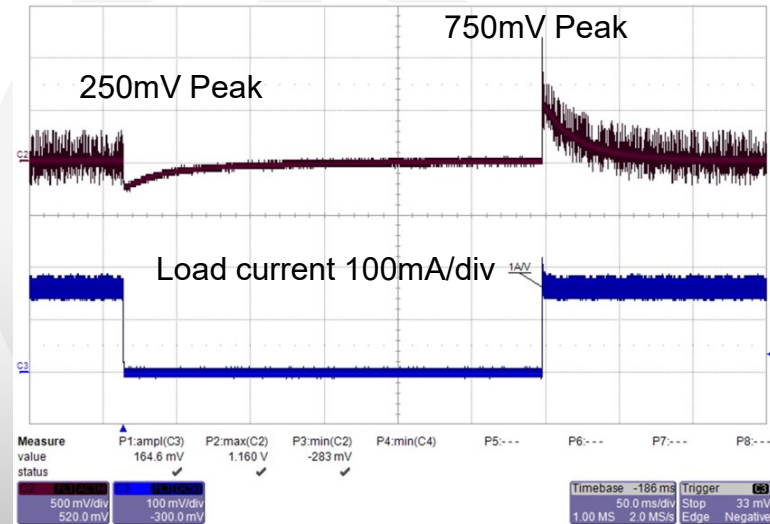
Load transient response of the -8V rail under  $V_{in} = 12V$  and  $I_{out}$  switching between 0 and 180mA (50ms/div)



250 mV peak undershoot  
750mV peak overshoot
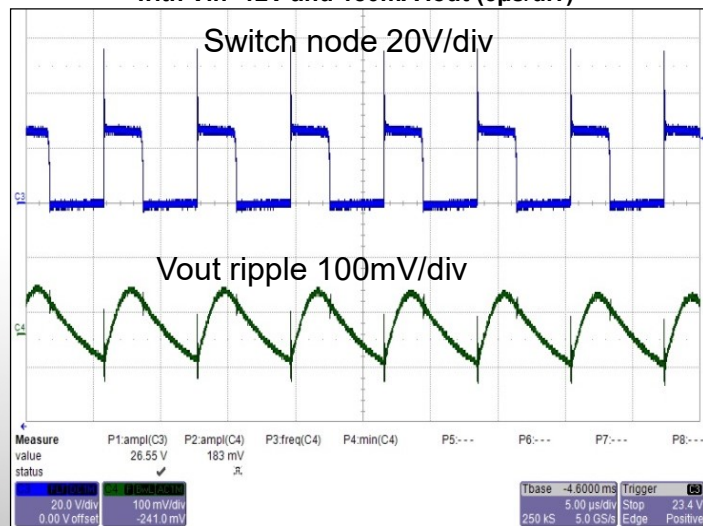
### LM5180-Q1 Output Voltage Ripple and Load Regulation

Switching node waveform and output voltage ripple of +15V rail with Vin=12V and 180mA iout (5µs/div)



**150 mV peak to peak output voltage ripple**


Load Regulation Under Input Voltages of 5V, 12V, and 18V



**2.28% decrease in load regulation between 0 and 180mA load**


### LM5180-Q1 Common Mode EMI Scan and CMTI

Common Mode EMI Scan

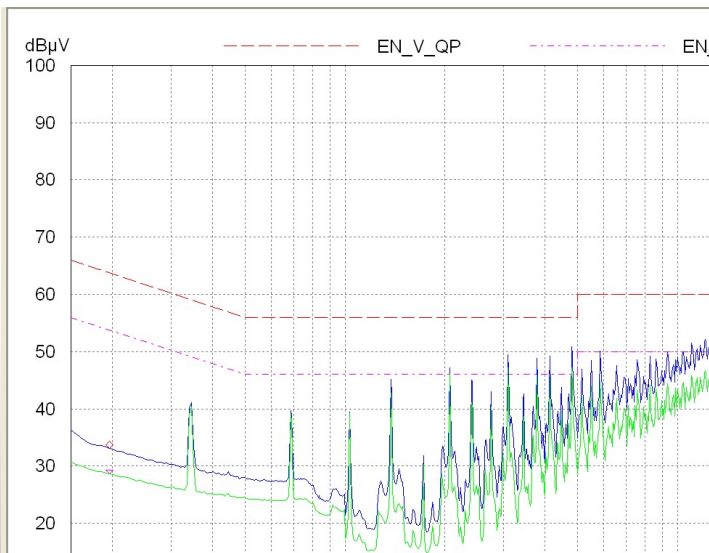




68 dBuV peak observed at 23 MHz

CMTI (570V Bus voltage, 10.8 V/ns)

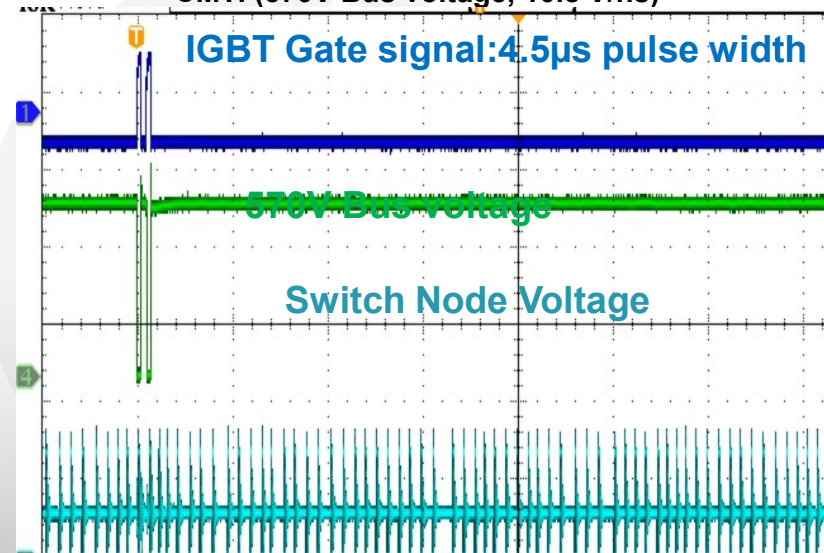

Supply operates smoothly without interruption to double pulse test

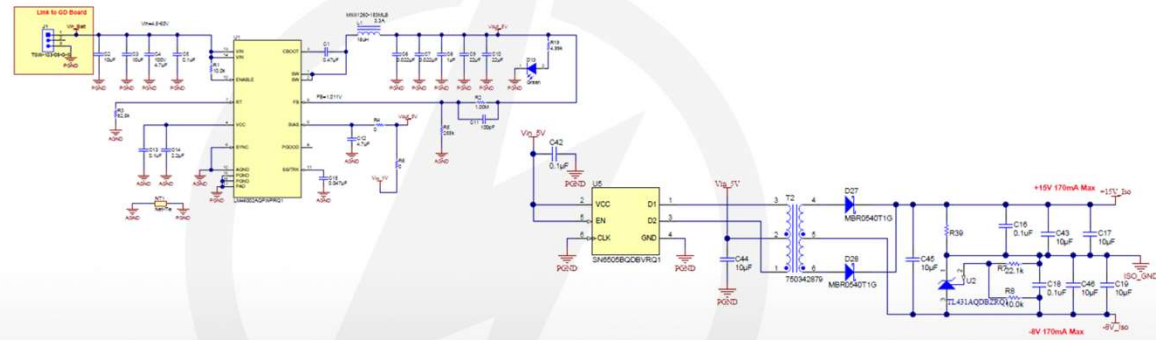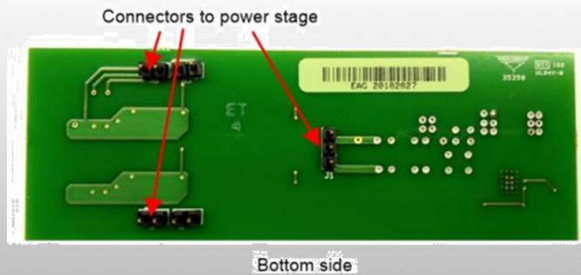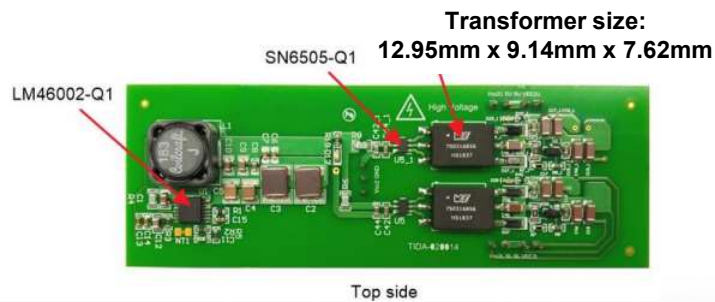
### LM46002A-Q1 Buck + SN6505B-Q1 Push-pull Solution Overview



PARAMETER	SPECIFICATION
Input voltage ( $V_{in}$ )	4.5V-60V (Buck stage) 5V +/- 5% (Push-pull stage)
Output voltage ( $V_{OUT}$ )	+15 V, -8 V
Output ripple	+/- 3%
Maximum output current ( $I_{out\_max}$ )	180mA
Switching frequency	<450 kHz
Output power ( $P_{out\_max}$ )	4.14W
Efficiency	78.5% peak at 12Vin

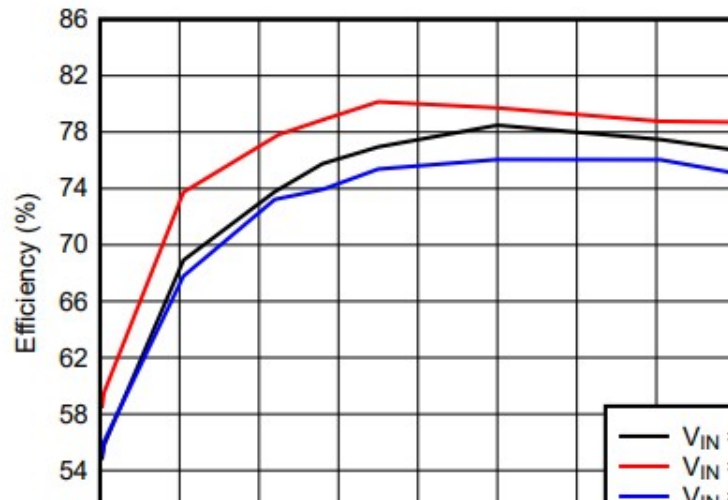
### Buck + SN6505B-Q1 Efficiency and Thermal Performance

Measured Efficiency Under Input Voltages of 5V, 12V, and 18V



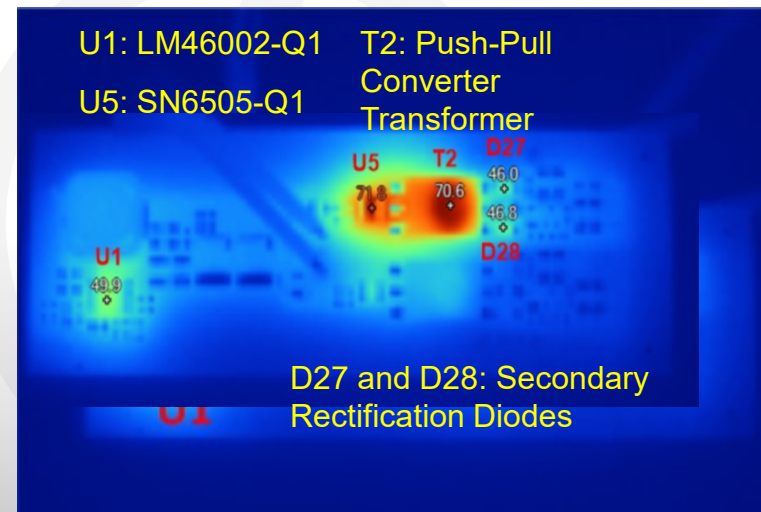78.5% peak efficiency at 12Vin


Thermal Image with  $V_{in} = 12V$  and  $I_{out} = 180mA$



Push-pull transformer: 70.6°C  
SN6505-Q1: 71.8°C

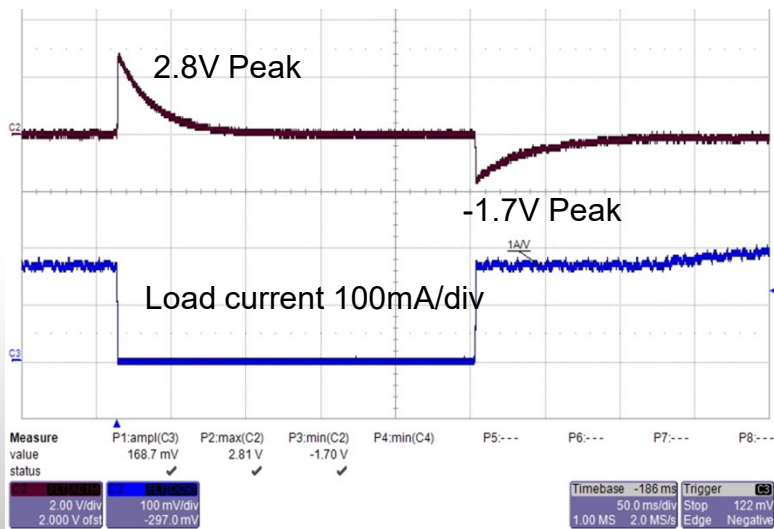
### Buck + SN6505B-Q1 Load Transient Response

Load transient response of the +15V rail under  $V_{in} = 12V$  and  $I_{out}$  switching between 0 and 180mA (50ms/div)



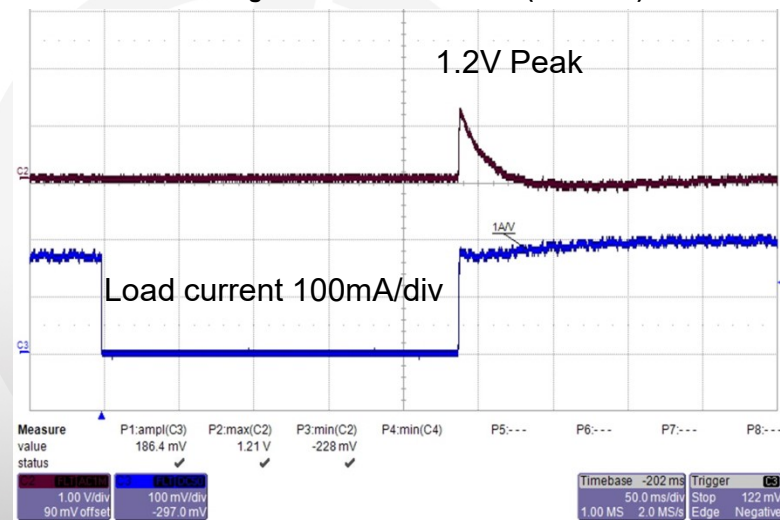2.8V peak overshoot  
1.7V peak undershoot


Load transient response of the -8V rail under  $V_{in} = 12V$  and  $I_{out}$  switching between 0 and 180mA (50ms/div)



1.2 V peak overshoot

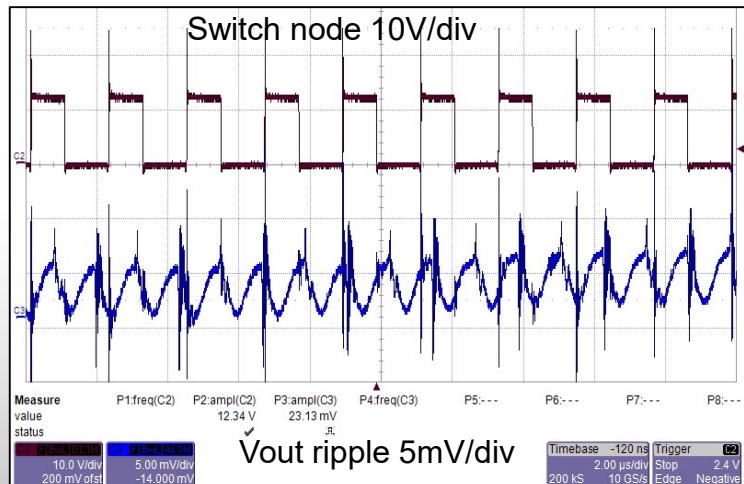
### Buck + SN6505B-Q1 Output Voltage Ripple and Load Regulation

Switching node waveform and output voltage ripple of +15V rail with  $V_{in}=12V$  and 180mA Iout (2 $\mu$ s/div)



7 mV peak to peak output voltage ripple

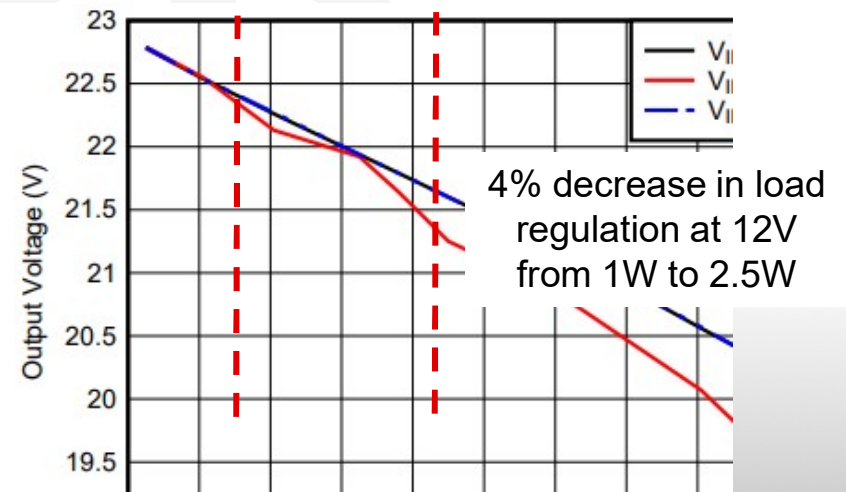
Load Regulation Under Input Voltages of 5V, 12V, and 18V



11.9% decrease in load regulation between 0 and 180mA load


### SN6505-Q1 Common Mode EMI Scan and CMTI

Common mode EMI scan

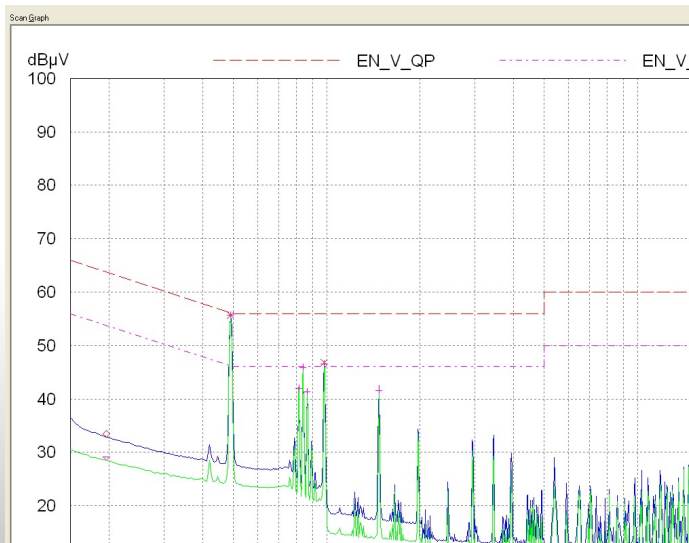

58 dBµV peak observed at 500 kHz

CMTI (570V Bus voltage, 10.26 V/ns)


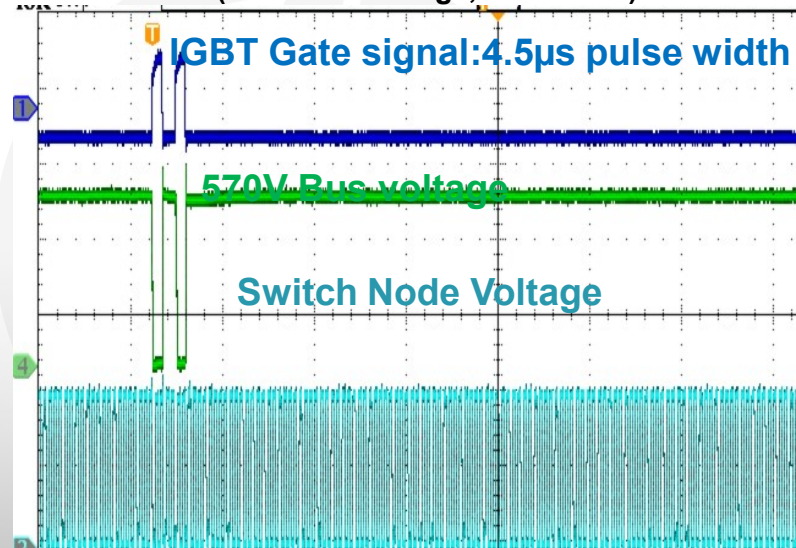


Supply operates smoothly without interruption to double pulse test


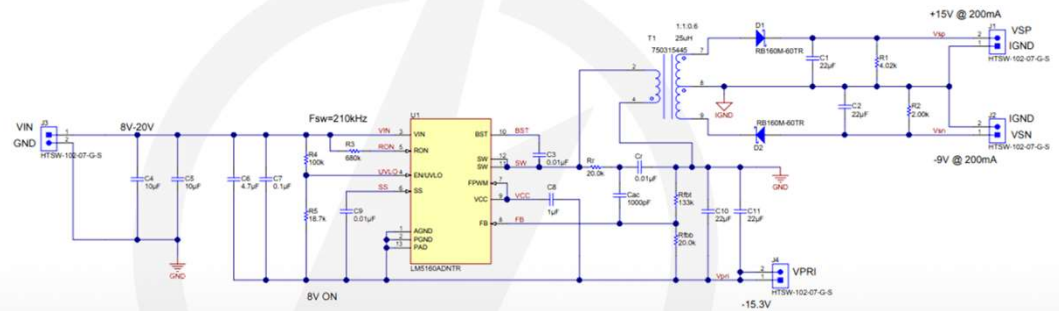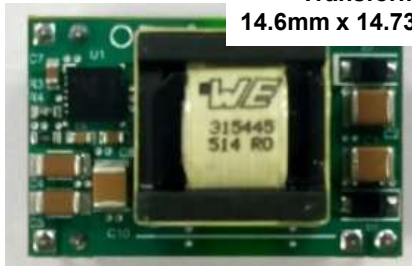
## LM5160-Q1 Fly-buck converter solution


Transformer size:  
14.6mm x 14.73mm x 8.5mm



PARAMETER	SPECIFICATION
Input voltage ( $V_{in}$ )	12V nominal, 8V – 20V
Output voltage ( $V_{OUT}$ )	+15 V, -9 V
Output ripple	+/- 3%
Maximum output current ( $I_{out,max}$ )	200mA
Switching frequency	210 kHz
Output power ( $P_{out,max}$ )	4.8W
Efficiency	86% peak at 12Vin

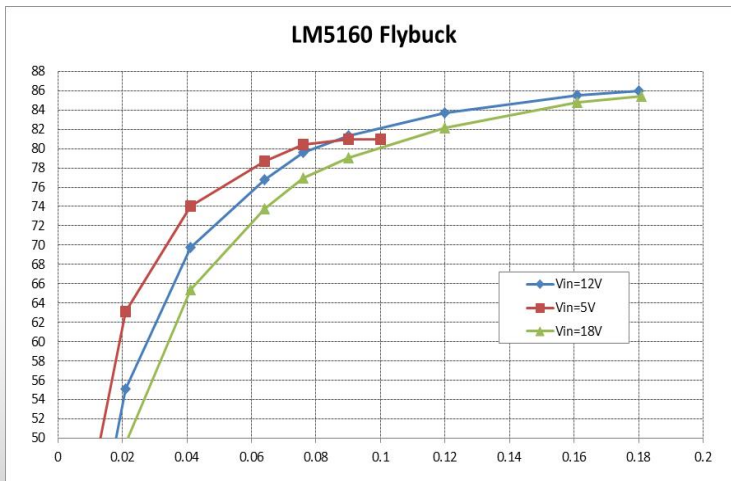
### LM5160-Q1 Efficiency and Thermal

Measured Efficiency Under Input Voltages of 5V, 12V, and 18V



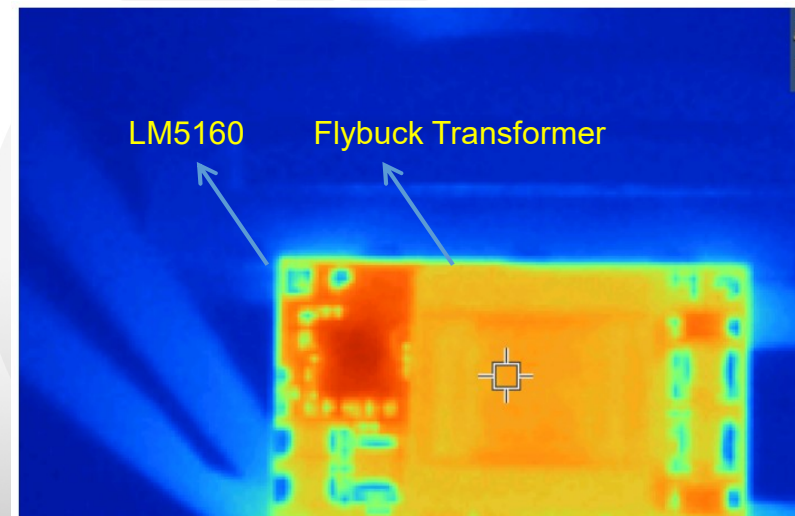85.9% peak efficiency at 12Vin


Thermal Image with Vin = 12V and Iout = 180mA



Flybuck transformer: 49°C  
LM5160: 53°C

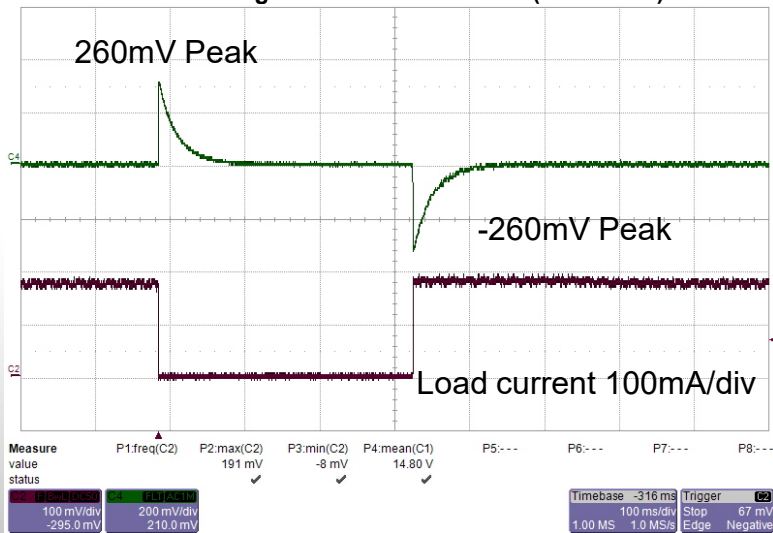
### LM5160-Q1 Load Transient Response

Load transient response of the +15V rail under Vin = 12V and Iout switching between 0 and 180mA (100ms/div)



260 mV peak overshoot  
260 mV peak undershoot

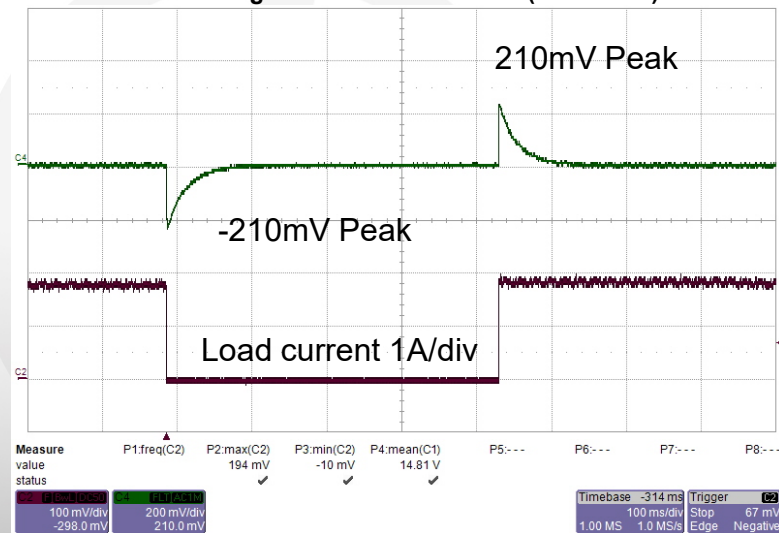
Load transient response of the -9V rail under Vin = 12V and Iout switching between 0 and 180mA (100ms/div)



210 mV peak overshoot  
210 mV peak undershoot

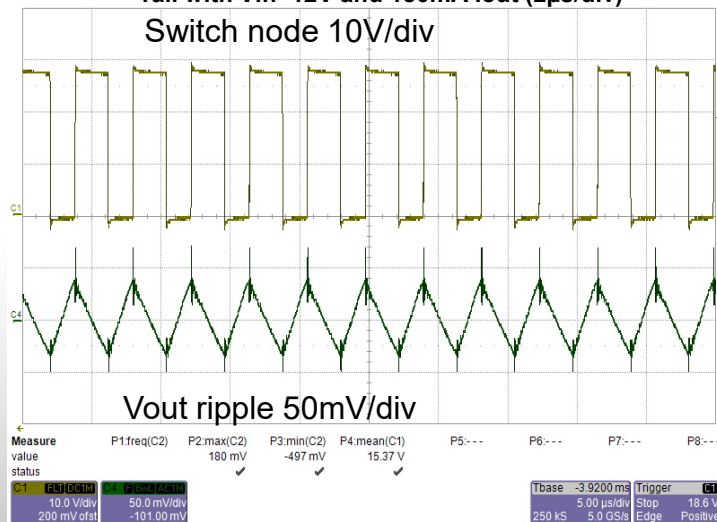
### LM5160-Q1 Output Voltage and Load Regulation

Switching node waveform and output voltage ripple of +15V rail with Vin=12V and 180mA Iout (2µs/div)



50mV peak to peak output voltage ripple

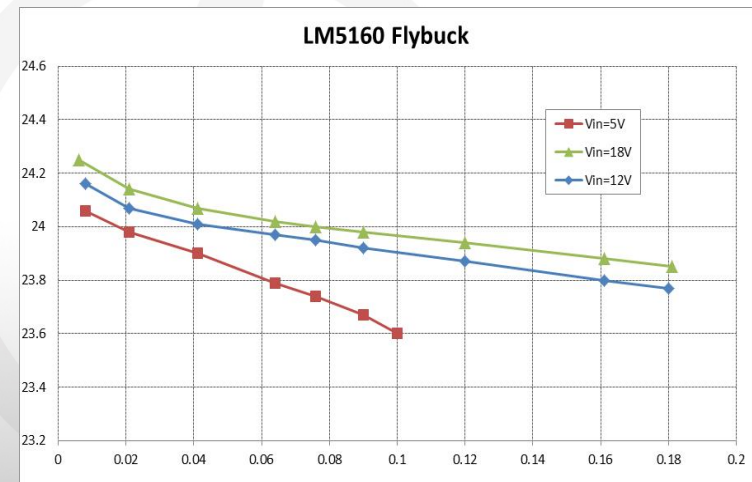Load Regulation Under Input Voltages of 5V, 12V, and 18V



1.6% decrease in load regulation between 0 and 180mA load

### Comparison of TI solutions

Solution	Cpri_Sec (pF)	Tx_Vol (mm <sup>3</sup> )	Isolation Voltage (kV <sub>RMS</sub> )	Sw Freq (kHz)	Common mode EMI Performance
TPS40210-Q1 Flyback Controller	31	4459	5000	110	75 dBuV peak at 20MHz
LM5180-Q1 Flyback Converter	24	1006	1500	340	68 dBuV peak at 28MHz
Buck with SN6505-Q1 push-pull transformer driver	8.7	947	3125	430	57 dBuV peak at 500kHz
LM5160-Q1 Flyback Converter		1827	2500	210	

### Comparison of TI solutions

Topology	Efficiency	Load Regulation	Load Transients	Solution Size (Dual)	Cost	Design Simplicity	Common mode EMI
LM5180-Q1 Flyback Converter	86.2% peak at 12Vin	2.28% decrease	3.3% Overshoot 5% Undershoot	37mm X38mm	High	Simple	
TPS40210-Q1 Flyback Controller	81.3% peak at 12Vin	5.1% decrease	8.6% Overshoot 13% Undershoot	160mm X64mm	Lowest	Simple	
Buck with SN6505-Q1 push-pull	78.5% peak at 12Vin	11.9% decrease	18.7% Overshoot 11.3% Undershoot	55mm x28mm	Low	Simple	
LM5160-Q1 Flyback Converter	85.9% peak at 12Vin	1.6% decrease	1.7% Overshoot 1.7% Undershoot	42mm X38mm	High	Complex	

## Summary

- **HEV/EV powertrain applications**
- Power architectures and their trade-offs
  - Centralized, Semi-Distributed, Distributed, and Two-stage Distributed
- Topology Comparison
  - Flyback, Fly-buck, Push-pull, and Half-Bridge
- TI solution comparison
  - TIDA-020014 and PMP10654

## Summary

- HEV/EV powertrain applications
- **Power architectures and their trade-offs**
  - **Centralized, Semi-Distributed, Distributed, and Two-stage Distributed**
- Topology Comparison
  - Flyback, Fly-buck, Push-pull, and Half-Bridge
- TI solution comparison
  - TIDA-020014 and PMP10654



### Power Architecture Summary

#### Centralized

##### Advantages

- ✓ Low component count
- ✓ Low cost
- ✓ Second sourcing

##### Disadvantages

- Bulky transformer
- Poor bias power quality
- Complex PCB layout
- Lack of redundancy

#### Semi-Distributed

##### Advantages

- ✓ Simpler transformer construction
- ✓ Simplified PCB Layout
- ✓ Better bias power quality
- ✓ Distribution of weight
- ✓ Second sourcing

##### Disadvantages

- Higher component count than centralized
- Higher cost than centralized
- Lack of redundancy

#### Distributed




##### Advantages

- ✓ Robustness against power supply failure
- ✓ Simpler transformer construction
- ✓ Simplified PCB Layout
- ✓ Better bias power quality
- ✓ Distribution of weight for ease of passing shock

##### Disadvantages

- Highest component count
- Highest cost

#### Distributed Power

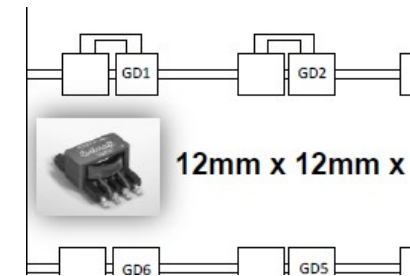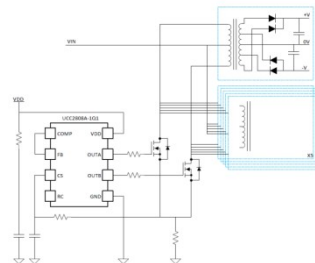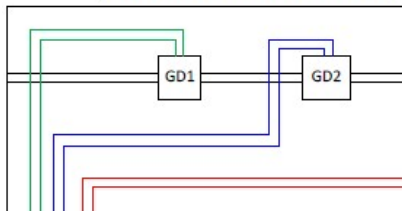

## Summary

- HEV/EV powertrain applications
- Power architectures and their trade-offs
  - Centralized, Semi-Distributed, Distributed, and Two-stage Distributed
- **Topology Comparison**
  - **Flyback, Fly-buck, Push-pull, and Half-Bridge**
- TI solution comparison
  - TIDA-020014 and PMP10654

### Topology Summary


#### Flyback

##### Advantages

- ✓ Operates directly off-battery
- ✓ Regulated output (PSR)
- ✓ Low Component count
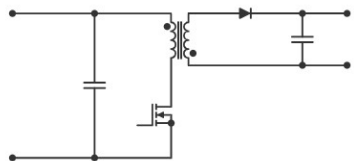
##### Disadvantages

- Switching frequency limitation
- Prone to EMI issues
- Requires a snubber



External FET: TPS40210-Q1, UCC2813-5-Q1, LM5155-Q1

Integrated FET: LM5180-Q1


#### Fly-buck

##### Advantages

- ✓ Operates directly off-battery
- ✓ Regulated output without opto
- ✓ Low Component count
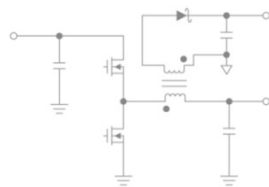
##### Disadvantages

- High leakage inductance can degrade load regulation
- Duty cycle limitation
- Magnetic design complexity



Integrated FET: LM5161-Q1, LM5160-Q1


#### Push-Pull

##### Advantages

- ✓ Design simplicity due to open loop configuration
- ✓ Suitable for high frequency
- ✓ Smaller magnetics
- ✓ Low primary-secondary capacitance
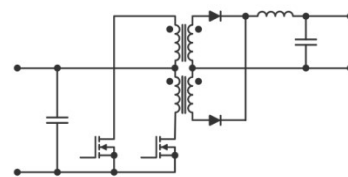
##### Disadvantages

- Requires a pre-regulated rail
- Output regulation can be challenging
- Two primary windings
- External FETs see twice the  $V_{in}$



External FET: UCC2808A-1Q1/2Q1, LM25037-Q1

Integrated FET: SN6505B-Q1


#### Half-Bridge

##### Advantages

- ✓ Design simplicity due to open loop configuration
- ✓ Suitable for high frequency
- ✓ Smaller magnetics
- ✓ Low primary-secondary capacitance
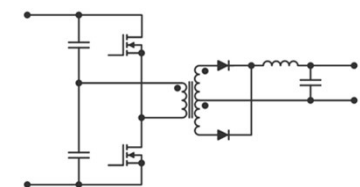
##### Disadvantages

- Requires a pre-regulated rail
- Output regulation can be challenging
- Requires floating high side gate driver



External FET: TPS28225-Q1

## Summary

- HEV/EV powertrain applications
- Power architectures and their trade-offs
  - Centralized, Semi-Distributed, Distributed, and Two-stage Distributed
- Topology Comparison
  - Flyback, Fly-buck, Push-pull, and Half-Bridge
- **TI solution comparison**
  - **TIDA-020014 and PMP10654**



© Copyright 2017 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly "as-is," for informational purposes only, and without any warranty.  
Use of this material is subject to TI's **Terms of Use**, viewable at TI.com