

# Precision Amplifiers for Battery Test Systems

## *Series Overview*




Precision Amplifiers

# Series Agenda

- **Series overview**
  - Testing theory
  - Charge/discharge cycles
- **Current sensing**
  - Important specs
- **Voltage sensing**
  - Important specs
- **Control loops**
  - CC control loop theory
  - CV control loop theory
  - Important specs

- **Drivers and buffers**
  - Driver (power amplifier)
  - Buffers (design dependent)
- **Simulation and results**
  - TINA-TI simulation
  - CC/CV accuracy results
  - Load regulation results


# CC and CV Control Precision

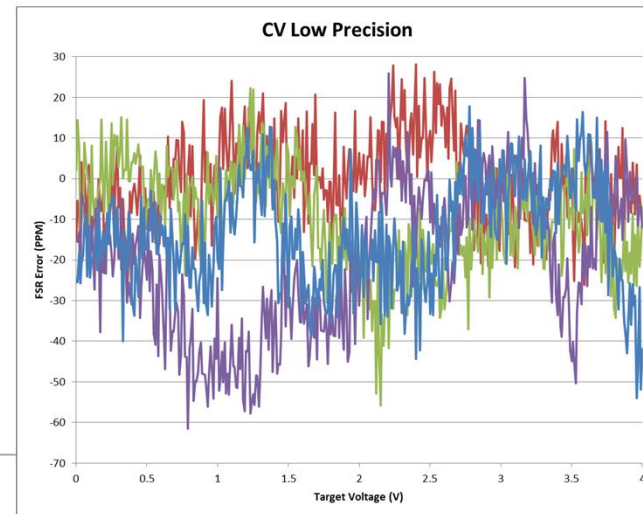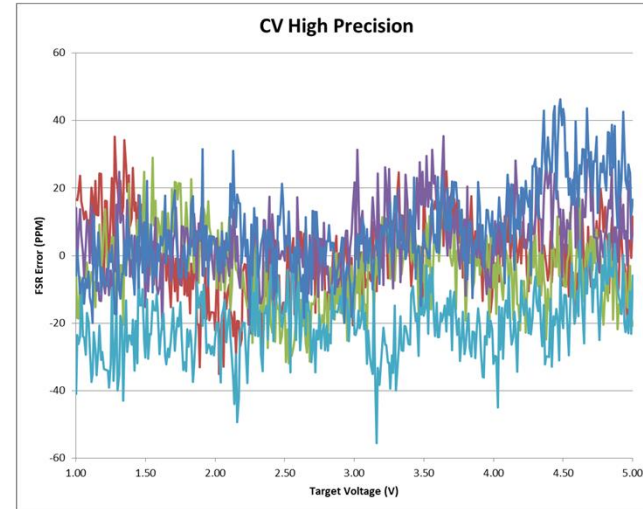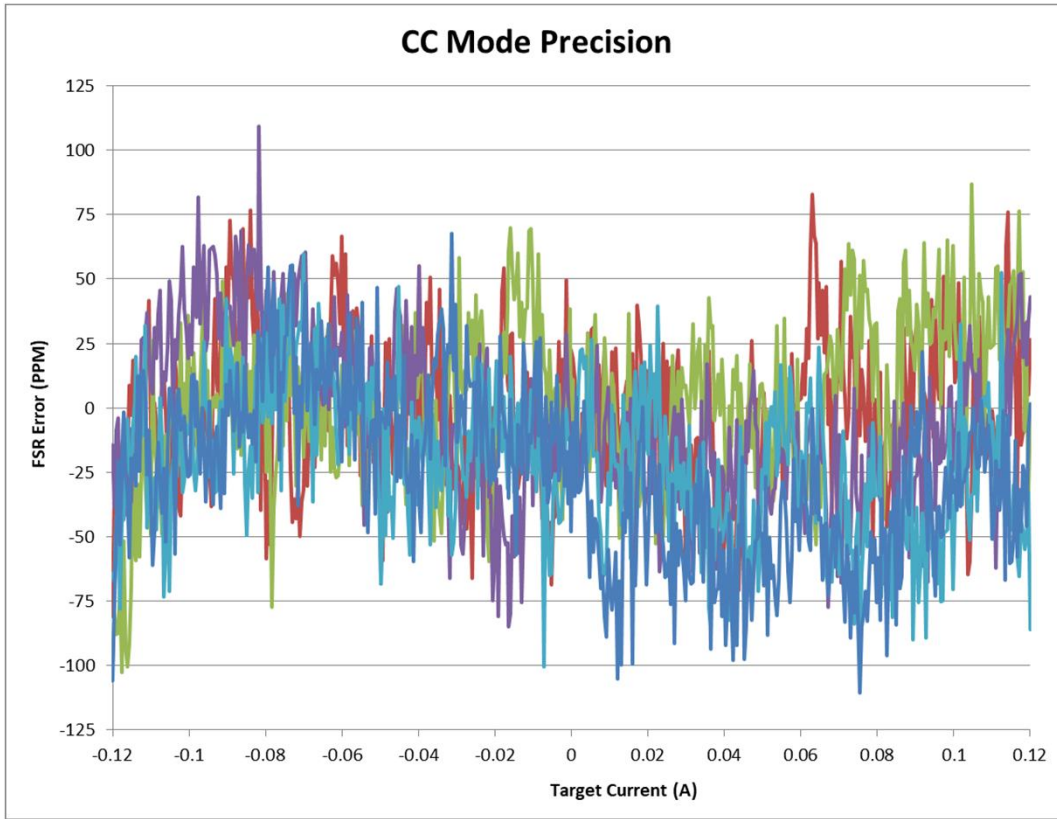

- Run 1
- Run 2
- Run 3
- Run 4
- Run 5


MENTS

# Battery Test Theory Overview

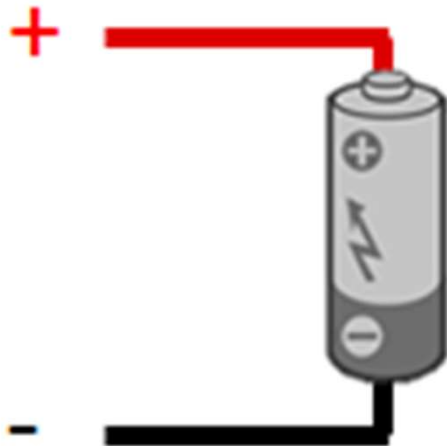


- For a single Li+/LiPo battery cell, there is a maximum battery voltage called the “regulation voltage” that represents the upper charging limit (usually ~4.2V, depending on the battery). There is also a minimum battery voltage called the “threshold voltage” that establishes the lower discharging limit (usually ~2.8V, any lower will damage the battery).
- For the purposes of this discussion, we will focus on charging/discharging only **one single-cell LiPo battery**
- Three main kinds of tests can be performed:
  - **Battery formation** – initialization charge/discharge cycle required for battery to store energy properly and to be graded
  - **Loop & Feature test** – repeated charge/discharge cycles to verify battery life and reliability are within tolerance
  - **Functional test** – test to make sure battery works properly before packaging
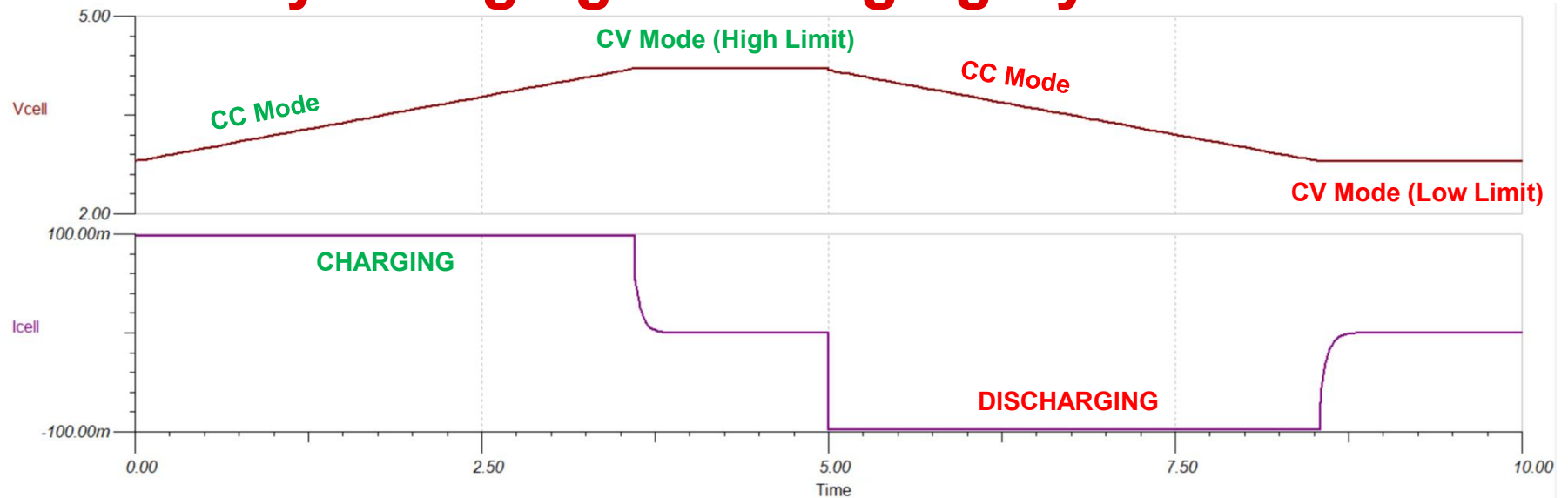
# $\text{Li}^+$ Battery Charging/Discharging Cycles



- When the battery is charging/discharging at a fixed current, we call this **constant current (CC) mode**.
- When the battery voltage nears the regulation or threshold voltage, **constant voltage (CV)** mode takes over and current rolls off until the charging cycle is terminated

# System Overview

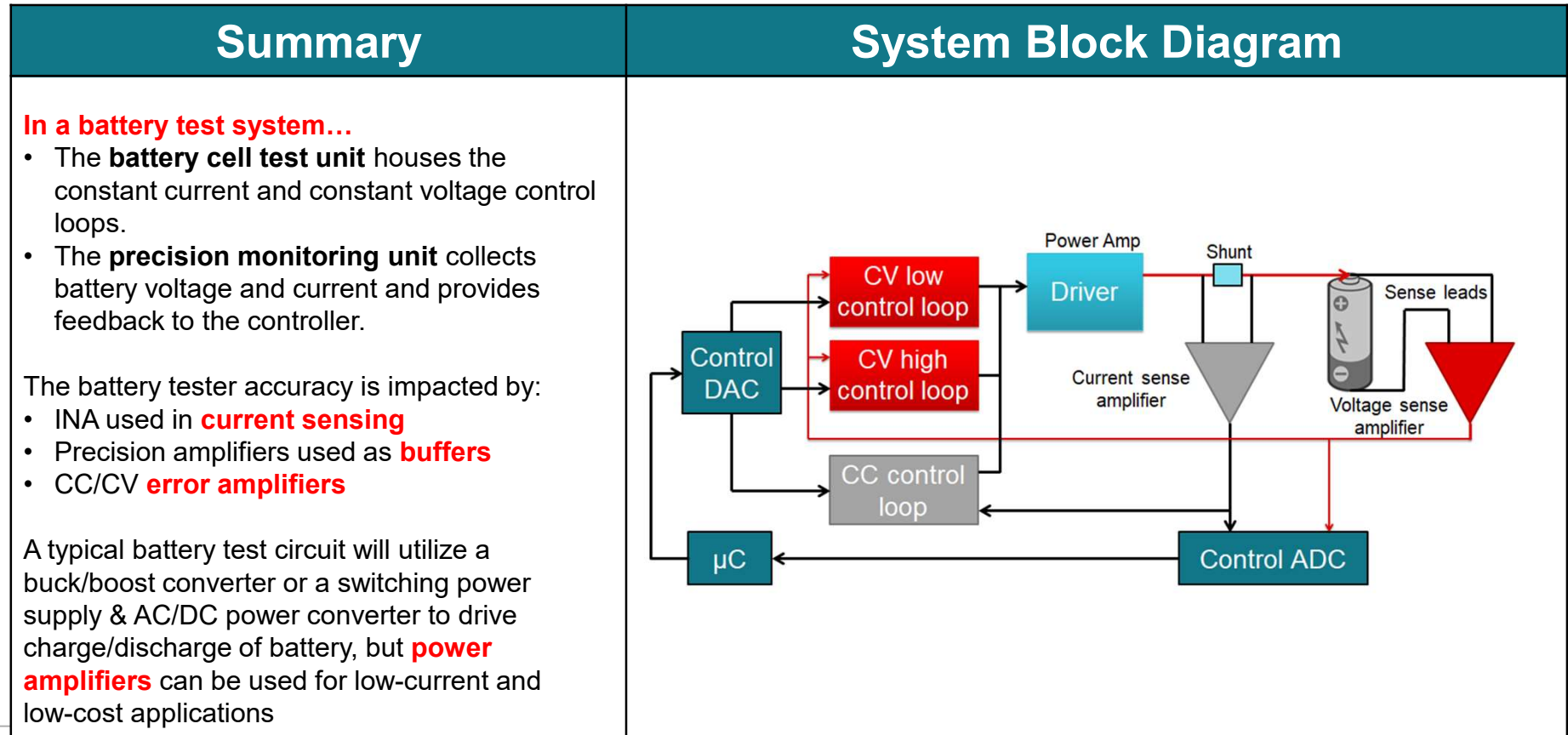

# Thank you for your time!

**Visit [ti.com](http://ti.com) for more BTS resources**


# Precision Amplifiers for Battery Test Systems

## *Current Sensing*


Precision Amplifiers



# Battery Current Sensing

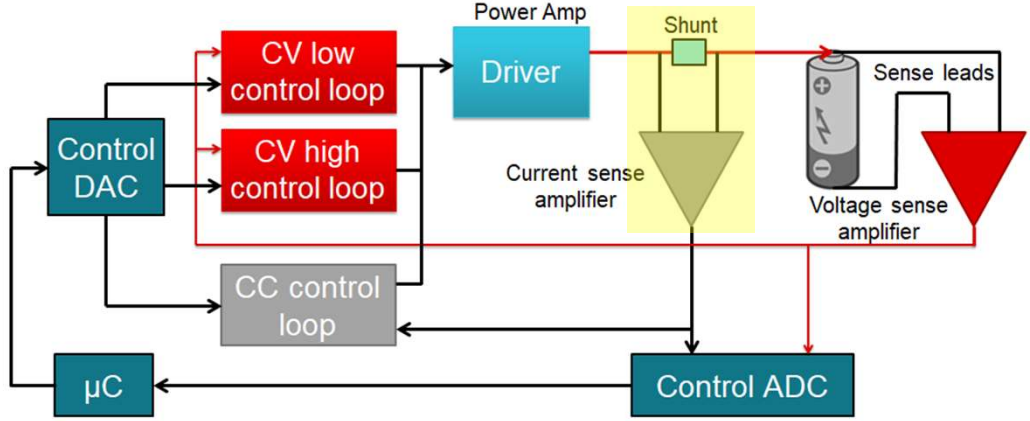Socket Function	System Block Diagram
<p><b>Function</b> – measure battery charge/discharge current via shunt resistor.</p> <ul style="list-style-type: none"><li>• Typical shunt values are around 0.5Ω, smaller shunts require higher gain to make full use of dynamic range of amplifier</li><li>• Accurate current measurement is crucial – used for calculating battery capacity, battery impedance, and even for battery health metrics</li></ul> <p>Typically done with an <b>INA (Instrumentation Amplifier)</b> – benefits over integrated shunt current sense amplifiers include:</p> <ul style="list-style-type: none"><li>• High input impedance</li><li>• Noise performance</li><li>• Gain optimization / configurability</li></ul> <p><b>Example product</b> – INA188</p>	 <p>The diagram illustrates the system architecture for battery current sensing. A microcontroller (μC) is connected to a Control DAC and a Control ADC. The Control DAC outputs to a CV low control loop and a CV high control loop, which both feed into a Driver (Power Amp). The Driver is connected to a Shunt resistor. The Shunt resistor is connected to a Current sense amplifier. The Current sense amplifier outputs to a CC control loop, which feeds back into the μC. The Shunt resistor is also connected to a Voltage sense amplifier, which outputs to the Control ADC. The Control ADC outputs to the μC. A battery is connected to the Shunt resistor and the Voltage sense amplifier. Sense leads are connected to the Voltage sense amplifier.</p>

# Important Specs for Current Sensing

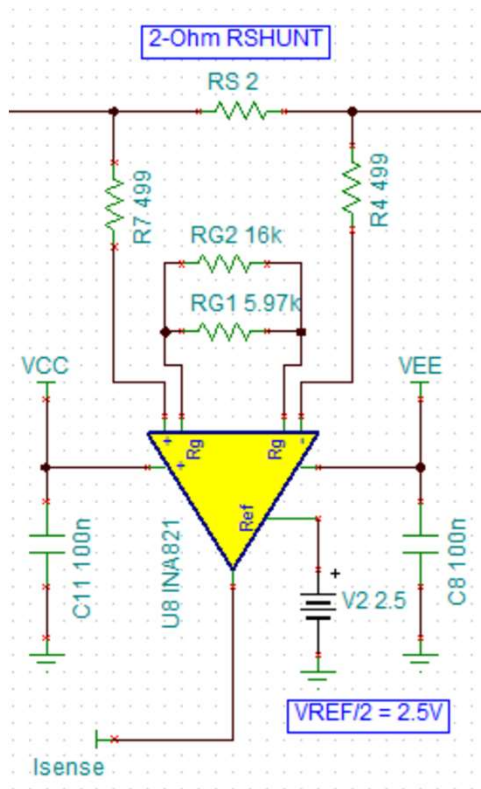

- Steady-state offsets may be accounted for the calibration. In this case, drift and linearity become the main error sources.
  - **Offset temperature drift** causes offset errors to worsen with increased temperature
  - **Bias current drift** increases input bias current IR drop across the current limiting resistors, worsening at higher temperatures
  - **Gain error drift** causes gain error to change with increased temperature
  - **Shunt resistance drifts** - high resistor tolerance and low drift are essential for robust accuracy
- **Linearity** – it is very important the amplifier has good gain linearity, in order to maintain a flat response across a wide range of load currents
- **Bandwidth** – want enough BW for the loop to update quickly, but not so much that high-frequency noise from nearby devices becomes a problem
- **Noise** – oversampling can reduce the effect of broadband noise, but 1/f noise cannot be averaged out

# Precision Current Sensing Devices

## Recommended Devices

	Highest BW Low Noise	Mid BW Lower Power	Lowest Drift
Specifications	INA821	INA818/9	INA188
Vs min/max (V)	4.5/36	4.5/36	4/36
Max Gain Nonlinearity (ppm, G=1)	10	10	8
GBW (MHz) (G=1)	4.7	2	0.6
Slew Rate (V/ $\mu$ s)	2.1	0.9	0.9
Vos max ( $\mu$ V)	35	35	55
Drift (Max) ( $\mu$ V/C)	0.4	0.4	0.2
CMRR (Max Gain) (Min) (dB)	140	140	118
Iq typ (mA)	0.6	0.35	1.6
1/f Input Voltage Noise ( $\mu$ Vpp)	0.14	0.19	0.25
Ibias (Max) (nA)	0.5	0.5	2.5
Gain Error (% Max)	0.15	0.15	0.5
Gain Drift (ppm/ $^{\circ}$ C)	35	35	50
Added Features	$\pm$ 40 OVP	$\pm$ 60 OVP	RFI-Filtered
Technologies	Super-beta	Super-beta	Zero-drift

<https://www.ti.com/amplifier-circuit/instrumentation/overview.html>

# Thank you for your time!


**Visit [ti.com](http://ti.com) for more BTS resources**

# Precision Amplifiers for Battery Test Systems

## *Voltage Sensing*

Precision Amplifiers


# Battery Voltage Sensing

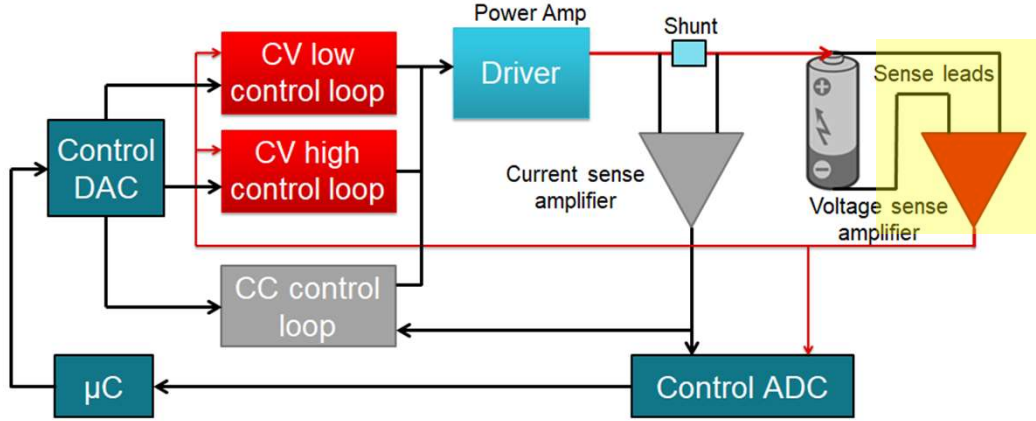Socket Function	System Block Diagram
<p><b>Function</b> – Precisely monitor the voltage across the battery terminals</p> <ul style="list-style-type: none"><li>• Accurate voltage measurement ensures the tester does not over-charge or over-discharge the battery (exceed the regulation voltage or go below the threshold voltage)</li><li>• Op amp selection depends on system accuracy requirements</li></ul> <p><b>Example product</b> – OPA188, INA188</p>	 <p>The diagram illustrates a battery charging system with voltage sensing. A microcontroller (μC) is connected to a Control DAC and a Control ADC. The Control DAC outputs to three control loops: CV low control loop, CV high control loop, and CC control loop. The CV loops control a Driver (Power Amp) which is connected to a Shunt resistor. The Shunt resistor is connected to a Current sense amplifier. The CC control loop also controls the Driver. The Current sense amplifier outputs to the Control ADC. The Control ADC also receives input from a Voltage sense amplifier, which is connected to the battery terminals via Sense leads. The battery is represented by a battery symbol with a lightning bolt icon.</p>

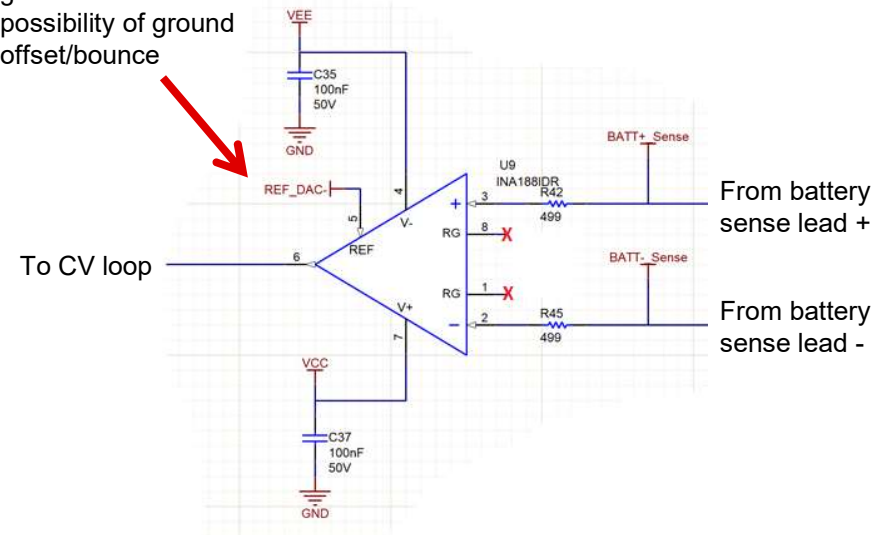
## 4-Lead Wire Battery Voltage Sense

- Sense leads to the terminals are monitored for **battery voltage measurement**, instead of the connections to the driver output
- This **4-wire remote sensing** reduces voltage offset error because the charge/discharge current does not pass through the sense leads, which only look into the high-impedance inputs of the amplifier. Therefore the only  $I \cdot R$  drop across the current limiting resistors is due to the input bias current

Referenced to DAC ground to reduce possibility of ground offset/bounce


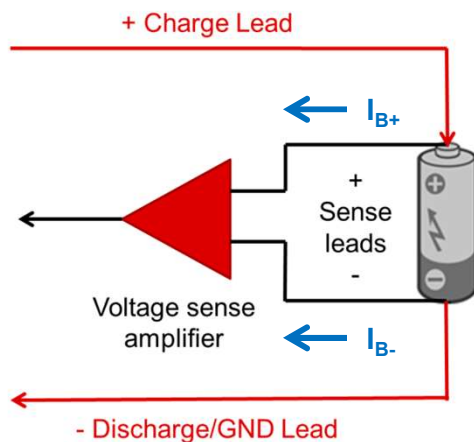
# Important Specs for Battery Voltage Sense



- **Offset voltage** results in incorrect measurement of battery terminals
- **Offset temperature drift** causes offset errors to worsen as temperature rises
- **CMRR** determines offset error due to common mode voltage
- **Input bias current** causes an IR drop across the current limiting resistors ( $R_{LIM}$ ), again worsening at higher temperatures

- **Input offset current** ( $I_{B+} - I_{B-}$ ) results in a different IR drop on the +/- inputs, resulting in incorrect differential measurement across terminals.
- If voltage sense amplifier bias current is high enough relative to charge/discharge current, some current intended for battery will be redirected, reducing current measurement accuracy

$$V_{ERR\_RTI} = V_{OS\_MAX} + \frac{dV_{OS}}{dT_{max}} * \Delta T + \frac{V_{BAT}}{CMRR} + (I_{B+} * R_{LIM+} - I_{B-} * R_{LIM-}) + \dots$$



# Precision Voltage Sensing Devices

## Recommended Devices

Specifications	Cost Optimized		OPAx188	OPAx182	OPAx189
	TLV07	TLV2186			
Vs min/max (V)	2.7 / 36	4.5 / 24	4 / 36	4.5 / 36	4.5 / 36
CMRR typ (dB)	120	134	146	168	168
GBW (MHz)	1	0.75	2	5	14
Slew Rate (V/ $\mu$ s)	0.4	0.35	0.8	10	20
Vos max @ 25C (mV)	0.1	0.25	0.025	0.004	0.005
Drift typ ( $\mu$ V/C)	0.9	0.1	0.03	0.003	0.007
Rail-to-Rail	Out	In, Out	In to V-, Out	Out	In to V-, Out
Iq typ (mA)	0.95	0.09	0.425	0.85	1.3
Vn (nV/ $\sqrt$ Hz)	19	38	8.8	5.7	5.2
IBias typ (pA)	40	100	160	50	70
Operating Temperature ( $^{\circ}$ C)	-40 to 125	-40 to 125	-40 to 125	-40 to 125	-40 to 125
Technology	-	Zero-drift	Zero-drift	Zero-drift	Zero-drift

<https://www.ti.com/amplifier-circuit/op-amps/precision/overview.html>

# Thank you for your time!


**Visit [ti.com](http://ti.com) for more BTS resources**

# Precision Amplifiers for Battery Test Systems


## *Control Loops*

Precision Amplifiers

# CC/CV Control Loops

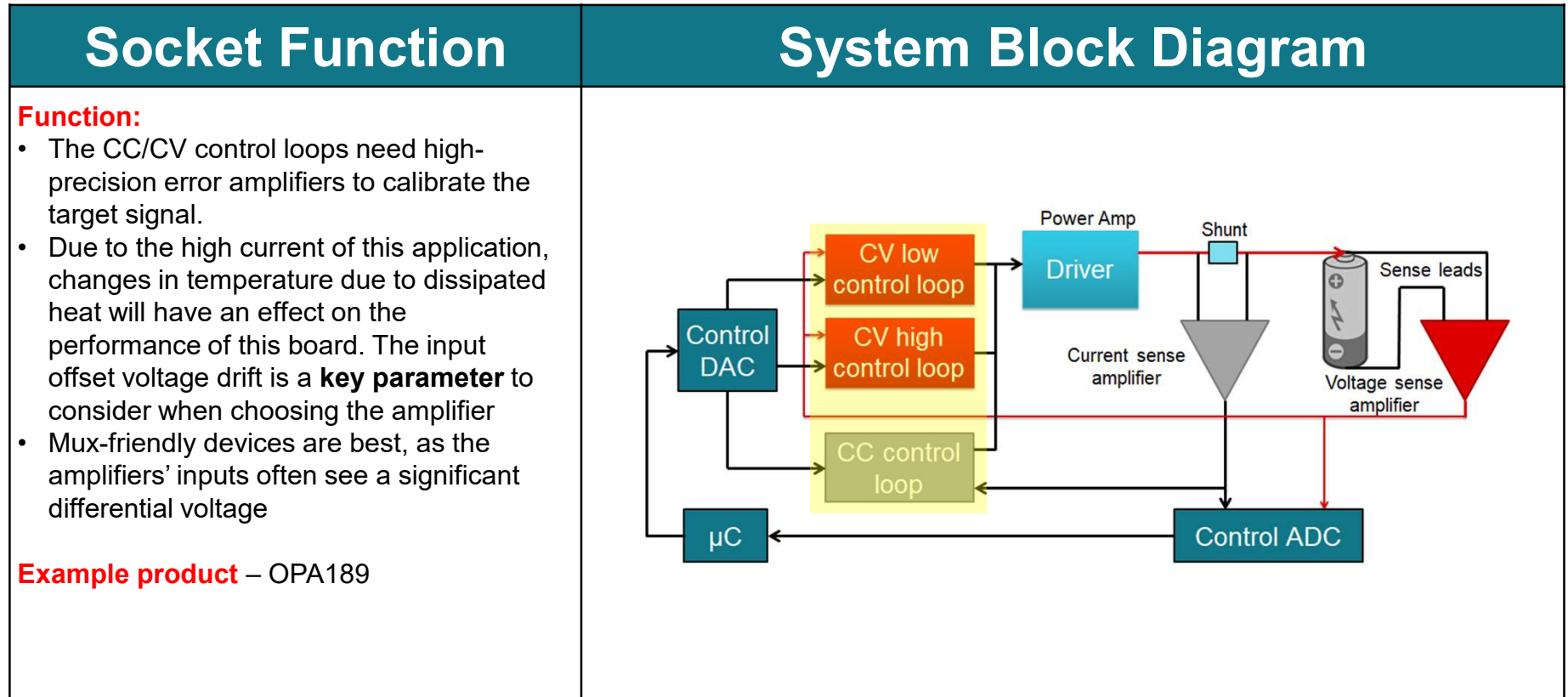


# Current Control Loop Example

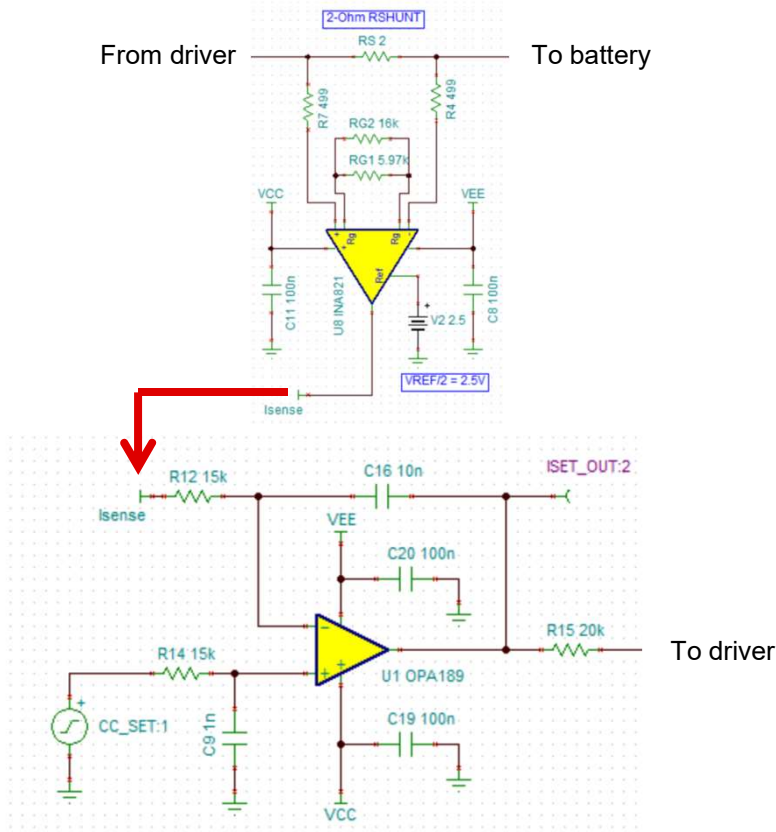

- Output of current sense amp feeds back to current error amplifier, which calibrates the ISET\_OUT output relative to the specified CC\_SET level from the DAC
- For  $CC\_SET < V_{REF/2}$ , the battery will **discharge down** to the threshold voltage.
- For  $CC\_SET > V_{REF/2}$ , the battery will **charge up** to the regulation voltage. The delta between  $CC\_SET$  and  $V_{REF/2}$  determines the drive current for charge or discharge.
- In example shown,  $CC\_SET$  ranges from 0V min to 5V max, and  $V_{REF/2} = 2.5V$

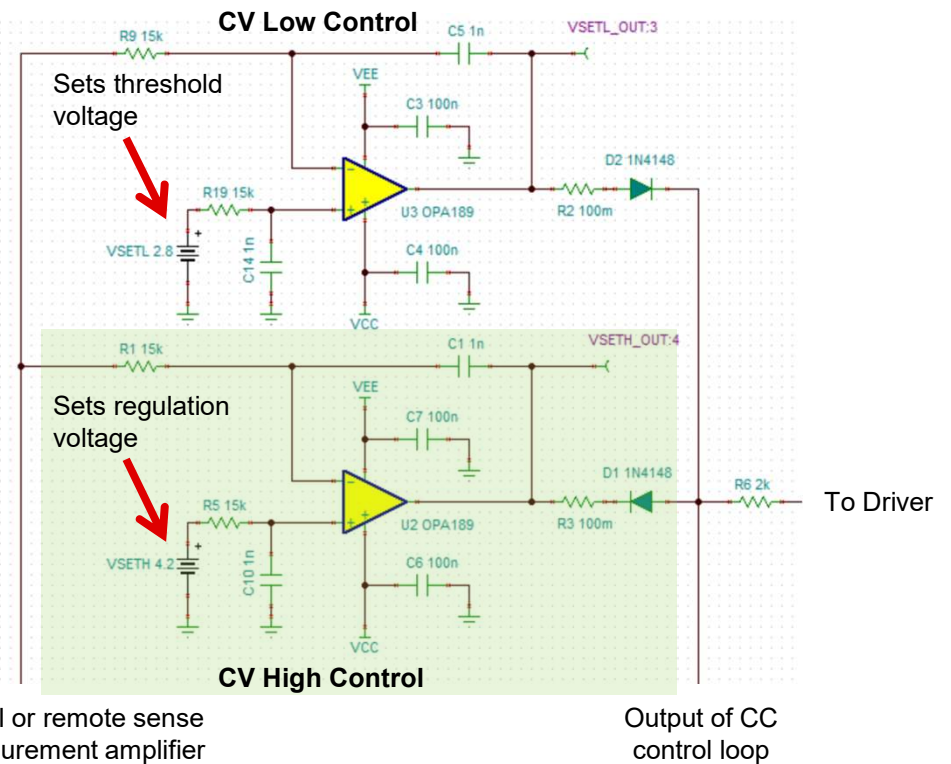
# $V_{battery}$ Upper Limit Detection in Control Loop

- To support both charge and discharge, both a **CV High** and **CV Low control** loop are needed.
- During charging, when battery voltage nears regulation voltage, **CV High** “turns on” to counter the CC loop.
- VSETH\_OUT falls to a diode drop below the desired battery voltage.
- VSETL\_OUT is low so D2 is off, and CV High overpowers the CC control loop amplifier to set the driver voltage


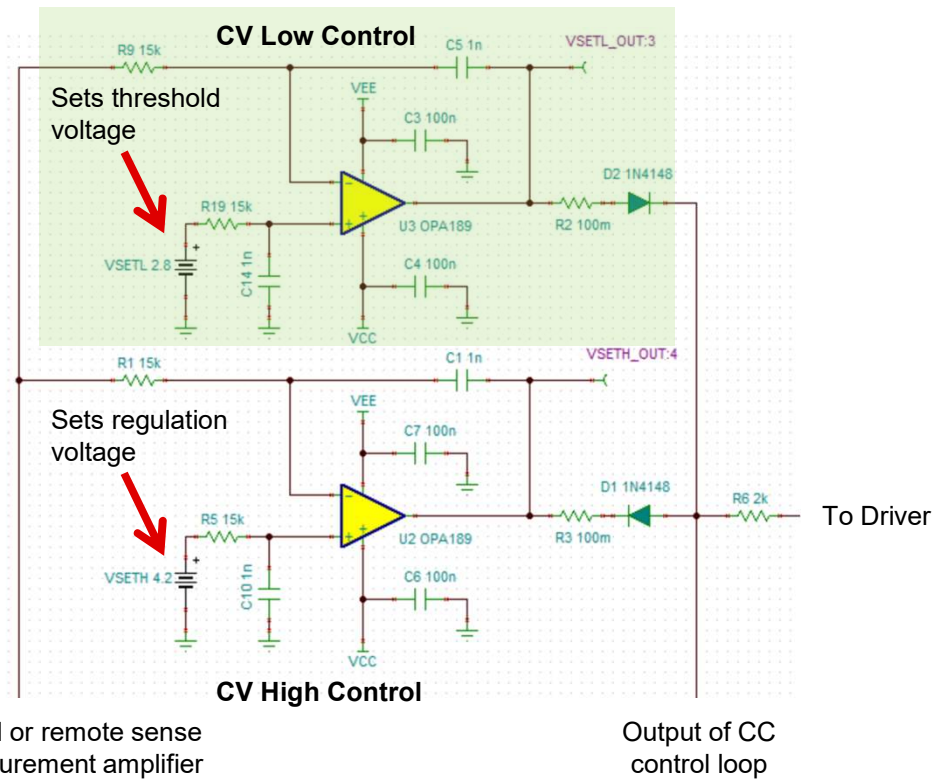
# $V_{battery}$ Lower Limit Detection in Control Loop

- When battery voltage nears the threshold voltage during discharge, **CV Low** activates to stop further discharge and hold battery voltage at threshold.
- VSETL\_OUT rises to a diode drop above the desired battery voltage.
- VSETH\_OUT is railed to VCC so D1 is off, and CV Low overpowers the CC control loop to set the driver voltage



# Precision Control Loop Devices

## Recommended Devices

Specifications	Mux-Friendly				
	Lowest system cost	e-Trim™ Low Cost	e-Trim™ Higher Performance	Zero-Drift Widest Bandwidth	
	TLV07	TLV2186	OPAx197	OPAx192	OPAx189
Vs min (V)	2.7	4.5	4.5	4.5	4.5
Vs max (V)	36	24	36	36	36
GBW (MHz)	1	0.75	10	10	14
Slew Rate (V/μs)	0.4	0.35	20	20	20
Vos max @ 25C (mV)	0.1	0.25	0.1	0.025	0.005
Drift typ (μV/C)	0.9	0.1	0.5	0.15	0.007
Rail-to-Rail	Out	In, Out	In, Out	In, Out	In to V-, Out
Iq typ (mA)	0.95	0.09	1	1	1.3
Vn (nV/√Hz)	19	38	5.5	5.5	5.2
IBias (Typ) (pA)	40	100	5	5	70
Operating Temperature (°C)	-40 to 125	-40 to 125	-40 to 125	-40 to 125	-40 to 125

<https://www.ti.com/amplifier-circuit/op-amps/precision/overview.html>



# Thank you for your time!


Visit [ti.com](http://ti.com) for more BTS resources

# Precision Amplifiers for Battery Test Systems

## *Drivers and Buffers*

Precision Amplifiers

# Power Amp Driver (Optional - Design Dependent)

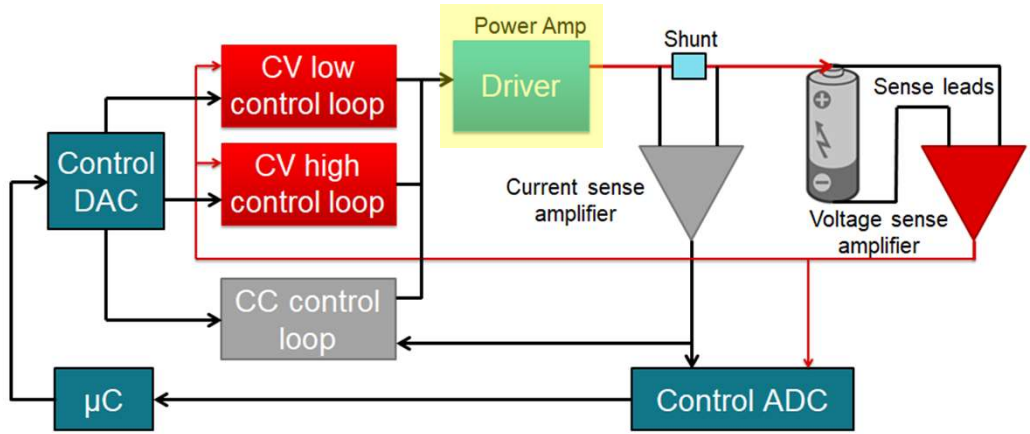Socket Function	System Block Diagram
<p><b>Function</b> – The driver should be chosen based on the current needs of the application and the supply voltages available. The supplies are often set much higher than the maximum battery voltage – this added headroom may be necessary to force a given current value</p> <ul style="list-style-type: none"><li>• Consider the thermal dissipation of the device when designing a high-current BTS system. Designing beyond 1A can be quite difficult due to self-heating</li><li>• Consider selecting a device with built-in current limiting features</li></ul> <p><b>Example product</b> – ALM2402F</p>	 <p>The diagram illustrates the system architecture for a power amp driver. A microcontroller (μC) is connected to a Control DAC and a Control ADC. The Control DAC outputs signals to three control loops: CV low control loop, CV high control loop, and CC control loop. The CV loops and the CC control loop are connected to a Driver block, which is part of a Power Amp. The Driver outputs current through a Shunt resistor. A Current sense amplifier is connected to the shunt to measure the current. The shunt also provides a voltage drop that is sensed by a Voltage sense amplifier. The Voltage sense amplifier is connected to a battery and sense leads. The Control ADC receives feedback signals from the Current sense amplifier and the Voltage sense amplifier, and sends data back to the μC.</p>

# Precision Power Amp Devices

## Recommended Devices

Smallest Package  
Lowest system cost

Highest Output Current Drive

Specifications	TLV4110/1	TLV4112/3	ALM2402F-Q1	OPA564
Num Channels	1	1	2	1
Vs min (V)	2.5	2.5	4.5	7
Vs max (V)	6	6	16	24
Output Current Drive (mA)	320	320	400	1500
Operating Temperature (°C)	-40 to 125	-40 to 125	-40 to 125	-40 to 85
Additional Features	Shutdown Pin	Shutdown Pin	Protection Features	Protection Features

<https://www.ti.com/amplifier-circuit/op-amps/power/overview.html>

# DAC Op Amp Buffer (Optional - Design Dependent)


## Socket Function

**Function** – Precision amps may be used to **buffer/gain up the DAC** control outputs to change the output range of the DAC and set the reference voltage

- This is design dependent – if DAC outputs look into **high impedance inputs** of control amplifiers, buffers not likely necessary. However, some DACs such as **current output DACs** may require buffering
- The  $V_{REF/2}$  current sense reference voltage may be achieved locally by using a precision device to buffer a high-tolerance voltage divider between the DAC supplies

**Example product** – OPA188

## System Block Diagram

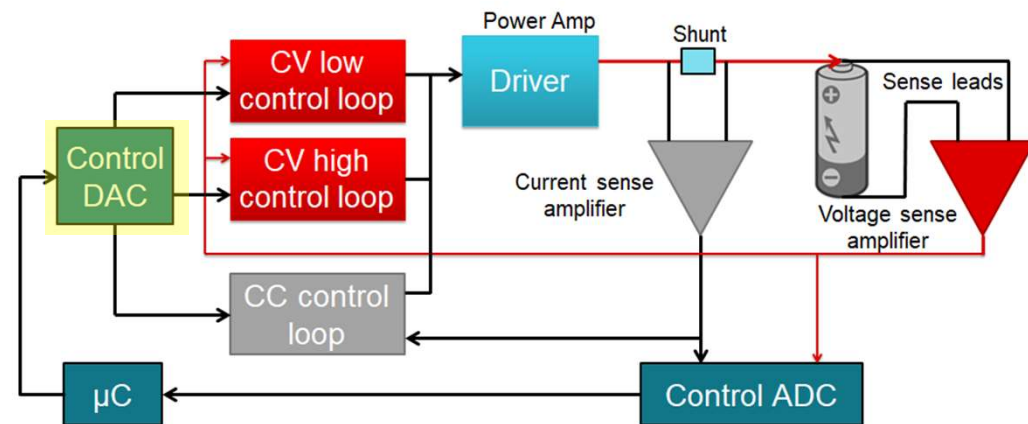

# Precision Buffer Devices

## Recommended Devices

Specifications	CMOS, e-Trim™		Bipolar, Super-beta		Zero-drift
	Low Cost	Higher Performance	Lowest power	Lowest noise, wide BW	Lowest offset & drift
	OPAx197	OPAx192	OPAx205	OPAx210	OPAx189
Vs min (V)	4.5	4.5	4.5	4.5	4.5
Vs max (V)	36	36	36	36	36
GBW (MHz)	10	10	3.6	18	14
Slew Rate (V/μs)	20	20	4	6.4	20
Vos max @ 25C (mV)	0.1	0.025	0.025	0.035	0.005
Drift typ (μV/C)	0.5	0.15	0.1	0.5	0.007
Rail-to-Rail	In, Out	In, Out	Out	Out	In to V-, Out
Iq typ (mA)	1	1	0.22	2.2	1.3
Vn (nV/√Hz)	5.5	5.5	7.2	2.2	5.2
IBias (Typ) (pA)	5	5	200	300	70
Operating Temperature (°C)	-40 to 125	-40 to 125	-40 to 125	-40 to 125	-40 to 125

<https://www.ti.com/amplifier-circuit/op-amps/precision/overview.html>

# Thank you for your time!

**Visit [ti.com](http://ti.com) for more BTS resources**


# Precision Amplifiers for Battery Test Systems

## *Simulation and Results*

Precision Amplifiers



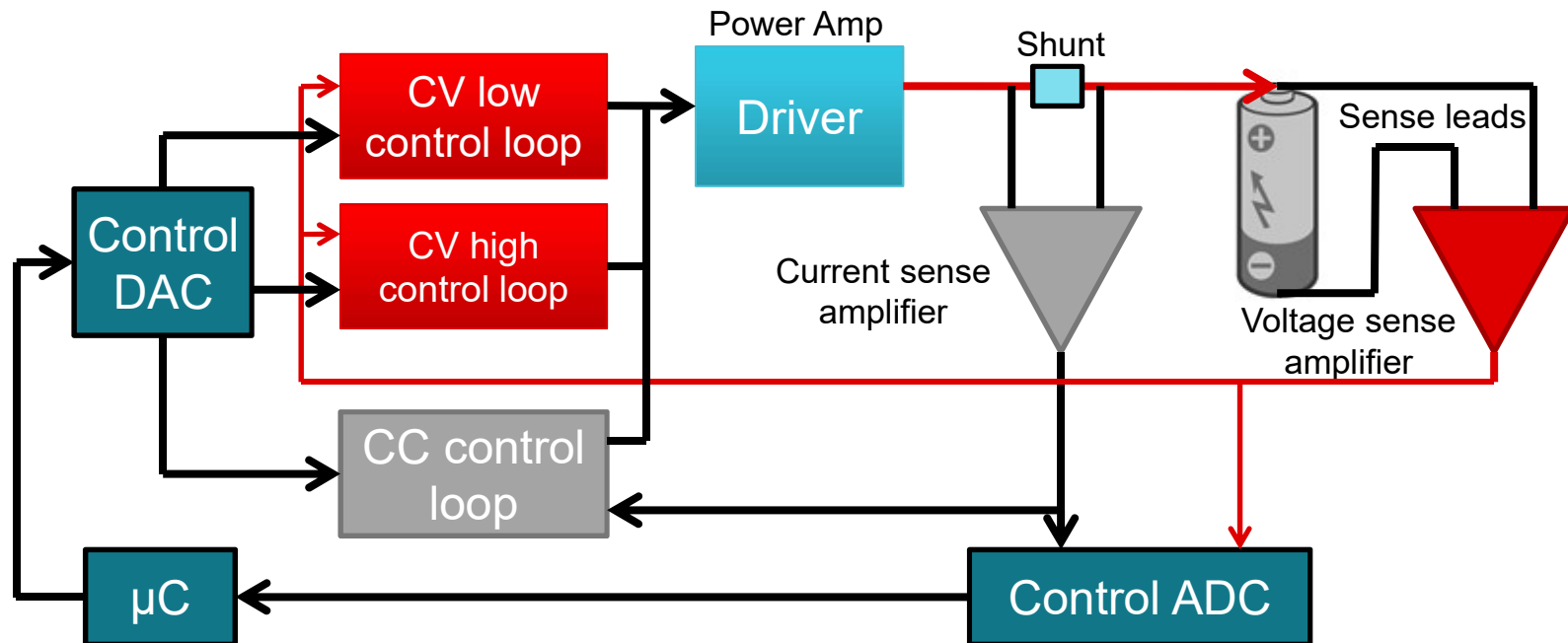
# Power Amp Charging/Discharging System Overview



# Exam


CV cont

CC con

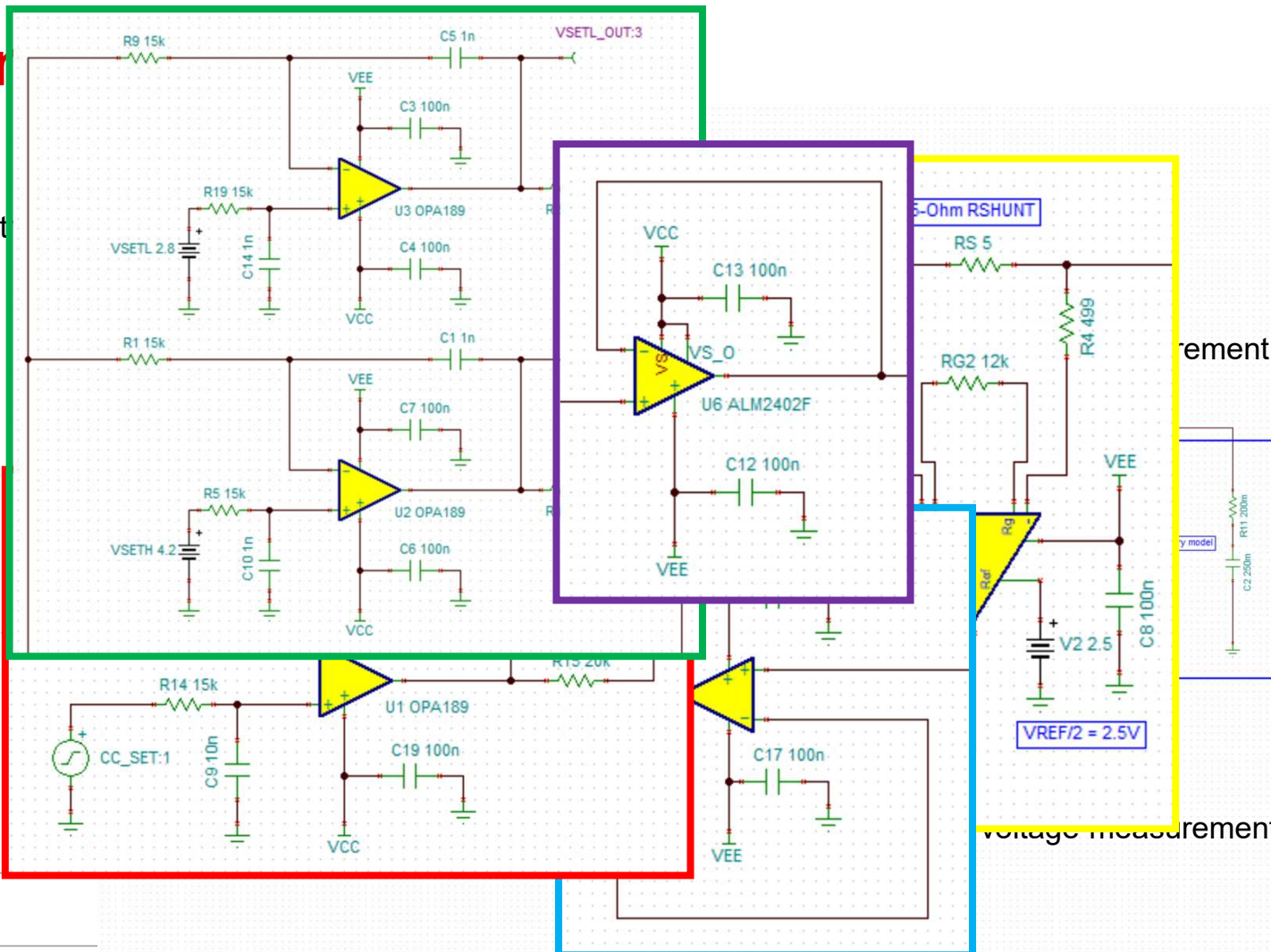


INSTRUMENTS




# Example Simulation

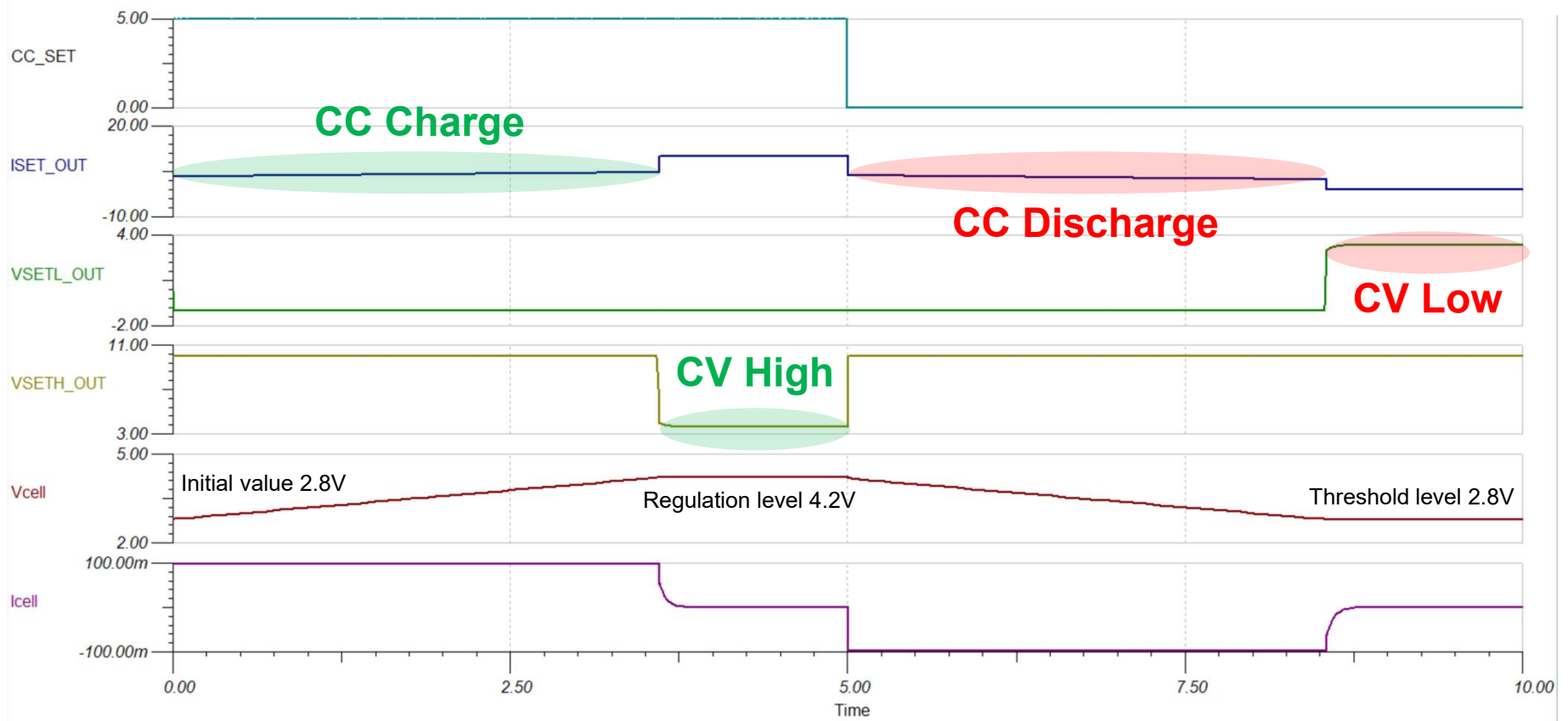

# Hardware Solution

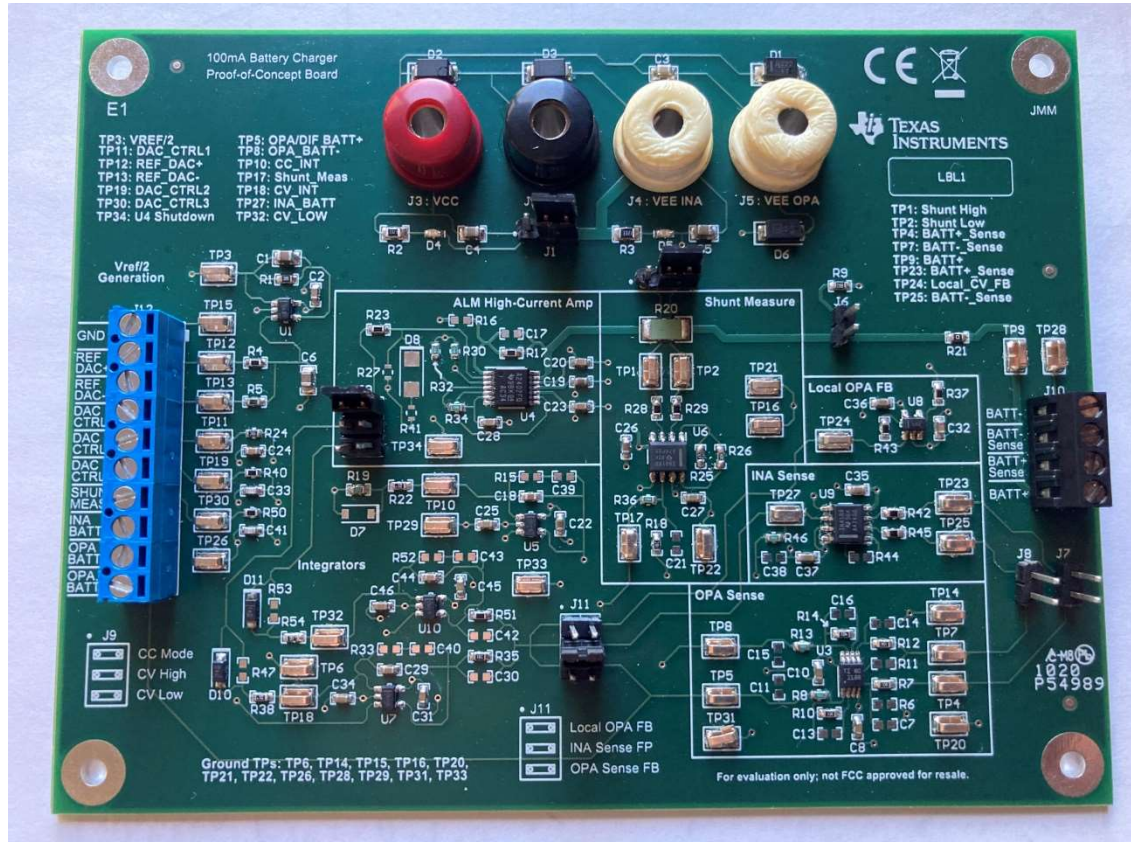



# CC and CV Control Precision

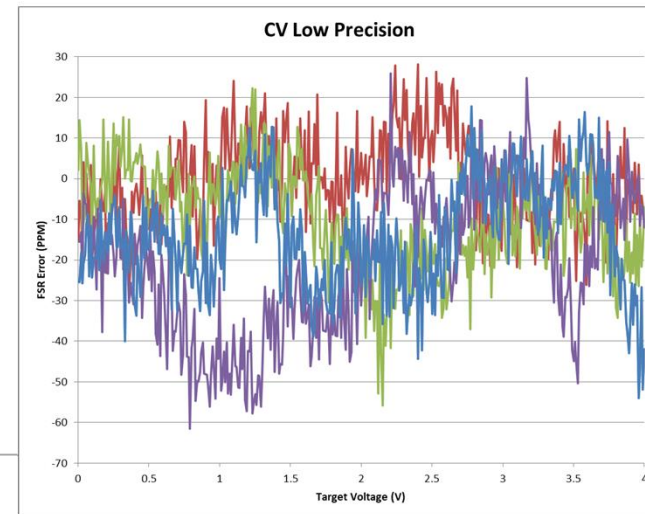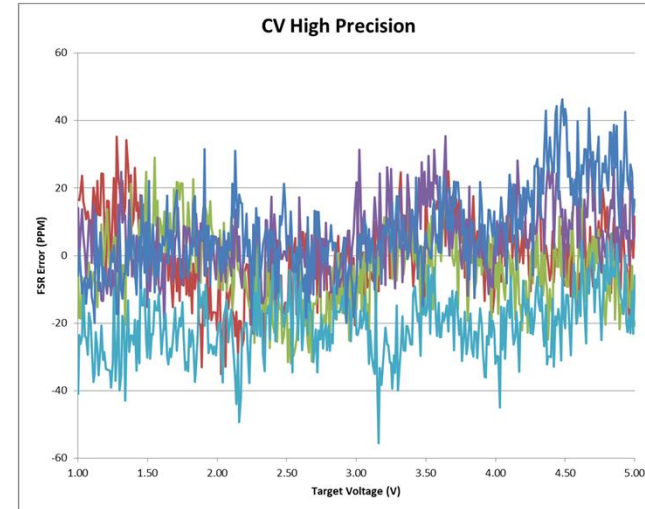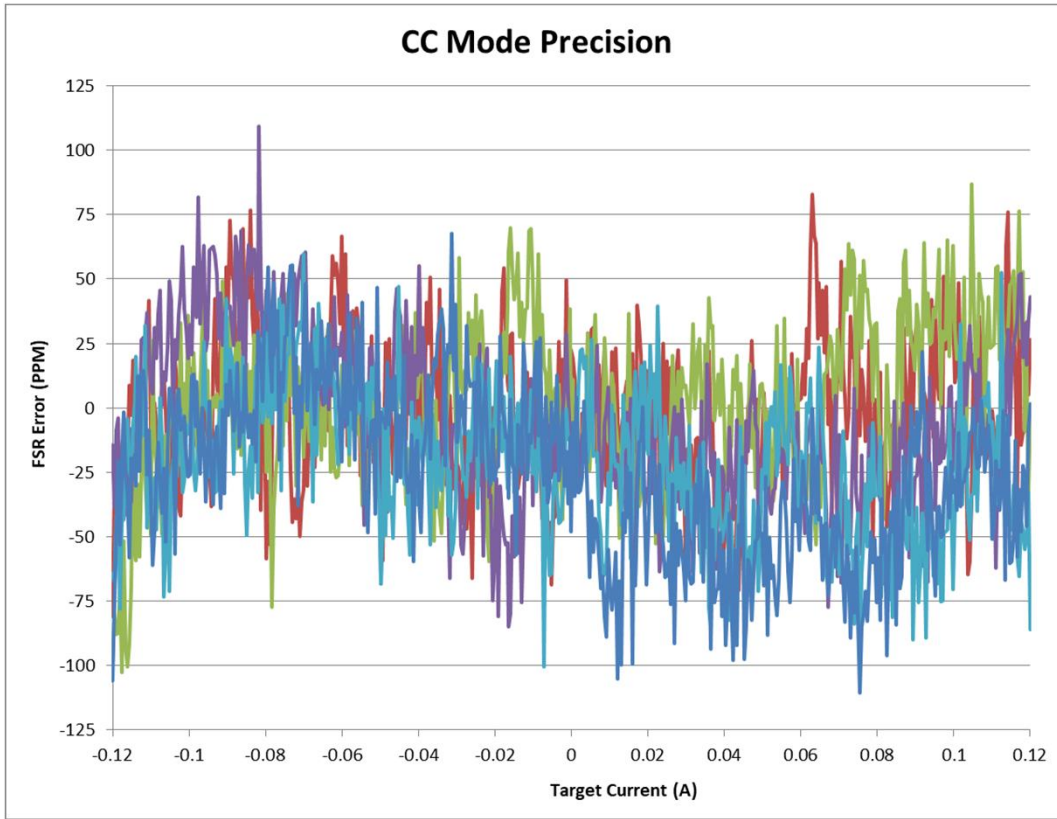

- Run 1
- Run 2
- Run 3
- Run 4
- Run 5

MENTS

# CC Precision vs Battery Voltage

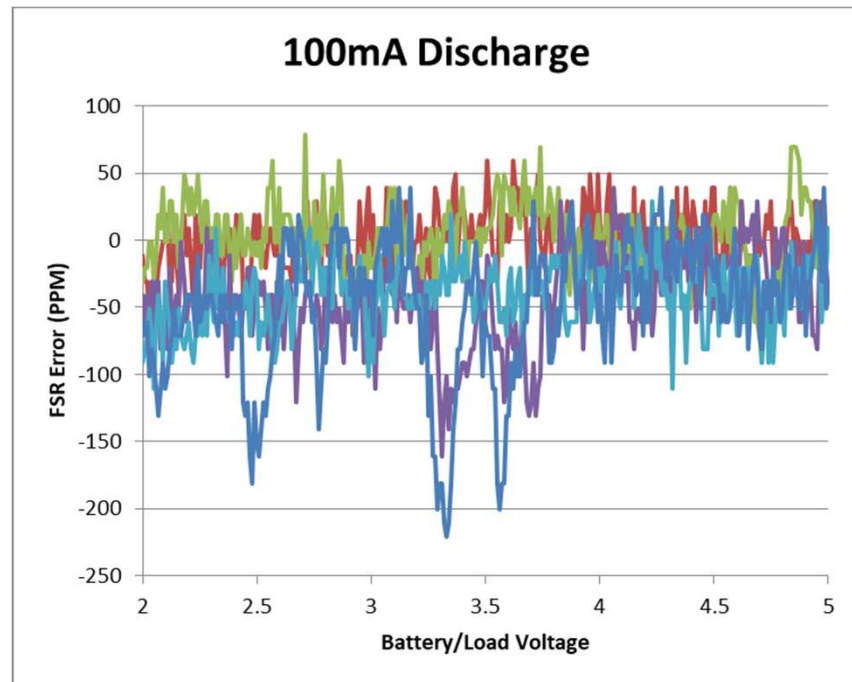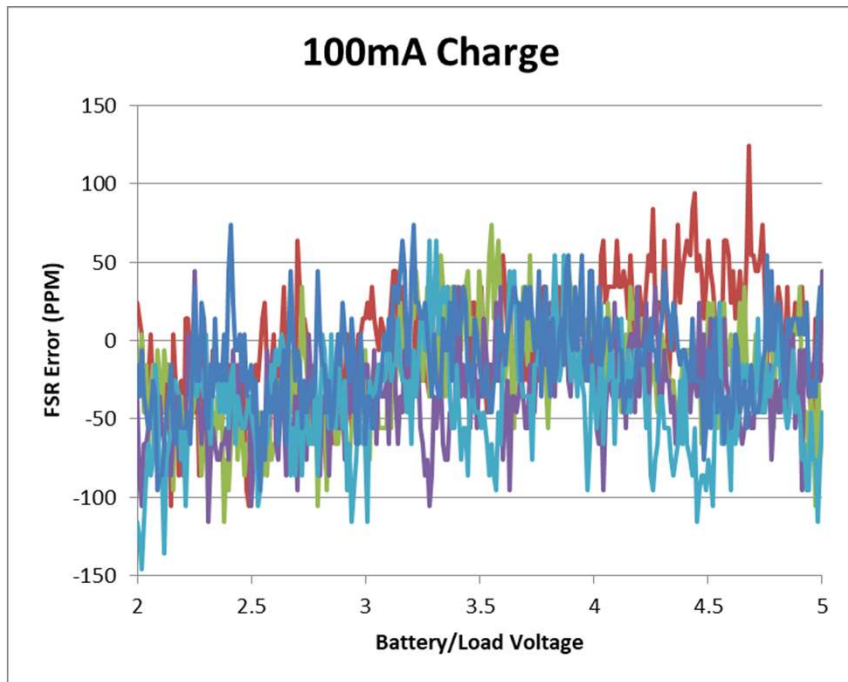

- Run 1
- Run 2
- Run 3
- Run 4
- Run 5

# Thank you for your time!

**Visit [ti.com](http://ti.com) for more BTS resources**