
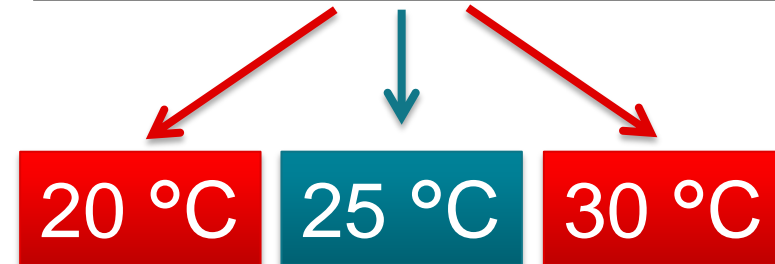
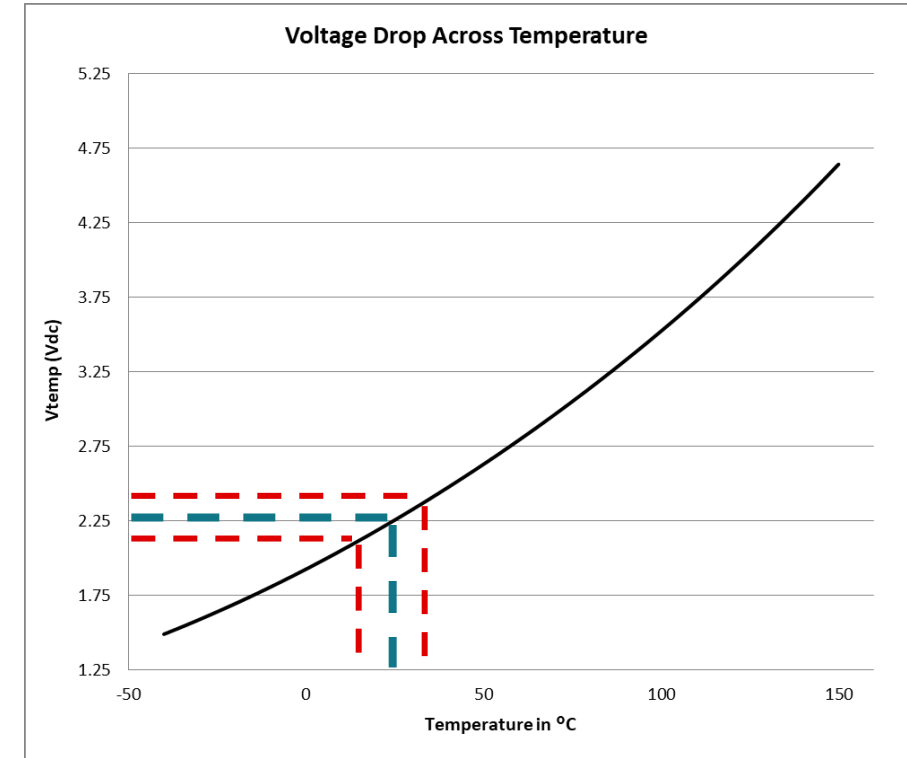
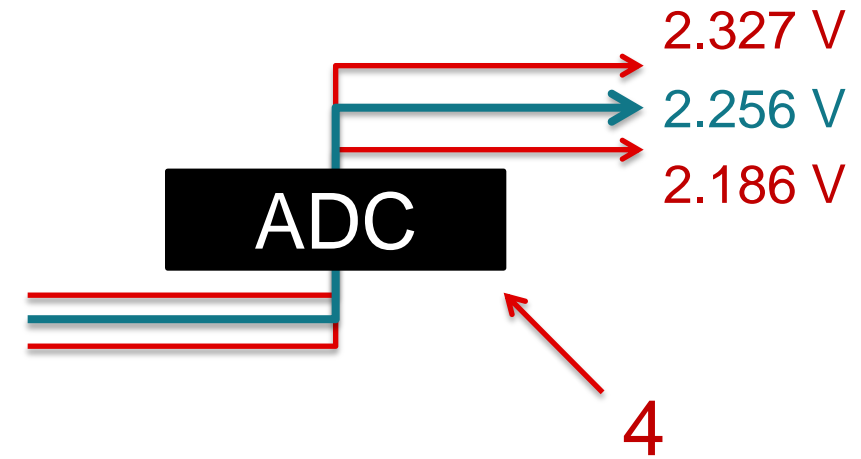


Optimizing thermistor designs for temperature sensing

TI Precision Labs – Thermistors

Presented and prepared by Bryan Padilla

Sources of error

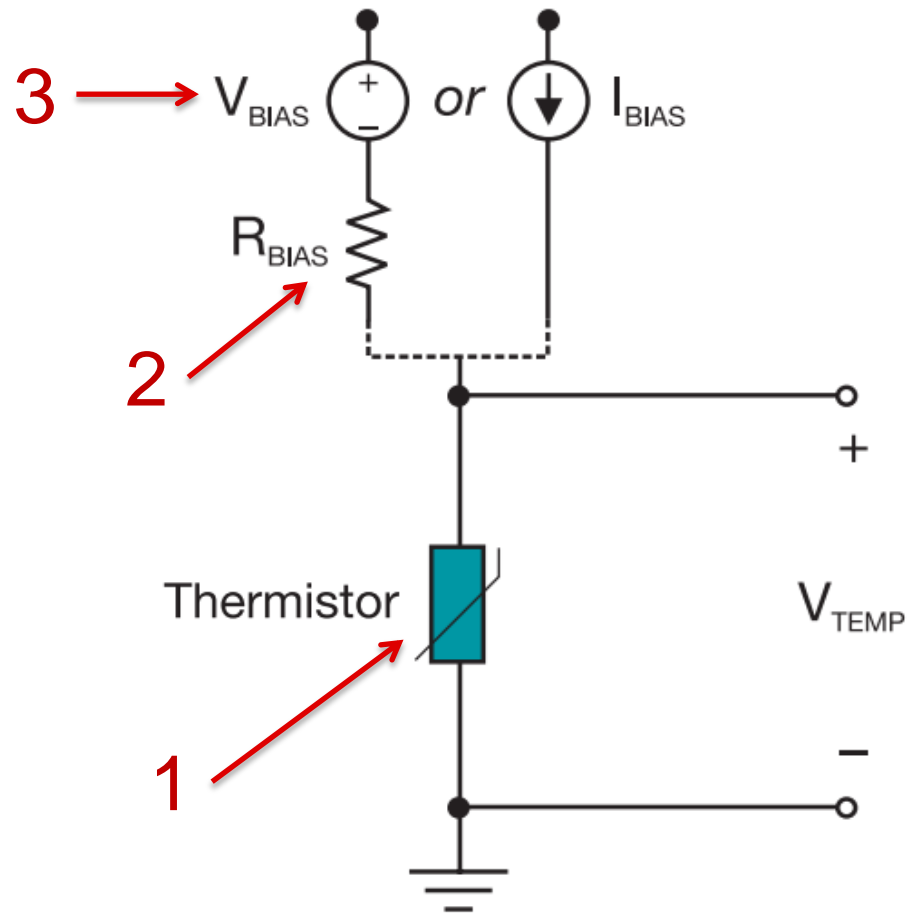

Why accuracy matters

Accuracy ↓


Margin of error ↑

Performance ↓

Accuracy ↑

Margin of error ↓


Performance ↑

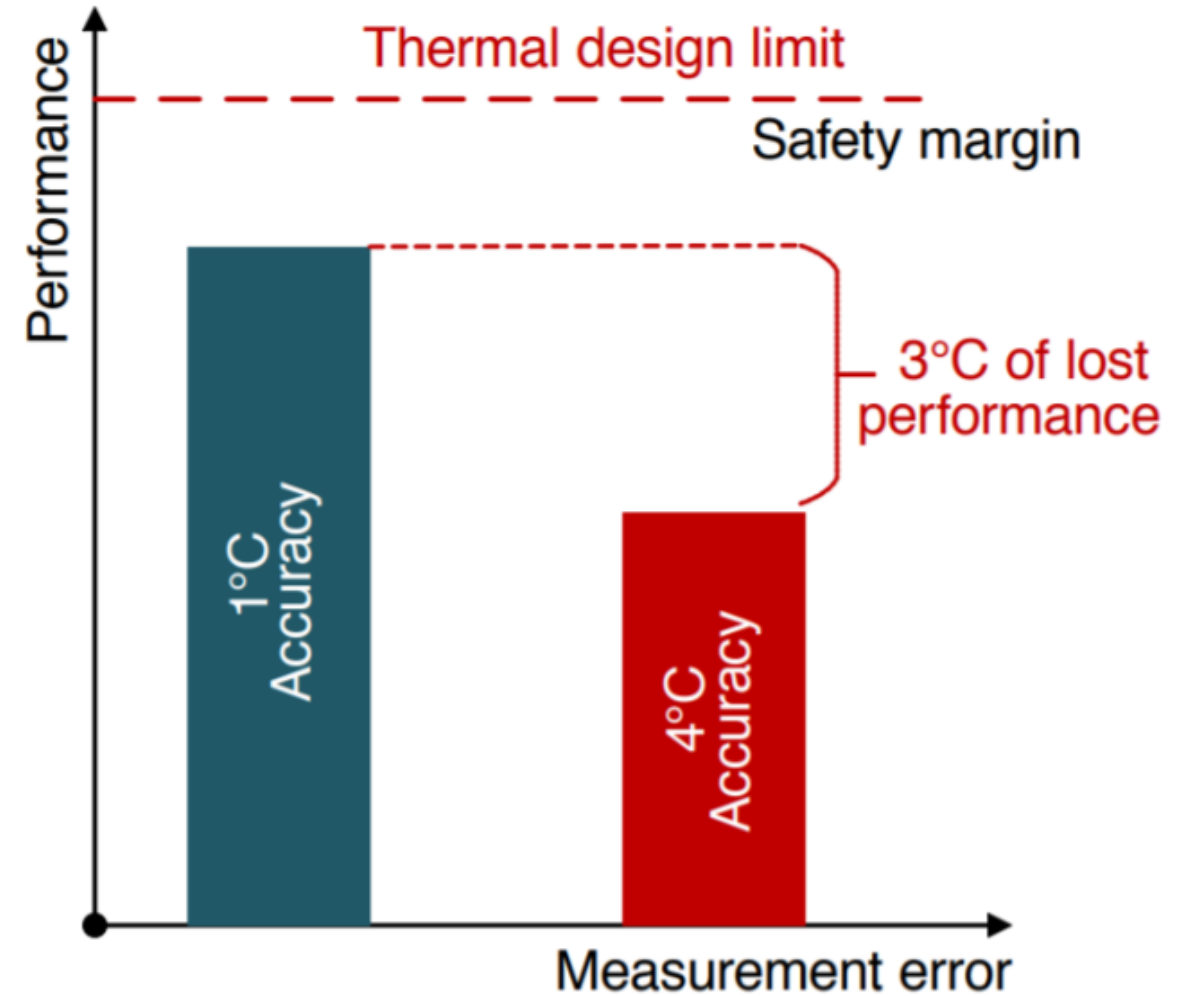

Methods to reduce error

1. Use precise components

Component	Recommendations
Thermistor	$R_{tol} \leq 1\%$, $Drift \leq 1\%$
Bias resistor	$R_{tol} \leq 0.5\%$, $TC \leq 25$ PPM
Voltage bias	V_o accuracy $\leq 0.5\%$, TC : Low PPM

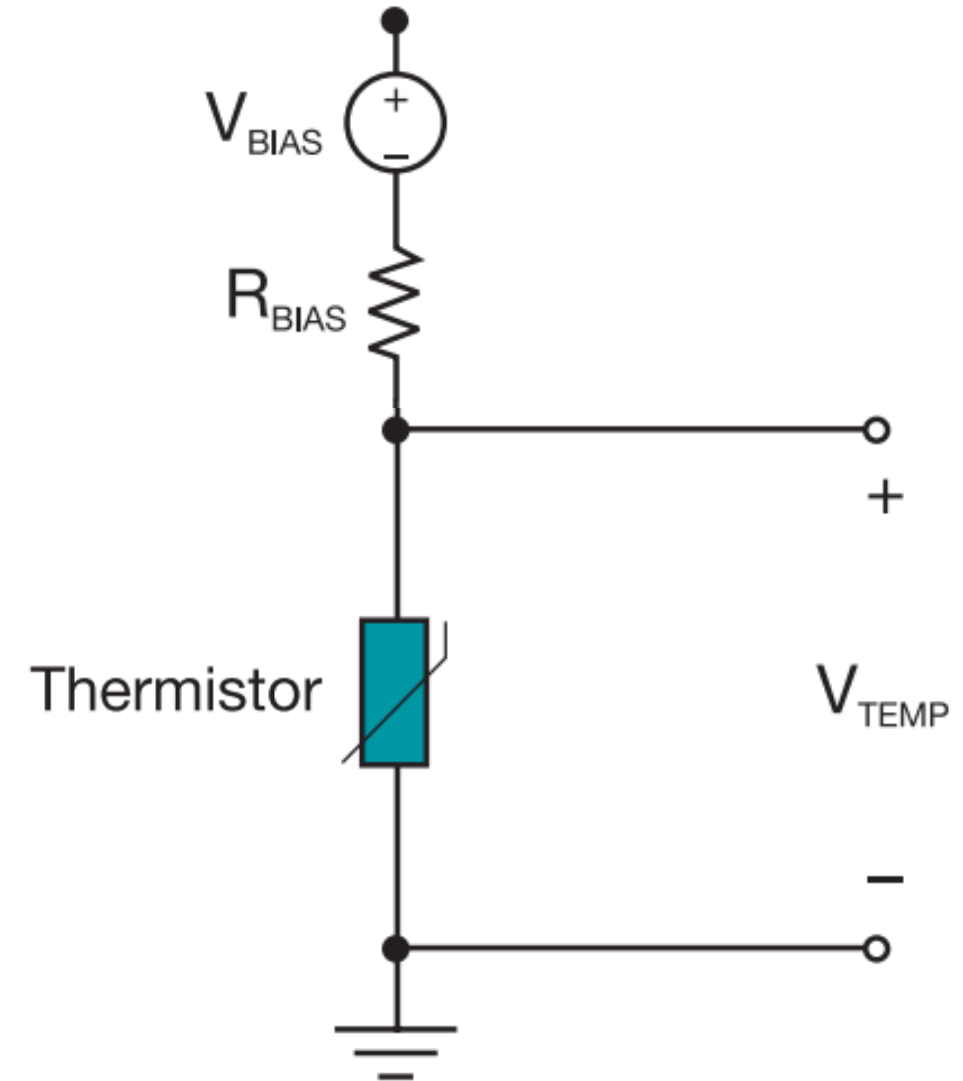


Methods to reduce error

1. Use precise components
2. Use a current source


Component	Recommendations
Thermistor	$R_{tol} \leq 1\%$, $Drift \leq 1\%$
Bias resistor	$R_{tol} \leq 0.5\%$, $TC \leq 25$ PPM
Voltage bias	V_o accuracy $\leq 0.5\%$, TC: Low PPM
Current bias	I_o accuracy $\leq 0.2\%$, TC: Low PPM

Eliminated

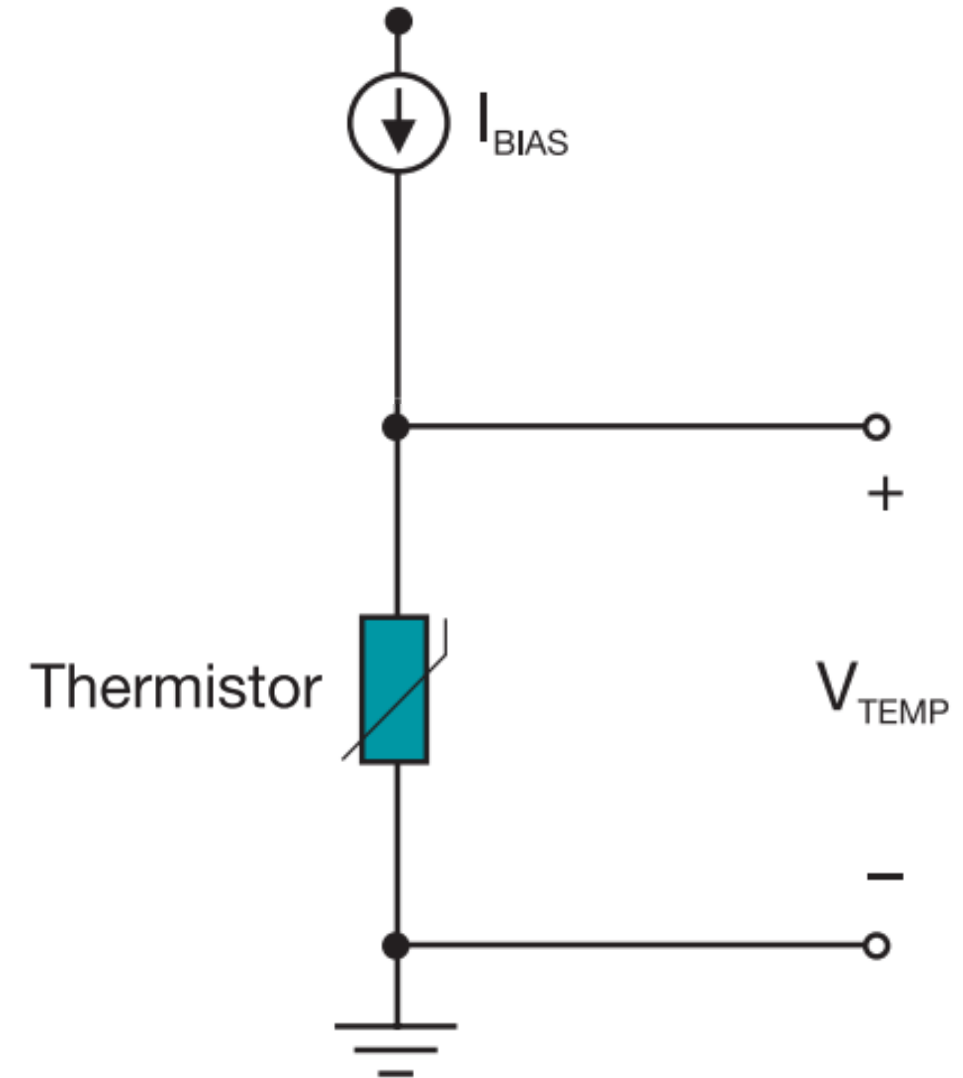

Methods to reduce error


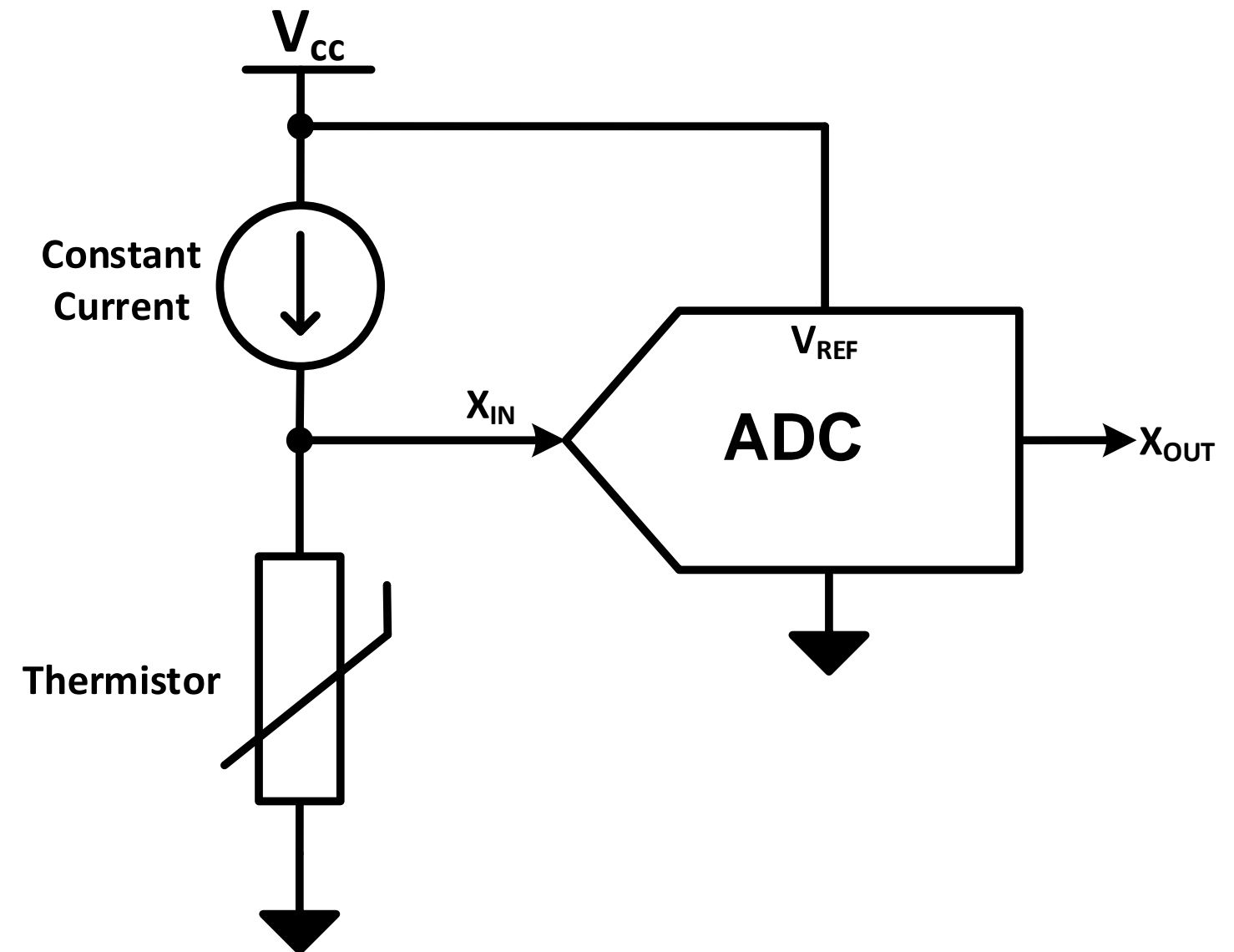
1. Use precise components
2. Use a current source
3. Use ratiometricity



For more information, check out video 2.5

Methods to reduce error

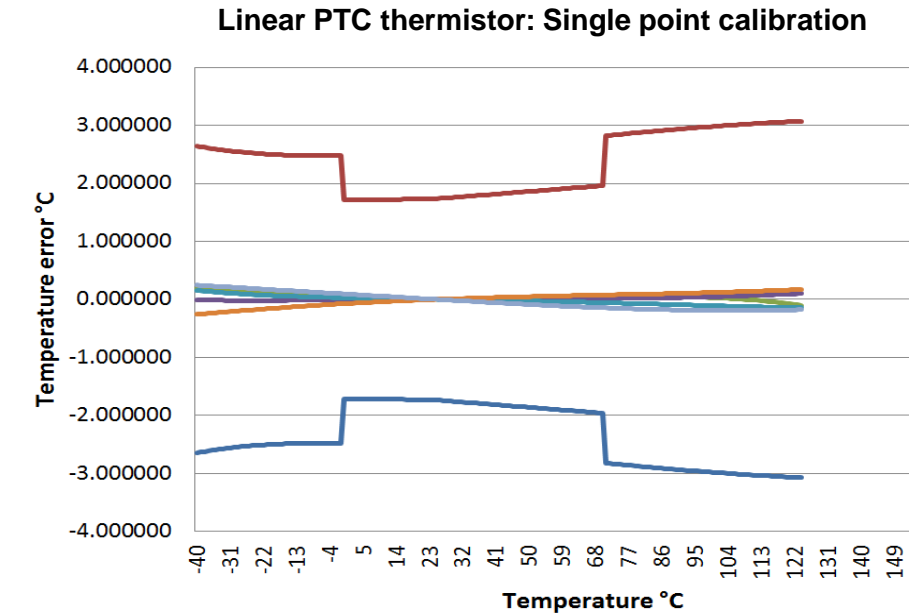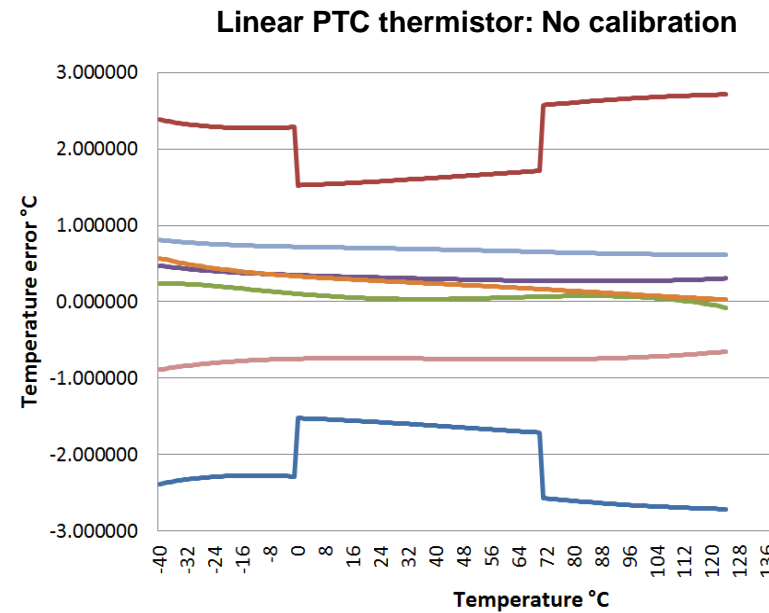1. Use precise components
2. Use a current source
3. Use ratiometricity
4. Calibrate/offset your thermistor



NTC: Multi-point calibration (requires temperature chamber)



Linear PTC: Single point offset correction at room temp (no chamber)

For more information, check out video 3.1

Single-point offset correction

TMP117
= 25 °C

← External temperature reference

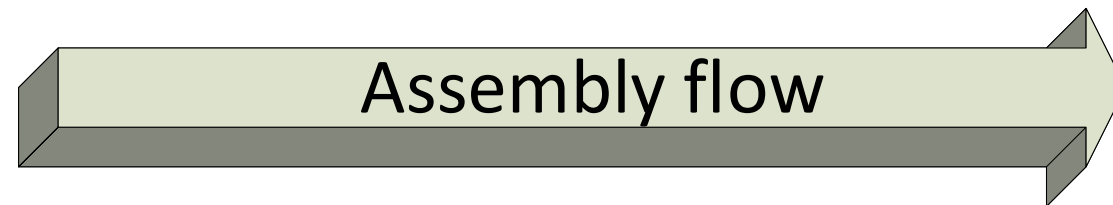
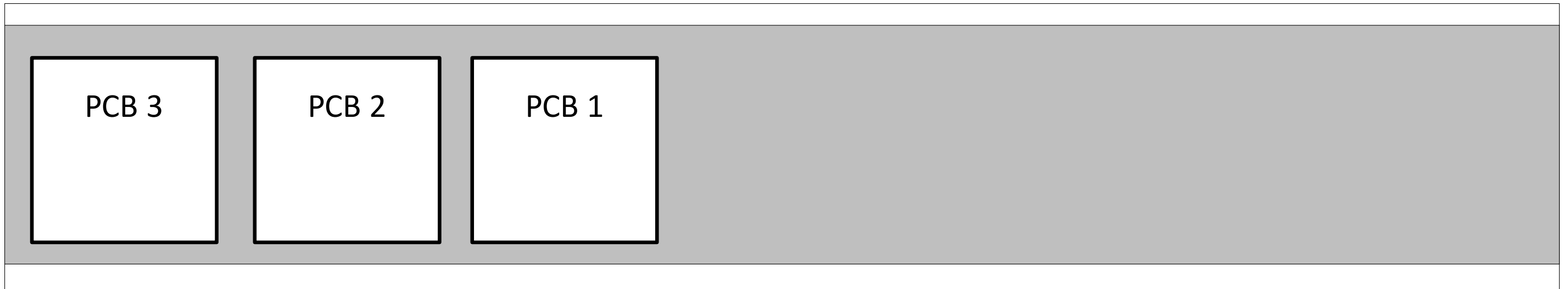


Single-point offset correction

Unit under test

TMP117
= 25 °C

External temperature reference

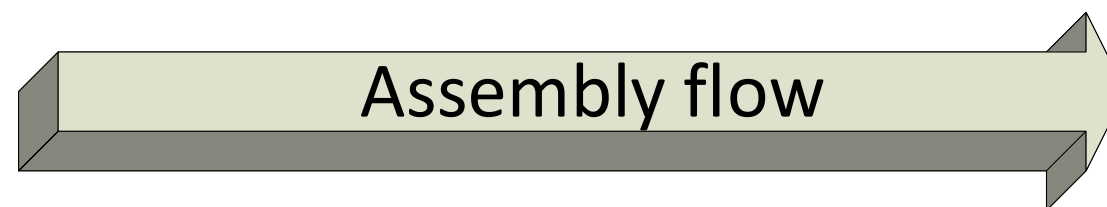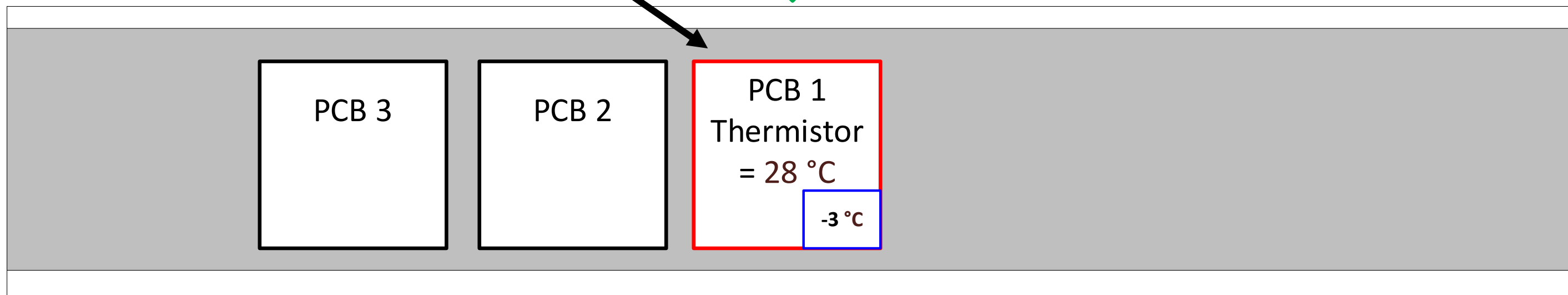



$$25 - 28 = -3$$

Single-point offset correction

Unit under test

TMP117
= 25 °C

External temperature reference

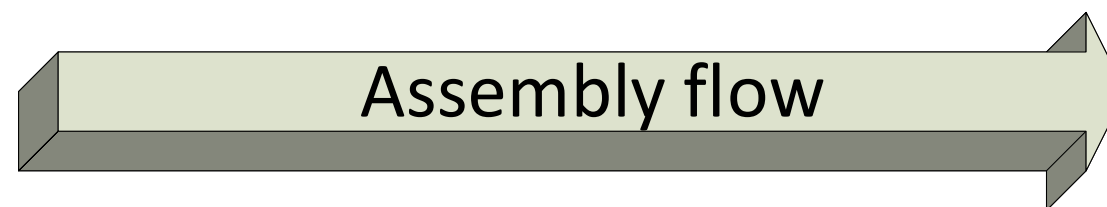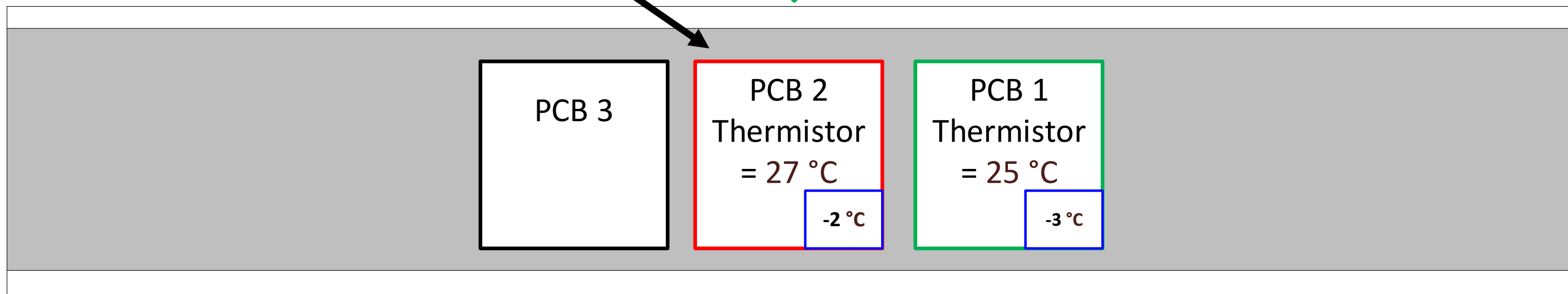



$$25 - 27 = -2$$

Single-point offset correction

Unit under test

TMP117
= 25 °C

External temperature reference

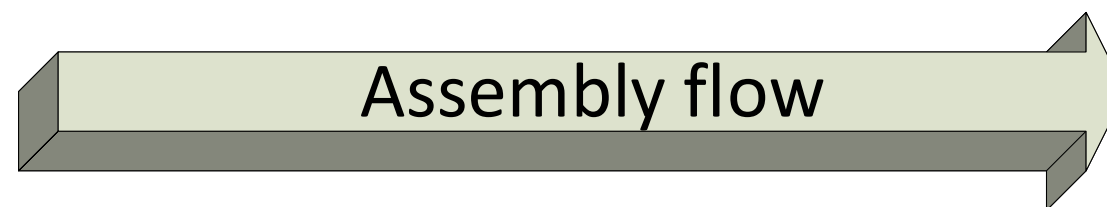
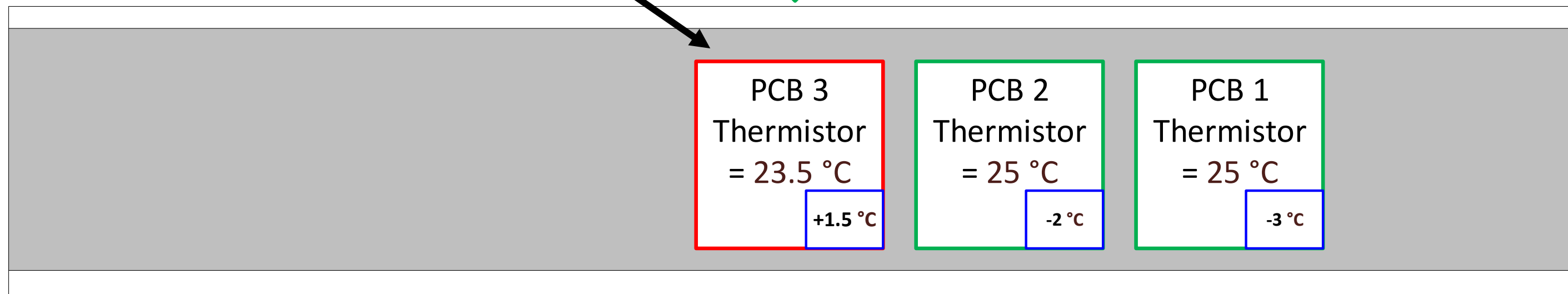


$$25 - 23.5 = +1.5$$

Single-point offset correction

TMP117
= 25 °C

← External temperature reference

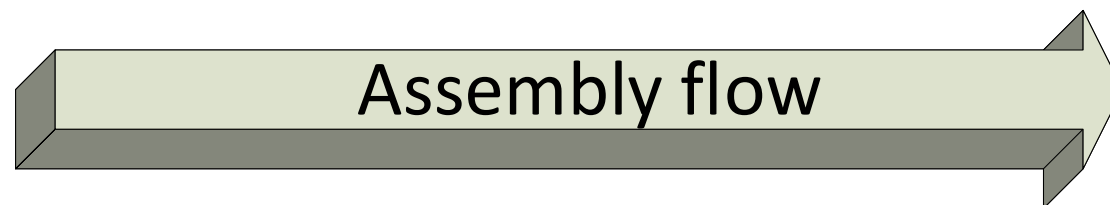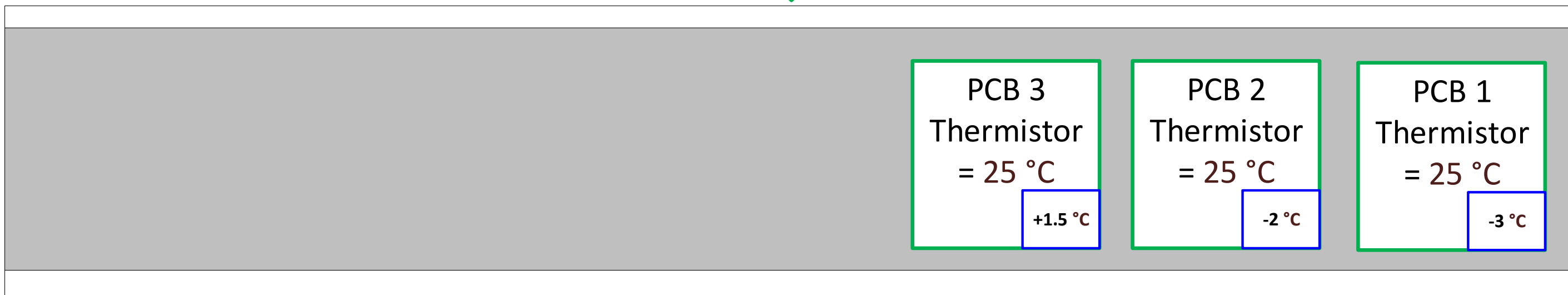

Oversampling



Improves resolution and SNR

# of samples	Bit resolution
4	+1
8	+2
16	+4

Ex:

10 bit ADC + 16x oversample = 14 effective bits of resolution

Cannot be used in a ratiometric circuit

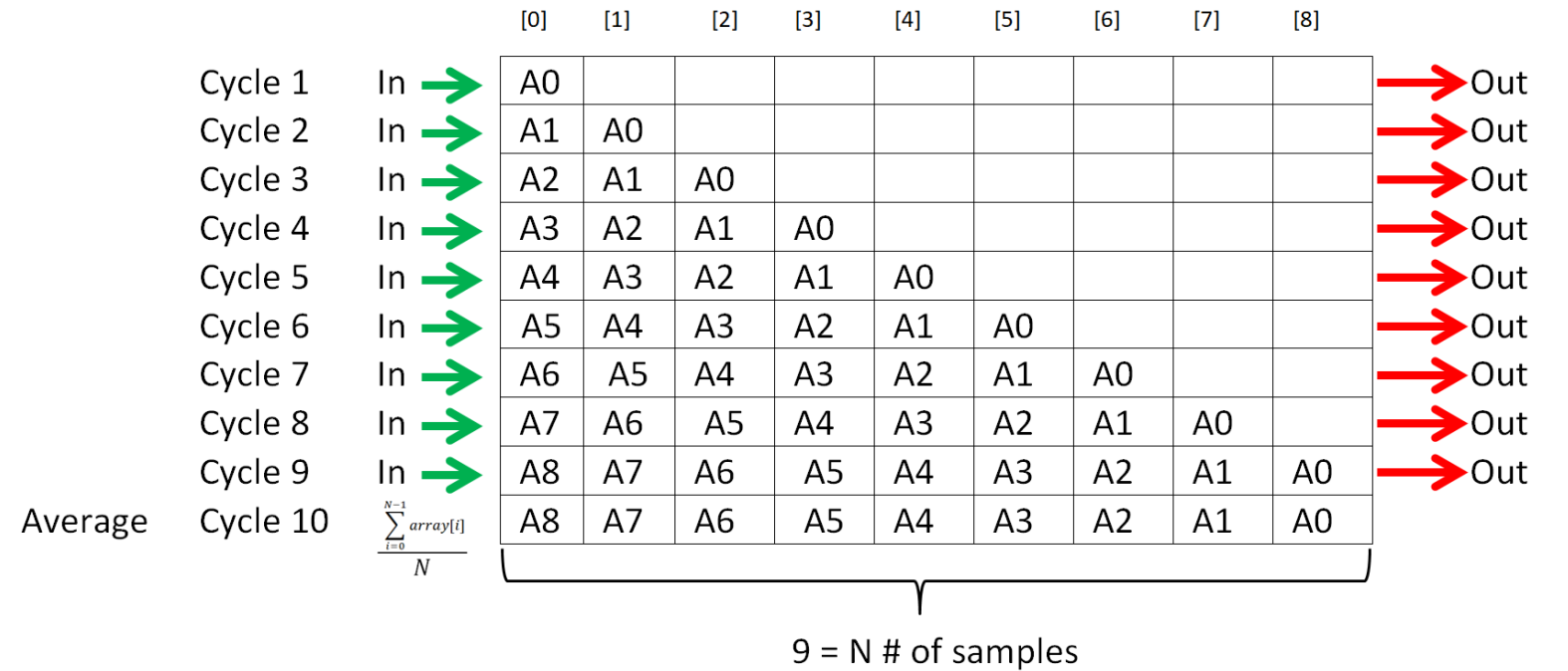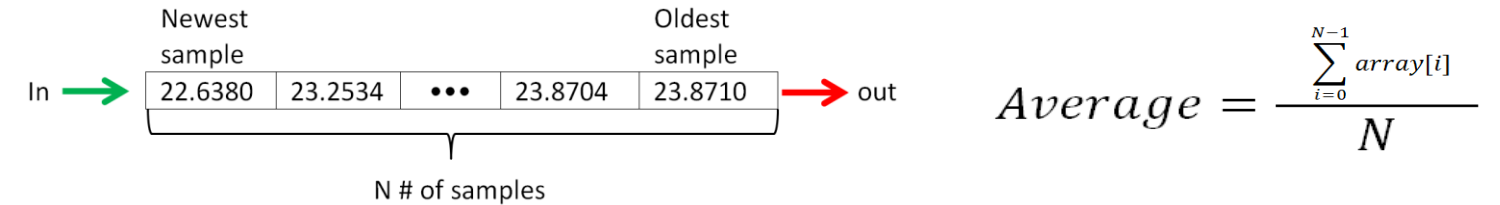


Oversampling

$$\frac{3.3V_{dc}}{2^{10}} = 0.0032V_{dc}$$

$$0.0032V_{dc} * 4 = 0.0128V_{dc}$$

$$\pm 0.0128V_{dc} = \mathbf{0.0256 V_{dc} (p2p)}$$

Recommended dithering noise

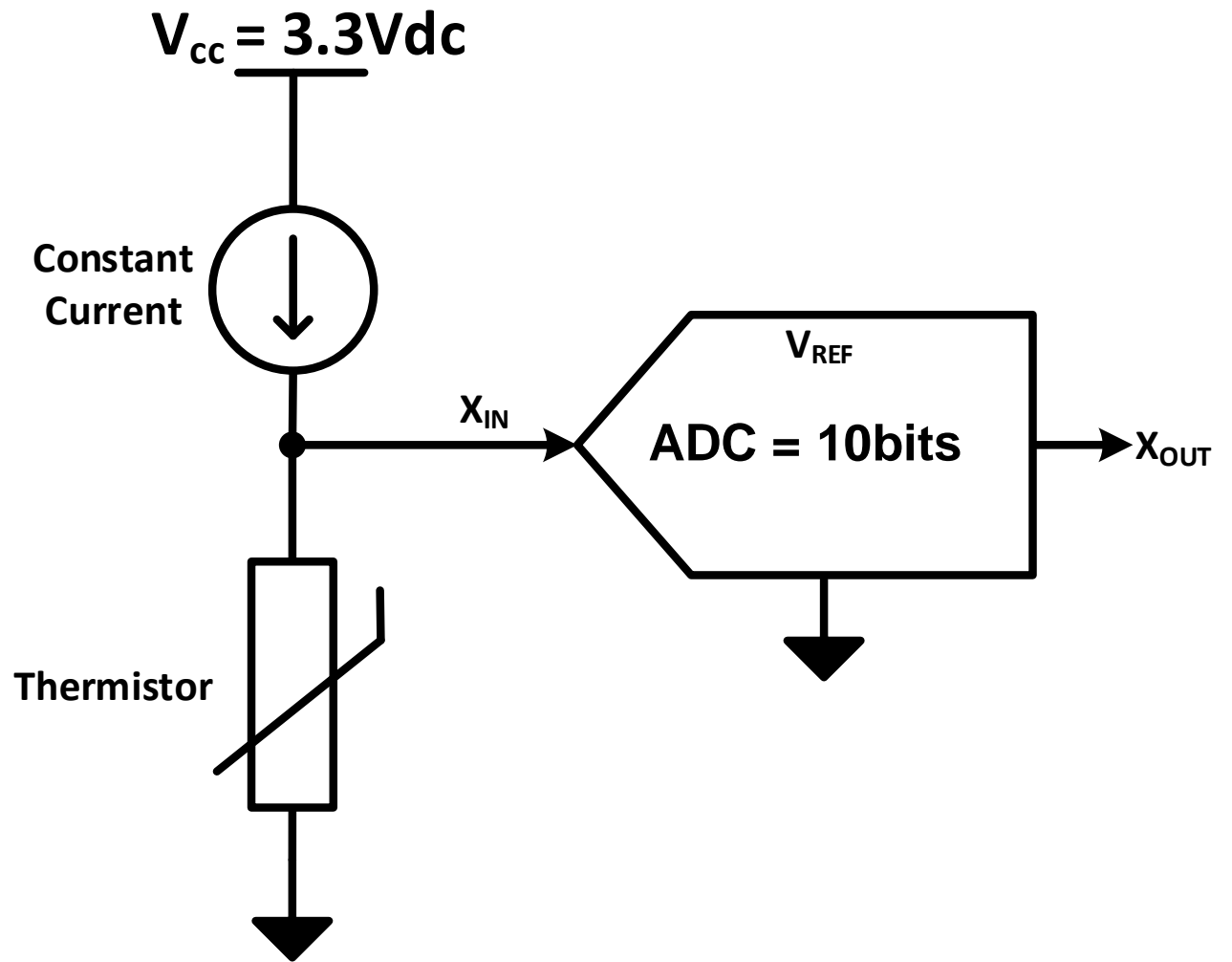

Summary

1. **Thermistor based solutions are discrete**
Accuracy is dependent on component tolerances
2. **Source variances**
(Can cause error if not referenced in ADC)
3. **Component tolerance and sensitivity errors**
4. **Poor ADC bit resolution**



1. **Use precise components & minimize BOM**
(Thermistor, resistors, voltage/current source)
2. **Implement ratiometricity**
(Can increase total accuracies in a system)
3. **Calibrate your thermistor to get high accuracy**
4. **Oversample in software**
(Improves resolution and SNR, cannot be done if implementing ratiometricity)

Thank you!

**To find more thermistor resources and products
visit [ti.com/thermistors](https://www.ti.com/thermistors)**