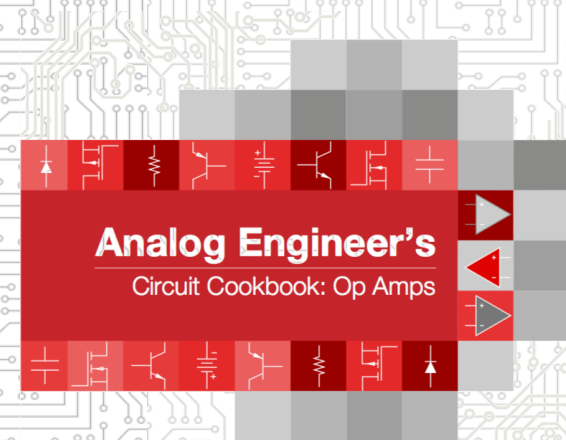


# How to Design Inverting Amplifier with T-Network Feedback Circuit


General Purpose Amplifiers

[www.ti.com/general-amps](http://www.ti.com/general-amps)

[www.ti.com/circuitcookbooks](http://www.ti.com/circuitcookbooks)




# Circuit Description

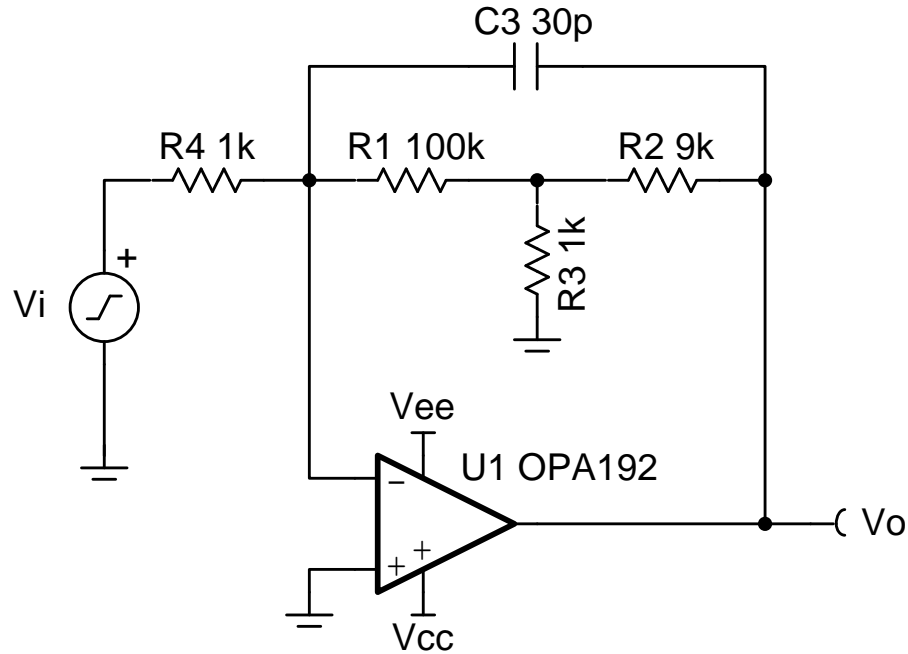

$$V_o = V_i \times \frac{R_1 + R_2 + \frac{R_1 \times R_2}{R_3}}{R_4}$$

# Design Steps

Input		Output		Supply		BW
$V_{iMin}$	$V_{iMax}$	$V_{oMin}$	$V_{oMax}$	$V_{cc}$	$V_{ee}$	$f_p$
-2.5mV	2.5mV	-2.5V	2.5V	5V	-5V	5kHz

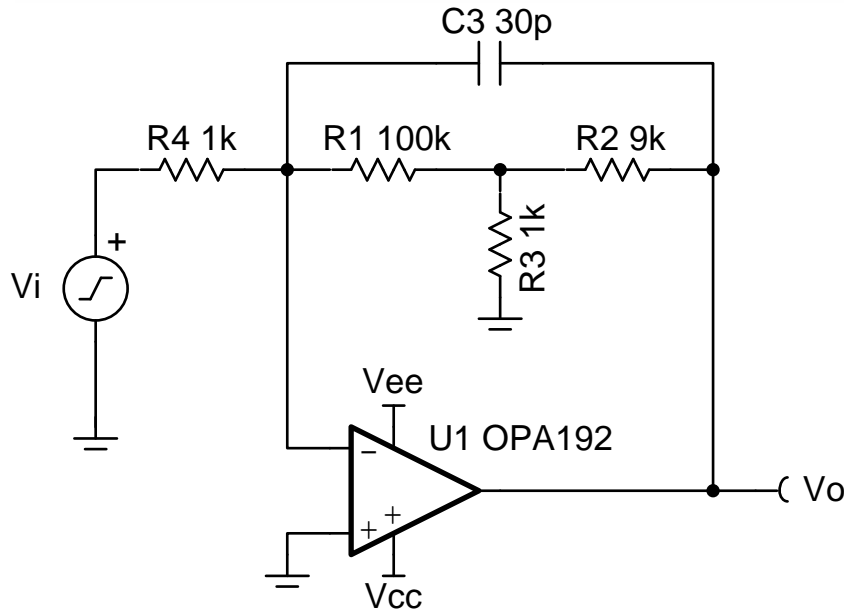

## Inverting Gain

$$\frac{V_o}{V_i} = \frac{R_1 + \boxed{R_2 || R_3}}{R_4} \times \boxed{\frac{R_2 + R_3}{R_3}}$$


Equivalent Resistance

Inverse Voltage Divider

$$\frac{V_o}{V_i} = \frac{R_1 + R_2 + \frac{R_1 \times R_2}{R_3}}{R_4}$$

# Design Steps

Input		Output		Supply		BW
$V_{iMin}$	$V_{iMax}$	$V_{oMin}$	$V_{oMax}$	$V_{cc}$	$V_{ee}$	$f_p$
-2.5mV	2.5mV	-2.5V	2.5V	5V	-5V	5kHz

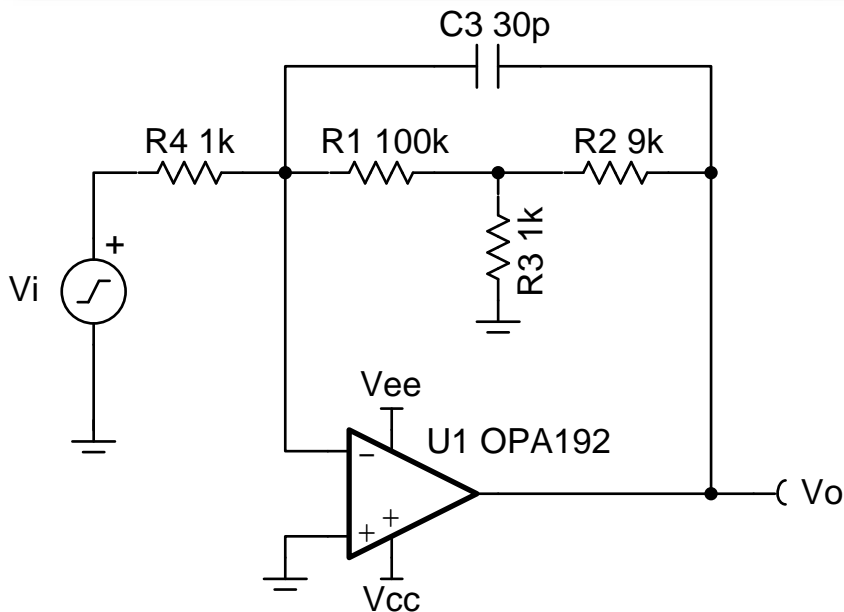


$$Gain = \frac{V_{oMax} - V_{oMin}}{V_{iMax} - V_{iMin}}$$

$$Gain = \frac{2.5V - (-2.5V)}{2.5mV - (-2.5mV)} = 1000V/V$$

# Design Steps

Input		Output		Supply		BW
$V_{iMin}$	$V_{iMax}$	$V_{oMin}$	$V_{oMax}$	$V_{cc}$	$V_{ee}$	$f_p$
-2.5mV	2.5mV	-2.5V	2.5V	5V	-5V	5kHz

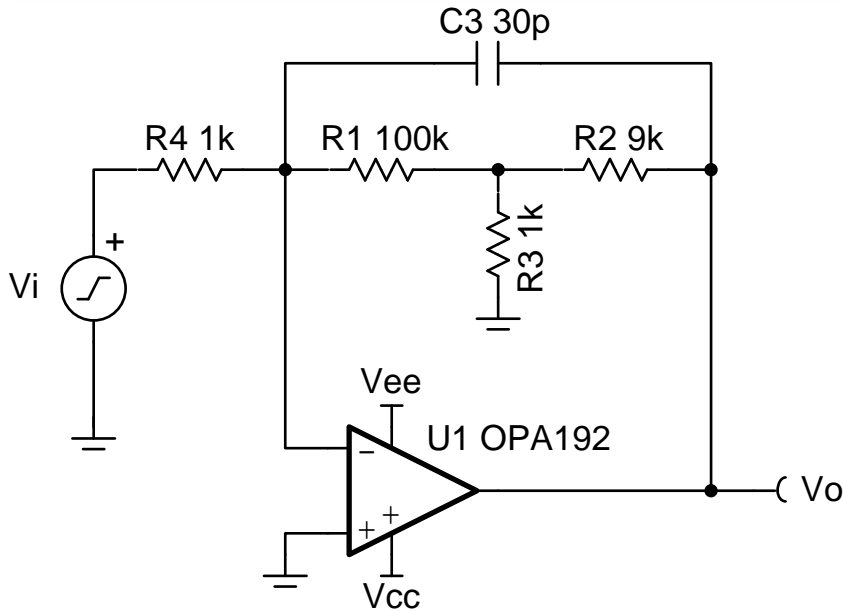

$$Gain = \frac{R_1 + R_2 + \frac{R_1 \times R_2}{R_3}}{R_4}$$

$$R_1 = 100k\Omega$$


$$R_2 = 9k\Omega$$

$$R_4 = 1k\Omega$$

$$R_3 = \frac{R_2 \times R_1}{(Gain \times R_4) - R_1 - R_2} = 1k\Omega$$

# Design Steps

Input		Output		Supply		BW
$V_{iMin}$	$V_{iMax}$	$V_{oMin}$	$V_{oMax}$	$V_{cc}$	$V_{ee}$	$f_p$
-2.5mV	2.5mV	-2.5V	2.5V	5V	-5V	5kHz

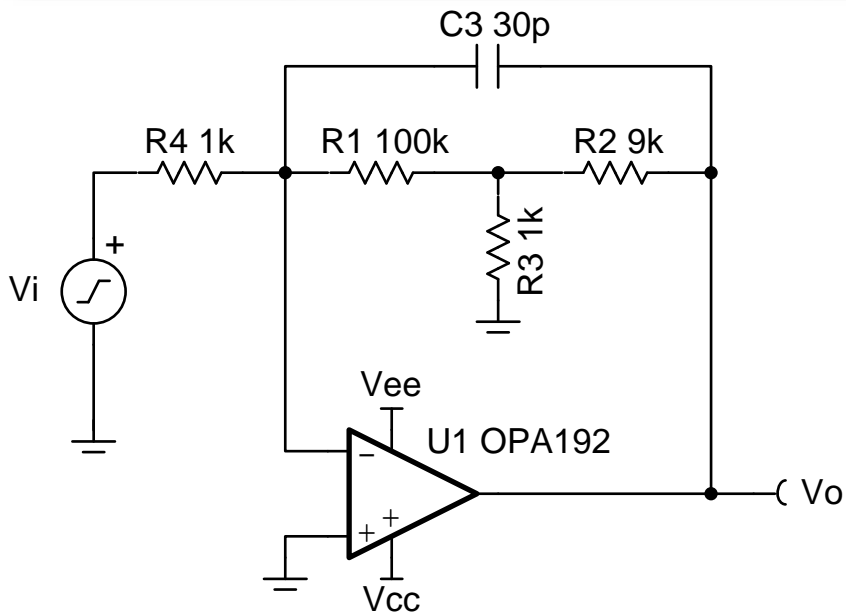


$$R_{eq} = R_1 + R_2 + \frac{R_1 \times R_2}{R_3} = 1.009M\Omega$$

$$C_3 = \frac{1}{2\pi \times R_{eq} \times f_p}$$

$$C_3 = \frac{1}{2\pi \times 1.009M\Omega \times 5kHz} = 31.55pF$$

# Design Steps

Input		Output		Supply		BW
$V_{iMin}$	$V_{iMax}$	$V_{oMin}$	$V_{oMax}$	$V_{cc}$	$V_{ee}$	$f_p$
-2.5mV	2.5mV	-2.5V	2.5V	5V	-5V	5kHz

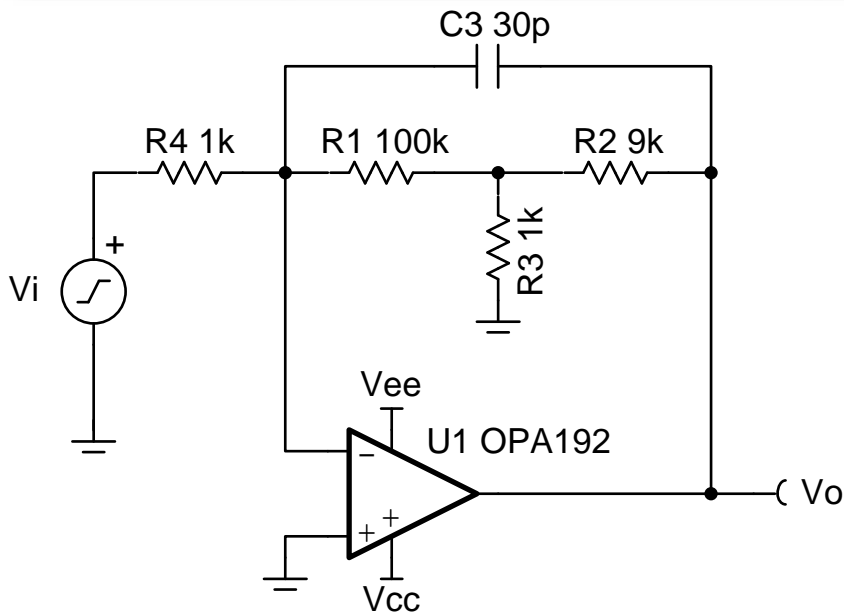



$$NG = 1 + \frac{R_{eq}}{R_4} = 1 + \frac{1.009M\Omega}{1k\Omega} = 1010 V/V$$

$$NG \times f_p < BW_{OPA192}$$

$$5.05MHz < 10MHz$$

# DC Results



Input		Output		Supply		BW
$V_{iMin}$	$V_{iMax}$	$V_{oMin}$	$V_{oMax}$	$V_{cc}$	$V_{ee}$	$f_p$
-2.5mV	2.5mV	-2.5V	2.5V	5V	-5V	5kHz

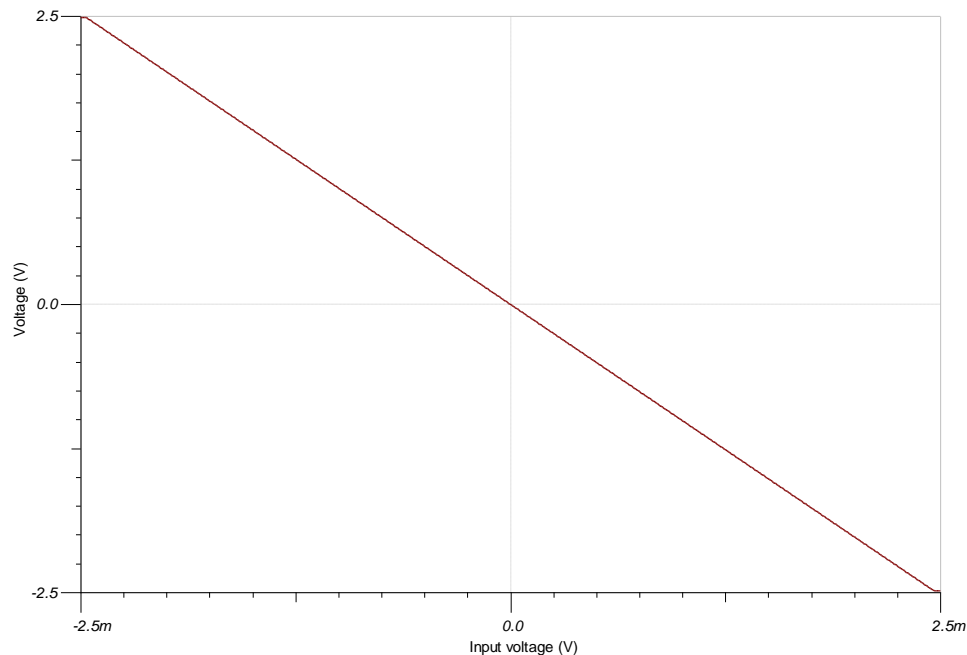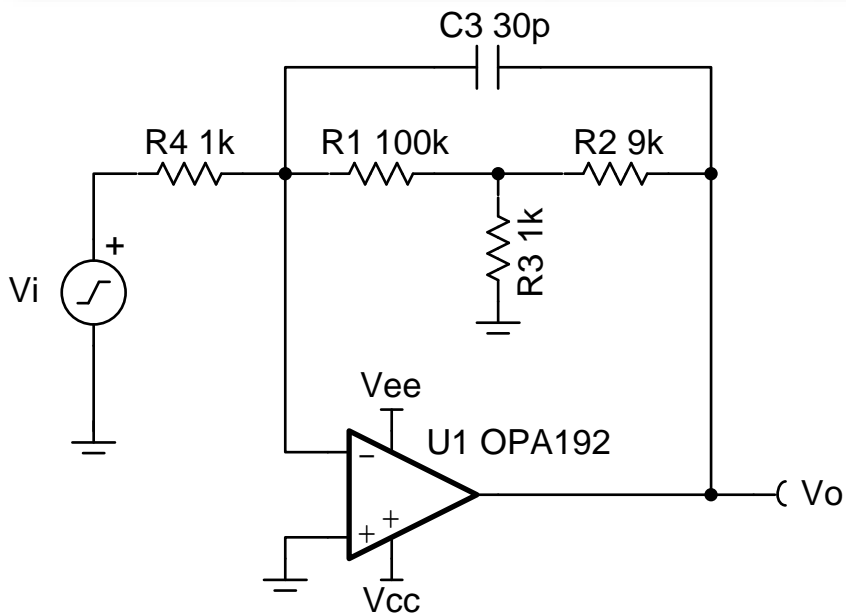




# AC Results

Input		Output		Supply		BW
$V_{iMin}$	$V_{iMax}$	$V_{oMin}$	$V_{oMax}$	$V_{cc}$	$V_{ee}$	$f_p$
-2.5mV	2.5mV	-2.5V	2.5V	5V	-5V	5kHz

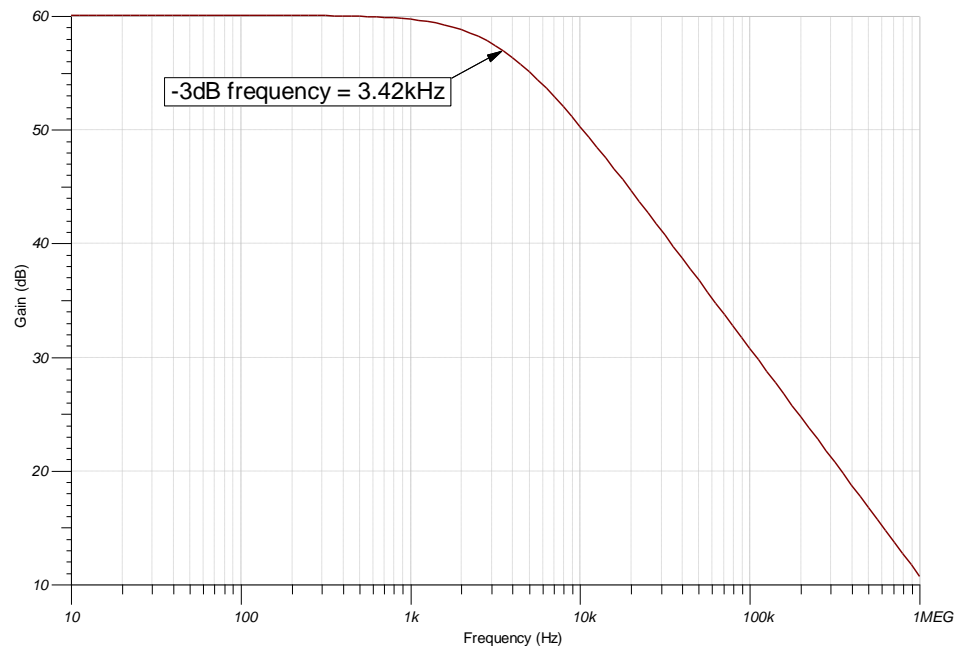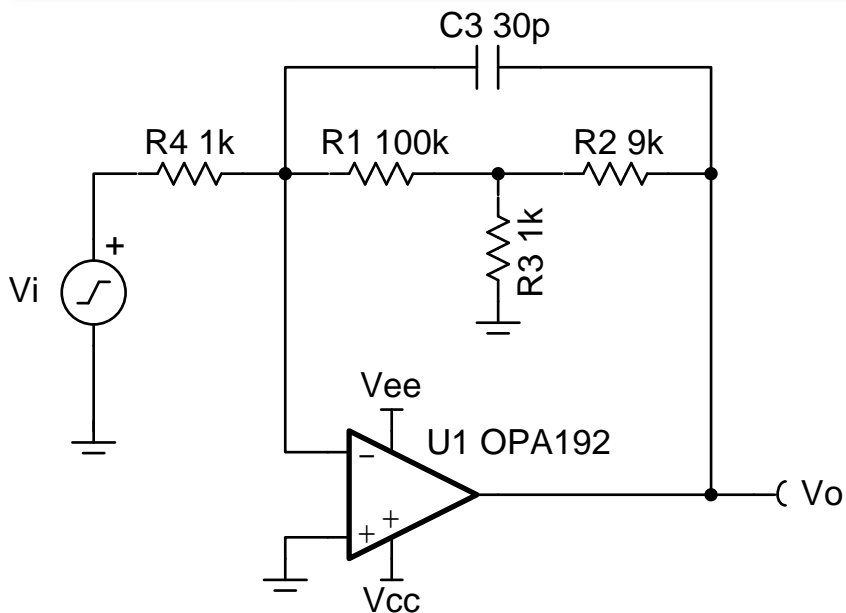

# Design Notes

Input		Output		Supply		BW
$V_{iMin}$	$V_{iMax}$	$V_{oMin}$	$V_{oMax}$	$V_{cc}$	$V_{ee}$	$f_p$
-2.5mV	2.5mV	-2.5V	2.5V	5V	-5V	5kHz

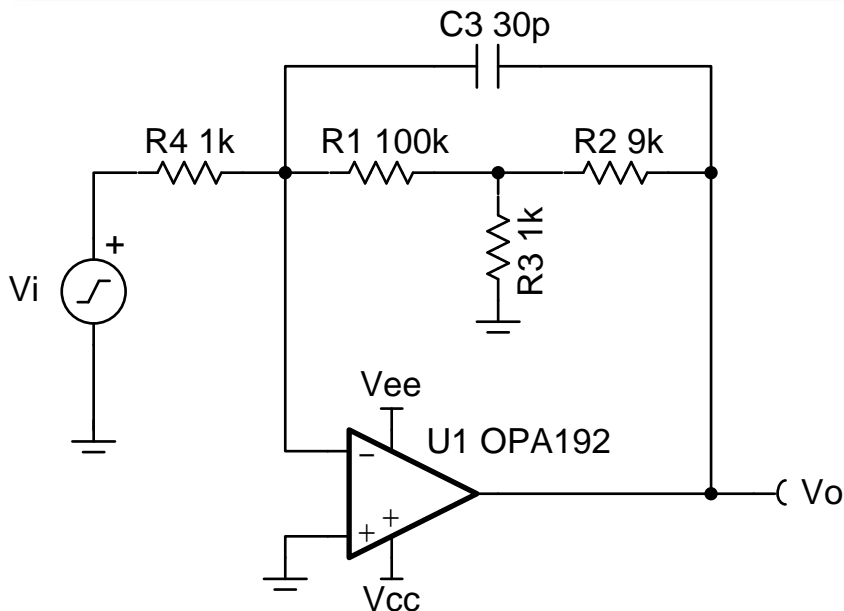

## Design Notes:

1. Use low offset devices due to the high gain of the circuit.
2.  $C_3$  and the equivalent resistance of feedback resistors set the inverting amplifier's cutoff frequency,  $f_p$ .
3. The common-mode voltage in this circuit does not vary with input voltage.

# Design Resources

## EE Cookbook: Op Amp

[www.ti.com/circuitcookbooks](http://www.ti.com/circuitcookbooks)

Step-by-step circuit design of common op amp building block circuits.

## TI Designs

[www.TI.com/tidesigns](http://www.TI.com/tidesigns)

Ready-to-use reference designs with theory, calculations, simulations schematics, PCB files, bench test results

## Analog Engineer's Pocket Reference

[www.TI.com/analogrefguide](http://www.TI.com/analogrefguide)

PDF, iTunes app and hardcopy available  
PCB, analog, mixed signal design formulae  
Conversions, tables, equations

## TI Precision Labs

[www.TI.com/precisionlabs](http://www.TI.com/precisionlabs)

Quiz questions, problems, solutions  
Labs and evaluation module (EVM) available

## TINA-TI™ simulation software

[www.TI.com/tool/tina-ti](http://www.TI.com/tool/tina-ti)

Complete SPICE simulator DC, AC, transient, noise analysis  
Schematic entry and post-processor for waveform math

## DIYAMP-EVM

[www.TI.com/DIYAMP-EVM](http://www.TI.com/DIYAMP-EVM)

Evaluation module providing engineers with SC70, SOT23, SOIC packaging and 12 popular amplifier configurations

## The Signal

[www.ti.com/thesignal](http://www.ti.com/thesignal)

PDF, iTunes app and hardcopy available  
A compendium of blog posts on op amp design topics including offset voltage, input bias current, stability, noise and more

## Analog Wire Blog

[www.TI.com/analogwire](http://www.TI.com/analogwire)

Technical blogs written by analog experts  
Tips, tricks, and design techniques

## TI E2E™ Community

[www.TI.com/e2e](http://www.TI.com/e2e)

Support forums for all TI products

## Op Amp Parametric Quick Search

[www.TI.com/amplifiers](http://www.TI.com/amplifiers)

Search for precision, high-speed, general-purpose, ultra-low-power, audio and power op amps

## Op Amp Parametric Cross-Reference

[www.TI.com/opampcrossreference](http://www.TI.com/opampcrossreference)

Find similar TI op amps using competitive part numbers

[www.ti.com/circuitcookbooks](http://www.ti.com/circuitcookbooks)



© Copyright 2021 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.  
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)