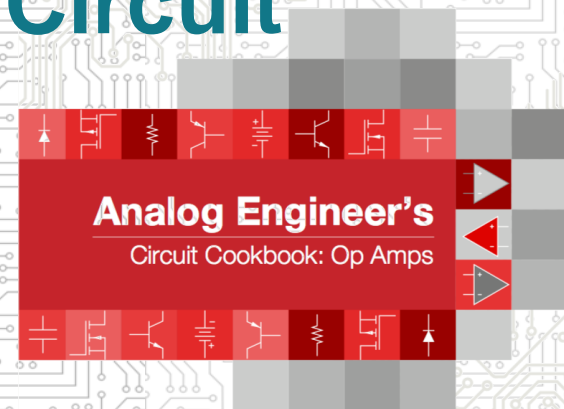


How to Design Adjustable Reference Voltage Circuit


General Purpose Amplifiers

www.ti.com/general-amps

www.ti.com/circuitcookbooks




Circuit Description

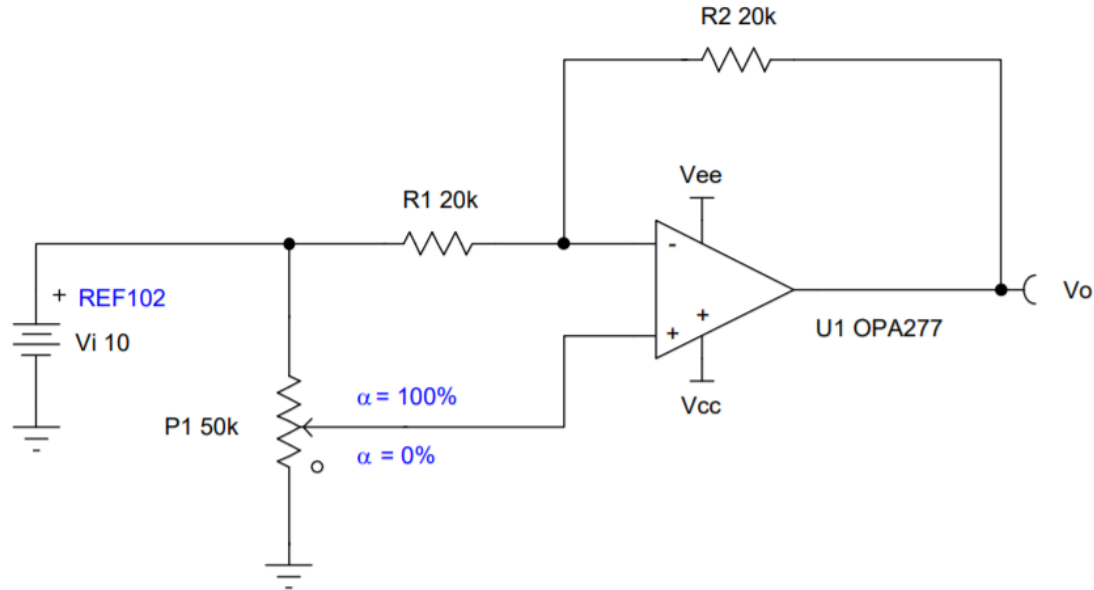

$$V_o = V_i \times \left(-\frac{R_2}{R_1} + \alpha \left(1 + \frac{R_2}{R_1} \right) \right)$$

Design Steps

Input	Output		Supply	
V_i	V_{oMin}	V_{oMax}	V_{dd}	V_{ee}
10V	-10V	10V	15V	-15V

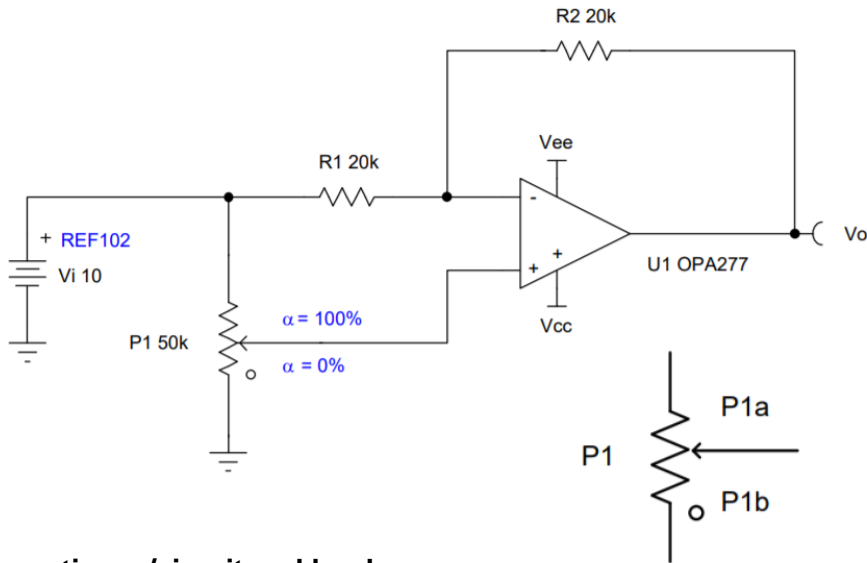

Inverting
Gain

$$\frac{V_o}{V_i} = -\frac{R_2}{R_1} + \alpha \left(1 + \frac{R_2}{R_1} \right)$$


Non-Inverting
Gain

$$\alpha = \frac{P1b}{P1}$$

$$P1 = P1a + P1b$$

Design Steps

Input	Output		Supply	
V_i	V_{oMin}	V_{oMax}	V_{dd}	V_{ee}
10V	-10V	10V	15V	-15V

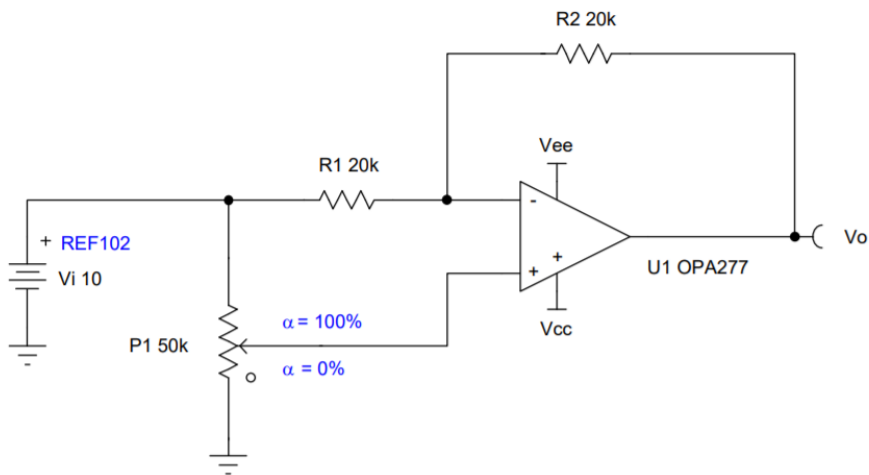

$$R_2 = R_1 = 20k\Omega$$



$$V_o = (2 \times \alpha - 1) \times V_i$$

$$\alpha = 0; V_o = -V_i$$

$$\alpha = 1; V_o = V_i$$


DC Results

Input	Output		Supply	
V_i	V_{oMin}	V_{oMax}	V_{dd}	V_{ee}
10V	-10V	10V	15V	-15V

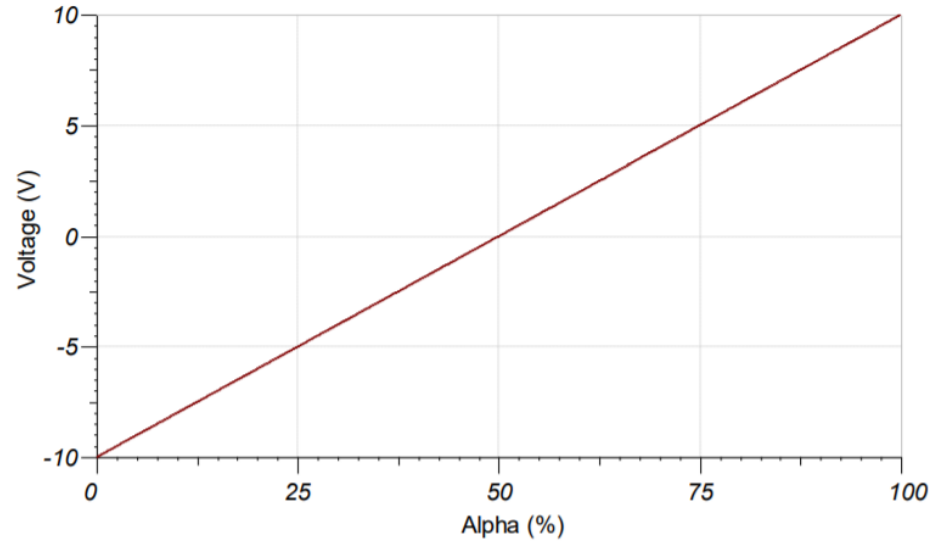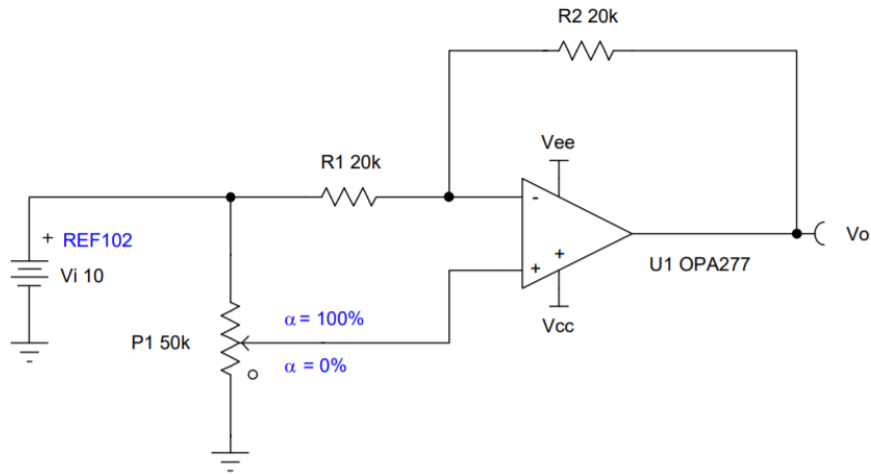

Design Notes

Input	Output		Supply	
V_i	V_{oMin}	V_{oMax}	V_{dd}	V_{ee}
10V	-10V	10V	15V	-15V

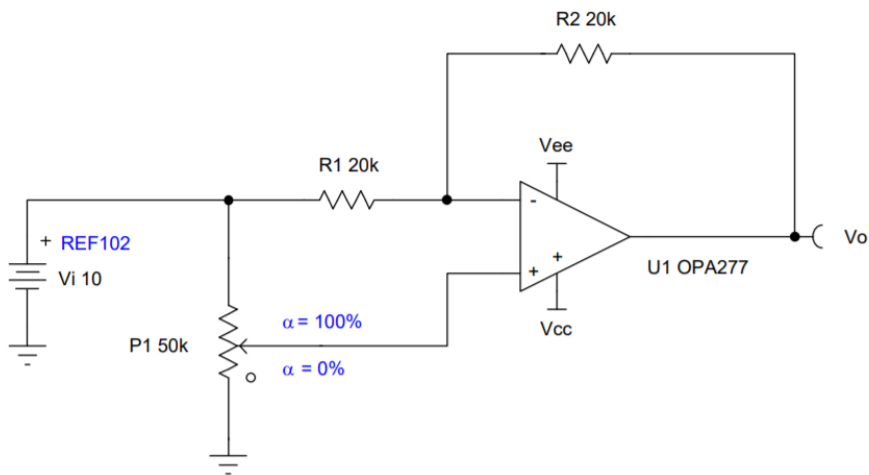

Design Notes:

1. Observe the common-mode and output swing limitations of the op amp.
2. Mismatch in R1 and R2 results in a gain error. Therefore, be sure to use precision resistors for high accuracy applications.
3. Select the potentiometer based on the desired resolution of the reference.

Design Resources

EE Cookbook: Op Amp

www.ti.com/circuitcookbooks

Step-by-step circuit design of common op amp building block circuits.

TI Designs

www.TI.com/tidesigns

Ready-to-use reference designs with theory, calculations, simulations schematics, PCB files, bench test results

Analog Engineer's Pocket Reference

www.TI.com/analogrefguide

PDF, iTunes app and hardcopy available
PCB, analog, mixed signal design formulae
Conversions, tables, equations

TI Precision Labs

www.TI.com/precisionlabs

Quiz questions, problems, solutions
Labs and evaluation module (EVM) available

TINA-TI™ simulation software

www.TI.com/tool/tina-ti

Complete SPICE simulator DC, AC, transient, noise analysis
Schematic entry and post-processor for waveform math

DIYAMP-EVM

www.TI.com/DIYAMP-EVM

Evaluation module providing engineers with SC70, SOT23, SOIC packaging and 12 popular amplifier configurations

The Signal

www.TI.com/signalbook

PDF, iTunes app and hardcopy available
A compendium of blog posts on op amp design topics including offset voltage, input bias current, stability, noise and more

Analog Wire Blog

www.TI.com/analogwire

Technical blogs written by analog experts
Tips, tricks, and design techniques

TI E2E™ Community

www.TI.com/e2e

Support forums for all TI products

Op Amp Parametric Quick Search

www.TI.com/amplifiers

Search for precision, high-speed, general-purpose, ultra-low-power, audio and power op amps

Op Amp Parametric Cross-Reference

www.TI.com/opampcrossreference

Find similar TI op amps using competitive part numbers

www.ti.com/circuitcookbooks



© Copyright 2021 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)