

# How to limit PFC re-rush current

Bosheng Sun

Power Design Services


## Introduction

The recently released Modular Hardware System – Common Redundant Power Supply (M-CRPS) specification [1] requires the re-rush current (which is different from the well-known inrush current) needs to be limited when the input voltage resumes after an input brownout or blackout event on the power supply used in data center. Previously, this re-rush current was unspecified, and no special control action for this event existed. In this article, I'll present a low-cost, simple and very effective method to meet the M-CRPS requirement.

## Inrush current vs. re-rush current


Power factor correction (PFC) is required for front-end power supplies (PSUs) greater than 75W. PFC forces the input current to follow the input voltage so that the electronics load appears as a resistor. PFC usually has a large output capacitor. Before startup, the PFC output capacitor is fully discharged. Because the PFC structure provides a current path when  $V_{AC} > V_{OUT}$ , applying the AC voltage will generate a huge current, since the input voltage is essentially applied to the PFC output capacitor directly. This current is called the inrush current.

Placing a thermistor ( $R_T$ ) with a positive temperature coefficient and a mechanical relay at the PFC input side will limit the inrush current, as shown in **Figure 1**. During PFC power up, the relay is off. The inrush current is limited by  $R_T$  to a low value, and the PFC output bulk capacitor ( $C_{BULK}$ ) charges gradually. Once the output voltage ( $V_{OUT}$ ) charges to equal the peak value of the AC voltage ( $V_{AC}$ ), the inrush current drops to 0. Then the relay turns on, with  $R_T$  bypassed to reduce power losses during normal operation.

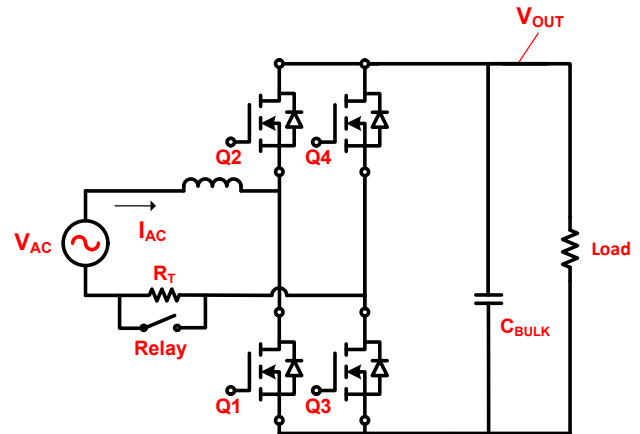

**Figure 1.** Using  $R_T$  and a relay to limit the PFC inrush current.

Re-rush current is different; it occurs during normal PFC operation. As shown in **Figure 2**, the AC input voltage suddenly drops out when PFC is operating normally. Since the load is still applied, the PFC  $V_{OUT}$  could drop to a lower value. Then when the AC voltage returns, if the AC input voltage is higher than  $V_{OUT}$ , there will be an inrush current again. This current is called the re-rush current.

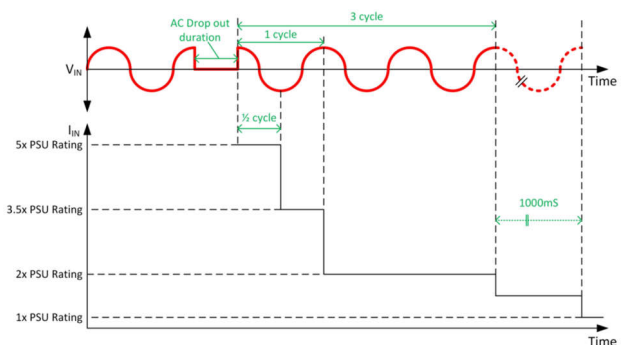

**Figure 2.** M-CRPS re-rush current limit and timing.

Previously, it is solely relies on the power stage components' ability to handle the re-rush current. Test results show that the re-rush current can jump to more than 10 times higher than the PFC-rated maximum input current. Such a high re-rush current can either damage the power supply or reduce its lifetime, which is why

the M-CRPS specification limits the amount of re-rush current after the AC voltage returns. The root-mean-square value of the re-rush current should be less than five times the maximum PSU current rating ( $5 \times I_{rated,RMS}$ ) over a half cycle of input frequency, and less than  $3.5 \times I_{rated,RMS}$  over one cycle of input frequency. In addition, the input current should settle to a value  $\leq 2 \times I_{rated,RMS}$  within two cycles of the input frequency after applying the AC input.

It gets more complicated when considering PFC pulse-width modulation (PWM) operation during this period. If the PFC is not well controlled, an inappropriate PWM duty cycle may occur when the AC voltage resumes, resulting in another large input current spike that may also exceed the M-CRPS specification.

On the other hand, when the AC voltage resumes, PFC needs to supply enough current to boost the PFC output voltage to its regulation level as soon as possible; otherwise,  $V_{OUT}$  will keep dropping because of the heavy load and eventually trip the input undervoltage lockout level of the DC/DC converter. Charging the PFC output capacitor once the AC voltage resumes will require a large input current, either from re-rush when  $V_{IN} > V_{OUT}$  or from the PFC control loop when  $V_{IN} < V_{OUT}$ .

This paper provides a solution to handle this re-rush current so that when the AC voltage comes back from dropout, both the re-rush current (when  $V_{IN} > V_{OUT}$ ) and the non-re-rush current (when  $V_{IN} < V_{OUT}$ ) are well controlled and high enough to rapidly boost  $V_{OUT}$  but not exceed the M-CRPS limit specification.

### Proposed re-rush current control method

Figure 3 illustrates the proposed low-cost re-rush current control method. There are two differences compared to Figure 1. First,  $R_T$  has moved from the AC side to the DC side. Second, a metal-oxide semiconductor field-effect transistor (MOSFET),  $Q_5$ , has replaced the traditional mechanical relay. The reason to choose a solid-state relay is that you need to rapidly turn the relay on and off, and a mechanical relay is too slow for this purpose. Also,

because the MOSFET cannot turn off the AC voltage, it is put on the DC side. The inrush current limit works the same as the traditional method. The first time that the input voltage is applied to the PSU,  $R_T$  will limit the inrush current. Once the inrush current passes,  $Q_5$  turns on and  $R_T$  is bypassed.

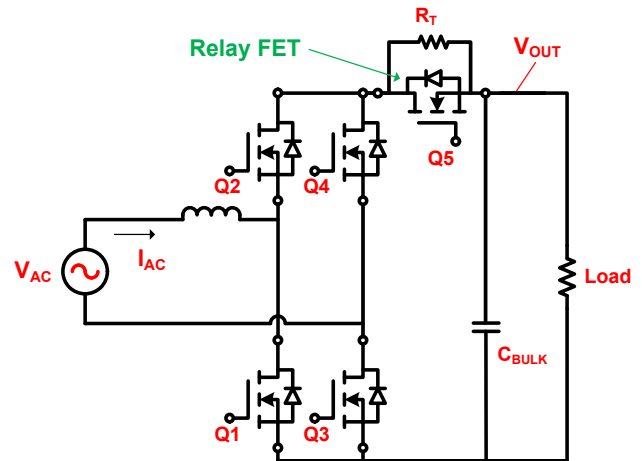


Figure 3. The proposed re-rush current limit hardware structure.

Figure 4 illustrates the proposed re-rush current control method.  $V_{AC}$  is the PFC input voltage,  $V_{OUT}$  is the PFC output voltage, and  $I_{AC}$  is the input current.  $Q_1$  and  $Q_2$  are high-frequency switches that work as either a PFC boost switch or a synchronous switch alternatively in each AC half cycle. The AC line drops for a period of 10ms and then comes back at its peak while the PFC operates at full load. This is the worst case for AC voltage dropout.


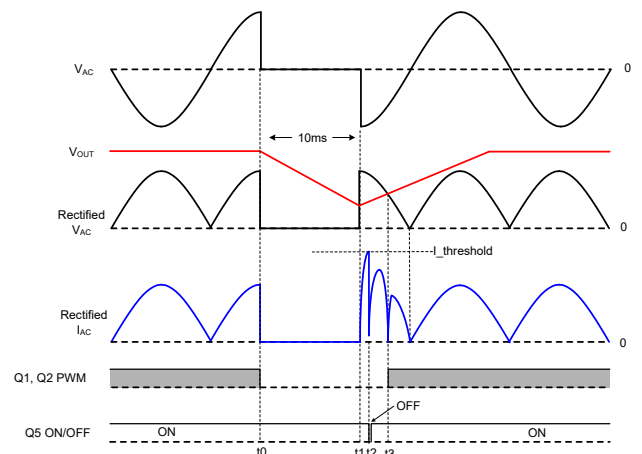


Figure 4. The proposed AC drop and re-rush current limit control algorithm.

This is the proposed re-rush current control method:

- At  $t_0$ : Upon detection of an AC voltage drop,  $Q_1$  and  $Q_2$  turn off. You must also turn off both the PFC voltage and current loops because if the voltage loop and current loop keep running, their integrators will accumulate. When the AC voltage comes back and PFC turns on, a large PWM duty cycle will then be present, resulting in a large current spike that may damage the power supply.
- Once the current loop is turned off, reset it to 0 and clear its integrator history. If you do not clear the integrator, when the AC voltage comes back and PFC turns on, PFC will turn on with the same PWM duty cycle before the AC voltage drop, and it may not be the appropriate duty cycle. For example, if the AC voltage dropout occurs at zero crossing, the PWM duty cycle is almost 100%. If the AC voltage comes back at the AC peak without a cleared current-loop integrator, an almost 100% duty cycle will occur at the AC peak and generate a large current spike, which could damage the power supply. For the voltage loop, once it turns off, freeze it to keep its internal value. The voltage loop output represents the load and is used for current loop-reference generation; therefore, you want to keep its value so that the load does not change during AC dropout.
- At  $t_1$ : The AC voltage returns. Because  $V_{AC} > V_{OUT}$ , a generated re-rush current will charge the bulk capacitor.  $Q_1$  and  $Q_2$  remain off.
- At  $t_2$ : The re-rush current exceeds a programmable threshold and trips a relay  $Q_5$  turnoff event. The re-rush current is then limited by  $R_T$  when  $Q_5$  is off, and its magnitude rapidly drops. Relay  $Q_5$  only turns off for a very short period of time (for example,  $10\mu s$ ), then turns on again. Once  $Q_5$  turns on, the re-rush current rises again until it exceeds the threshold. This process repeats until the re-rush current never exceeds the limit again. **Figure 5** shows the flow chart for this process.

- At  $t_3$ :  $V_{AC} < V_{OUT}$ . Now it is time to turn on PFC. Set the voltage loop reference equal to the instantaneous  $V_{OUT}$  value at  $t_3$ , then turn on the voltage loop. After that, gradually increase the voltage loop reference until it reaches the normal setpoint. For the current loop, first calculate a duty cycle  $D = (V_{OUT} - V_{AC}) / V_{OUT}$  and inject it into the current loop such that the current loop output starts from the calculated  $D$  when the current loop is on. Then turn on the current loop. Finally, turn on  $Q_1$  and  $Q_2$  to allow PFC normal operation.

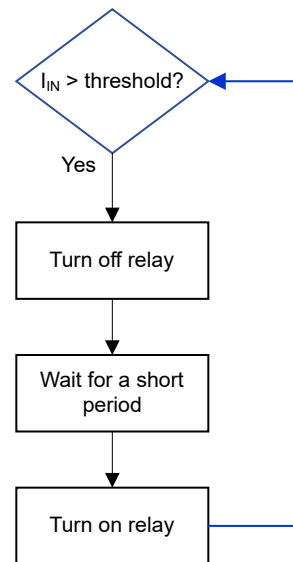


**Figure 5.** Flowchart of the proposed relay on and off control algorithm.

This process repeats until  $V_{OUT}$  exceeds  $V_{AC}$ .

### Test result


I tested the proposed method on a 3.6kW totem-pole bridgeless PFC [2]. **Figure 6** shows that when the AC voltage drops out, it comes back in 10ms at its peak. Channel 1 (blue) is the PFC input current waveform ( $I_{IN}$ ), while channel 2 (turquoise) is the relay on and off control signal. **Figure 7** is the zoom in at relay on and off. During the AC drop period, relay  $Q_5$  remains on.  $C_{BULK}$  continuously delivers the stored energy to the load and  $V_{OUT}$  drops. After the AC voltage resumes, because the relay is on and  $V_{AC} > V_{OUT}$ , the re-rush current quickly rises. Once the re-rush current reaches

a predefined current limit threshold (40A in this example), the relay turns off, and the re-rush current reduces to a very low value because of  $R_T$ . The relay only remains off for  $10\mu\text{s}$ , then turns on again. The re-rush current rises once again. This entire process allows the limiting of re-rush current within the M-CRPS specification while still supplying substantial current to rapidly charge  $C_{\text{BULK}}$ . The waveform also shows that the non-re-rush current, where  $V_{\text{AC}} < V_{\text{OUT}}$ , is well controlled without large current spikes.

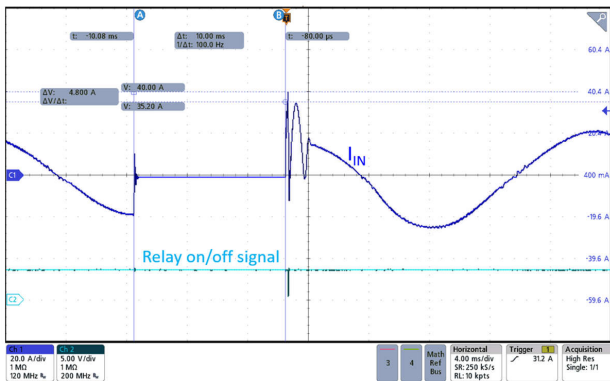

**Figure 6.** Re-rush current control when the AC voltage resumes after dropout.

**Figure 7** shows the second re-rush current rising up with a limited slope, which occurs because the PFC input impedance – including the electromagnetic interference filter impedance and printed circuit board trace impedance – limit the current rising slope. The magnitude of the second re-rush current does not exceed the 40A threshold in this example; therefore, the relay turns off only once. If the second re-rush current also exceeds the threshold, the relay will turn off again.

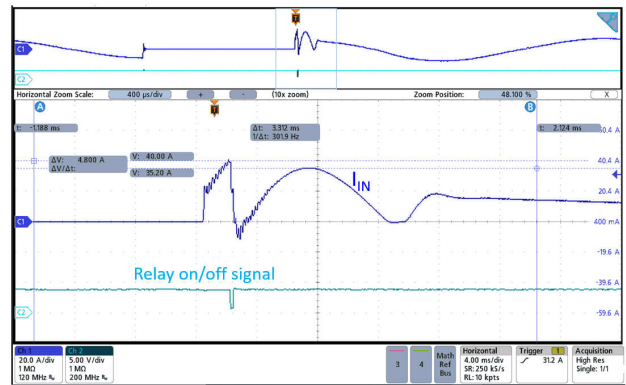

**Figure 7.** Zoomed-in Figure 6 at the relay on and off instant.

## Conclusion

The power supply used in data centers requires the re-rush current when the AC voltage resumes from dropout should not exceed a limitation defined in M-CRPS specification. By replacing the traditional mechanical relay with a solid-state relay, and rapidly turn off/on the relay when re-rush current exceeds a programmable threshold, the re-rush current can be well controlled to not exceed the M-CRPS limit specification but high enough to rapidly boost  $V_{\text{OUT}}$ . Moreover, this firmware-based method leverages the existing  $R_T$ , resulting in a low-cost and very effective re-rush current control solution.

## References

1. **Modular Hardware System – Common Redundant Power Supply (M-CRPS) Base Specification.** Version 1.05 RC5. Open Compute Project: Austin, Texas, Sep. 25, 2024.
2. Texas Instruments. n.d. **3.6kW Single-Phase Totem-Pole Bridgeless PFC Reference Design with E-Meter Functionality.** Texas Instruments reference design No. PMP23338. Accessed March 24, 2025.

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

All trademarks are the property of their respective owners.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2025, Texas Instruments Incorporated