

Ratiometric Measurement - Improving Bridge Sensor Sampling Accuracy



Yunjing Wang

Analog FAE

This document was translated from a simplified Chinese source. (ZHCTA15)

The Wheatstone bridge sensor is a common sensor type for various industrial equipment, often used to sense changes in physical quantities such as strain, pressure, and temperature. This article will introduce how ratiometric measurement reduces the sampling error of the Wheatstone bridge sensor and improves system sampling accuracy.

As shown in Figure 1, it is a typical Wheatstone bridge - quarter-bridge resistor sensor, which consists of two parallel resistor branches, including three static resistor elements R and a variable resistor sensor $R + \Delta R$. Changes in physical parameters can be converted into the resistance change of the variable resistor sensor.

When the change in physical parameters is 0, $\Delta R = 0\Omega$, and the bridge output $V_{out} = 0$; when the physical parameters change, $\Delta R \neq 0\Omega$, and the bridge output V_{out} is as shown in Equation 1;

$$V_{out} = V_{excitation} \times \left[\left(\frac{R + \Delta R}{R + R + \Delta R} \right) - \left(\frac{R}{R + R} \right) \right] = V_{excitation} \cdot \left[\left(\frac{\Delta R}{2(2R + \Delta R)} \right) \right] \quad (1)$$

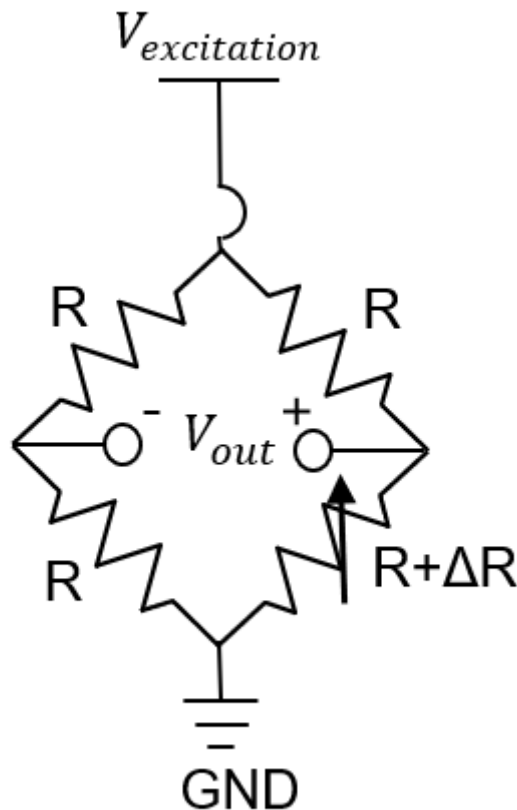


Figure 1. Quarter-Bridge Resistor Sensor

A traditional sampling system for the bridge output is usually shown in Figure 2.

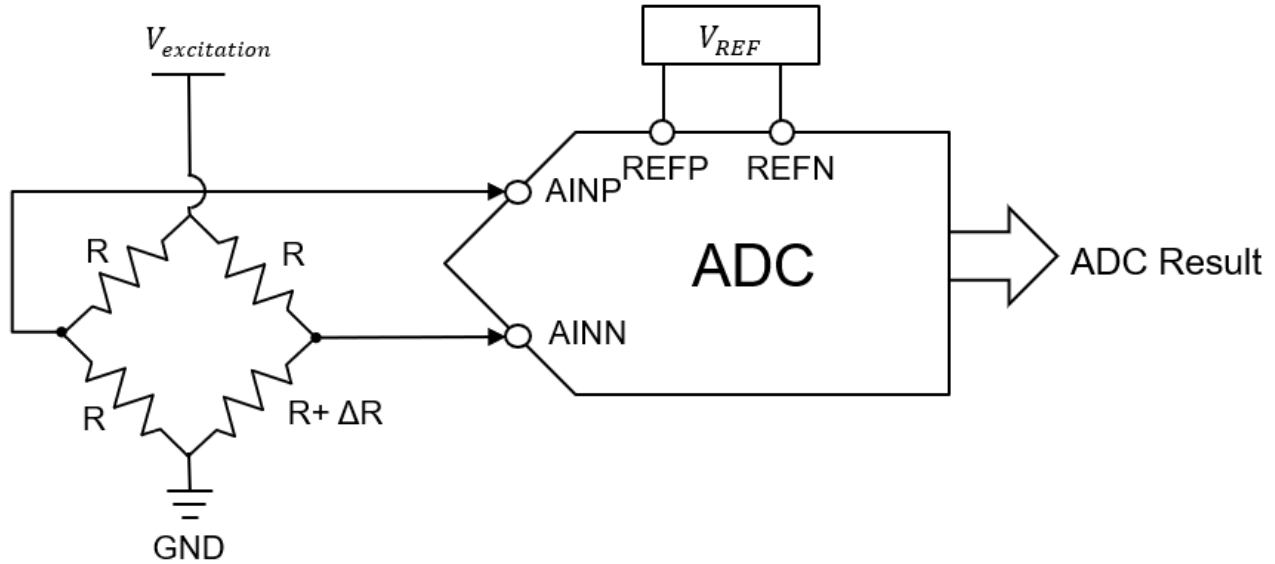


Figure 2. Bridge Sensor - Traditional Sampling Circuit

By substituting the bridge output voltage in Equation 1 into the ADC output code formula, the ADC conversion code of the bridge voltage can be obtained as follows:

$$ADC_{result} = (V_{excitation} + V_{exc_noise}) \cdot \left[\left(\frac{\Delta R}{2(2R + \Delta R)} \right) \right] \cdot \frac{2^N}{V_{REF} + V_{REF_noise}} \quad (2)$$

It can be seen that when there is any error such as noise or temperature drift in the ADC reference voltage and the bridge excitation voltage, they will be included in the ADC conversion code error of the bridge voltage, and such errors are usually a larger contribution to the error of the ADC conversion result.

Using the ratiometric measurement method can easily cancel these two error sources of the bridge sampling system, as shown in Figure 3, using the ADC reference voltage as the resistor bridge excitation voltage.

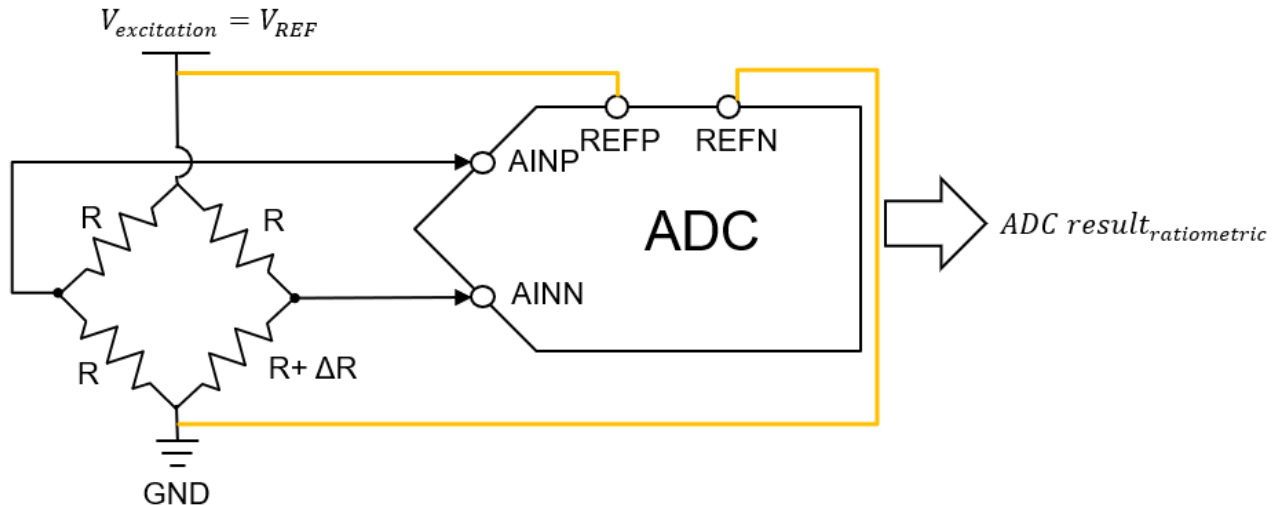


Figure 3. Bridge Sensor - Ratiometric Measurement Sampling

Then $V_{excitation} + V_{exc_noise} = V_{REF} + V_{REF_noise}$. By substituting this into Equation 2, the code output of the bridge voltage configured with ratiometric measurement after sampling ADC conversion can be obtained:

$$ADCresult_{ratiometric} = \frac{2^N \Delta R}{2(2R + \Delta R)} \quad (3)$$

It can be seen that the resistor bridge excitation voltage and the ADC reference voltage in the original [Equation 2](#) are canceled out in the ADC results [Equation 3](#) of the ratiometric measurement. Correspondingly, the contribution of the excitation voltage and reference voltage to the system error can also be eliminated.

Taking ADS124S06 as an example, use ADS124S06 to perform resistor bridge measurement, and compare the system errors under two configurations: non-ratiometric measurement and ratiometric measurement. If using a non-ratiometric measurement configuration with the lowest BOM cost configuration: the resistor bridge excitation voltage is provided by the 5V of the system power rail Buck, and the ADC reference voltage uses the on-chip reference. After room temperature calibration, under a 350mV resistor bridge voltage, the system error is approximately 552ppm; using a ratiometric measurement configuration, as long as the ADC on-chip reference is simultaneously provided to the resistor bridge excitation, without adding any additional system BOM cost, the errors of the resistor bridge excitation voltage and the ADC reference voltage can be canceled out, and the system error is reduced to 130ppm.

Absolute vs Ratiometric Measurement Accuracy				
Parameter	Maximum			
Initial error specs	VIN = 30 mV	VIN = 150 mV	VIN=350mV	Units
INL	15	15	15	ppm
Offset	66.67	13.33	5.71	ppm
Gain Error	200	120	120	ppm
RREF initial accuracy	500	500	500	ppm
Temperature drift specs				
Offset Drift (no cal)	41.67	8.33	3.57	ppm
Offset Drift (cal at 25°C)	21.67	4.33	1.86	ppm
Gain Drift (no cal)	250	250	250	ppm
Gain Drift (cal at 25°C)	130	130	130	ppm
RREF Drift (no cal)	375	375	375	ppm
RREF Drift (cal at 25°C)	195	195	195	ppm
Total error				
Total error (Absolute measure, cal at 25°C)	552.83	552.42	552.41	ppm
Total error (Ratio measure, cal at 25°C)	132.644052	130.9342498	130.8757005	ppm

Therefore, using ratiometric measurement can eliminate the largest error source in sampling—the REF reference error—without increasing the original BOM cost, thereby significantly reducing system error and improving bridge sensor sampling accuracy.

References

1. [ADS124S06 datasheet](#)
2. [Fundamentals of Precision ADC Noise Analysis \(Rev. A\)](#)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you fully indemnify TI and its representatives against any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#), [TI's General Quality Guidelines](#), or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products. Unless TI explicitly designates a product as custom or customer-specified, TI products are standard, catalog, general purpose devices.

TI objects to and rejects any additional or different terms you may propose.

Copyright © 2026, Texas Instruments Incorporated

Last updated 10/2025