

# Precision Brightness and Color Mixing in LED Lighting Using Discrete Current Sense Amplifiers

Arjun Prakash, Current Sensing Products



Light Emitting Diode (LED) lighting has grown exponentially in residential and industrial applications. According to ENERGY STAR, the reduction in operating costs from LED lighting are 75% and lasts 35 to 50 times longer than traditional incandescent lighting. The government regulations to reduce energy consumption have also fueled and accelerated the growth of LED. LEDs are now being used in several diverse applications like automotive headlamps, aviation industry, street lighting, emergency lights to name a few.

LEDs are a special purpose p-n junction diode and emits light when activated with an electrical signal. When a precise and controlled current is applied to the LED due to the recombination of electron and "holes" the device releases photons. The release of photons is what translates to light to a human eye. By proportionally controlling current across the LED the color and the brightness can be precisely controlled. A common technique of precisely controlling current is to create a color contrast using RGY LEDs.

## LED Driver Control System

The most common technique to control the LED is to force a constant current across the LED. By controlling the current flowing to the LED, brightness and dimming can be precisely controlled. [Figure 1](#) explains briefly on a system implementation of a LED driver. In an industrial lighting systems the 110V/220V AC voltage is converted to a DC voltage using rectifiers and switching regulators. The DC voltage can vary from 48V, 60V or even as high as 400V. The DC voltage is connected directly to the LED driver.

A current sense amplifier is connected to the DC bus voltage bus for the following applications

- Detect open-short LED strings in a multiple parallel string environment
- Maintain constant lumen output over the years of usage of luminaire
- Measure precise current for brightness control
- Implement accurate linear or logarithmic dimming control
- Accurate current measurement is needed for LED Luminaires which supports Constant Lumen Output (CLO) feature.


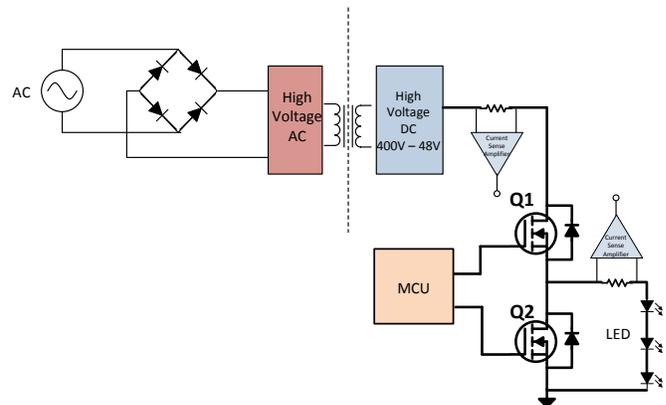


Figure 1. LED driver system control

## Pulse Width Modulation (PWM) Dimming

One of the key specifications of LED lighting for maintaining the light output and protection is the maximum current rating. Precise control of current output determines precision dimming of LED lighting. PWM dimming is achieved by turning on and off the current flow to the LED for a fixed time period with a variable duty cycle. As the duty cycle of PWM is varied the peak current flow to the LED is controlled. As the duty cycle is controlled the peak current during turn on and virtually no current flowing during turn off dictates the average current output to the LED. This technique is the simplest to implement but does have several disadvantages. As the LED heats up due to usage the impedance characteristics of the LED changes. Without tracking the impedance characteristics, the brightness due to dimming can be inconsistent resulting in color changes and varying brightness. This issue can simply be solved by adding a current sensing amplifier at the output of the LED driver as described in [Figure 2](#). Current sensing amplifiers with feedback control can accurately vary the duty cycle to maintain consistent light output irrespective of LED characteristics changes. However the system challenges with EMI, flickering effect and inrush current, still needs to be resolved by operating at higher switching frequencies and ferrite beads present at the output.

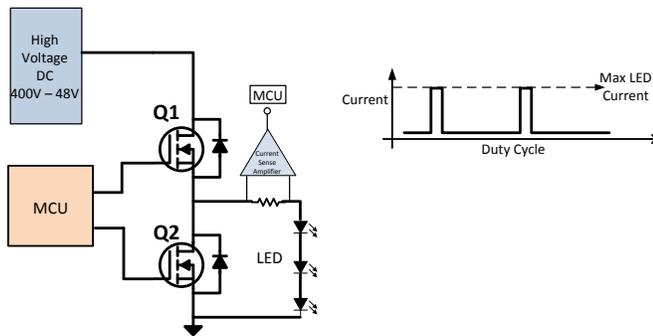

**Figure 2. PWM dimming using current sense amplifier**


**Analog Dimming or Constant Current Control**

In analog dimming, the average current flow is maintained to be constant. Current flow through the LED lighting directly relates to the light output. Analog dimming is preferred over PWM dimming for applications that require UL class 2 certification. UL Class 2 certification requires power supplies to limit PWM frequencies between 10Hz and 200Hz. At these lower frequencies the LED output creates a flickering effect to the human eye that can be undesirable.

Analog dimming is also very widely used for color mixing applications. LEDs color temperature is rated at a specific current output level. For example, a LED color temperature maybe 2800K at 1300mA and at 1500mA the color temperature may go up to 5000K. A precise current control system can maintain the desired color temperature. One of the main applications analog dimming is used widely for is color contrast creation. In automotive infotainment LED lights are used to recreate background color to make it appeal and look as true as possible. As explained in Figure 3 a combination of LED lighting, LED driver and precision current sense amplifier with analog dimming can accomplish recreation of true background color. Analog dimming is also preferred in applications that have very stringent EMI restrictions. However, one of the drawbacks of analog dimming is its property to change the color temperature. In applications where dimming is required to lower the brightness and yet maintain the color temperature, analog dimming falls shorts here.

The INA240 current sense amplifier can operate from a common mode voltage ranging from -4V to 80V. A low offset of (25µV) and low voltage offset drift (0.25µV/°C) combined with a low gain error (0.2%) and gain drift (2.5ppm/°C) makes it applicable for precise measurements regardless of system temperature. A low offset of 25µV enables the application to use lower

shunt resistance and also enhances the total dynamic range for current measurements. The dynamic range of current sense amplifier directly relates to the dynamic range available for dimming. In addition to high performance DC specifications, the INA240 is also designed to operate and reject dv/dt transients enabling real time LED current measurements at the in-line measurement location.

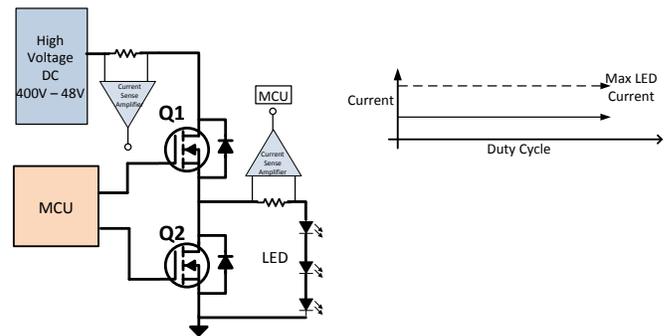

**Figure 3. Analog dimming using current sense amplifier**

**Alternate Device Recommendations**

The LMP8646 is a precision current limiter used to improve current limit accuracy of any switching or linear regulator that can directly be connected to the feedback node of the regulator. The LMP8646 can support from a common mode range fo -2V to 76V making it ideal for 48V/60V systems. The LMP8646 has an adjustable bandwidth and gain which can be set by external capacitors and resistors respectively. The output stage of the LMP8646 is a current source only making it ideal to be connected to feedback node of the switching regulator.

**Table 1. Alternate Device Recommendations**

Device	Optimized Parameter	Performance Trade-Off
INA168	Bandwidth : 800kHz, Package: SOT-23	Adjustable gain, external components
LMP8601	V <sub>CM</sub> -22V to 60V	Offset voltage: 1mV, bandwidth: 60kHz
INA282	DC CMRR: 140dB	Bandwidth: 10kHz

**Table 2. Related TI TechNotes**

SBOA174	Current Sensing in an H-Bridge
SBOA176	Switching Power Supply Current Measurements
SBOA166	High-Side Drive, High-Side Solenoid Monitor With PWM Rejection

## IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2017, Texas Instruments Incorporated