


Half-wave rectifier circuit

Design Goals

Input		Output		Supply	
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}
$\pm 0.2mV_{pp}$	$\pm 4V_{pp}$	$0.1V_p$	$2V_p$	2.5V	-2.5V

Design Description

The precision half-wave rectifier inverts and transfers only the negative-half input of a time varying input signal (preferably sinusoidal) to its output. By appropriately selecting the feedback resistor values, different gains can be achieved. Precision half-wave rectifiers are commonly used with other op amp circuits such as a peak-detector or bandwidth limited non-inverting amplifier to produce a DC output voltage. This configuration has been designed to work for sinusoidal input signals between $0.2mV_{pp}$ and $4V_{pp}$ at frequencies up to 50kHz.

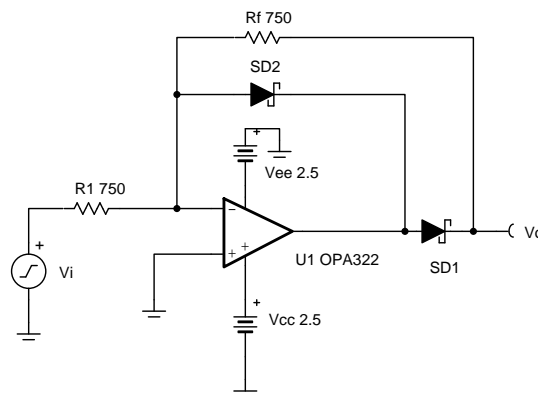

Design Notes

1. Select an op amp with a high slew rate. When the input signal changes polarities, the amplifier output must slew two diode voltage drops.
2. Set output range based on linear output swing (see A_{ol} specification).
3. Use fast switching diodes. High-frequency input signals will be distorted depending on the speed by which the diodes can transition from blocking to forward conducting mode. Schottky diodes might be a preferable choice, since these have faster transitions than pn-junction diodes at the expense of higher reverse leakage.
4. The resistor tolerance sets the circuit gain error.
5. Minimize noise errors by selecting low-value resistors.

Design Steps

1. Set the desired gain of the half-wave rectifier to select the feedback resistors.

$$V_o = \text{Gain} \times V_i$$

$$\text{Gain} = - \frac{R_f}{R_1} = - 1$$

$$R_f = R_1 = 2 \times R_{eq}$$

- Where R_{eq} is the parallel combination of R_1 and R_f

2. Select the resistors such that the resistor noise is negligible compared to the voltage broadband noise of the op amp.

$$E_{nr} = \sqrt{4 \times k_b \times T \times R_{eq}}$$


$$R_{eq} \leq \frac{E_{nbb}^2}{4 \times k_b \times T \times 3^2} = (E_{nbb})$$

$$= 7.5 \frac{\text{nV}}{\sqrt{\text{Hz}}} = \frac{(7.5 \times 10^{-9})^2}{4 \times 1.381 \times 10^{-23} \times 298 \times 3^2} = 380\Omega$$


$$R_f = R_1 \leq 760\Omega \rightarrow 750\Omega \text{ (Standard Value)}$$

Design Simulations


DC Simulation Results

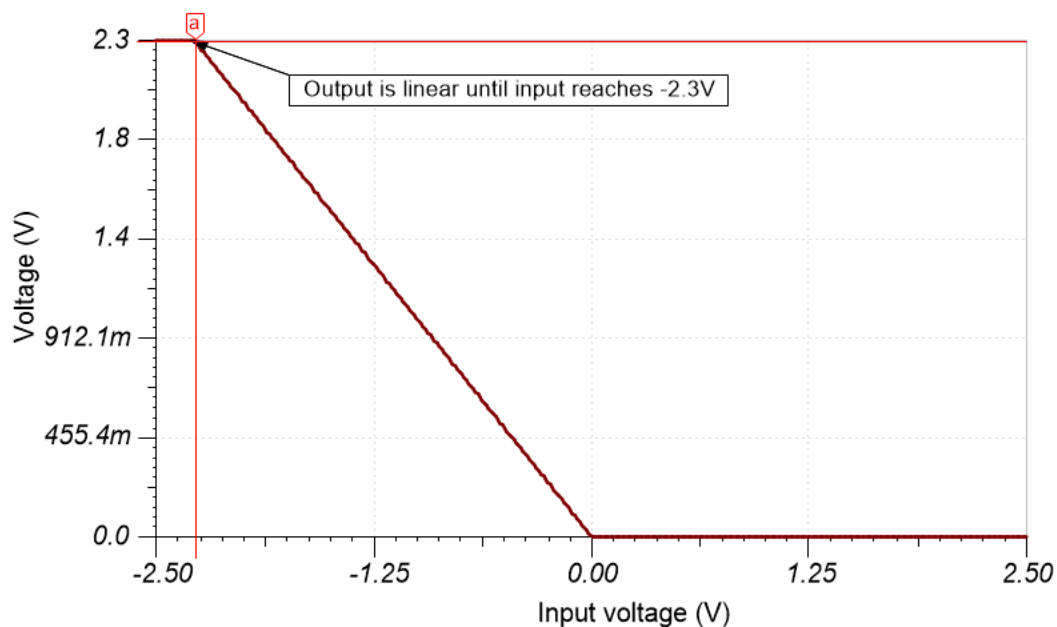

Transient Simulation Results

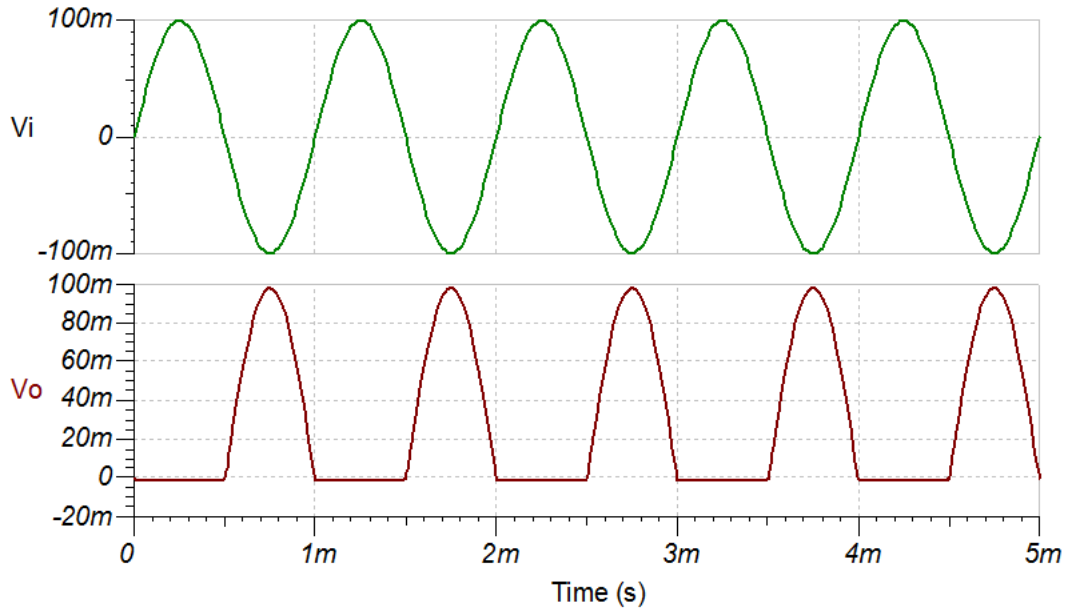

200mV_{pp} at 1kHz

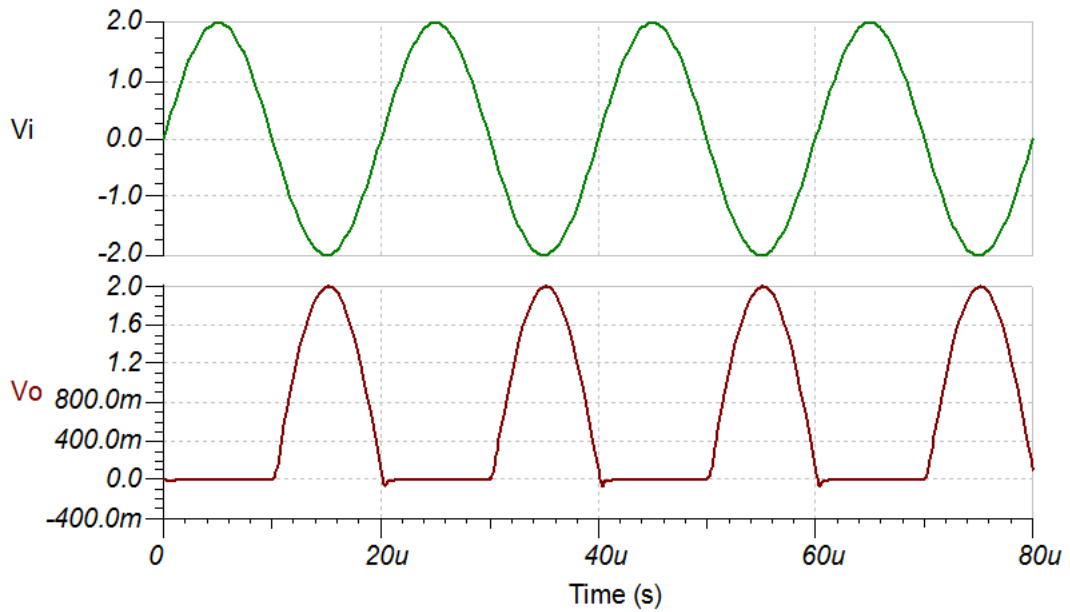

2V_{pp} at 50kHz

Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

See circuit SPICE simulation file [SBOC509](#).

Design Featured Op Amp

OPA322	
V_{SS}	1.8V to 5.5V
V_{inCM}	Rail-to-rail
V_{out}	Rail-to-rail
V_{OS}	500 μ V
I_q	1.6mA/Ch
I_b	0.2pA
UGBW	20MHz
SR	10V/ μ s
#Channels	1, 2, 4
www.ti.com/product/opa322	

Design Alternate Op Amp

OPA2325	
V_{SS}	2.2V to 5.5V
V_{inCM}	Rail-to-rail
V_{out}	Rail-to-rail
V_{OS}	40 μ V
I_q	0.65mA/Ch
I_b	0.2pA
UGBW	10MHz
SR	5V/ μ s
#Channels	2 μ
www.ti.com/product/opa2325	

Revision History

Revision	Date	Change
A	January 2019	Downscale the title and changed title role to 'Amplifiers'. Added link to circuit cookbook landing page and link to Spice simulation file.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](#) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated