



Carmen Parisi

## ABSTRACT

This application report covers the basics of multiphase buck regulators. A comparison versus single-phase regulators is presented before diving into a detailed design example aimed at powering the core rail of a generic networking ASIC setting up a second application report discussing printed-circuit board (PCB) layout techniques and performance testing.

## Table of Contents

<b>1 Introduction</b> .....	2
<b>2 Multiphase Buck Regulator Overview</b> .....	2
<b>3 Advantages of Multiphase Regulators</b> .....	4
<b>4 Multiphase Challenges</b> .....	9
<b>5 Multiphase Design Example - Component Selection</b> .....	10
<b>6 Conclusion</b> .....	17
<b>7 References</b> .....	18
<b>8 Revision History</b> .....	18

## List of Figures

Figure 2-1. Multiphase Regulator Example.....	2
Figure 2-2. TPS53679 Demo Board With Controller and Power Stage ICs Highlighted.....	3
Figure 3-1. Input Current Waveforms.....	4
Figure 3-2. Normalized Input Capacitance RMS Current.....	5
Figure 3-3. Inductor Ripple Current Waveforms.....	6
Figure 3-4. Normalized Output Capacitance Ripple.....	7
Figure 3-5. Efficiency vs Phase Number.....	8
Figure 3-6. TPS53661 5-PH Efficiency Curve.....	8
Figure 4-1. Simplified Comparison Between Current Sense Methods.....	9
Figure 5-1. Capacitor Derating Curves Courtesy of Murata Left: 1210 Case, GRM32ER61C226ME20L, Right: 1206 Case, GRM31CR61C226ME15.....	13
Figure 5-2. Load Transient Waveforms.....	14
Figure 5-3. Load Transient with DC Load Line.....	15

## List of Tables


Table 5-1. Multiphase Design Targets.....	10
Table 5-2. Summary of Driver and FET Implementations.....	11
Table 5-3. Power Stage Loss Calculations per Phase.....	12
Table 5-4. Output Capacitor Options.....	15
Table 5-5. Output Capacitor Solution Comparison.....	15
Table 5-6. Multiphase Design Comparison.....	16
Table 5-7. Case Study Design Summary.....	16

## 1 Introduction


In today's computing environment CPUs, FPGAs, ASICs, and even peripherals are growing increasingly complex. In turn so do their power delivery requirements. To handle the higher demands, multiphase regulators are becoming more common on motherboards in many areas of computing from laptops and tablets to servers and Ethernet switches. Designing with these regulators is more challenging than using conventional switchers and linear regulators but the benefits of multiphase outweigh the complexity for high-performance power applications. This tutorial is designed to provide the necessary equations and guidance to get a new multiphase design up and running and ready for validation. After an overview of multiphase benefits, an in-depth design example of a multiphase buck regulator for an ASIC core rail is presented. Part 1 of this series focuses on the design specifications and component selection. Part 2 covers the PCB layout and basic performance testing.

## 2 Multiphase Buck Regulator Overview

A multiphase buck regulator is a parallel set of buck power stages as shown in [Figure 2-1](#) and [Figure 2-2](#), each with its own inductor and set of power MOSFETs. Collectively, these components are called a phase. These phases are connected in parallel and share both input and output capacitors. During steady-state operation, individual phases are active at spaced intervals equal to  $360^\circ / n$  throughout the switching period where  $n$  is the total number of phases. [Figure 2-2](#) shows a TPS53679 multiphase controller demonstration board and TI power stages for a six-phase design.

 

**Figure 2-1. Multiphase Regulator Example**

 

**Figure 2-2. TPS53679 Demo Board With Controller and Power Stage ICs Highlighted**

Today's controllers most commonly support applications needing two to eight phases. Techniques exist to extend the phase count to 12 or more, but these are outside the scope of this document. As a general guideline, the maximum phase current should be kept between 30 to 40 A. Depending on budget, efficiency targets, and available cooling methods the maximum phase current can be increased but it is highly recommended to do a thorough study of the ramifications before committing to the design.


### 3 Advantages of Multiphase Regulators

Compared to single-phase buck regulators, multiphase converters offer several key performance advantages that make them the default choice for high-power, high-performance applications:

- Reduced input capacitance
- Reduced output capacitance
- Improved thermal performance and efficiency at high load currents
- Improved overshoot and undershoot during load transients

#### 3.1 Input Capacitance Reduction

Adding additional phases to a design decreases the RMS input current flowing through the decoupling capacitors thereby reducing the ripple on the input voltage,  $V_{IN}$ . Fewer capacitors are then needed to keep  $V_{IN}$  ripple within specifications. Self-heating effects within the capacitors themselves due to equivalent series resistance (ESR) are also reduced.

 

**Figure 3-1. Input Current Waveforms**


Figure 3-1 shows the input current waveforms for a two-phase buck compared to a single-phase design (dashed line). Lower RMS and peak currents from the addition of a second phase not only reduces the input capacitance,  $C_{IN}$ , but also provides less stress on the upper MOSFET of each phase.

$$I_{CIN_{norm}(RMS)} = \sqrt{\left(D - \frac{m}{n}\right) \times \left(\frac{1+m}{n} - D\right)} \quad (1)$$

where

- $D = V_{OUT} / V_{IN}$
- $n = \#$  of phases
- $m = \text{floor}(n \times D)$

Calculating the normalized RMS input current of a regulator can be done using the formula in Equation 1. Plotting this equation as a function of duty cycle and phase number gives the curves in Figure 3-2. These graphs show a higher phase count can reduce the amount of current the input capacitors have to handle by 50% or more depending on the duty cycle.

 


**Figure 3-2. Normalized Input Capacitance RMS Current**

At several points on the graphs in [Figure 3-2](#), the input RMS current drops to zero as the individual ripple currents for each phase cancel one another out. While mathematically it may be possible set the phase number and duty cycle of a design to operate at a zero current point and eschew input caps altogether, in reality this is unachievable. Noise, line transients, load transients, and natural variations in the duty cycle make no input current ripple unrealizable in practice. Spacing between phases can reach several inches for 4+ phase designs causing PCB inductance to reduce the effects of ripple cancellation and so capacitors must always be used.

### 3.2 Output Capacitance Reduction


Because all phases of a multiphase design are tied together at the output node, the inductor currents of each phase are concurrently charging and discharging the output capacitors depending on whether or not a given phase is active. This charging and discharging produce one overall current,  $I_{SUM}$ , the AC portion of which gets absorbed by the output capacitance,  $C_{OUT}$ . Compared to the ripple current of an individual phase  $I_{SUM}$  has a lower peak-to-peak value in steady state as shown in [Figure 3-3](#). Smaller ripple current in the output capacitors lowers the overall output voltage ripple which in turn lowers the amount of capacitance needed to keep  $V_{OUT}$  within tolerance.

 

**Figure 3-3. Inductor Ripple Current Waveforms**

The normalized ripple current for the output capacitors is calculated using [Equation 2](#) and plotted in [Figure 3-4](#) for two-, three-, and four-phase buck converters. Setting  $n = 1$  gives  $I_{COUT_{norm}} = 1$  for all duty cycles making [Equation 2](#) invalid for single-phase calculations. Much like with the input capacitor current, at various duty cycles the currents of the inductors mathematically cancel out suggesting no output current ripple. Even when designed to operate at one of these points, a converter always requires some amount of output capacitance due to noise, transients, and duty cycle variation. However, for fixed output applications, operating near one of these zero points leads to an optimal design with the fewest number of output capacitors.

$$I_{COUT_{ripple,norm}} = \frac{n}{D \times (1-D)} \times \left( D - \frac{m}{n} \right) \times \left( \frac{1+m}{n} - D \right) \quad (2)$$

 

**Figure 3-4. Normalized Output Capacitance Ripple**


Unlike with input ripple cancellation, output ripple cancellation is less affected by the PCB layout. Usually, a significant number of output capacitors are tightly packed close to the CPU or point of load reducing the effects of parasitic inductance between components. Also, the inductor value of each phase dominates parasitics for all but the highest frequency designs allowing for better cancellation between phases.

### 3.3 Thermal Performance and Efficiency Improvements

Single-phase converters by definition have all the output power flowing through a single inductor and pair of FETs. Any power loss is contained solely within those components. For an application with greater than 100 A of output current, sourcing FETs and inductors rated to such large currents becomes difficult and expensive. Concentrating the entirety of the losses of a design into one small area of a PCB and set of components comes at an undesirable loss of efficiency.

Multiphase regulators spread power loss evenly across all phases. Since each phase is dealing with only a portion of the total output current, selecting FETs and inductors becomes easier as less thermal strain is placed on these components. Regulator efficiency is also able to remain much higher over the entire load range when compared to an equivalent single-phase design. Performance is further improved by the reductions in  $C_{IN}$  and  $C_{OUT}$  discussed previously as lower ripple current in the capacitors produces less self-heating and lower power loss.


Modern DC/DC controllers allow for phases to be added and dropped as needed depending on the load current as shown in [Figure 3-5](#). These add and drop points can be tuned to account for various FET and inductor combinations for optimal efficiency across many applications and conditions.

 

**Figure 3-5. Efficiency vs Phase Number**

At low currents, fewer phases are used, down to a single phase operating in *Discontinuous Conduction Mode*, to minimize the FET switching losses and the current draw associated with the power stage and gate drivers of each phase. As the load current increases, conduction losses begin to dominate over switching loss and more phases are activated to keep the efficiency as high as possible. The optimum set point to turn on a phase occurs at the intersection of two efficiency curves. For example, phase two should be turned on where the falling single-phase efficiency curve crosses the rising two-phase efficiency curve.

Figure 3-6 depicts an efficiency curve taken of a five-phase design using the TPS53661 controller and CSD95372B power stage. The design called for  $V_{IN} = 12\text{ V}$ ,  $V_{OUT} = 1.8\text{ V}$ , used a switching frequency of 600-kHz and 150-nH inductors. An efficiency > 90% is maintained from 5 A to 200 A, a feat which for all intents and purposes is impossible to do with only a single-phase buck.

 

**Figure 3-6. TPS53661 5-PH Efficiency Curve**

### 3.4 Transient Response Improvements

In many high-performance applications the capacitance requirements demanded by load transients far exceed what is called for to successfully hit DC ripple targets. During load transients multiphase converters offer the advantage of needing fewer output capacitors to keep  $V_{OUT}$  within the specifications of a given design.

During a transient a multiphase controller overlaps phases during a load step or turns all phases off during a load release, effectively putting the inductors in parallel with one another. This reduces equivalent inductance, ( $L_{EQ}$ ) seen at the output node by a factor of  $n$ , where  $n$  is the total number of phases. With a smaller  $L_{EQ}$ , charge can quickly be supplied from the supply to the output caps reducing undershoot. Similarly, overshoot is reduced as less excess charge stored in the inductors is transferred to the output capacitors when the phases are all shut off.

## 4 Multiphase Challenges

While multiphase bucks offer many benefits over single-phase converters, they do present some challenges that must be overcome in order to successfully implement a design. Adding additional phases to a converter increases bill of materials (BOM) cost and PCB area. The price of more inductors and FETs must be weighed against the increased cost of sourcing more robust components and needing higher capacitor counts to implement a single-phase regulator instead. To minimize the greater board area needed for multiphase solutions, a balance between current capabilities and thermal performance versus overall phase number must be found.

Perhaps the biggest challenge of multiphase converters is phase management. In order to achieve the highest possible performance, current must be evenly balanced between active phases to avoid thermally stressing any one phase and provide optimal ripple cancellation. Additionally, phases must be quickly added or removed during transients to minimize excursions on the output voltage. Keeping the phases balanced requires a more sophisticated controller versus a single-phase buck. The sophistication comes from more sense lines, signal routing, current sense components, and so forth, that must be fed back to the controller in order to accurately balance phase currents.

Determining the phase current is traditionally done through a current sense resistor in series with each inductor or by utilizing the parasitic DC resistance (DCR) of the inductor. These methods are sensitive to component placement and signal routing making implementation difficult. The sense circuitry for each phase requires additional passive components to provide filtering and in the case of resistor sensing, adds an additional point of power loss. However, *Smart Power Stages*, such as the CSD95372B and CSD95490, have recently hit the market integrating current sense capabilities directly in the Driver-MOSFET package. When paired with a compatible controller, these ICs offer increased current sense accuracy, eliminate a number of passive components, and require fewer differential signals, if any, to be routed across the PCB as seen in [Figure 4-1](#).

 


Figure 4-1. Simplified Comparison Between Current Sense Methods

## 5 Multiphase Design Example - Component Selection

To illustrate the benefits of multiphase buck regulators a design using the specifications in [Table 5-1](#) is worked through from initial component selection, to PCB layout, and finally performance testing. Only the initial design is currently discussed; layout and testing are the subjects of a future application report. While working through the design process component count, efficiency, and layout complexity are studied to strike a balance between performance and ease of implementation.

**Table 5-1. Multiphase Design Targets**

$V_{IN}$	12 V	Input Voltage
$V_{OUT}$	0.9 V	Nominal Output Voltage
$I_{TDC}$	200 A	Thermal Design Current
$I_{MAX}$	240 A	Max Current
$I_{STEP}$	150 A	Max Load Step
$D_{CLL}$	0.5 m $\Omega$	DC Load Line
$\Delta V_{OUT(DC)}$	$\pm 1\%$	$V_{OUT}$ DC Ripple
$\Delta V_{OUT(AC)}$	$\pm 5\%$	$V_{OUT}$ Transient Specifications
$\Delta V_{IN(DC)}$	240 mVpp	$V_{IN}$ DC Ripple
$\Delta V_{IN(AC)}$	$\pm 360$ mV	$V_{IN}$ Overshoot and Undershoot
<b>PMBus with Telemetry</b>	Yes	Requires PMBus interface with $V_{IN}$ , $I_{IN}$ , $V_{OUT}$ , $I_{OUT}$ , and Temp readings

The requirements in [Table 5-1](#) are typical specifications for the core voltage rail of a generic networking ASIC that may be found on an enterprise motherboard. Most of the specifications are fairly straightforward to anyone who has done a DC/DC switcher design before with the possible exception of the DC load line and PMBUS requirements.

With a DC load line, a buck regulator essentially presents itself as a fixed resistance to the output load. From the example numbers - with a 200-A load being pulled by the ASIC the nominal output voltage of 0.9 V drops by  $200 \text{ A} \times 0.5 \text{ m}\Omega$ , or 100 mV, to 0.8 V. This lowers the power consumption of the processor by 20 W, easing the strain on whatever heatsink or thermal solution is in place. This 20 W difference is not dissipated by the regulator; it simply is not drawn from the input supply. When the load current drops below 200 A the output voltage rises accordingly. Load lines also make meeting the transient specifications much easier by reducing the amount of output caps needed, as discussed in [Section 5.5](#).

*Power Management Bus* or, PMBus™, is an open, industry standard interface based on I2C that can be found on many modern single and multiphase regulators. When implemented, the bus allows for easy adjustment of the output voltage, reporting of load conditions and FET temperature, as well as fault recording. If a digital or hybrid modulator is used in the controller PMBus can also be used to change the compensation of a converter during design validation.

### 5.1 Phase Count

With a 200-A TDC and 240-A maximum current, the design requires six phases to keep the individual phase currents below 40 A. Four- and five-phase designs result in TDC current levels that make power loss through the inductors and FETs difficult to manage. Conversely, a six-phase solution only has 33 A flowing per phase at  $I_{TDC}$  and 40 A while at  $I_{MAX}$ , providing a more manageable power loss scenario. The additional phases also provide a significant reduction in the amount of capacitors required to maintain regulation during load transients which can be seen in [Table 5-6](#) of the *Design Summary* section.

### 5.2 Inductor

To choose an inductor, the switching frequency must first be decided. Frequencies around 300 kHz can provide low switching loss and high efficiency at the price of slow transient response as larger inductors are needed and the control loop bandwidth must be set lower than it otherwise would be at higher frequencies. Similarly, higher switching frequencies around 1 MHz suffer from greater switching loss but offer faster transient response.

For this design, a switching frequency of 600 kHz is used to provide a balanced tradeoff between transient response and efficiency. Using the standard buck design equation for calculating inductance and a ripple current

target of 25%, an inductance of 0.138  $\mu\text{H}$  per phase is calculated using Equation 3. Rounding towards the closest standard value gives an inductance of 0.15  $\mu\text{H}$  per phase.

$$L = \frac{V_{\text{OUT}} \times (1 - D)}{f_{\text{SW}} \times I_{\text{PP}}} = \frac{0.9 \text{ V} \times \left(1 - \frac{0.9 \text{ V}}{12 \text{ V}}\right)}{600 \text{ kHz} \times \left(0.25 \times \frac{240 \text{ A}}{6}\right)} = 0.138 \mu\text{H} \quad (3)$$

The inductor for this design was chosen from the popular IHLF line of inductors from Vishay Dale, specifically the IHLF-5050FD series. The 150-nH choke from this series has a typical DCR of 0.53 m $\Omega$  for low conduction losses as well as minimal AC loss that can be estimated using the Vishay online calculator. It is also thermally rated out to 55 A, providing margin since only 40 A per phase is expected.

The soft saturation curve of the powdered core on this inductor means the inductance remains relatively flat out to its saturation current rating before slowly rolling off giving predictable performance over the range of expected operating conditions. Should a severe over-current event occur above the saturation current rating, a powdered core makes damage to the FETs and PCB much less likely than with a ferrite core. With a ferrite core, the inductance drops off quickly at the saturation point and the inductor essentially becomes a short which can pull a damaging amount of current.

### 5.3 Driver and Power MOSFETs

When working through a multiphase design there are three options available to a designer when it comes to deciding how to implement the controller, drivers, and power MOSFETs. Table 5-2 summarizes the general pros and cons of each option.

1. Discrete ICs for the controller, MOSFET drivers, and FETs
2. A controller with integrated drivers and discrete FETs
3. A driverless controller with the FETs and IC combined into one IC package

Option 1 offers the most design flexibility, provided common footprints are used, as the FETs and drivers can be swapped out easily if requirements change. The controller sends a PWM signal out to each driver IC which then converts the signal into the upper and lower gate drive signals for the MOSFETs. This option may also prove to be the cheapest since the individual ICs themselves are neither highly integrated nor sophisticated. However, going with an all discrete solution places the optimization of the driver-FET combination on the designer which increases the design complexity and may not be an option in a time-constrained scenario. Performance is also much more affected by the PCB layout as opposed to more integrated solutions as there are a greater number of high-power nodes, drive signals, and sense lines to route along with additional parasitic elements.

Option 2 restricts the design freedom an engineer has since the drivers are paired with the controller and may not be suitable for driving all possible FETs. It also requires that the controller be located relatively close to the phases because the gate signals cannot be run for long distances without compromising performance. Layout area and complexity compared to an all discrete solution depends on the phase count. As the phase count increases, the controller size balloons out as at least four additional pins per phase (*Upper Gate Drive*, *Lower Gate Drive*, *Phase Sense*, and *Boot*) are needed. For designs greater than two or three phases, maintaining a proper layout with this option becomes difficult at best. Finding a controller that supports a high phase count with integrated drivers may not be possible at all. Stacking multiple controllers together only further complicates the design.

Option 3 provides the easiest design and layout at the expense of BOM cost because of the high integration in the ICs. Only PWM signals are sent between the controller and driver-FET IC. No gate drive signal routing is required. This option also provides the optimal driver FET combination, with the lowest parasitics, translating into higher efficiency and a lower chance of shoot-through. If telemetry data for parameters such as input current, output current, and temperature are required, these features can be easily added into a driver-FET power stage instead of requiring additional discrete circuitry.

**Table 5-2. Summary of Driver and FET Implementations**

Design Parameter	Option 1 – Discrete Solution	Option 2 – Controller+Driver with FETs	Option 3 – Controller with Driver+FET
Flexibility	High	Average	Average

**Table 5-2. Summary of Driver and FET Implementations (continued)**

Design Parameter	Option 1 – Discrete Solution	Option 2 – Controller+Driver with FETs	Option 3 – Controller with Driver+FET
BOM Cost	Low	Phase # Dependent	High
Complexity	High	High	Low
Density	Low	Phase # Dependent	High
Performance	Average	Average	High

For the current design, Option 2 can be eliminated right away. A controller and driver package that can handle six phases does not exist and stacking multiple controllers adds unneeded complexity when controllers exist with six PWM outputs. Option 1 looks attractive because of the potential for a cheaper BOM cost but the PCB area needed to layout a driver, FETs, and associated passives, multiplied by six phases increases the board area and raises the cost of its production and assembly.

Choosing Option 3 reduces the overall component count and provides for the simplest board layout. It also eliminates the challenge of selecting an optimal pair of FETs and drivers to use for each phase, a topic that merits its own application note ([Multiphase Buck Regulator Portal](#)). Choosing a *Smart Power Stage* provides support for PMBus telemetry by integrating the needed circuitry on the chip.

Two possible options for power stages to consider for this design are the CSD95372AQ5M and the CSD95490Q5MC. Each stage is rated for a continuous current of 60 A and 75 A respectively, and supports the input/output voltages required, can switch at 600 kHz, and has a built in temperature monitor pin. Both parts come in low inductance packages to reduce parasitics that can affect steady-state switching and transient response. Finally, both are compatible with 3.3-V and 5-V PWM signals allowing for more flexibility when choosing a controller IC.

Upon closer inspection, the CSD95490Q5MC proves to be a better fit for powering the networking ASIC. No DCR matching or resistor sense filter circuit is needed, thanks to the integrated bi-directional current-sense capability, removing six differential current sense signals routed back to the controller. An amplified, single-ended, current sense signal per phase is reported back instead. Because this current sense signal is amplified at the power stage it is much less susceptible to corruption from noise and other switching signals simplifying the circuit layout. A single resistor value on the LSET pin is all that is needed to properly configure this part. Additionally, a small amount of power loss is eliminated because a minimum sense resistor or DCR value is no longer needed to keep the sense signal SNR high enough to accurately balance the phase currents.

Most importantly, the CSD95490Q5MC has much lower power loss than the CSD95372AQ5M under identical conditions. Power loss is calculated at 33 A (TDC) and 40 A (maximum) and shown in [Table 5-3](#) using the loss curves in both data sheets for the following conditions:  $V_{IN} = 12\text{ V}$ ,  $V_{OUT} = 0.9\text{ V}$ ,  $f_{SW} = 600\text{ kHz}$ ,  $L = 150\text{ nH}$ ,  $T_J = 100^\circ\text{C}$ . With losses 1.4 W less per phase at TDC and 3 W less at maximum current, the CSD95490Q5MC is the clear choice.

**Table 5-3. Power Stage Loss Calculations per Phase**

Phase Current	CSD95490Q5MC	CSD95372AQ5M
33 A (TDC)	3.36 W	4.71 W
40 A (MAX)	4.56 W	7.54 W

## 5.4 Input Capacitors

Typically input capacitor requirements are met via a combination of multi-layer ceramic capacitors (MLCCs) and either aluminum or polymer electrolytic bulk capacitors. The MLCCs are sized to handle the RMS current and DC ripple in steady-state conditions while the bulk capacitance is used to provide charge and keep  $V_{IN}$  within tolerance during load transients.

To calculate the number of MLCCs simply multiply the RMS current value calculated from [Equation 1](#) by the maximum current and divide by RMS current rating for an individual MLCC, rounding up to the nearest whole number. Capacitor current rating can be obtained from the manufacturer's website. The RMS input current for this application is 19.9 Arms. A 22- $\mu\text{F}$ , X5R, 1210, 16-V capacitor is rated at approximately 5 A of RMS ripple current at 600 kHz with a  $20^\circ\text{C}$  rise. Under these conditions, four total capacitors would be needed to carry the current.


Equation 4 calculates the amount of ceramic capacitance per phase needed to keep the input voltage ripple within its limits. In order to get a better estimate of the capacitance required the duty cycle can be divided by the target efficiency,  $\eta$ , at the maximum phase current in order to get an adjusted duty cycle term,  $D_{ADJ}$ .

$$C_{IN\text{phase}} = \frac{I_{PHASE\text{max}} \times D_{ADJ} \times \eta(1 - D_{ADJ})}{f_{SW} \times \Delta V_{IN(DC)}} = \frac{40\text{A} \times 0.0882 \times (1 - 0.0882)}{600\text{kHz} \times (240\text{mVpp})} = 22.3\mu\text{F} \quad (4)$$

where

- $D_{ADJ} = V_{OUT} / V_{IN} \times \eta$

Assuming a conservative efficiency of 85%,  $\eta = 0.85$ , at 40 A, a minimum of 22  $\mu\text{F}$  is needed to keep  $V_{IN}$  within tolerance. You may initially think only one ceramic capacitor is needed per phase to hit both the ripple and RMS current requirements but the derating of each capacitor as a function of the DC bias voltage proves otherwise. From Figure 5-1, a single 1210, 22- $\mu\text{F}$  capacitor derates to approximately 15  $\mu\text{F}$  with a 12-V bias. Taking this into account, two 22- $\mu\text{F}$  capacitors per phase are needed to meet the input ripple requirements. Using identical capacitors from the same vendor but in a smaller 1206 package, a 22- $\mu\text{F}$  capacitor derates to about 5  $\mu\text{F}$  at 12 V, requiring four capacitors per phase instead of two.

 

**Figure 5-1. Capacitor Derating Curves Courtesy of Murata Left:1210 Case, GRM32ER61C226ME20L, Right: 1206 Case, GRM31CR61C226ME15**

Choosing a bulk capacitor to decouple the input voltage is more of an art than a science. Equations can give an engineer a starting point for a design but ultimately the performance must be verified on the board during validation. A tradeoff must be made between minimizing the ESR spike caused by the bulk capacitor while at the same time maintaining a high enough resistance to dampen any oscillations caused by ceramic capacitor ringing during a transient.

For this design, the process outlined in the [How to Select Input Capacitors for a Buck Converter Technical Brief](#) is used to get a starting bulk capacitance value assuming a 10-kHz bandwidth for the 12-V bus regulator. After completing the process, 550  $\mu\text{F}$  should be the minimum capacitance with an ESR of less than 27 m $\Omega$ . Two 330- $\mu\text{F}$ , 16-V, 20-m $\Omega$  Aluminum polymer capacitors are used as bulk decoupling on  $V_{IN}$ .

Additionally, a single 0.33- $\mu\text{F}$ , 0603 ceramic capacitor is placed on each phase to help suppress ringing on the phase node and reduce the requirements of a snubbing circuit should testing reveal one to be needed.

## 5.5 Output Capacitors


Calculating the output capacitance requires taking into account both the DC ripple and AC transient specifications of an application. As previously discussed, the AC transient requirements are typically more demanding than the DC ripple specifications and dictate how much total output capacitance is needed. Just as when choosing input capacitors, a mix of MLCCs and bulk caps are used.

Ceramic capacitors keep the output impedance of the converter low before the control loop can respond during fast transients, minimizing overshoot and undershoot. Bulk capacitors provide enough of a charge reservoir for the output voltage to stay within tolerance as the controller ramps the inductor current the new load current level.

Assuming minimal ESR and ESL in the capacitor network, the amount of output capacitance needed to handle the DC ripple can be calculated using Equation 5. In this equation,  $I_{PP}$  is the ripple current for a single phase of the converter (calculated using the 150nH inductor value) as there is no inductor current cancellation in single-phase operation making it the worst-case scenario.

$$C_{OUT,Ripple} = \frac{I_{PP}}{8 \times f_{sw} \times \Delta V_{OUT(DC)}} = \frac{9.25 A_{PP}}{8 \times 600 \text{ kHz} \times (0.01 \times 0.9 \text{ V})} = 214 \mu\text{F} \quad (5)$$

Figure 5-2 and Equation 6 to Equation 9 explain the process behind calculating starting capacitance values needed to handle load transients. During a load step the inductance,  $L$  or  $L_{EQ}$  – depending on the total phase number – takes some amount of time,  $t_{Undershoot}$ , to slew to the high current level. In that time, an amount of charge equal to  $Q_{Undershoot}$  is pulled from the output capacitors while  $V_{OUT}$  dips below its set point. Upon load release, excess charge in the inductor,  $Q_{Overshoot}$ , is dumped into the output capacitors during time  $t_{Overshoot}$ , causing  $V_{OUT}$  to swing above its regulation point.

 

**Figure 5-2. Load Transient Waveforms**

$$t_{UNDERSHOOT} = \frac{L_{EQ} \times I_{STEP}}{V_{IN} - V_{OUT}} = \frac{150 \text{ nH} \times 150 \text{ A}}{12 \text{ V} - 0.9 \text{ V}} = 338 \text{ ns} \quad (6)$$

$$Q_{UNDERSHOOT} = \frac{1}{2} \times t_{UNDERSHOOT} \times I_{STEP} = \frac{1}{2} \times 338 \text{ ns} \times 150 \text{ A} = 25.35 \mu\text{C} \quad (7)$$

$$t_{OVERSHOOT} = \frac{L_{EQ} \times I_{STEP}}{V_{OUT}} = \frac{150 \text{ nH} \times 150 \text{ A}}{0.9 \text{ V}} = 4.16 \mu\text{s} \quad (8)$$

$$Q_{OVERSHOOT} = \frac{1}{2} \times t_{OVERSHOOT} \times I_{STEP} = \frac{1}{2} \times 4.3 \mu\text{s} \times 150 \text{ A} = 312.5 \mu\text{C} \quad (9)$$

After calculating  $Q_{Overshoot}$  and  $Q_{Undershoot}$ , finding the output capacitance is simply a matter of dividing the charge by the allowable swing on  $V_{OUT}$ . The current design specifies a DC load line which must be taken into account as shown in Figure 5-3. The total capacitance needed to handle the maximum transient of the application is calculated in Equation 10 for the load step and Equation 11 for the load release. For applications without a DC load line, simply set  $DCLL = 0$ .

 


Figure 5-3. Load Transient with DC Load Line

$$C_{\text{UNDERSHOOT}} = \frac{Q_{\text{UNDERSHOOT}}}{\Delta V_{\text{OUT(AC)}} + I_{\text{STEP}} \times \text{DCLL}} = \frac{25.35 \mu\text{C}}{0.05 \times 0.9\text{V} + 150 \text{A} \times 0.5 \text{m}\Omega} = 211.1 \mu\text{F} \quad (10)$$

$$C_{\text{OVERSHOOT}} = \frac{Q_{\text{OVERSHOOT}}}{\Delta V_{\text{OUT(AC)}} + I_{\text{STEP}} \times \text{DCLL}} = \frac{312.5 \mu\text{C}}{0.05 \times 0.9 \text{V} + 150 \text{A} \times 0.5 \text{m}\Omega} = 2,604 \mu\text{F} \quad (11)$$

Comparing the values calculated for  $C_{\text{Ripple}}$ ,  $C_{\text{Undershoot}}$ , and  $C_{\text{Overshoot}}$ , the load release dictates the amount of capacitance needed to keep  $V_{\text{OUT}}$  within regulation.  $C_{\text{Overshoot}}$  comes out to be much greater than  $C_{\text{Undershoot}}$  because during load release, less energy is required by the processor and so any excess stored in the inductor gets transferred to the output capacitors causing  $V_{\text{OUT}}$  to overshoot. During a load step the processor is pulling energy from the capacitors and the energy stored in the inductor refills them helping mitigate undershoot.

Table 5-4 and Table 5-5 are used to come up with a mix of output capacitors that can satisfy the transient requirements while balancing component count and BOM cost. Table 5-4 compares the prices and specifications of several popular capacitor options while Table 5-5 looks at combinations of capacitors that meet the necessary requirements and can be used as a starting point for the design. Depending on bench results, the amount and type of capacitors may be adjusted. The total capacitance of each option is set higher than  $C_{\text{Overshoot}}$  to provide margin and account for derating on the MLCCs. Since the DC bias on each capacitor is lower than on the input side of the regulator, less derating occurs and the capacitors still retain most of their nominal capacitance.

Table 5-4. Output Capacitor Options

Capacitor Type	Capacitance	Specifications	Price/1000 Units
Ceramic	22 $\mu\text{F}$	0805, 6.3 V, X5R	\$0.054
Ceramic	47 $\mu\text{F}$	0805, 6.3 V, X5R	\$0.131
Organic Polymer	470 $\mu\text{F}$	V-Case, 2.5 V, 6 m $\Omega$	\$1.357
Organic Polymer	680 $\mu\text{F}$	D-Case, 2.5 V, 6 m $\Omega$	\$2.537

Table 5-5. Output Capacitor Solution Comparison

Capacitor Mix	Total Capacitance	Component Count	Price
3 $\times$ 470 $\mu\text{F}$ + 20 $\times$ 47 $\mu\text{F}$ + 25 $\times$ 22 $\mu\text{F}$	2900 $\mu\text{F}$	48	\$8.04
1 $\times$ 680 $\mu\text{F}$ + 32 $\times$ 47 $\mu\text{F}$ + 35 $\times$ 22 $\mu\text{F}$	2950 $\mu\text{F}$	68	\$8.62
2 $\times$ 680 $\mu\text{F}$ + 20 $\times$ 47 $\mu\text{F}$ + 20 $\times$ 22 $\mu\text{F}$	2850 $\mu\text{F}$	47	\$9.04
47 $\times$ 47 $\mu\text{F}$ + 35 $\times$ 22 $\mu\text{F}$	2980 $\mu\text{F}$	82	\$8.05

From Table 5-5, a combination of 470- $\mu\text{F}$  bulk capacitors and MLCCs provide the best balance between component count and price. For applications that may require an all ceramic solution, the component count increases substantially though not necessarily at the expense of BOM cost.

## 5.6 Controller

Studying the TPS53679 Dual-Channel Multiphase Controller data sheet ([SLUSC47](#)) proves it to be a good fit for this ASIC core rail. The D-CAP+ modulator is optimized for multiphase control and keeping the current balanced between phases. Six PWM channels offer a great deal of design flexibility to work with a variety of power stages, including the chosen CSD95490, while minimizing the size of the controller package. Support for PMBus communication checks the box to meet the telemetry specification of the design. The PMBus also enables tuning functionality of the phase add and drop points so that optimal efficiency can be achieved over the whole load range. For a deeper look into the D-CAP+ modulator see the [Synchronous Buck NexFET Power Stage, CSD95372AQ5M Data Sheet](#) and [Enabling Loadline for Memory and ASIC VR Applications to Save Output Capacitors Application Report](#).

As an added bonus, the controller also supports full digital compensation through the PMBus making tuning the design on the board much easier than reworking components on an analog compensation pin. Finally, the second single-phase buck regulator can be used to power any auxiliary rails that the ASIC may require saving money and PCB area.

## 5.7 Design Summary

[Table 5-6](#) gives a comparison of the current six-phase design compared to alternatives using one, two, or four phases with the same power stage and inductor. Fewer phases are not a feasible option for this design when looking at the results. Power loss can be mitigated to some degree by selecting components rated to the higher currents but between component cost, power loss concentration, plus modifications to fans and heatsinks, any benefits from these changes are likely be equivalent when compared to a six-phase solution.

The output capacitance to hit the overshoot requirement drops by thousands of micro-Farads as the phase count increases. Input ceramic capacitor count is also more manageable with a higher phase count.

As an academic exercise, the benefit of a DC load line is shown for each case by recalculating the value of  $C_{\text{Overshoot}}$  after setting  $D_{\text{CLL}} = 0$  from [Equation 11](#). Without a load line,  $V_{\text{OUT}}$  cannot swing more than 45 mV, 5%, in either direction during a 150-A transient. The ability of the ASIC to handle a 0.5-m $\Omega$  load line on its core voltage rail allows  $V_{\text{OUT}}$  to swing an additional 75 mV for the same transient for a total of 120 mV, drastically reducing the output capacitance.

**Table 5-6. Multiphase Design Comparison**

Phases	1	2	4	6	
$I_{\text{IN}}$ (Arms)	63.2	42.8	27.5	19.9	RMS Input Current
$I_{\text{MAX,PH}}$ (A)	240.0	120.0	60.0	40.0	Max Current per Phase
$I_{\text{TDC,PH}}$ (A)	200	100	50	40	Thermal Design Current per Phase
$P_{\text{FET,TDC}}$ (W)	-	-	6.81	3.36	FET Loss @ TDC
$P_{\text{IND,TDC}}$ (W)	-	7.04	2.07	1.15	Inductor Loss @ TDC
$C_{\text{IN,MLCC}}$ ( $\mu\text{F}$ )	134.1	57.0	33.5	22.3	Ceramic Input Capacitance per Phase
$C_{\text{Overshoot}}$ ( $\mu\text{F}$ )	15 625	7812	3906	2604	Output Capacitance to Meet Overshoot
$C_{\text{Overshoot}}$ ( $\mu\text{F}$ )	41 666	20 833	10 416	6944	Output Capacitance to Meet Overshoot, no load line

[Table 5-7](#) displays a brief summary of the major design decisions and components selected for this case study. These components are used in Part 2 of this multiphase series when the PCB is laid out and tested in the lab.

**Table 5-7. Case Study Design Summary**

$V_{\text{IN}}$	12 V
$V_{\text{OUT}}$	0.9 V
$I_{\text{MAX}}$	240 A
TDC	200 A
Phase Count	6
Inductor	150nH, 0.53 m $\Omega$ , 55 A $I_{\text{TEMP}}$
FETs	CSD95490

**Table 5-7. Case Study Design Summary (continued)**

<b>TDC Power Loss</b>	FETs - 20.1 W
	Inductors - 6.87 W
<b>TDC Eff. Estimate</b>	86.9%
<b>C<sub>IN</sub></b>	2 × 330 μF, 10 mΩ, 16 V, Al Poly
	12 × 22 μF, 1210, X5R, 16 V
<b>C<sub>OUT</sub></b>	3 × 470 μF, 6 mΩ, 6.3 V
	20 × 47 μF, 0805, X5R, 2.5 V
	25 × 22 μF, 0805, X5R, 6.3 V
<b>Controller</b>	TPS53679

## 6 Conclusion

After an introduction to the pros and cons of multiphase regulators, a paper design of a high-performance, six-phase buck has been completed. During the design tradeoffs between component count, power loss, ease of design, and BOM cost were made resulting in an optimal solution. Looking forward to the next portion of the tutorial, a PCB based on this design is completed and tested on the bench against the target specifications. For more information on TI's multiphase controllers, both with and without PMBus, visit the web portal referred to in the [D-CAP+™ Control for Multiphase Step-Down Voltage Regulators for Powering Microprocessors Application Report](#).

## 7 References

- Texas Instruments, [Benefits of a Multiphase Buck Converter Technical Brief \(SLYT449\)](#)
- Texas Instruments, [Choosing the Right Variable Frequency Buck Regulator Control Strategy White Paper \(SLUP319\)](#)
- Texas Instruments, [Synchronous Buck NexFET Power Stage, CSD95372AQ5M Data Sheet \(SLPS416\)](#)
- Texas Instruments, [How to Select Input Capacitors for a Buck Converter Technical Brief \(SLYT670\)](#)
- Texas Instruments, [D-CAP+™ Control for Multiphase Step-Down Voltage Regulators for Powering Microprocessors Application Report \(SLVA867\)](#)
- Texas Instruments, [Enabling Loadline for Memory and ASIC VR Applications to Save Output Capacitors Application Report \(SLUA819\)](#)
- Texas Instruments, [CSD95490Q5MC Synchronous Buck NexFET™ Smart Power Stage Data Sheet \(SLPS669\)](#)
- Texas Instruments, [Power Loss Calculation With CSI Consideration for Synchronous Buck Converters Application Note \(SLPA009\)](#)
- [Multiphase Buck Regulator Portal](#)
- [IHLP Inductor Loss Calculator Tool](#)
- [Introduction to the PMBus](#)
- [Under the Hood of a DC/DC Boost Converter Seminar](#)
- Vishay Dale, “Low Profile, High Current IHLP Inductors,” data sheet 34123, 2016

## 8 Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

<b>Changes from Revision A (May 2019) to Revision B (April 2021)</b>	<b>Page</b>
• Updated the numbering format for tables, figures and cross-references throughout the document.....	2
<hr/>	
<b>Changes from Revision * (April 2017) to Revision A (May 2019)</b>	<b>Page</b>
• Edited list of performance advantages.....	4
• Changed "out power" to "output power".....	7
• Added "(calculated using the 150 nH inductor value)".....	13
• Changed the bottom rows in the Multiphase Design Comparison table.....	16

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](http://ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2022, Texas Instruments Incorporated