

# Synchronous rectification boosts efficiency by reducing power loss

By **Anthony Fagnani**  
Power Applications Engineer

## Introduction

Some applications require the highest possible power efficiency. For example, in a harsh environment that requires a DC/DC power supply to operate in high ambient temperatures, low-power dissipation is needed to keep the junction temperature of semiconductor devices within their rated range. Other applications may have to meet the strict efficiency requirements of ENERGY STAR® specifications or green-mode criteria. Users of battery-operated applications desire the longest run time possible, and reducing the power loss can directly improve run time. Today it is well known that using a synchronous rectifier can reduce power loss and improve thermal capability. Designers of buck converters and controllers for step-down applications are already employing this technique. Synchronous boost controllers also have been developed to address power efficiency in step-up applications.

## Typical application

Two typical boost applications can be used to demonstrate the difference between synchronous and nonsynchronous rectification. The first is a lower-input-voltage application that may operate at low duty cycles or, in other words, when the output voltage is close to the input voltage.


Example inputs for this system are a USB port or a lithium-ion (Li-Ion) battery pack with two or three series cells. The DC/DC power supply steps up the voltage for charging a two-cell Li-Ion battery or the battery of a tablet PC. The other application boosts the voltage of a system power rail to a high output voltage that can operate at higher duty cycles where the output voltage is much higher than the input voltage. An example input is a 12-V power rail. The high output voltage may be needed for power amplifiers, industrial PCs, or pump-and-dump energy storage for higher energy density.

To evaluate the benefits of synchronous rectification, each application is tested with a real circuit to compare efficiency and power loss. The TPS43060/61 synchronous boost controllers from Texas Instruments (TI) are used to demonstrate the synchronous designs. These current-mode boost controllers integrate the control and gate-drive circuitry for both low-side and high-side MOSFETs. TI's TPS40210 current-mode, low-side-switch boost controller is used for the nonsynchronous designs.

## Basic operation

A typical block diagram for a step-up (boost) topology is shown in Figure 1. This topology consists of the low-side power MOSFET (Q1), the power inductor (L1), and the output capacitor (C1). For a synchronous topology, the high-side MOSFET (Q2) is used for the rectifying switch.

**Figure 1. Synchronous and nonsynchronous boost circuits**

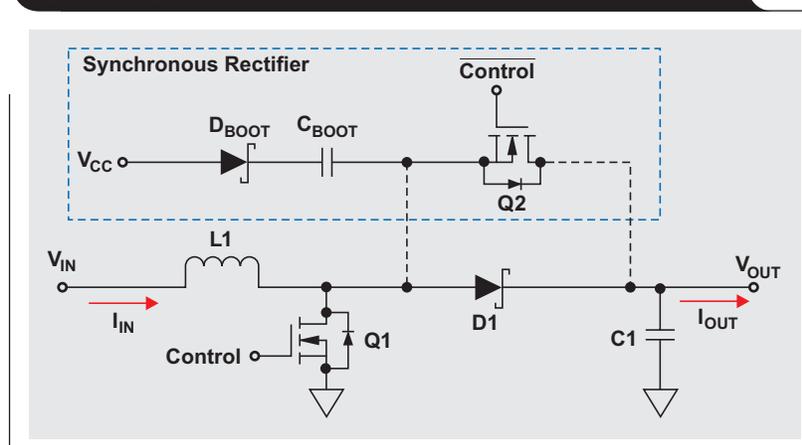

In a nonsynchronous boost topology, a power diode (D1) is used. Figure 2 shows the equivalent waveforms for the voltage and current through the switches and inductor. During the ON time of Q1, the inductor current ramps up, and  $V_{OUT}$  is disconnected from  $V_{IN}$ . The output capacitor must supply the load during this time. During the OFF time, the inductor current ramps down and charges the output capacitor through the rectifying switch. The peak current in the rectifier is equal to the peak current in the switch.

### Selecting the rectifying switch

Nonsynchronous controllers use an external power diode as the rectifying switch. Three main considerations when selecting the power diode are reverse voltage, forward current, and forward voltage drop. The reverse voltage should be greater than the output voltage, including some margin for ringing on the switching node. The forward current rating should be at least the same as the peak current in the inductor. The forward voltage should be small to increase efficiency and reduce power loss. The average diode current is equal to the average output current. The package of the diode chosen must be capable of handling the power dissipation.


Synchronous controllers control another MOSFET for the rectifying switch. If an n-channel MOSFET is used, a voltage higher than the output voltage must be generated for the gate driver. A bootstrap circuit is used to generate this voltage. Figure 1 also includes the typical block diagram for a standard bootstrap circuit consisting of the bootstrap capacitor ( $C_{BOOT}$ ) and the bootstrap diode ( $D_{BOOT}$ ). During the ON time of Q1, the bootstrap capacitor is charged to a regulated voltage ( $V_{CC}$ ), which typically is regulated by a low-dropout regulator internal to the controller. When Q1 turns off, the voltage across the capacitor to ground is  $V_{OUT} + V_{CC}$ , and the required voltage is available to turn on the high-side switch. The control circuitry also must be more complicated to ensure that there is enough delay before the rectifying switch turns on to avoid both switches turning on at the same time. If this occurs, the output voltage shorts to ground through both switches, causing high currents that can damage the switches.

### Power loss of the rectifying switch

To compare the efficiencies of the two different rectifiers, the power dissipation should be calculated. In the nonsynchronous topology, the power dissipation in the rectifying power diode is estimated with Equation 1:

$$P_{D1} = I_{OUT} \times V_{FWD} \quad (1)$$

**Figure 2. Ideal voltage and current waveforms in a boost circuit**

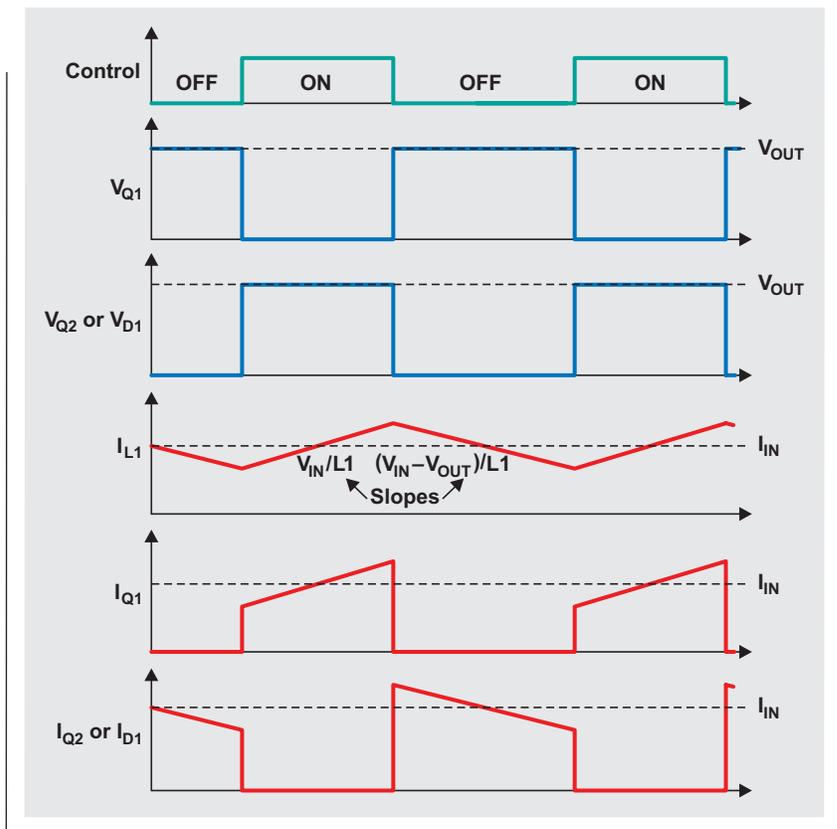

With a synchronous rectifier, there are two main sources of power dissipation—conduction and dead-time loss. When the low-side switch turns off, there is a time delay ( $t_{DELAY}$ ) before the high-side switch turns on. During this delay, the body diode ( $V_{SD}$ ) of the high-side switch conducts current. Typically this is referred to as dead time. When the high-side switch is turned on, there is also conduction loss due to the  $R_{DS(ON)}$  of the MOSFET. Equation 2 calculates the duty cycle ( $D$ ), and Equation 3 estimates the losses ( $P_{Q2}$ ):

$$D = \frac{V_{OUT} - V_{IN}}{V_{OUT}} \quad (2)$$

$$P_{Q2} = \left( \frac{I_{OUT}^2}{1-D} \times R_{DS(ON)} \right) + \left( V_{SD} \times \frac{I_{OUT}}{1-D} \times 2 \times t_{DELAY} \times f_{SW} \right) \quad (3)$$

In an application requiring a low duty cycle, the rectifying switch conducts for a larger percentage of each switching period. However, the power loss in a nonsynchronous rectifier in a boost topology is independent of duty-cycle changes caused by variations in  $V_{IN}$ . This is because variations in  $V_{IN}$  also cause an equal but opposite change in the current the diode conducts. The rectifier loss is simply the forward voltage drop times output current per Equation 1. With a synchronous rectifier, there is some dependence on the duty cycle for power dissipation

because the conduction losses are caused by the resistance of the FET. This is unlike a diode, where the losses are caused by the forward voltage drop. A resistive conduction loss varies with current squared, leading to a dependence on duty cycle, with a higher duty cycle increasing the conduction power loss.


### Efficiency of low-duty-cycle applications

To evaluate the power efficiency of low-duty-cycle applications, a synchronous design and a nonsynchronous design can be compared. The synchronous design uses the TPS43061 synchronous boost controller paired with TI's CSD86330Q3D power block. The power block integrates both the low-side and high-side MOSFETs. The nonsynchronous design uses the TPS40210 nonsynchronous boost controller and a CSD17505Q5A low-side switch, with specifications similar to those of the power block. This design has a Schottky diode for the rectifier that is rated for at least 15 V and 7 A. The smallest package size available for a Schottky diode with these ratings is a TO-277A (SMPC). A comparison of solution sizes based only on typical switch package sizes finds that the nonsynchronous switch and diode occupy an area of 65 mm<sup>2</sup>, and the synchronous power-block switches occupy an area of 12 mm<sup>2</sup>. The latter is a space savings of 53 mm<sup>2</sup>. Both designs use the same LC filter and a 750-kHz switching frequency. Figure 3 shows the efficiency and power loss of both designs with a 12-V input and a 15-V output. The ideal duty cycle is 20%. The benefit of the synchronous rectifier is clear in this example. The full-load efficiency is improved by about 3%, whereas the power loss in the nonsynchronous design is almost double that in the synchronous design.


### Efficiency of high-duty-cycle applications

To evaluate the power efficiency of high-duty-cycle applications, a synchronous and a nonsynchronous design can again be compared. The synchronous design uses the TPS43060 synchronous boost controller with a pair of power MOSFETs for the low-side and high-side switches. The MOSFETs come in a 30-mm<sup>2</sup> typical 8-pin SON package. The nonsynchronous design uses the TPS40210 nonsynchronous boost controller and one of these same MOSFETs for the low-side switch. The Schottky diode for the rectifier is rated for at least 48 V and 16 A. The Schottky rectifier is in a D<sup>2</sup>PAK package with a typical area of 155 mm<sup>2</sup>. The synchronous solution saves 125 mm<sup>2</sup> of board space over


**Figure 3. Measured efficiency and power loss in a low-duty-cycle application**

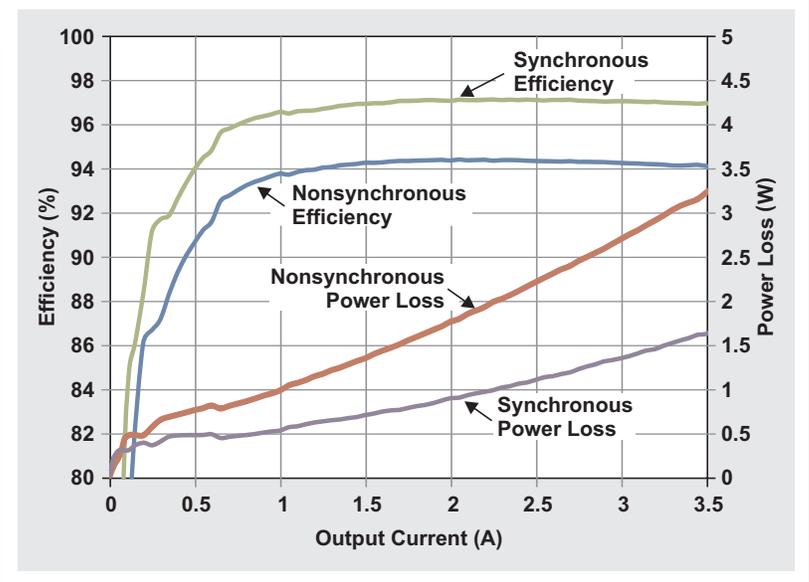

**Figure 4. Measured efficiency and power loss in a high-duty-cycle application**

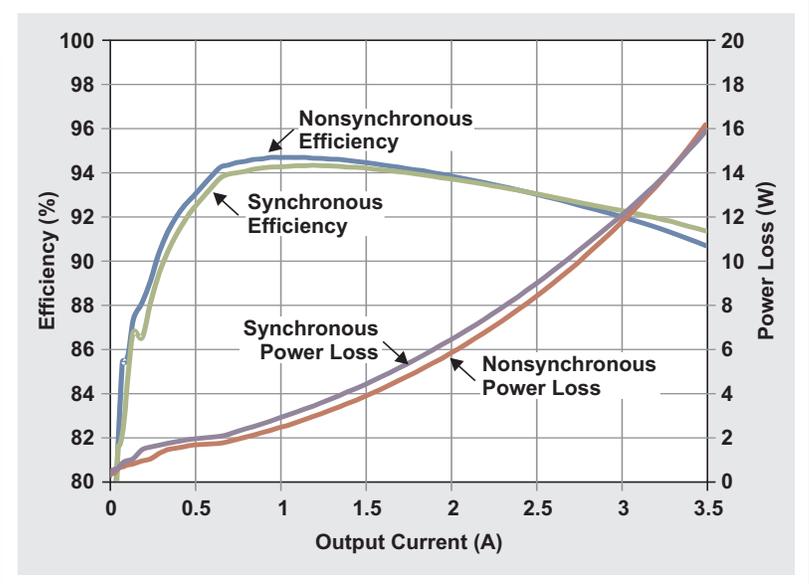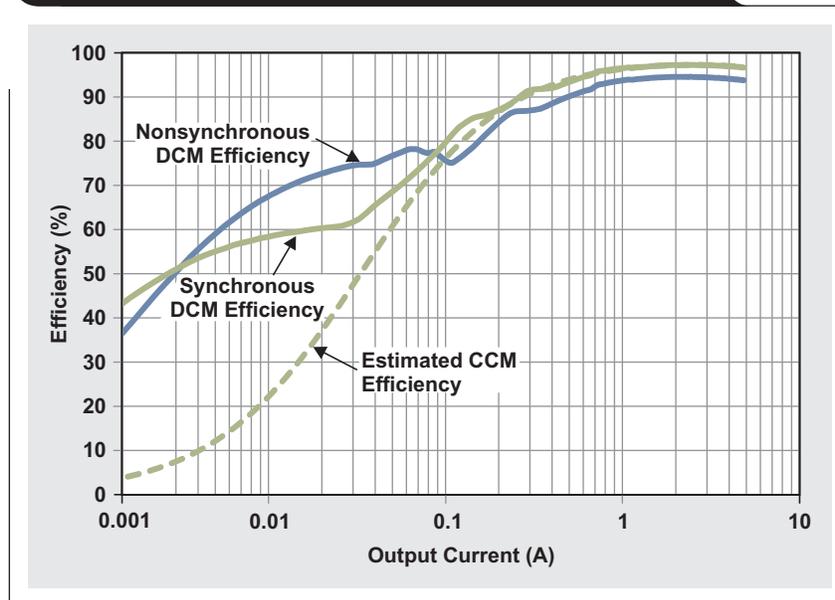

the nonsynchronous design. Both designs use the same LC filter and a 300-kHz switching frequency. Figure 4 shows the efficiency and power loss of both designs with a 12-V input and 48-V output. The ideal duty cycle is 75%. The efficiency curves show that there is no benefit in using a synchronous rectifier in this application. From 2.5 to 3.5 A of load current, the synchronous solution begins to improve efficiency. However, the primary benefit of synchronous rectification is that less board space is required.

**Figure 5. Light-load efficiency of DCM and CCM designs**

### Light-load efficiency

Both the TPS43060 and TPS43061 used in the synchronous designs feature reverse-current detection for discontinuous-conduction mode (DCM), improving efficiency at lighter loads. This reduces conduction losses in the switches, inductor, and sense resistor, enabling the light-load efficiency to be similar to that of the nonsynchronous solutions. For reference, Figure 5 shows a dashed curve for the estimated efficiency of a converter operating in forced continuous-conduction mode (CCM). This efficiency is determined by estimating losses in the switches, inductor, and sense resistor during CCM operation. The curves show the relative improvement in efficiency at light loads for converters operating in DCM. However, for some low-noise applications or applications requiring a fast transient response from light loads, it may be preferable to sacrifice improved light-load efficiency to keep CCM operation over the entire load range.

### Conclusion

The benefits of synchronous rectification are evident, especially in low-duty-cycle applications as the load current increases. However, in high-duty-cycle applications with

lower output current, a nonsynchronous design may have adequate efficiency. The lower losses with synchronous rectification can improve efficiency and reduce temperature rise and solution size.

### References

1. "Low quiescent current synchronous boost DC-DC controller with wide  $V_{IN}$  range," TPS43060/61 Datasheet. Available: [www.ti.com/slvsbp4-aaj](http://www.ti.com/slvsbp4-aaj)
2. "4.5-V to 52-V input current mode boost controller," TPS40210/11 Datasheet. Available: [www.ti.com/slus772-aaj](http://www.ti.com/slus772-aaj)

### Related Web sites

Power Management:

[www.ti.com/power-aaj](http://www.ti.com/power-aaj)

[www.ti.com/csd17505q5a-aaj](http://www.ti.com/csd17505q5a-aaj)

[www.ti.com/csd86330q3d-aaj](http://www.ti.com/csd86330q3d-aaj)

[www.ti.com/tps40210-aaj](http://www.ti.com/tps40210-aaj)

[www.ti.com/tps43060-aaj](http://www.ti.com/tps43060-aaj)

[www.ti.com/tps43061-aaj](http://www.ti.com/tps43061-aaj)

Subscribe to the AAJ:

[www.ti.com/subscribe-aaj](http://www.ti.com/subscribe-aaj)

# TI Worldwide Technical Support

---

## Internet

### TI Semiconductor Product Information Center Home Page

[support.ti.com](http://support.ti.com)

### TI E2E™ Community Home Page

[e2e.ti.com](http://e2e.ti.com)

## Product Information Centers

|                 |                |  |
|-----------------|----------------|--|
| <b>Americas</b> | Phone          | +1(512) 434-1560   |
| <b>Brazil</b>   | Phone          | 0800-891-2616  |
| <b>Mexico</b>   | Phone          | 0800-670-7544  |
|                 | Fax            | +1(972) 927-6377   |
|                 | Internet/Email | <a href="http://support.ti.com/sc/pic/americas.htm">support.ti.com/sc/pic/americas.htm</a> |

### Europe, Middle East, and Africa

|                    |                                      |
|--------------------|--------------------------------------|
| Phone              |                                      |
| European Free Call | 00800-ASK-TEXAS<br>(00800 275 83927) |
| International      | +49 (0) 8161 80 2121                 |
| Russian Support    | +7 (4) 95 98 10 701                  |

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

|              |  |
|--------------|--|
| Fax          | + (49) (0) 8161 80 2045                                      |
| Internet     | <a href="http://www.ti.com/asktexas">www.ti.com/asktexas</a> |
| Direct Email | <a href="mailto:asktexas@ti.com">asktexas@ti.com</a>         |

### Japan

|                |               |  |
|----------------|---------------|--|
| Phone          | Domestic      | 0120-92-3326   |
| Fax            | International | +81-3-3344-5317  |
|                | Domestic      | 0120-81-0036   |
| Internet/Email | International | <a href="http://support.ti.com/sc/pic/japan.htm">support.ti.com/sc/pic/japan.htm</a> |
|                | Domestic      | <a href="http://www.tij.co.jp/pic">www.tij.co.jp/pic</a>                             |

### Asia

|   |  |
|---|--|
| Phone   |  |
| International   | +91-80-41381665  |
| Domestic  | <u>Toll-Free Number</u>  |
| <b>Note:</b> Toll-free numbers do not support mobile and IP phones. |  |
| Australia   | 1-800-999-084  |
| China   | 800-820-8682   |
| Hong Kong   | 800-96-5941  |
| India   | 1-800-425-7888   |
| Indonesia   | 001-803-8861-1006  |
| Korea   | 080-551-2804   |
| Malaysia  | 1-800-80-3973  |
| New Zealand   | 0800-446-934   |
| Philippines   | 1-800-765-7404   |
| Singapore   | 800-886-1028   |
| Taiwan  | 0800-006800  |
| Thailand  | 001-800-886-0010   |
| Fax   | +8621-23073686   |
| Email   | <a href="mailto:tiasia@ti.com">tiasia@ti.com</a> or <a href="mailto:ti-china@ti.com">ti-china@ti.com</a> |
| Internet  | <a href="http://support.ti.com/sc/pic/asia.htm">support.ti.com/sc/pic/asia.htm</a>                       |

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A090712

E2E is a trademark of Texas Instruments. ENERGY STAR is a registered trademark of the U.S. Environmental Protection Agency. All other trademarks are the property of their respective owners.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

|                              |  |
|------------------------------|--|
| Audio                        | <a href="http://www.ti.com/audio">www.ti.com/audio</a>                               |
| Amplifiers                   | <a href="http://amplifier.ti.com">amplifier.ti.com</a>                               |
| Data Converters              | <a href="http://dataconverter.ti.com">dataconverter.ti.com</a>                       |
| DLP® Products                | <a href="http://www.dlp.com">www.dlp.com</a>   |
| DSP                          | <a href="http://dsp.ti.com">dsp.ti.com</a>   |
| Clocks and Timers            | <a href="http://www.ti.com/clocks">www.ti.com/clocks</a>                             |
| Interface                    | <a href="http://interface.ti.com">interface.ti.com</a>                               |
| Logic                        | <a href="http://logic.ti.com">logic.ti.com</a>                                       |
| Power Mgmt                   | <a href="http://power.ti.com">power.ti.com</a>                                       |
| Microcontrollers             | <a href="http://microcontroller.ti.com">microcontroller.ti.com</a>                   |
| RFID                         | <a href="http://www.ti-rfid.com">www.ti-rfid.com</a>                                 |
| OMAP Applications Processors | <a href="http://www.ti.com/omap">www.ti.com/omap</a>                                 |
| Wireless Connectivity        | <a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a> |

### Applications

|                               |  |
|-------------------------------|--|
| Automotive and Transportation | <a href="http://www.ti.com/automotive">www.ti.com/automotive</a>                         |
| Communications and Telecom    | <a href="http://www.ti.com/communications">www.ti.com/communications</a>                 |
| Computers and Peripherals     | <a href="http://www.ti.com/computers">www.ti.com/computers</a>                           |
| Consumer Electronics          | <a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>                   |
| Energy and Lighting           | <a href="http://www.ti.com/energy">www.ti.com/energy</a>                                 |
| Industrial                    | <a href="http://www.ti.com/industrial">www.ti.com/industrial</a>                         |
| Medical                       | <a href="http://www.ti.com/medical">www.ti.com/medical</a>                               |
| Security                      | <a href="http://www.ti.com/security">www.ti.com/security</a>                             |
| Space, Avionics and Defense   | <a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a> |
| Video and Imaging             | <a href="http://www.ti.com/video">www.ti.com/video</a>                                   |

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)