

How to Compensate With the TPS6510x and the TPS6514x

Ilona Weiss

Display Power Application

ABSTRACT

The boost converters in the TPS6510x (TPS65100, TPS65101, TPS65105) and the TPS6514x (TPS65140, TPS65141, TPS65145) series use external loop compensation providing high flexibility in LCD supply design. If designing a typical application scheme, use the recommended components from the TPS6510x datasheet ([SLVS496](#)) and the TPS6514x datasheet ([SLVS497](#)). This application note gives a deeper understanding on how to select the external components and how they can influence the performance.

General Description of the Boost Converter

The boost converter as it is implemented in the mentioned devices is a voltage-mode regulator. [Figure 1](#) shows a high-level circuit description of the power stage and the control loop. The following section explains how this works.

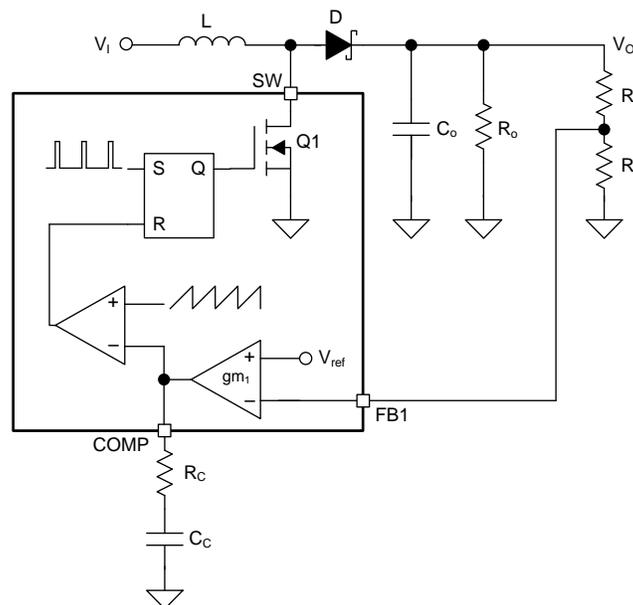


Figure 1. High-level Scheme Voltage-Mode Control

The output voltage from the feedback-divider is compared to a reference voltage V_{ref} . The error between the two voltages is amplified by the compensated error amplifier (gm_1). This signal goes into the duty cycle modulator (gm_2) which drives the gate of the power switch. The compensation components are connected to the COMP pin which is the output of the internal error amplifier gm_1 .

Compensating the right-half-plane zero (RHPZ) is the main complex problem that must be solved. This is due to the nature of every boost converter. When the main switch Q1 is turned on, the inductor is disconnected from the load for a longer period of time and this causes the output voltage to drop initially.

Although the control signal is trying to increase the initial response of the output, it will react in a decrease. Only after the time delay that corresponds to the RHPZ has passed will the output follow the control signal. To limit the time delay, and therefore limit the RHPZ effect, the compensation circuit limits the bandwidth of the LC filter and stabilizes the system.

The frequency of the RHPZ in a boost converter in continuous-conduction mode is defined as:

$$f_{RHPZ} = \frac{V_O (1 - D)^2}{I_O (2\pi \times L)}$$

where

- V_O is the output voltage
- I_O is the output current

- D is the duty cycle of a boost converter $\left(\frac{V_O - V_I}{V_O} \right)$

- L is the inductance.

(1)

This formula shows that the RHPZ is dependent of the output power and the input voltage.

Note that the RHPZ decreases with higher output current and lower input voltage. For best performance, calculate the worst-case scenario which means the highest output load and lowest input voltage.

The next step is to set the crossover frequency (f_z) that needs to be set by the RC components of the compensation network. A reasonable approximation commonly used is:

$$f_z \ll \frac{f_{RHPZ}}{10}$$

(2)

A good start is to set $C_C = 1$ nF for a 3.3-V input or $C_C = 2.2$ nF for a 5-V input. Lower input voltages require a higher gain; therefore, a lower compensation capacitor value.

To test the converters performance it is the best to apply a load step to the converters output. The images in [Figure 2](#) show the effect of different compensation components on the performance.

A larger compensation capacitor, such as 4.7 nF, corresponds to a slower response and a smaller compensation capacitor corresponds to a faster response but lower gain.

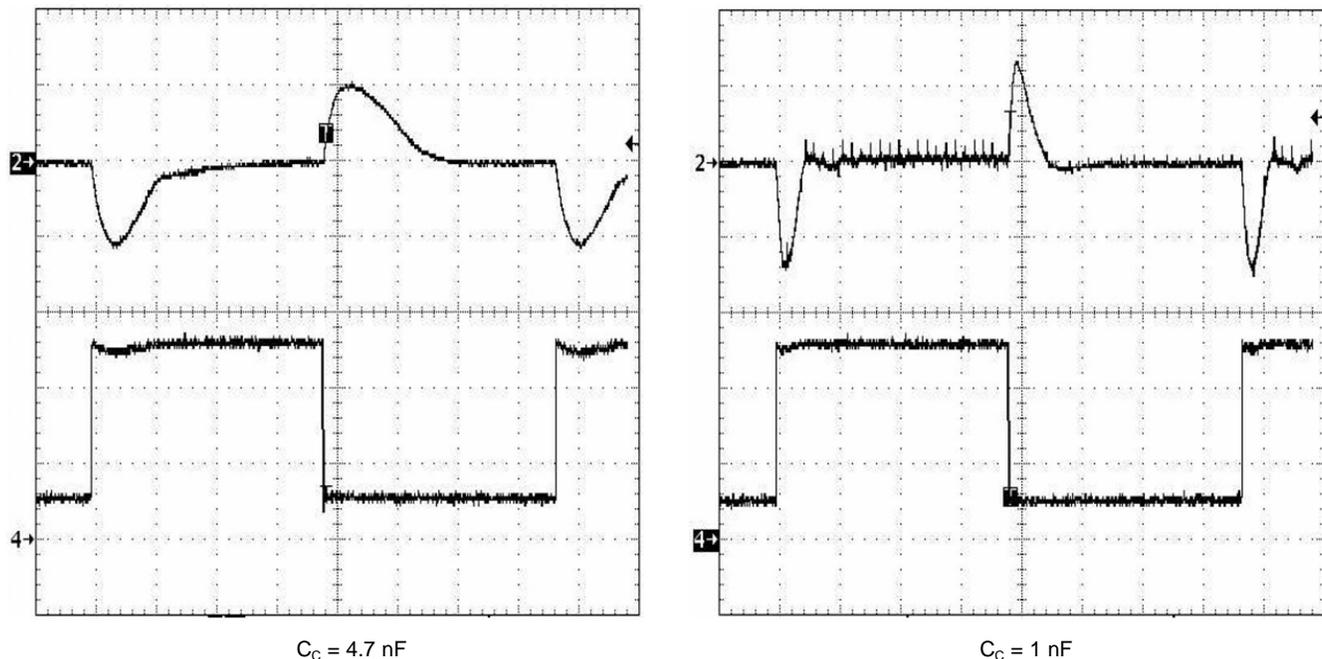


Figure 2. Load Transient Big-Small Comp Cap (Load Step: 50 mA – 150 mA – 50 mA)

NOTE: If the device operates over the entire input voltage range from 2.7 V to 5.8 V, a large compensation capacitor, up to 10 nF, is recommended.

Lastly the compensation resistor must be calculated. The formula can be derived from the crossover frequency of an R-C- filter:

$$f_z = \frac{1}{2\pi C_C R_C} \tag{3}$$

Reshaping this formula to get R_C is:

$$R_C = \frac{1}{2\pi C_C f_z} \tag{4}$$

Figure 3 and Figure 4 show how the load transient looks if you select incorrect R_C components and Figure 5 gives an example for an ideal selection.

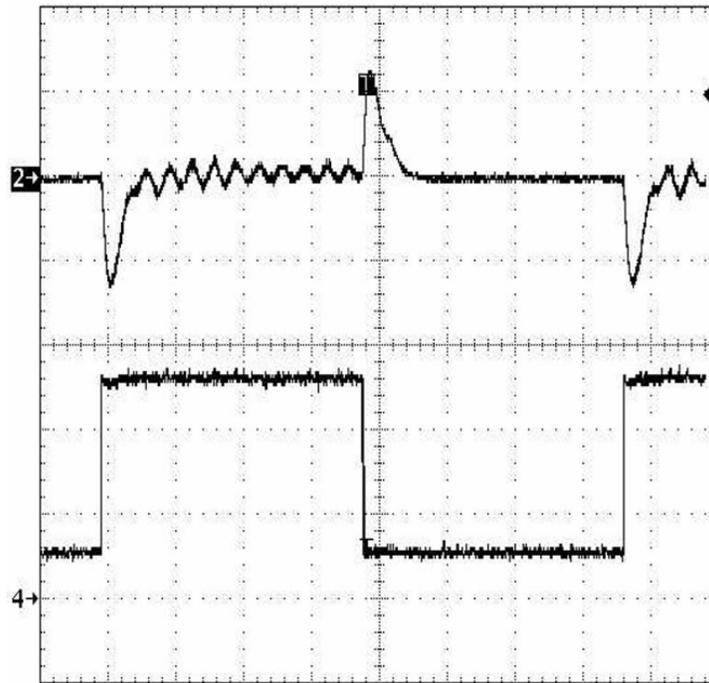


Figure 3. Overcompensated → R_C is Too Big



Figure 4. Undercompensated $\rightarrow R_C$ is Too Small

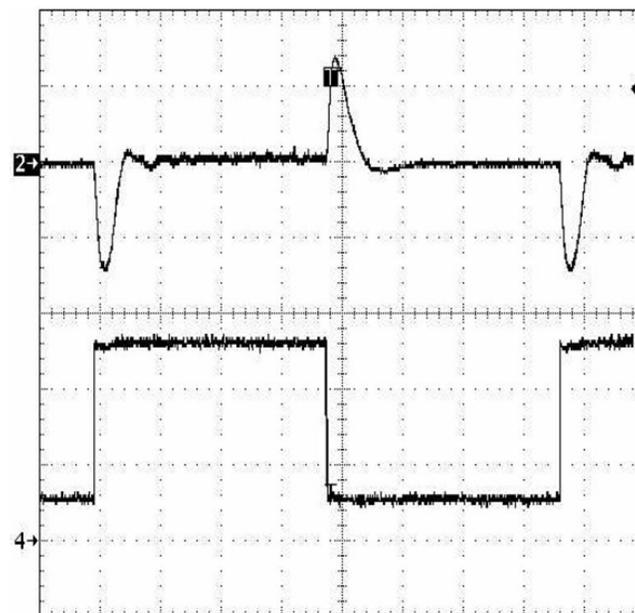


Figure 5. Ideal Selection of R_C

Example Calculation for Notebook Supply Applications

$$V_I = 2.7 \text{ V}, V_O = 10 \text{ V}, I_O = 300 \text{ mA}, L = 3.3 \text{ } \mu\text{H}, D = 0.73, C_c = 1 \text{ nF}$$

1. Calculate RHPZ

$$f_{\text{RHPZ}} = \frac{10 \text{ V} (1 - 0.73)^2}{0.3 \text{ A} (2\pi \times 3.3 \text{ } \mu\text{H})} = 118 \text{ kHz}$$

2. Set crossover frequency:

$$f_Z = 10 \text{ kHz}$$

3. Calculate R_C:

$$R_C = \frac{1}{2\pi \times 1 \text{ nF} \times 10 \text{ kHz}} = 15 \text{ k}\Omega$$

Example Calculation for Monitor Supply Applications

$$V_I = 5 \text{ V}, V_O = 13.5 \text{ V}, I_O = 400 \text{ mA}, L = 4.7 \text{ } \mu\text{H}, D = 0.63, C_c = 2.2 \text{ nF}$$

1. Calculate RHPZ

$$f_{\text{RHPZ}} = \frac{13.5 \text{ V} (1 - 0.63)^2}{0.4 \text{ A} (2\pi \times 4.7 \text{ } \mu\text{H})} = 160 \text{ kHz}$$

2. Set crossover frequency:

$$f_Z = 16 \text{ kHz}$$

3. Calculate R_C:

$$R_C = \frac{1}{2\pi \times 2.2 \text{ nF} \times 16 \text{ kHz}} = 4.5 \text{ k}\Omega$$

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com