

# Remote sensing for power supplies

By Tiger Zhou

Senior Applications Engineer

Remote sensing is widely used in telecommunication applications to meet the demanding accuracy requirements of critical ASICs and processors. This article discusses design considerations for remote sensing, including power-plane shortages, component placement, parasitic resistance, and potential oscillations. Also, a practical example demonstrates the effectiveness of a high-frequency bypass capacitor for mitigating oscillations associated with remote sensing.

In high-end telecommunication applications, the designer often faces the challenges of delivering power across large-scale printed circuit boards. To give precious real estate to critical ASICs and processors, the power supplies are often allocated to the corner or edge of the board. To compensate for the resistive drop of the power path, remote sensing is often used—especially for low-voltage, high-current applications. If not attended to, the dynamic nature of the load coupled with the parasitic resistance of the power path may affect the operation of the power supply.


## Reducing power-path impedance

The available power planes can be used to reduce the DC voltage gradient to within regulation tolerance. The power plane helps with DC-regulation accuracy and improves system efficiency by reducing the resistive drop along the power path.


## Splitting the output capacitance

It is important for a dynamic load such as a gate driver to split the output capacitance between the supply and the remote load. The output capacitance at the remote load acts as a bypass capacitor for the dynamic load, reducing the ripple/noise current from the delivering path. It also stabilizes the output voltage at a remote sensing point, which makes both the monitoring and the sensing circuitry more accurate and reliable.

**Figure 1. Remote feedback to differential amplifier compensates for parasitic-resistance voltage drop**

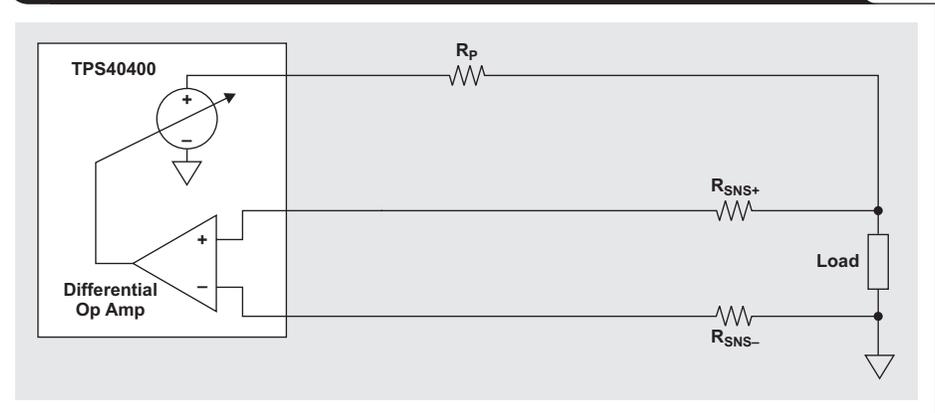

**Figure 2. Remote sensing via resistor  $R_{SNS}$  regulates the output for  $R_P$  voltage drop**

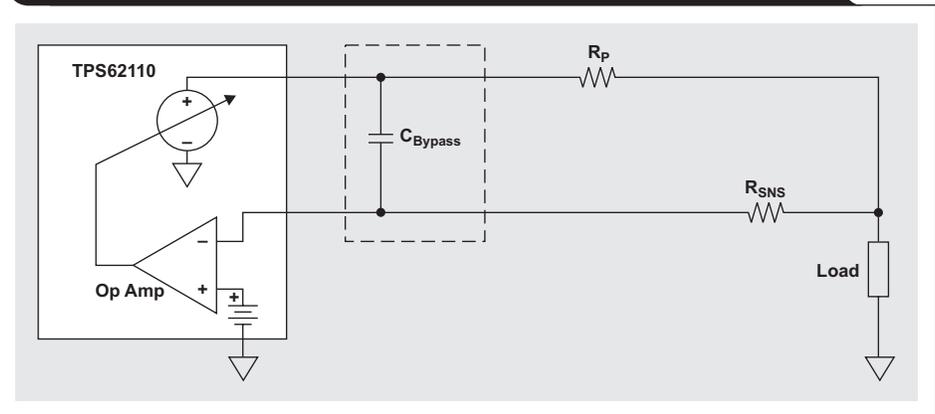

## High-frequency bypass capacitor

Adding a high-frequency bypass capacitor at the local power supply is also beneficial. Modern converters are often equipped with a differential amplifier for remote sensing. Two sensing resistors are located near the remote side and connect the load voltage back to the controller by differential pairs. As shown in Figure 1, the Texas Instruments (TI) TPS40400 synchronous buck controller has a dedicated differential amplifier that compensates for the voltage drop across the power-path parasitic resistance ( $R_P$ ).

If there is no dedicated differential amplifier, the power supply can still be remotely sensed. A remote sense resistor can connect the load voltage back to the converter, compare the load voltage to the reference voltage, and regulate the output voltage. Figure 2 shows the TI TPS62110 step-down converter configured to remotely

sense the load and regulate the output for any parasitic-resistance ( $R_p$ ) voltage drop.

However, when a dynamic load is applied as illustrated in Figure 2, the remote sense line picks up the dynamic voltage and tries to compensate for the voltage drop across the parasitic resistance ( $R_p$ ). This may result in a low-frequency oscillation due to the controller propagation delay. It appears as slight jittering on the switching waveform and causes elevated ripple on the output side. A high-frequency bypass capacitor ( $C_{Bypass}$ ) can easily remedy the situation. It filters out the high-frequency dynamic voltage while keeping the characteristics of DC remote sensing.

A 7-V gate-drive power supply with a 1- $\mu$ F bypass capacitor was tested with the TPS62110 step-down converter. Figure 3 shows an output ripple with 33-kHz oscillation that occurred when no bypass capacitor was used. Figure 4 shows that the addition of a 1- $\mu$ F bypass capacitor clearly removed the 33-kHz oscillation from the output voltage and resulted in a low output ripple of 20 mV, which was 0.3% of the regulated voltage.


### Related Web sites

[power.ti.com](http://power.ti.com)


[www.ti.com/product/TPS40400](http://www.ti.com/product/TPS40400)

[www.ti.com/product/TPS62110](http://www.ti.com/product/TPS62110)

**Figure 3. Original output ripple with 33-kHz oscillation**

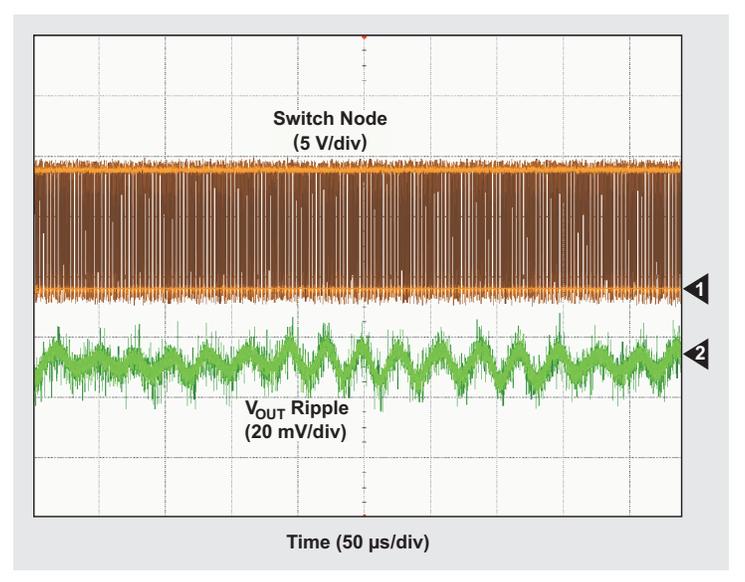

**Figure 4. Low output ripple with oscillation removed by 1- $\mu$ F bypass capacitor**

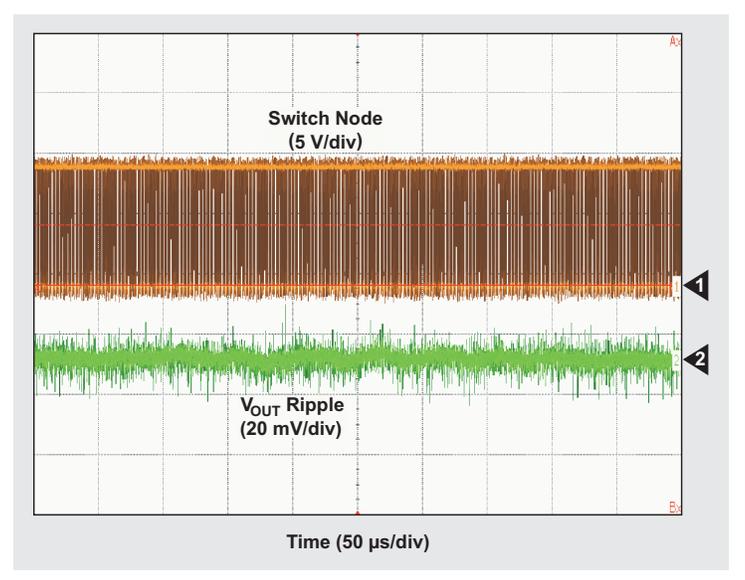

# TI Worldwide Technical Support

---

## Internet

### TI Semiconductor Product Information Center Home Page

[support.ti.com](http://support.ti.com)

### TI E2E™ Community Home Page

[e2e.ti.com](http://e2e.ti.com)

## Product Information Centers

<b>Americas</b>	Phone	+1(972) 644-5580
<b>Brazil</b>	Phone	0800-891-2616
<b>Mexico</b>	Phone	0800-670-7544
	Fax	+1(972) 927-6377
	Internet/Email	<a href="http://support.ti.com/sc/pic/americas.htm">support.ti.com/sc/pic/americas.htm</a>

### Europe, Middle East, and Africa

Phone	
European Free Call	00800-ASK-TEXAS (00800 275 83927)
International	+49 (0) 8161 80 2121
Russian Support	+7 (4) 95 98 10 701

**Note:** The European Free Call (Toll Free) number is not active in all countries. If you have technical difficulty calling the free call number, please use the international number above.

Fax	+ (49) (0) 8161 80 2045
Internet	<a href="http://www.ti.com/asktexas">www.ti.com/asktexas</a>
Direct Email	<a href="mailto:asktexas@ti.com">asktexas@ti.com</a>

### Japan

Phone	Domestic	0120-92-3326
Fax	International	+81-3-3344-5317
	Domestic	0120-81-0036
Internet/Email	International	<a href="http://support.ti.com/sc/pic/japan.htm">support.ti.com/sc/pic/japan.htm</a>
	Domestic	<a href="http://www.tij.co.jp/pic">www.tij.co.jp/pic</a>

### Asia

Phone	
International	+91-80-41381665
Domestic	<u>Toll-Free Number</u>
<b>Note:</b> Toll-free numbers do not support mobile and IP phones.	
Australia	1-800-999-084
China	800-820-8682
Hong Kong	800-96-5941
India	1-800-425-7888
Indonesia	001-803-8861-1006
Korea	080-551-2804
Malaysia	1-800-80-3973
New Zealand	0800-446-934
Philippines	1-800-765-7404
Singapore	800-886-1028
Taiwan	0800-006800
Thailand	001-800-886-0010
Fax	+8621-23073686
Email	<a href="mailto:tiasia@ti.com">tiasia@ti.com</a> or <a href="mailto:ti-china@ti.com">ti-china@ti.com</a>
Internet	<a href="http://support.ti.com/sc/pic/asia.htm">support.ti.com/sc/pic/asia.htm</a>

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A011012

E2E is a trademark of Texas Instruments. All other trademarks are the property of their respective owners.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Mobile Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

TI E2E Community Home Page

[e2e.ti.com](http://e2e.ti.com)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2012, Texas Instruments Incorporated