

Test Report: PMP22288

15-W Flyback Reference Design for Automotive Inverter Power



Description:

This reference design uses the UCC28730-Q1 flyback controller to produce an isolated 15-V output. The design is capable of 0.33-A from a 40-V to 250-Vdc input and 1-A from a 250-V to 550-Vdc input. This power system is designed for an inverter bias supply application and is an automotive-qualified solution.



Figure 1. Board Top



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

 


Figure 2. Board Bottom

1 Flyback Stage

1.1 Test Prerequisites

1.1.1 Voltage and Current Requirements

PARAMETER	SPECIFICATIONS
Input Voltage Range	40 Vdc – 550 Vdc
Output Voltage	15 V
Output Current	0.33A max for $V_{in} = 40\text{-}250\text{V}$ 1A max for $V_{in} = 250\text{-}550\text{V}$
Switching Frequency	70 kHz

1.1.2 Considerations

- 1) For all tests an electronic load was used.
- 2) The circuit needs a pre-load of 0.04 A to start up.

1.2 Testing and Results

1.2.1 Efficiency Graphs

 


Figure 3. Efficiency for 250 Vdc input

 


Figure 4. Efficiency for 550 Vdc input

1.2.2 Efficiency Data

Input Voltage (V)	Input Current (A)	Input Power (W)	Output Voltage (V)	Output Current (A)	Output Power (W)	Power Loss (W)	Efficiency (%)
39.985	0.158	6.317	15.348	0.327	5.026	1.291	79.562
80.085	0.074	5.950	15.372	0.327	5.026	0.923	84.476
150.07	0.038	5.837	15.369	0.328	5.044	0.793	86.405
249.70	0.025	6.262	15.392	0.351	5.408	0.853	86.367
250.01	0.047	11.750	15.446	0.659	10.185	1.565	86.678
249.96	0.071	17.872	15.511	1.001	15.526	2.345	86.875
550.12	0.01173	6.452	15.380	0.350	5.384	1.068	83.443
550.15	0.0216	11.883	15.433	0.651	10.054	1.828	84.611
550.14	0.033	15.494	15.494	1.002	15.537	2.683	85.273

Figure 5. Efficiency data from light load and full load at varying input voltage

1.2.3 Thermal Images

Thermal images (with no airflow) were taken for 40V_{in}, 250V_{in}, and 550V_{in} at varying loads. The board had a soak time of 10 minutes.

 


Figure 6. Board top thermal image, 40V_{in}, 0.33 A out

 


Figure 7. Board top thermal image, 250Vin, 1 A out

 


Figure 8. Board top thermal image, 550Vin, 1 A out

1.3 Waveforms

1.3.1 Switching

The switch node was measured at both the primary and secondary side at various loading conditions.

The primary side was measured from the drain (Pin 4) of 950V FET (Q1) to GND.

The secondary side was measured using two probes at each side of the diode (D1) and the math function. Channel 1 was measured from Pin 2 of D1 to GND, Channel 3 was measured from Pin 1 of D1 to GND, and the Math function shows C1-C3.

 


Figure 9. Primary Switch Node at 40 Vdc Input, 0.33 A out

 


Figure 10. Primary Switch Node at 250 Vdc Input, 1 A out

 


Figure 11. Primary Switch Node at 550 Vdc Input, 1 A out

 


Figure 12. Secondary Switch Node at 250 Vdc Input, 1 A out

 


Figure 13. Secondary Switch Node at 550 Vdc Input, 1 A out

1.3.2 Output Voltage Ripple

Measurements were taken from Pin 2 of D1 to GND. The ripple measurements shown are with a 0 Ohm resistor (R1) at the output. The schematic has a placeholder for an output inductor (L1) to reduce ripple, if needed.

 


Figure 14. Output Ripple at 250 Vdc Input, 1 A out

 


Figure 15. Output Ripple at 550 Vdc Input, 1 A out

1.3.3 Load Transients

The load step applied is between 0.25 A and 0.75 A (25% to 75% of full load). The slew rate is 4.000 A/uS. The output voltage (AC coupled) was measured at the output of D1 (pin 2).

 


Figure 16. Load transient rising edge, 250Vin

 


Figure 17. Load transient falling edge, 250V_{in}

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated