

TEXAS INSTRUMENTS INCORPORATED

PMP20054 Rev A

Power Design Services Test Report

Sarmad Abedin

4/14/2016





Table of Contents

1	PMP20054 REVA 0.85V/40A – TPS40322-DUAL PHASE.....	Error! Bookmark not defined.
1.1	Board Photos.....	2
1.2	Efficiency and Power Loss.....	3
1.3	Thermal.....	4
1.4	Startup.....	5
1.5	Shutdown.....	5
1.6	Output Ripple.....	6
1.7	Transient response.....	7
1.8	Switch waveforms.....	Error! Bookmark not defined.
1.9	Loop Response.....	11

1. PMP20054 REVA 0.85V/40A – TPS40322-DUAL PHASE

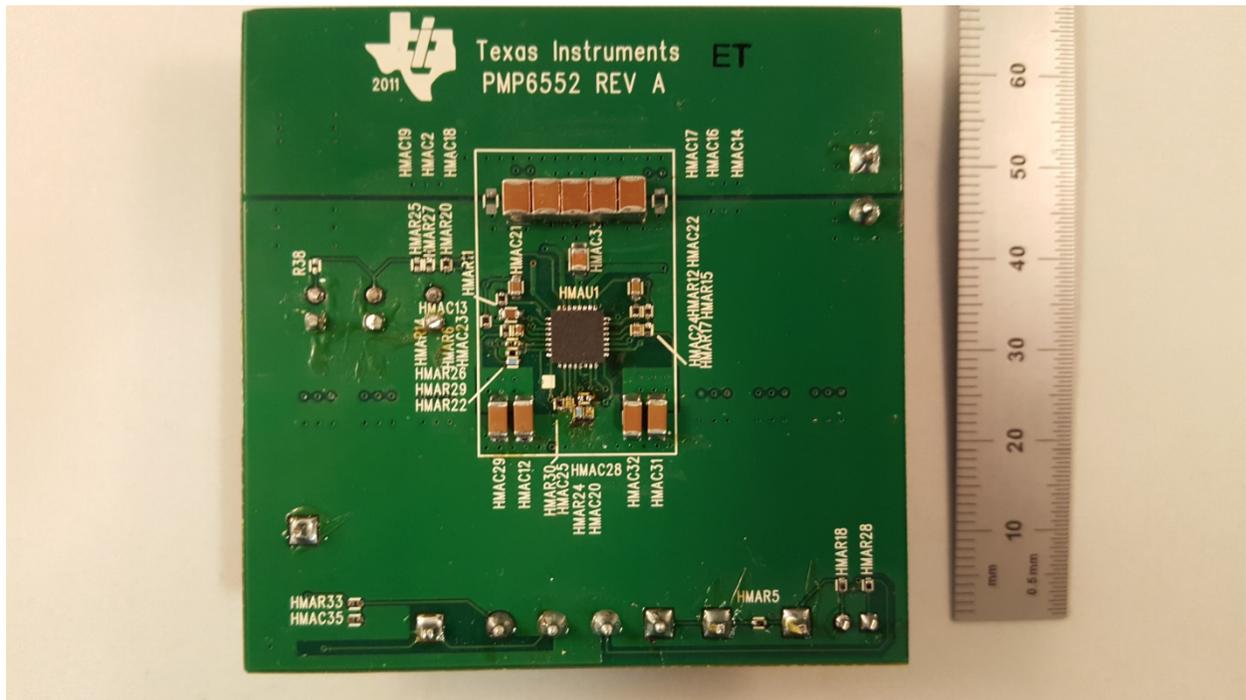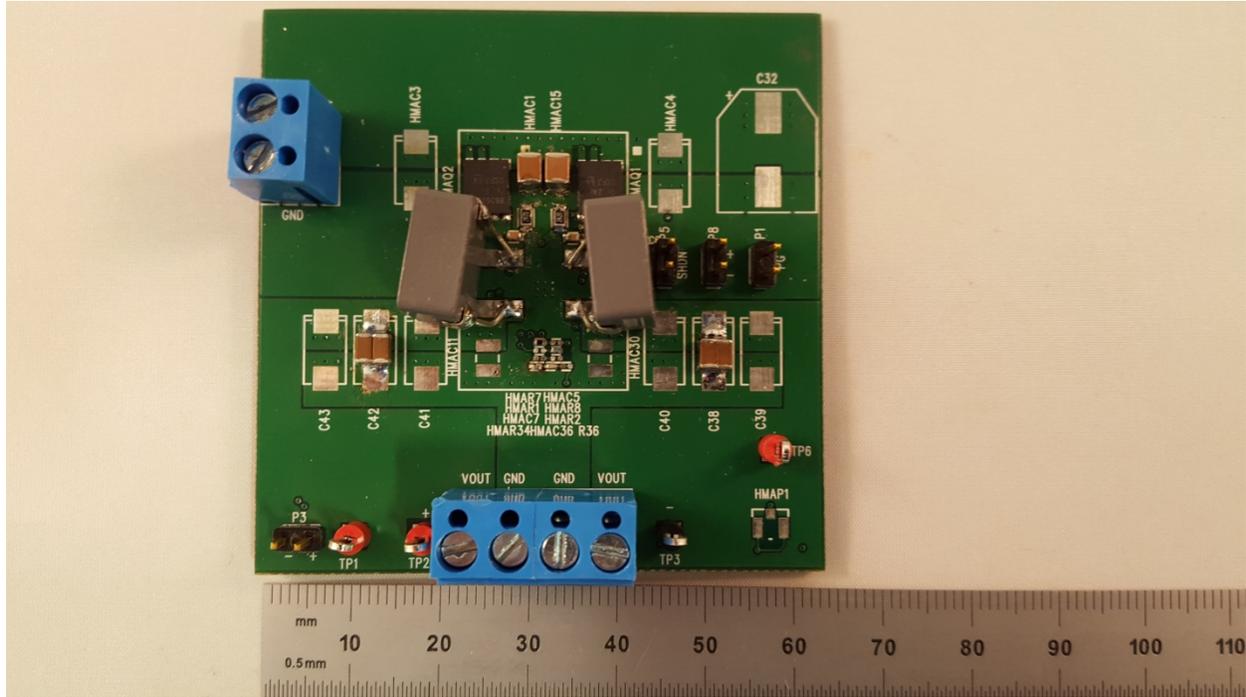
1.1 Board Photos

The top and bottom images of PMP20054 are shown below.



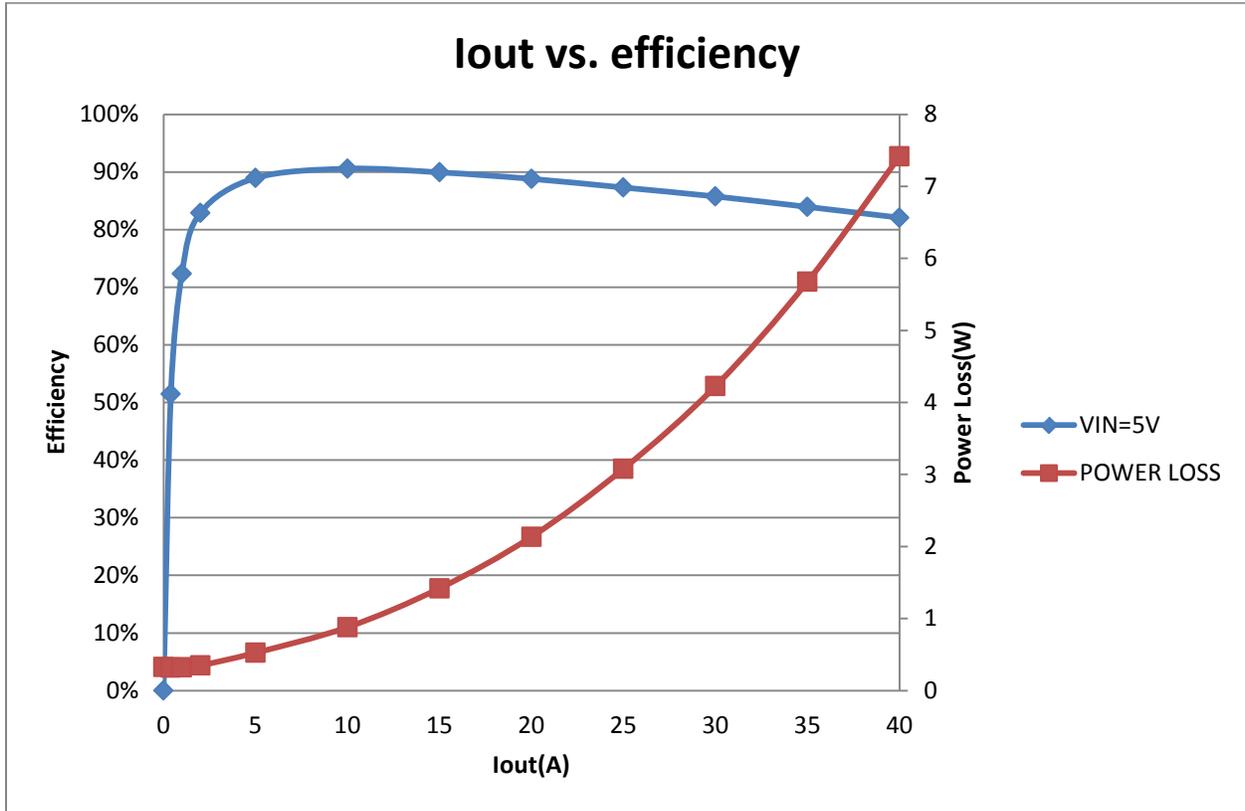1.2 Efficiency and Power Loss

The efficiency and power loss of the power supply is shown below at 5V_{in} with natural convection.




4/14/2016

PMP20054 Rev A Test Results



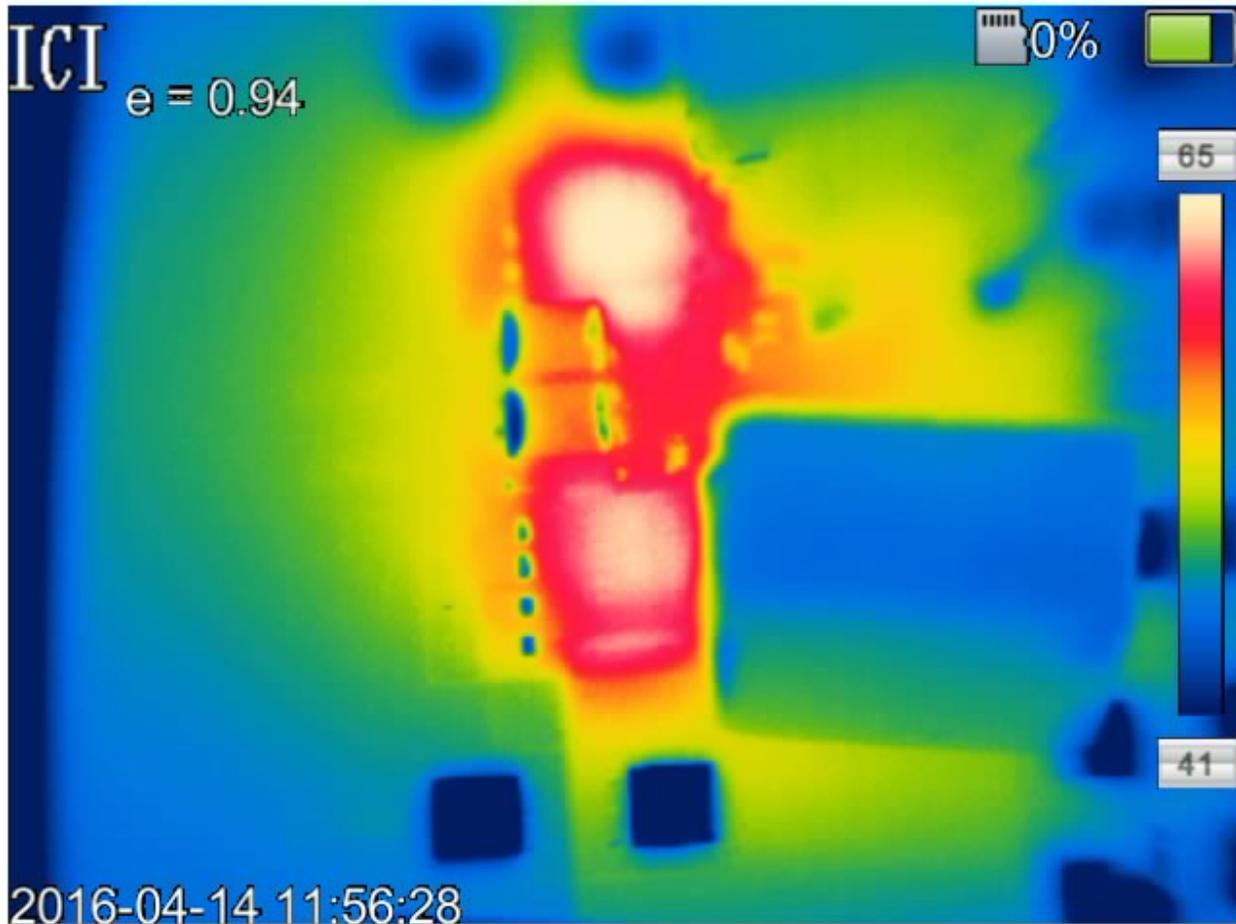
1.3 Thermal

The thermal image of the power supply is shown at room temperature with 5Vin, 40A out, and natural convection. The power supply was held on for 2 min at 40A before the measurement was taken.



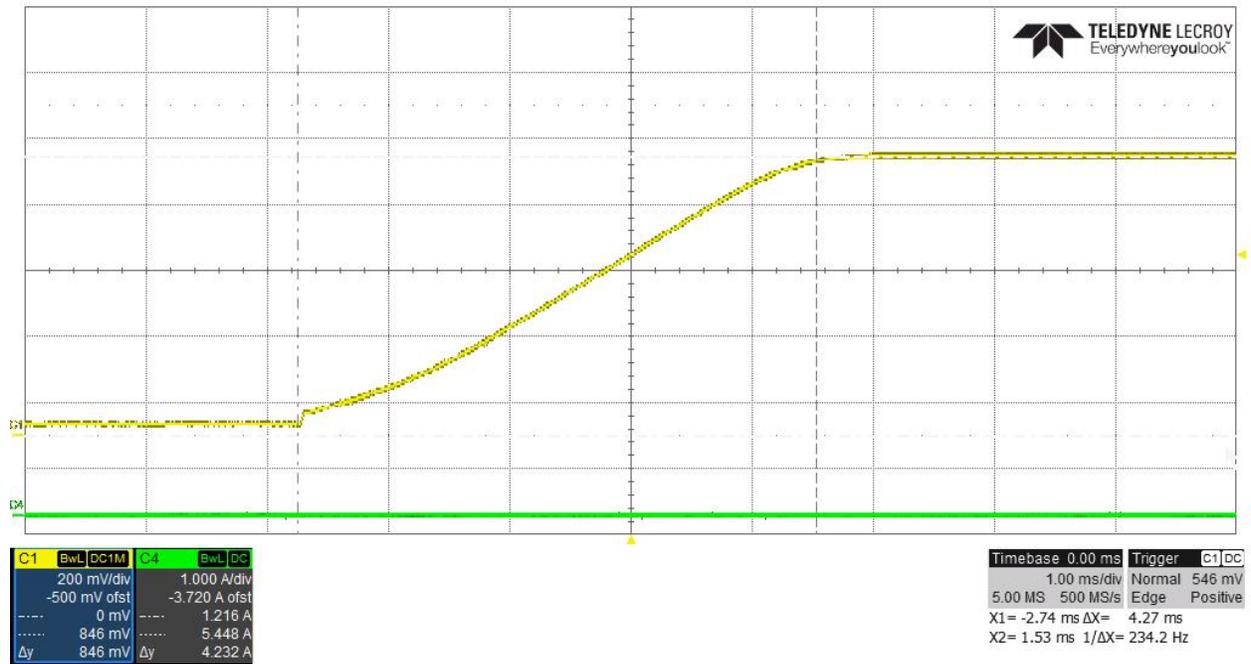
1.4 Startup

The power supply startup at 0A is shown below. The startup time is 4.27ms.



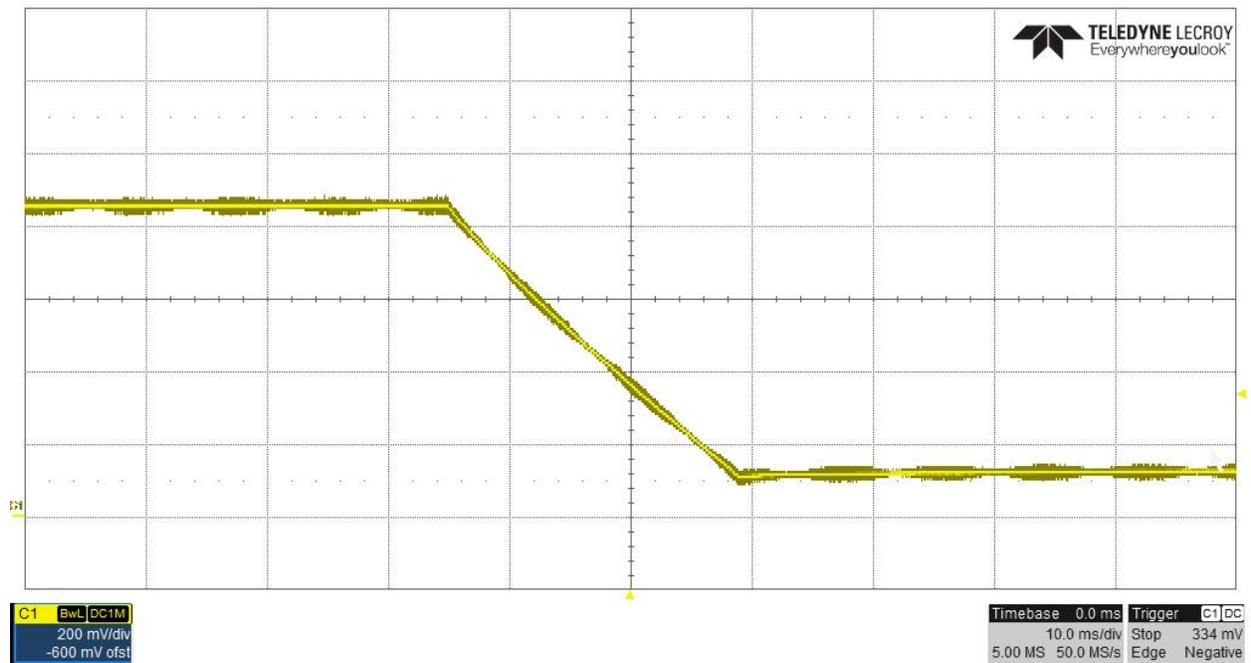1.5 Shutdown

The shutdown of the power supply with 0A load is shown below.




PMP20054 Rev A Test Results



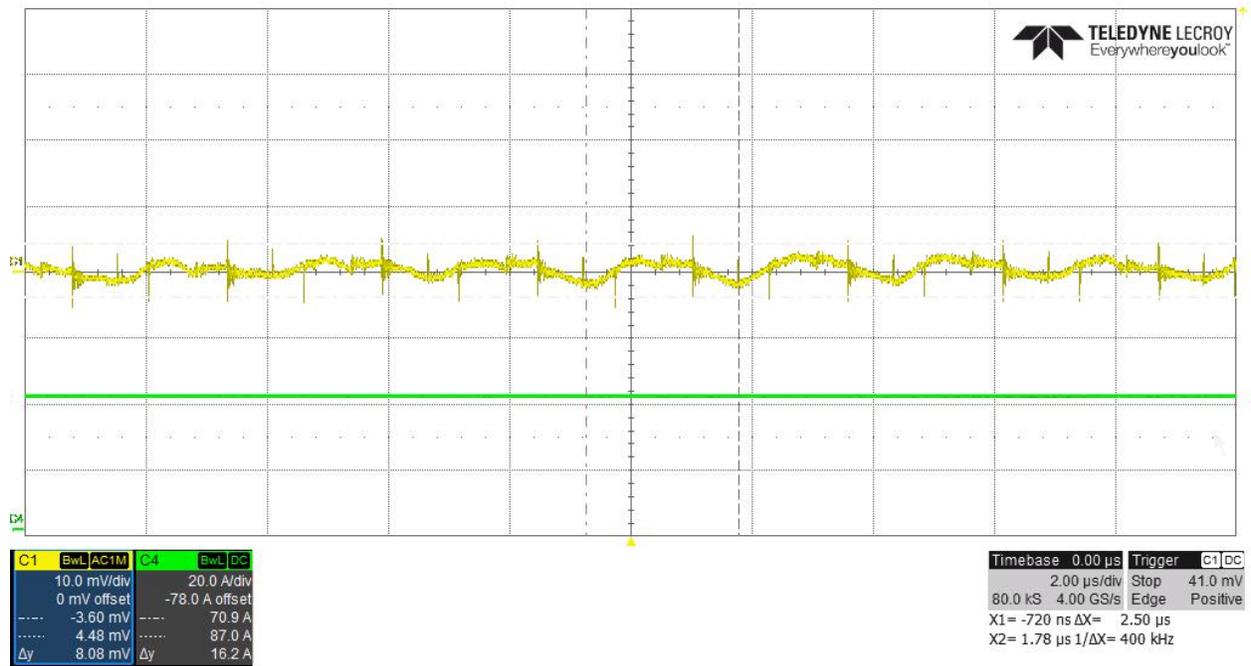
1.6 Output Ripple

The 0.85V output ripple is shown in Yellow below. The Iout is shown in green at 0A and 40A out. Vripple was ~5.2mVpp with no load and ~8.08mVpp




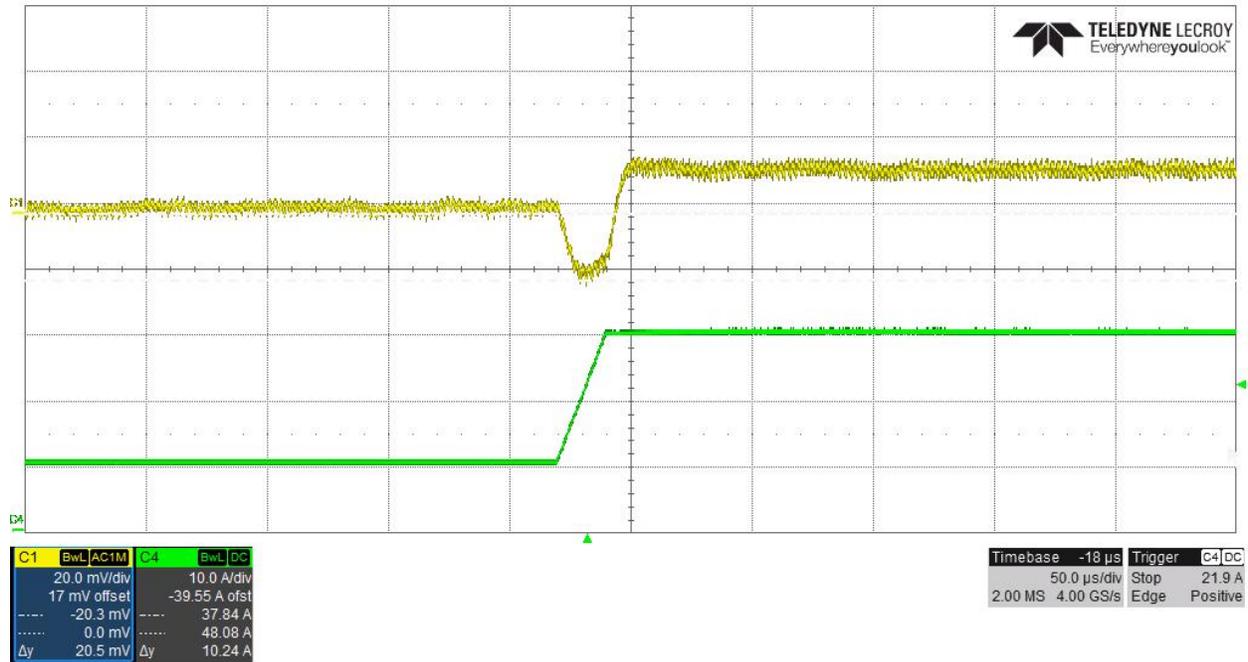1.7 Transient response


The transient response is shown in the plots below where the yellow trace is the AC coupled output voltage. Green trace represents the output current. The current step is 10A-30A at 1A/us slew rate.



Load step- Vtrans= 20.5mV

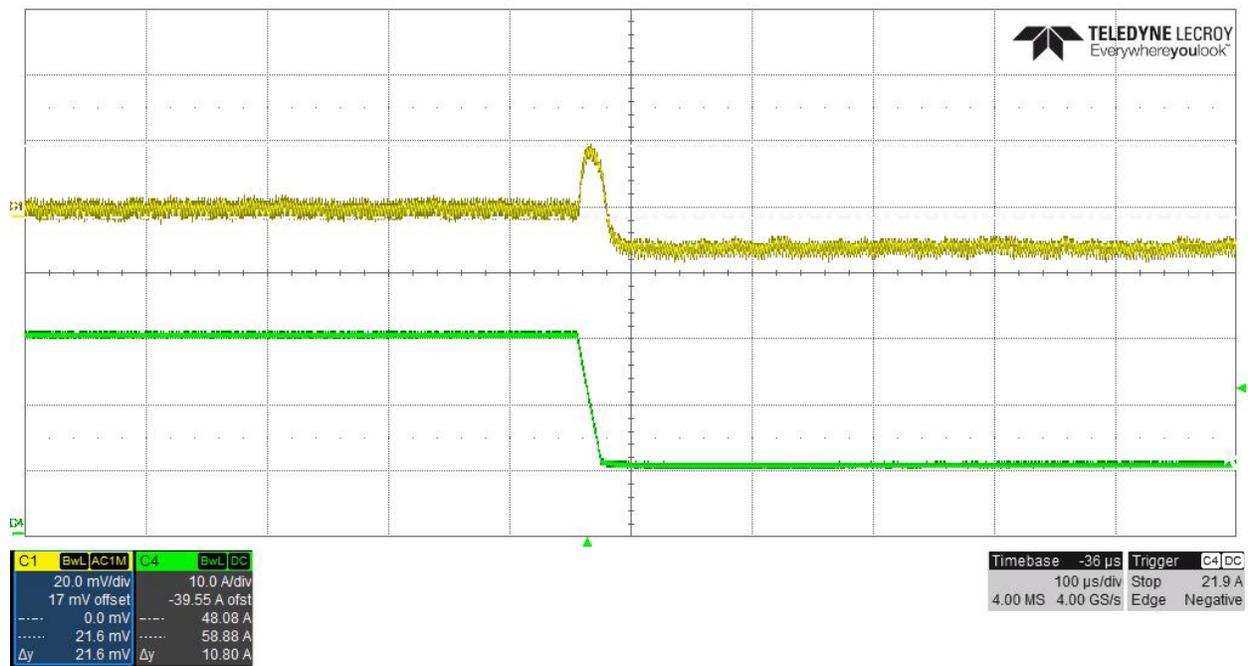


Load dump- Vtrans= 21.6mV

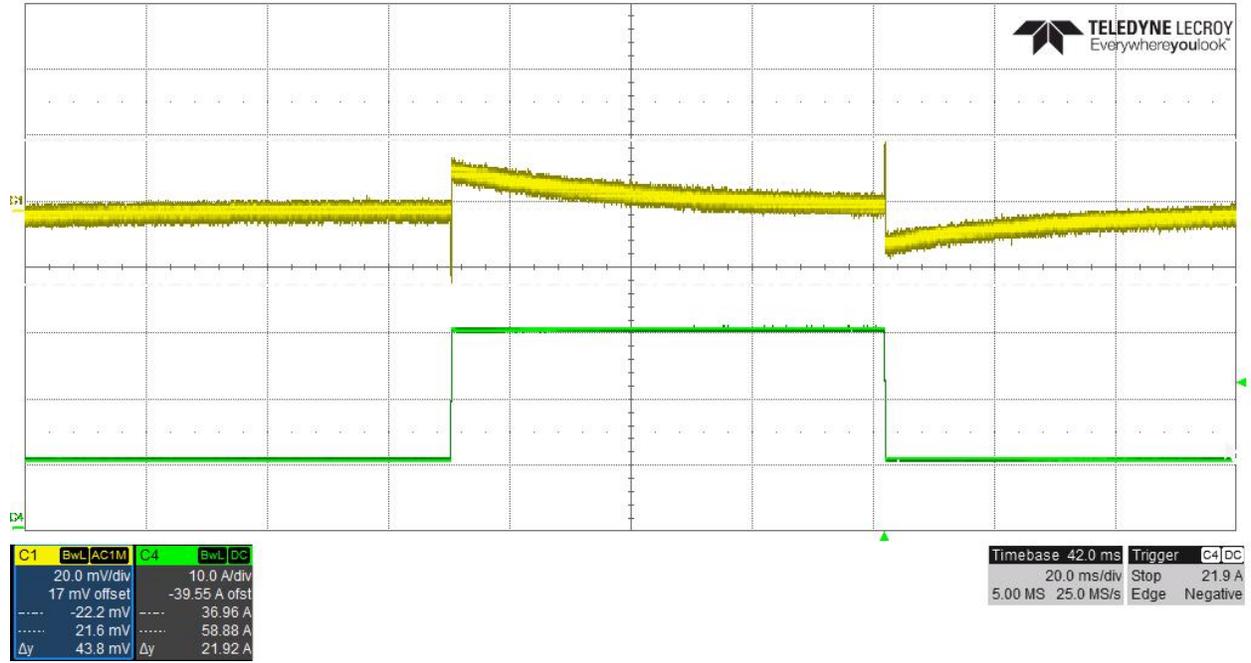


Full load Transient- $V_{trans} = 43.8\text{mVpp}$

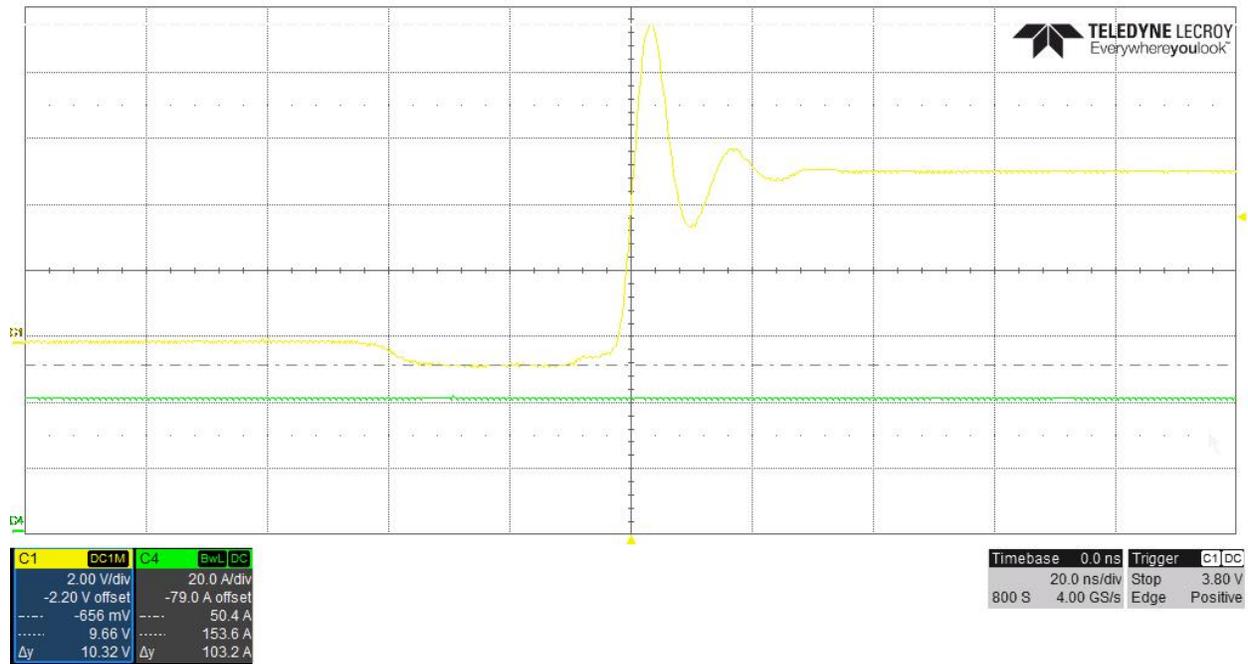1.8 Switch waveforms


The switch node is shown for one phase below at 40A load with the full bandwidth.




Vsw max = 9.66V @ 40A out

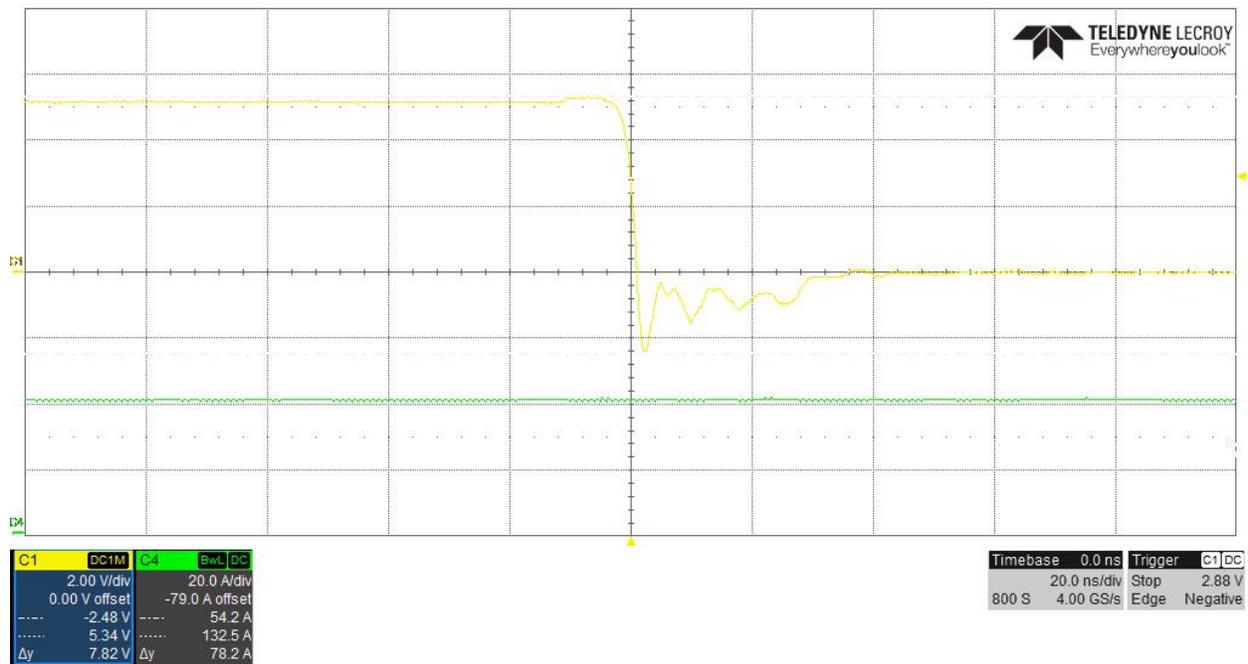

Vsw min = -2.48V @ 40A out

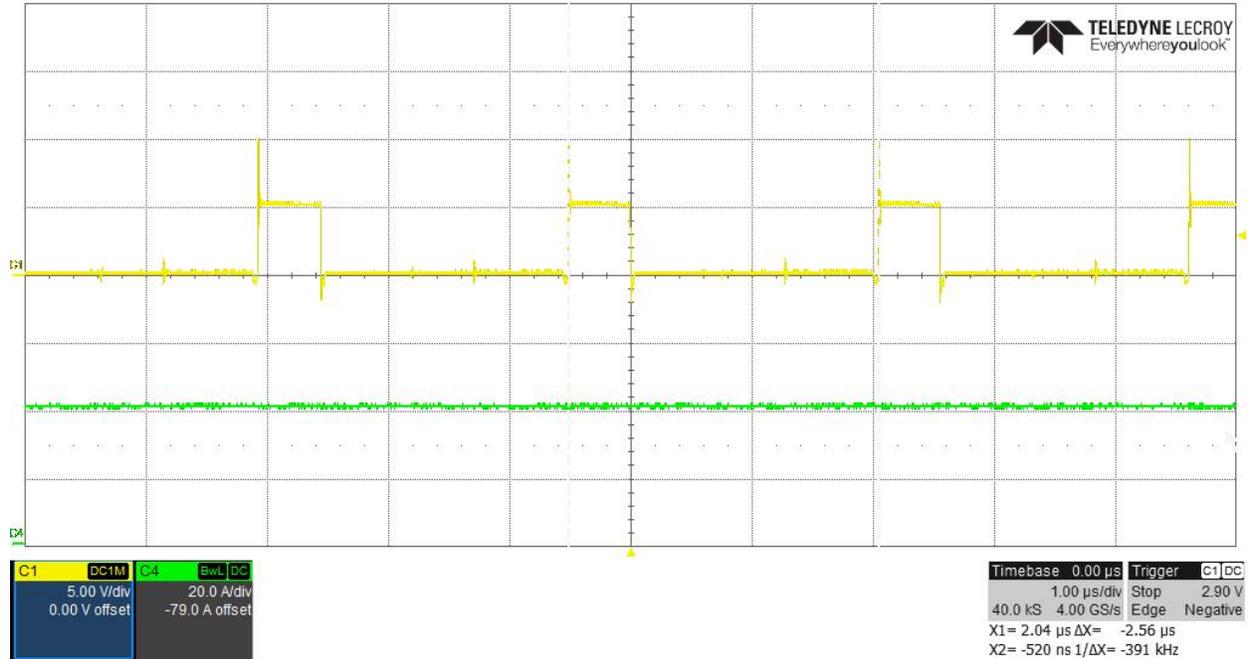

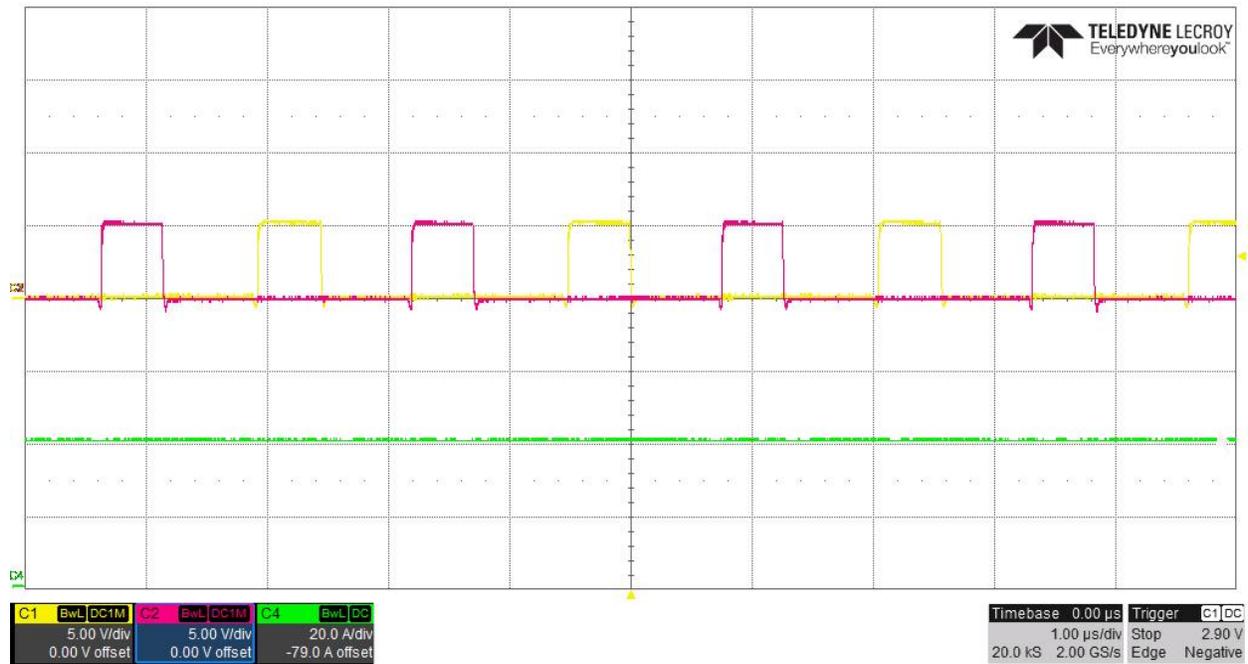
Multiple switching cycles showing fsw = 391Khz



Dual Phase switch node showing 180deg out of phase operation

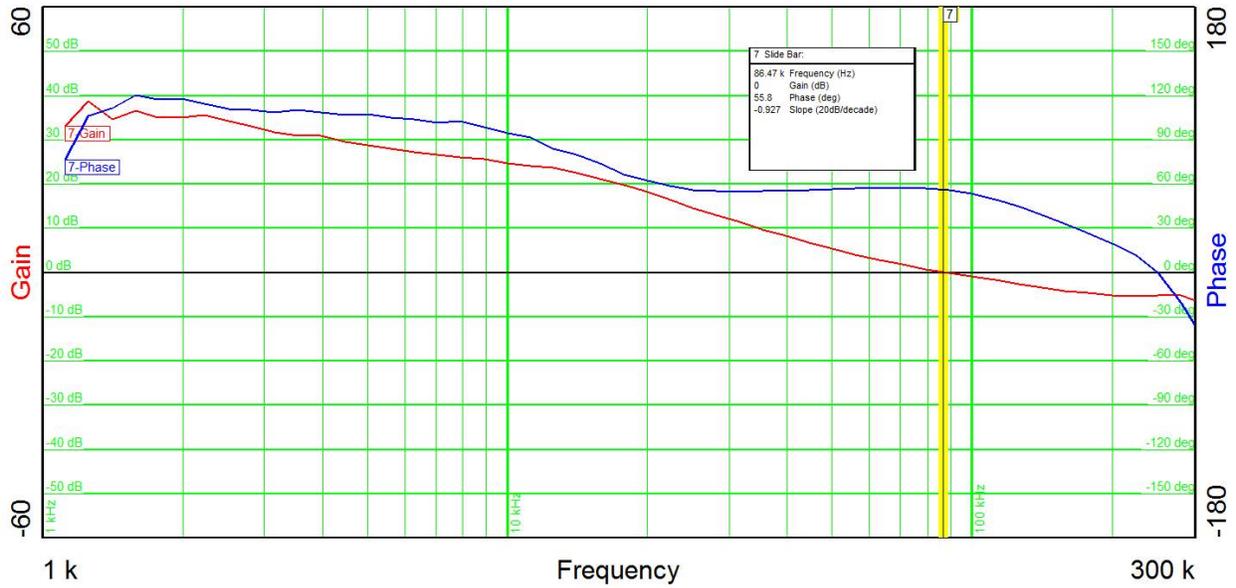1.9 Loop Response

The loop response of the power supply at 5V_{in} and 40A load current is shown below. The bandwidth is 86.47kHz with ~55° of phase margin.



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated