

# How to Prevent Errors in Voltage Readings When Using Multiplexers with High Input Impedance Op-Amps



Kameron Hill

## Multiplexers in Cost-Optimized Signal Processing Applications

To achieve cost-effective sensor data processing, system designers often use a bidirectional analog multiplexer with operational amplifiers (op-amps) to create an input interface. This combination allows one multiplexer to connect to multiple downstream signal paths, each with different gain configurations for the op-amps. This combination enhances data transmission efficiency and functionality from a single sensor.

A problem can occur when the input resistance of an op-amp, such as the TLV9004, is significantly greater than the off resistance of a multiplexer. If these compatibility issues are not considered during system design, voltage errors can arise on the multiplexer's unselected signal path. This can lead to incorrect voltage readings being transmitted downstream to various data processing devices, resulting in measurement errors in the application.

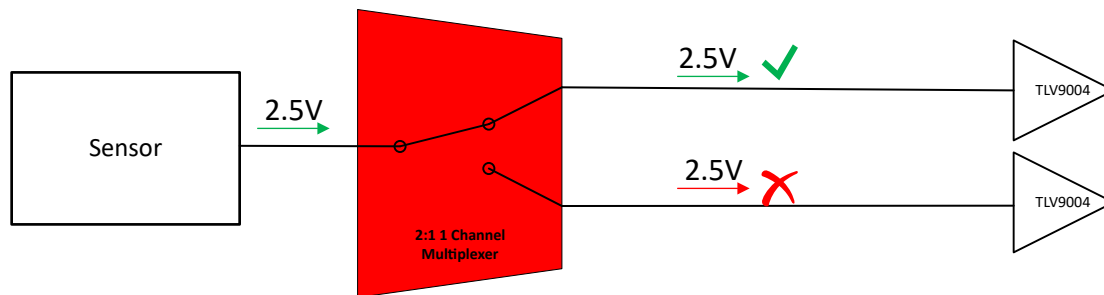


Figure 1. Example of Voltage Error on Unselected Signal Path of Multiplexer

## How to Prevent Voltage Error on Unselected Signal Paths


To prevent voltage errors that may arise on the unselected signal path in this application, designers can implement a bleeder switch in combination with a pull-down resistor placed parallel to the operational amplifier (op-amp). This approach is effective because when the bleeder switch is closed, the pull-down resistor becomes parallel to the input resistance of the op-amp. This arrangement alters the resistance ratio between the off-resistance of the multiplexer and the op-amp load resistance. As a result, the off-resistance is greater than the load resistance, allowing more voltage to drop across the multiplexer. This reduces the voltage at the op-amp's input, effectively discharging the floating node or high impedance of the op-amp input. Ultimately, if a strong pull-down resistor is used, the voltage seen by the op-amp's input on the unselected signal path can be approximately 0V.

To implement this solution, the bleeder switch must connect when the signal path is unselected and disconnect when it is selected. This allows the system to transmit the correct voltage reading from the sensor to the op-amp through the selected multiplexer signal path. [Figure 2](#) and [Figure 3](#) show the implementation of the bleeder switch solution, while [Figure 4](#) shows a system implementation of this solution. Furthermore, system designers can alternatively use a bleeder multiplexer to connect pulldown resistors in their application. [Figure 5](#) illustrates how a multiplexer can be used to connect and disconnect multiple pulldown resistors.


To help designers understand the relationship between a multiplexer's off resistance and an op amp's input resistance, as well as to estimate the necessary bleeder resistor for their application, they should start by determining an acceptable voltage level for the op amp's input when the multiplexer signal path is unselected.

Once this voltage level is established, they can use the multiplexer's maximum off-leakage current along with the acceptable voltage level of the unselected signal path to estimate the required bleeder resistor.


For example, if the acceptable voltage on the unselected signal path is 0.2V and the maximum off-leakage current of the multiplexer is 1000nA, then by rearranging Ohm's Law ( $V/I = R$ ), we can find that the bleeder resistor needs to be less than 200 kilohms.

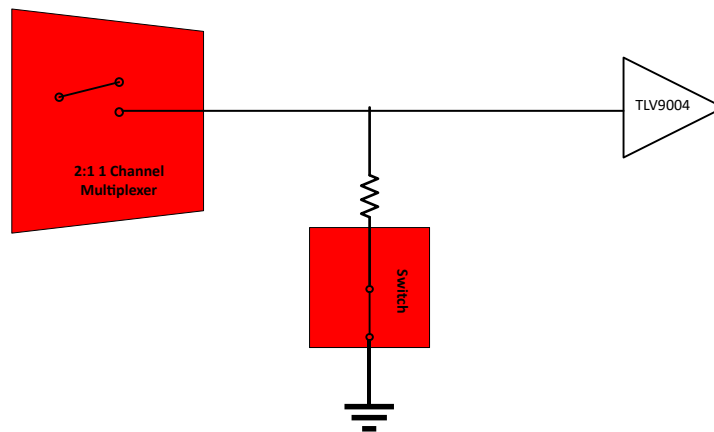


**Figure 2. Bleeder Switch Activated on unselected signal path**

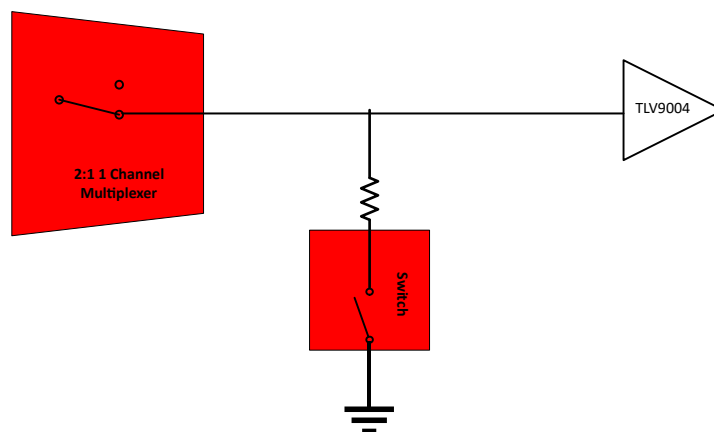

**Figure 3. Bleeder Switch De-activated on selected signal path**

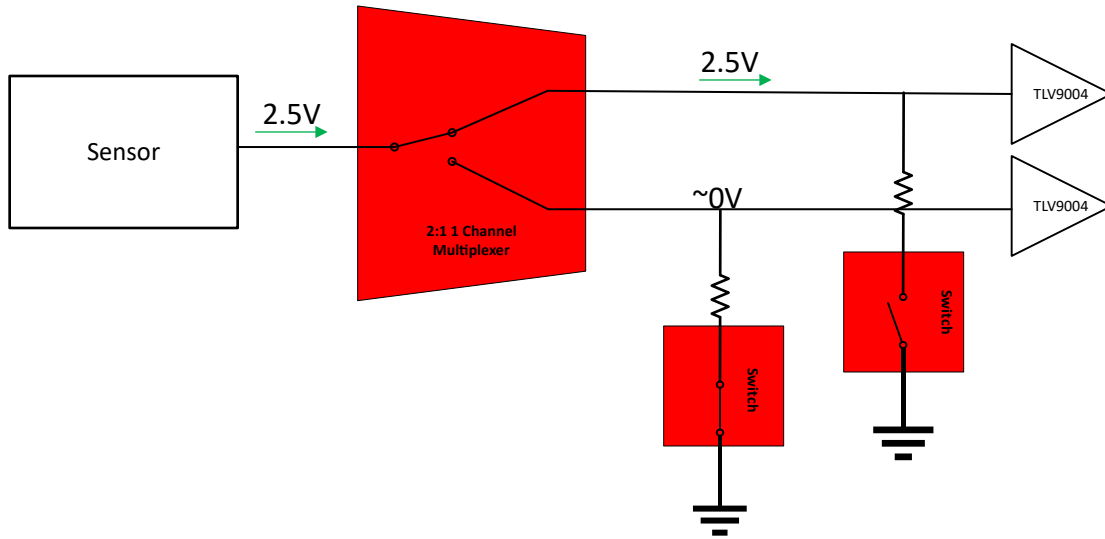

**Figure 4. System Implementation of Bleeder Switch Solution**

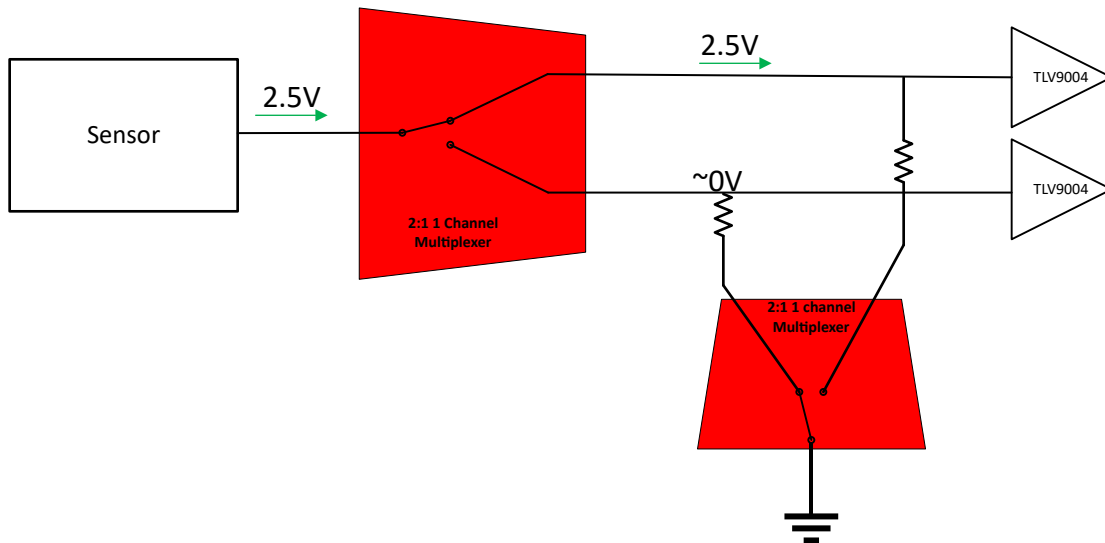

**Figure 5. System Implementation of Bleeder Multiplexer Solution**

## Design Considerations

- The bleeder switch or multiplexer connected to the design must be rated for the same voltage and current specifications as the multiplexer connected to the sensor. This compatibility is crucial to prevent damage to the bleeder switch or multiplexer.
- Learn about multiplexer [off resistance here](#).
- Learn about multiplexer parameters with [TI Precision Labs Videos](#).
- Ask a question on our [TI E2E™ Design Support Forum](#).

**Table 1. Recommended Parts for Bleeder Switch/Multiplexers**

| Part Number   | Supply Range (V) | Configuration         | Channel Count | Control Logic       |
|---------------|------------------|-----------------------|---------------|---------------------|
| TS5A3166      | 1.65 to 5.5V     | 1:1(SPST) Switch      | 1             | Active High         |
| SN74LVC1G66   | 1.65 to 5.5V     | 1:1(SPST) Switch      | 1             | Active High         |
| CD74HC4066    | 2 to 10V         | 1:1(SPST) Switch      | 4             | Active High         |
| TS5A3167      | 1.65 to 5.5V     | 1:1(SPST) Switch      | 1             | Active Low          |
| TMUX1219      | 1.08 to 5.5V     | 2:1(SPDT) Multiplexer | 1             | Active High and Low |
| SN74LVC1G3157 | 1.65 to 5.5V     | 2:1(SPDT) Multiplexer | 1             | Active High and Low |
| TMUX4053      | 5 to 24V         | 2:1(SPDT) Multiplexer | 3             | Active High and Low |

## Trademarks

All trademarks are the property of their respective owners.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265

Copyright © 2025, Texas Instruments Incorporated