

How to cut PLC output power dissipation in half using an adaptive supply

Ahmed Noeman, systems engineer, precision amplifiers

The 4-20 mA current loop is a common signaling scheme for control systems. Field transmitters send sensor readings as 4-20 mA signals, and programmable logic controller (PLC) 4-20 mA outputs control many actuators. Increased channel count for PLC modules is a major industrial trend but creates a challenge for PLC current output modules because of power dissipation.

The output stage of the PLC current output channel shown in **Figure 1** is powered by a supply voltage (V_S) and connected to an external load (R_L). If the maximum R_L specified is 800Ω and the assumed headroom voltage (V_H) is 4V, for driving 20mA, V_S needs to be $\geq 20V$.

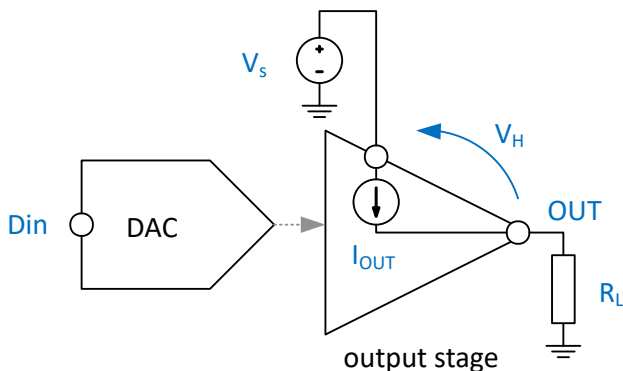


Figure 1. Power losses at the output stage.

If you connect the same module to a small load or short circuit, the power loss within the channel will be $V_H \times 20\text{mA} = 0.4\text{W}$. This is quite high. Many modules limit the maximum load to 600Ω to reduce overall power losses. Derating the module output is another approach that manufacturers use, where the ambient temperature determines how many channels the user can enable, and the maximum current in each.

Equation 1 calculates power loss in the output stage.

$$P_{\text{loss}} = I_{\text{OUT}}(V_S - R_L I_{\text{OUT}}) \quad (1)$$

Note

The most convenient approach to adaptive power is to use a DAC that intrinsically supports adaptive power and integrates the output stage. TI's one-channel DAC8771 and four-channel DAC8775 integrate a buck-boost converter per channel with V_S between 12V and 36V, generating both negative and positive variable supplies (with a maximum span of 36V) using a single external inductor per channel.

Choosing the right DC/DC

Finding the proper DC/DC converter for adaptive power is challenging because of these requirements, which are contradictory:

- High efficiency at low loads (4-20 mA). Because this is generally possible in pulse frequency modulation (PFM), the DC/DC has to support this mode. Expect an approximate 50% efficiency improvement vs. forced pulse-width modulation (PWM) mode.
- Relatively high peak current ($>0.5\text{A}$) for fast settling. The peak current divided by the decoupling capacitances determines the output maximum voltage rate of change.
- V_{OUT} within 4V to 24V, achieved by either a buck or boost converter based on the input voltage.
- A relatively small inductor to reduce solution size. A high switching frequency ($\geq 300\text{kHz}$) is required.
- Available in a small package.

Some parts that fulfill these requirements are:

LMR516xx: 65V input, PFM versions at 400kHz/1.1MHz, 0.6A/1A output current

LMR544xx: 36V input, PFM at 1.1MHz, 0.6A/1A output

LMR3650x: 3V-65V input, adjustable 200kHz-2.2MHz, 0.1A/0.15A output (if fast settling is not critical)

Controlling the DC/DC output

Nonfixed DC/DC converters use a feedback node kept at a constant reference voltage level through a high gain amplifier. By connecting a resistive potential divider between the converter output voltage and the feedback node, you can control the output voltage, as shown in **Figure 3**.

Figure 3.

Because the converter keeps VREF fixed, you can calculate VS using **Equation 2**.

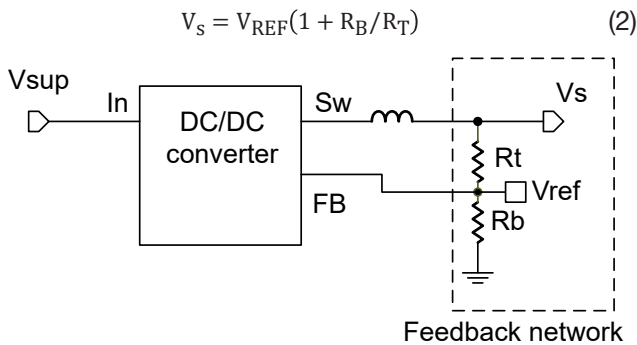


Figure 2. Feedback network for a DC/DC converter.

The change of output voltage requires changing the feedback divider. **Figure 3** shows three different ways to change the divider: variable sourcing current (a), variable sinking current (b), or using a variable voltage source and resistor (c). **Figure 3** also shows the transfer function (control variable, current or voltage vs. VS).

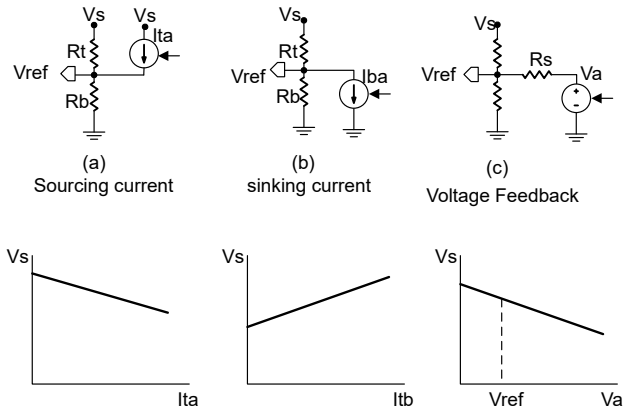


Figure 3. Adaptive control circuits and their transfer functions.

Applying Kirchoff's current law on the VREF node in each case yields the transfer function for case a:

$$I_{ta} + (V_S - V_{REF})/R_t = V_{REF}/R_b \tag{3}$$

Rearranging **Equation 3** results in **Equation 4**:

$$V_S = (1 + R_t/R_b)V_{REF} - I_{ta}R_t \tag{4}$$

Equation 5 shows similar calculation for case b:

$$V_S = (1 + R_t/R_b)V_{REF} + I_{ba}R_t \tag{5}$$

Equation 6 calculates case c:

$$V_S = (1 + R_t/R_b + R_t/R_s)V_{REF} - R_t/R_s V_a \tag{6}$$

A simple calculation can find the proper range of the control variable to achieve the required VS range given the reference voltage level present on the feedback pin and the chosen resistor values.

Example circuit using sourcing current

Figure 4 shows the construction of a high-side current source using an operational amplifier, PMOS transistor M1, and a resistor. Equation 8 calculates the current generated as:

$$I_{ta} = (V_S - V_{OUT})/R_c \tag{7}$$

You will need to consider the input/output and supply range of the operational amplifier and the maximum gate-to-source voltage (VGS) of M1. Further simplifying

the circuit by removing the operational amplifier, **Equation 8** calculates the current generated as:

$$I_{ta} = (V_S - V_{OUT} + V_{th})/R_c \tag{8}$$

This saves power, cost and area, with some inaccuracy of current from the variation in threshold voltage (V_{th}).

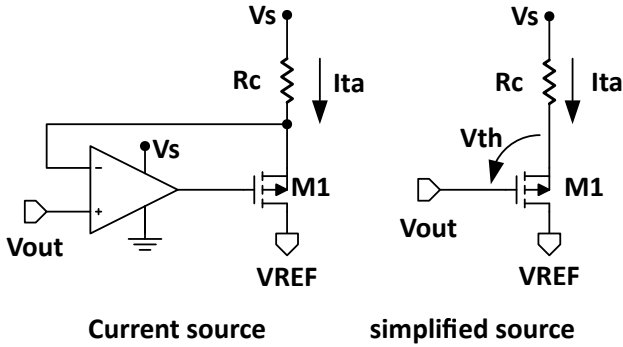


Figure 4. Current source feedback circuit.

The TI XTR200 is a 4-20 mA current transmitter with V_S from 8V to 60V and V_H of 3V. If the load is up to 800Ω, V_{OUT} goes up to 16V with 20mA of current. This V_S has to track the output. At $V_{OUT} = 0V$, $V_S = 8V$, and at $V_{OUT} = 16V$, $V_S = 19V$. Use **Equation 8** and **Equation 5** to calculate resistors R_t , R_b and R_c . You will find that it is not possible to maintain $V_H > 3V$ without increasing the headroom for the low V_{OUT} .

Values $R_t = 80k\Omega$, $R_b = 3k\Omega$ and $R_c = 60k\Omega$ produce the output-supply curve shown in **Figure 5**. Headroom is dependent on the output because this simple design uses only R_c as design variable. More complex circuits can overcome this limitation. But even with this simple circuit, the maximum power dissipation drops to half or less compared to the nonadaptive case. Any low-power rail-to-rail operational amplifier such as the OPA2990 will work in place of U_2 , as shown in **Figure 6**.

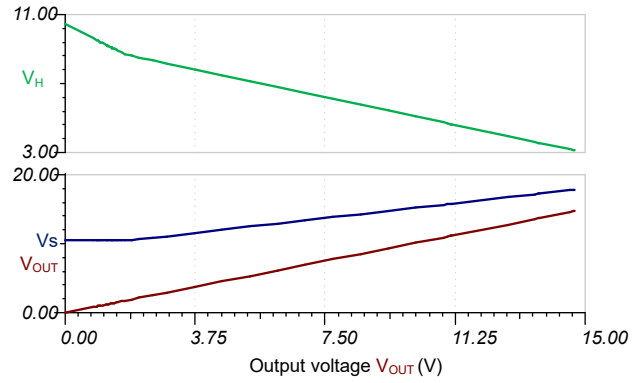


Figure 5. V_S - V_{OUT} , V_H - V_{OUT} relation.

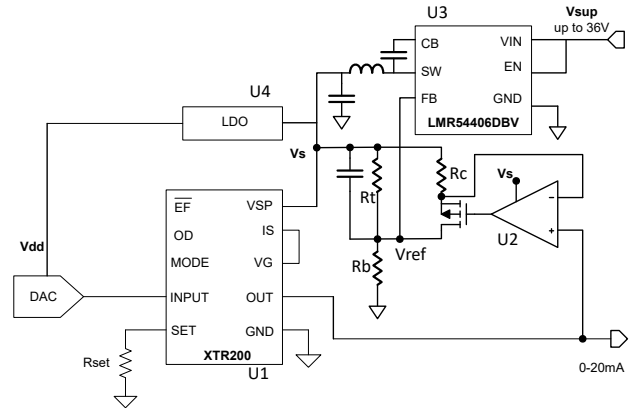


Figure 6. Output stage using the XTR200 with an adaptive supply.

Note

Simulation: The switching regulator simulation is quite long. Replacing the DC/DC with a low-dropout regulator (LDO) that has a similar V_{REF} and similar input and output ranges can speed up DC simulation and enable easy creation of the transfer function graph. If the LDO has a different V_{REF} , insert a voltage-controlled voltage source (VCVS) between the feedback node and the LDO's actual feedback node. For example, if $V_{REF} = 1.2V$, and you want to design for the TI LMR54406 buck converter, which has a $V_{REF} = 0.8V$, you can add a VCVS with gain of 1.5 to convert the 0.8V into 1.2V.

Example circuit using voltage feedback

For lower VS applications, use the output stage shown in my application note, "**Protected, Low-Noise, Combined V-I Output Stage as Analog Output Building Block,**" working down to 5V.

The LMR51606 DC/DC simplified circuit shown in **Figure 7** omits the input capacitance and electromagnetic interference protection filters. The buck converter uses a small inductor ($L1 = 15\mu\text{H}$) and output capacitance ($22\mu\text{F}$) optimized to provide low ripple and enable fast supply ramping.

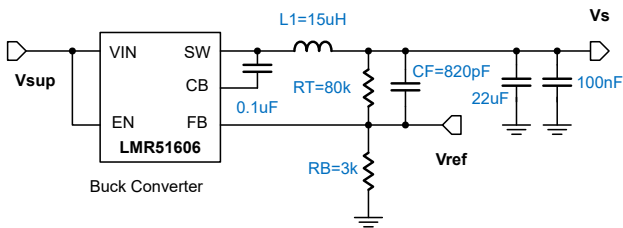


Figure 7. DC/DC circuit.

Use **Equation 2** to calculate the values of R_t and R_b so that $V_s = 20.8\text{V}$ when no current is injected into the feedback node so that these values set the maximum supply level.

To achieve better efficiency, the difference amplifier shown in **Figure 8** senses the output headroom, where $V_H = V_S - V_{OUT}$. The difference amplifier has a gain of 0.33V/V so that the steady-state headroom is between 3V and 2.7V based on V_S . The $1\text{M}\Omega$ input impedance reduces error on the output current to $<0.1\%$. It is possible to compensate for this error during calibration.

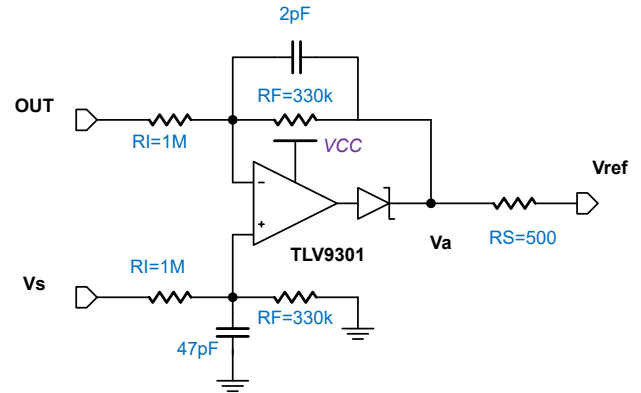


Figure 8. Difference amplifier.

The diode at the operational amplifier output prevents turning sourcing current into sinking, so if the operational amplifier output has a lower voltage than the feedback node, the loop will break. This keeps the upper limit of the VS set by R_t and R_b . The capacitors in the feedback path are essential for dynamic stability of the larger loop, including the DC/DC.

Figure 9 is a simplified overall circuit.

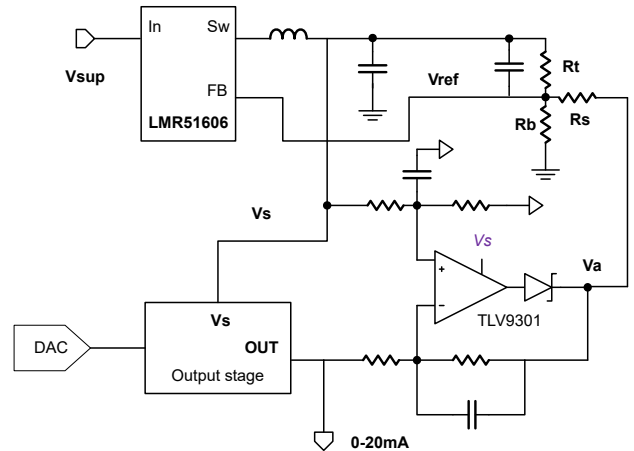


Figure 9. Simplified schematic for adaptive power with a difference amplifier.

Note

Dynamic performance: The output stage response to a DAC output change is typically fast. In contrast, the DC/DC is much slower, and the V_S cannot follow the output at the same pace. Limiting the difference amplifier bandwidth helps smooth this change and allows the converter to ramp properly. In addition, it is necessary to limit the slew rate of the DAC output if it doesn't inherently support slew-rate control. You will have to divide large DAC code changes into smaller changes over a longer period, creating a staircase DAC output that allows the DC/DC converter to settle without overshoot or oscillation.

Measurements and performance

Figure 10 shows the power losses for different output currents as well as various loads. Power losses are calculated as the input power to the DC/DC converter minus the output power to the load. The power losses never exceed 180mW, which translates to >50% of power savings.

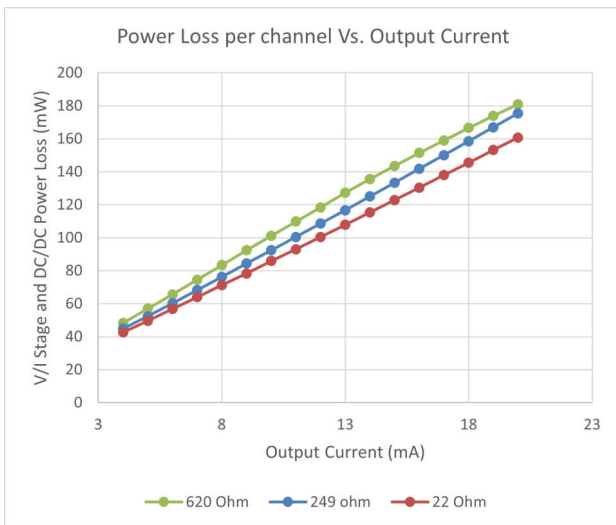


Figure 10. Power losses vs. output current.

Figure 11 shows the efficiency for different currents and loads. The efficiency of the DC/DC converter is calculated as the output power from the converter

divided by the input power. The efficiency ranges between 75% and 90%.

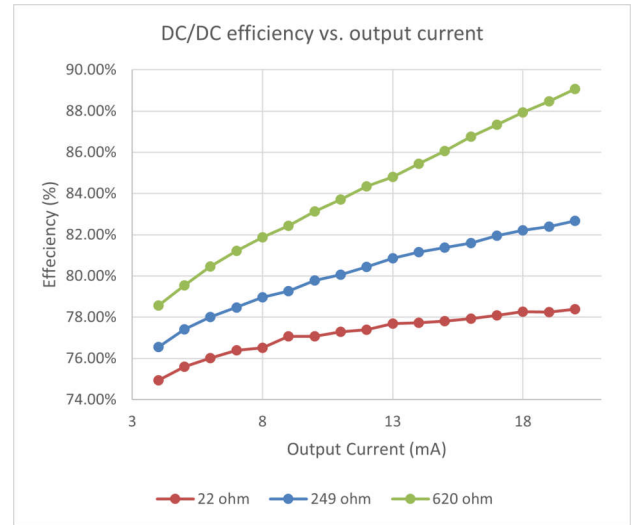


Figure 11. DC/DC efficiency vs. output current.

Precision and noise

A high-resolution analog-to-digital converter measures the effect of the DC/DC ripples on the output, converting 16,000 samples with a 640Ω load at 4 mA and 20 mA, respectively.

Table 1 summarizes the noise calculation and corresponding precision.

Output	4mA	20mA	Unit
Mean	4.019	20.17	mA
Root mean square (RMS) noise	325	530	nA
Peak-to-peak noise	2.78	3.51	μA
RMS resolution	18.2	17.5	Bits

Table 1. Noise performance of the adaptive circuit.

The results show that adaptive power doesn't affect the output stage performance, and can support 16-bit output resolution.

Settling time and dynamic performance

Settling time and the stability of the adaptive power loop are of great importance. Figure 12 shows that input ramping to full-scale in 200μs results in a stable output with simple stepping of the input of the output stage.

Figure 12 shows a 10V step over a 560Ω load, with the full-scale input voltage to the output stage ramped over seven steps to the full scale of 2.5V. The figure also shows a settling time <math><200\mu\text{s}</math>.

The falling edge is slow because the decoupling and output capacitors need to discharge through the circuit and external load. This doesn't affect performance and is not critical.

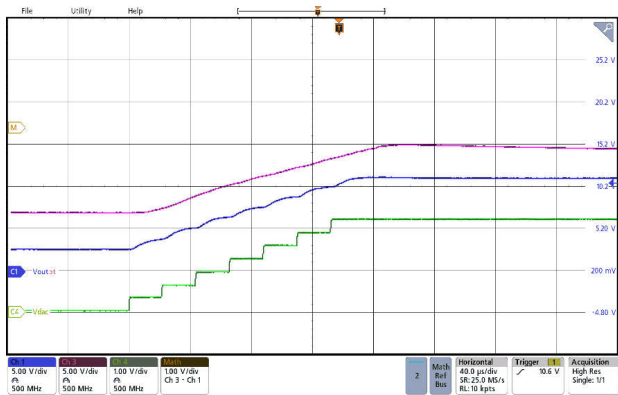


Figure 12. Settling performance of the output stage and adaptive supply.

Conclusion

The measurement results demonstrate that adaptive supply techniques deliver tangible benefit by achieving over 50% power savings compared to fixed-supply implementation. The 17.5 to 18.2 bits of RMS resolution prove that thermal management improvements don't come at the expense of signal quality. As PLC modules continue to pack more channels into smaller footprints, the techniques presented here transition from optimization strategies to practical necessities for next-generation industrial automation systems.

Additional resources

- See the TI Developer Conference presentation, "[System Power Savings Using Dynamic Voltage Scaling.](#)"
- Check out the [Less Than 1-W, Quad-Channel, Analog Output Module With Adaptive Power Management Reference Design.](#)
- For more insight into the role of the feedforward capacitor to enhance dynamic performance, read the application report, "[Optimizing Transient Response of Internally Compensated DC/DC Converters With Feedforward Capacitor.](#)"

About the author

Ahmed Noeman is a systems engineer at Texas Instruments, specializing in defining integrated solutions for industrial applications. Ahmed has more than 20 years of semiconductor experience in areas including system design, IC design and IC verification. Ahmed received an M.S. and B.S. in electrical engineering from Ain Shams University in Egypt.

Important Notice: The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

All trademarks are the property of their respective owners.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you fully indemnify TI and its representatives against any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#), [TI's General Quality Guidelines](#), or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products. Unless TI explicitly designates a product as custom or customer-specified, TI products are standard, catalog, general purpose devices.

TI objects to and rejects any additional or different terms you may propose.

Copyright © 2026, Texas Instruments Incorporated

Last updated 10/2025