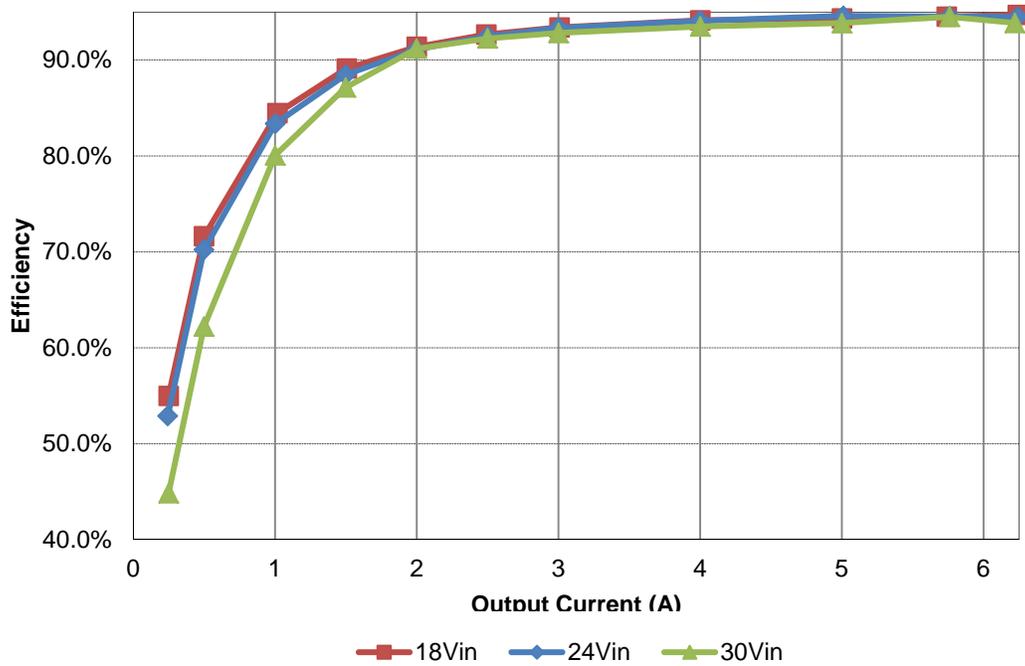


1 Photo

The photographs below show the top and bottom views of the PMP8944 Rev A demo board. The circuit is built on PMP8424 Rev A PCB board.



2 Efficiency



Vin	Iin	Vout	Iout	Pout	Losses	Efficiency	Vin	Iin	Vout	Iout	Pout	Losses	Efficiency
17.99	8.75	23.89	6.24	149.0736	8.3389	94.7%	24.05	6.56	23.89	6.24	149.0736	8.6944	94.5%
18.02	8.05	23.89	5.74	137.1286	7.9324	94.5%	24.02	6.06	23.89	5.76	137.6064	7.9548	94.5%
18.01	7.03	23.89	5	119.45	7.1603	94.3%	24.01	5.27	23.89	5.01	119.6889	6.8438	94.6%
18.03	5.63	23.89	4	95.56	5.9489	94.1%	24.01	4.23	23.89	4	95.56	6.0023	94.1%
18.02	4.27	23.9	3.007	71.8673	5.0781	93.4%	24.02	3.198	23.9	3	71.7	5.11596	93.3%
18	3.569	23.9	2.491	59.5349	4.7071	92.7%	24.02	2.691	23.9	2.501	59.7739	4.86392	92.5%
18	2.906	23.9	2	47.8	4.508	91.4%	24.02	2.181	23.9	1.997	47.7283	4.65932	91.1%
17.99	2.245	23.9	1.506	35.9934	4.39415	89.1%	24.02	1.685	23.9	1.498	35.8022	4.6715	88.5%
17.99	1.598	23.9	1.016	24.2824	4.46562	84.5%	24.02	1.196	23.9	1.002	23.9478	4.78012	83.4%
18.02	0.924	23.9	0.499	11.9261	4.72438	71.6%	24.02	0.707	23.9	0.499	11.9261	5.05604	70.2%
18.01	0.601	23.9	0.249	5.9511	4.87291	55.0%	24.03	0.457	23.9	0.243	5.8077	5.17401	52.9%
18	0.2835	23.9	0	0	5.103	0.0%	24.01	0.2249	23.9	0	0	5.399849	0.0%

Vin	Iin	Vout	Iout	Pout	Losses	Efficiency
30.04	5.27	23.89	6.22	148.5958	9.715	93.9%
30.01	4.85	23.88	5.76	137.5488	7.9997	94.5%
30.02	4.24	23.89	5	119.45	7.8348	93.8%
30	3.407	23.89	4	95.56	6.65	93.5%
30.01	2.573	23.89	3	71.67	5.54573	92.8%
29.99	2.158	23.89	2.499	59.70111	5.01731	92.2%
30.01	1.745	23.9	1.998	47.7522	4.61525	91.2%
29.99	1.37	23.9	1.498	35.8022	5.2841	87.1%
30.03	0.995	23.9	1.001	23.9239	5.95595	80.1%
30	0.639	23.9	0.499	11.9261	7.2439	62.2%
30.04	0.442	23.9	0.249	5.9511	7.32658	44.8%
30.03	0.2513	23.89	0	0	7.546539	0.0%


3 Startup

The input was 24V and the output was unloaded.




4 Output Ripple Voltage

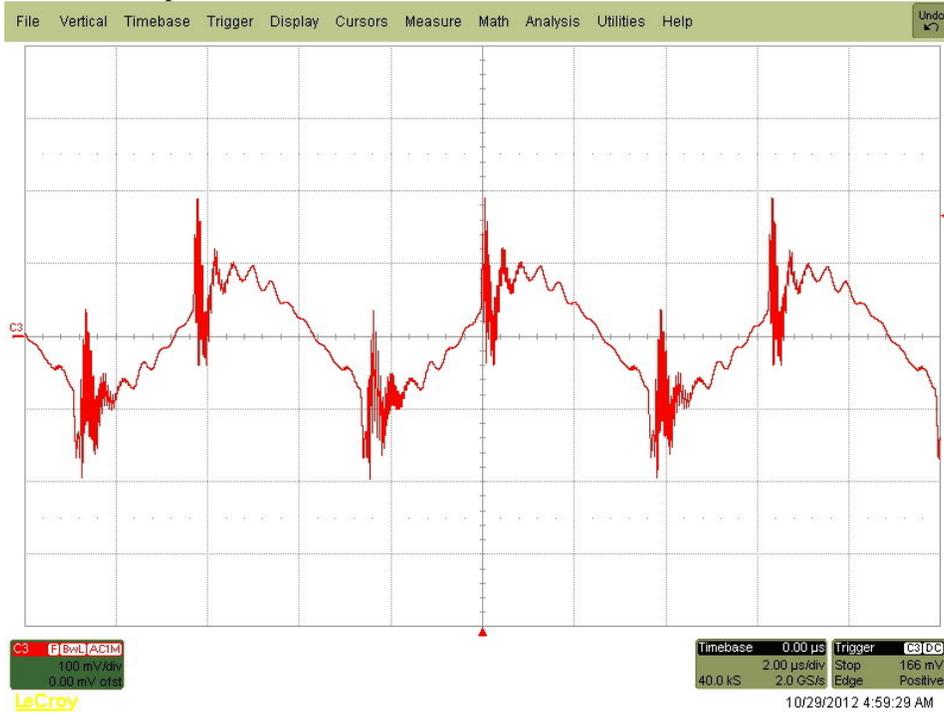The input was 24V and the output was loaded with 6.25A.




5 Frequency Response

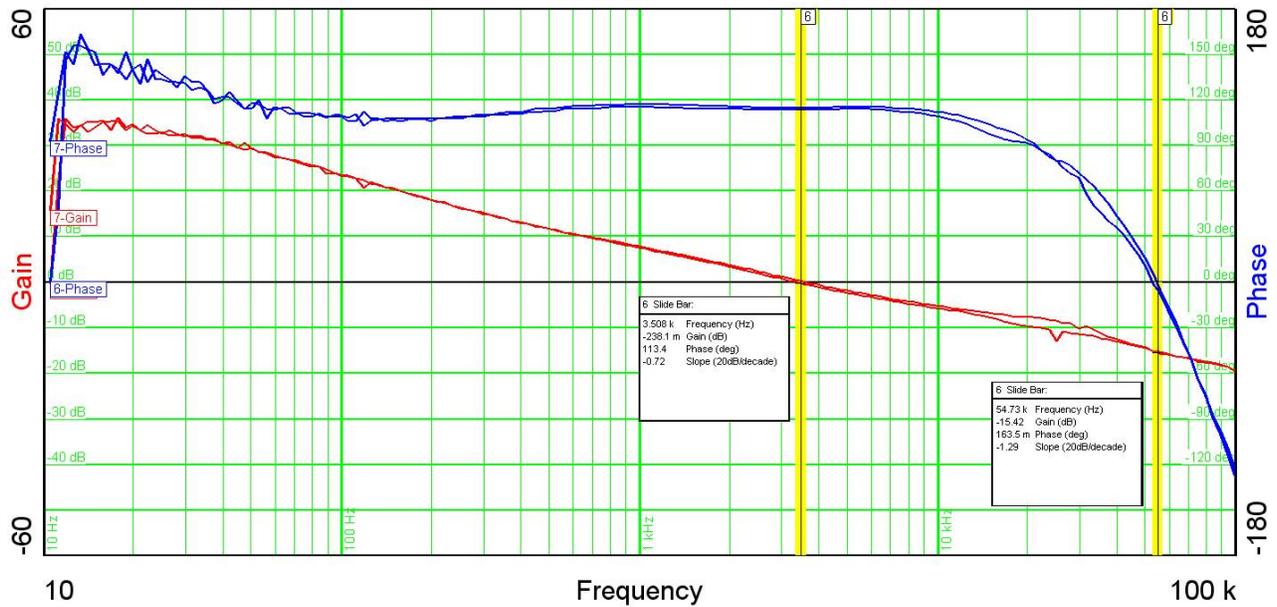The output was loaded with 6.25A. Curve 6 is the frequency response with 18V as input voltage, and Curve 7 is the frequency response with 30V as input voltage.



6 Load Transient Response

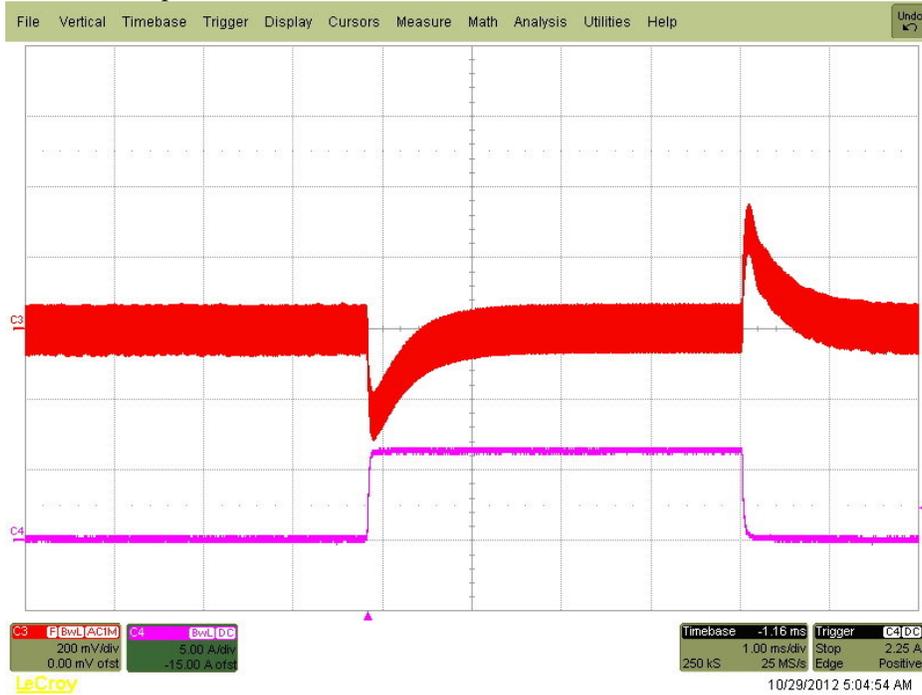The image below shows the response to a 0A to 6.25A load transient.




7 Switching waveforms

The outputs were unloaded in this measurement.


7.1 18Vin

CH1: Q4 & Q5, CH2: Q6, and CH3: Q7.

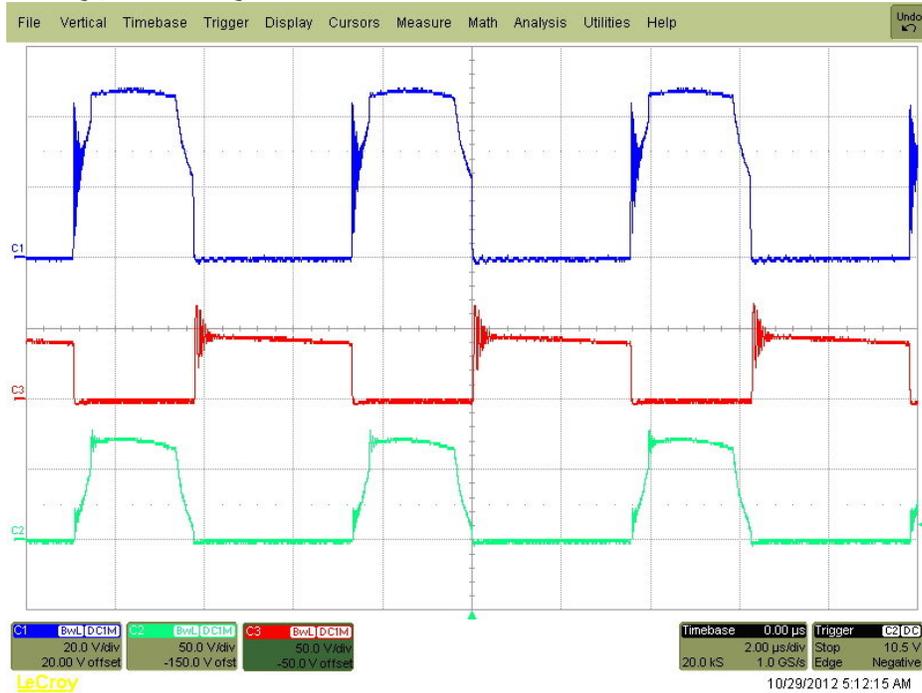

7.2 30Vin

CH1: Q4 & Q5, CH2: Q6, and CH3: Q7.

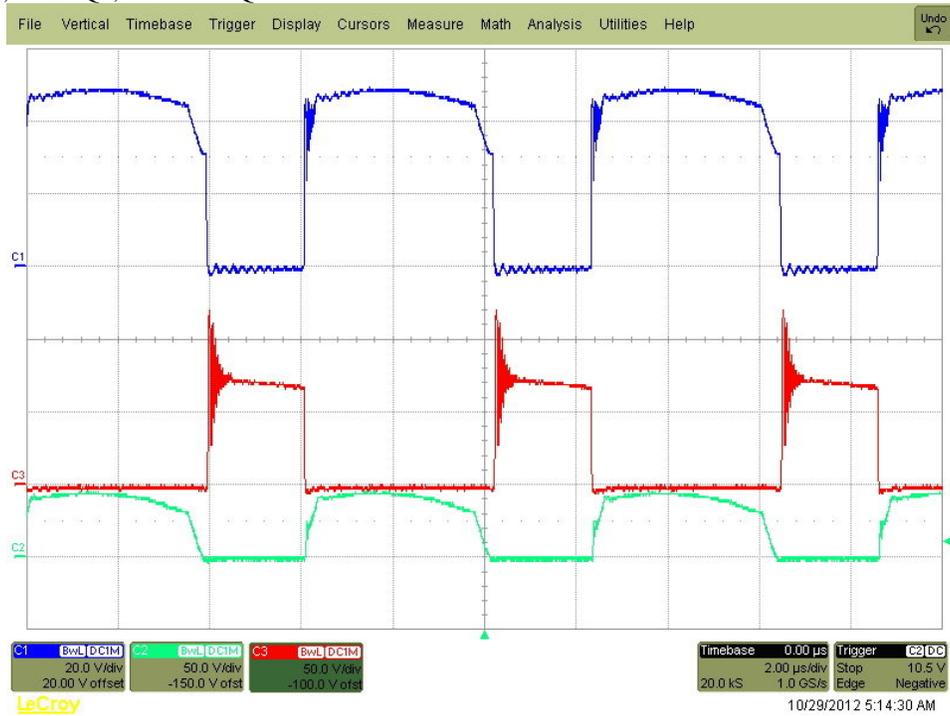

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated