


## 1 Photo

The photographs below show the PMP9073 Rev A assembly. This circuit was built on a PMP9073 Rev A PCB.

### Top side




### Bottom side

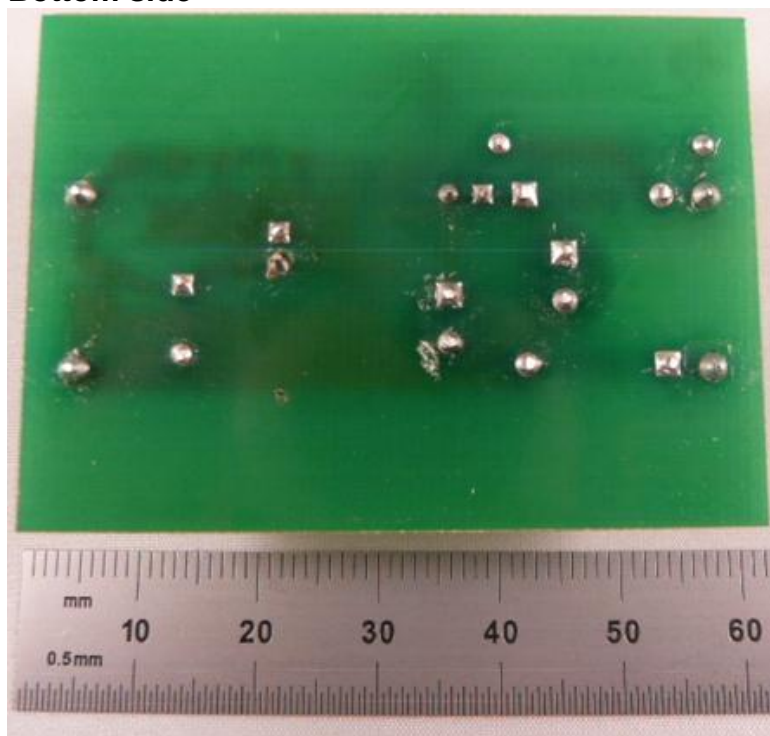
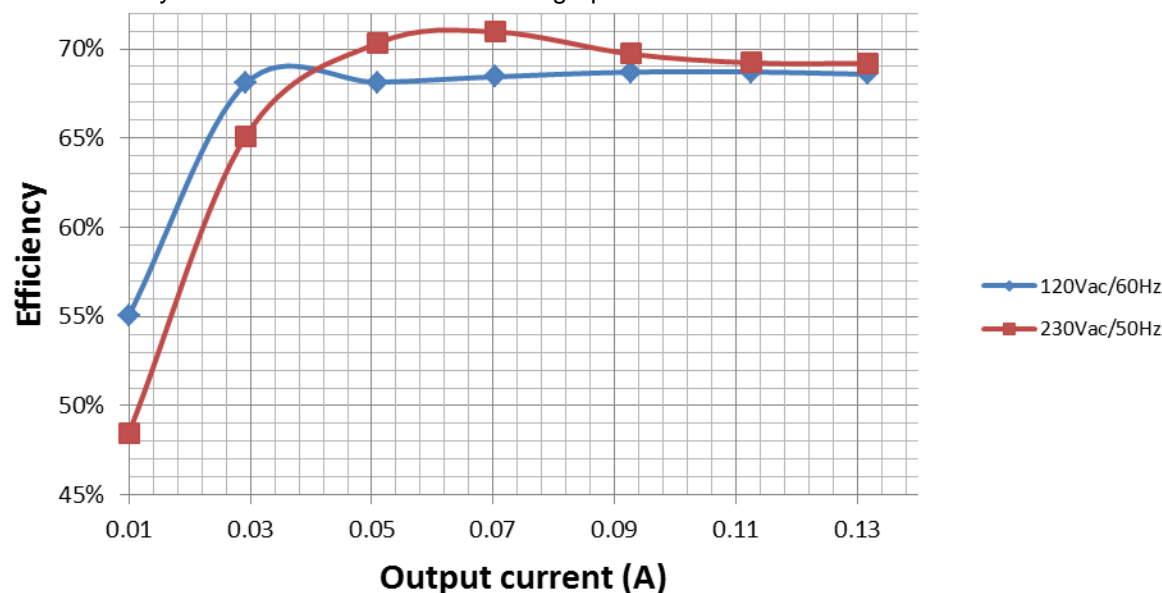
## 2 Converter Efficiency

The efficiency data is shown in the tables and graph below.



### $V_{in}=120V_{AC}/60Hz$

Vin(V)	Iin(mA)	Pin(W)	Vout(V)	Iout(A)	Pout(W)	Losses(W)	Efficiency (%)
120.01	79.63	3.501	18.23	0.1317	2.400891	1.100109	68.58%
119.92	68.94	2.993	18.28	0.1125	2.0565	0.9365	68.71%
120.02	58.61	2.468	18.31	0.0926	1.695506	0.772494	68.70%
119.94	46.59	1.884	18.34	0.0703	1.289302	0.594698	68.43%
119.95	35.52	1.375	18.37	0.051	0.93687	0.43813	68.14%
119.94	22.03	0.7916	18.41	0.02927	0.538861	0.2527393	68.07%
120.03	10.314	0.3381	18.62	0.01	0.1862	0.1519	55.07%
120.07	3.395	0.10576	19.67	0	0	0.10576	0.00%

### $V_{in}=230V_{AC}/50Hz$


Vin(V)	Iin(mA)	Pin(W)	Vout(V)	Iout(A)	Pout(W)	Losses(W)	Efficiency (%)
230	51.08	3.474	18.25	0.1317	2.403525	1.070475	69.19%
230	44.72	2.971	18.28	0.1125	2.0565	0.9145	69.22%
230	37.7	2.432	18.31	0.0926	1.695506	0.736494	69.72%
230	29.12	1.816	18.33	0.0703	1.288599	0.527401	70.96%
230	22.05	1.329	18.34	0.05096	0.934606	0.3943936	70.32%
230	14.243	0.827	18.4	0.02927	0.538568	0.288432	65.12%
230	6.742	0.3842	18.63	0.01	0.1863	0.1979	48.49%
230	2.335	0.15156	19.74	0	0	0.15156	0.00%

### 3 Thermal Images


The thermal images below show a top view and bottom view of the board under 120V<sub>ac</sub>/60Hz and 230V<sub>ac</sub>/50Hz input conditions. The ambient temperature was 20°C with no forced air flow. The output was at full load: 18V/0.13A.



**V<sub>in</sub>=120V<sub>AC</sub>/60Hz**

**Top Side**

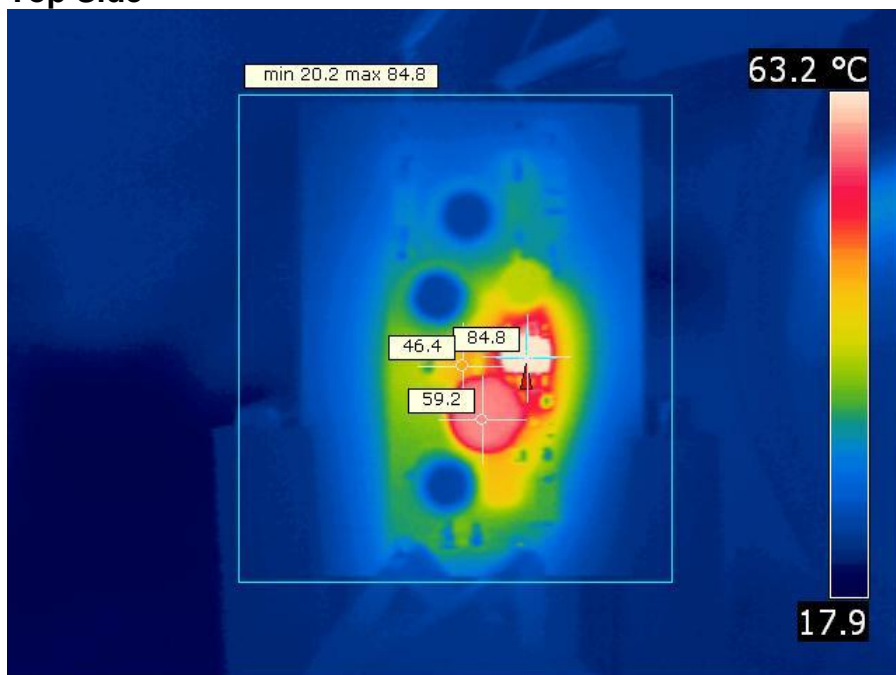

**Bottom Side**

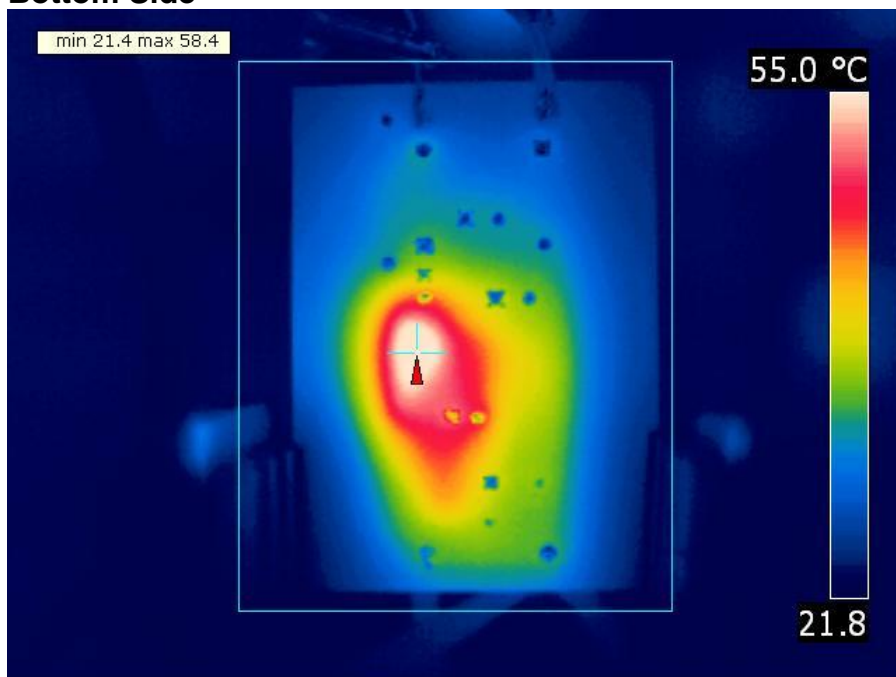


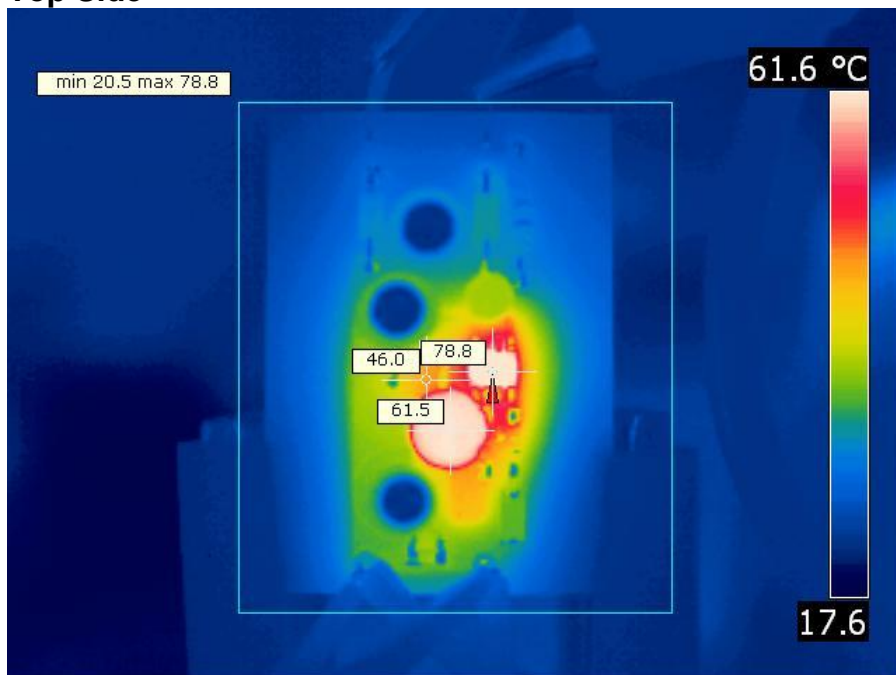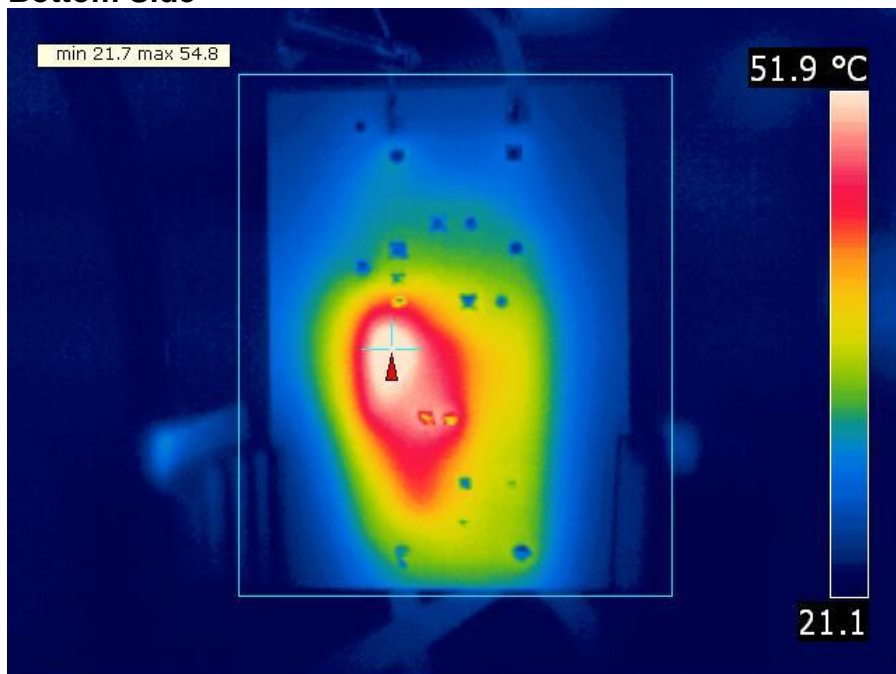**$V_{in}=230V_{AC}/60Hz$** **Top Side****Bottom Side**


## 4 Startup Waveforms

The output voltages at startup are shown in the images below.


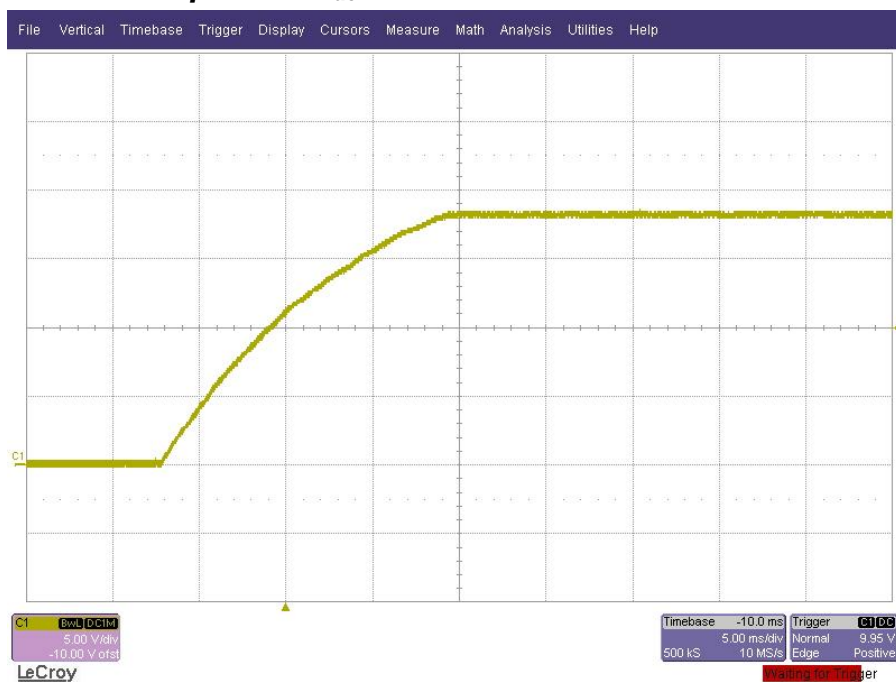
### 4.1 Start Up @ 120V<sub>ac</sub>: 18V/0.13A.


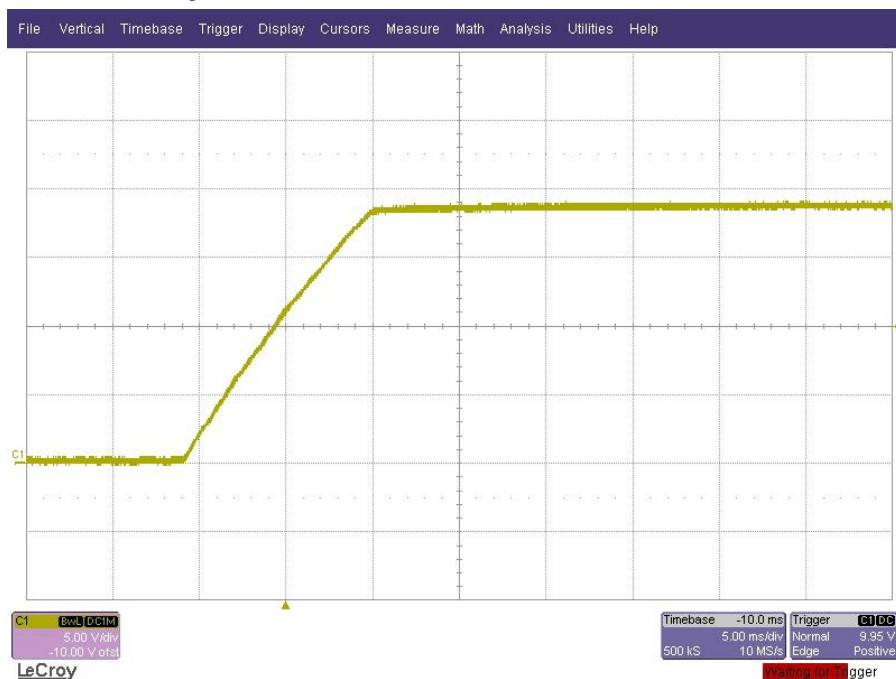
### 4.2 Start Up @ 120V<sub>ac</sub>: no load.



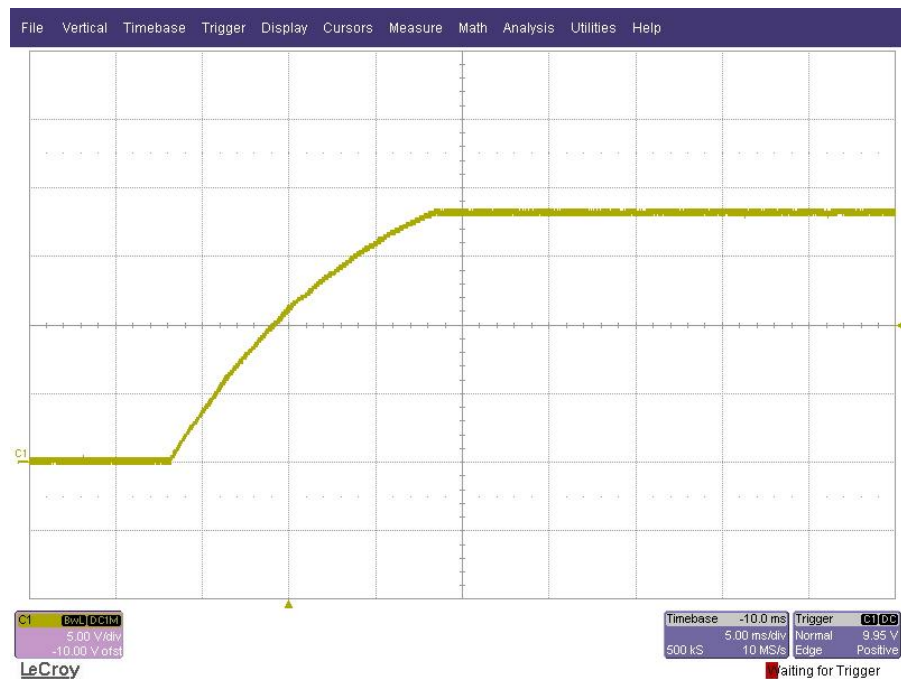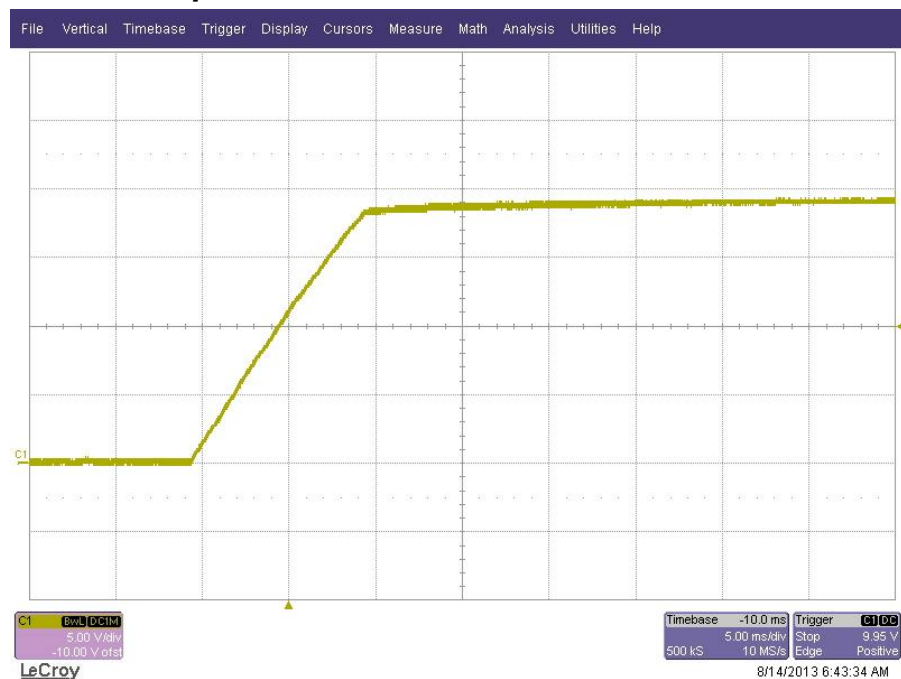

**4.3 Start Up @ 230V<sub>ac</sub>: 18V/0.13A.****4.4 Start Up @ 230V<sub>ac</sub>: no load.**

## 5 Turn off

The output voltage at turn off transient is shown in the image below at full load (18V/0.13A).

### 5.1 Turn off @ 120V<sub>ac</sub>: 18V/0.13A.




### 5.2 Turn off @ 230V<sub>ac</sub>: 18V/0.13A.




## 6 Output Ripple Voltages

The output ripple voltages are shown in the plots below.



### 6.1 120V<sub>ac</sub>: 18V/0.13A:

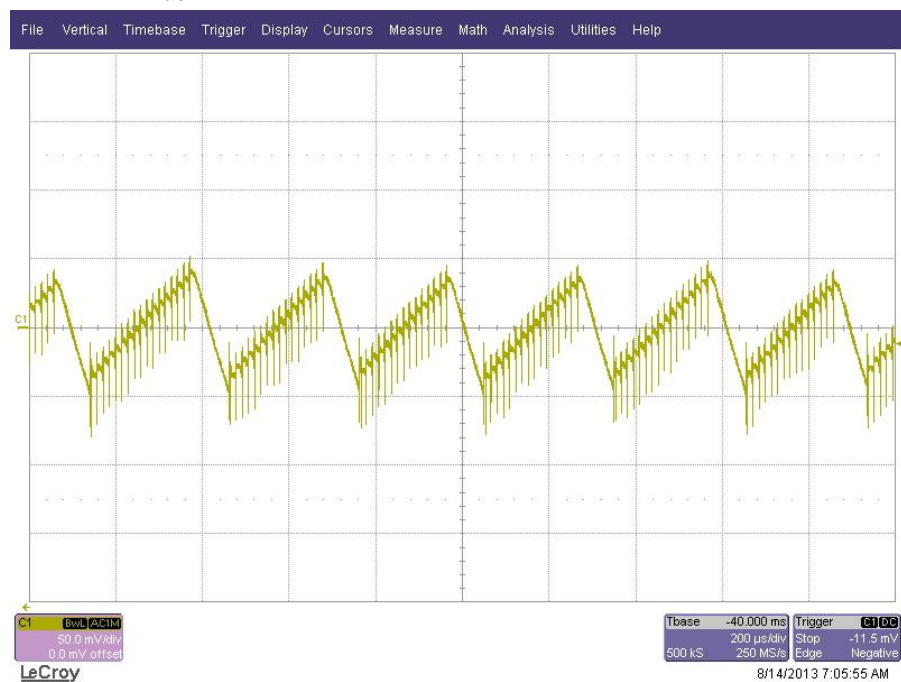

### 6.2 120V<sub>ac</sub>: no load:

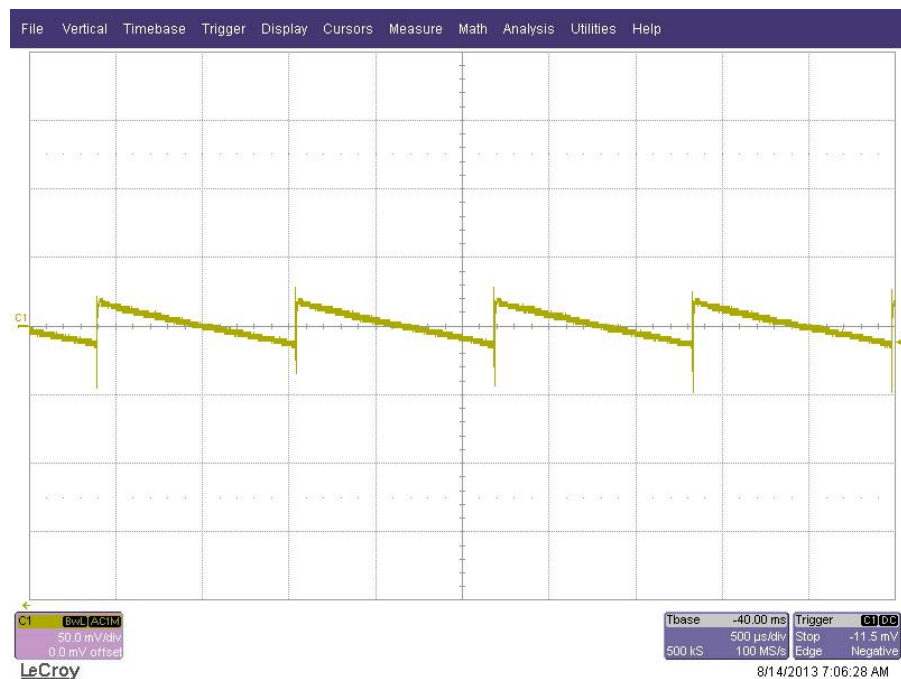

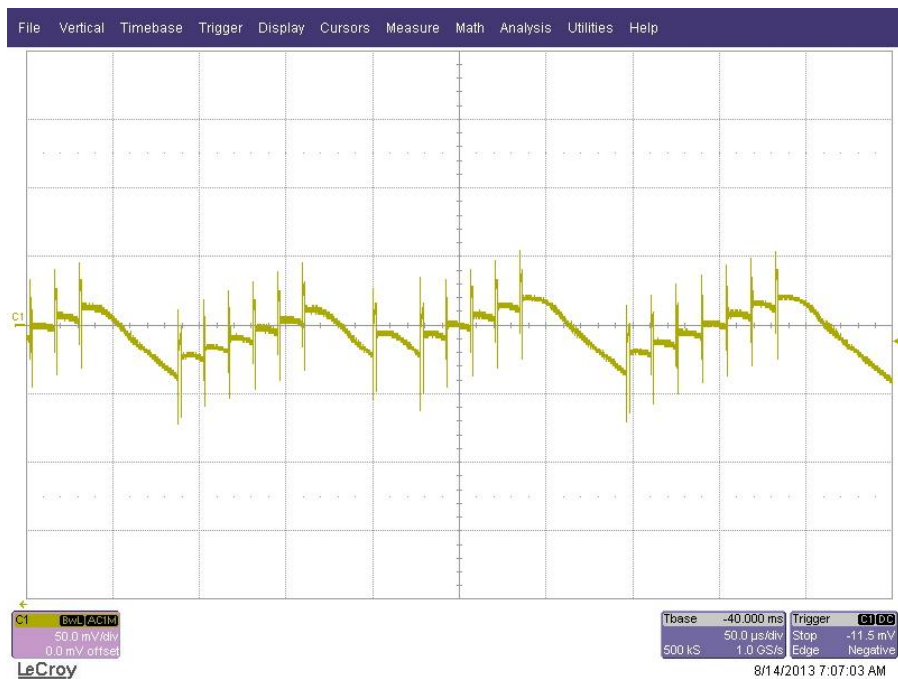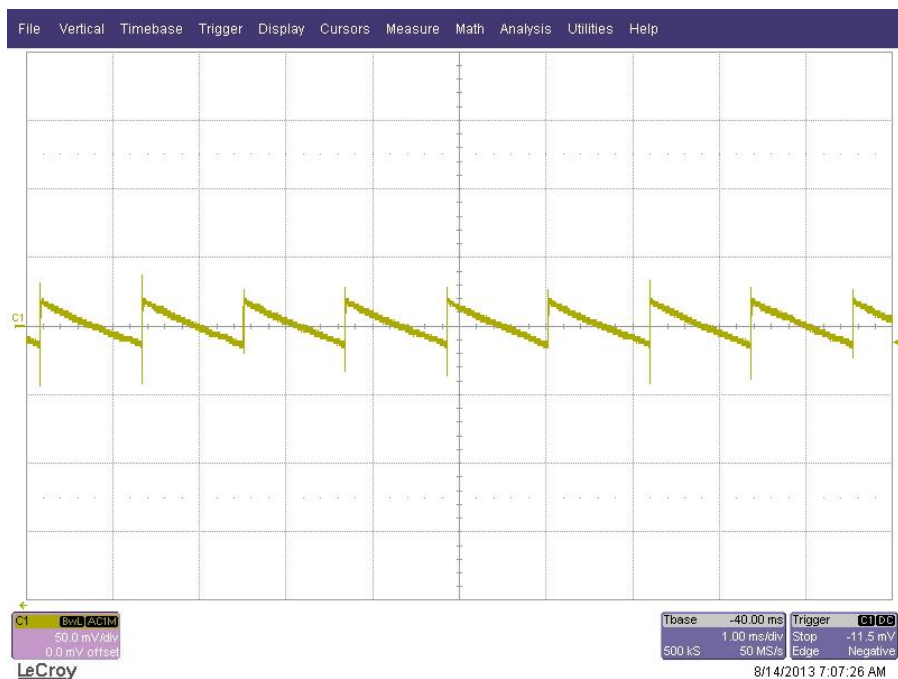

**6.3 230V<sub>ac</sub>: 18V/0.13A:****6.4 230V<sub>ac</sub>: no load:**

## 7 Load Transient


The image below shows  $18V_{out}$  voltage response to a **0.06A** to **0.13A** load transient at  $120V_{ac}/60Hz$ .




## 8 Switching Waveforms

The images below show key switching waveforms of PMP9073RevA. The waveforms are measured with 0.13A full load.
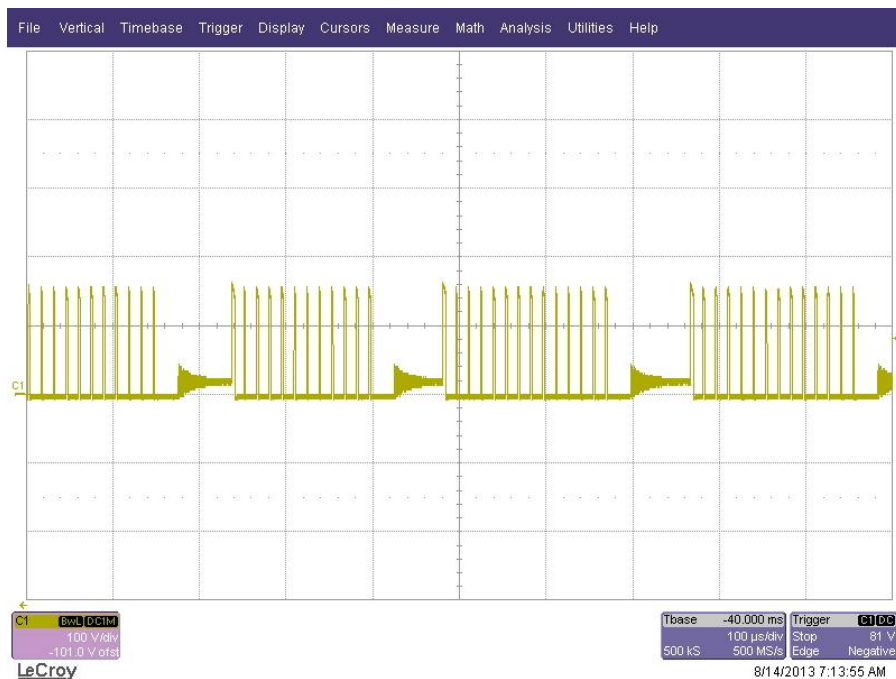
### 8.1 Diode D3 @ 120V<sub>ac</sub>/60Hz


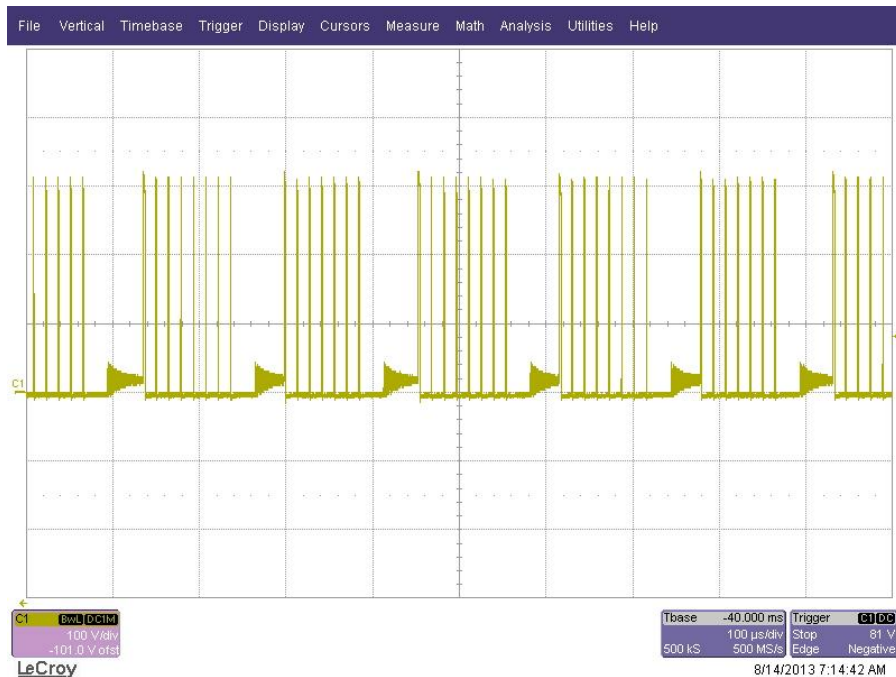
### 8.2 Diode D3 @ 230V<sub>ac</sub>/60Hz



## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated