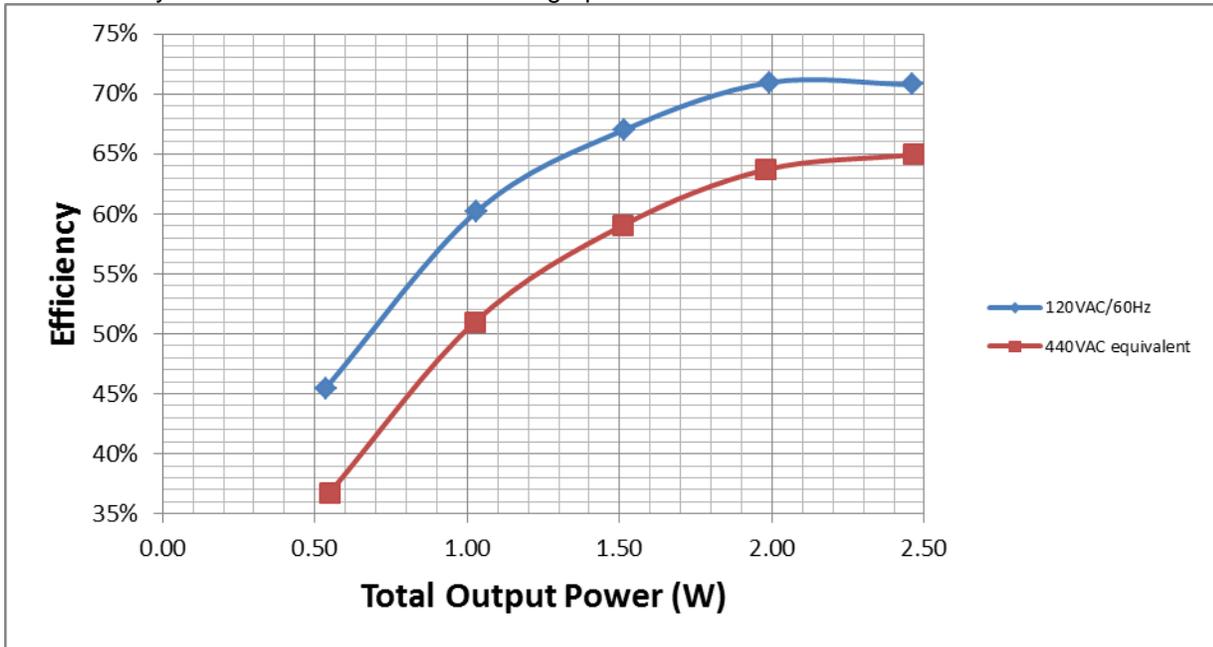




## 2 Converter Efficiency

The efficiency data is shown in the tables and graph below.



### V<sub>in</sub>=120V<sub>AC</sub>/60Hz

V <sub>in</sub> (V)	I <sub>in</sub> (mA)	P <sub>in</sub> (W)	V <sub>o1</sub> (V)	I <sub>o1</sub> (A)	V <sub>o2</sub> (V)	I <sub>o2</sub> (A)	P <sub>out</sub> (W)	Losses(W)	Efficiency (%)
120.04	59.44	3.48	23.63	0.100	4.96	0.020	2.46	1.02	70.77%
120.06	50.22	2.81	23.92	0.080	4.97	0.016	1.99	0.82	70.95%
120.08	42.35	2.26	24.27	0.060	4.97	0.012	1.51	0.75	67.00%
120.10	34.14	1.71	24.74	0.040	4.97	0.008	1.03	0.68	60.22%
120.10	25.58	1.18	25.43	0.020	4.98	0.004	0.53	0.64	45.46%
120.11	15.62	0.64	26.79	0.000	4.99	0.000	0.00	0.64	0.00%

### V<sub>in</sub>=622V<sub>DC</sub> (622V<sub>DC</sub> is generated by an AC source with a voltage doubler circuit)


V <sub>in</sub> (V)	I <sub>in</sub> (mA)	P <sub>in</sub> (W)	V <sub>o1</sub> (V)	I <sub>o1</sub> (A)	V <sub>o2</sub> (V)	I <sub>o2</sub> (A)	P <sub>out</sub> (W)	Losses(W)	Efficiency (%)
221.60	47.20	3.79	23.50	0.101	4.96	0.020	2.46	1.33	64.94%
221.60	39.69	3.11	23.87	0.080	4.96	0.016	1.98	1.13	63.69%
221.60	33.49	2.56	24.28	0.060	4.97	0.012	1.51	1.05	59.04%
221.60	27.20	2.01	24.82	0.040	4.97	0.008	1.03	0.98	51.00%
221.60	20.93	1.49	25.58	0.021	4.98	0.004	0.55	0.94	36.74%
221.60	13.94	0.93	27.08	0.000	4.99	0.000	0.00	0.93	0.00%

### 3 Thermal Images

The thermal images below show a top view and bottom view of the board under 120V<sub>AC</sub>/60Hz and 622V<sub>DC</sub> input conditions. The ambient temperature was 20°C with no forced air flow. The output was at full load: 24V/100mA and 5V/20mA.


**V<sub>in</sub>=120V<sub>AC</sub>/60Hz**

**Top Side**

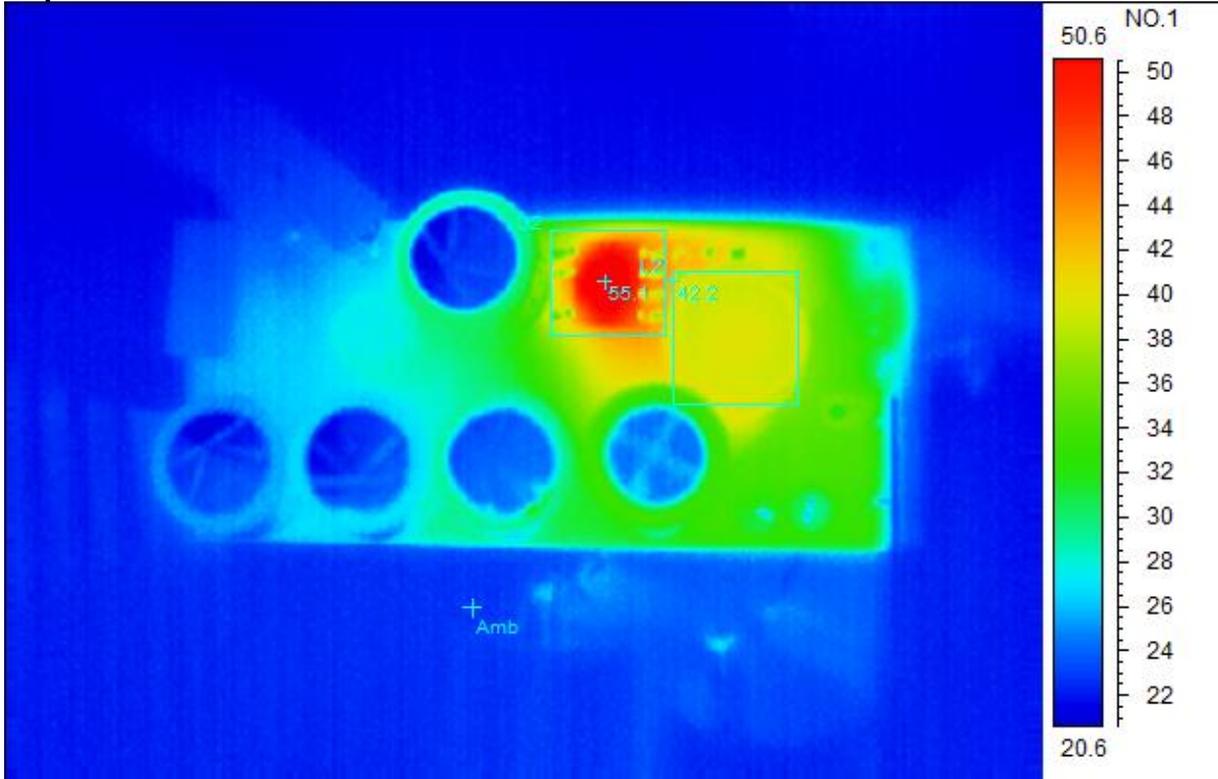


Spot analysis	Value
Amb Temperature	23.1°C
Area analysis	Value
U2Max	55.1°C
L2Max	42.2°C

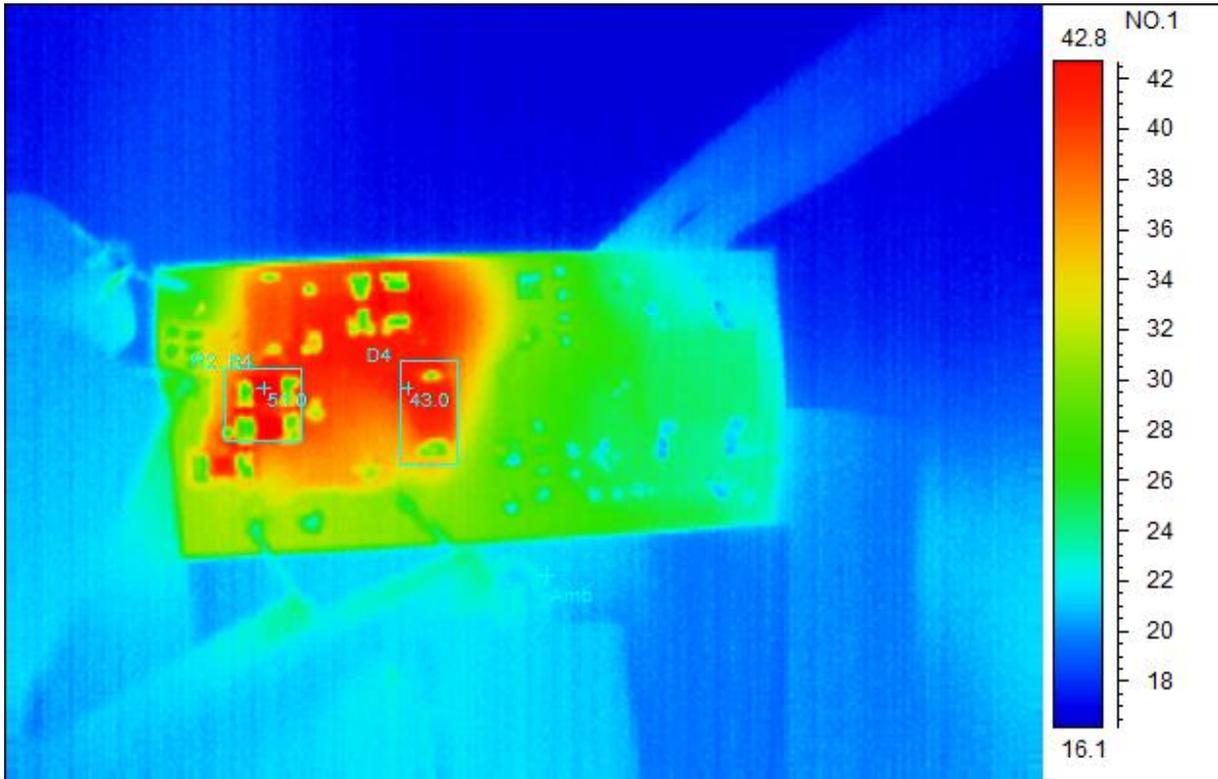**V<sub>in</sub>=120V<sub>AC</sub>/60Hz**  
**Bottom Side**



Spot analysis	Value
Amb Temperature	21.9°C
Area analysis	Value
D4Max	43.0°C
R2, R4Max	51.0°C

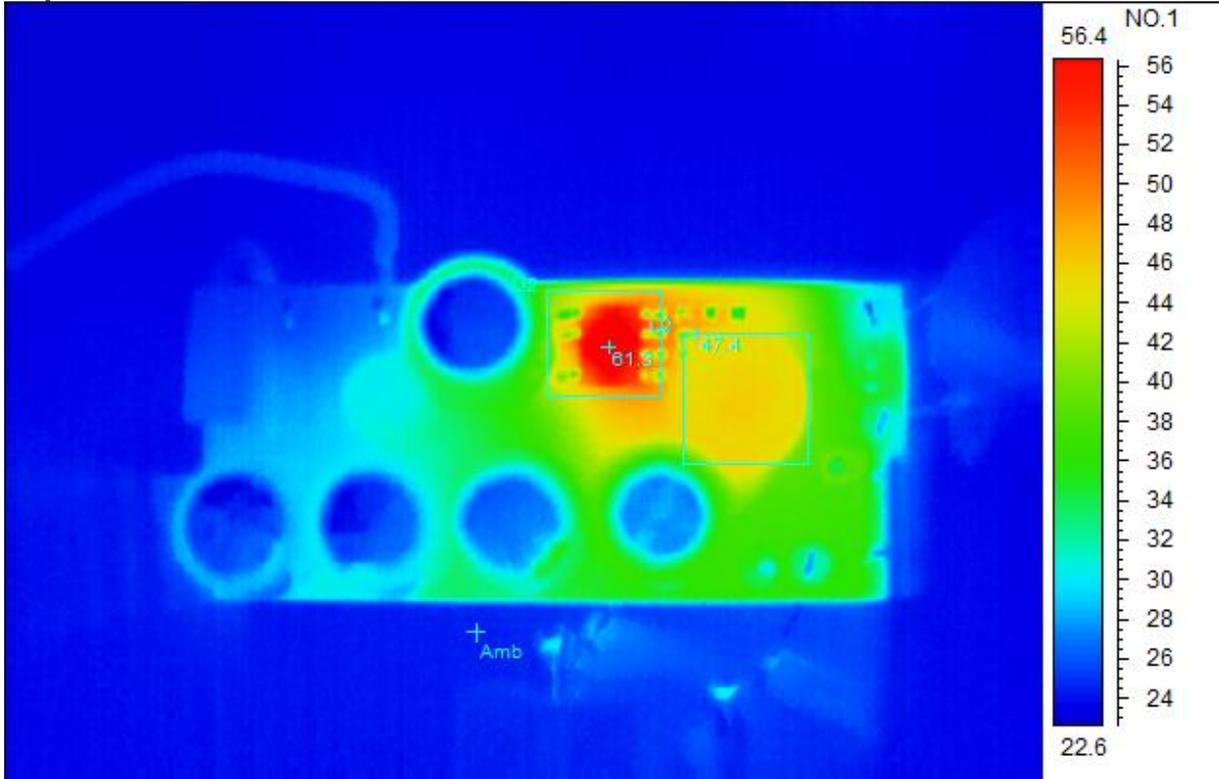$V_{in}=622V_{DC}$  ( $622V_{DC}$  is generated by an AC source with a voltage doubler circuit)  
 Top Side



Spot analysis	Value
Amb Temperature	24.4°C
Area analysis	Value
U2Max	61.3°C
L2Max	47.4°C

$V_{in}=622V_{DC}$  ( $622V_{DC}$  is generated by an AC source with a voltage doubler circuit)  
**Bottom Side**




Spot analysis	Value
Amb Temperature	25.3°C
Area analysis	Value
D4Max	50.3°C
R2, R4Max	54.2°C


## 4 Startup Waveforms

The output voltages at startup are shown in the images below. CH3: Voltage after input rectifier, CH4: Vout

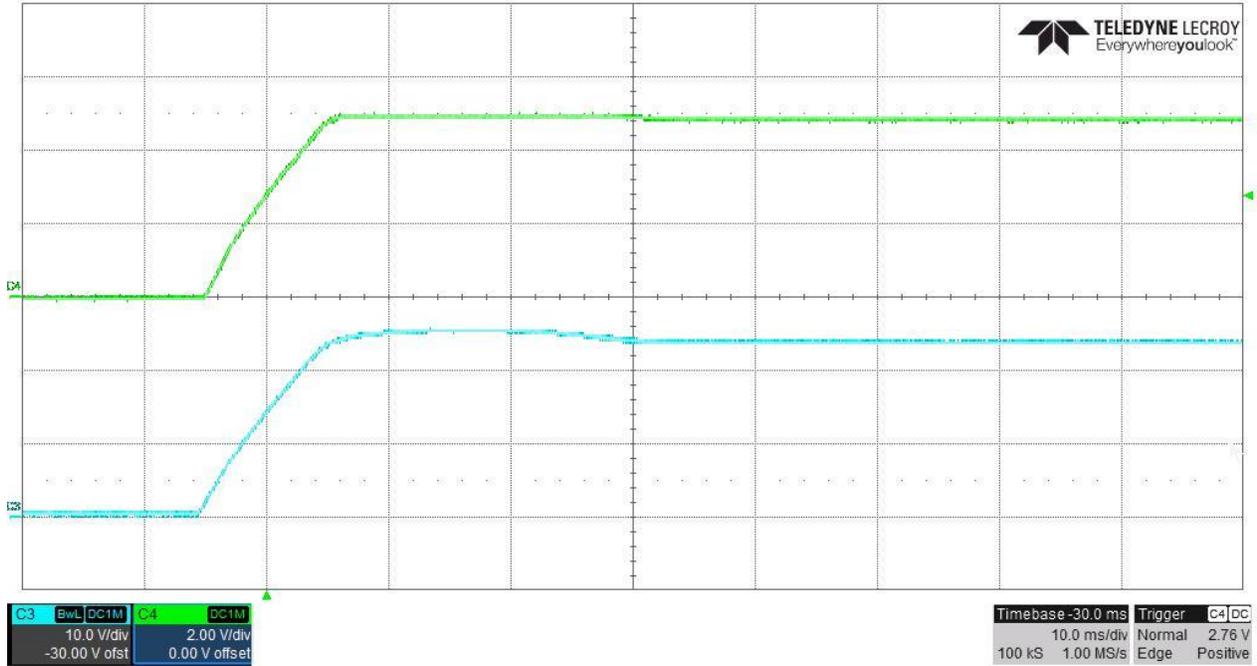
### 4.1 Start Up @ 120V<sub>AC</sub>/60Hz input, 24V/100mA and 5V/20mA outputs.



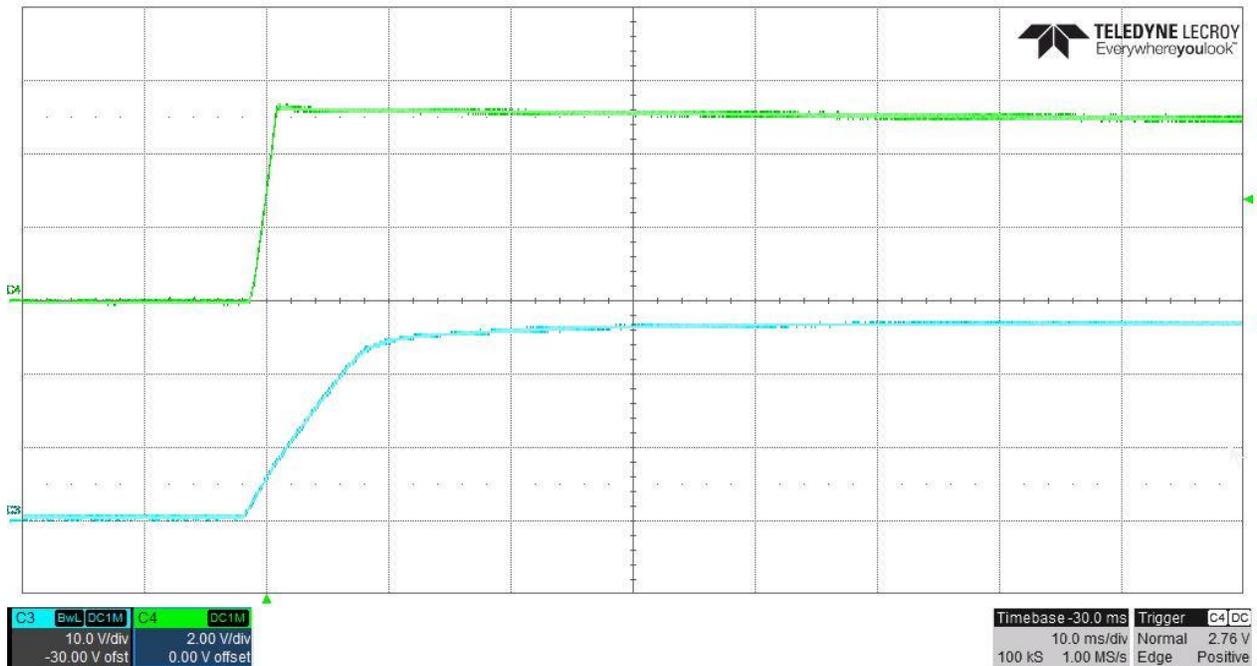
### 4.2 Start Up @ 120V<sub>AC</sub>/60Hz input and no loads.


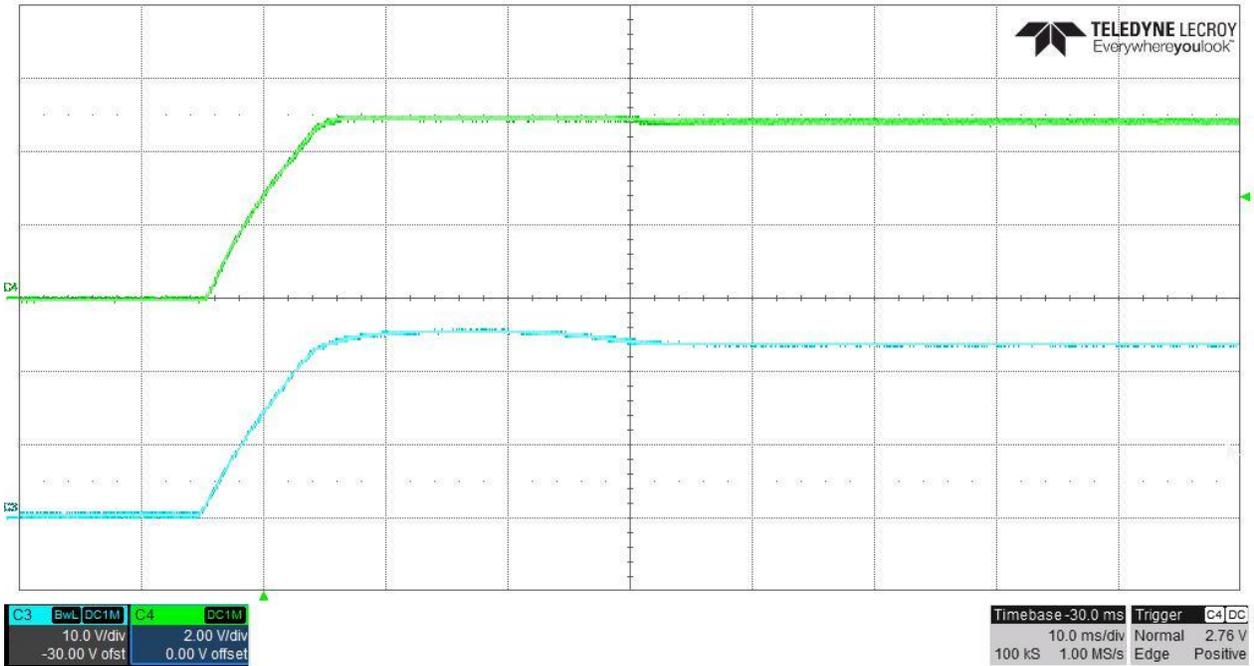
### 4.3 Start Up @ 622V<sub>DC</sub> (622V<sub>DC</sub> is generated by an AC source with a voltage doubler circuit) input, 24V/100mA and 5V/20mA outputs.


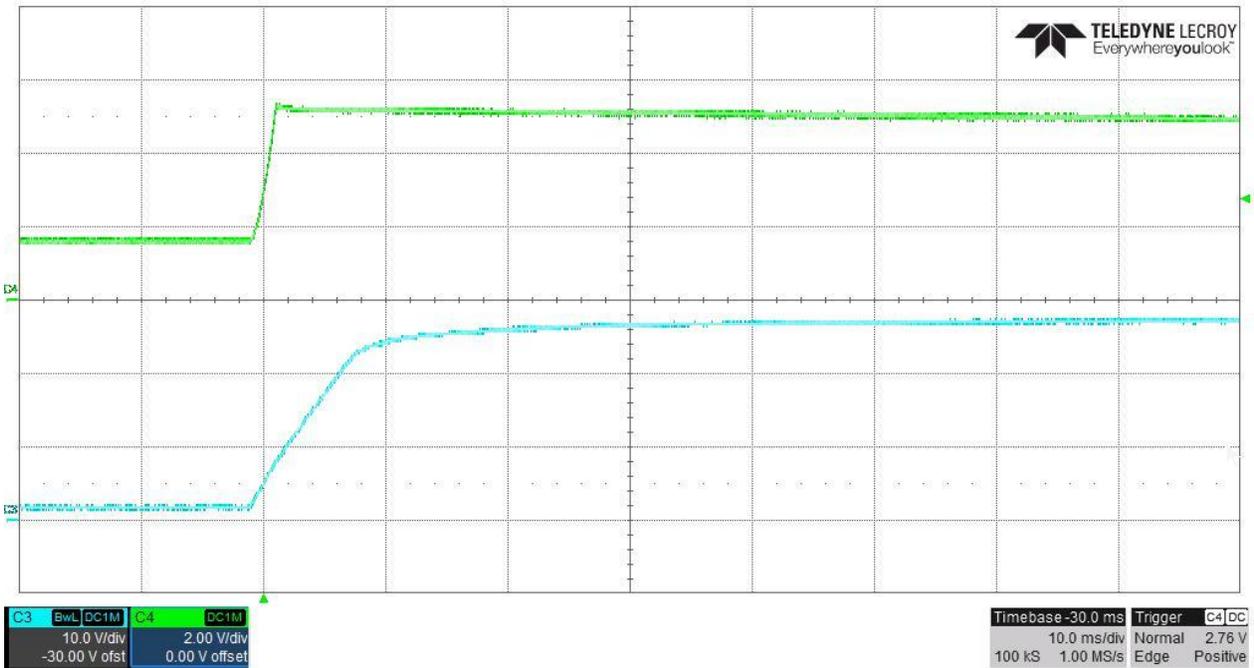
### 4.4 Start Up @ 622V<sub>DC</sub> (622V<sub>DC</sub> is generated by an AC source with a voltage doubler circuit) input and no load.




## 5 Output Ripple Voltages


The output ripple voltages are shown in the plots below.

### 5.1 120V<sub>AC</sub>/60Hz: 24V/100mA and 5V/20mA.

24V ripple:

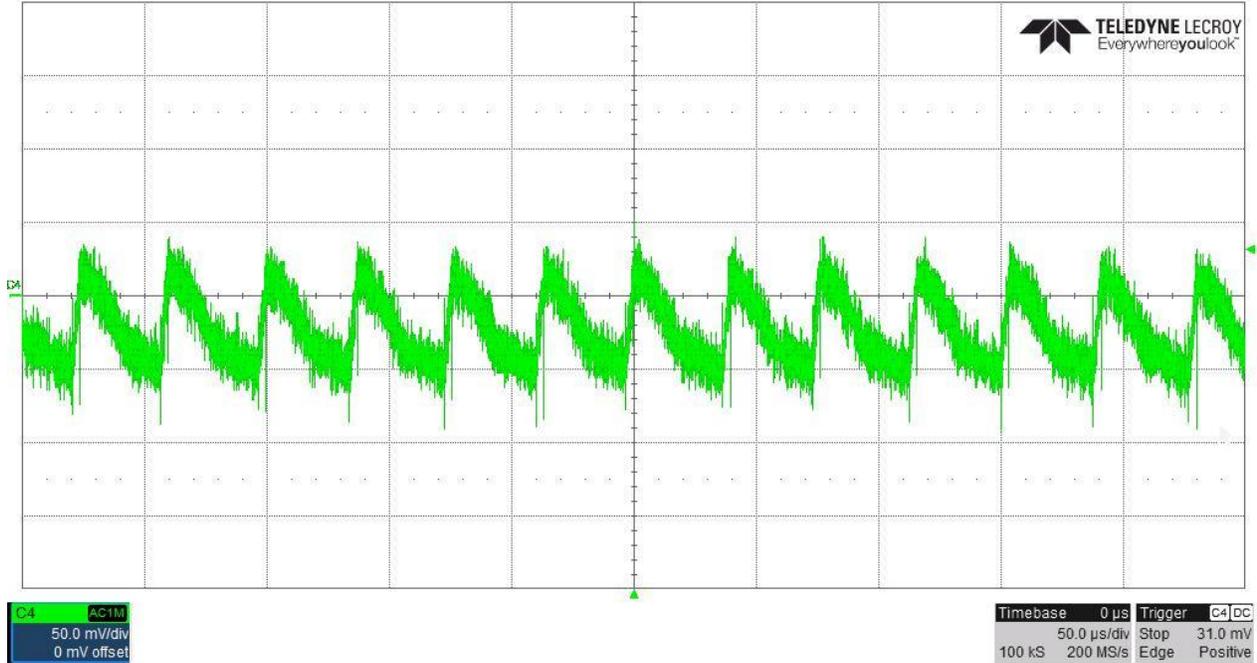


5V ripple:

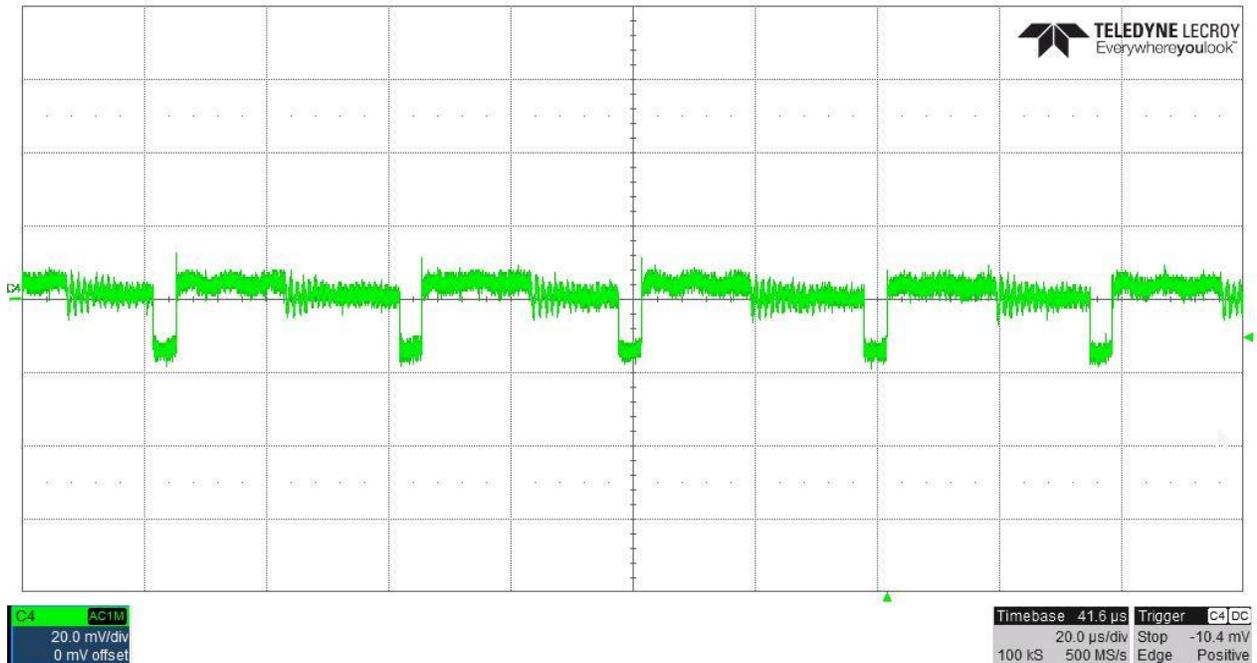


## 5.2 120V<sub>AC</sub>/60Hz: no load applied to both 5V and 24V.

24V ripple:

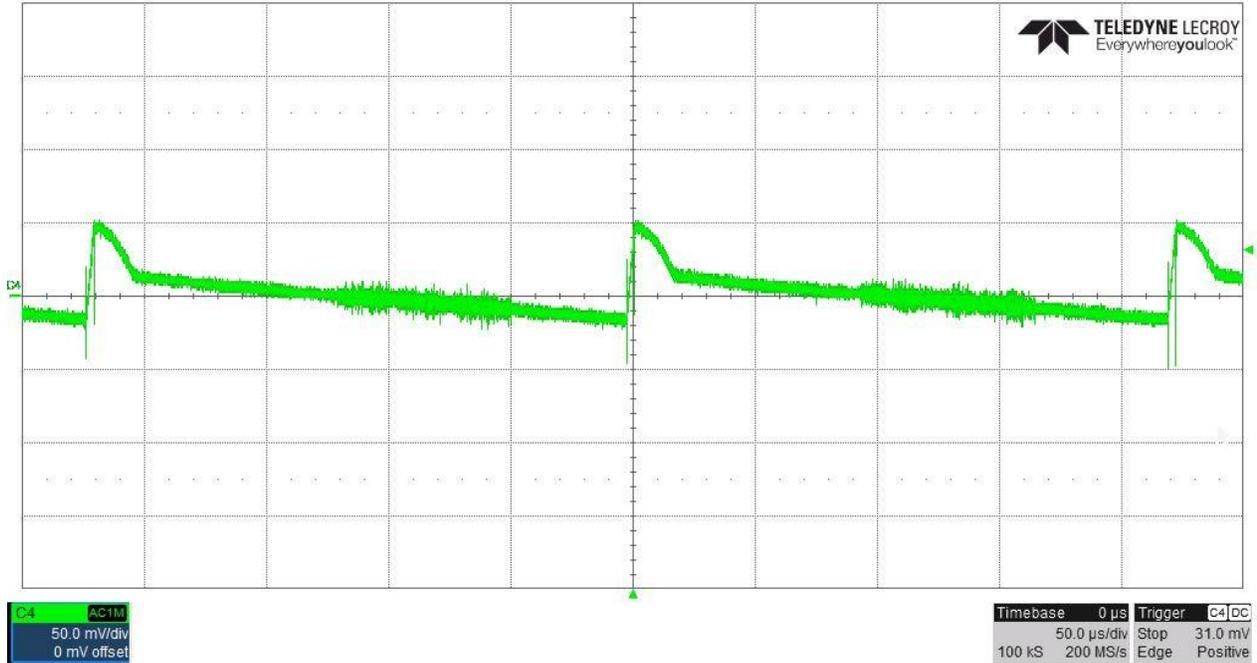


5V ripple:

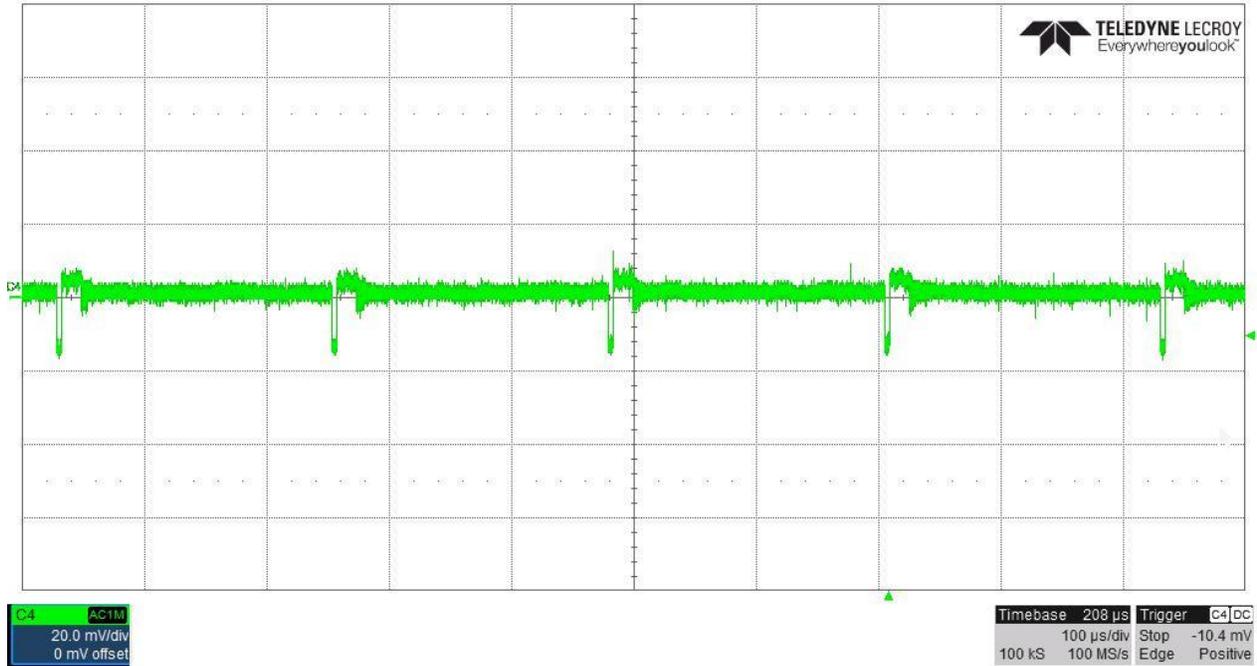

### 5.3 $622V_{DC}$ ( $622V_{DC}$ is generated by an AC source with a voltage doubler circuit): 24V/100mA and 5V/20mA.


24V ripple:

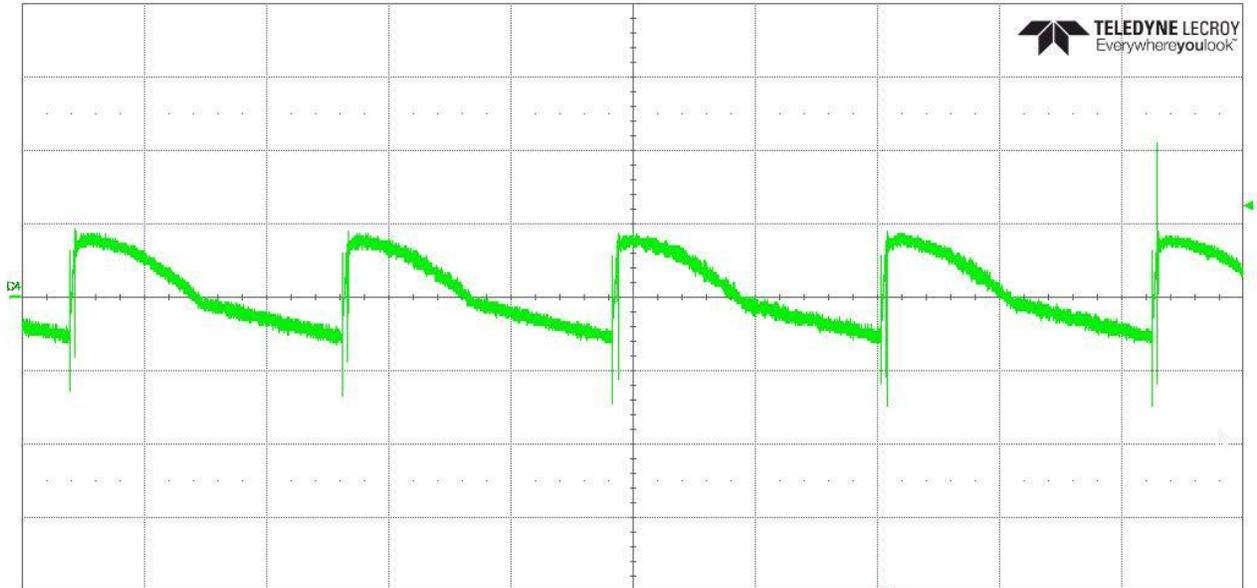

C4 AC1M  
50.0 mV/div  
0 mV offset

Timebase 41.6 µs Trigger C4[DC]  
20.0 µs/div Stop 62.5 mV  
100 kS 500 MS/s Edge Positive

5V ripple:

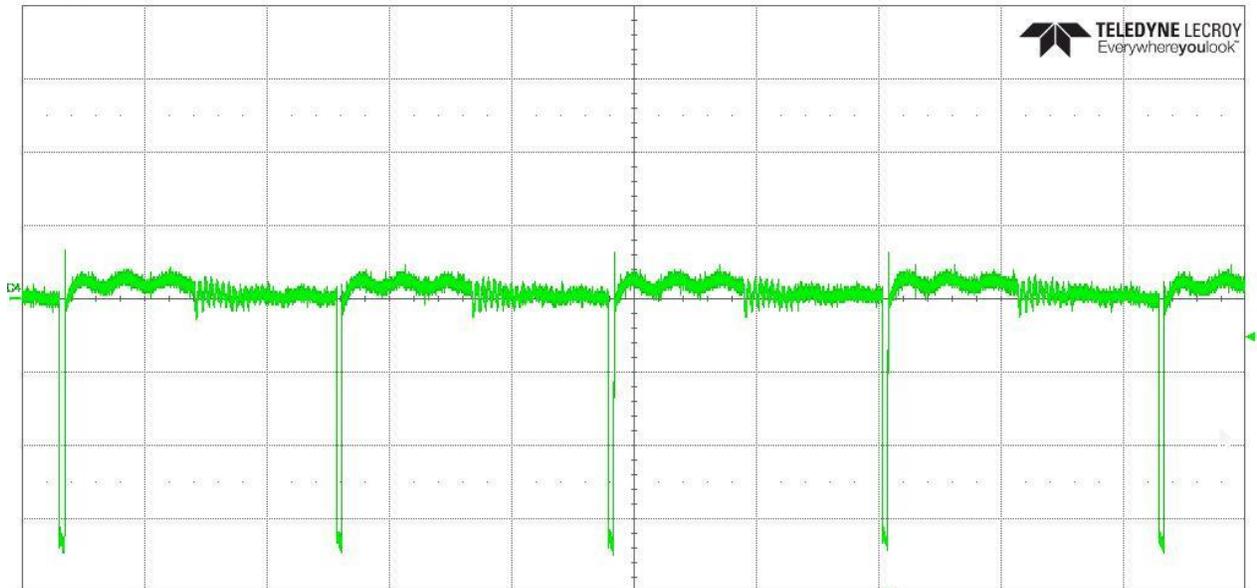


C4 AC1M  
20.0 mV/div  
0 mV offset

Timebase 41.6 µs Trigger C4[DC]  
20.0 µs/div Stop -10.4 mV  
100 kS 500 MS/s Edge Positive

### 5.4 622V<sub>DC</sub> (622V<sub>DC</sub> is generated by an AC source with a voltage doubler circuit): no load applied to both 5V and 24V.


24V ripple:

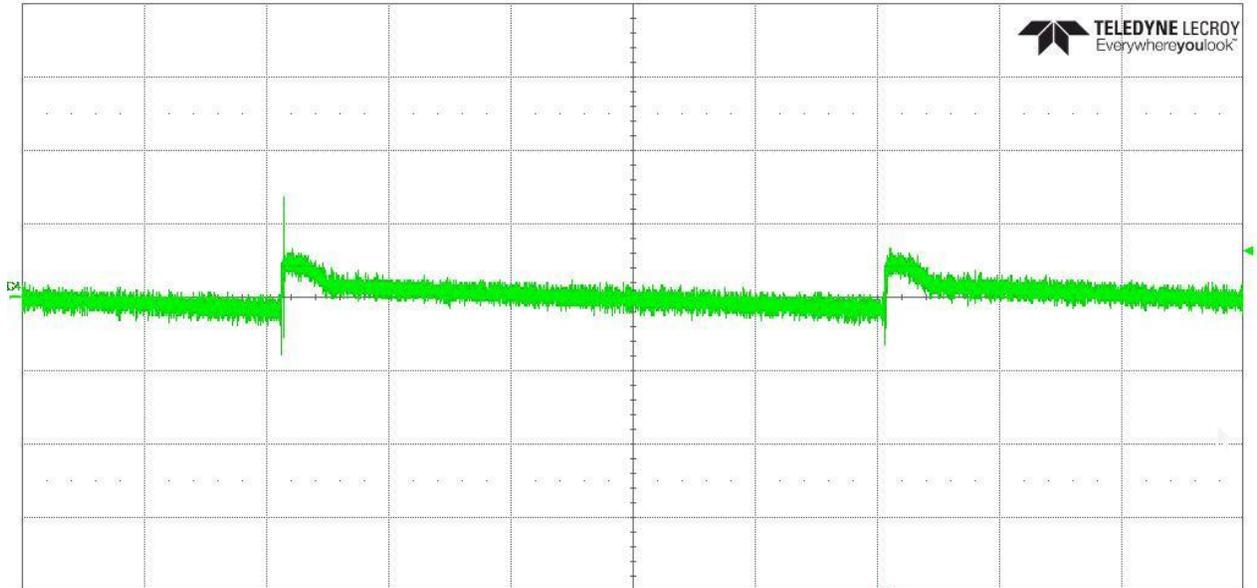

C4 AC1M  
100 mV/div  
0 mV offset

Timebase 104  $\mu$ s Trigger C4[DC]  
50.0  $\mu$ s/div Stop 63 mV  
100 kS 200 MS/s Edge Positive

5V ripple:

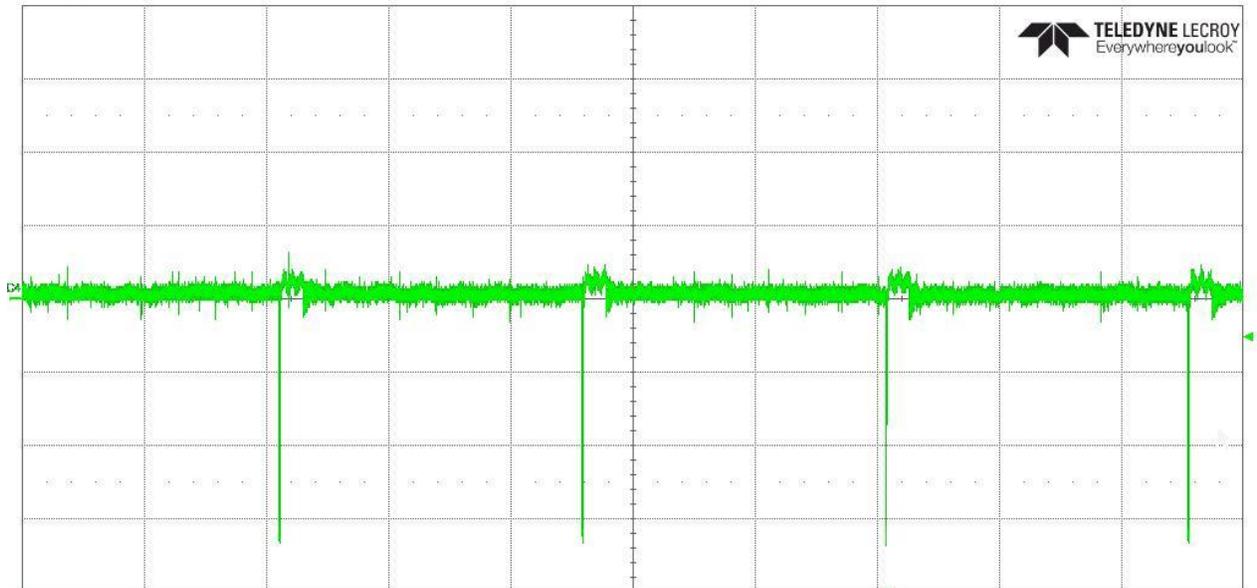


C4 AC1M  
20.0 mV/div  
0 mV offset

Timebase 208  $\mu$ s Trigger C4[DC]  
100  $\mu$ s/div Stop -10.4 mV  
100 kS 100 MS/s Edge Positive


## 6 Switching Waveforms

The images below show key switching waveforms of PMP11236RevB. The waveforms are measured with 5V/0A and 24V/120mA.
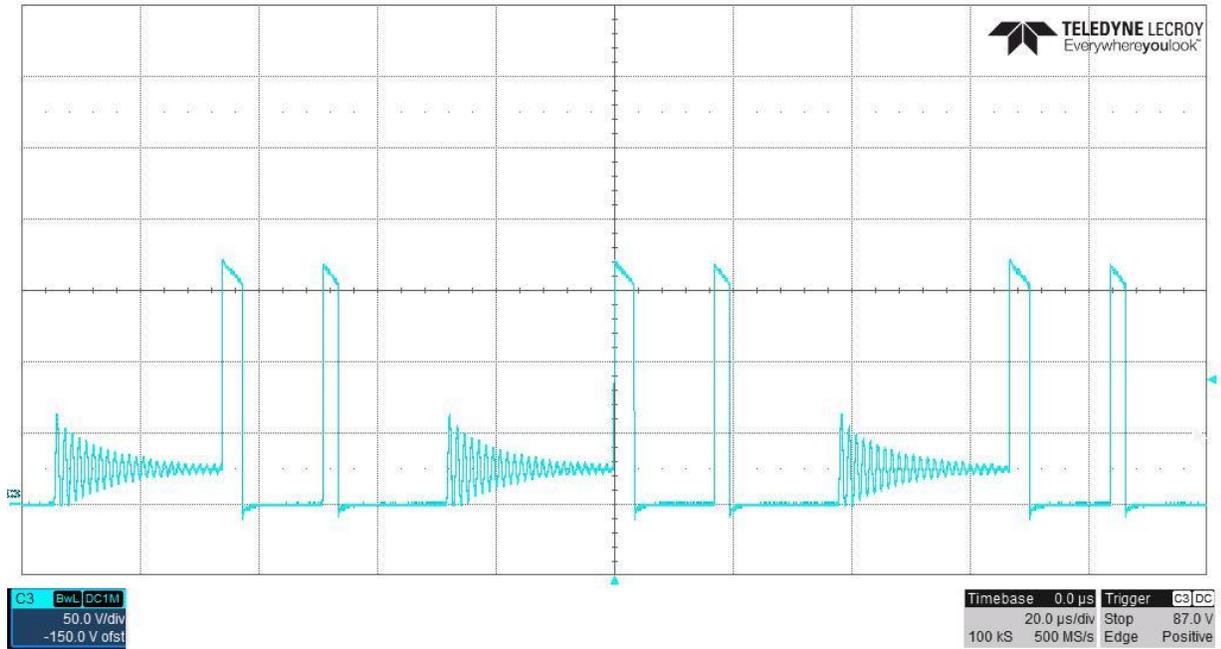
### 6.1 Diode D4 @ 120V<sub>AC</sub>/60Hz input



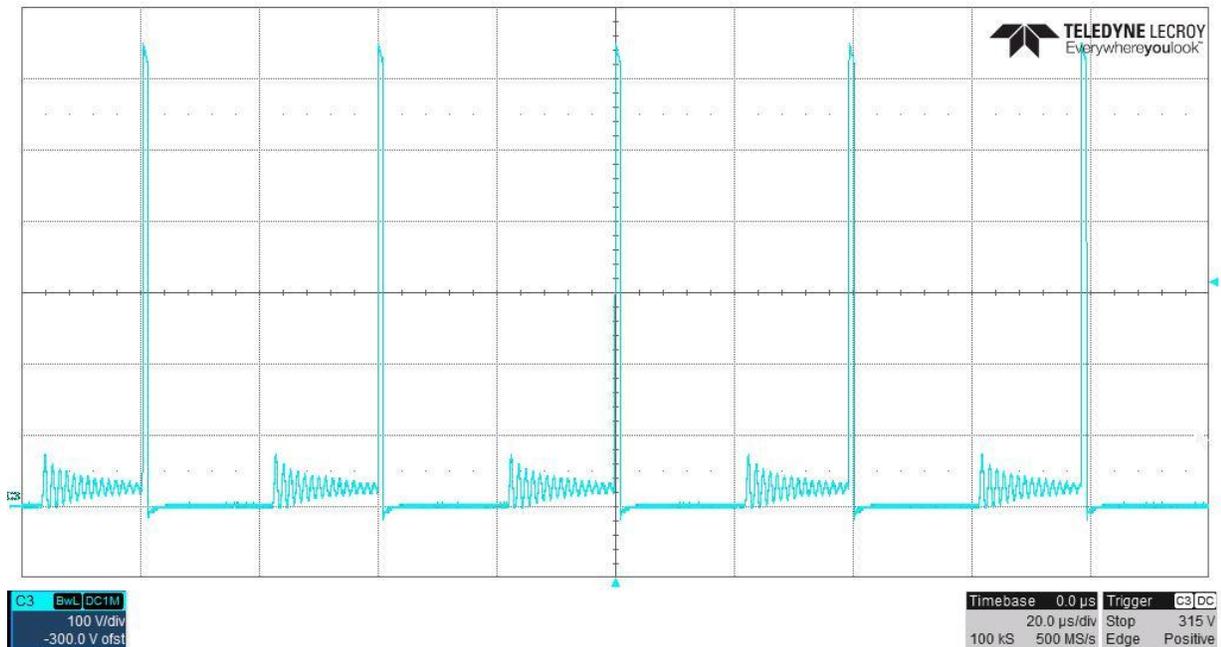
### 6.2 Diode D4 @ 622V<sub>DC</sub> (622V<sub>DC</sub> is generated by an AC source with a voltage doubler circuit) input




## 7 Conduction EMI

Scan is done with **peak detector** and **max hold**.  
Load condition: 24V output with 200Ω load resistor.


### 7.1 120V<sub>AC</sub>/60Hz, Line 1:

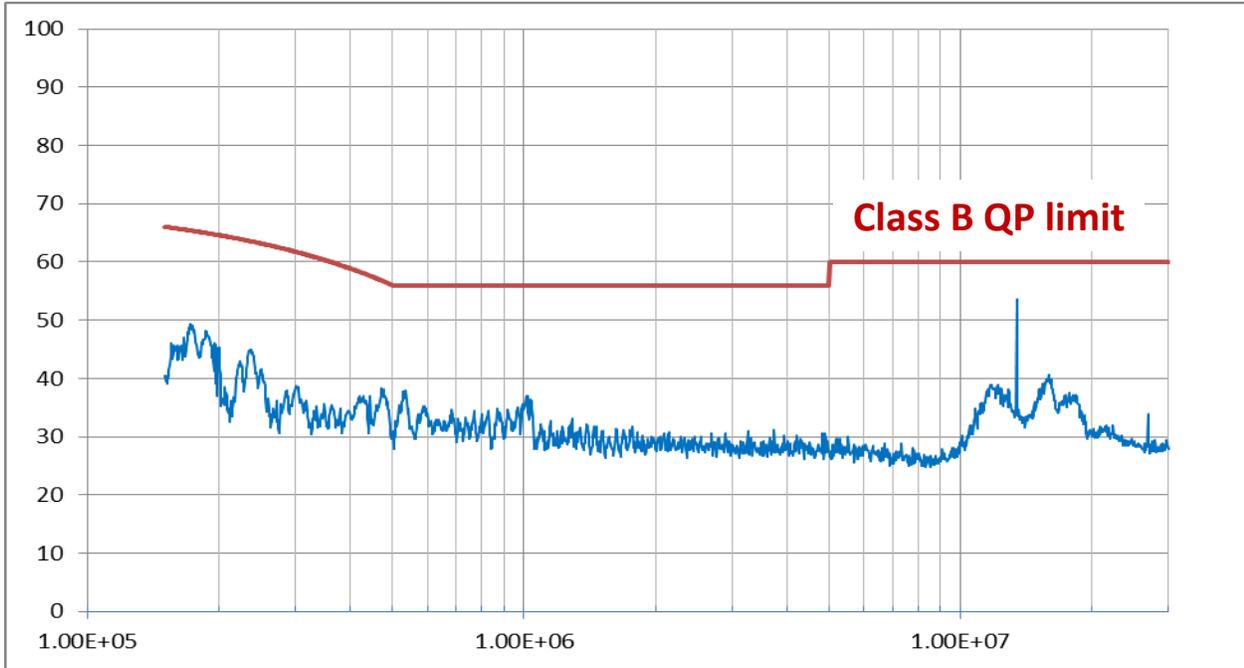


### 7.2 120V<sub>AC</sub>/60Hz, Line 2:

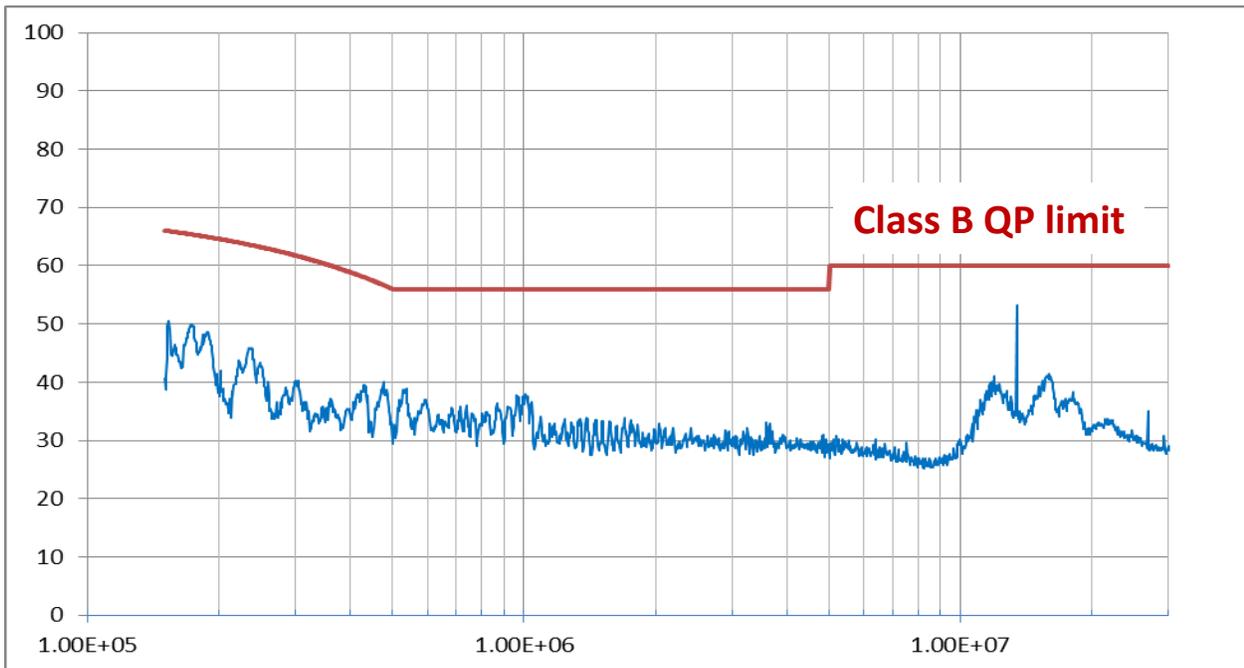

### 7.3 230V<sub>AC</sub>/50Hz, Line 1:

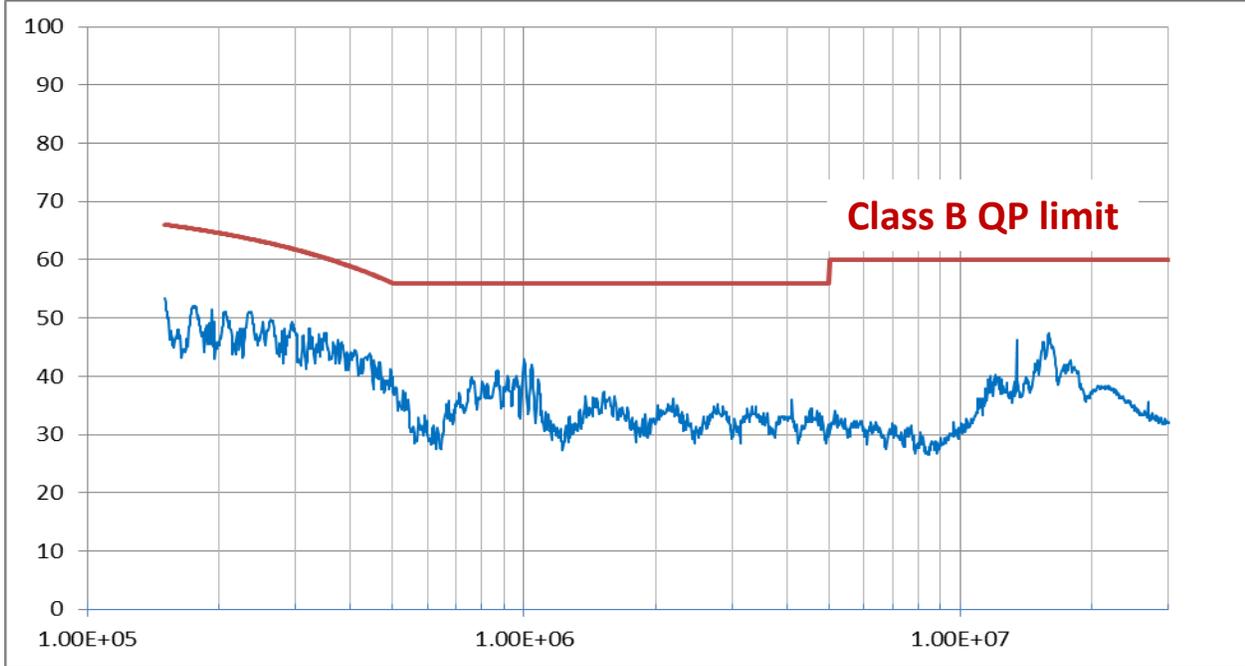

### 7.4 230V<sub>AC</sub>/50Hz, Line 2:

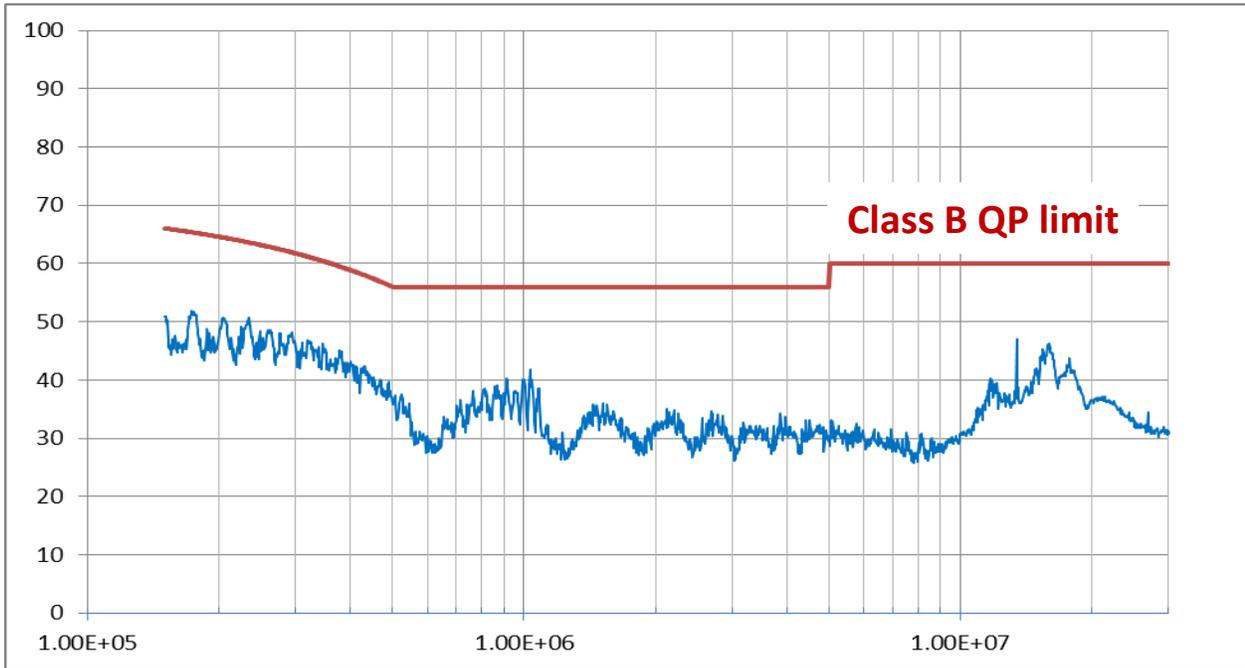

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated