
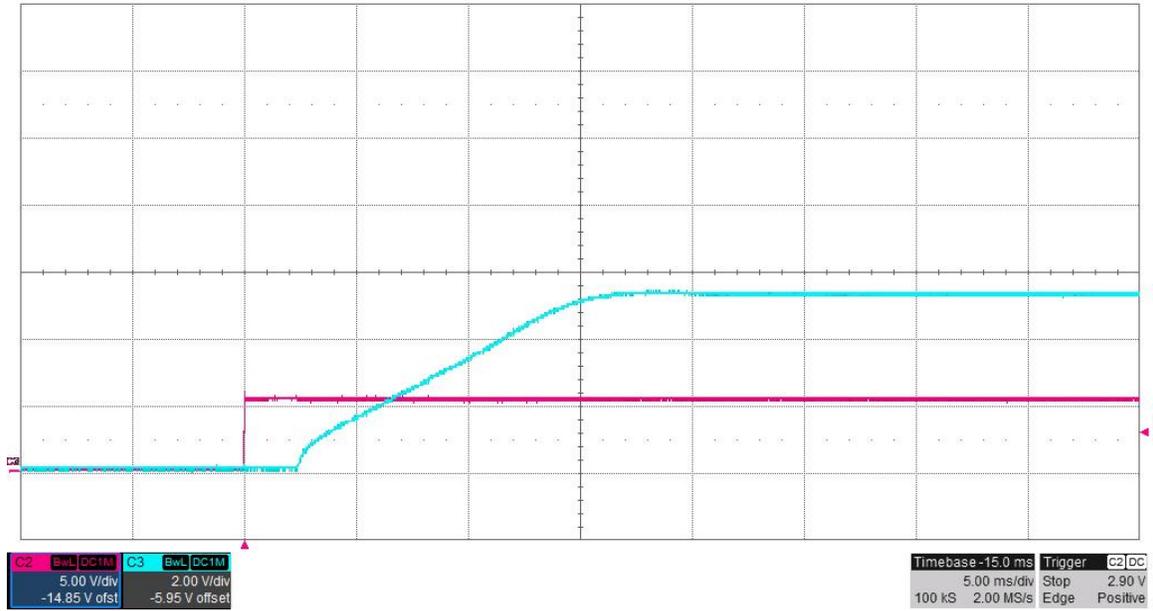


1 Startup

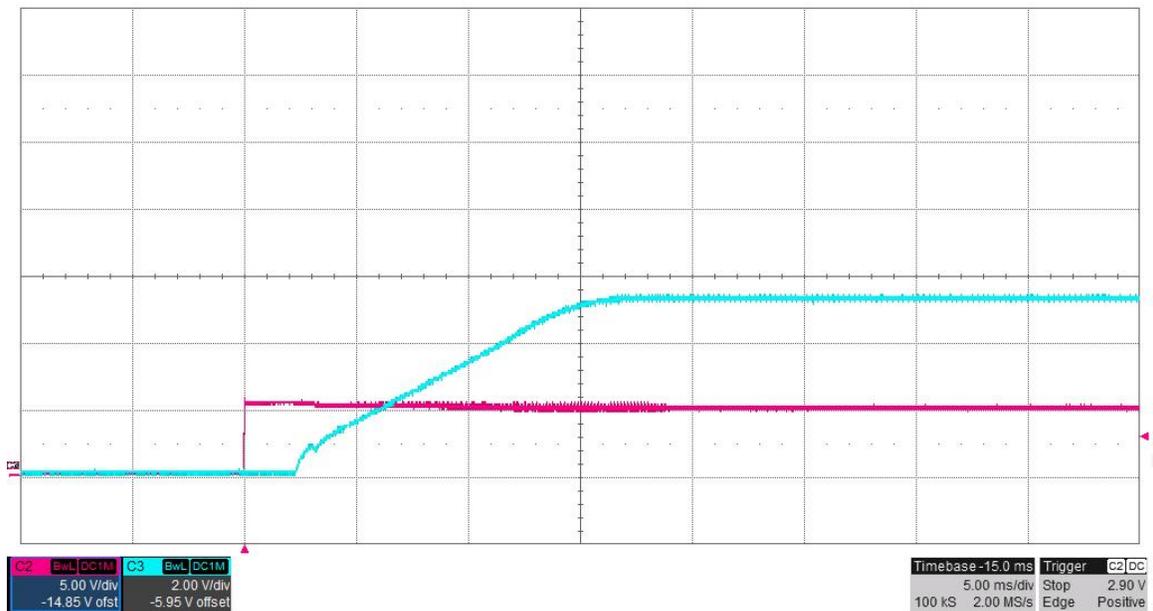
The photo below shows the output voltage startup waveforms after the application of 5V in. The 5.2V output was loaded to 0A. (Vin is 5V/DIV, Vout is 2V/DIV, 5mS/DIV)




The photo below shows the output voltage startup waveforms after the application of 5V in. The 5.2V output was loaded to 2A. (Vin is 5V/DIV, Vout is 2V/DIV, 5mS/DIV)



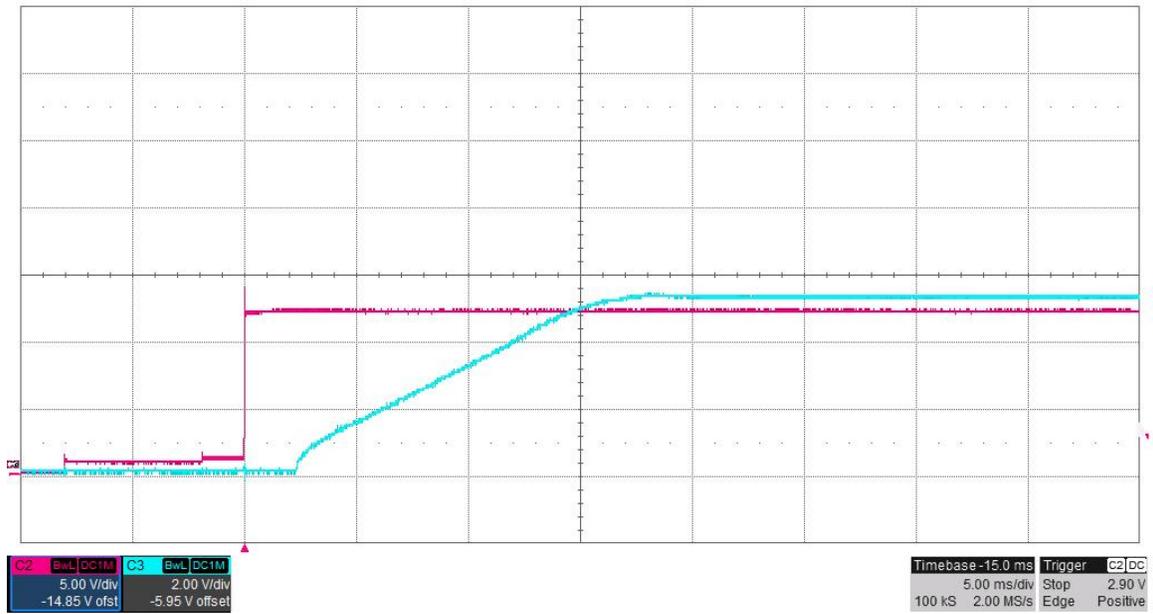
The photo below shows the output voltage startup waveforms after the application of 12V in. The 5.2V output was loaded to 0A. (Vin is 5V/DIV, Vout is 2V/DIV, 5mS/DIV)



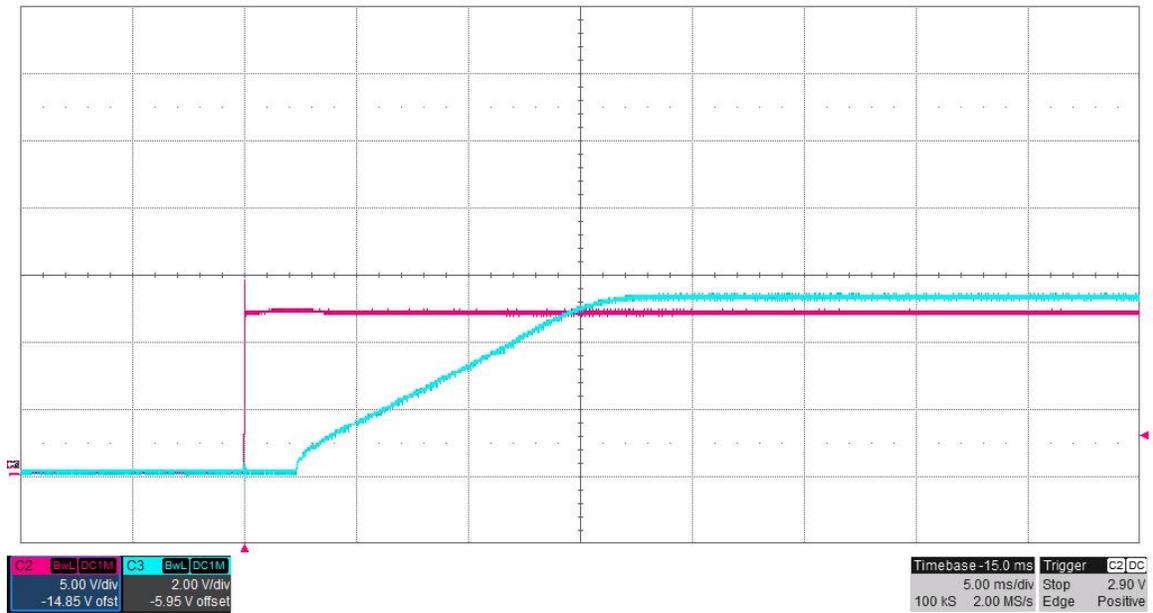
The photo below shows the output voltage startup waveforms after the application of 12V in. The 5.2V output was loaded to 2A. (Vin is 5V/DIV, Vout is 2V/DIV, 5mS/DIV)



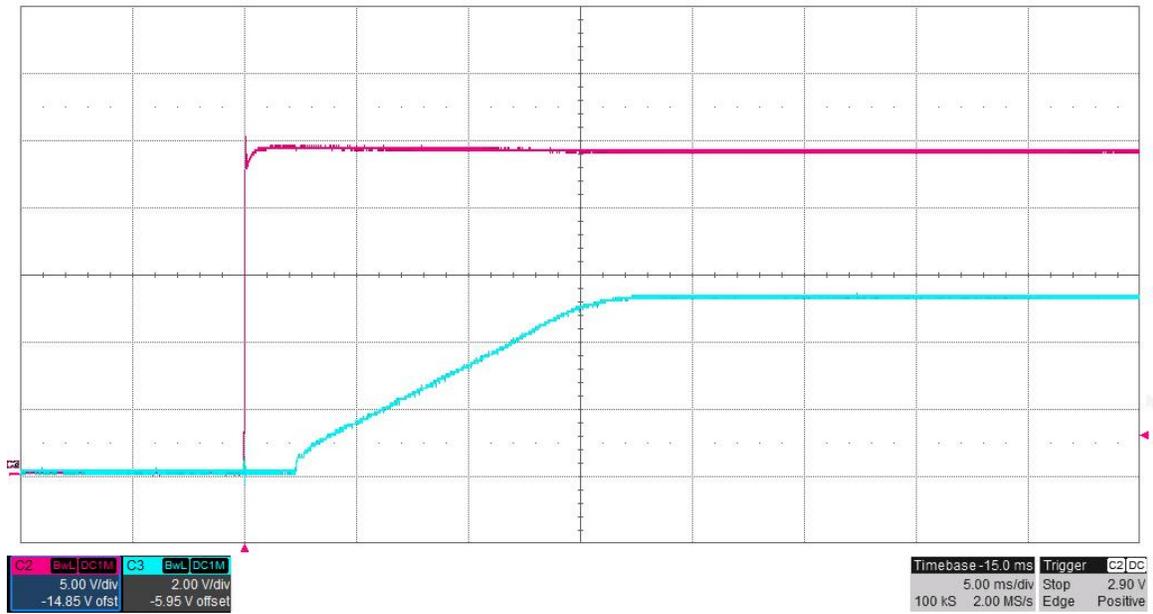The photo below shows the output voltage startup waveforms after the application of 24V in. The 5.2V output was loaded to 0A. (Vin is 5V/DIV, Vout is 2V/DIV, 5mS/DIV)





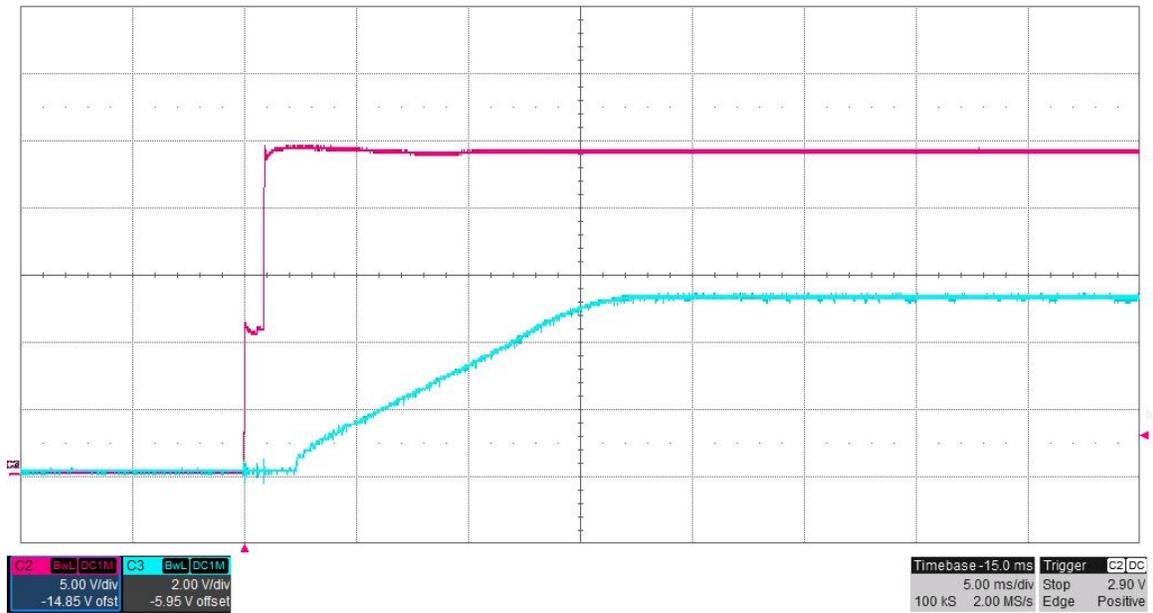
The photo below shows the output voltage startup waveforms after the application of 24V in. The 5.2V output was loaded to 2A. (Vin is 5V/DIV, Vout is 2V/DIV, 5mS/DIV)



2 Efficiency

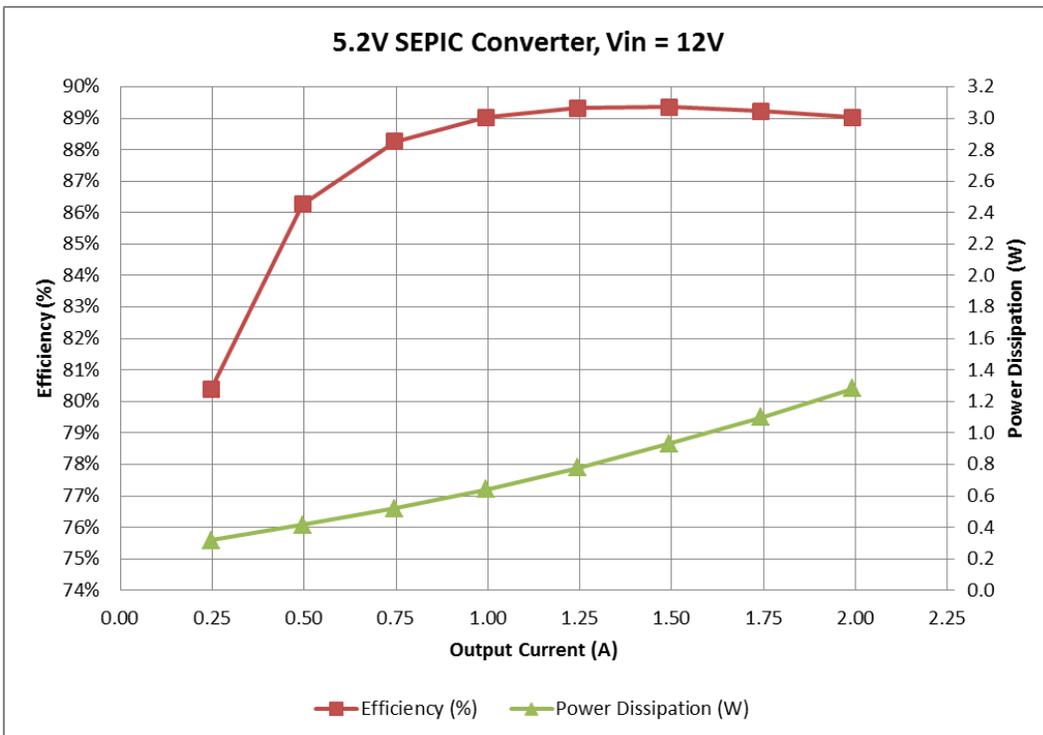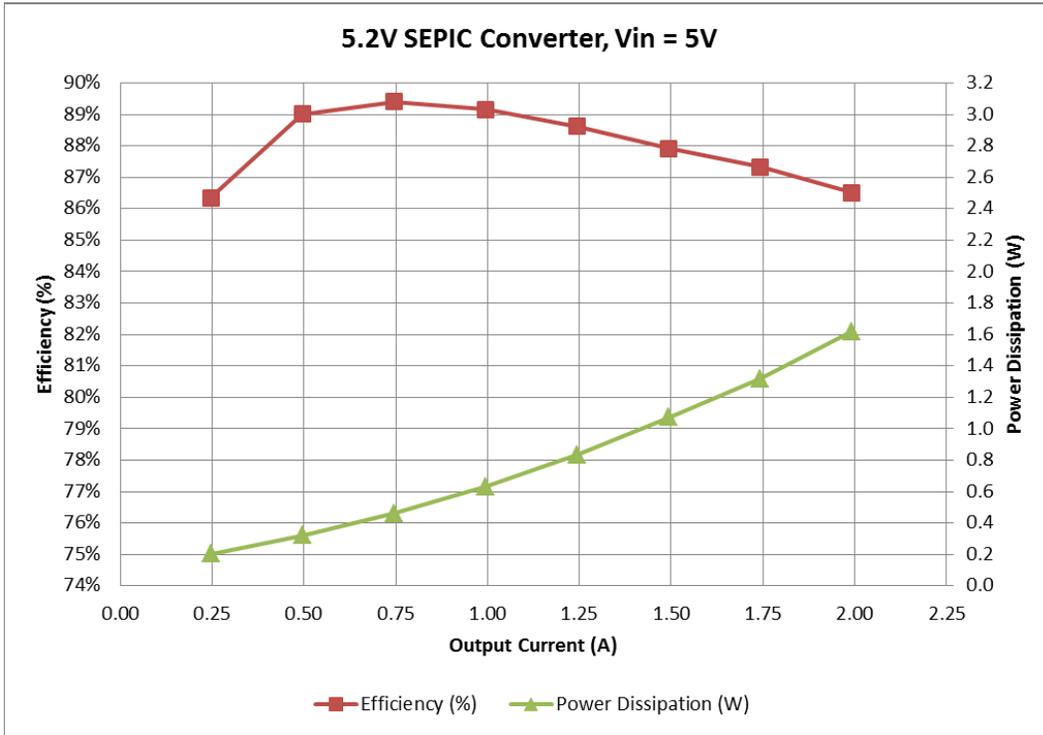
The converter efficiency is shown in the figures below for input voltages of 5V, 12V and 24V.



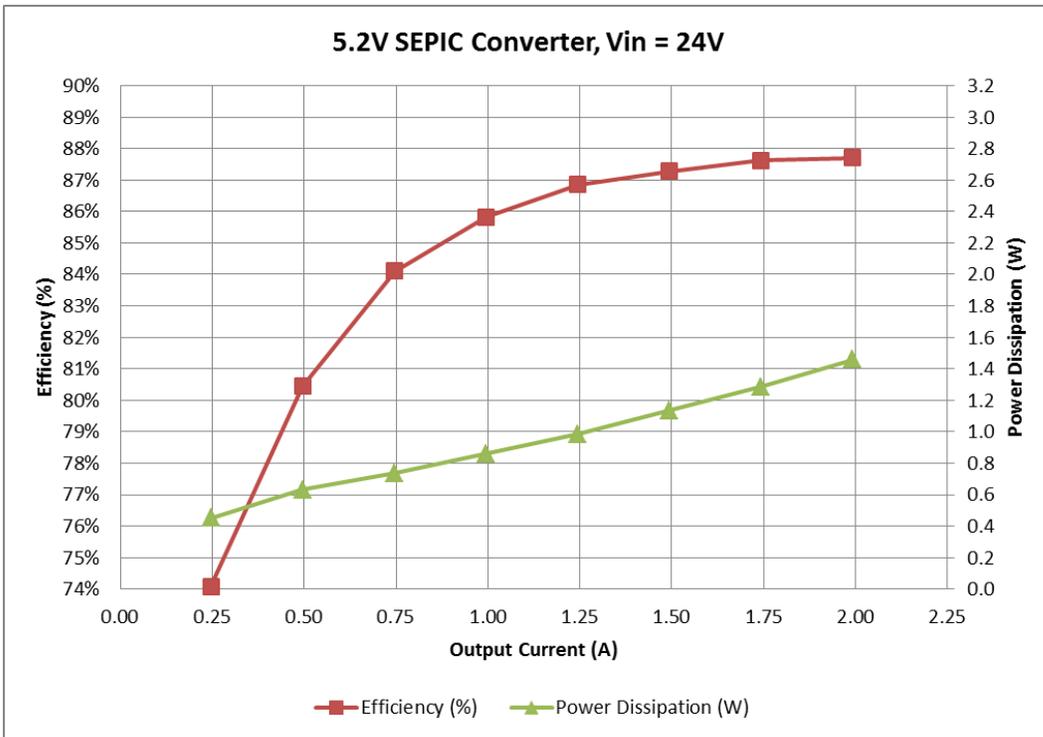


3 Output Ripple Voltage


The 5.2V output ripple voltage is shown in the figure below. The image was taken with the output loaded to 2A. The input voltage is set to 5V. (50mV/DIV, 2uS/DIV)

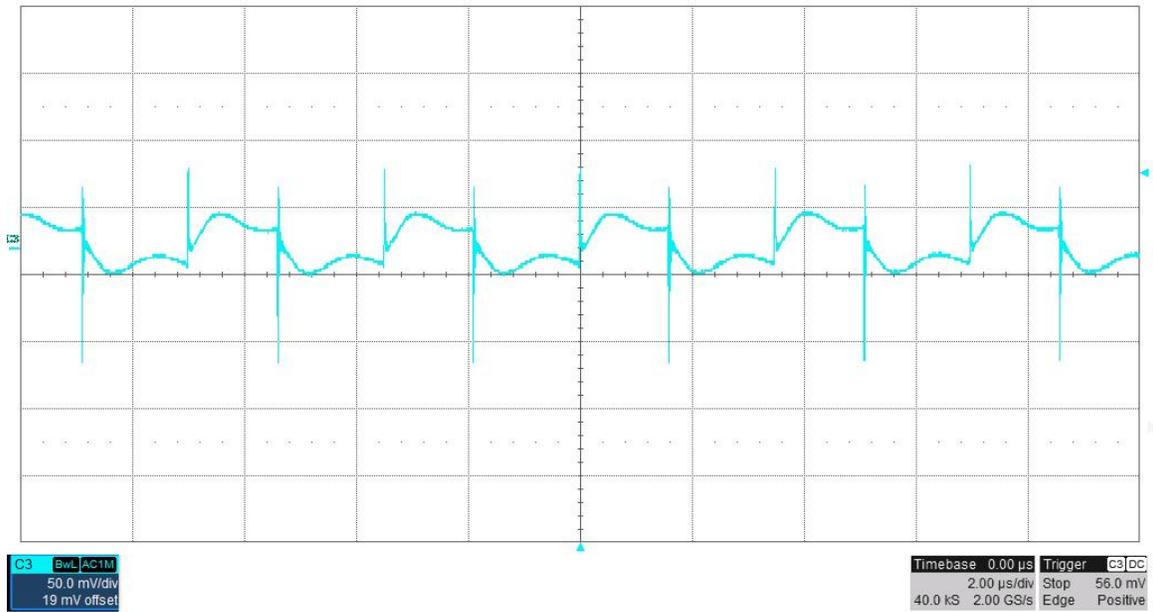


The 5.2V output ripple voltage is shown in the figure below. The image was taken with the output loaded to 2A. The input voltage is set to 12V. (50mV/DIV, 2uS/DIV)

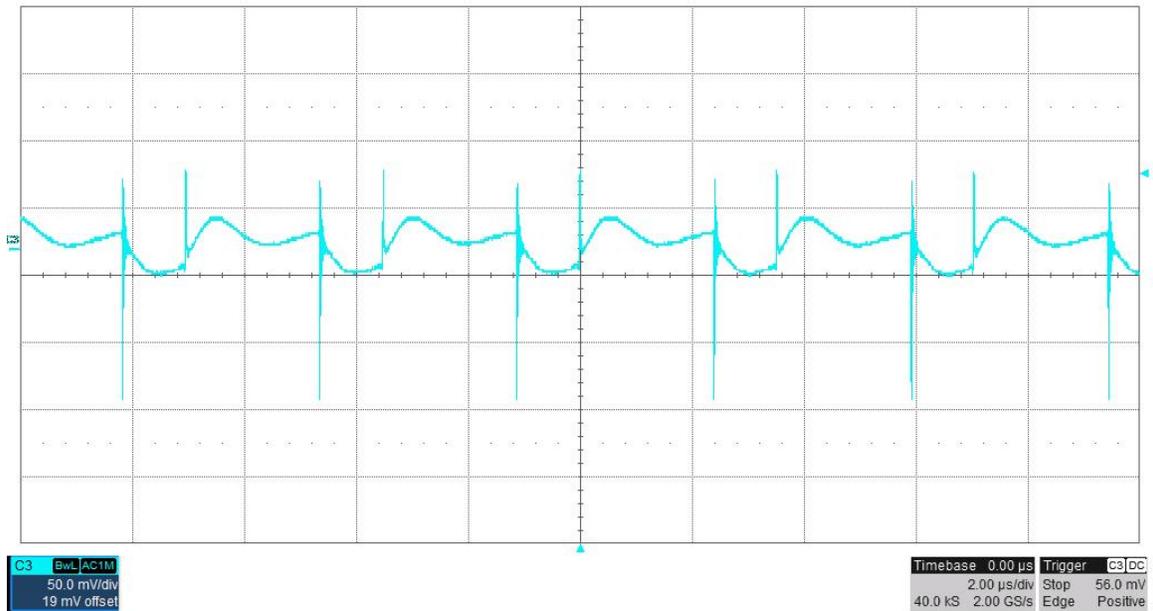

The 5.2V output ripple voltage is shown in the figure below. The image was taken with the output loaded to 2A. The input voltage is set to 24V. (50mV/DIV, 2uS/DIV)

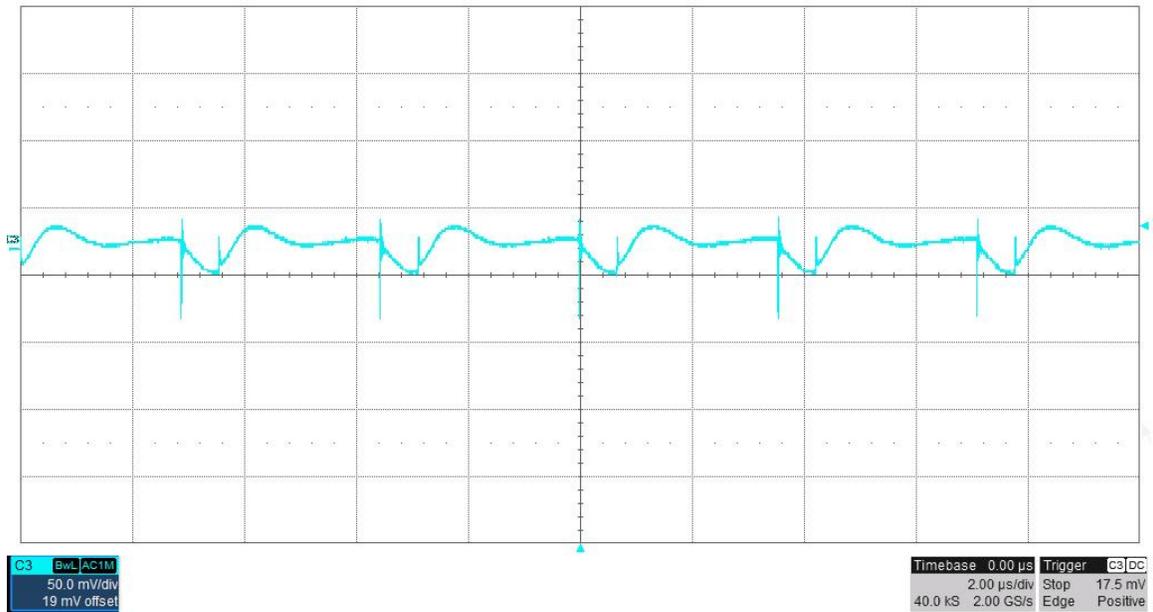


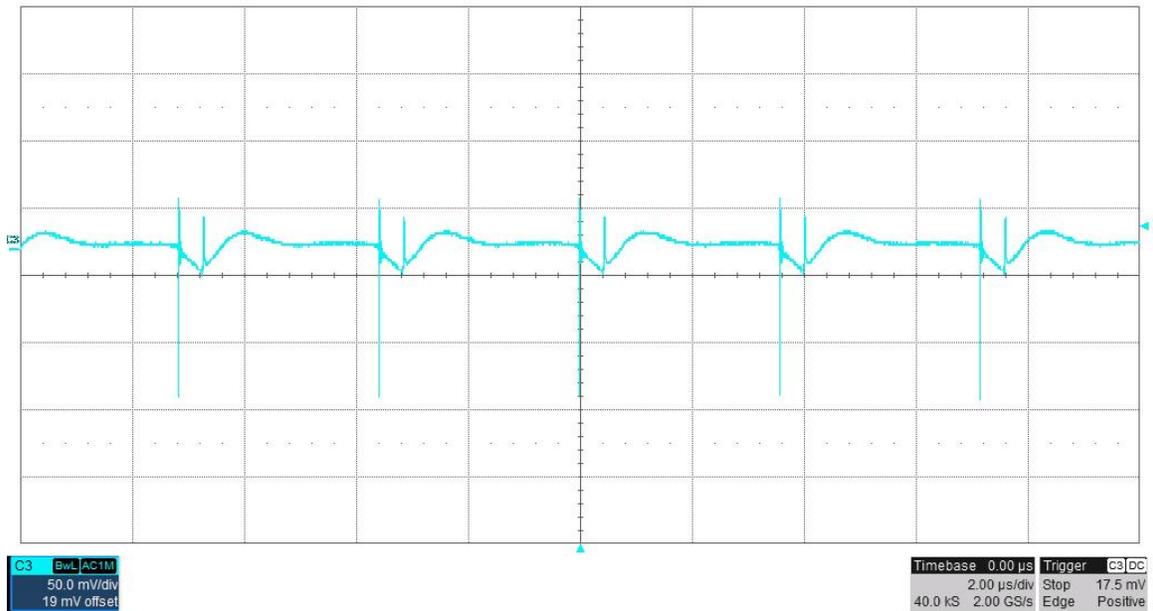The 5.2V output ripple voltage is shown in the figure below. The image was taken with the output loaded to 2A. The input voltage is set to 40V. (50mV/DIV, 2uS/DIV)




4 Load Transients

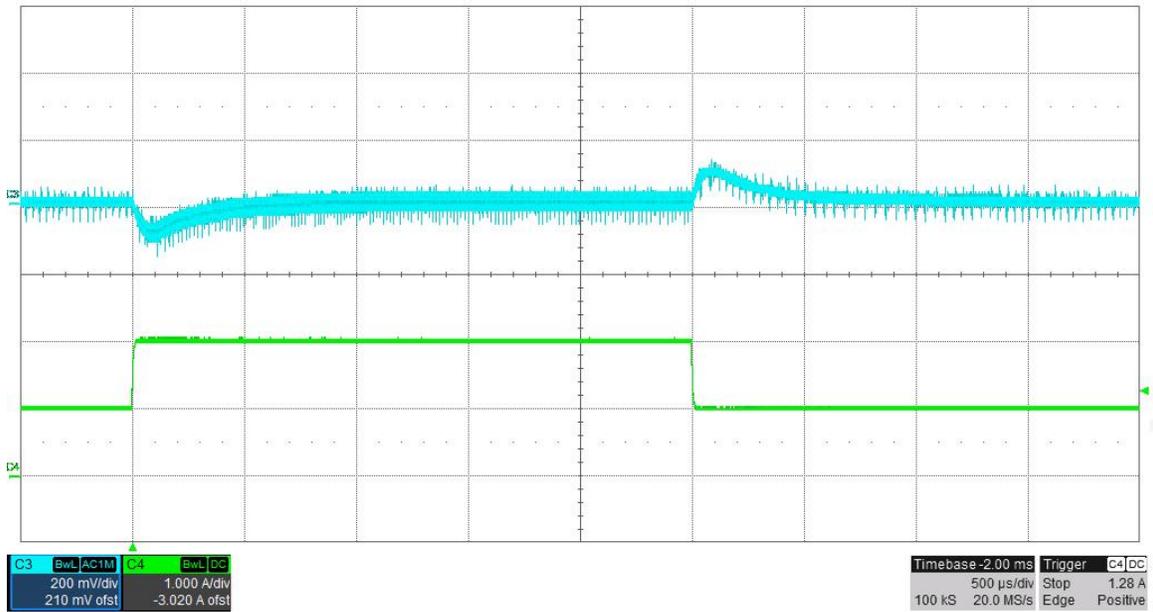
The waveform below shows the output voltage (ac coupled) when the load current is stepped between 1A and 2A. $V_{in} = 5V$. (200mV/DIV, 1A/DIV, 500uS/DIV)



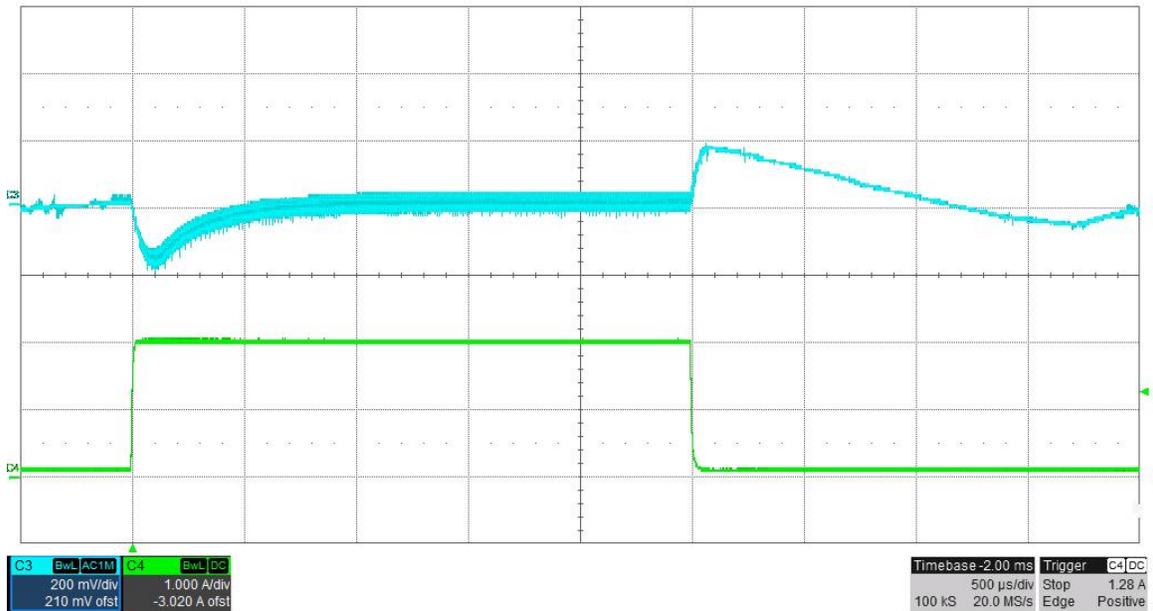
The waveform below shows the output voltage (ac coupled) when the load current is stepped between 0.1A and 2A. $V_{in} = 5V$. (200mV/DIV, 1A/DIV, 500uS/DIV)



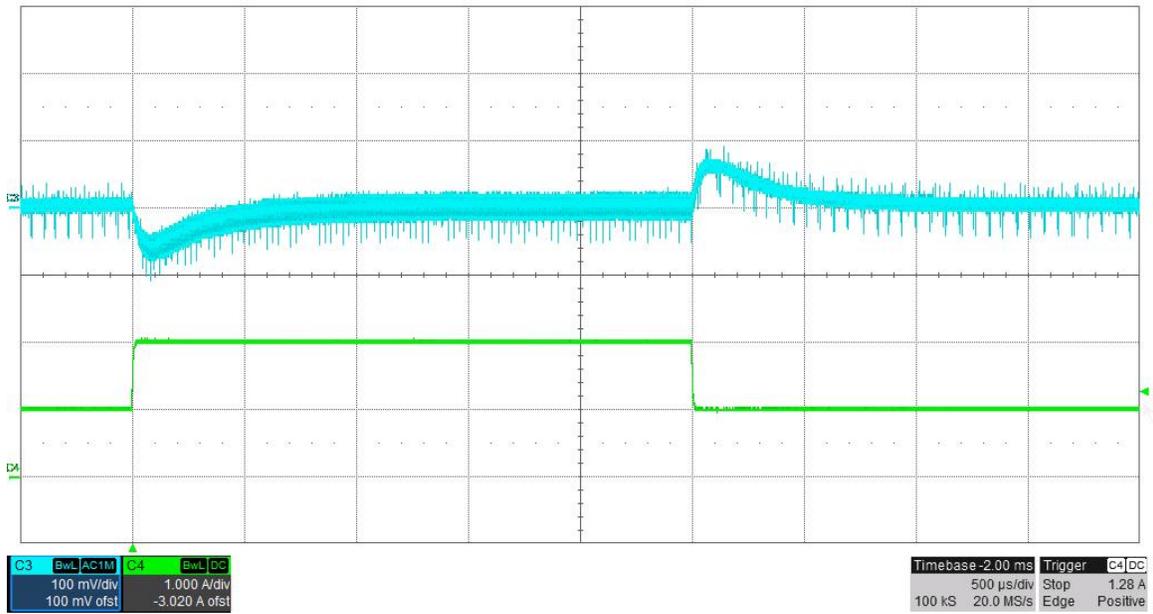
The waveform below shows the output voltage (ac coupled) when the load current is stepped between 1A and 2A. $V_{in} = 12V$. (100mV/DIV, 1A/DIV, 500uS/DIV)



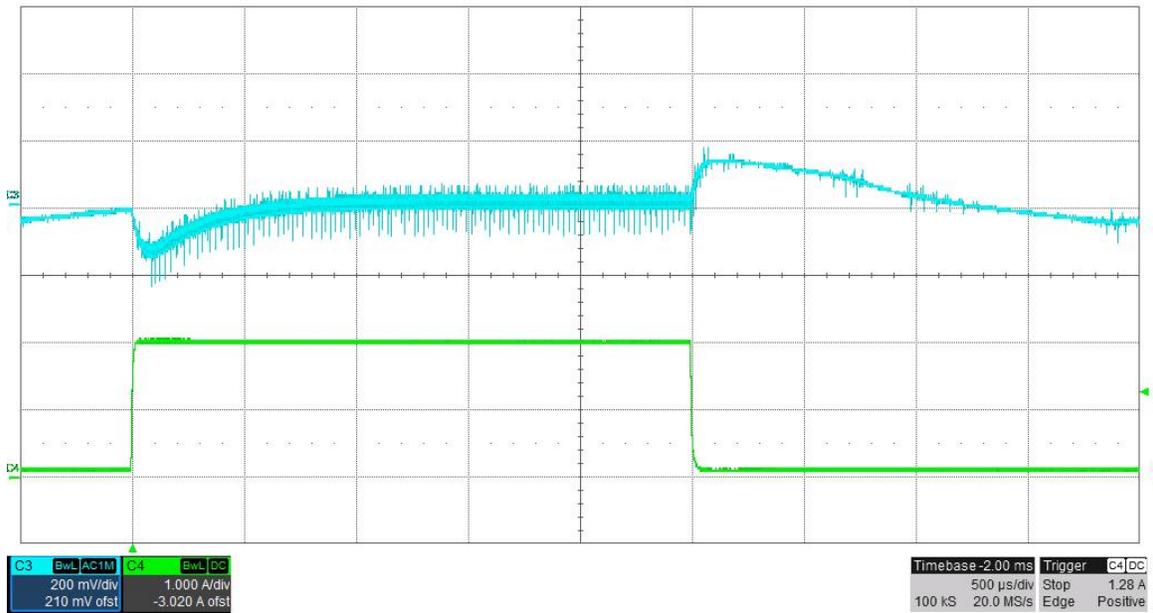
The waveform below shows the output voltage (ac coupled) when the load current is stepped between 0.1A and 2A. $V_{in} = 12V$. (200mV/DIV, 1A/DIV, 500uS/DIV)



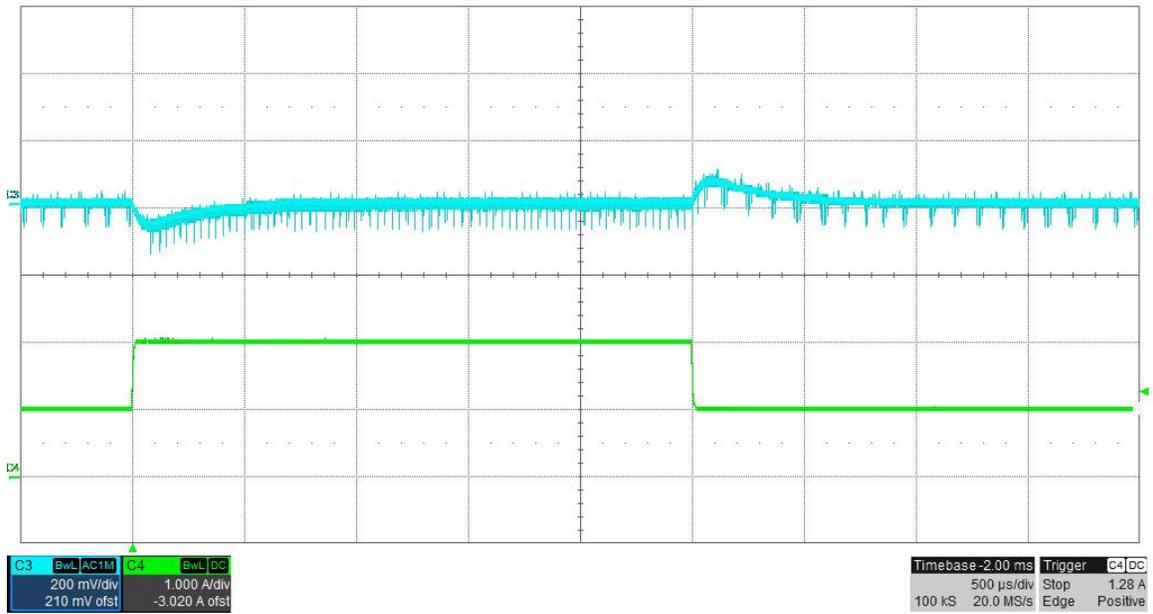The waveform below shows the output voltage (ac coupled) when the load current is stepped between 1A and 2A. $V_{in} = 40V$. (200mV/DIV, 1A/DIV, 500uS/DIV)




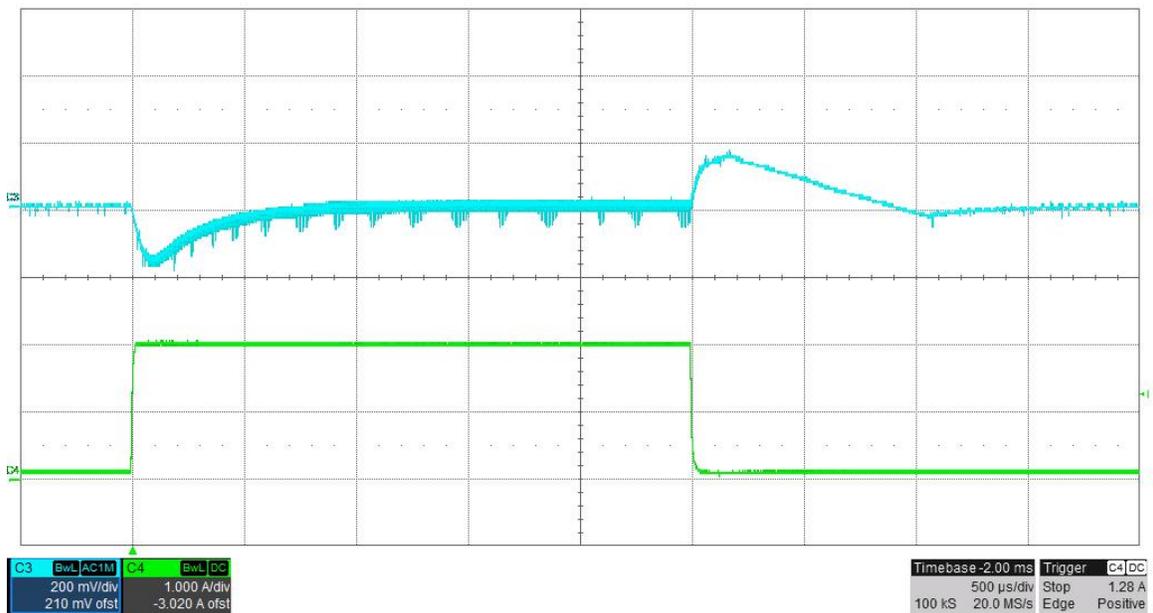The waveform below shows the output voltage (ac coupled) when the load current is stepped between 0.1A and 2A. $V_{in} = 40V$. (200mV/DIV, 1A/DIV, 500uS/DIV)




5 Switch Node Waveforms

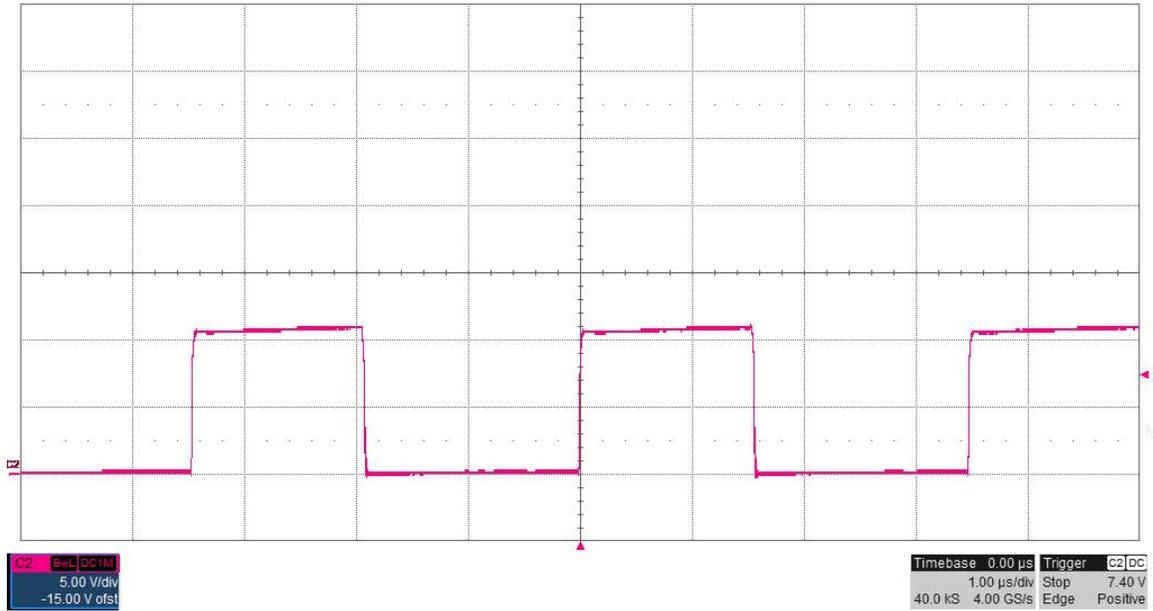
The photo below shows the 5.2V SEPIC switch node (TP1). The input voltage is 4.75V and the output is loaded to 2A. (5V/DIV, 1uS/DIV)



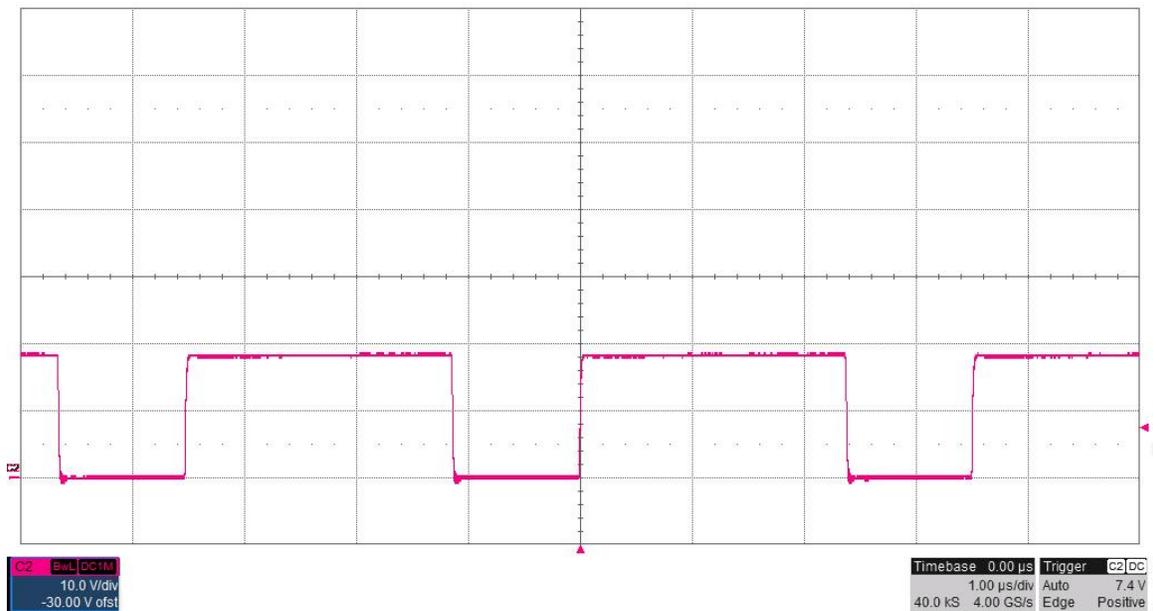
The photo below shows the 5.2V SEPIC switch node (TP1). The input voltage is 12V and the output is loaded to 2A. (10V/DIV, 1uS/DIV)



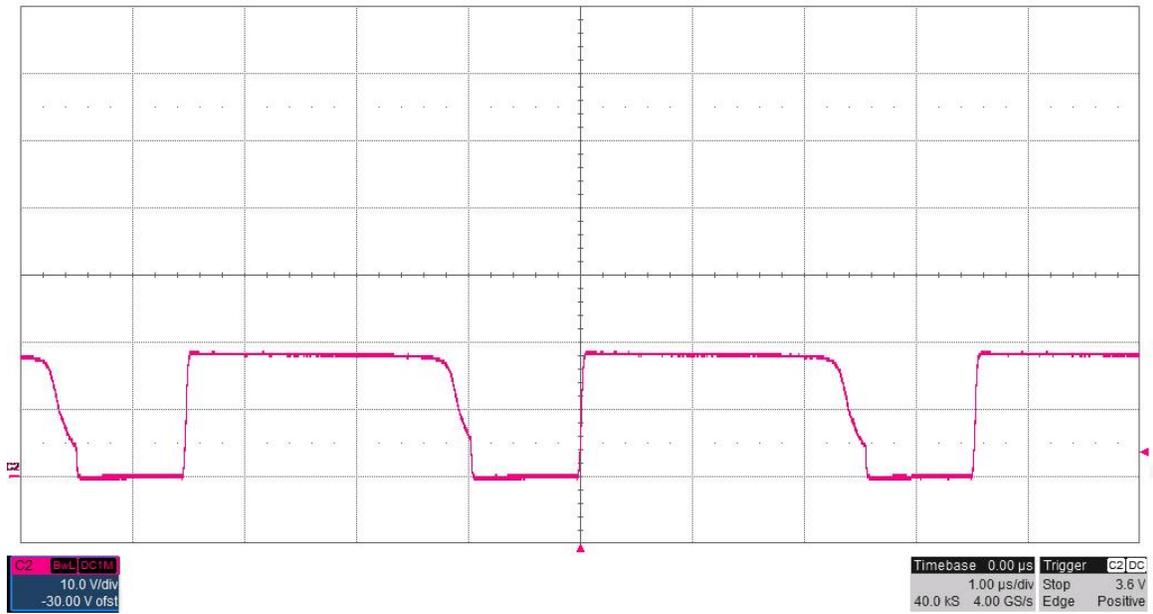The photo below shows the 5.2V SEPIC switch node (TP1). The input voltage is 12V and the output is loaded to 0.15A. The converter is operating in discontinuous mode. (10V/DIV, 1uS/DIV)



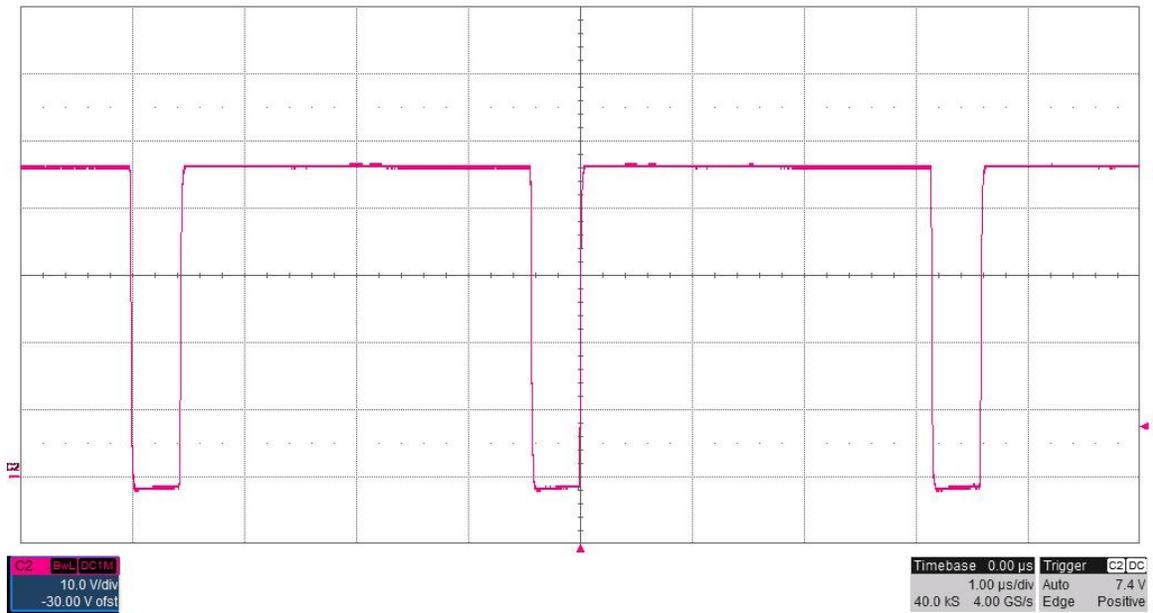The photo below shows the 5.2V SEPIC switch node (TP1). The input voltage is 40V and the output is loaded to 2A. (10V/DIV, 1uS/DIV)




6 Control Loop Gain / Stability

The plot below shows the 5.2V loop gain and phase margin with the output loaded to 2A. The input voltage was set to 5V.

Band Width = 3.10KHz,


Phase Margin = 50 degrees

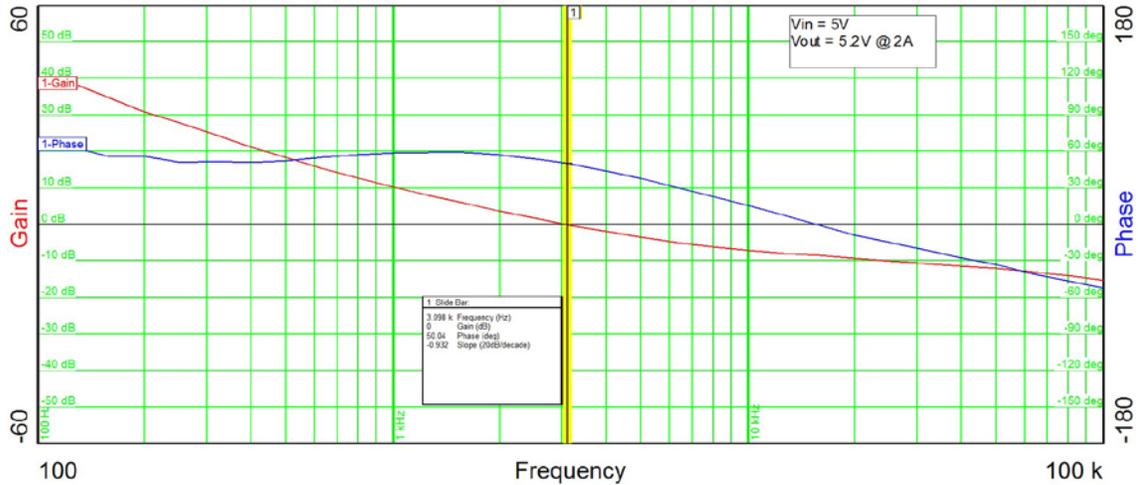

The plot below shows the 5.2V loop gain and phase margin with the output loaded to 2A. The input voltage was set to 12V.


Band Width = 4.03KHz,

Phase Margin = 75 degrees

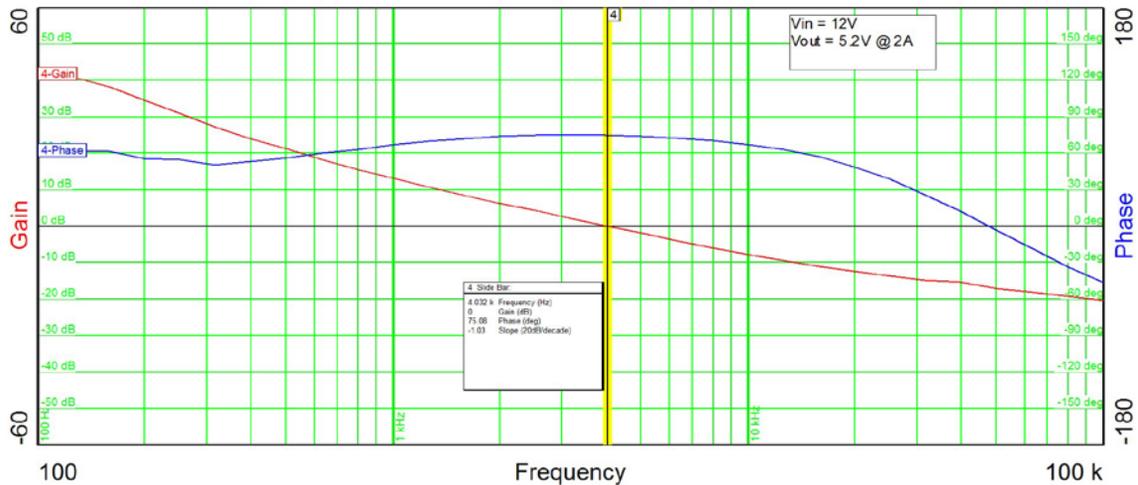


The plot below shows the 5.2V loop gain and phase margin with the output loaded to 2A. The input voltage was set to 24V.

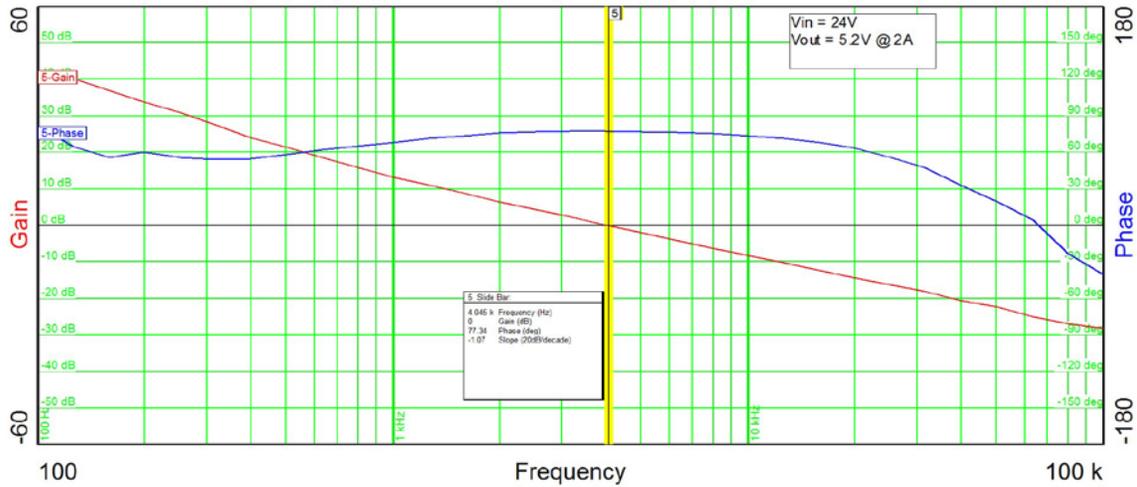Band Width = 4.05KHz, Phase Margin = 77 degrees




The plot below shows the 5.2V loop gain and phase margin with the output loaded to 2A. The input voltage was set to 40V.

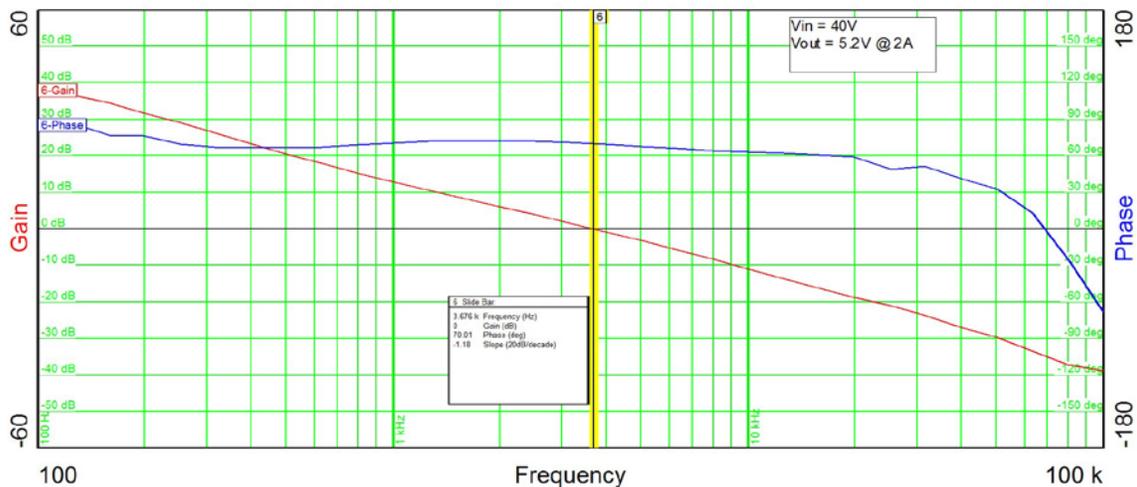Band Width = 3.68KHz, Phase Margin = 70 degrees




7 Photo

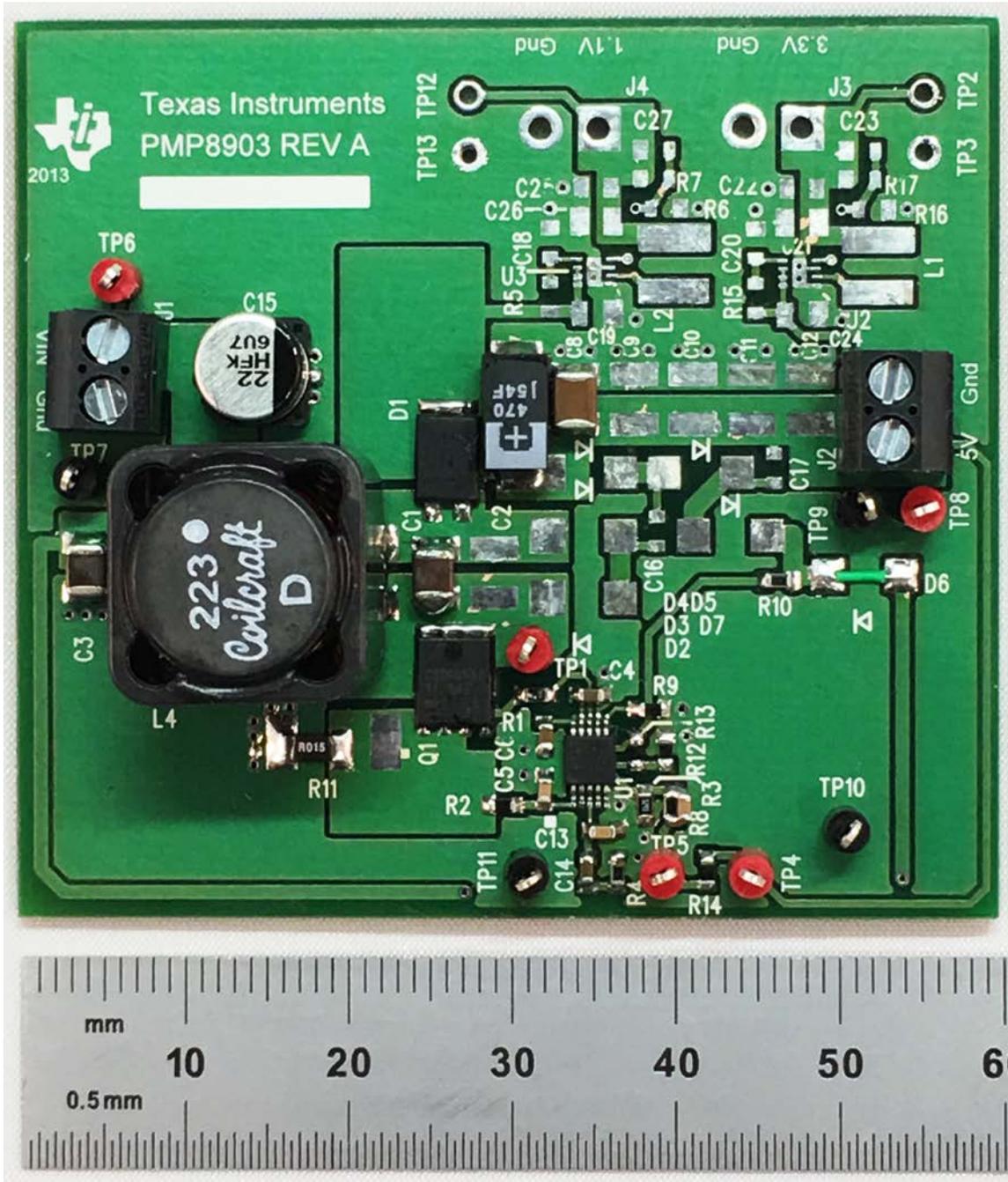The photo below shows the PMP20016 REVB assembly built on the PMP8903 REVA PWB.




8 Thermal Image

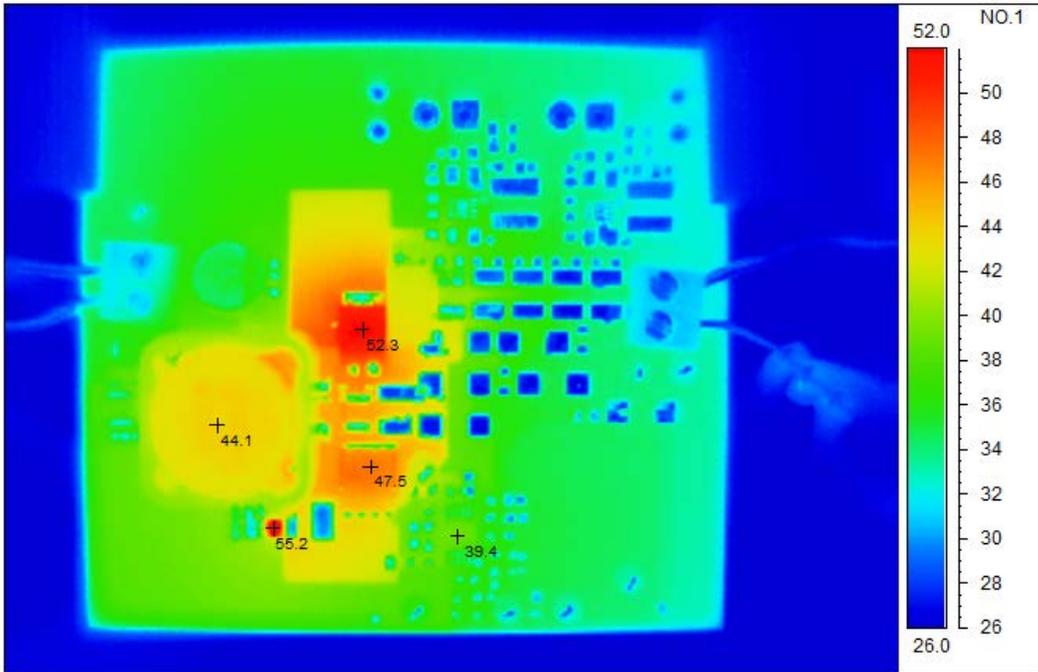A thermal image is shown below when operating at 5V input and 2A output, with no airflow.



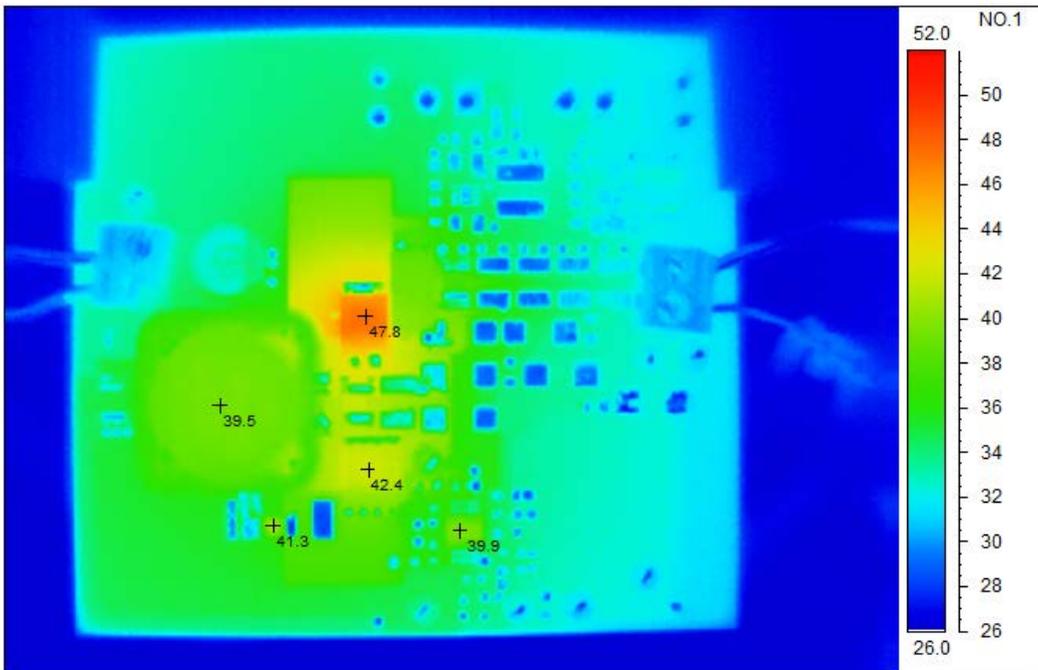A thermal image is shown below when operating at 12V input and 2A output, with no airflow.



IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated