



Test Report: PMP21455

Wide V_{AC} Input Flyback With an Integrated MOSFET Reference Design



Description

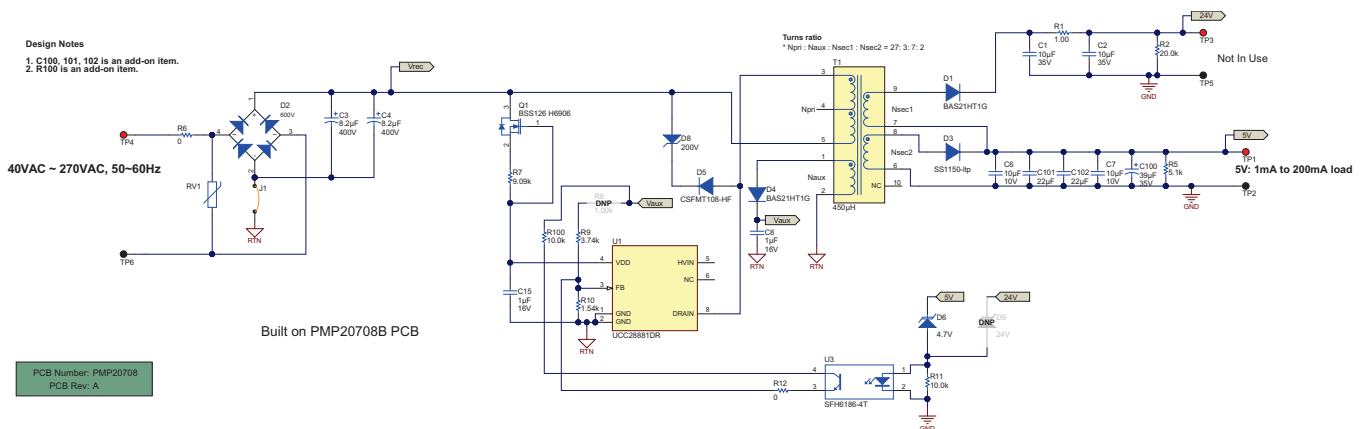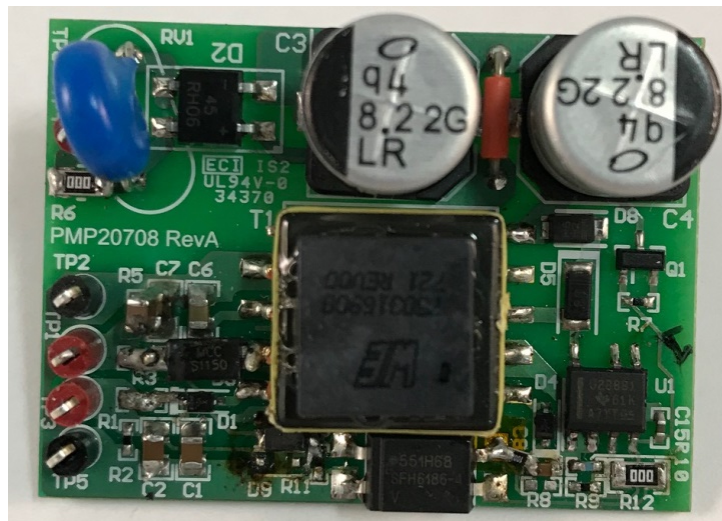This reference design uses an off-line switcher with an integrated MOSFET to provide 5 V and 200 mA output from an ultra-wide 40- V_{AC} to 270- V_{AC} input. The board is in a small form factor of 30 mm x 41 mm x 12 mm with minimized populated parts.



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 Test Prerequisites

1.1 Voltage and Current Requirements


Table 1. Voltage and Current Requirements

PARAMETER	SPECIFICATIONS
V_{IN}	40 V _{AC} –270 V _{AC}
V_{OUT}	5 V
I_{OUT}	200 mA

2 Testing and Results

2.1 Efficiency Graphs

Figure 1, Figure 2, and Figure 3 show the converter efficiency for a 40-, 120-, and 270-V_{AC} input with a 5-V output

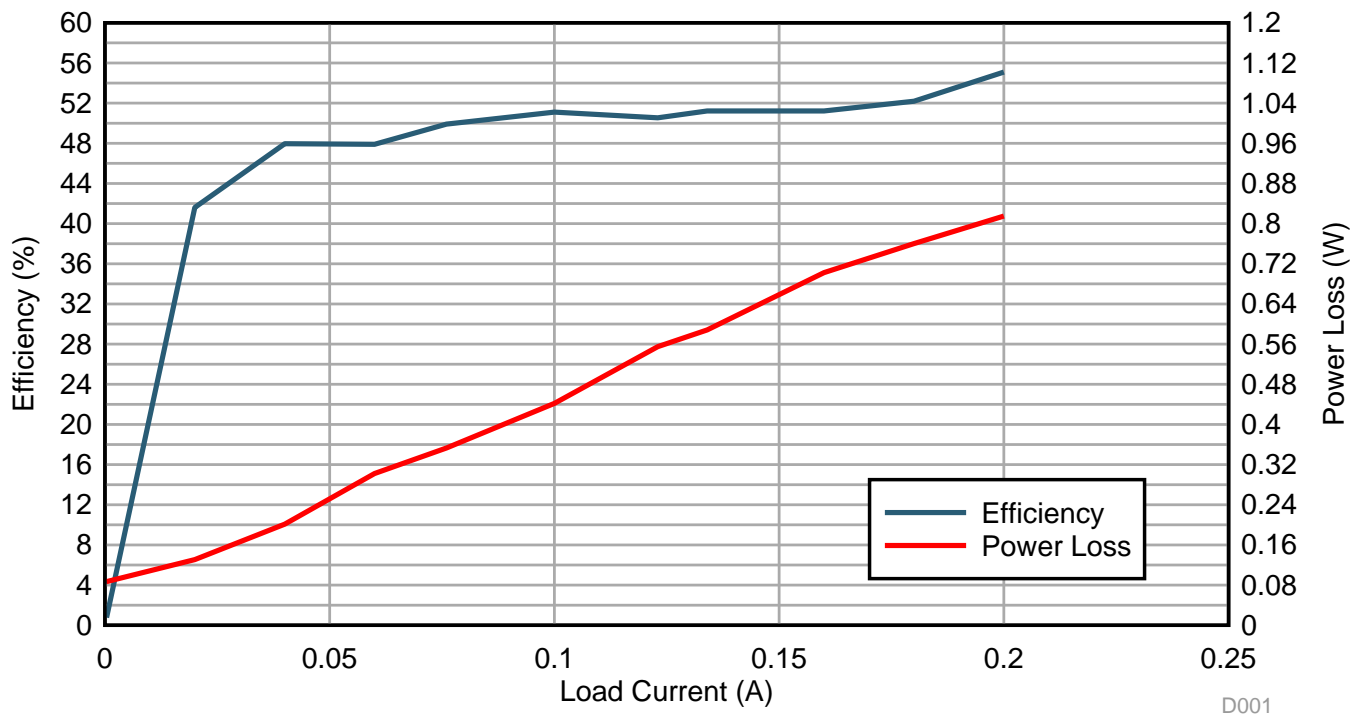
Figure 1. Converter Efficiency, 40 V_{AC}, 5-V Output

D001

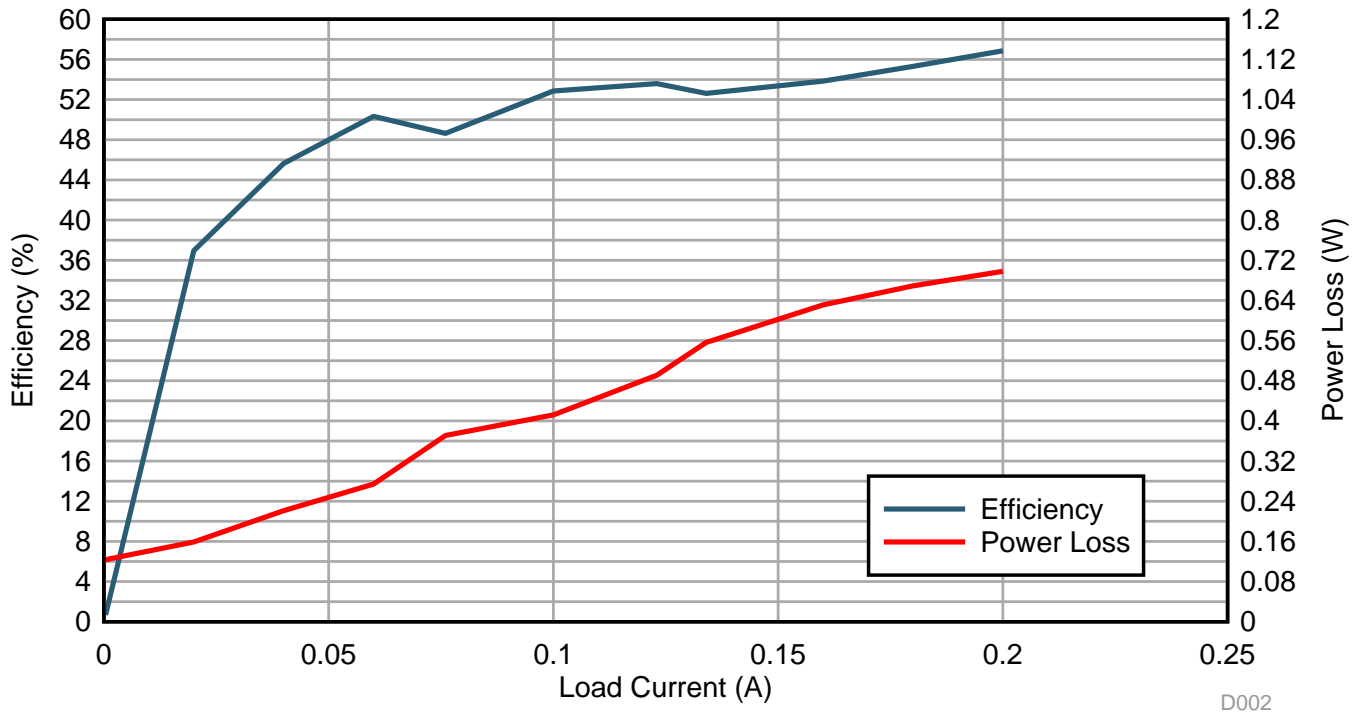


Figure 2. Converter Efficiency, 120 V_{AC}, 5-V Output

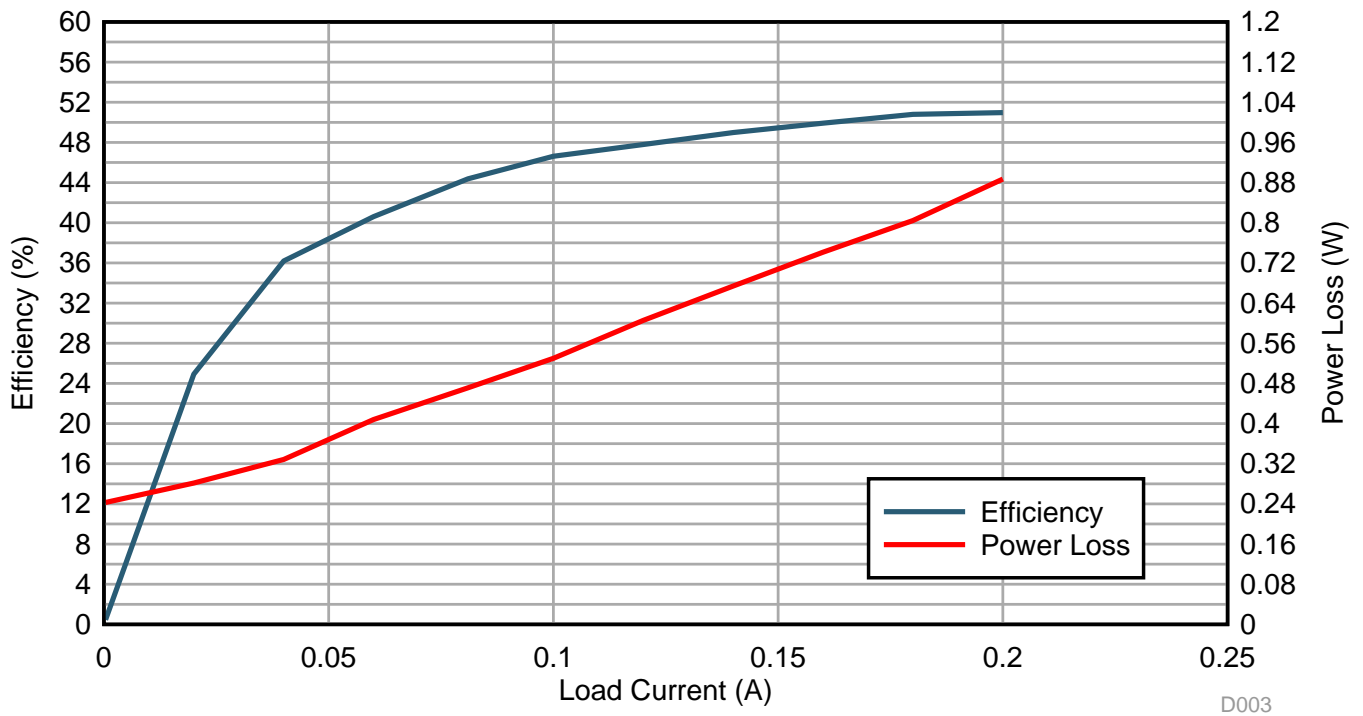


Figure 3. Converter Efficiency, 270 V_{AC}, 5-V Output

2.2 Efficiency Data

Table 2, Table 3, and Table 4 show the efficiency data for a 40-, 120-, and 270--V input with a 1-V output.

Table 2. Efficiency Data 40-V_{AC} Input With 1-V Output

I _{OUT}	V _{OUT}	V _{IN AC}	I _{IN Arms} (mA)	P _{IN}	P _{OUT}	LOSSES	EFFICIENCY
0.000	5.250	40.0	5.90000	0.0860	0.00	0.09	0.0%
0.020	4.660	40.0	13.6400	0.2240	0.09	0.13	41.6%
0.040	4.640	40.0	21.630	0.3870	0.19	0.20	48.0%
0.060	4.630	40.0	30.000	0.5800	0.28	0.30	47.9%
0.076	4.630	40.0	35.000	0.7050	0.35	0.35	49.9%
0.100	4.620	40.0	43.000	0.9040	0.46	0.44	51.1%
0.123	4.610	40.0	52.000	1.1220	0.57	0.55	50.5%
0.134	4.610	40.0	55.000	1.2060	0.62	0.59	51.2%
0.160	4.610	40.0	64.000	1.4400	0.74	0.70	51.2%
0.180	4.610	40.0	70.000	1.5900	0.83	0.76	52.2%
0.200	5.000	40.0	78.000	1.8150	1.00	0.82	55.1%

Table 3. Efficiency Data 120-V_{AC} Input With 1-V Output

I _{OUT}	V _{OUT}	V _{IN AC}	I _{IN Arms} (mA)	P _{IN}	P _{OUT}	LOSSES	EFFICIENCY
0.000	5.330	120.0	4.16000	0.1230	0.00	0.12	0.0%
0.020	4.657	120.0	7.5000	0.2520	0.09	0.16	37.0%
0.040	4.644	120.0	11.000	0.4070	0.19	0.22	45.6%
0.060	4.630	120.0	15.000	0.5520	0.28	0.27	50.3%
0.076	4.620	120.0	18.000	0.7220	0.35	0.37	48.6%
0.100	4.620	120.0	22.000	0.8740	0.46	0.41	52.9%
0.123	4.610	120.0	26.000	1.0580	0.57	0.49	53.6%
0.134	4.610	120.0	28.000	1.1740	0.62	0.56	52.6%
0.160	4.600	120.0	31.000	1.3670	0.74	0.63	53.8%
0.180	4.600	120.0	34.000	1.4970	0.83	0.67	55.3%
0.200	4.600	120.0	36.000	1.6180	0.92	0.70	56.9%

Table 4. Efficiency Data 270-V_{AC} Input With 1-V Output

I _{OUT}	V _{OUT}	V _{IN AC}	I _{IN Arms} (mA)	P _{IN}	P _{OUT}	LOSSES	EFFICIENCY
0.000	5.420	270.0	3.73000	0.2420	0.00	0.24	0.0%
0.022	4.673	270.0	6.0000	0.3750	0.10	0.27	27.4%
0.040	4.660	270.0	8.000	0.5150	0.19	0.33	36.2%
0.060	4.650	270.0	10.000	0.6870	0.28	0.41	40.6%
0.081	4.640	270.0	12.000	0.8470	0.38	0.47	44.4%
0.100	4.630	270.0	14.000	0.9930	0.46	0.53	46.6%
0.120	4.620	270.0	16.000	1.1600	0.55	0.61	47.8%
0.140	4.622	270.0	18.000	1.3210	0.65	0.67	49.0%
0.160	4.617	270.0	20.000	1.4800	0.74	0.74	49.9%
0.180	4.614	270.0	22.000	1.6350	0.83	0.80	50.8%
0.200	4.610	270.0	24.000	1.8090	0.92	0.89	51.0%

2.3 Thermal Images

Figure 4 shows the thermal image operation at 120-V_{AC} input and 5 V at 0.2-A output, with no airflow. The board ran for 20 minutes under these conditions before the thermal image was taken.

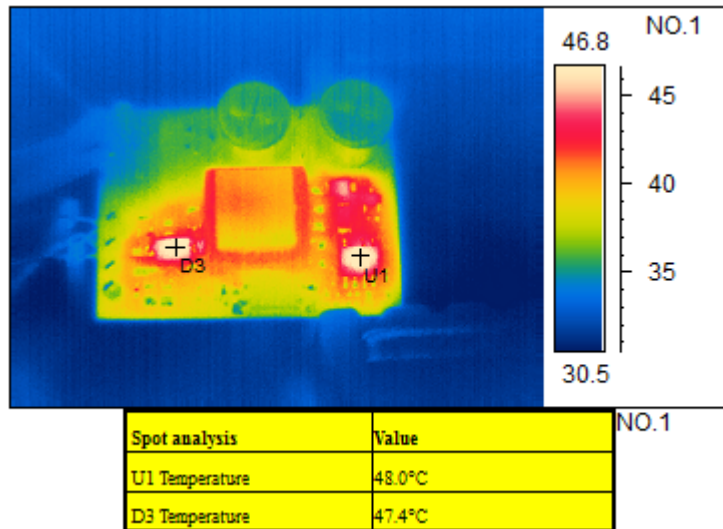


Figure 4. Top Thermal

2.4 Dimensions

Figure 5 and Figure 5 present the top and bottom PMP21455 photos (and their dimensions) with a 5-V output.

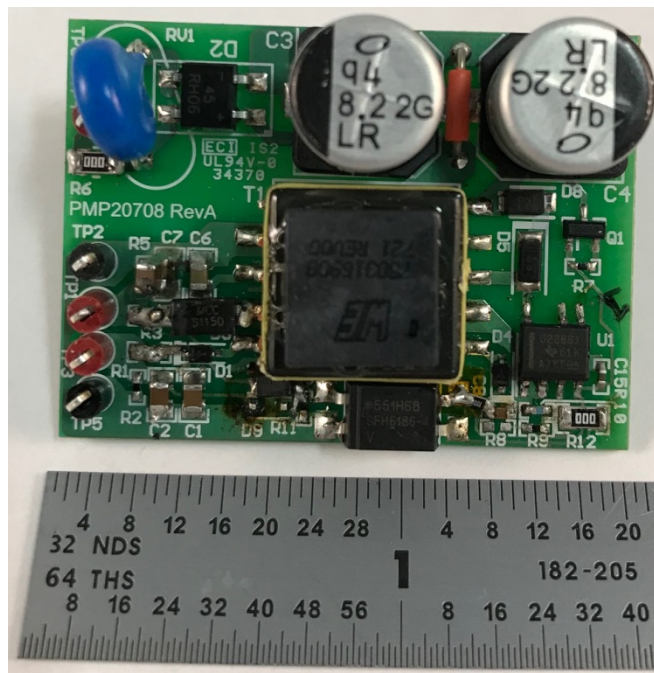


Figure 5. PMP21455 Device Dimensions (Top View)

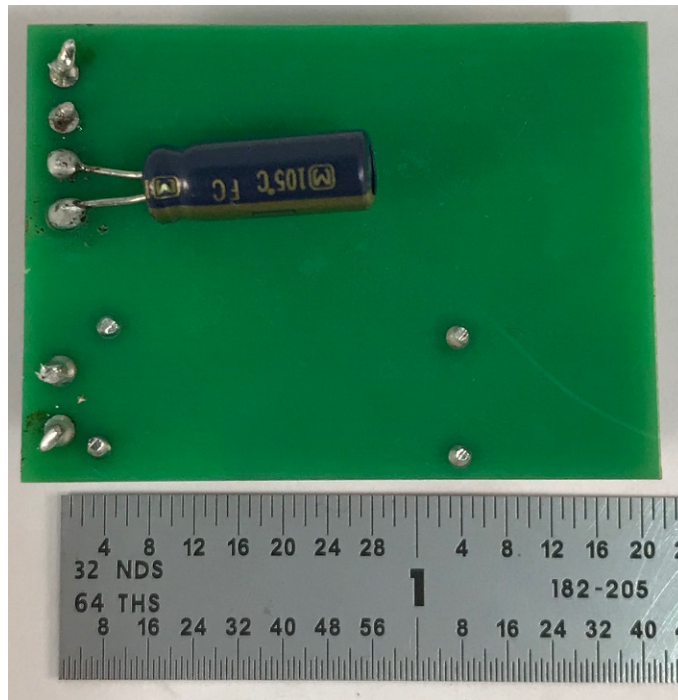


Figure 6. PMP21455 Device Dimensions (Bottom View)

3 Waveforms

3.1 Switching

Figure 7 and Figure 8 show the switch node voltage with the input voltage at 40 V_{AC} and the 5-V output is at no load then full load (0.2 A), respectively.

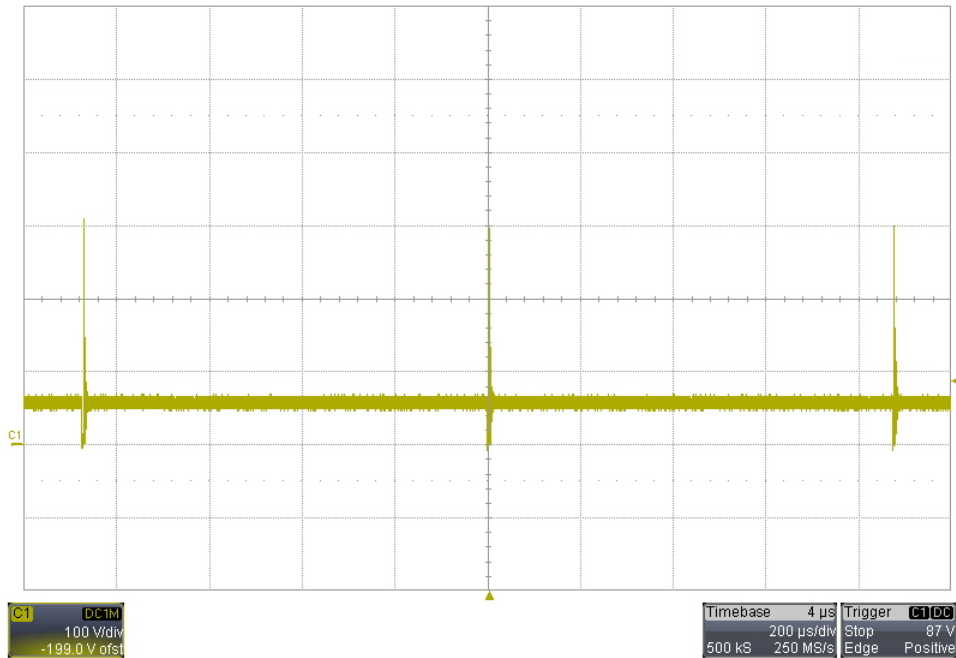


Figure 7. Switch Node Voltage, V_{IN} = 40 V, 5-V V_{OUT} = 0-mA Load

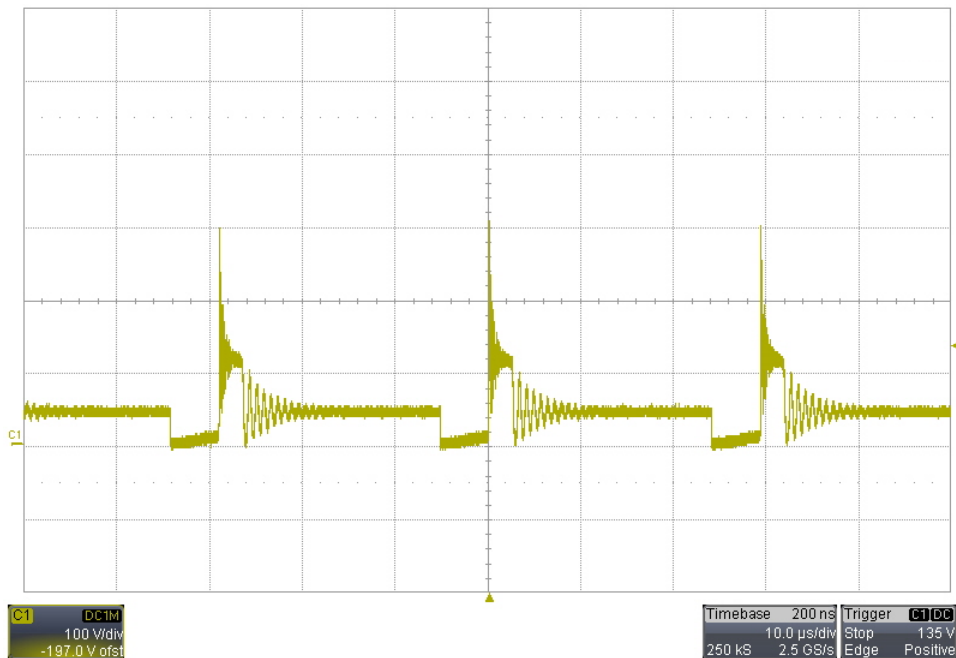


Figure 8. Switch Node Voltage, V_{IN} = 40 V, 5-V V_{OUT} = 200-mA Load

Figure 9 and Figure 10 show the switch node voltage with the input voltage at 120 V_{AC} and the 5-V output is at no load then full load (0.2 A), respectively.

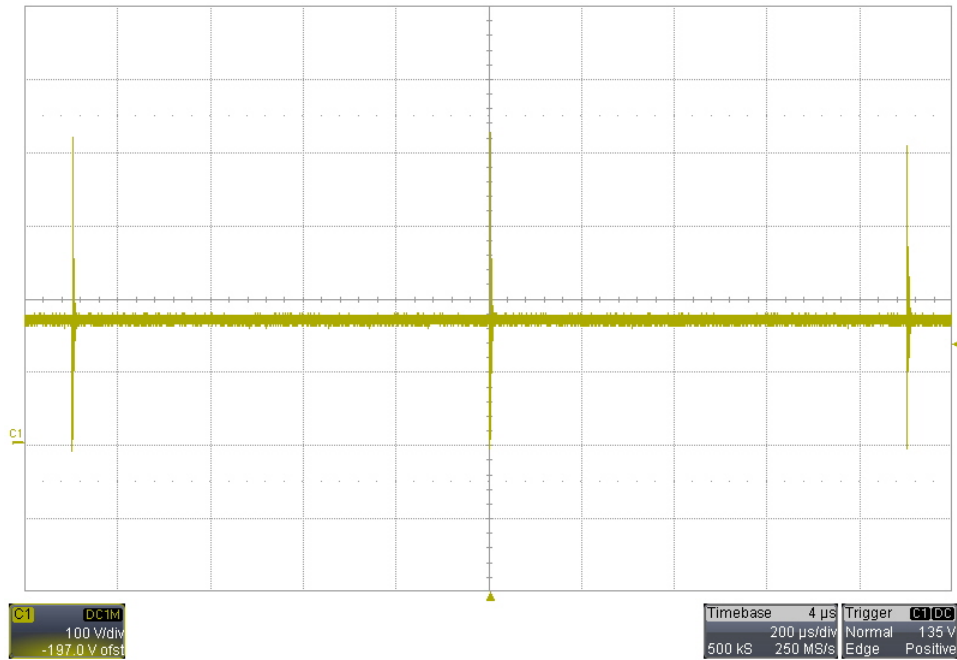


Figure 9. Switch Node Voltage, V_{IN} = 120 V, 5-V V_{OUT} = 0-mA Load

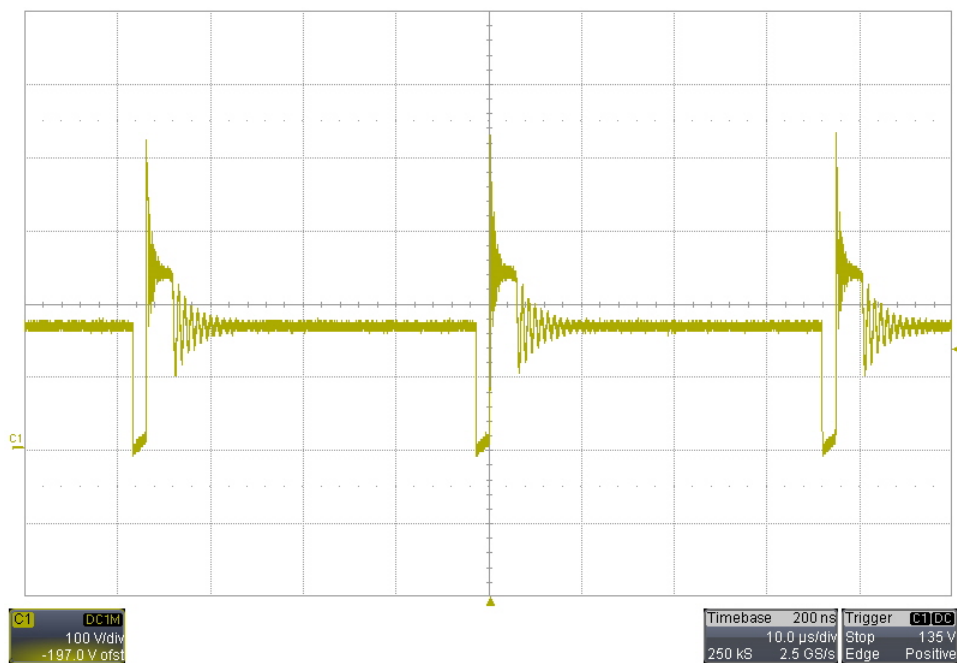


Figure 10. Switch Node Voltage, V_{IN} = 120 V, 5-V V_{OUT} = 200-mA Load

Figure 11 and Figure 12 show the switch node voltage with the input voltage at 40 V_{AC} and the 5-V output is at no load then full load (0.2 A), respectively.

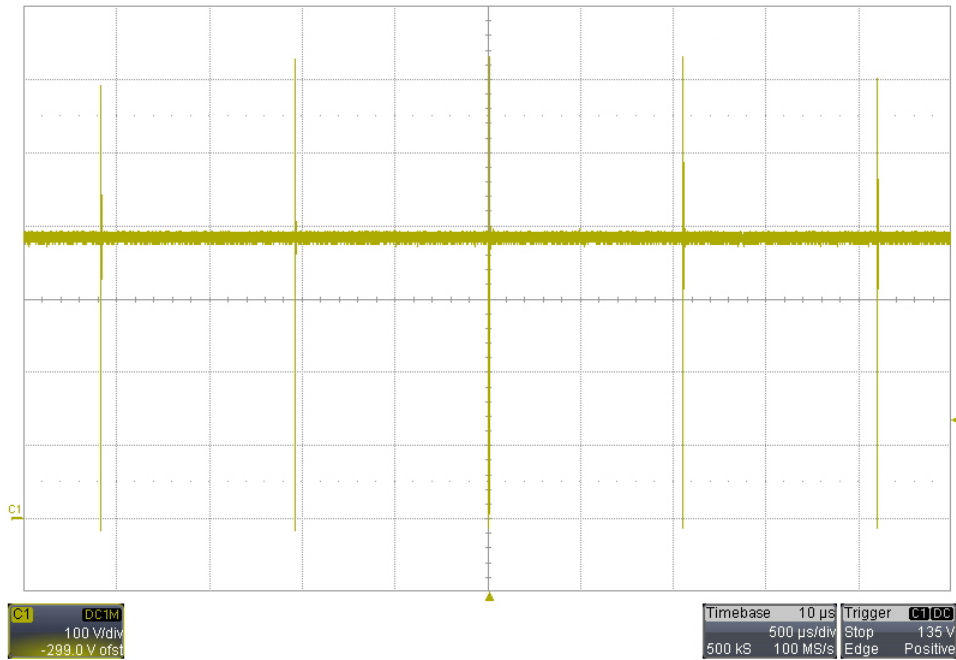


Figure 11. Switch Node Voltage, V_{IN} = 270 V, 5-V V_{OUT} = 0-mA Load

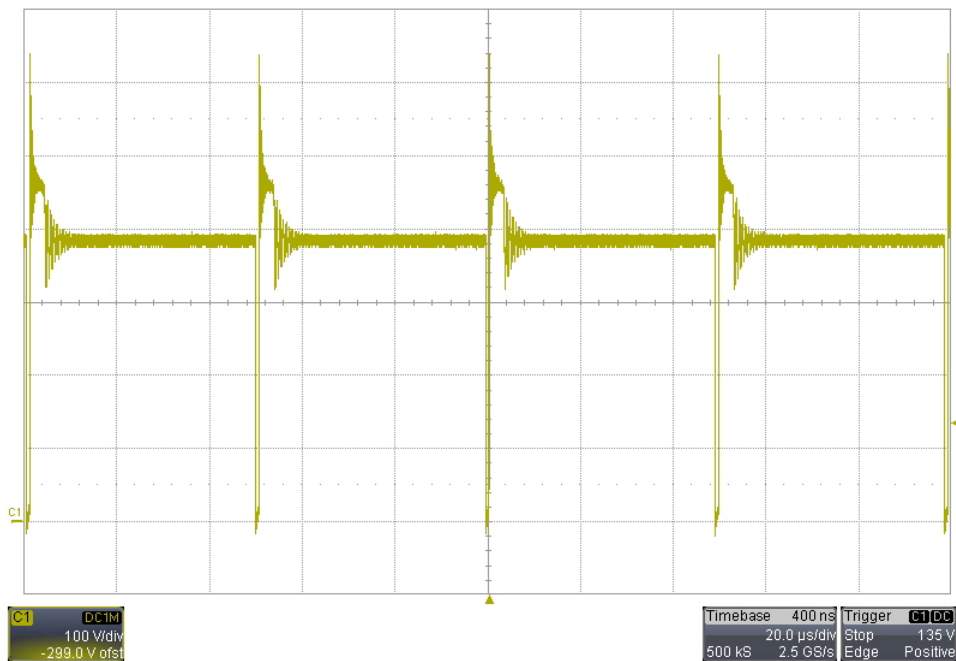


Figure 12. Switch Node Voltage, V_{IN} = 270 V, 5-V V_{OUT} = 200-mA Load

3.2 Output Voltage Ripple

Figure 13 shows the output ripple voltage with an input voltage of 40 V_{AC} and the 5-V output loaded to 0 mA.

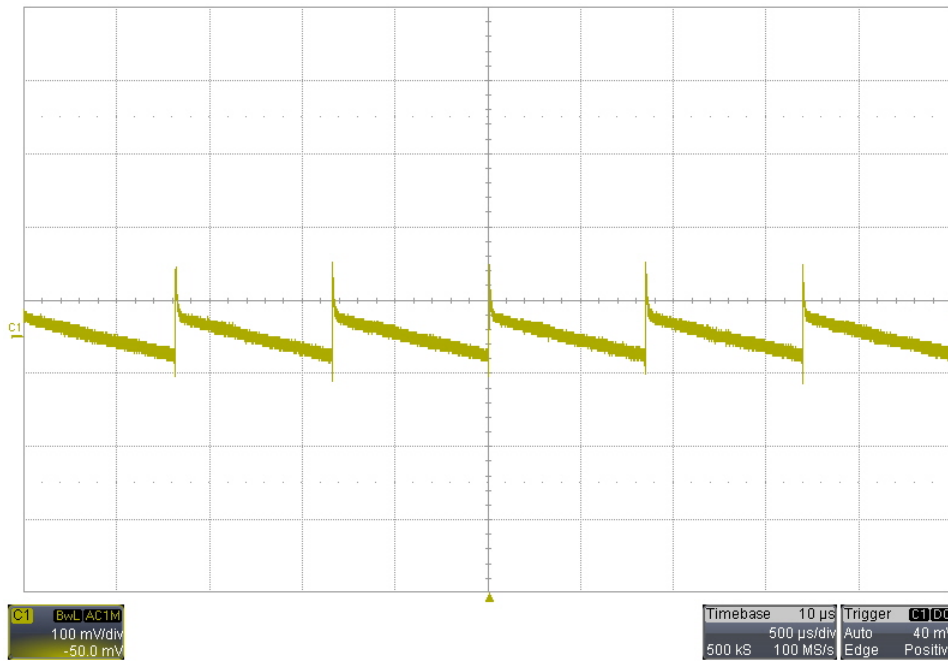


Figure 13. Output Voltage Ripple, V_{IN} = 40 V_{AC}, 5-V V_{OUT} = 0-mA Load

Figure 14 shows the output ripple voltage with an input voltage of 40 V_{AC} and the 5-V output loaded to 200 mA.

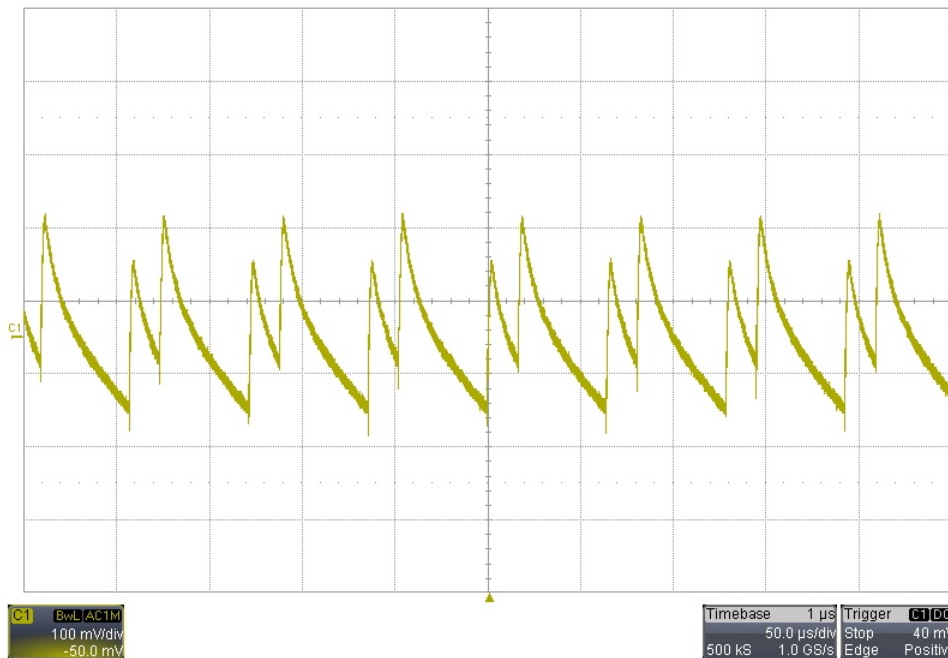


Figure 14. Output Voltage Ripple, V_{IN} = 40 V_{AC}, 5-V V_{OUT} = 200-mA Load

Figure 15 shows the output ripple voltage with an input voltage of 120 V_{AC} and the 5-V output loaded to 0 mA.

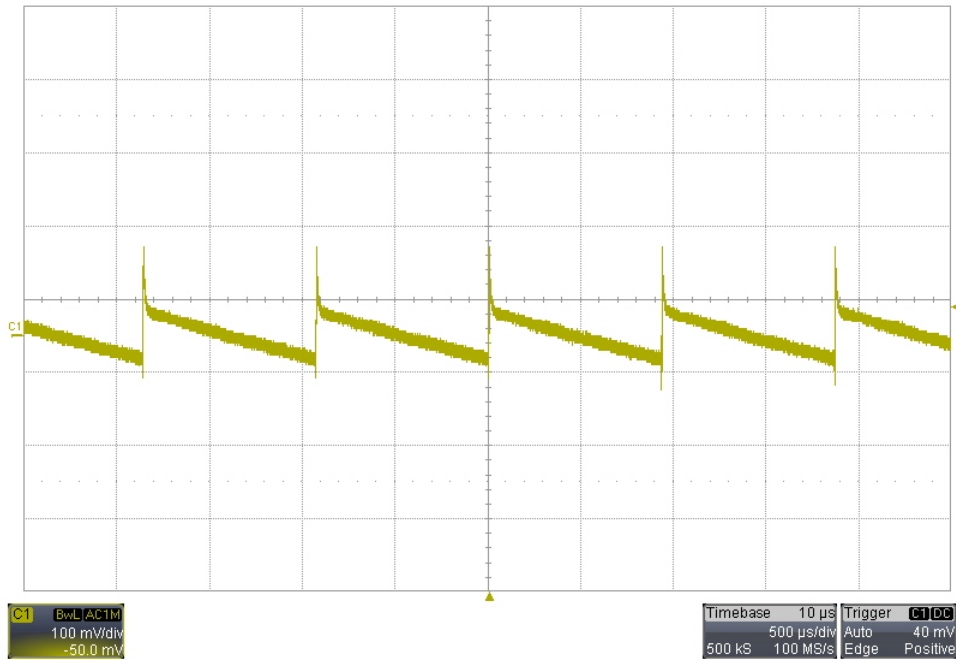


Figure 15. Output Voltage Ripple, V_{IN} = 120 V_{AC}, 5-V V_{OUT} = 0-mA Load

Figure 16 shows the output ripple voltage with an input voltage of 120 V_{AC} and the 5-V output loaded to 200 mA.

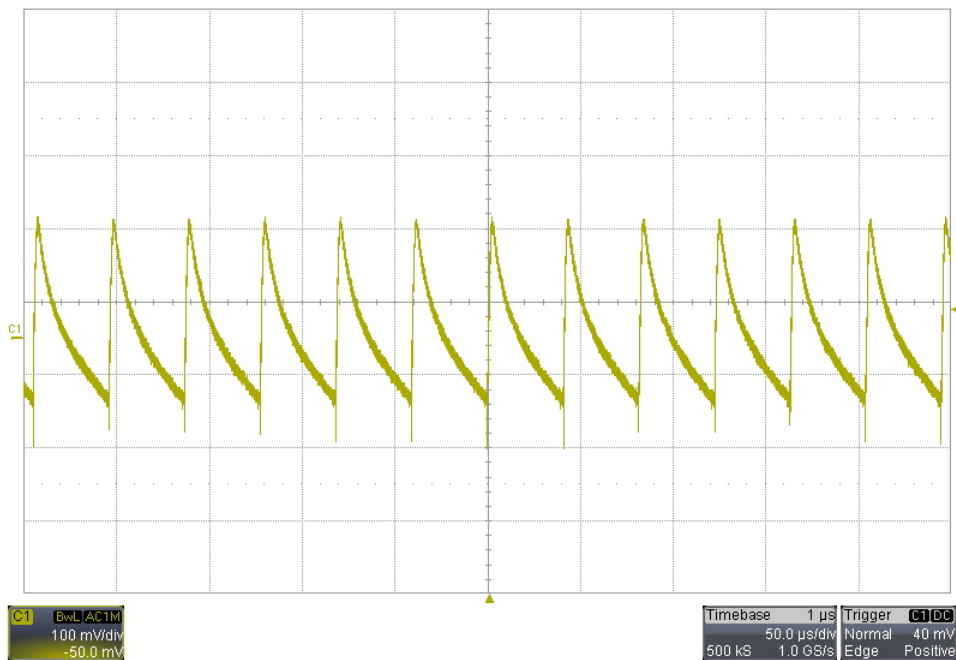


Figure 16. Output Voltage Ripple, V_{IN} = 120 V_{AC}, 5-V V_{OUT} = 200-mA Load

Figure 17 shows the output ripple voltage with an input voltage of 270 V_{AC} and the 5-V output loaded to 0 mA.

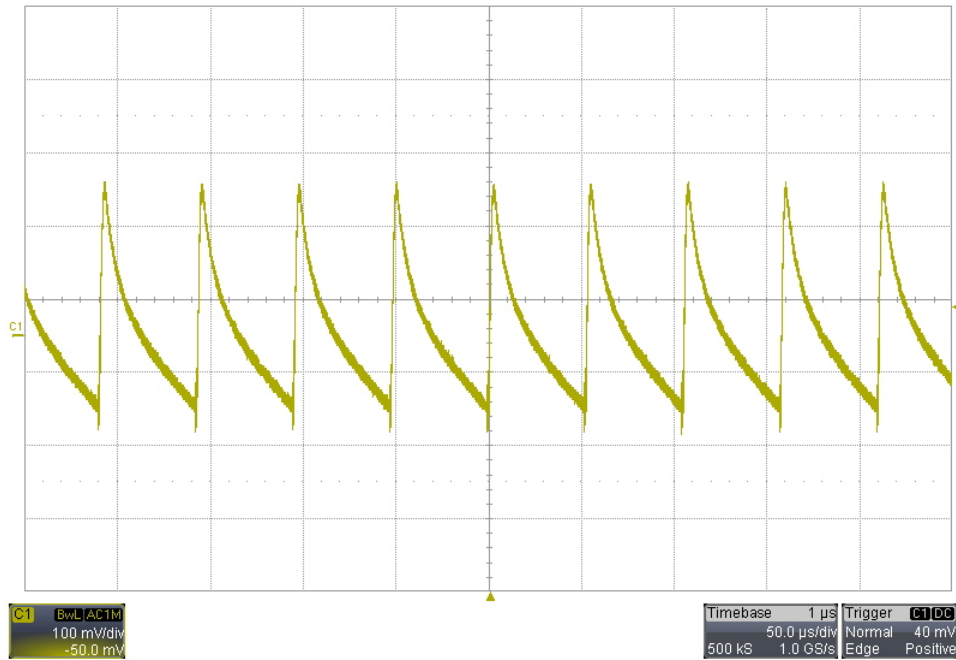


Figure 17. Output Voltage Ripple, V_{IN} = 270 V_{AC}, 5-V V_{OUT} = 0-mA Load

Figure 18 shows the output ripple voltage with an input voltage of 270 V_{AC} and the 5-V output loaded to 200 mA.

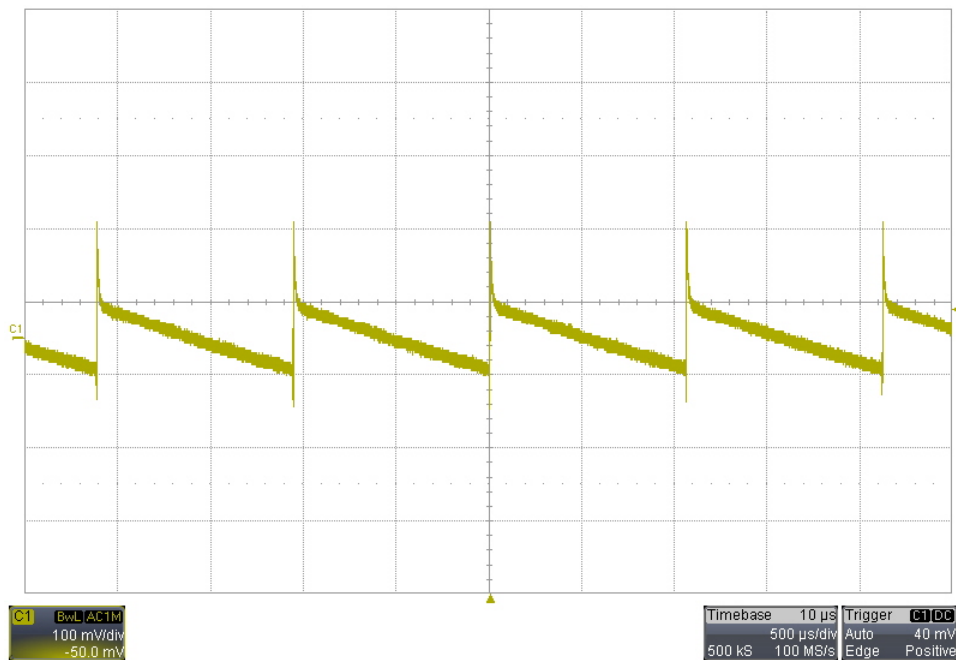


Figure 18. Output Voltage Ripple, V_{IN} = 270 V_{AC}, 5-V V_{OUT} = 200-mA Load

3.3 Start-up Sequence

Figure 19 and Figure 20 show the output voltage start-up waveform for 40 -V_{AC} input at no load then full load (0.2 A), respectively.

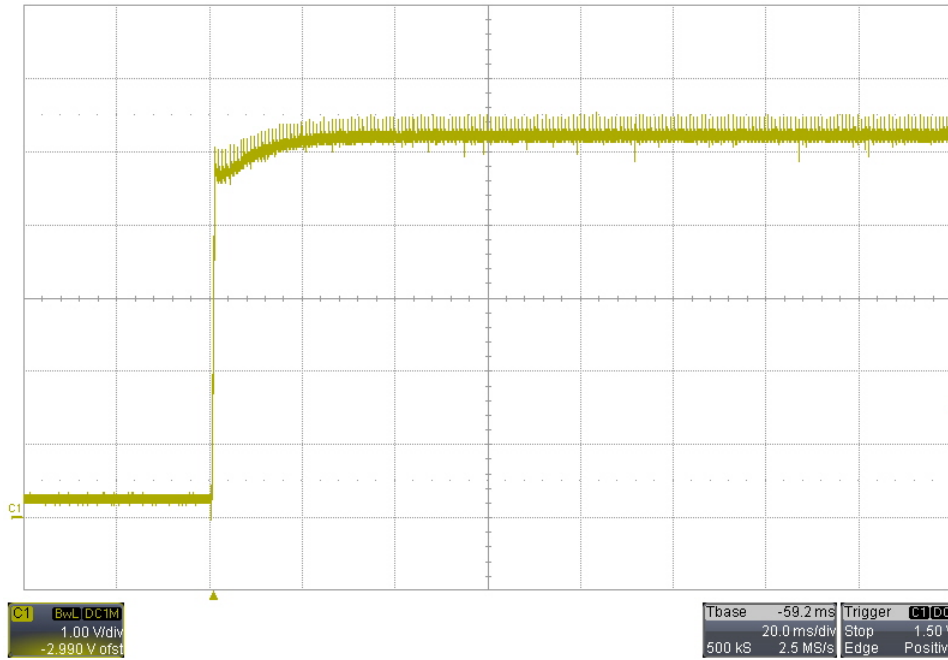


Figure 19. Output Voltage Start-up Waveform, 40 V_{AC}, 5-V V_{OUT} = 0-mA Load

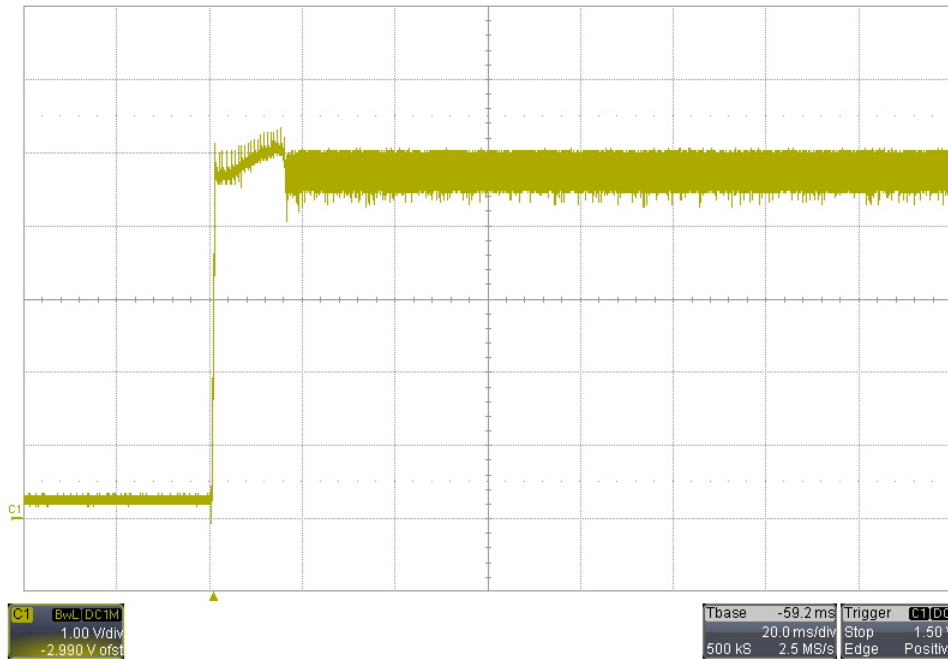


Figure 20. Output Voltage Start-up Waveform, 40 V_{AC}, 5-V V_{OUT} = 200-mA Load

Figure 21 and Figure 22 show the output voltage start-up waveform for 120-V_{AC} input at no load then full load (0.2 A), respectively.

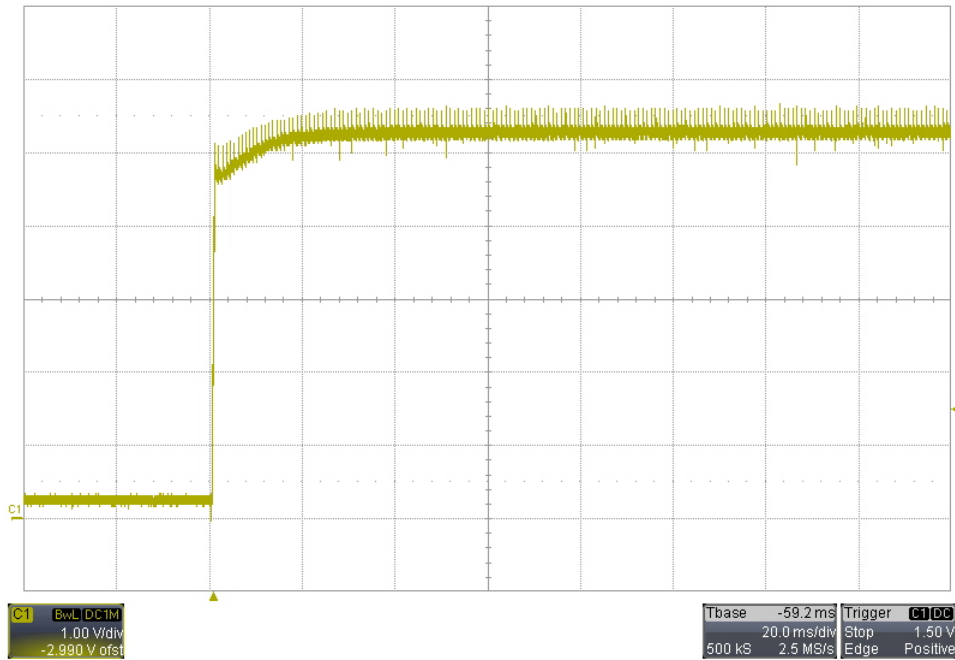


Figure 21. Output Voltage Start-up Waveform, 120 V_{AC}, 5-V V_{OUT} = 0-mA Load

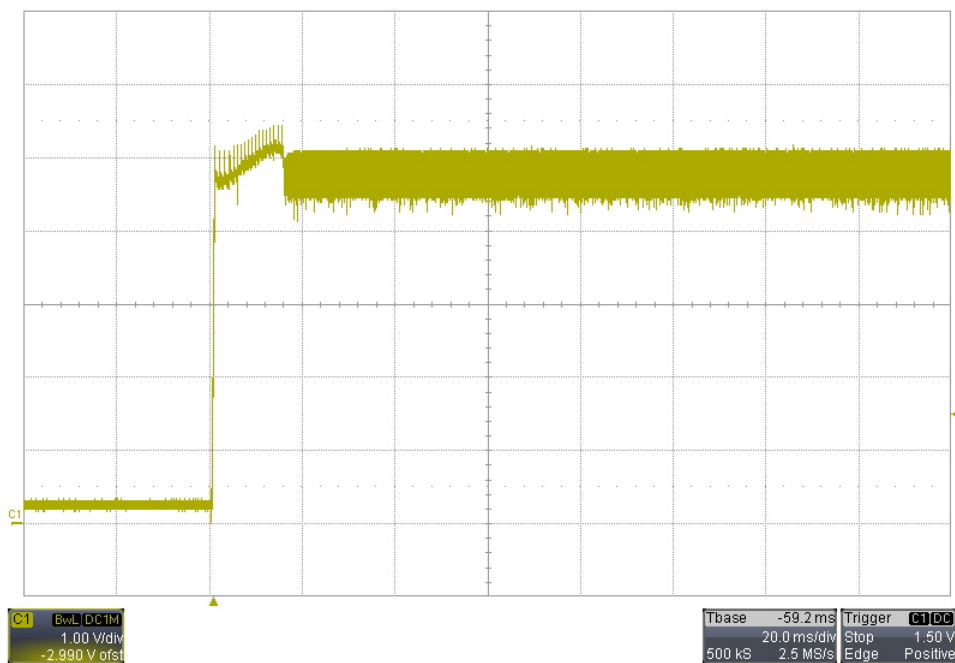


Figure 22. Output Voltage Start-up Waveform, 120 V_{AC}, 5-V V_{OUT} = 200-mA Load

Figure 23 and Figure 24 show the output voltage start-up waveform for 120-V_{AC} input at no load then full load (0.2 A), respectively.

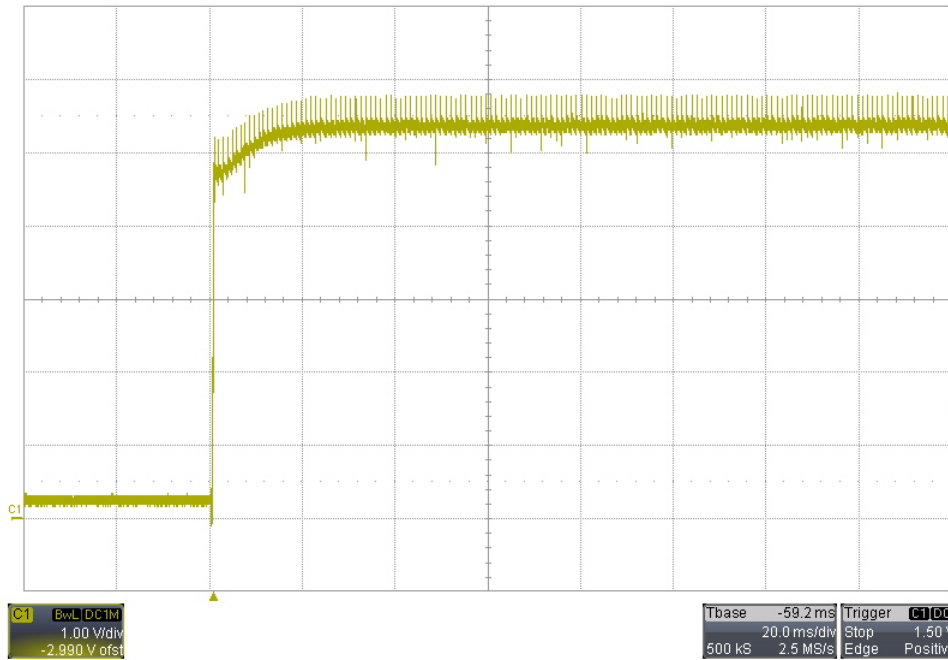


Figure 23. Output Voltage Start-up Waveform, 270 V_{AC}, 5-V V_{OUT} = 0-mA Load

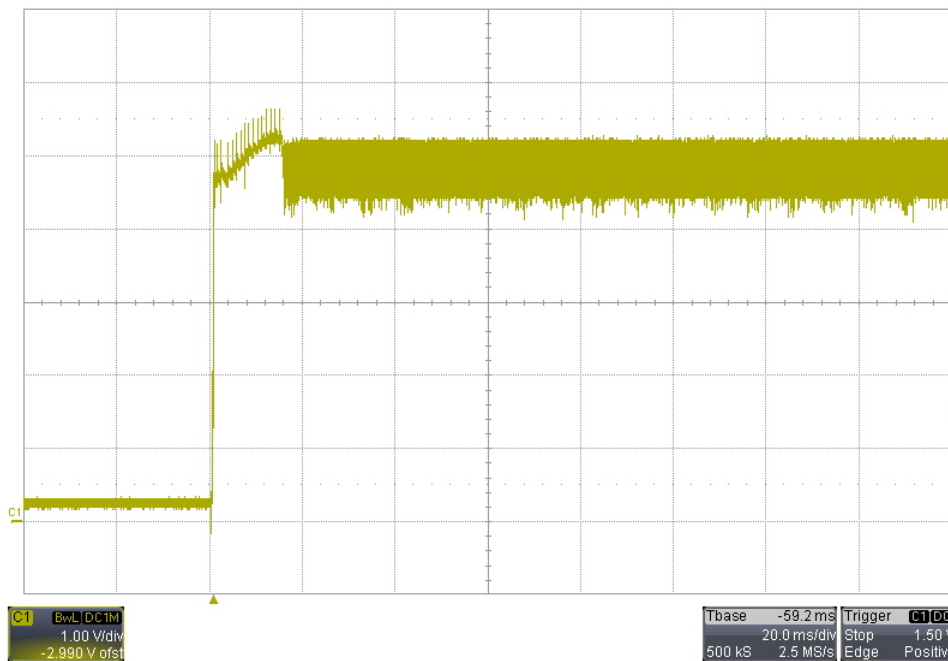


Figure 24. Output Voltage Start-up Waveform, 270 V_{AC}, 5-V V_{OUT} = 200-mA Load

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated