

Bill of Materials

TI DESIGNS TIDA-00447

24V Dual Brushless DC Motor Drive Reference Design for Dishwasher Pumps

Qty	Reference	Part Description	Manufacturer	Manufacturer Part Number	Note		
1	!PCB	Printed Circuit Board	Any	Printed Circuit Board	Fitted		
3	C1, C11, C12	CAP, CERM, 0.1 uF, 25 V, +/- 10%, X8R, 0603	TDK	C1608X8R1E104K	Fitted		
1	C2	CAP, CERM, 10 uF, 10 V, +/- 20%, X5R, 0603	TDK	C1608X5R1A106M	Fitted		
1	C3	CAP, CERM, 10 uF, 50 V, +/- 10%, X5R, 1210	MuRata	GRM32ER61H106KA12L	Fitted		
2	C4, C5	CAP, CERM, 0.1 uF, 50 V, +/- 10%, X7R, 0603	TDK	C1608X7R1H104K	Fitted		
2	C6, C7	CAP, CERM, 1 uF, 6.3 V, +/- 10%, X5R, 0603	TDK	C1608X5R0J105K	Fitted		
1	C8	CAP, AL, 100uF, 6.3V, +/-20%, 0.027 ohm, SMD	Nippon Chemi-Con	APXA6R3ARA101MF60G	Fitted		
1	C13	CAP, CERM, 2200 pF, 50 V, +/- 10%, X7R, 0603	TDK	C1608X7R1H222K	Fitted		
4	C14, C22, C25, C26	CAP, CERM, 0.1 uF, 50 V, +/- 10%, X7R, 0603	AVX	06035C104KAT2A	Fitted		
1	C15	CAP, CERM, 4.7 uF, 50 V, +/- 10%, X5R, 0805	TDK	C2012X5R1H475K125AB	Fitted		
3	C16, C17, C18	CAP, CERM, 1 uF, 50 V, +/- 10%, X7R, 0805	TDK	C2012X7R1H105K125AB	Fitted		
1	C19	CAP, CERM, 0.022 uF, 50 V, +/- 10%, X8R, 0603	TDK	C1608X8R1H223K	Fitted		
1	C20	CAP, CERM, 2.2 uF, 35 V, +/- 10%, X7R, 0805	TDK	C2012X7R1V225K085AC	Fitted		
2	C21, C28	CAP, AL, 270 uF, 35 V, +/- 20%, 20 ohm, SMD	Panasonic	EEHZA1V271P	Fitted		
1	C24	CAP, CERM, 0.1 uF, 10 V, +/- 10%, X7R, 0603	Kemet	C0603X104K8RACTU	Fitted		
1	C27	CAP, CERM, 1000 pF, 50 V, +/- 5%, COG/NPO, 0603	TDK	C1608C0G1H102J	Fitted		
1	C29	CAP, CERM, 0.01 uF, 50 V, +/- 5%, X7R, 0805	AVX	08055C103JAT2A	Fitted		
_		CAP, CERM, 0.01 uF, 25 V, +/- 5%, C0G/NP0,					
2	C30, C31	0603	TDK	C1608C0G1E103J	Fitted		
2	C32, C33	CAP, CERM, 1 uF, 25 V, +/- 10%, X5R, 0603	TDK	C1608X5R1E105K080AC	Fitted		
1	C37	CAP, CERM, 0.47 uF, 10 V, +/- 10%, X5R, 0603	TDK	C1608X5R1A474K	Fitted		
3	D1, D9, D10	Diode, LED, [Color], x-V, 20-mA, y-mcd	Lite On	D_LED_603	Fitted		
1	D2	Diode, Zener, 3.6 V, 500 mW, SOD-123	Diodes Inc.	MMSZ5227B-7-F	Fitted		
2	D3, D4	Diode, Zener, 5.6 V, 200 mW, SOD-323	Diodes Inc.	MMSZ5232BS-7-F	Fitted		
1	D5	Diode, TVS, Bi, 30 V, 400 W, SMA	Littelfuse	SMAJ30CA	Fitted		
1	D7	Diode, Zener, 16 V, 300 mW, SOD-523	Diodes Inc.	BZT52C16T-7	Fitted		
1	D8	Diode, TVS, Uni, 3.3 V, 350 W, SOD-323	Protek Devices	GBLC03-LF-T7	Fitted		
1	J1	Header, 2.54 mm, 3x1, Gold, TH	Wurth Elektronik	61300311121	Fitted		
2	J2, J8	TERMINAL BLOCK 5.08MM VERT 3POS, TH	On-Shore Technology	ED120/3DS	Fitted		
2	J4, J5	Header, 2.54 mm, 4x1, Gold, TH	Wurth Elektronik	61300411121	Fitted		
1	J9	TERMINAL BLOCK 5.08MM VERT 2POS, TH	Molex	ED1817-ND	Fitted		
1	J10	Header, Male 2-pin, 100mil spacing,	Sullins	JUMPER 2X100MIL	Fitted		
1	L1	Inductor, Wirewound, Ferrite, 47 ??H, 0.11 A, 1.235 ohm, SMD	Taiyo Yuden	 СВ2518Т470К	Fitted		
3	L2, L3, L4	Ferrite Bead, 100 ohm @ 100 MHz, 4 A, 0805	TDK	MPZ2012S300A	Fitted		
3	L5, L6, L7	Inductor, Shielded, Composite, 470 nH, 3.5 A, 0.0076 ohm, SMD	Coilcraft	XFL4015-471MEC	Fitted		
3	Q1, Q2, Q3	MOSFET, N-CH, 60 V, 6.3 A, SO-8	Texas Instruments	CSD88539ND	Fitted		
1	Q4	MOSFET, N-CH, 30 V, 56 A, SON 3.3x3.3mm	Texas Instruments	CSD17304Q3	Fitted		

Qty	Reference	Part Description	Manufacturer	Manufacturer Part Number	Note
3	R2, R3, R4	RES, 4.75 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW06034K75FKEA	Fitted
2	R5, R6	RES, 0, 5%, 0.1 W, 0603	Yageo America	RC0603JR-070RL	Fitted
1	R7	RES, 270, 5%, 0.1 W, 0603	Vishay-Dale	CRCW0603270RJNEA	Fitted
2	R8, R10	RES, 0, 5%, 0.1 W, 0603	Vishay-Dale	CRCW06030000Z0EA	Fitted
1	R9	RES, 47 k, 5%, 0.1 W, 0603	Vishay-Dale	CRCW060347K0JNEA	Fitted
4	R11, R12, R13, R14	RES, 100, 5%, 0.1 W, 0603	Vishay-Dale	CRCW0603100RJNEA	Fitted
3	R15, R18, R45	RES, 27, 5%, 0.1 W, 0603	Vishay-Dale	CRCW060327R0JNEA	Fitted
4	R16, R17, R29, R30	RES, 10.0 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW060310K0FKEA	Fitted
1	R19	RES, 1.00, 1%, 0.1 W, 0603	Vishay-Dale	CRCW06031R00FKEA	Fitted
6	R20, R21, R22, R23, R25, R28	RES, 3.9, 5%, 0.1 W, 0603	Vishay-Dale	CRCW06033R90JNEA	Fitted
1	R24	RES, 0.01, 1%, 2 W, 2512	Stackpole Electronics Inc	CSRN2512FK10L0	Fitted
1	R26	RES, 3.3, 5%, 0.1 W, 0603	Vishay-Dale	CRCW06033R30JNEA	Fitted
1	R27	RES, 3.0 k, 5%, 0.1 W, 0603	Vishay-Dale	CRCW06033K00JNEA	Fitted
6	R31, R32, R37, R38, R39, R40	RES, 1.00 k, 1%, 0.1 W, 0603	Vishay-Dale	CRCW06031K00FKEA	Fitted
4	R33, R34, R35, R36	RES, 40.2 k, 1%, 0.1 W, 0603	Yageo America	RC0603FR-0740K2L	Fitted
4	R41, R42, R43, R44	RES, 3.6 k, 1%, 0.1 W, 0603	Yageo America	RC0603FR-073K6L	Fitted
1	U1	Microcontroller	Texas Instruments	MSP430G2544_DA_3	Fitted
1	U2	12- to 24-V, Three-Phase, Sensorless BLDC Motor Driver, PWP0024B	Texas Instruments	DRV10983PWP	Fitted
1	U4	1 Mbps Dual Channels, 1 / 1, Digital Isolator, 3.3 V / 5 V, -40 to +105 degC, 8-pin SOIC (D), Green (RoHS & no Sb/Br)	Texas Instruments	ISO7421D	Fitted
1	U5	THREE PHASE PRE-DRIVER WITH DUAL CURRENT SHUNT AMPLIFIERS, DCA0048A	Texas Instruments	DRV8303DCA	Fitted
1	U6	Analog Temperature Sensors with Class-AB Output, DCK0005A	Texas Instruments	LMT84DCK	Fitted
1	U7	ESD Solution for High-Speed Differential Interface, 4 Channels, -40 to +85 degC, 6-pin SOT-23 (DBV), Green (RoHS & no Sb/Br)	Texas Instruments	TPD4S009DBVRG4	Fitted
1	U8	3-Pin Voltage Supervisors with Active-Low, Open-Drain Reset, DBZ0003A	Texas Instruments	TLV803SDBZR	Fitted
0	C34, C35, C36	CAP, CERM, 0.47 uF, 10 V, +/- 10%, X5R, 0603	TDK	C1608X5R1A474K	Not Fitted
0	R1	RES, 0, 5%, 0.75 W, 2010	Vishay-Dale	CRCW20100000Z0EF	Not Fitted

IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design. TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have *not* been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.