

# Optimizing Signal Chain Noise on PCM186x Devices

Dafydd Roche

## ABSTRACT

The PCM1860/1/2/3/4/5 devices have a highly flexible input front end that can handle very low level single ended, pseudo-differential and higher voltage differential inputs. The architecture of the PCM186x family of devices allows system designers to optimize the signal chain to avoid any increased noise floor, depending on how they have their system configured.

## Contents

1	Introduction .....	1
2	Explanation .....	2
3	Sensitive Configurations .....	3
4	Configurations to avoid noise modulation .....	3
5	Impacts on Additional Features in the PCM186x Family .....	4

## List of Figures

1	ADC Signal Chain Architecture of PCM186x .....	2
2	Input vs Output graph of a Delta Sigma Modulator .....	2
3	SW Controlled Compensation to Ensure 2.1 VRMS Inputs Avoid Noise Modulation.....	3
4	HW Controlled Compensation to Ensure 2.1 VRMS Inputs Avoid Noise Modulation .....	4
5	Workflow to Use Auto Gain Suppression With a -2 dBFS Input Signal .....	5

## List of Tables

## 1 Introduction

The PCM186x family has a highly flexible input structure allowing the device to support single ended, differential and psuedo-differential inputs. Some customers can use the Single Ended input mode to support a 2 VRMS Audio source (such as a DVD player), others may choose to use the Psuedo-Differential modes ground noise cancellation and for others, fully differential modes are used, with an input swing of 4.2 VRMS differential.


The PCM186x was designed to handle all of these input conditions, and to support a programmable gain amplifier that can boost or attenuate the signal as needed.

As the Pseudo-Differential mode (signal on positive input, ground sense on the negative input) doesn't exercise the entire range of the ADC, the architecture was designed so that lower input voltages could achieve higher Signal to Noise Ratio. The architecture was defined, so that at typical lower signal amplitudes, the ADC would provide higher performance, whilst at very high amplitudes (within -2 dBFS of ADC input) the noise floor would be allowed to increase.

## 2 Explanation

The ADC was designed to support maximum input signals that may be as low as 1 VRMS in differential mode all the way to a full 4.2 VRMS differential. Given market trends towards portable products connecting through AUX inputs to docks, amplifiers and AV systems, more emphasis was put on increasing sensitivity and noise floors at lower ranges, than full dynamic range.


The internal architecture of a delta sigma ADC (in this case the PCM186x) is shown in [Figure 1](#).

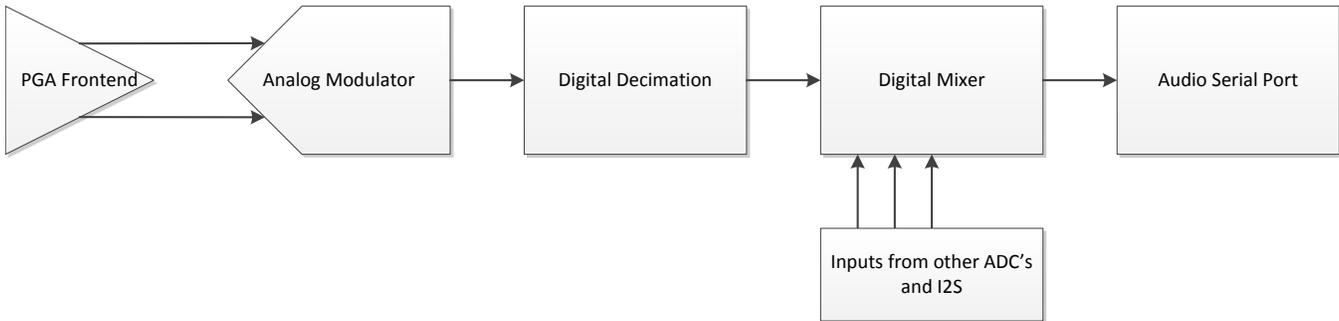

**Figure 1. ADC Signal Chain Architecture of PCM186x**

The modulator is the high speed oversampling converter who's data is passed to a decimator that converts the high speed multi-bit data to a lower rate 24 bit data stream. The modulator has an analog input range defined as a "modulation index" between 0 and 100%. The noise floor is not linear between 0 and 100% and silicon designers typically have to scale their analog inputs so that the maximum expected analog input lies within the flat noise floor. This is typically between 0 and ~95% modulation. Any higher can cause a noise floor that increases.

On PCM186x, given the large variance of "maximum input signal" and the availability of the PGA, we offer the capability to tune the maximum modulation index to improve performance at lower ranges, or push the signal as high as possible, even at the sacrifice of some noise floor.

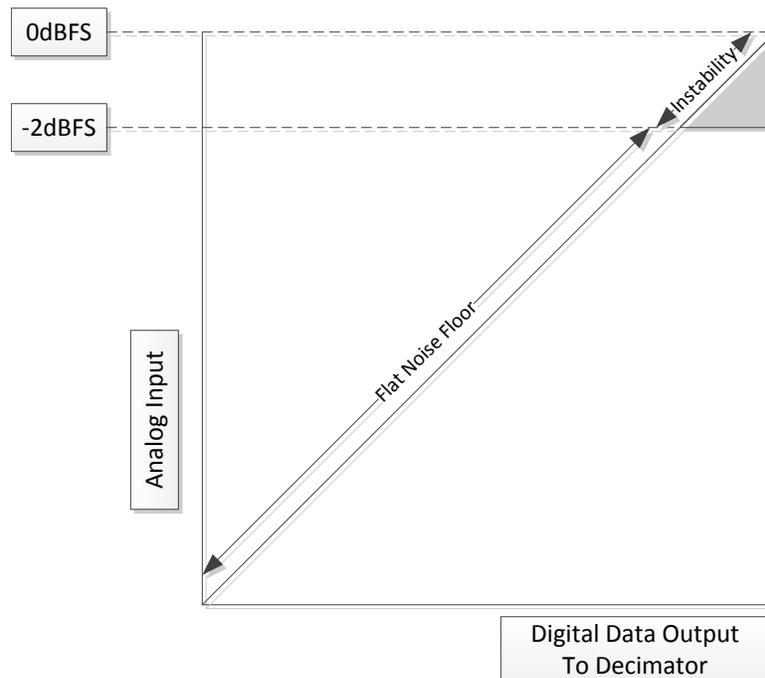

**Figure 2. Input vs Output graph of a Delta Sigma Modulator**

### 3 Sensitive Configurations

The noise floor will begin to increase when the post-PGA output is within -2 dB of the modulator full scale input (defined as 2.1 VRMS in single ended mode and 4.2VRMS in differential mode). The PCM186x PGA maps the incoming voltage to the ADC differently based on the input configuration.

#### 3.1 Single Ended Systems

If using the system with 2.1 VRMS Single Ended Inputs, then there is a possibility that any signals over ~1.65 VRMS can cause noise modulation. Systems in single ended configurations expecting 1 VRMS input (e.g. from a smartphone) do not have noise modulation, providing their PGA gain is configured to be less than 4 dB. This can be compensated for either using attenuation in the analog PGA, or external signal conditioning. (see [Section 4](#))

#### 3.2 Differential Systems

Differential systems require a 3.34 VRMS differential signal before any kind of noise modulation can occur (that is -2 dB below 4.2 VRMS). Again, this can be compensated for using the PGA if the input signal really is 4.2 VRMS.

#### 3.3 Psuedo-Differential Systems

Pseudo Differential systems, expecting a 1 VRMS or 2.1 VRMS single ended signal, along with a "grounded" input are not impacted. Even with a 2.1 VRMS input on the positive pin, the modulator, by default will see data at -6 dBFS. No more analog gain can be added to such systems, as the each input of the device has a voltage limit of 2.1 VRMS. The PGA will clip before the modulator will clip.

### 4 Configurations to avoid noise modulation

When working in single ended input modes (for example 2 VRMS Single Ended Mode) the recommended configuration is to limit the output of the PGA to the modulator. This can be achieved in software programmable devices (PCM1862/3/4/5), by configuring the PGA to -2 dB gain below what would be required to clip the ADC. The decimator then outputs data that is -2 dBFS. This can be compensated for in the digital mixer by adding 2 dB of gain, to bring the full scale analog signal to be fullscale of the I2S stream. The 4 channel PCM1864 and PCM1865 can have their analog and digital PGA's controlled separately, as such, the 2 dB gain can be done in the Digital PGA instead of the digital mixer.


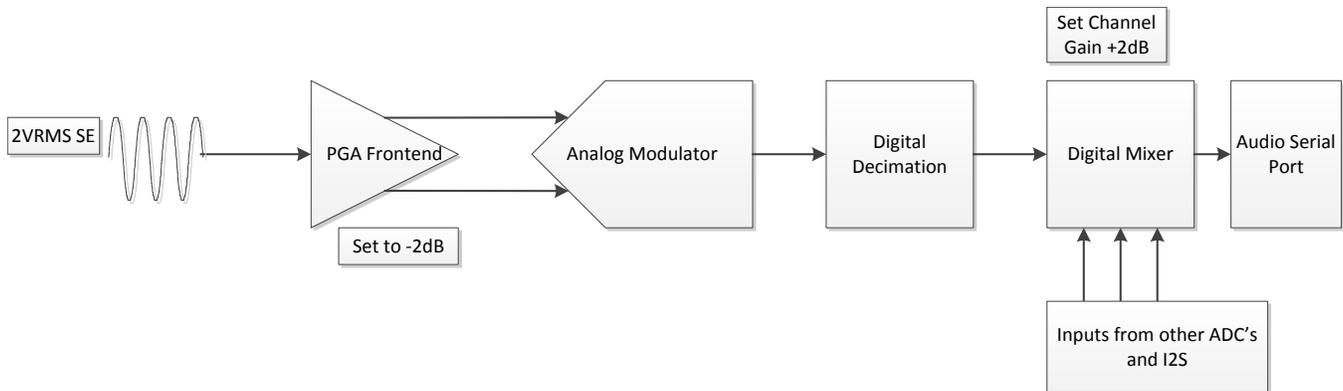


Figure 3. SW Controlled Compensation to Ensure 2.1 VRMS Inputs Avoid Noise Modulation

For hardware controlled devices (PCM1860/1), a resistor is recommended to be used to lower the input voltage to the device. The input impedance of the PCM1860/1 is nominally 20 K $\Omega$  but can vary  $\pm 20\%$  due to manufacturing tolerance. -2 dB attenuation requires a ~5.2-K $\Omega$  resistor. Input voltage control can also be done using a standard voltage divider on the input. Designers should consider the 20 K $\Omega$  input impedance when designing their voltage divider.

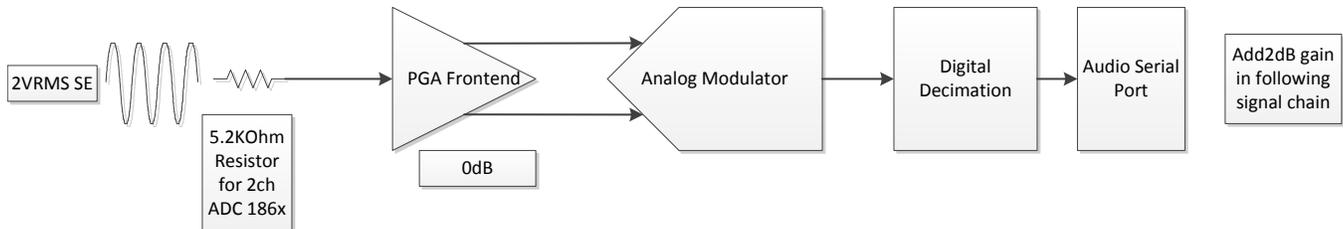

**Figure 4. HW Controlled Compensation to Ensure 2.1 VRMS Inputs Avoid Noise Modulation**

### Analog performance with attenuated modulator inputs

With the modulator now running 2 dB below full scale, the performance of the higher grade PCM1861/3/5 will be impacted to 108dB Differential. The low grade PCM1860/2/4 remains at 103 dB.

## 5 Impacts on Additional Features in the PCM186x Family

The PCM186x family, especially those which are software controlled have a number of features that can assist with configuring the input signal chain

### 5.1 Energysense

This noise floor at high input has no impact on the Energysense system wake and system sleep detection. However, if the PGA gain is modified, then signal thresholds is 2 dB lower. For example, a if the signal wake up threshold was set to -50dBFS previously, it will now take a -48 dBFS to wake the system.

### 5.2 Auto Gain Suppression and Clipping detection

Once the PGA gain has been compensated with -2 dB gain the modulator will receive reduced input levels. The Auto Gain Suppression and Clipping Detection requires compensation for the attenuation that has been added to signal before the modulator.

A real world application would be an Aux system expecting 1 VRMS inputs from a smartphone in most cases, but still needs the ability to accept a 2.1 VRMS input, should a customer decide to connect a DVD player. Designers can use the Auto Gain Suppression feature to optimize the input signal at all times.

The application [Figure 5](#) configures the device for 1 VRMS input SE, but responds to a 2.1 VRMS input by automatically attenuating the signal to full scale. An additional -2 dB of attenuation is added to maintain the flat noise floor.

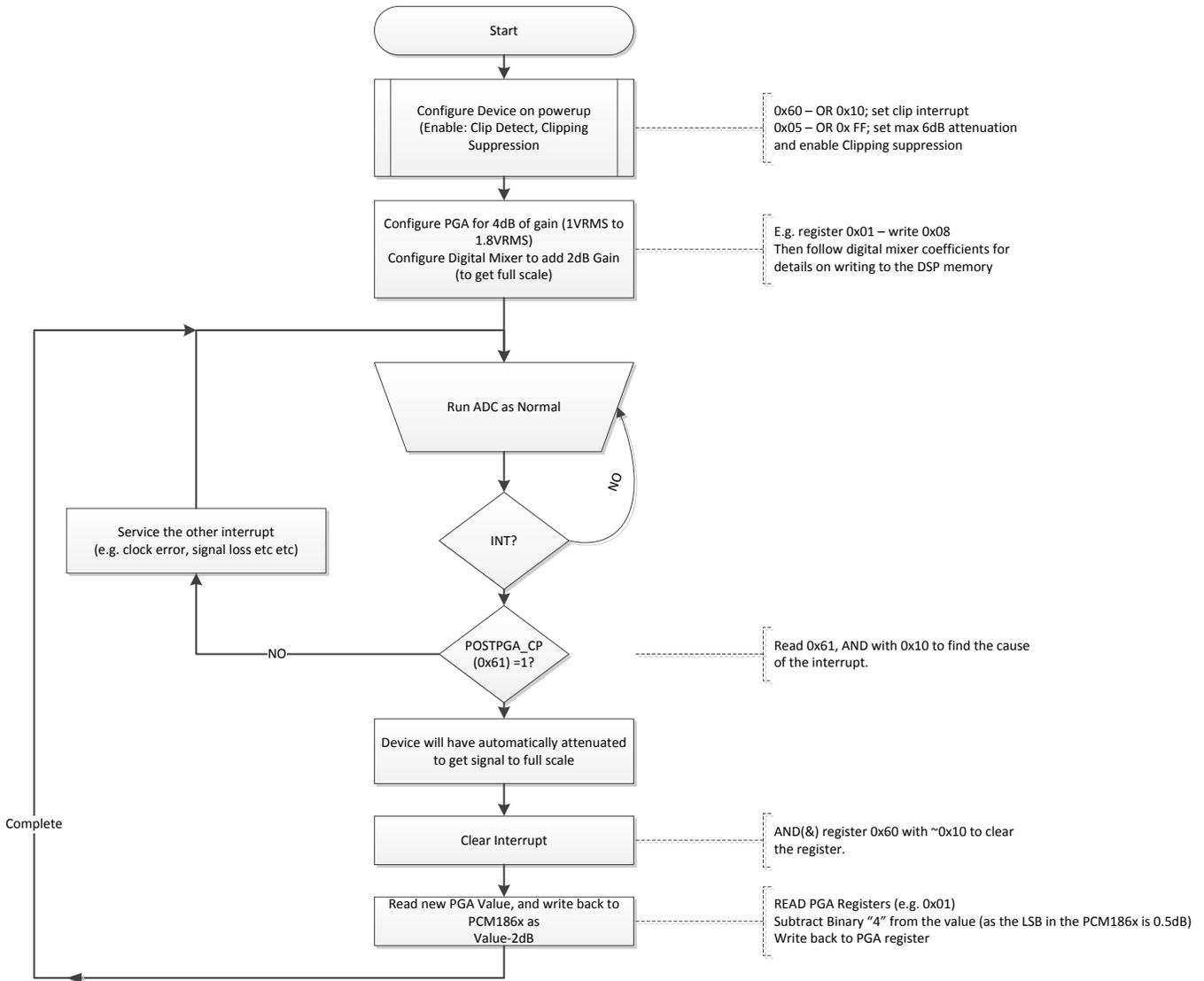


Figure 5. Workflow to Use Auto Gain Suppression With a -2 dBFS Input Signal

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)